

EE101: RC and RL Circuits (with DC sources)




M. B. Patil

mbpatil@ee.iitb.ac.in


www.ee.iitb.ac.in/~sequel

Department of Electrical Engineering
Indian Institute of Technology Bombay

Capacitors


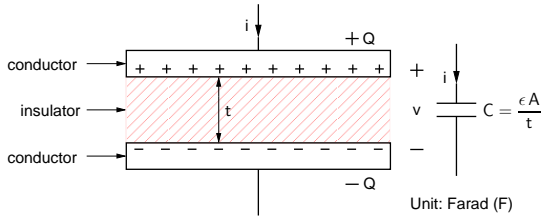


Capacitors

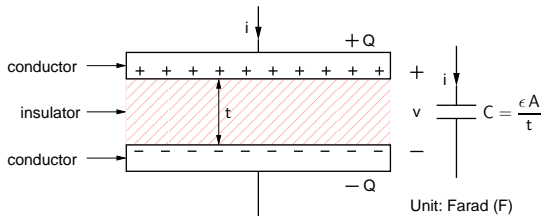


- * In practice, capacitors are available in a wide range of shapes and values, and they differ significantly in the way they are fabricated.
(<http://en.wikipedia.org/wiki/Capacitor>)

Capacitors

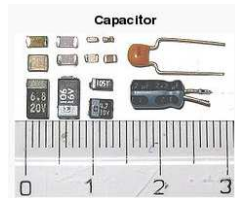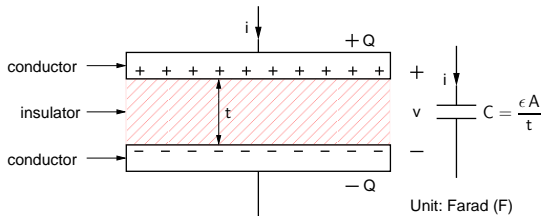

- * In practice, capacitors are available in a wide range of shapes and values, and they differ significantly in the way they are fabricated. (<http://en.wikipedia.org/wiki/Capacitor>)
- * To make C larger, we need (a) high ϵ , (b) large area, (c) small thickness.


Capacitors

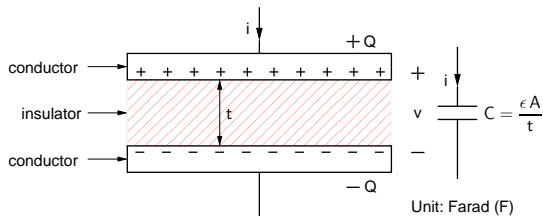

- * In practice, capacitors are available in a wide range of shapes and values, and they differ significantly in the way they are fabricated. (<http://en.wikipedia.org/wiki/Capacitor>)
- * To make C larger, we need (a) high ϵ , (b) large area, (c) small thickness.
- * For a constant capacitance,

$$Q(t) = C v(t), \quad \frac{dQ}{dt} = C \frac{dv}{dt}, \text{ i.e., } i(t) = C \frac{dv}{dt}.$$

Capacitors

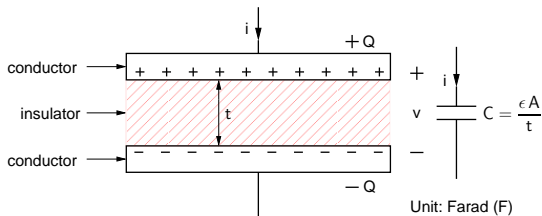

- * In practice, capacitors are available in a wide range of shapes and values, and they differ significantly in the way they are fabricated. (<http://en.wikipedia.org/wiki/Capacitor>)
- * To make C larger, we need (a) high ϵ , (b) large area, (c) small thickness.
- * For a constant capacitance,
$$Q(t) = C v(t), \quad \frac{dQ}{dt} = C \frac{dv}{dt}, \text{ i.e., } i(t) = C \frac{dv}{dt}.$$
- * If $v = \text{constant}$, $i = 0$, i.e., a capacitor behaves like an open circuit in DC conditions as one would expect from two conducting plates separated by an insulator.

Example

Plot v , p , and W versus time for the given source current. Assume $v(0) = 0$ V, $C = 5$ mF.



Example

Plot v , p , and W versus time for the given source current. Assume $v(0) = 0$ V, $C = 5$ mF.



$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$




Example

Plot v , p , and W versus time for the given source current. Assume $v(0) = 0$ V, $C = 5$ mF.



$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

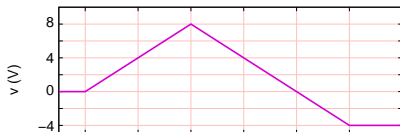

Example



Plot v , p , and W versus time for the given source current. Assume $v(0) = 0$ V, $C = 5$ mF.



$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

$$p(t) = v(t) \times i(t)$$

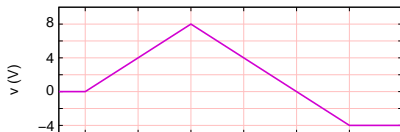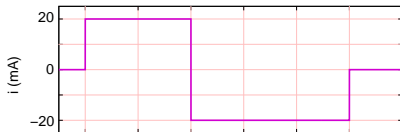

Example


Plot v , p , and W versus time for the given source current. Assume $v(0) = 0$ V, $C = 5$ mF.



$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

$$p(t) = v(t) \times i(t)$$

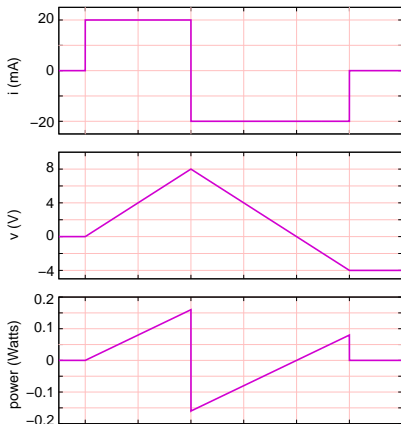

Example

Plot v , p , and W versus time for the given source current. Assume $v(0) = 0$ V, $C = 5$ mF.





$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

$$p(t) = v(t) \times i(t)$$

$$W(t) = \int p(t) dt$$

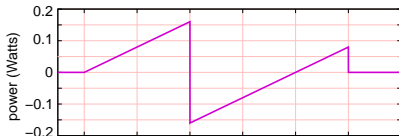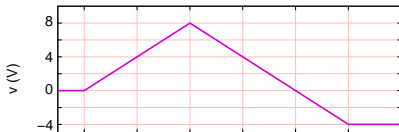

Example

Plot v , p , and W versus time for the given source current. Assume $v(0) = 0$ V, $C = 5$ mF.




$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

$$p(t) = v(t) \times i(t)$$

$$W(t) = \int p(t) dt$$

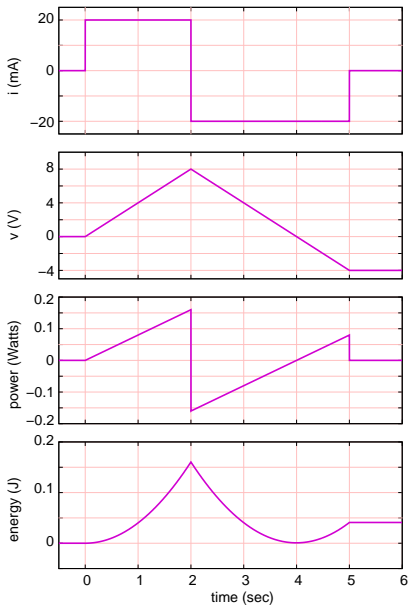

Example

Plot v , p , and W versus time for the given source current. Assume $v(0) = 0$ V, $C = 5$ mF.




$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$


$$p(t) = v(t) \times i(t)$$

$$W(t) = \int p(t) dt$$

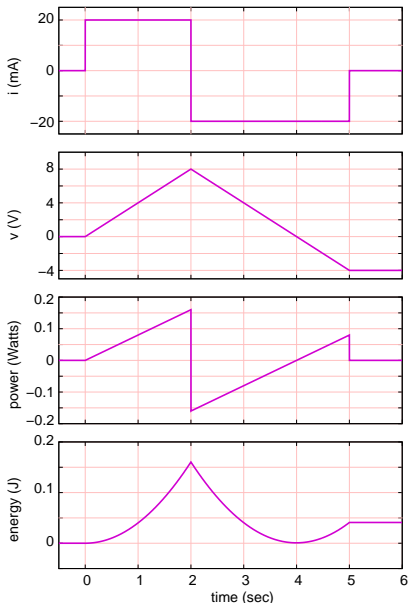
$$\begin{aligned} W(t) &= \int p(t) dt \\ &= C \int v \frac{dv}{dt} dt \\ &= C \int v dv \\ &= \frac{1}{2} C v^2 \end{aligned}$$



Home work

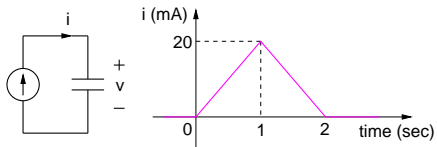


Home work

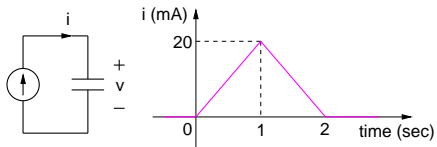


- * For the given source current, plot $v(t)$, $p(t)$, and $W(t)$, assuming $v(0) = 0$ V, $C = 5$ mF.

Home work

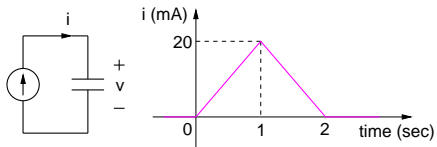


- * For the given source current, plot $v(t)$, $p(t)$, and $W(t)$, assuming $v(0) = 0$ V, $C = 5$ mF.
- * Verify your results with circuit simulation.

Inductors

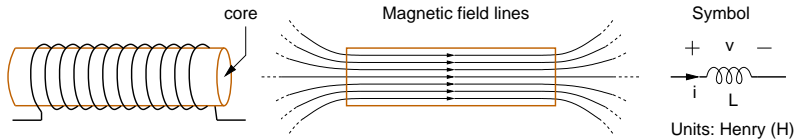


Inductors

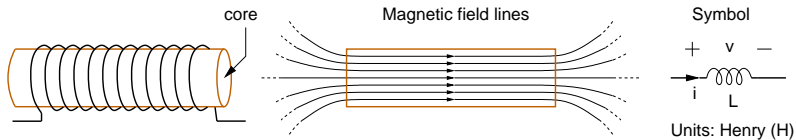

* An inductor is basically a conducting coil wound around a "core."

Inductors

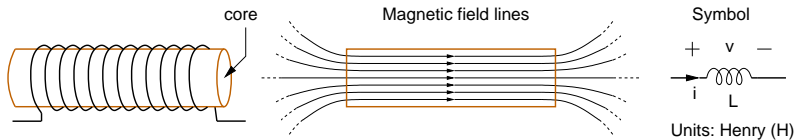


* An inductor is basically a conducting coil wound around a “core.”

$$* V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} \left[\left(\frac{\mu N i}{l} \right) A \right].$$

$$\text{Compare with } v = L \frac{di}{dt}.$$

$$\Rightarrow L = \mu N^2 \frac{A}{l} = \mu_r \mu_0 N^2 \frac{A}{l}.$$

Inductors

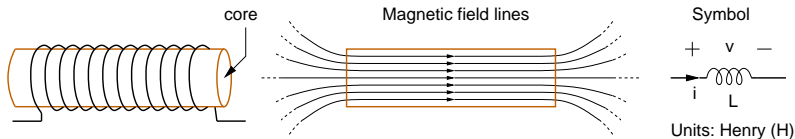

* An inductor is basically a conducting coil wound around a “core.”


$$* V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} \left[\left(\frac{\mu N i}{l} \right) A \right].$$

Compare with $v = L \frac{di}{dt}$.

$$\Rightarrow L = \mu N^2 \frac{A}{l} = \mu_r \mu_0 N^2 \frac{A}{l}.$$

* To make L larger, we need (a) high μ_r , (b) large area, (c) large number of turns.

Inductors

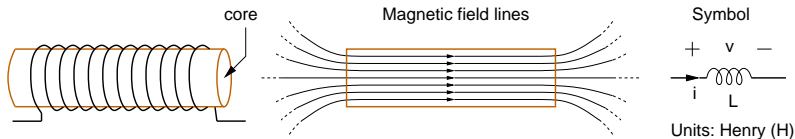

* An inductor is basically a conducting coil wound around a “core.”

$$* V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} \left[\left(\frac{\mu N i}{l} \right) A \right].$$

$$\text{Compare with } v = L \frac{di}{dt}.$$


$$\Rightarrow L = \mu N^2 \frac{A}{l} = \mu_r \mu_0 N^2 \frac{A}{l}.$$

* To make L larger, we need (a) high μ_r , (b) large area, (c) large number of turns.

* For 99.8 % pure iron, $\mu_r \simeq 5,000$.

For “supermalloy” (Ni: 79 %, Mo: 5 %, Fe): $\mu_r \simeq 10^6$.

Inductors

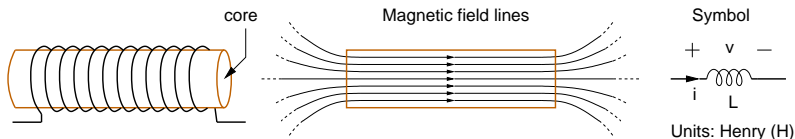

* An inductor is basically a conducting coil wound around a “core.”


$$* V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} \left[\left(\frac{\mu N i}{l} \right) A \right].$$

$$\text{Compare with } v = L \frac{di}{dt}.$$

$$\Rightarrow L = \mu N^2 \frac{A}{l} = \mu_r \mu_0 N^2 \frac{A}{l}.$$

- * To make L larger, we need (a) high μ_r , (b) large area, (c) large number of turns.
- * For 99.8 % pure iron, $\mu_r \simeq 5,000$.
For “supermalloy” (Ni: 79 %, Mo: 5 %, Fe): $\mu_r \simeq 10^6$.
- * If $i = \text{constant}$, $v = 0$, i.e., an inductor behaves like a short circuit in DC conditions as one would expect from a highly conducting coil.

Inductors

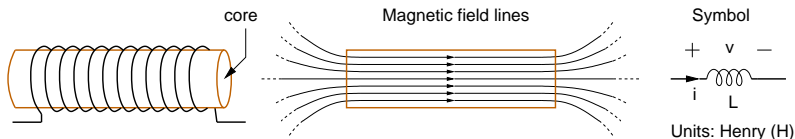

* An inductor is basically a conducting coil wound around a “core.”


$$* V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} \left[\left(\frac{\mu N i}{l} \right) A \right].$$

$$\text{Compare with } v = L \frac{di}{dt}.$$


$$\Rightarrow L = \mu N^2 \frac{A}{l} = \mu_r \mu_0 N^2 \frac{A}{l}.$$

- * To make L larger, we need (a) high μ_r , (b) large area, (c) large number of turns.
- * For 99.8 % pure iron, $\mu_r \simeq 5,000$.
For “supermalloy” (Ni: 79 %, Mo: 5 %, Fe): $\mu_r \simeq 10^6$.
- * If $i = \text{constant}$, $v = 0$, i.e., an inductor behaves like a short circuit in DC conditions as one would expect from a highly conducting coil.
- * Note: $B = \mu H$ is an approximation. In practice, B may be a nonlinear function of H , depending on the core material.


RC circuits with DC sources

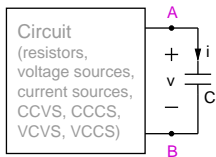

RC circuits with DC sources

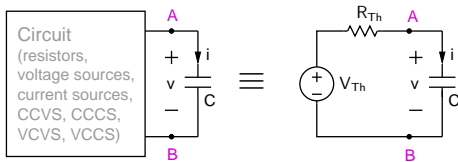


RC circuits with DC sources

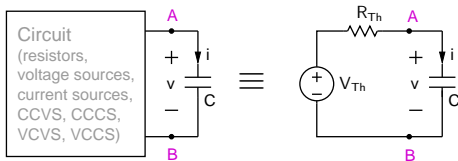


* If all sources are DC (constant), $V_{Th} = \text{constant}$.

RC circuits with DC sources

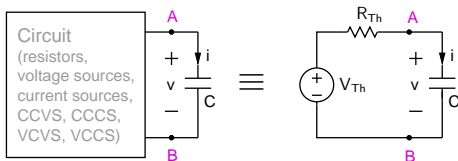

- * If all sources are DC (constant), $V_{Th} = \text{constant}$.
- * KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$.

RC circuits with DC sources

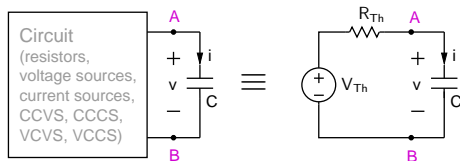

* If all sources are DC (constant), $V_{Th} = \text{constant}$.


* KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$.

* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant."}$$


$$\rightarrow v^{(h)} = K \exp(-t/\tau).$$

RC circuits with DC sources

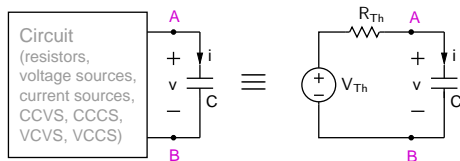


- * If all sources are DC (constant), $V_{Th} = \text{constant}$.
- * KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$.
- * Homogeneous solution:
$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant."}$$
$$\rightarrow v^{(h)} = K \exp(-t/\tau).$$
- * Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $i = 0$, and we get $v^{(p)} = V_{Th}$ as a particular solution (which happens to be simply a constant).

RC circuits with DC sources

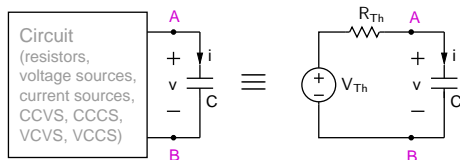

- * If all sources are DC (constant), $V_{Th} = \text{constant}$.
- * KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$.
- * Homogeneous solution:
$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant."}$$
$$\rightarrow v^{(h)} = K \exp(-t/\tau).$$
- * Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $i = 0$, and we get $v^{(p)} = V_{Th}$ as a particular solution (which happens to be simply a constant).
- * $v = v^{(h)} + v^{(p)} = K \exp(-t/\tau) + V_{Th}$.

RC circuits with DC sources

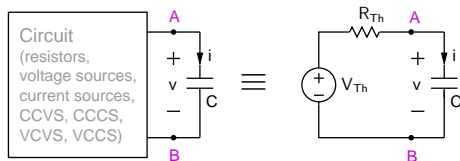

* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$.

* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant."}$$


$$\rightarrow v^{(h)} = K \exp(-t/\tau).$$

* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $i = 0$, and we get $v^{(p)} = V_{Th}$ as a particular solution (which happens to be simply a constant).

* $v = v^{(h)} + v^{(p)} = K \exp(-t/\tau) + V_{Th}$.


* In general, $v(t) = A \exp(-t/\tau) + B$, where A and B can be obtained from known conditions on v .

RC circuits with DC sources (continued)

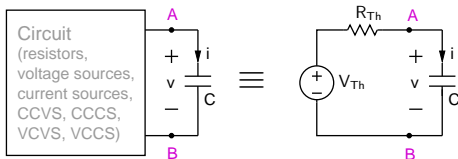

- * If all sources are DC (constant), we have $v(t) = A \exp(-t/\tau) + B$, $\tau = RC$.


RC circuits with DC sources (continued)

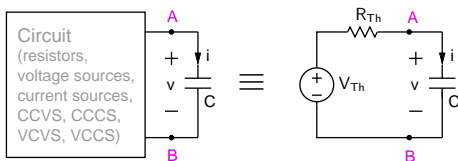

- * If all sources are DC (constant), we have $v(t) = A \exp(-t/\tau) + B$, $\tau = RC$.


- * $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau} \right) \equiv A' \exp(-t/\tau)$.

RC circuits with DC sources (continued)

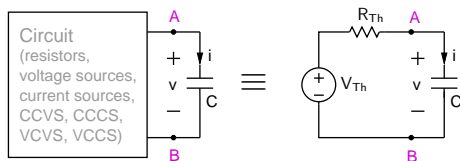


- * If all sources are DC (constant), we have $v(t) = A \exp(-t/\tau) + B$, $\tau = RC$.
- * $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.
- * As $t \rightarrow \infty$, $i \rightarrow 0$, i.e., the capacitor behaves like an open circuit since all derivatives vanish.

RC circuits with DC sources (continued)

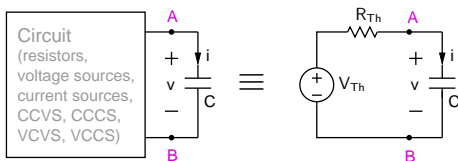


- * If all sources are DC (constant), we have $v(t) = A \exp(-t/\tau) + B$, $\tau = RC$.
- * $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.
- * As $t \rightarrow \infty$, $i \rightarrow 0$, i.e., the capacitor behaves like an open circuit since all derivatives vanish.
- * Since the circuit in the black box is linear, any variable (current or voltage) in the circuit can be expressed as $x(t) = K_1 \exp(-t/\tau) + K_2$, where K_1 and K_2 can be obtained from suitable conditions on $x(t)$.


RL circuits with DC sources

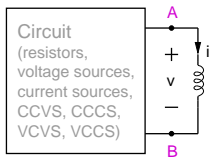

RL circuits with DC sources

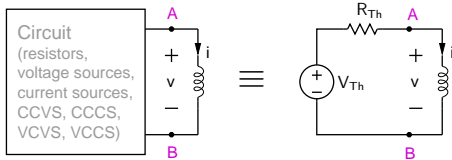


RL circuits with DC sources

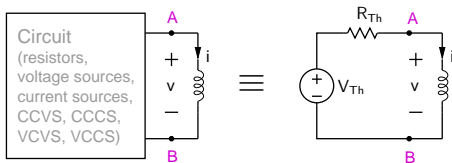


* If all sources are DC (constant), $V_{Th} = \text{constant}$.

RL circuits with DC sources

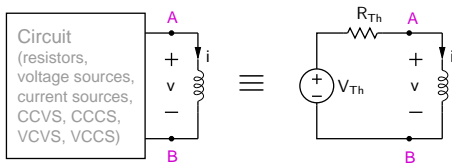

- * If all sources are DC (constant), $V_{Th} = \text{constant}$.
- * KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.

RL circuits with DC sources

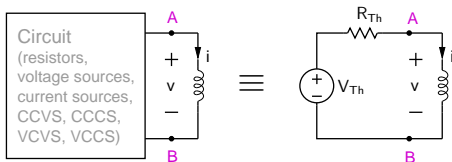

* If all sources are DC (constant), $V_{Th} = \text{constant}$.


* KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.

* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$

$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

RL circuits with DC sources

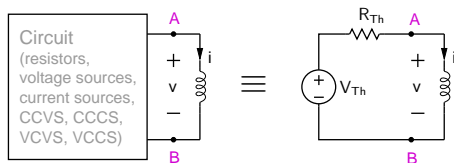

* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.


* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$

$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$


* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $v = 0$, and we get $i^{(p)} = V_{Th}/R_{Th}$ as a particular solution (which happens to be simply a constant).

RL circuits with DC sources

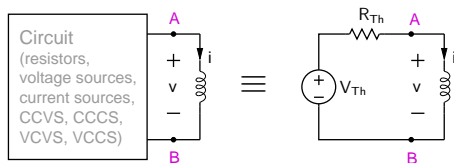

- * If all sources are DC (constant), $V_{Th} = \text{constant}$.
- * KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.
- * Homogeneous solution:
$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$
$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$
- * Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $v = 0$, and we get $i^{(p)} = V_{Th}/R_{Th}$ as a particular solution (which happens to be simply a constant).
- * $i = i^{(h)} + i^{(p)} = K \exp(-t/\tau) + V_{Th}/R_{Th}$.

RL circuits with DC sources

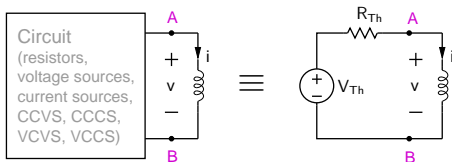

* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.

* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$


$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $v = 0$, and we get $i^{(p)} = V_{Th}/R_{Th}$ as a particular solution (which happens to be simply a constant).

* $i = i^{(h)} + i^{(p)} = K \exp(-t/\tau) + V_{Th}/R_{Th}$.


* In general, $i(t) = A \exp(-t/\tau) + B$, where A and B can be obtained from known conditions on i .

RL circuits with DC sources (continued)

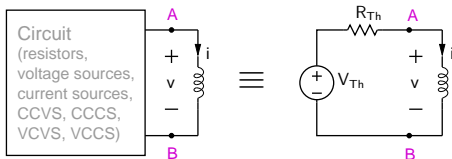

- * If all sources are DC (constant), we have $i(t) = A \exp(-t/\tau) + B$, $\tau = L/R$.


RL circuits with DC sources (continued)

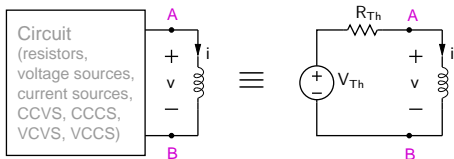

- * If all sources are DC (constant), we have $i(t) = A \exp(-t/\tau) + B$, $\tau = L/R$.


- * $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.

RL circuits with DC sources (continued)

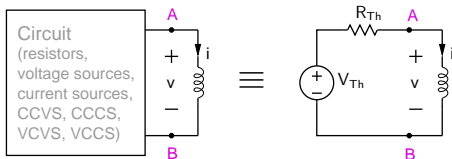


- * If all sources are DC (constant), we have $i(t) = A \exp(-t/\tau) + B$, $\tau = L/R$.
- * $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.
- * As $t \rightarrow \infty$, $v \rightarrow 0$, i.e., the inductor behaves like a short circuit since all derivatives vanish.

RL circuits with DC sources (continued)

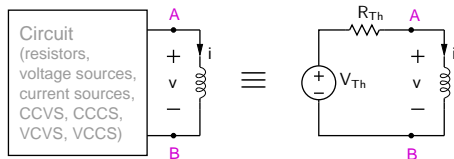


- * If all sources are DC (constant), we have $i(t) = A \exp(-t/\tau) + B$, $\tau = L/R$.
- * $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.
- * As $t \rightarrow \infty$, $v \rightarrow 0$, i.e., the inductor behaves like a short circuit since all derivatives vanish.
- * Since the circuit in the black box is linear, any variable (current or voltage) in the circuit can be expressed as $x(t) = K_1 \exp(-t/\tau) + K_2$, where K_1 and K_2 can be obtained from suitable conditions on $x(t)$.

RC circuits: Can V_C change “suddenly?”

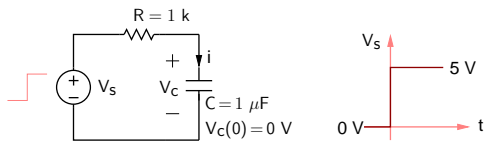


RC circuits: Can V_C change “suddenly?”

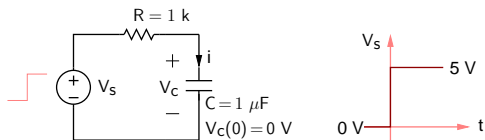


- * V_s changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?

RC circuits: Can V_C change “suddenly?”

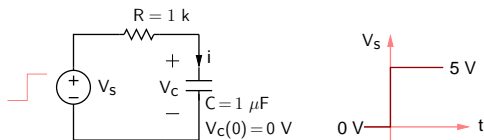


- * V_s changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\text{ }\mu\text{s}$ at a constant rate of $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$?

RC circuits: Can V_C change “suddenly?”

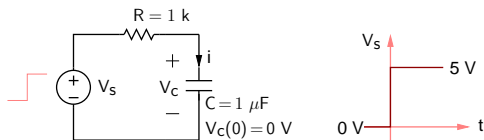


- * V_S changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\text{ }\mu\text{s}$ at a constant rate of $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$?
- * $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$.

RC circuits: Can V_C change “suddenly?”

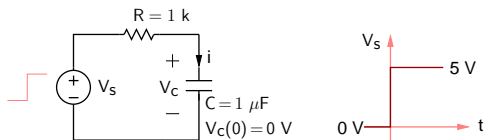


- * V_S changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\text{ }\mu\text{s}$ at a constant rate of $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$?
- * $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$.
- * With $i = 1\text{ A}$, the voltage drop across R would be 1000 V! Not allowed by KVL.

RC circuits: Can V_C change “suddenly?”

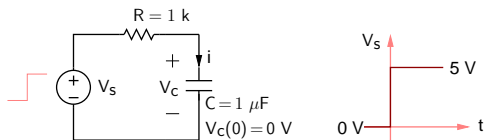

- * V_S changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\text{ }\mu\text{s}$ at a constant rate of $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$?
- * $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$.
- * With $i = 1\text{ A}$, the voltage drop across R would be 1000 V ! Not allowed by KVL.
- * We conclude that $V_C(0^+) = V_C(0^-) \Rightarrow$ A capacitor does not allow abrupt changes in V_C if there is a finite resistance in the circuit.


RC circuits: Can V_C change “suddenly?”

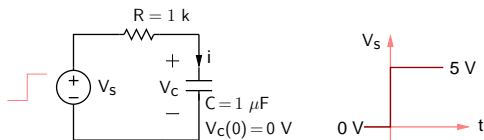

- * V_S changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\text{ }\mu\text{s}$ at a constant rate of $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$?
- * $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$.
- * With $i = 1\text{ A}$, the voltage drop across R would be 1000 V! Not allowed by KVL.
- * We conclude that $V_C(0^+) = V_C(0^-) \Rightarrow$ A capacitor does not allow abrupt changes in V_C if there is a finite resistance in the circuit.
- * Similarly, an inductor does not allow abrupt changes in i_L .

Analysis of RC/RL circuits with a piece-wise constant source

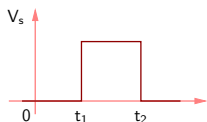- * Identify intervals in which the source voltages/currents are constant.
For example,




(1) $t < t_1$

(2) $t_1 < t < t_2$

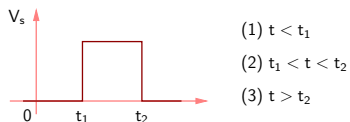(3) $t > t_2$

Analysis of RC/RL circuits with a piece-wise constant source


- * Identify intervals in which the source voltages/currents are constant.
For example,



- * For *any* current or voltage $x(t)$, write general expressions such as,
 $x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$
 $x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$
 $x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$

Analysis of RC/RL circuits with a piece-wise constant source

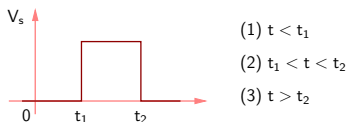
- * Identify intervals in which the source voltages/currents are constant.
For example,



- * For *any* current or voltage $x(t)$, write general expressions such as,
 $x(t) = A_1 \exp(-t/\tau) + B_1$, $t < t_1$,
 $x(t) = A_2 \exp(-t/\tau) + B_2$, $t_1 < t < t_2$,
 $x(t) = A_3 \exp(-t/\tau) + B_3$, $t > t_2$.
- * Work out suitable conditions on $x(t)$ at specific time points using

Analysis of RC/RL circuits with a piece-wise constant source

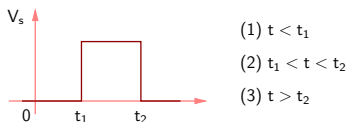- * Identify intervals in which the source voltages/currents are constant.
For example,




- * For any current or voltage $x(t)$, write general expressions such as,
 $x(t) = A_1 \exp(-t/\tau) + B_1$, $t < t_1$,
 $x(t) = A_2 \exp(-t/\tau) + B_2$, $t_1 < t < t_2$,
 $x(t) = A_3 \exp(-t/\tau) + B_3$, $t > t_2$.
- * Work out suitable conditions on $x(t)$ at specific time points using
 - (a) If the source voltage/current has not changed for a "long" time (long compared to τ), all derivatives are zero.

$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$

Analysis of RC/RL circuits with a piece-wise constant source

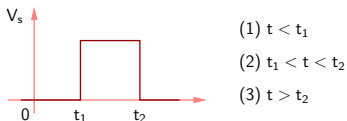
- * Identify intervals in which the source voltages/currents are constant.
For example,



- * For *any* current or voltage $x(t)$, write general expressions such as,
 $x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$
 $x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$
 $x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$
- * Work out suitable conditions on $x(t)$ at specific time points using
 - (a) If the source voltage/current has not changed for a “long” time (long compared to τ), all derivatives are zero.
$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$
 - (b) When a source voltage (or current) changes, say, at $t = t_0$, $V_C(t)$ or $i_L(t)$ cannot change abruptly, i.e.,
$$V_C(t_0^+) = V_C(t_0^-), \text{ and } i_L(t_0^+) = i_L(t_0^-).$$


Analysis of RC/RL circuits with a piece-wise constant source

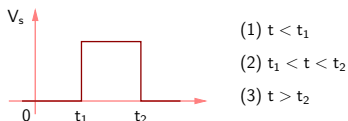- * Identify intervals in which the source voltages/currents are constant.
For example,




- * For *any* current or voltage $x(t)$, write general expressions such as,
 $x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$
 $x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$
 $x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$
- * Work out suitable conditions on $x(t)$ at specific time points using
 - (a) If the source voltage/current has not changed for a “long” time (long compared to τ), all derivatives are zero.
$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$
 - (b) When a source voltage (or current) changes, say, at $t = t_0$,
 $V_C(t)$ or $i_L(t)$ cannot change abruptly, i.e.,
 $V_C(t_0^+) = V_C(t_0^-),$ and $i_L(t_0^+) = i_L(t_0^-).$
- * Compute A_1, B_1, \dots using the conditions on $x(t)$.

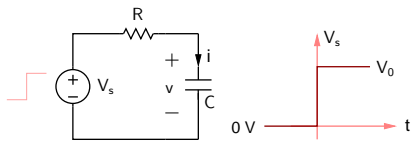RC circuits: charging and discharging transients




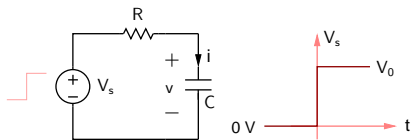RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

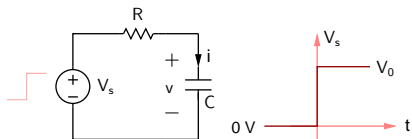RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_s(0^-) = 0 \text{ V}$$


$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$

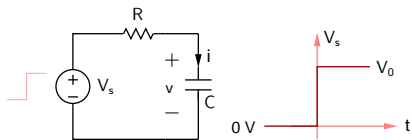RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

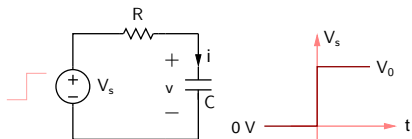RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$

Imposing (1) and (2) on Eq. (A), we get


$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

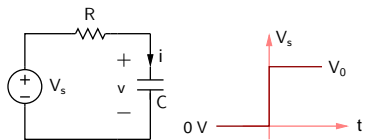RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$


$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

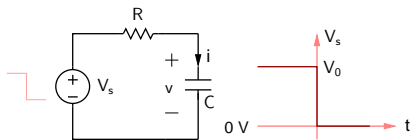

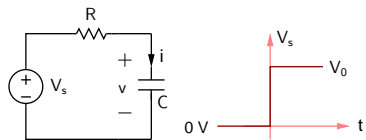RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$


$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

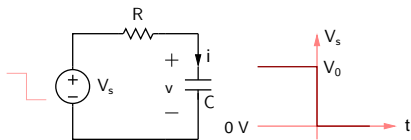

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

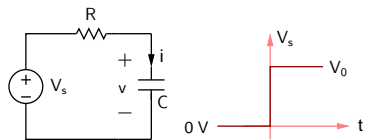RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-) because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

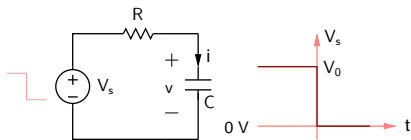

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:


$$(1) v(0^-) = V_S(0^-) = V_0$$

$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at 0^+ (and not at 0^-) because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = 0 \text{ V}$$

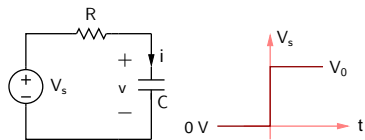RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-) because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

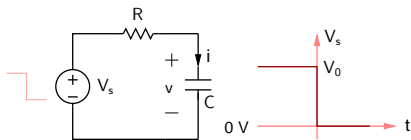

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_S(0^-) = V_0$$

$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at 0^+ (and not at 0^-) because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = 0 \text{ V}$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: V_0 = A + B,$$

$$t \rightarrow \infty: 0 = B.$$

$$\text{i.e., } A = V_0, B = 0$$

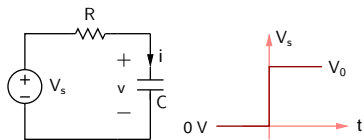RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-) because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

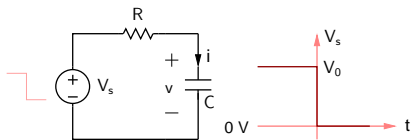

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_S(0^-) = V_0$$

$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at 0^+ (and not at 0^-) because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = 0 \text{ V}$$

Imposing (1) and (2) on Eq. (A), we get


$$t = 0^+: V_0 = A + B,$$

$$t \rightarrow \infty: 0 = B.$$

$$\text{i.e., } A = V_0, B = 0$$


$$v(t) = V_0 \exp(-t/\tau)$$

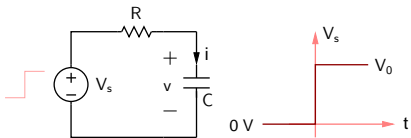RC circuits: charging and discharging transients



Compute $i(t)$, $t > 0$.

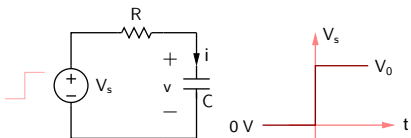
RC circuits: charging and discharging transients



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A) } i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$

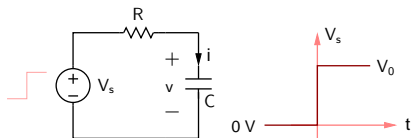RC circuits: charging and discharging transients



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$

(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.


$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain

$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

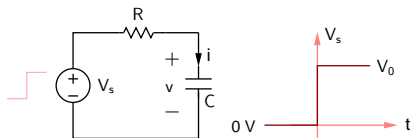RC circuits: charging and discharging transients



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$


Using these conditions, we obtain
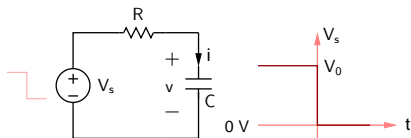
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute $i(t)$, $t > 0$.

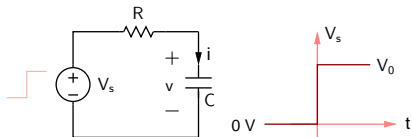RC circuits: charging and discharging transients



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain

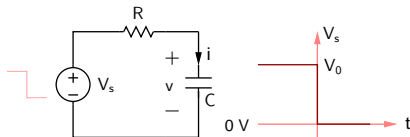
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [\exp(-t/\tau)] \\ &= -\frac{CV_0}{\tau} \exp(-t/\tau) = -\frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$

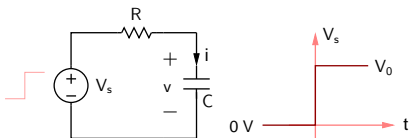RC circuits: charging and discharging transients



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain
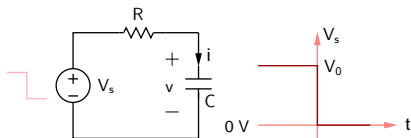
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [\exp(-t/\tau)] \\ &= -\frac{CV_0}{\tau} \exp(-t/\tau) = -\frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$

(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.


$$t = 0^+: v = V_0, V_s = 0 \Rightarrow i(0^+) = -V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain

$$A' = -\frac{V_0}{R}, B' = 0 \Rightarrow i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

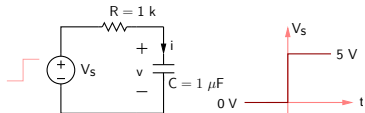
RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$


$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

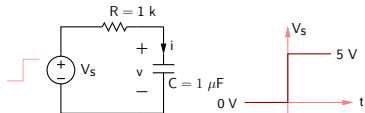RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

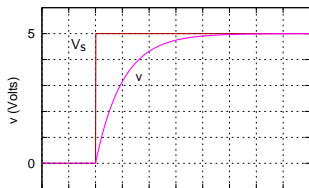


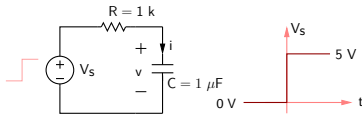RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



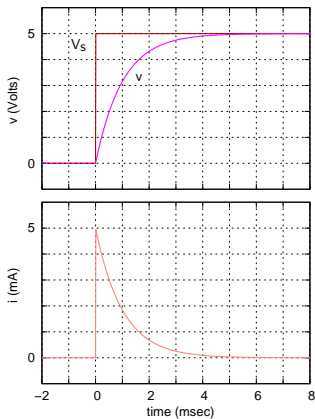


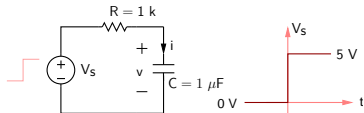RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$


$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

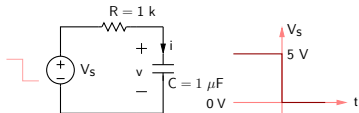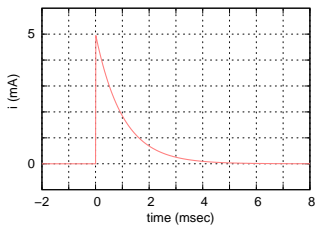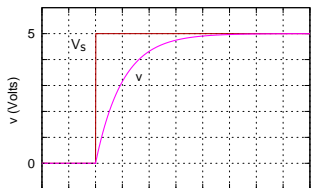

$$v(t) = V_0 \exp(-t/\tau)$$




$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

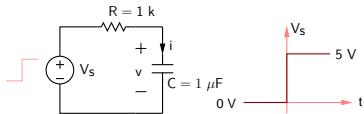RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

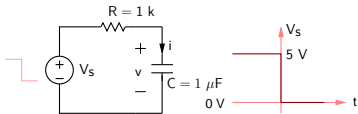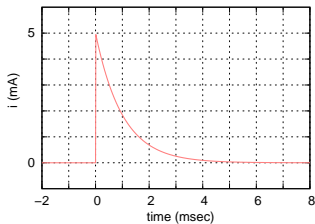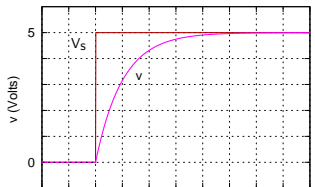


$$v(t) = V_0 \exp(-t/\tau)$$

$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$



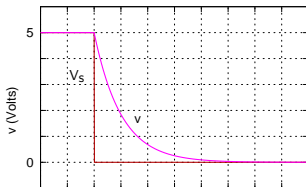


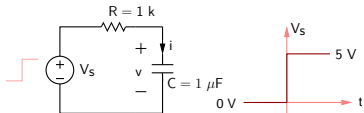RC circuits: charging and discharging transients





$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

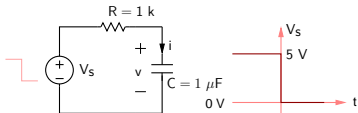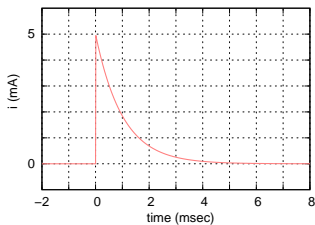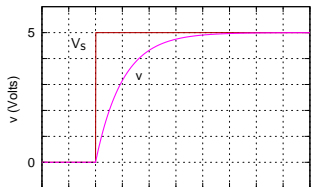

$$v(t) = V_0 \exp(-t/\tau)$$

$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

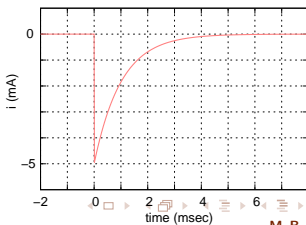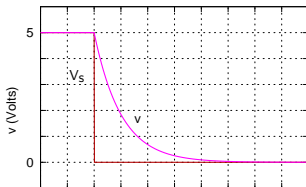

Significance of the time constant (τ)

x	e^{-x}	$1 - e^{-x}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	4.9787×10^{-2}	0.9502
4.0	1.8315×10^{-2}	0.9817
5.0	6.7379×10^{-3}	0.9933

Significance of the time constant (τ)

x	e^{-x}	$1 - e^{-x}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	4.9787×10^{-2}	0.9502
4.0	1.8315×10^{-2}	0.9817
5.0	6.7379×10^{-3}	0.9933

* For $x = 5$, $e^{-x} \simeq 0$, $1 - e^{-x} \simeq 1$.


Significance of the time constant (τ)

x	e^{-x}	$1 - e^{-x}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	4.9787×10^{-2}	0.9502
4.0	1.8315×10^{-2}	0.9817
5.0	6.7379×10^{-3}	0.9933

- * For $x = 5$, $e^{-x} \simeq 0$, $1 - e^{-x} \simeq 1$.
- * In RC circuits, $x = t/\tau \Rightarrow$ When $t = 5\tau$, the charging (or discharging) process is almost complete.


Significance of the time constant (τ)

x	e^{-x}	$1 - e^{-x}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	4.9787×10^{-2}	0.9502
4.0	1.8315×10^{-2}	0.9817
5.0	6.7379×10^{-3}	0.9933


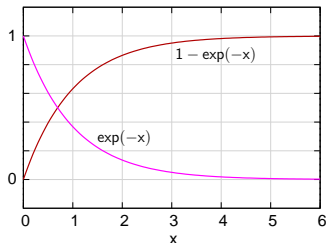


- * For $x = 5$, $e^{-x} \simeq 0$, $1 - e^{-x} \simeq 1$.
- * In RC circuits, $x = t/\tau \Rightarrow$ When $t = 5\tau$, the charging (or discharging) process is almost complete.

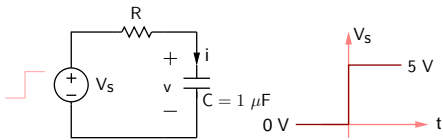
RC circuits: charging and discharging transients





$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

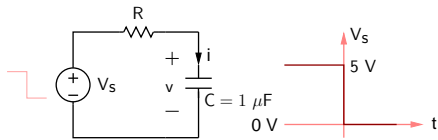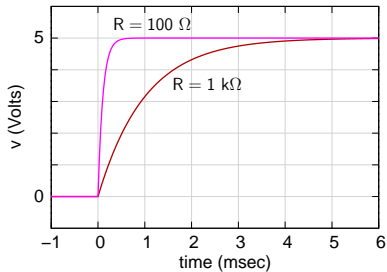

$$v(t) = V_0 \exp(-t/\tau)$$

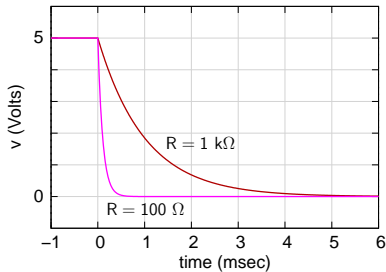

RL circuit: example

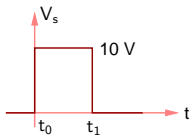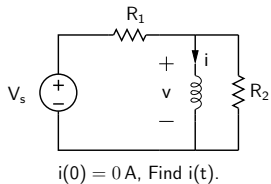

$$R_1 = 10 \Omega$$



$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

RL circuit: example

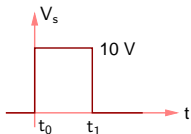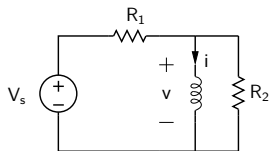

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$



$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$, Find $i(t)$.

There are three intervals of constant V_s :

- (1) $t < t_0$
- (2) $t_0 < t < t_1$
- (3) $t > t_1$

RL circuit: example

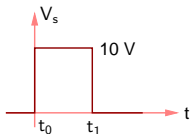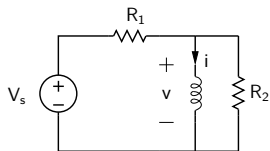

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$, Find $i(t)$.


There are three intervals of constant V_s :

(1) $t < t_0$

(2) $t_0 < t < t_1$

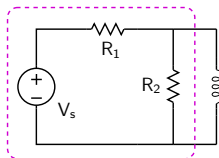(3) $t > t_1$



R_{Th} seen by L is the same in all intervals:



$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

RL circuit: example

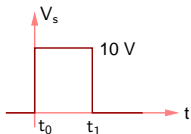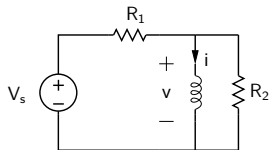

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$, Find $i(t)$.


There are three intervals of constant V_s :

(1) $t < t_0$

(2) $t_0 < t < t_1$

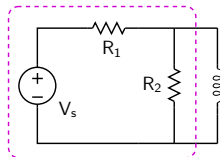(3) $t > t_1$

R_{Th} seen by L is the same in all intervals:





$$R_{\text{Th}} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{\text{Th}} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

At $t = t_0^-$, $v = 0 \text{ V}$, $V_s = 0 \text{ V}$.

$\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$.

RL circuit: example

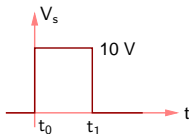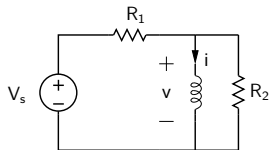

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$


$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$, Find $i(t)$.

There are three intervals of constant V_s :

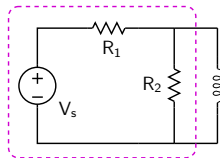- (1) $t < t_0$
- (2) $t_0 < t < t_1$
- (3) $t > t_1$

R_{Th} seen by L is the same in all intervals:




$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$



At $t = t_0^-$, $v = 0 \text{ V}$, $V_s = 0 \text{ V}$.
 $\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$.

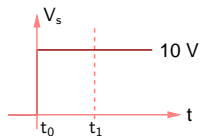If V_s did not change at $t = t_1$,
 we would have



$v(\infty) = 0 \text{ V}$, $i(\infty) = 10 \text{ V}/10 \Omega = 1 \text{ A}$.

RL circuit: example

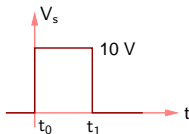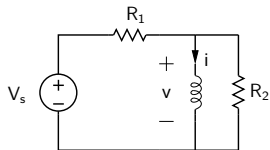

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$


$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$, Find $i(t)$.

There are three intervals of constant V_s :

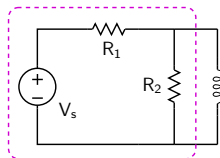- (1) $t < t_0$
- (2) $t_0 < t < t_1$
- (3) $t > t_1$

R_{Th} seen by L is the same in all intervals:




$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

At $t = t_0^-$, $v = 0 \text{ V}$, $V_s = 0 \text{ V}$.
 $\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$.


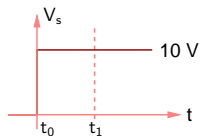
If V_s did not change at $t = t_1$,
 we would have



$v(\infty) = 0 \text{ V}$, $i(\infty) = 10 \text{ V}/10 \Omega = 1 \text{ A}$.

Using $i(t_0^+)$ and $i(\infty)$, we can obtain
 $i(t)$, $t > 0$ (See next slide).

RL circuit: example

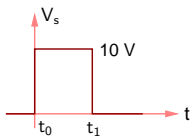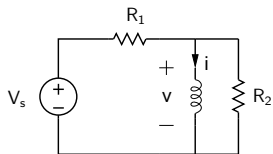


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$



$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

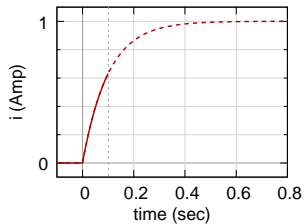

RL circuit: example

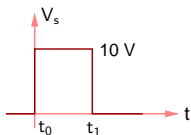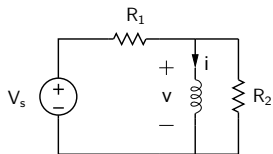


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$



$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

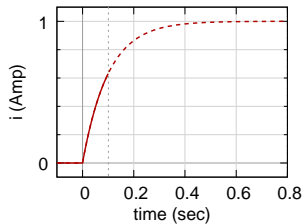

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

RL circuit: example

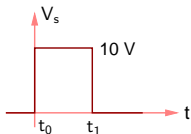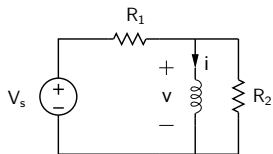


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$


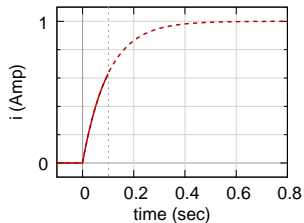


For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.

Consider $t > t_1$.

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

RL circuit: example

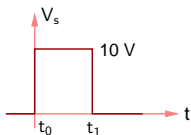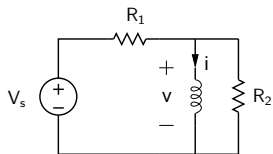


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

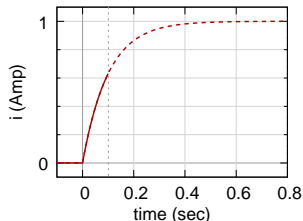

For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.



Consider $t > t_1$.

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

RL circuit: example

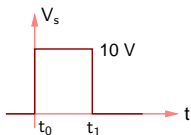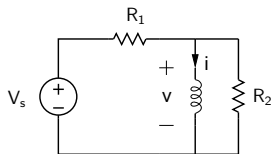


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

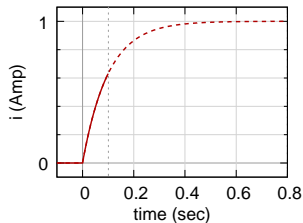

For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.

Consider $t > t_1$.



$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

RL circuit: example

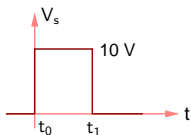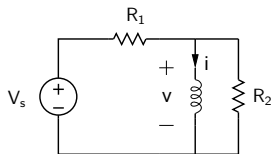


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

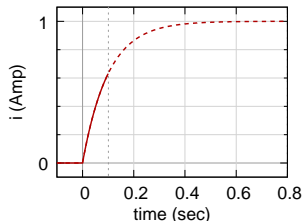

For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.

Consider $t > t_1$.

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$



$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$

It is convenient to rewrite $i(t)$ as

$$i(t) = A' \exp[-(t - t_1)/\tau] + B.$$

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

RL circuit: example

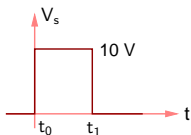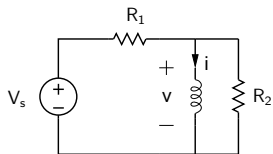


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

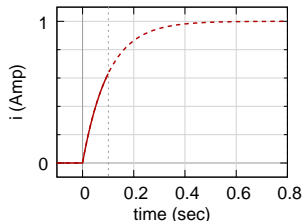

In reality, V_s changes at $t = t_1$, and we need to work out the solution for $t > t_1$ separately.

For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.

Consider $t > t_1$.

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1\text{)}.$$

$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$



It is convenient to rewrite $i(t)$ as

$$i(t) = A' \exp[-(t - t_1)/\tau] + B.$$

Using $i(t_1^+)$ and $i(\infty)$, we get

$$i(t) = 0.693 \exp[-(t - t_1)/\tau] \text{ A.}$$

RL circuit: example

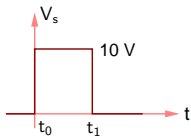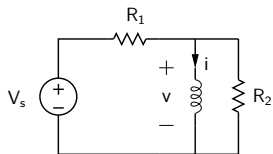

$$R_1 = 10 \Omega$$


$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$



$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$
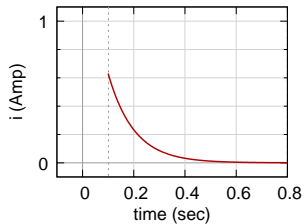
$$i(t) = 0.693 \exp[-(t - t_1)/\tau] \text{ A.}$$



RL circuit: example

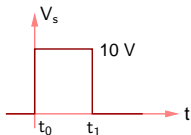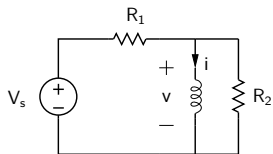

$$R_1 = 10 \Omega$$


$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$


$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$
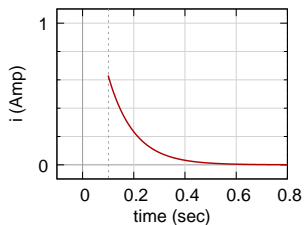
$$i(t) = 0.693 \exp[-(t - t_1)/\tau] \text{ A.}$$




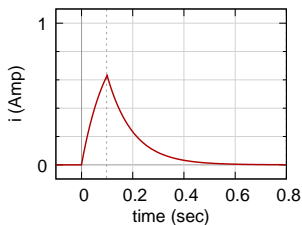Combining the solutions for $t_0 < t < t_1$ and $t > t_1$, we get




(SEQUEL file: ee101_r11.sqproj)


RC circuit: example

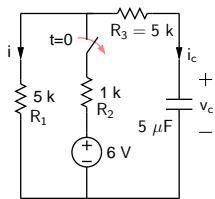

RC circuit: example

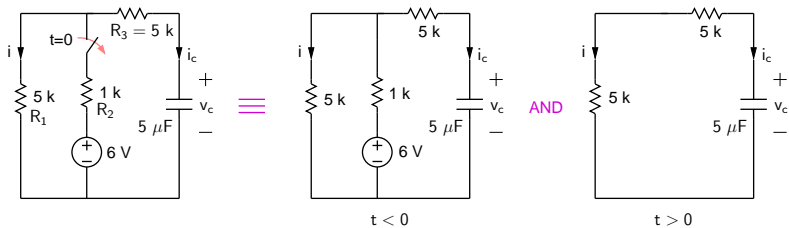


RC circuit: example

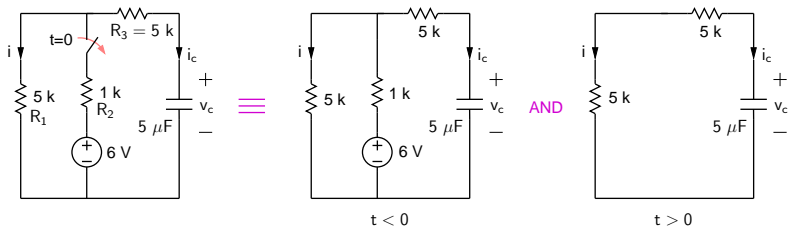

$t = 0^-$: capacitor is an open circuit, $\Rightarrow i(0^-) = 6\text{ V}/(5\text{ k} + 1\text{ k}) = 1\text{ mA}$.


RC circuit: example

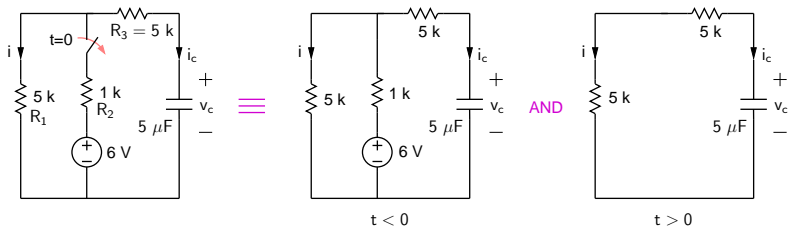

$t = 0^-$: capacitor is an open circuit, $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$.

$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$.

RC circuit: example

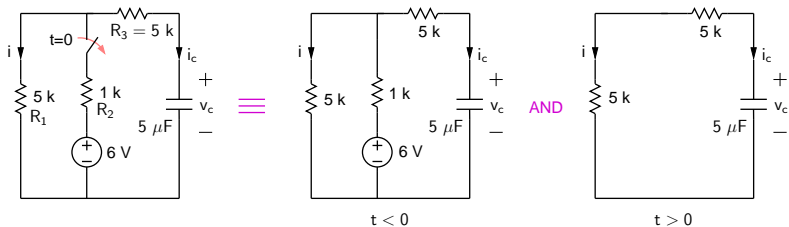


$t = 0^-$: capacitor is an open circuit, $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$.

$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$.

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$.

RC circuit: example

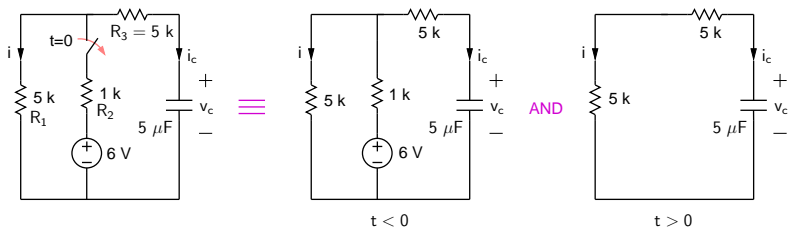


$t = 0^-$: capacitor is an open circuit, $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$.

$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$.

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$.

Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$.

RC circuit: example

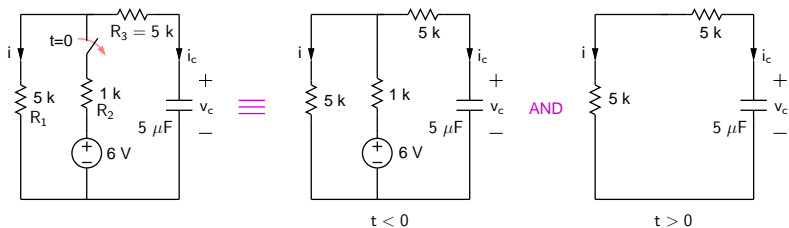

$t = 0^-$: capacitor is an open circuit, $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$.

$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$.


$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$.

Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$.

Using $i(0^+)$ and $i(\infty) = 0 \text{ A}$, we get

$i(t) = 0.5 \exp(-t/\tau) \text{ mA}$.

RC circuit: example

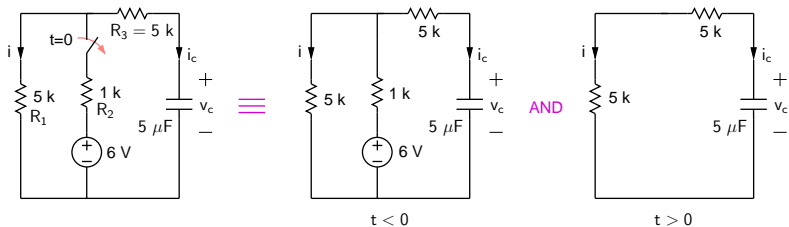

$t = 0^-$: capacitor is an open circuit, $\Rightarrow i(0^-) = 6\text{ V}/(5\text{ k} + 1\text{ k}) = 1\text{ mA}$.


$v_c(0^-) = 6\text{ V} - 1\text{ mA} \times R_2 = 5\text{ V} \Rightarrow v_c(0^+) = 5\text{ V}$.

$\Rightarrow i(0^+) = 5\text{ V}/(5\text{ k} + 5\text{ k}) = 0.5\text{ mA}$.


Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10\text{ k} \times 5\text{ }\mu\text{F} = 50\text{ ms}$.

Using $i(0^+)$ and $i(\infty) = 0\text{ A}$, we get

$i(t) = 0.5 \exp(-t/\tau)\text{ mA}$.

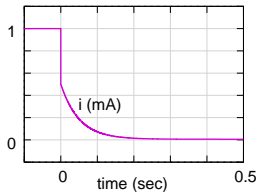

RC circuit: example

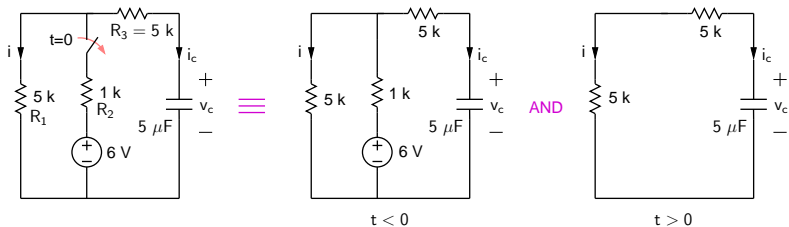

$t = 0^-$: capacitor is an open circuit, $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$.


$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$.

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$.


Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$.

Using $i(0^+)$ and $i(\infty) = 0 \text{ A}$, we get

$i(t) = 0.5 \exp(-t/\tau) \text{ mA}$.

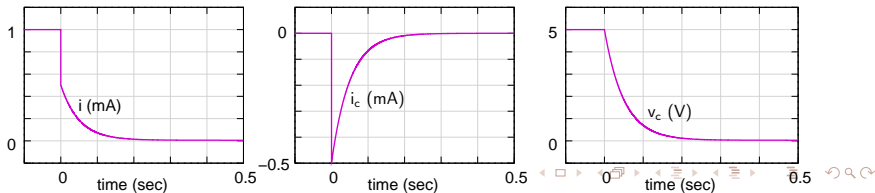

RC circuit: example

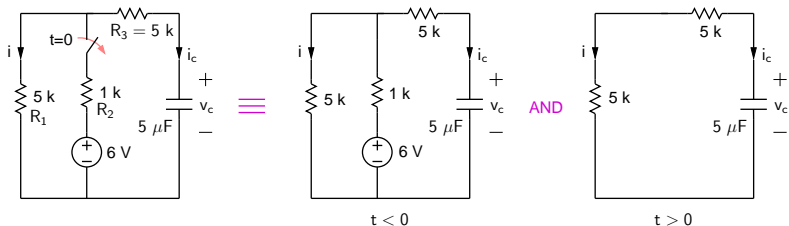

$t = 0^-$: capacitor is an open circuit, $\Rightarrow i(0^-) = 6\text{ V}/(5\text{ k} + 1\text{ k}) = 1\text{ mA}$.

$v_c(0^-) = 6\text{ V} - 1\text{ mA} \times R_2 = 5\text{ V} \Rightarrow v_c(0^+) = 5\text{ V}$.


$\Rightarrow i(0^+) = 5\text{ V}/(5\text{ k} + 5\text{ k}) = 0.5\text{ mA}$.

Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10\text{ k} \times 5\text{ }\mu\text{F} = 50\text{ ms}$.


Using $i(0^+)$ and $i(\infty) = 0\text{ A}$, we get


$i(t) = 0.5 \exp(-t/\tau)\text{ mA}$.

(SEQUEL file: ee101_rc2.sqproj)

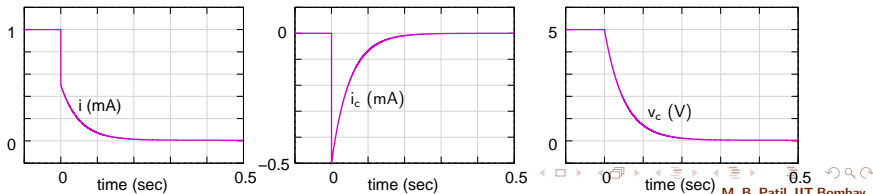


RC circuits: home work

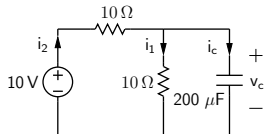


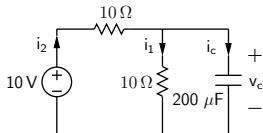

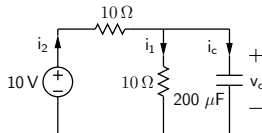- * Given $v_c(0) = 0\text{ V}$, find $v_c(t)$ for $t > 0$. Using this $v_c(t)$, find i_1 , i_2 , i_c for $t > 0$. Plot v_c , i_1 , i_2 , i_c versus t .




- * Given $v_c(0) = 0$ V, find $v_c(t)$ for $t > 0$. Using this $v_c(t)$, find i_1 , i_2 , i_c for $t > 0$. Plot v_c , i_1 , i_2 , i_c versus t .
- * Find i_1 , i_2 , i_c directly (i.e., without getting v_c) by finding the initial and final conditions for each of them ($i_1(0^+)$ and $i_1(\infty)$, etc.) and then using them to compute the coefficients in the general expression, $x(t) = A \exp(-t/\tau) + B$.

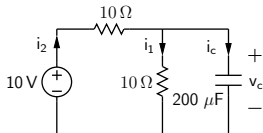


- * Given $v_c(0) = 0 \text{ V}$, find $v_c(t)$ for $t > 0$. Using this $v_c(t)$, find i_1 , i_2 , i_c for $t > 0$. Plot v_c , i_1 , i_2 , i_c versus t .
- * Find i_1 , i_2 , i_c directly (i.e., without getting v_c) by finding the initial and final conditions for each of them ($i_1(0^+)$ and $i_1(\infty)$, etc.) and then using them to compute the coefficients in the general expression, $x(t) = A \exp(-t/\tau) + B$.
- * Verify your results with SEQUEL (file: ee101_rc3.sqproj).

RC circuits: home work

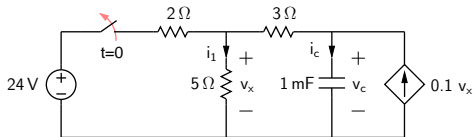


RC circuits: home work

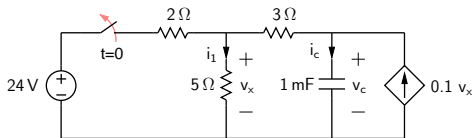


* Find $v_c(0^-)$, $v_c(\infty)$.


RC circuits: home work

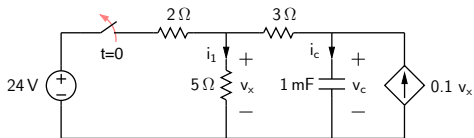

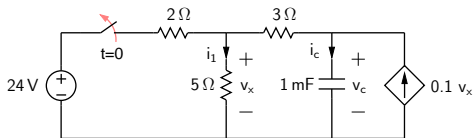- * Find $v_c(0^-)$, $v_c(\infty)$.
- * Find R_{Th} as seen by the capacitor for $t > 0$.




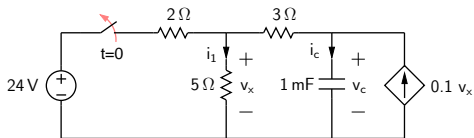- * Find $v_c(0^-)$, $v_c(\infty)$.
- * Find R_{Th} as seen by the capacitor for $t > 0$.
- * Solve for $v_c(t)$ and $i_1(t)$, $t > 0$.




- * Find $v_c(0^-)$, $v_c(\infty)$.
- * Find R_{Th} as seen by the capacitor for $t > 0$.
- * Solve for $v_c(t)$ and $i_1(t)$, $t > 0$.
- * Verify your results with SEQUEL (file: ee101_rc4.sqproj).

RL circuits: home work

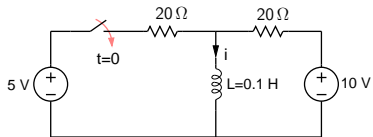


RL circuits: home work

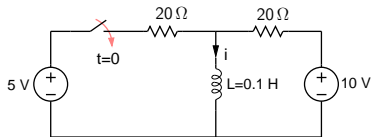


* Find $i(0^-)$, $i(\infty)$.

RL circuits: home work

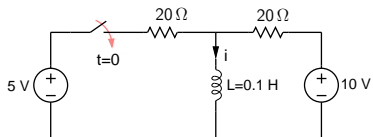


- * Find $i(0^-)$, $i(\infty)$.
- * Find R_{Th} as seen by the inductor for $t > 0$.

RL circuits: home work

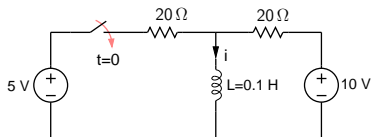

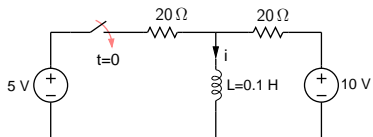- * Find $i(0^-)$, $i(\infty)$.
- * Find R_{Th} as seen by the inductor for $t > 0$.
- * Solve for $i(t)$, $t > 0$.



- * Find $i(0^-)$, $i(\infty)$.
- * Find R_{Th} as seen by the inductor for $t > 0$.
- * Solve for $i(t)$, $t > 0$.
- * Verify your results with SEQUEL (file: ee101_r12.sqproj).