

# EE101: BJT basics

---





**M. B. Patil**



[mbpatil@ee.iitb.ac.in](mailto:mbpatil@ee.iitb.ac.in)  
[www.ee.iitb.ac.in/~sequel](http://www.ee.iitb.ac.in/~sequel)

Department of Electrical Engineering  
Indian Institute of Technology Bombay

# Bipolar Junction Transistors

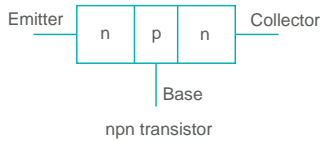
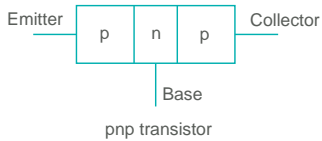


# Bipolar Junction Transistors

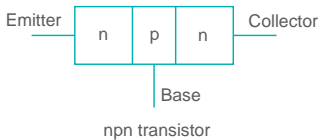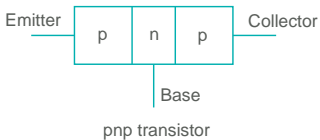



- \* Bipolar: both electrons and holes contribute to conduction

# Bipolar Junction Transistors

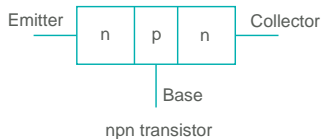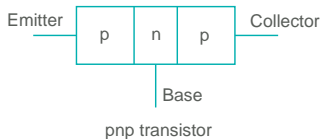

- \* Bipolar: both electrons and holes contribute to conduction
- \* Junction: device includes two  $p$ - $n$  junctions (as opposed to a “point-contact” transistor, the first transistor)

# Bipolar Junction Transistors

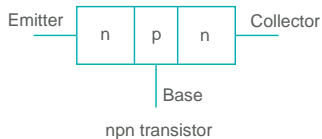
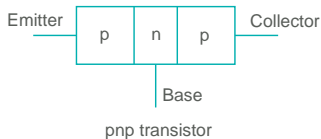


- \* Bipolar: both electrons and holes contribute to conduction
- \* Junction: device includes two  $p$ - $n$  junctions (as opposed to a “point-contact” transistor, the first transistor)
- \* Transistor: “transfer resistor”

When Bell Labs had an informal contest to name their new invention, one engineer pointed out that it acts like a resistor, but a resistor where the voltage is transferred across the device to control the resulting current.

(<http://amasci.com/amateur/trshort.html>)

# Bipolar Junction Transistors

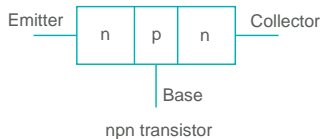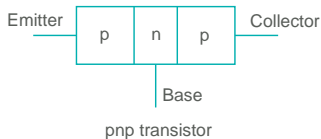

- \* Bipolar: both electrons and holes contribute to conduction
- \* Junction: device includes two  $p$ - $n$  junctions (as opposed to a “point-contact” transistor, the first transistor)



- \* Transistor: “transfer resistor”

When Bell Labs had an informal contest to name their new invention, one engineer pointed out that it acts like a resistor, but a resistor where the voltage is transferred across the device to control the resulting current.

(<http://amasci.com/amateur/trshort.html>)

- \* invented in 1947 by Shockley, Bardeen, and Brattain at Bell Laboratories.

# Bipolar Junction Transistors

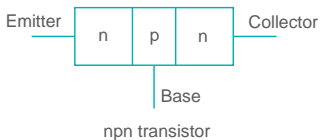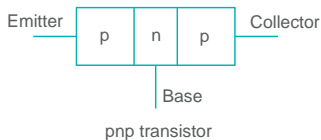

- \* Bipolar: both electrons and holes contribute to conduction
- \* Junction: device includes two  $p$ - $n$  junctions (as opposed to a “point-contact” transistor, the first transistor)



- \* Transistor: “transfer resistor”

When Bell Labs had an informal contest to name their new invention, one engineer pointed out that it acts like a resistor, but a resistor where the voltage is transferred across the device to control the resulting current.

(<http://amasci.com/amateur/trshort.html>)

- \* invented in 1947 by Shockley, Bardeen, and Brattain at Bell Laboratories.
- \* “A BJT is two diodes connected back-to-back.”

# Bipolar Junction Transistors

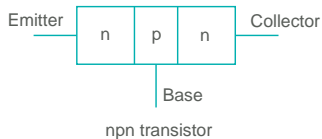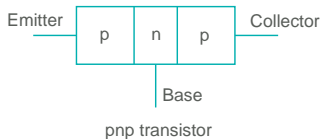

- \* Bipolar: both electrons and holes contribute to conduction
- \* Junction: device includes two  $p$ - $n$  junctions (as opposed to a “point-contact” transistor, the first transistor)

- \* Transistor: “transfer resistor”

When Bell Labs had an informal contest to name their new invention, one engineer pointed out that it acts like a resistor, but a resistor where the voltage is transferred across the device to control the resulting current.

(<http://amasci.com/amateur/trshort.html>)


- \* invented in 1947 by Shockley, Bardeen, and Brattain at Bell Laboratories.
- \* “A BJT is two diodes connected back-to-back.”

**WRONG!** Let us see why.



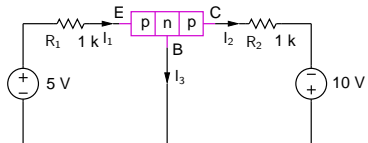
# Bipolar Junction Transistors

Consider a *pnp* BJT in the following circuit:



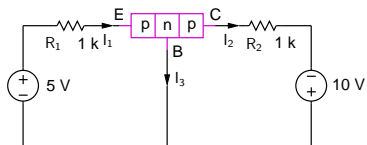
# Bipolar Junction Transistors

Consider a *pnp* BJT in the following circuit:




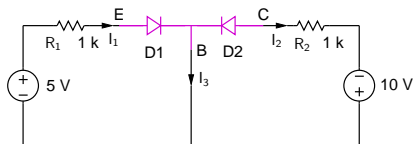If the transistor is replaced with two diodes connected back-to-back, we get,



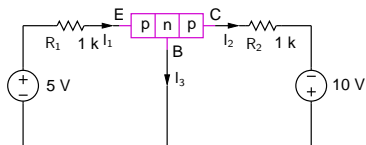
# Bipolar Junction Transistors

Consider a *pnp* BJT in the following circuit:



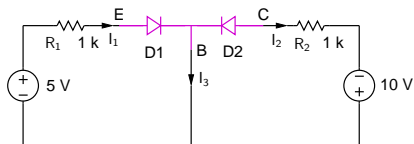If the transistor is replaced with two diodes connected back-to-back, we get,



Assuming  $V_{on} = 0.7 \text{ V}$  for D1, we get


$$I_1 = \frac{5 \text{ V} - 0.7 \text{ V}}{R_1} = 4.3 \text{ mA},$$

$I_2 = 0$  (since D2 is reverse biased), and

$$I_3 \approx I_1 = 4.3 \text{ mA}.$$

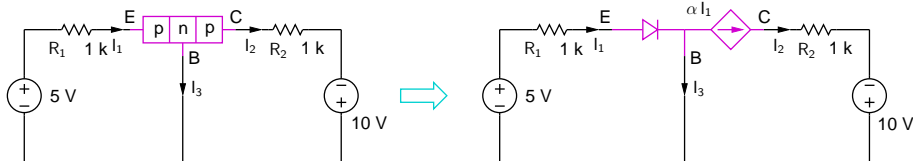
# Bipolar Junction Transistors

Using a more accurate equivalent circuit for the BJT, we obtain,


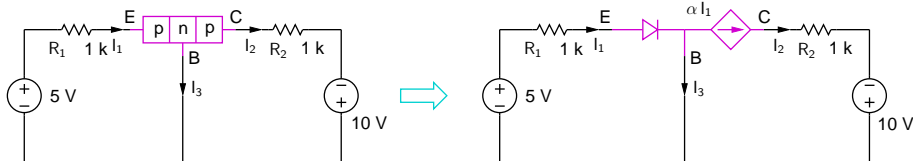
# Bipolar Junction Transistors

Using a more accurate equivalent circuit for the BJT, we obtain,




We now get,

$$I_1 = \frac{5\text{ V} - 0.7\text{ V}}{R_1} = 4.3\text{ mA (as before),}$$
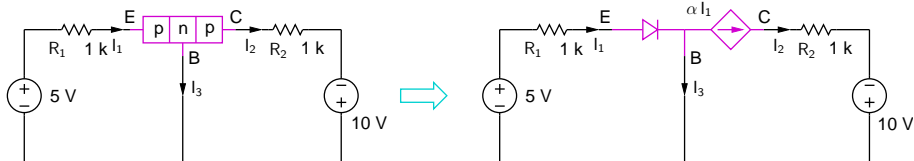
# Bipolar Junction Transistors

Using a more accurate equivalent circuit for the BJT, we obtain,




We now get,

$$I_1 = \frac{5\text{ V} - 0.7\text{ V}}{R_1} = 4.3\text{ mA (as before),}$$

$$I_2 = \alpha I_1 \approx 4.3\text{ mA (since } \alpha \approx 1 \text{ for a typical BJT), and}$$
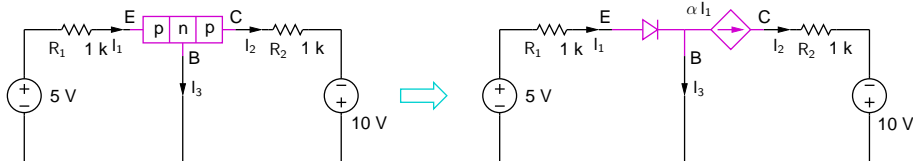
# Bipolar Junction Transistors

Using a more accurate equivalent circuit for the BJT, we obtain,



We now get,


$$I_1 = \frac{5\text{ V} - 0.7\text{ V}}{R_1} = 4.3\text{ mA (as before),}$$

$I_2 = \alpha I_1 \approx 4.3\text{ mA}$  (since  $\alpha \approx 1$  for a typical BJT), and

$$I_3 = I_1 - I_2 = (1 - \alpha) I_1 \approx 0\text{ A.}$$
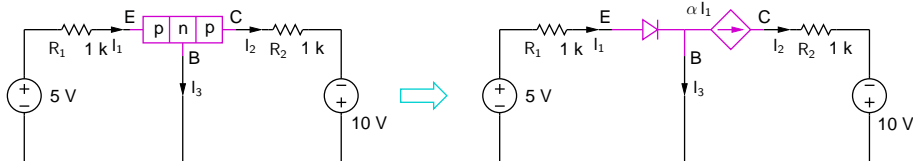
# Bipolar Junction Transistors

Using a more accurate equivalent circuit for the BJT, we obtain,



We now get,

$$I_1 = \frac{5\text{ V} - 0.7\text{ V}}{R_1} = 4.3\text{ mA (as before),}$$

$$I_2 = \alpha I_1 \approx 4.3\text{ mA (since } \alpha \approx 1 \text{ for a typical BJT), and}$$


$$I_3 = I_1 - I_2 = (1 - \alpha) I_1 \approx 0\text{ A.}$$

The values of  $I_2$  and  $I_3$  are *dramatically* different than the ones obtained earlier.


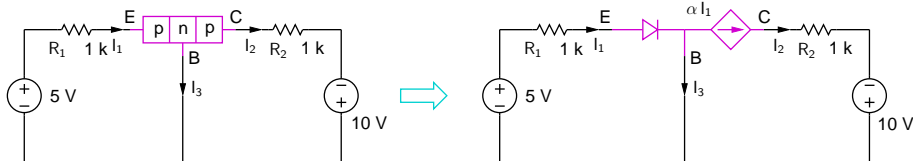
# Bipolar Junction Transistors

Using a more accurate equivalent circuit for the BJT, we obtain,



We now get,

$$I_1 = \frac{5\text{ V} - 0.7\text{ V}}{R_1} = 4.3\text{ mA (as before),}$$

$$I_2 = \alpha I_1 \approx 4.3\text{ mA (since } \alpha \approx 1 \text{ for a typical BJT), and}$$

$$I_3 = I_1 - I_2 = (1 - \alpha) I_1 \approx 0\text{ A.}$$

The values of  $I_2$  and  $I_3$  are *dramatically* different than the ones obtained earlier.

Conclusion: A BJT is NOT the same as two diodes connected back-to-back (although it does have two  $p$ - $n$  junctions).


# Bipolar Junction Transistors

What is wrong with the two-diode model of a BJT?
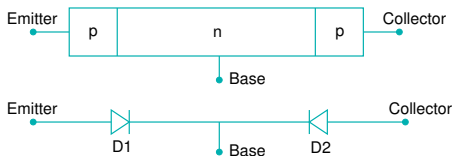
# Bipolar Junction Transistors

What is wrong with the two-diode model of a BJT?


- \* When we replace a BJT with two diodes, we assume that there is no interaction between the two diodes, which may be expected if they are “far apart.”



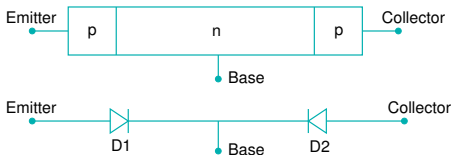
# Bipolar Junction Transistors

What is wrong with the two-diode model of a BJT?

- \* When we replace a BJT with two diodes, we assume that there is no interaction between the two diodes, which may be expected if they are “far apart.”



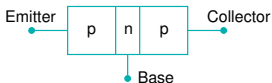
- \* However, in a BJT, exactly the opposite is true. For a higher performance, the base region is made as short as possible (subject to certain constraints), and the two diodes therefore cannot be treated as independent devices.



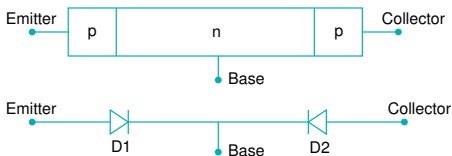
# Bipolar Junction Transistors

What is wrong with the two-diode model of a BJT?

- \* When we replace a BJT with two diodes, we assume that there is no interaction between the two diodes, which may be expected if they are “far apart.”







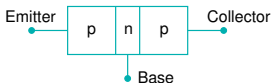- \* However, in a BJT, exactly the opposite is true. For a higher performance, the base region is made as short as possible (subject to certain constraints), and the two diodes therefore cannot be treated as independent devices.




- \* Later, we will look at the “Ebers-Moll model” of a BJT, which is a fairly accurate representation of the transistor action.

# BJT in active mode

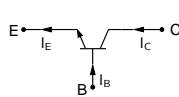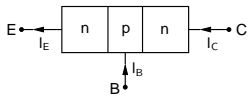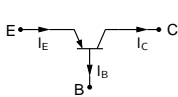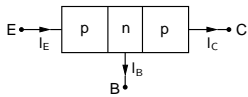


## BJT in active mode

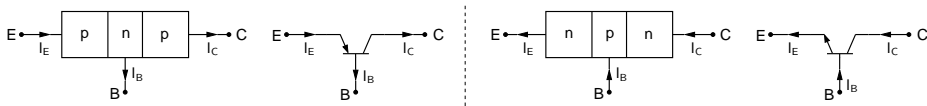

- \* In the active mode of a BJT, the B-E junction is under forward bias, and the B-C junction is under reverse bias.

- For a *pnp* transistor,  $V_{EB} > 0$  V, and  $V_{CB} < 0$  V.
- For an *nnp* transistor,  $V_{BE} > 0$  V, and  $V_{BC} < 0$  V.


## BJT in active mode

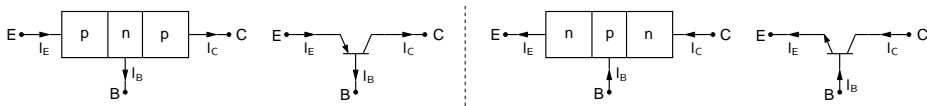

- \* In the active mode of a BJT, the B-E junction is under forward bias, and the B-C junction is under reverse bias.
  - For a *pnp* transistor,  $V_{EB} > 0$  V, and  $V_{CB} < 0$  V.
  - For an *npn* transistor,  $V_{BE} > 0$  V, and  $V_{BC} < 0$  V.
- \* Since the B-E junction is under forward bias, the voltage (magnitude) is typically 0.6 to 0.75 V.




## BJT in active mode

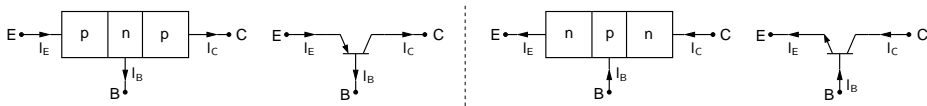


- \* In the active mode of a BJT, the B-E junction is under forward bias, and the B-C junction is under reverse bias.
  - For a *pnp* transistor,  $V_{EB} > 0$  V, and  $V_{CB} < 0$  V.
  - For an *nnp* transistor,  $V_{BE} > 0$  V, and  $V_{BC} < 0$  V.
- \* Since the B-E junction is under forward bias, the voltage (magnitude) is typically 0.6 to 0.75 V.
- \* The B-C voltage can be several Volts (or even hundreds of Volts), and is limited by the breakdown voltage of the B-C junction.

## BJT in active mode

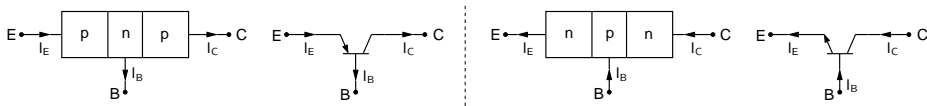



- \* In the active mode of a BJT, the B-E junction is under forward bias, and the B-C junction is under reverse bias.
  - For a *pnp* transistor,  $V_{EB} > 0$  V, and  $V_{CB} < 0$  V.
  - For an *npn* transistor,  $V_{BE} > 0$  V, and  $V_{BC} < 0$  V.
- \* Since the B-E junction is under forward bias, the voltage (magnitude) is typically 0.6 to 0.75 V.
- \* The B-C voltage can be several Volts (or even hundreds of Volts), and is limited by the breakdown voltage of the B-C junction.
- \* The symbol for a BJT includes an arrow for the emitter terminal, its direction indicating the current direction when the transistor is in active mode.

## BJT in active mode

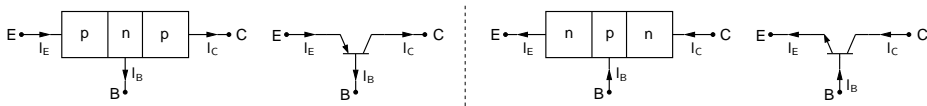


- \* In the active mode of a BJT, the B-E junction is under forward bias, and the B-C junction is under reverse bias.
  - For a *pnp* transistor,  $V_{EB} > 0$  V, and  $V_{CB} < 0$  V.
  - For an *npn* transistor,  $V_{BE} > 0$  V, and  $V_{BC} < 0$  V.
- \* Since the B-E junction is under forward bias, the voltage (magnitude) is typically 0.6 to 0.75 V.
- \* The B-C voltage can be several Volts (or even hundreds of Volts), and is limited by the breakdown voltage of the B-C junction.
- \* The symbol for a BJT includes an arrow for the emitter terminal, its direction indicating the current direction when the transistor is in active mode.
- \* Analog circuits, including amplifiers, are generally designed to ensure that the BJTs are operating in the active mode.

# BJT in active mode

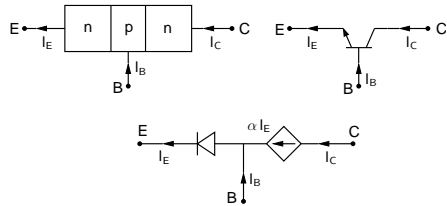
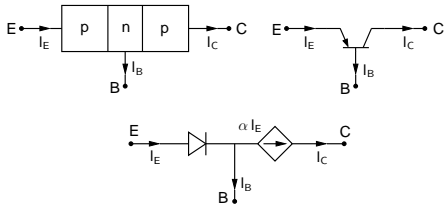


## BJT in active mode

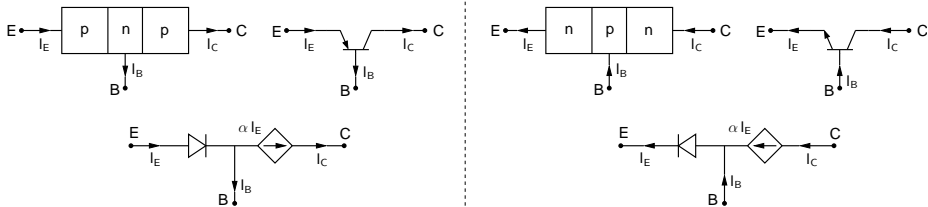



\* In the active mode,  $I_C = \alpha I_E$ ,  $\alpha \approx 1$  (slightly less than 1).

## BJT in active mode

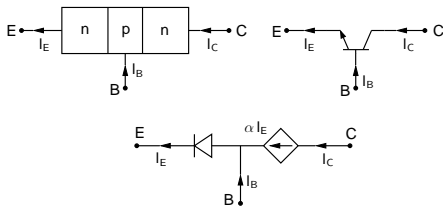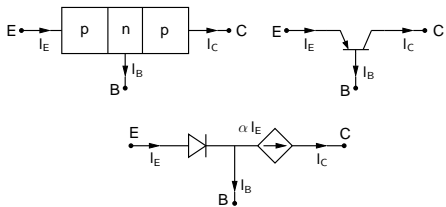

- \* In the active mode,  $I_C = \alpha I_E$ ,  $\alpha \approx 1$  (slightly less than 1).
- \*  $I_B = I_E - I_C = I_E(1 - \alpha)$ .


## BJT in active mode

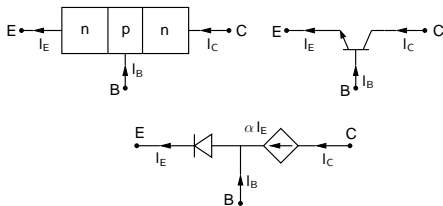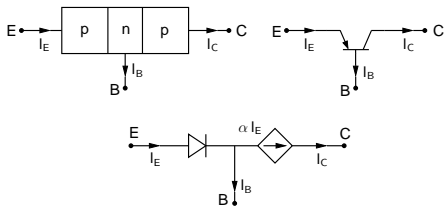

- \* In the active mode,  $I_C = \alpha I_E$ ,  $\alpha \approx 1$  (slightly less than 1).
- \*  $I_B = I_E - I_C = I_E(1 - \alpha)$ .
- \* The ratio  $I_C/I_B$  is defined as the current gain  $\beta$  of the transistor.

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}.$$

## BJT in active mode

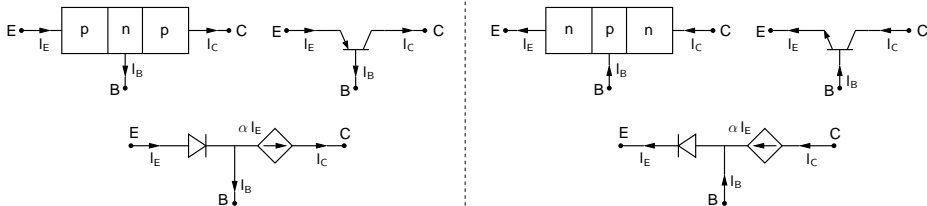



- \* In the active mode,  $I_C = \alpha I_E$ ,  $\alpha \approx 1$  (slightly less than 1).
- \*  $I_B = I_E - I_C = I_E(1 - \alpha)$ .
- \* The ratio  $I_C/I_B$  is defined as the current gain  $\beta$  of the transistor.

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}.$$

- \*  $\beta$  is a function of  $I_C$  and temperature. However, we will generally treat it as a constant, a useful approximation to simplify things and still get a good insight.





# BJT in active mode

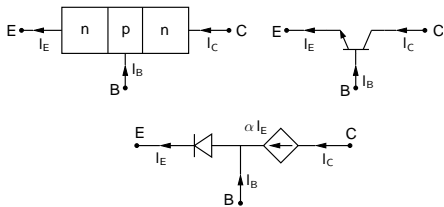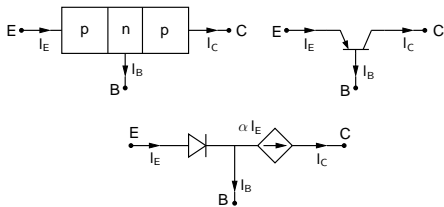

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

$\alpha$	$\beta$
0.9	9
0.95	19
0.99	99
0.995	199

# BJT in active mode

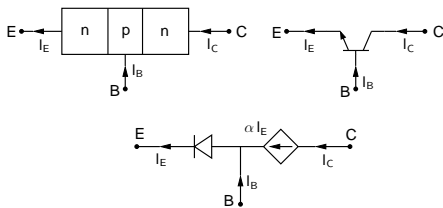
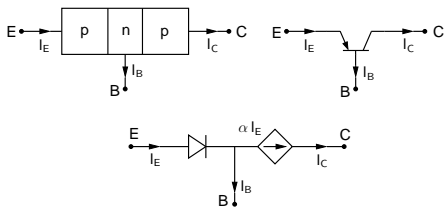


$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

\*  $\beta$  is a sensitive function of  $\alpha$ .

$\alpha$	$\beta$
0.9	9
0.95	19
0.99	99
0.995	199

## BJT in active mode

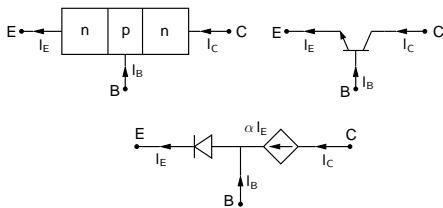
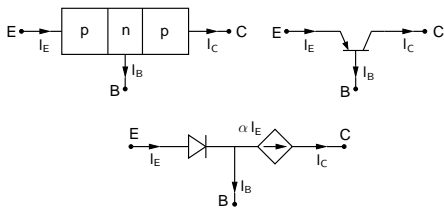


$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

$\alpha$	$\beta$
0.9	9
0.95	19
0.99	99
0.995	199

- \*  $\beta$  is a sensitive function of  $\alpha$ .
- \* Transistors are generally designed to get a high value of  $\beta$  (typically 100 to 250, but can be as high as 2000 for "super- $\beta$ " transistors).

## BJT in active mode

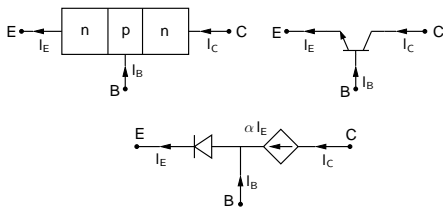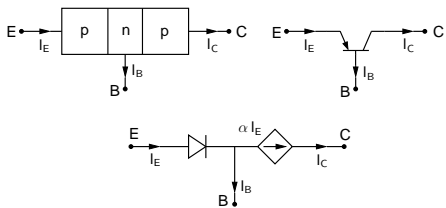


$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$


$\alpha$	$\beta$
0.9	9
0.95	19
0.99	99
0.995	199

- \*  $\beta$  is a sensitive function of  $\alpha$ .
- \* Transistors are generally designed to get a high value of  $\beta$  (typically 100 to 250, but can be as high as 2000 for "super- $\beta$ " transistors).
- \* A large  $\beta \Rightarrow I_B \ll I_C$  or  $I_E$  when the transistor is in the active mode.


# A simple BJT circuit

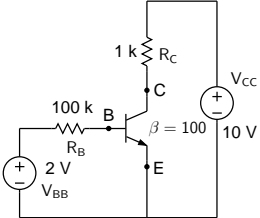


# A simple BJT circuit

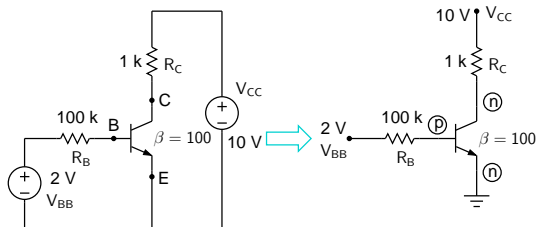

# A simple BJT circuit

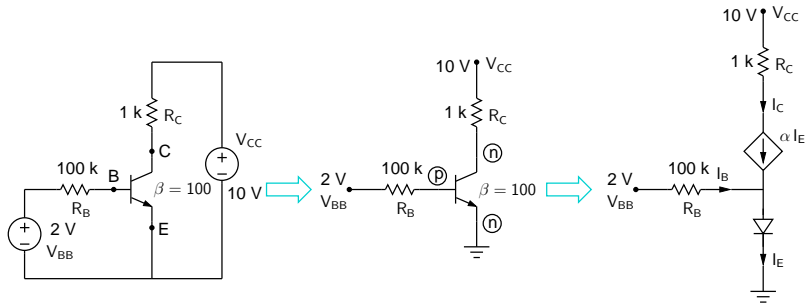


## A simple BJT circuit

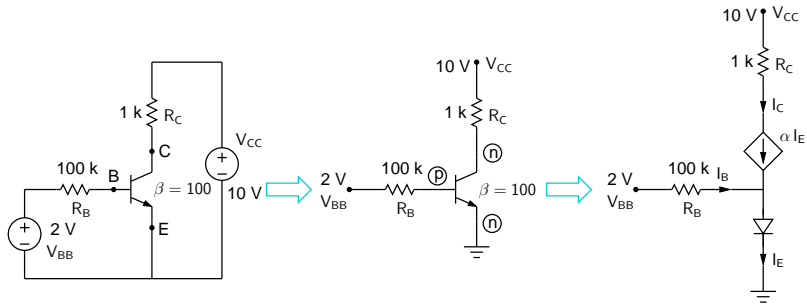

Assume the BJT to be in the active mode  $\Rightarrow V_{BE} = 0.7\text{ V}$  and  $I_C = \alpha I_E = \beta I_B$ .




## A simple BJT circuit

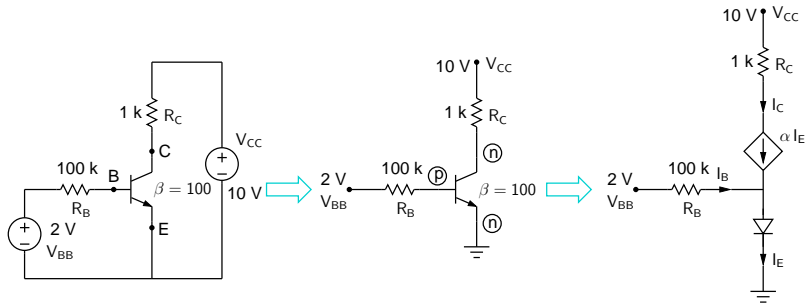

Assume the BJT to be in the active mode  $\Rightarrow V_{BE} = 0.7\text{ V}$  and  $I_C = \alpha I_E = \beta I_B$ .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2\text{ V} - 0.7\text{ V}}{100\text{ k}} = 13\text{ }\mu\text{A}.$$

## A simple BJT circuit

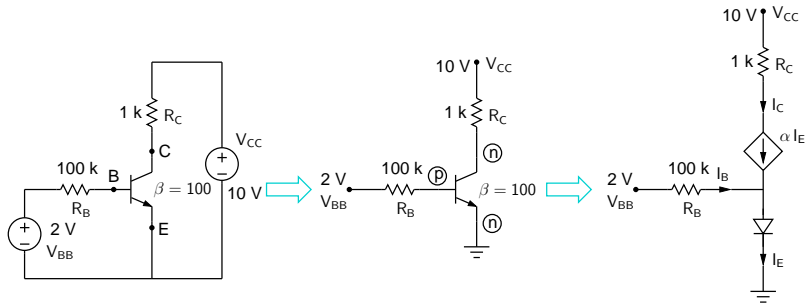


Assume the BJT to be in the active mode  $\Rightarrow V_{BE} = 0.7 \text{ V}$  and  $I_C = \alpha I_E = \beta I_B$ .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2 \text{ V} - 0.7 \text{ V}}{100 \text{ k}} = 13 \mu\text{A}.$$

$$I_C = \beta \times I_B = 100 \times 13 \mu\text{A} = 1.3 \text{ mA}.$$

## A simple BJT circuit

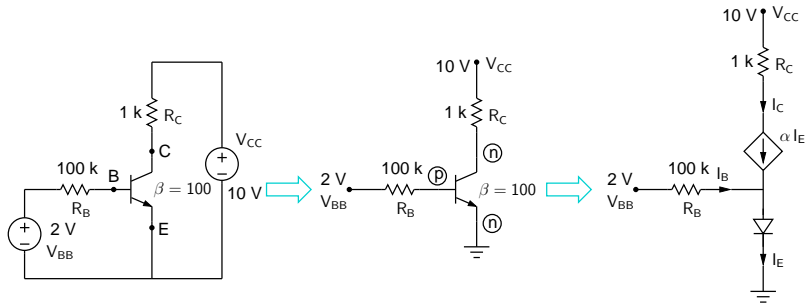


Assume the BJT to be in the active mode  $\Rightarrow V_{BE} = 0.7\text{ V}$  and  $I_C = \alpha I_E = \beta I_B$ .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2\text{ V} - 0.7\text{ V}}{100\text{ k}} = 13\ \mu\text{A}.$$

$$I_C = \beta \times I_B = 100 \times 13\ \mu\text{A} = 1.3\text{ mA}.$$

$$V_C = V_{CC} - I_C R_C = 10\text{ V} - 1.3\text{ mA} \times 1\text{ k} = 8.7\text{ V}.$$

## A simple BJT circuit

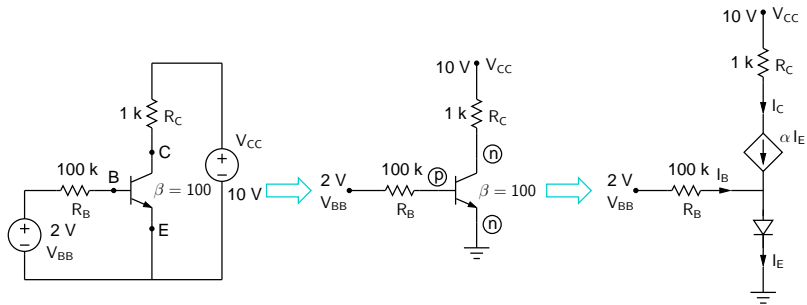

Assume the BJT to be in the active mode  $\Rightarrow V_{BE} = 0.7 \text{ V}$  and  $I_C = \alpha I_E = \beta I_B$ .


$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2 \text{ V} - 0.7 \text{ V}}{100 \text{ k}} = 13 \mu\text{A}.$$

$$I_C = \beta \times I_B = 100 \times 13 \mu\text{A} = 1.3 \text{ mA}.$$

$$V_C = V_{CC} - I_C R_C = 10 \text{ V} - 1.3 \text{ mA} \times 1 \text{ k} = 8.7 \text{ V}.$$

Let us check whether our assumption of active mode is correct. We need to check whether the B-C junction is under reverse bias.

## A simple BJT circuit

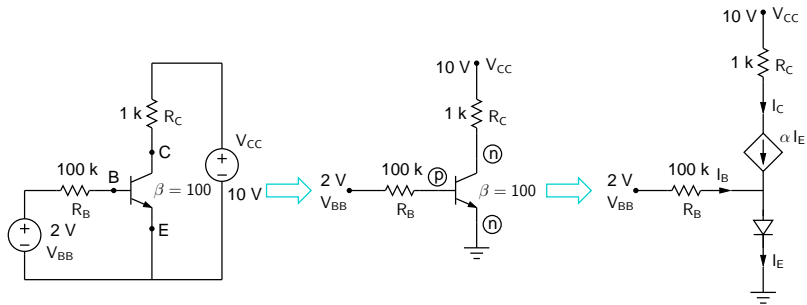

Assume the BJT to be in the active mode  $\Rightarrow V_{BE} = 0.7 \text{ V}$  and  $I_C = \alpha I_E = \beta I_B$ .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2 \text{ V} - 0.7 \text{ V}}{100 \text{ k}} = 13 \mu\text{A}.$$

$$I_C = \beta \times I_B = 100 \times 13 \mu\text{A} = 1.3 \text{ mA}.$$


$$V_C = V_{CC} - I_C R_C = 10 \text{ V} - 1.3 \text{ mA} \times 1 \text{ k} = 8.7 \text{ V}.$$

Let us check whether our assumption of active mode is correct. We need to check whether the B-C junction is under reverse bias.

$$V_{BC} = V_B - V_C = 0.7 \text{ V} - 8.7 \text{ V} = -8.0 \text{ V},$$


i.e., the B-C junction is indeed under reverse bias.

## A simple BJT circuit (continued)

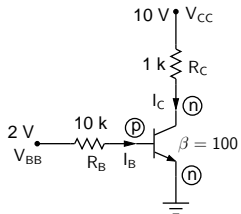

What happens if  $R_B$  is changed from 100 k to 10 k?


## A simple BJT circuit (continued)

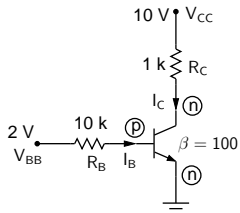

What happens if  $R_B$  is changed from 100 k to 10 k?

Assuming the BJT to be in the active mode again, we have  $V_{BE} \approx 0.7\text{ V}$ , and  $I_C = \beta I_B$ .

## A simple BJT circuit (continued)

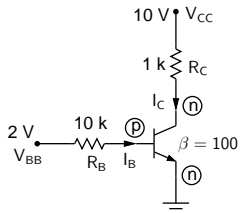

What happens if  $R_B$  is changed from 100 k to 10 k?

Assuming the BJT to be in the active mode again, we have  $V_{BE} \approx 0.7 \text{ V}$ , and

$$I_C = \beta I_B.$$


$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2 \text{ V} - 0.7 \text{ V}}{10 \text{ k}} = 130 \mu\text{A}.$$

$$I_C = \beta \times I_B = 100 \times 130 \mu\text{A} = 13 \text{ mA}.$$

$$V_C = V_{CC} - I_C R_C = 10 \text{ V} - 13 \text{ mA} \times 1 \text{ k} = -3 \text{ V}.$$



## A simple BJT circuit (continued)

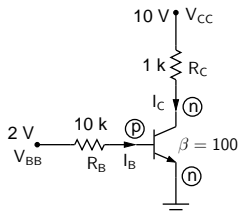

What happens if  $R_B$  is changed from 100 k to 10 k?

Assuming the BJT to be in the active mode again, we have  $V_{BE} \approx 0.7 \text{ V}$ , and

$$I_C = \beta I_B.$$


$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2 \text{ V} - 0.7 \text{ V}}{10 \text{ k}} = 130 \mu\text{A}.$$

$$I_C = \beta \times I_B = 100 \times 130 \mu\text{A} = 13 \text{ mA}.$$

$$V_C = V_{CC} - I_C R_C = 10 \text{ V} - 13 \text{ mA} \times 1 \text{ k} = -3 \text{ V}.$$

$$V_{BC} = V_B - V_C = 0.7 \text{ V} - (-3) \text{ V} = 3.7 \text{ V},$$

## A simple BJT circuit (continued)

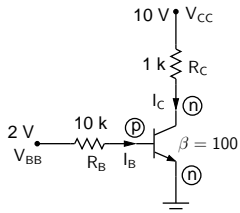

What happens if  $R_B$  is changed from 100 k to 10 k?

Assuming the BJT to be in the active mode again, we have  $V_{BE} \approx 0.7 \text{ V}$ , and  $I_C = \beta I_B$ .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2 \text{ V} - 0.7 \text{ V}}{10 \text{ k}} = 130 \mu\text{A}.$$

$$I_C = \beta \times I_B = 100 \times 130 \mu\text{A} = 13 \text{ mA}.$$

$$V_C = V_{CC} - I_C R_C = 10 \text{ V} - 13 \text{ mA} \times 1 \text{ k} = -3 \text{ V}.$$


$$V_{BC} = V_B - V_C = 0.7 \text{ V} - (-3) \text{ V} = 3.7 \text{ V},$$

$V_{BC}$  is not only positive, it is *huge*!

The BJT cannot be in the active mode, and we need to take another look at the circuit.

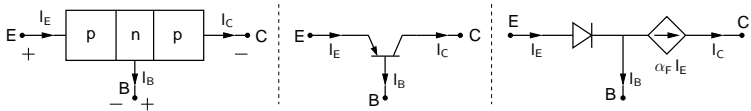
# Ebers-Moll model for a *pnp* transistor

Active mode ("forward" active mode): B-E in f. b., B-C in r. b.



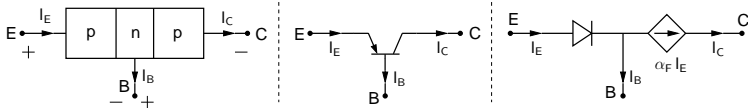
# Ebers-Moll model for a *pnp* transistor

Active mode ("forward" active mode): B-E in f. b., B-C in r. b.




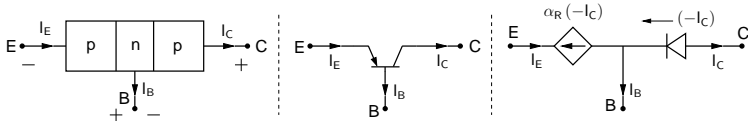Reverse active mode: B-E in r. b., B-C in f. b.



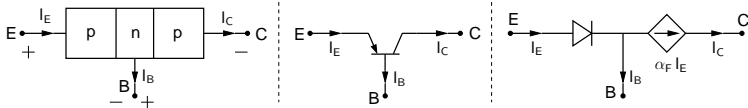
# Ebers-Moll model for a *pnp* transistor

Active mode ("forward" active mode): B-E in f. b., B-C in r. b.



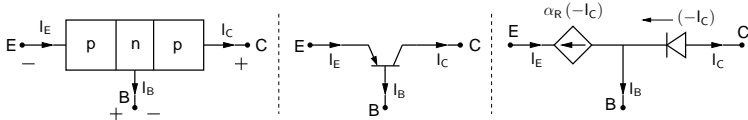
Reverse active mode: B-E in r. b., B-C in f. b.




In the reverse active mode, emitter  $\leftrightarrow$  collector. (However, we continue to refer to the terminals with their original names.)
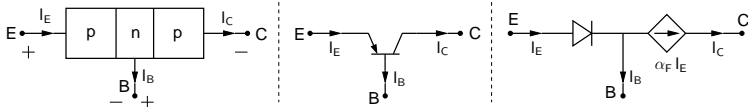
# Ebers-Moll model for a *pnp* transistor

Active mode ("forward" active mode): B-E in f. b., B-C in r. b.



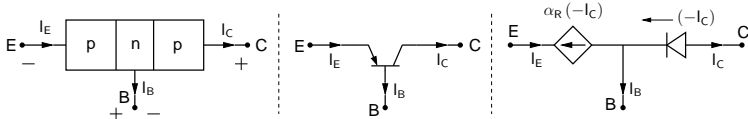Reverse active mode: B-E in r. b., B-C in f. b.




In the reverse active mode, emitter  $\leftrightarrow$  collector. (However, we continue to refer to the terminals with their original names.)


The two  $\alpha$ 's,  $\alpha_F$  ("forward"  $\alpha$ ) and  $\alpha_R$  ("reverse"  $\alpha$ ) are generally quite different.
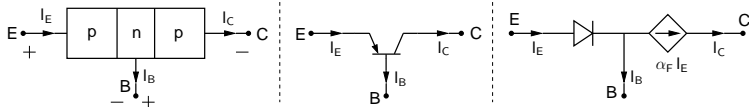
# Ebers-Moll model for a *pnp* transistor

Active mode ("forward" active mode): B-E in f. b., B-C in r. b.



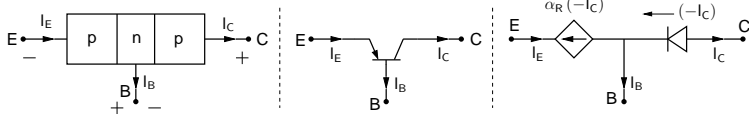Reverse active mode: B-E in r. b., B-C in f. b.




In the reverse active mode, emitter  $\leftrightarrow$  collector. (However, we continue to refer to the terminals with their original names.)

The two  $\alpha$ 's,  $\alpha_F$  ("forward"  $\alpha$ ) and  $\alpha_R$  ("reverse"  $\alpha$ ) are generally quite different.


Typically,  $\alpha_F > 0.98$ , and  $\alpha_R$  is in the range from 0.02 to 0.5.
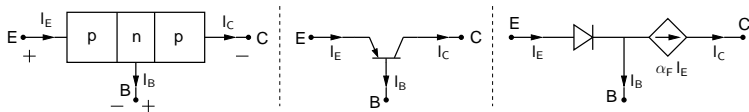
# Ebers-Moll model for a *pnp* transistor

Active mode ("forward" active mode): B-E in f. b., B-C in r. b.



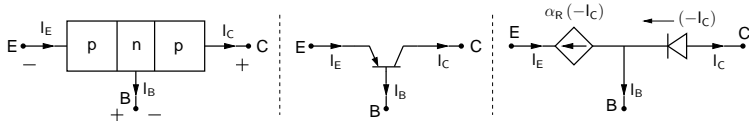Reverse active mode: B-E in r. b., B-C in f. b.



In the reverse active mode, emitter  $\leftrightarrow$  collector. (However, we continue to refer to the terminals with their original names.)

The two  $\alpha$ 's,  $\alpha_F$  ("forward"  $\alpha$ ) and  $\alpha_R$  ("reverse"  $\alpha$ ) are generally quite different.


Typically,  $\alpha_F > 0.98$ , and  $\alpha_R$  is in the range from 0.02 to 0.5.

The corresponding current gains ( $\beta_F$  and  $\beta_R$ ) differ significantly, since  $\beta = \alpha / (1 - \alpha)$ .



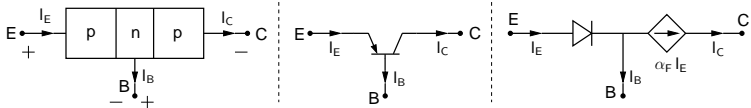
# Ebers-Moll model for a *pnp* transistor

Active mode ("forward" active mode): B-E in f. b., B-C in r. b.



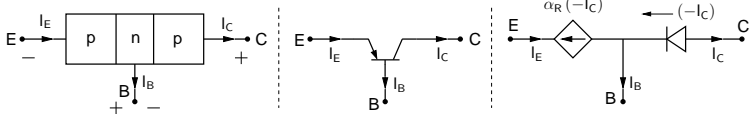Reverse active mode: B-E in r. b., B-C in f. b.



In the reverse active mode, emitter  $\leftrightarrow$  collector. (However, we continue to refer to the terminals with their original names.)

The two  $\alpha$ 's,  $\alpha_F$  ("forward"  $\alpha$ ) and  $\alpha_R$  ("reverse"  $\alpha$ ) are generally quite different.


Typically,  $\alpha_F > 0.98$ , and  $\alpha_R$  is in the range from 0.02 to 0.5.

The corresponding current gains ( $\beta_F$  and  $\beta_R$ ) differ significantly, since  $\beta = \alpha / (1 - \alpha)$ .

In amplifiers, the BJT is biased in the forward active mode (simply called the "active mode") in order to make use of the higher value of  $\beta$  in that mode.

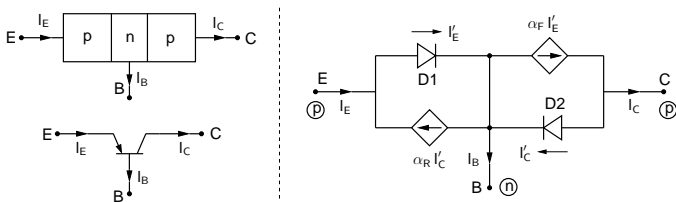
# Ebers-Moll model for a *pnp* transistor

The Ebers-Moll model combines the forward and reverse operations of a BJT in a single comprehensive model.


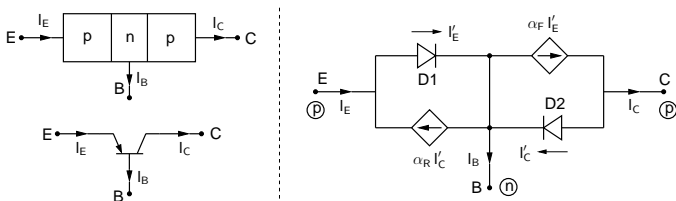
# Ebers-Moll model for a *pnp* transistor

The Ebers-Moll model combines the forward and reverse operations of a BJT in a single comprehensive model.




The currents  $I'_E$  and  $I'_C$  are given by the Shockley diode equation:

$$I'_E = I_{ES} \left[ \exp \left( \frac{V_{EB}}{V_T} \right) - 1 \right], \quad I'_C = I_{CS} \left[ \exp \left( \frac{V_{CB}}{V_T} \right) - 1 \right].$$
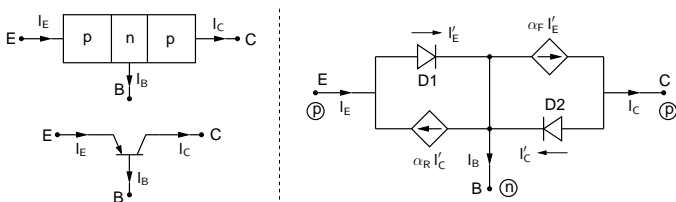
# Ebers-Moll model for a *pnp* transistor

The Ebers-Moll model combines the forward and reverse operations of a BJT in a single comprehensive model.




The currents  $I'_E$  and  $I'_C$  are given by the Shockley diode equation:


$$I'_E = I_{ES} \left[ \exp\left(\frac{V_{EB}}{V_T}\right) - 1 \right], \quad I'_C = I_{CS} \left[ \exp\left(\frac{V_{CB}}{V_T}\right) - 1 \right].$$

Mode	B-E	B-C	
Forward active	forward	reverse	$I'_E \gg I'_C$
Reverse active	reverse	forward	$I'_C \gg I'_E$
Saturation	forward	forward	$I'_E$ and $I'_C$ are comparable.
Cut-off	reverse	reverse	$I'_E$ and $I'_C$ are negligblbe.

# Ebers-Moll model

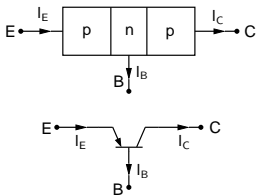


pnp transistor

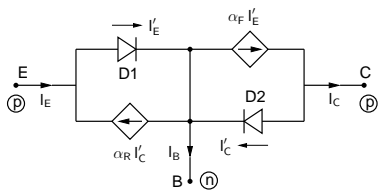


$$I'_E = I_{ES} [\exp(V_{EB}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{CB}/V_T) - 1]$$

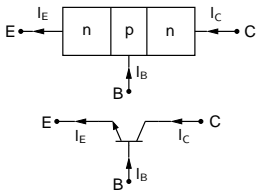


npn transistor

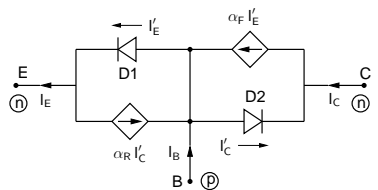


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

# Ebers-Moll model

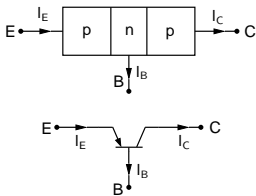


pnp transistor

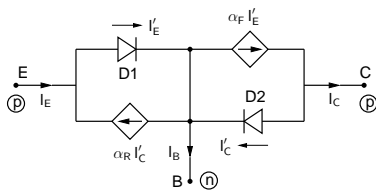


$$I'_E = I_{ES} [\exp(V_{EB}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{CB}/V_T) - 1]$$

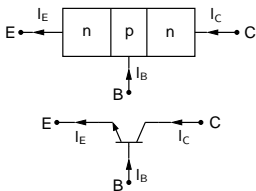

npn transistor


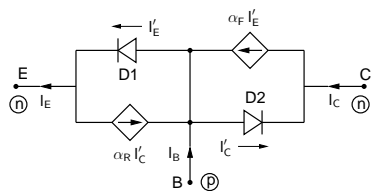


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

For an *n*pn transistor, the same model holds with current directions and voltage polarities suitably changed.

## $I_C$ - $V_{CE}$ characteristics

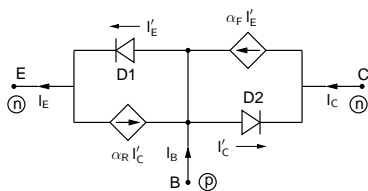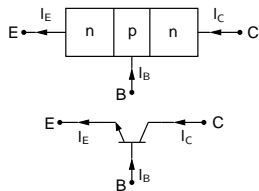

$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$



$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

A BJT is a three-terminal device, and its  $I$ - $V$  characteristics can therefore be represented in several different ways. The  $I_C$  versus  $V_{CE}$  characteristics are very useful in amplifiers.

## $I_C$ - $V_{CE}$ characteristics

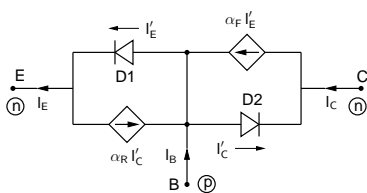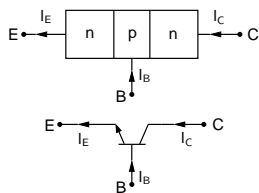

$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$



$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

A BJT is a three-terminal device, and its  $I$ - $V$  characteristics can therefore be represented in several different ways. The  $I_C$  versus  $V_{CE}$  characteristics are very useful in amplifiers.

To start with, we consider a single point,  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .



## $I_C$ - $V_{CE}$ characteristics

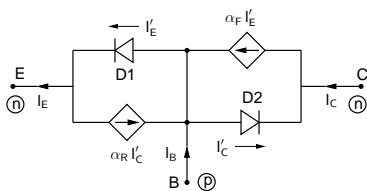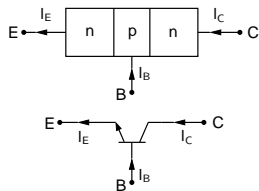

$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$



A BJT is a three-terminal device, and its  $I$ - $V$  characteristics can therefore be represented in several different ways. The  $I_C$  versus  $V_{CE}$  characteristics are very useful in amplifiers.

To start with, we consider a single point,  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .

There are several ways to assign  $V_{BE}$  and  $V_{CB}$  so that they satisfy the constraint:

$$V_{CB} + V_{BE} = (V_C - V_B) + (V_B - V_E) = V_{CE} = 5 \text{ V}.$$

## $I_C$ - $V_{CE}$ characteristics

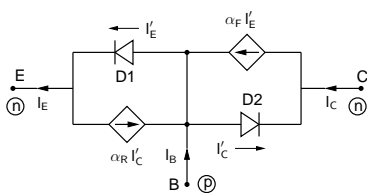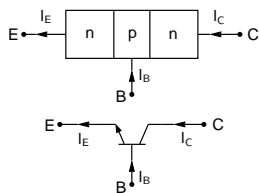

$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

A BJT is a three-terminal device, and its  $I$ - $V$  characteristics can therefore be represented in several different ways. The  $I_C$  versus  $V_{CE}$  characteristics are very useful in amplifiers.



To start with, we consider a single point,  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .

There are several ways to assign  $V_{BE}$  and  $V_{CB}$  so that they satisfy the constraint:

$$V_{CB} + V_{BE} = (V_C - V_B) + (V_B - V_E) = V_{CE} = 5 \text{ V}.$$

Let us consider some of these possibilities.

## $I_C$ - $V_{CE}$ characteristics

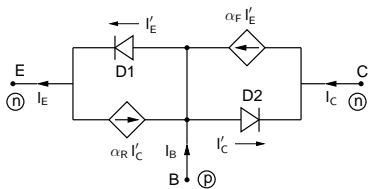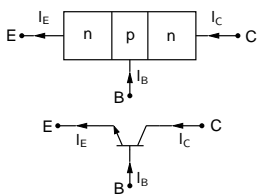

$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$



$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .

# $I_C$ - $V_{CE}$ characteristics

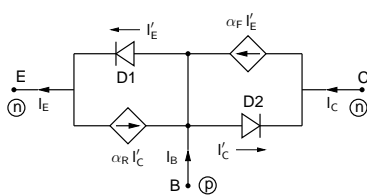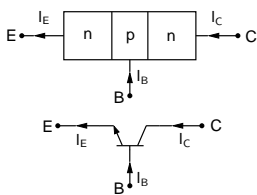


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$



$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

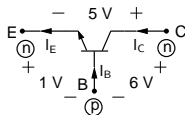Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .



# $I_C$ - $V_{CE}$ characteristics

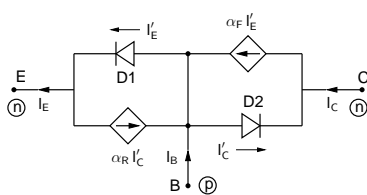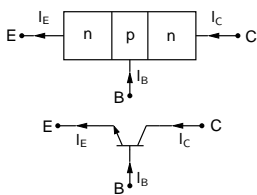


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$



$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

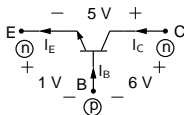Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .



D1 and D2 are both off, and we cannot satisfy the condition,  $I_B = 10 \mu\text{A}$ , since all currents are much smaller than  $10 \mu\text{A}$ .

# $I_C$ - $V_{CE}$ characteristics

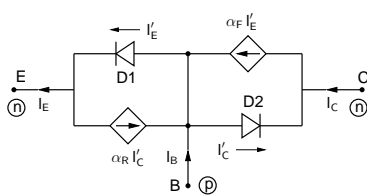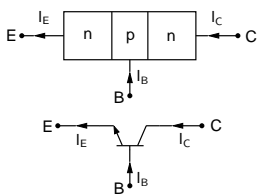


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$


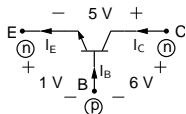
Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .



D1 and D2 are both off, and we cannot satisfy the condition,  $I_B = 10 \mu\text{A}$ , since all currents are much smaller than  $10 \mu\text{A}$ .

$\Rightarrow$  This possibility (and similarly others with both junctions reverse biased) is ruled out.

# $I_C$ - $V_{CE}$ characteristics

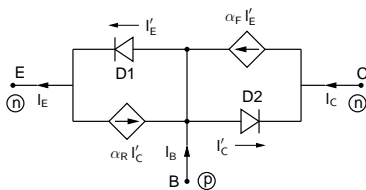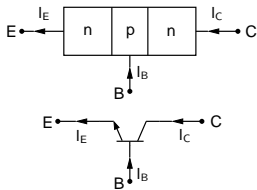

$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$



$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .

# $I_C$ - $V_{CE}$ characteristics

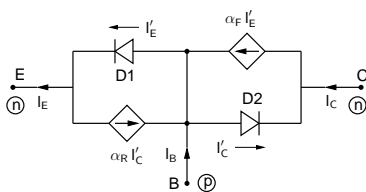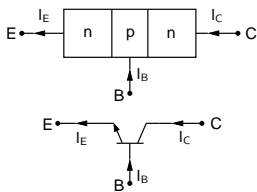


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$



$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

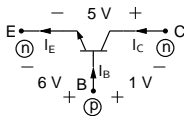Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .





# $I_C$ - $V_{CE}$ characteristics

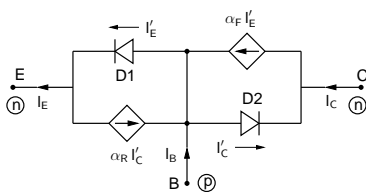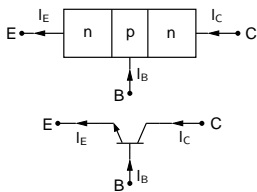


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$



$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

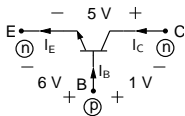Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .



D1 and D2 are both conducting; however, the forward bias for the B-E junction is impossibly large.

# $I_C$ - $V_{CE}$ characteristics

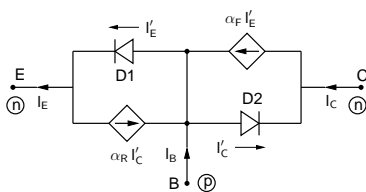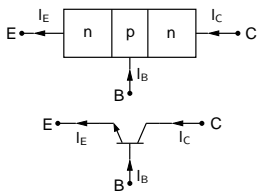


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$


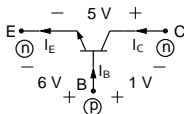
Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .



D1 and D2 are both conducting; however, the forward bias for the B-E junction is impossibly large.

⇒ This possibility is also ruled out.

# $I_C$ - $V_{CE}$ characteristics

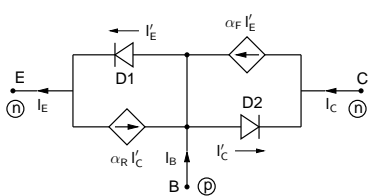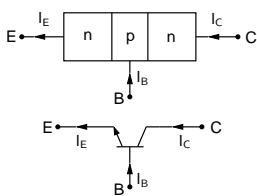

$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$



$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .

# $I_C$ - $V_{CE}$ characteristics

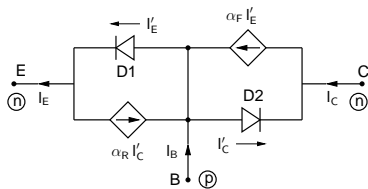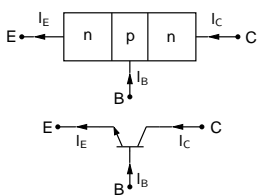


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$



$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$

$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

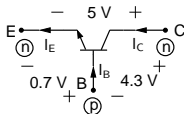Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .



# $I_C$ - $V_{CE}$ characteristics

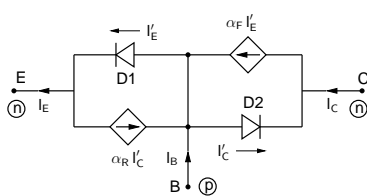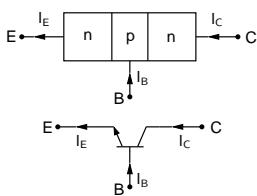


$$I'_E = I_{ES} [\exp(V_{BE}/V_T) - 1]$$

$$I'_C = I_{CS} [\exp(V_{BC}/V_T) - 1]$$

$$\alpha_F = 0.99, \quad I_{SE} = 1 \times 10^{-14} \text{ A}$$


$$\alpha_R = 0.50, \quad I_{SC} = 2 \times 10^{-14} \text{ A}$$

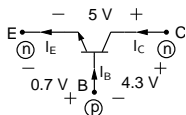Constraints:  $I_B = 10 \mu\text{A}$ ,  $V_{CE} = 5 \text{ V}$ .



D1 is on, D2 is off. This is a realistic possibility. Since the B-C junction is under reverse bias,  $I'_C$  and  $\alpha_R I'_C$  are much smaller than  $I'_E$ , and therefore the lower branches in the Ebers-Moll model can be dropped (see next slide).

## $I_C$ - $V_{CE}$ characteristics

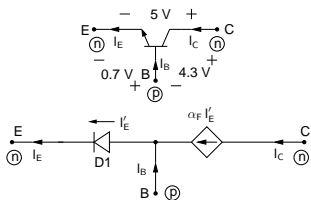


(The actual values for  $V_{BE}$  and  $V_{CB}$  obtained by solving the Ebers-Moll equations are  $V_{BE} = 0.656$  V and  $V_{CB} = 4.344$  V.)

The BJT is in the active mode, and therefore

$$I_C = \beta I_B = \frac{\alpha_F}{1 - \alpha_F} I_B = 99 \times 10 \mu\text{A} = 0.99 \text{ mA}.$$

## $I_C$ - $V_{CE}$ characteristics

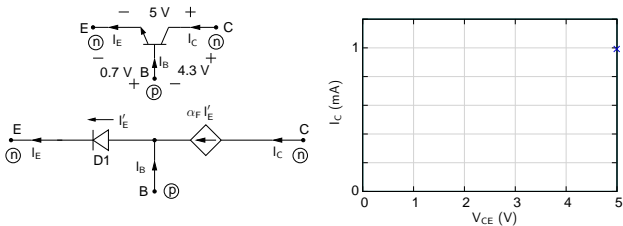


(The actual values for  $V_{BE}$  and  $V_{CB}$  obtained by solving the Ebers-Moll equations are  $V_{BE} = 0.656$  V and  $V_{CB} = 4.344$  V.)

The BJT is in the active mode, and therefore

$$I_C = \beta I_B = \frac{\alpha_F}{1 - \alpha_F} I_B = 99 \times 10 \mu A = 0.99 \text{ mA}.$$

## $I_C$ - $V_{CE}$ characteristics

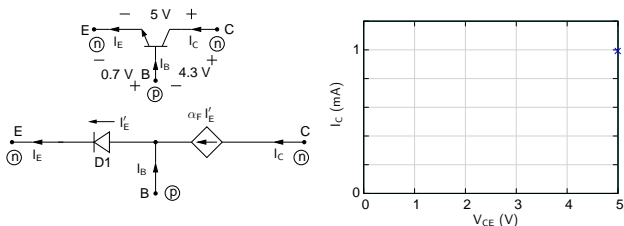

(The actual values for  $V_{BE}$  and  $V_{CB}$  obtained by solving the Ebers-Moll equations are  $V_{BE} = 0.656$  V and  $V_{CB} = 4.344$  V.)


The BJT is in the active mode, and therefore

$$I_C = \beta I_B = \frac{\alpha_F}{1 - \alpha_F} I_B = 99 \times 10 \mu\text{A} = 0.99 \text{ mA}.$$

If  $V_{CE}$  is reduced to, say, 4 V, and  $I_B$  kept at  $10 \mu\text{A}$ , our previous argument holds, and once again, we find that  $I_C = \beta I_B = 0.99$  mA.



## $I_C$ - $V_{CE}$ characteristics

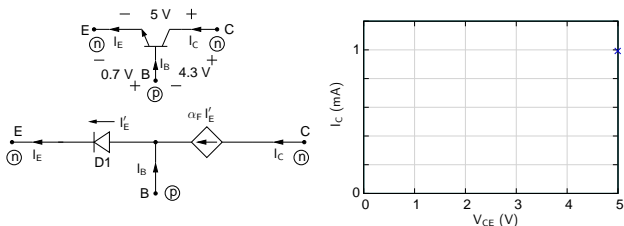

(The actual values for  $V_{BE}$  and  $V_{CB}$  obtained by solving the Ebers-Moll equations are  $V_{BE} = 0.656$  V and  $V_{CB} = 4.344$  V.)


The BJT is in the active mode, and therefore

$$I_C = \beta I_B = \frac{\alpha_F}{1 - \alpha_F} I_B = 99 \times 10 \mu A = 0.99 \text{ mA}.$$

If  $V_{CE}$  is reduced to, say, 4 V, and  $I_B$  kept at  $10 \mu A$ , our previous argument holds, and once again, we find that  $I_C = \beta I_B = 0.99$  mA.

Thus, the plot of  $I_C$  versus  $V_{CE}$  is simply a horizontal line.

## $I_C$ - $V_{CE}$ characteristics

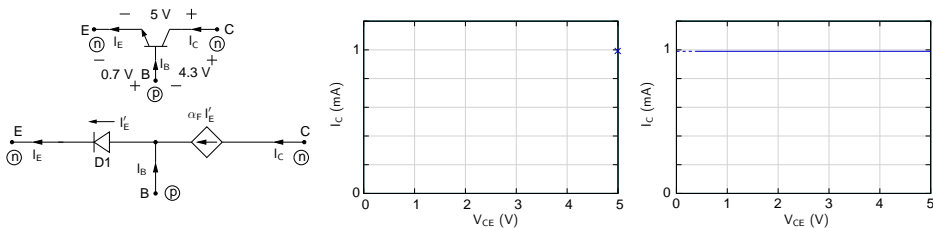

(The actual values for  $V_{BE}$  and  $V_{CB}$  obtained by solving the Ebers-Moll equations are  $V_{BE} = 0.656$  V and  $V_{CB} = 4.344$  V.)




The BJT is in the active mode, and therefore

$$I_C = \beta I_B = \frac{\alpha_F}{1 - \alpha_F} I_B = 99 \times 10 \mu A = 0.99 \text{ mA.}$$

If  $V_{CE}$  is reduced to, say, 4 V, and  $I_B$  kept at  $10 \mu A$ , our previous argument holds, and once again, we find that  $I_C = \beta I_B = 0.99$  mA.

Thus, the plot of  $I_C$  versus  $V_{CE}$  is simply a horizontal line.

## $I_C$ - $V_{CE}$ characteristics

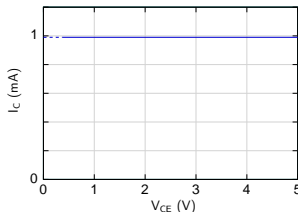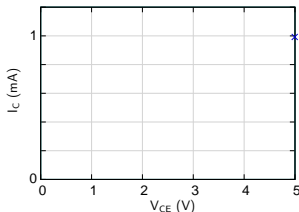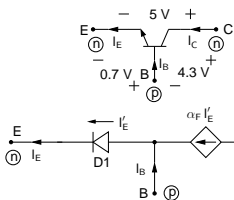

(The actual values for  $V_{BE}$  and  $V_{CB}$  obtained by solving the Ebers-Moll equations are  $V_{BE} = 0.656$  V and  $V_{CB} = 4.344$  V.)

The BJT is in the active mode, and therefore


$$I_C = \beta I_B = \frac{\alpha_F}{1 - \alpha_F} I_B = 99 \times 10 \mu A = 0.99 \text{ mA}.$$

If  $V_{CE}$  is reduced to, say, 4 V, and  $I_B$  kept at  $10 \mu A$ , our previous argument holds, and once again, we find that  $I_C = \beta I_B = 0.99$  mA.

Thus, the plot of  $I_C$  versus  $V_{CE}$  is simply a horizontal line.


However, as  $V_{CE} \rightarrow 0$  V, things change (see next slide).

## $I_C$ - $V_{CE}$ characteristics

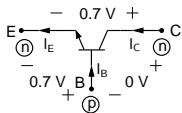

When  $V_{CE} \approx 0.7 \text{ V}$  (and  $I_B$  kept at  $10 \mu\text{A}$ ), the B-C drop is about  $0 \text{ V}$ .

## $I_C$ - $V_{CE}$ characteristics

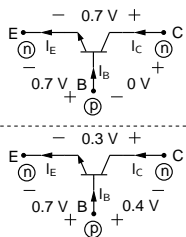


When  $V_{CE} \approx 0.7 \text{ V}$  (and  $I_B$  kept at  $10 \mu\text{A}$ ), the B-C drop is about  $0 \text{ V}$ .

As  $V_{CE}$  is reduced further, the B-C junction gets forward biased. For example, with  $V_{CE} = 0.3 \text{ V}$ , we may have a voltage distribution shown in the figure.

(The numbers are only representative; the actual  $V_{BE}$  and  $V_{BC}$  values can be obtained by solving the E-M equations.)

## $I_C$ - $V_{CE}$ characteristics

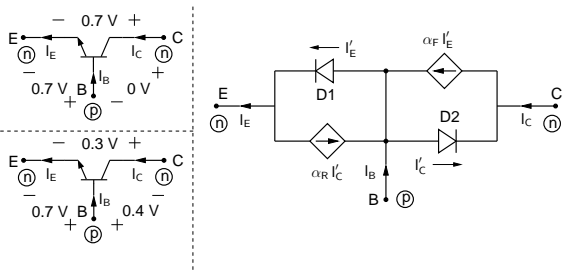





When  $V_{CE} \approx 0.7\text{ V}$  (and  $I_B$  kept at  $10\ \mu\text{A}$ ), the B-C drop is about  $0\text{ V}$ .

As  $V_{CE}$  is reduced further, the B-C junction gets forward biased. For example, with  $V_{CE} = 0.3\text{ V}$ , we may have a voltage distribution shown in the figure.

(The numbers are only representative; the actual  $V_{BE}$  and  $V_{BC}$  values can be obtained by solving the E-M equations.)

Now, the component  $I'_C$  in the E-M model becomes significant,  $I_C = \alpha_F I'_E - I'_C$  reduces, and  $I_C$  becomes smaller than  $\beta I_B$ .

# $I_C$ - $V_{CE}$ characteristics

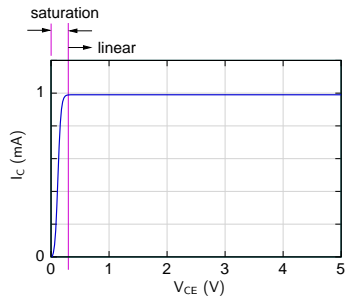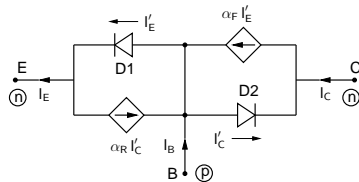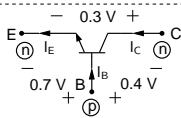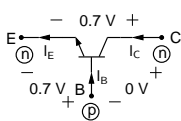

When  $V_{CE} \approx 0.7 \text{ V}$  (and  $I_B$  kept at  $10 \mu\text{A}$ ), the B-C drop is about  $0 \text{ V}$ .


As  $V_{CE}$  is reduced further, the B-C junction gets forward biased. For example, with  $V_{CE} = 0.3 \text{ V}$ , we may have a voltage distribution shown in the figure.

(The numbers are only representative; the actual  $V_{BE}$  and  $V_{BC}$  values can be obtained by solving the E-M equations.)

Now, the component  $I'_C$  in the E-M model becomes significant,  $I_C = \alpha_F I'_E - I'_C$  reduces, and  $I_C$  becomes smaller than  $\beta I_B$ .

The region where  $I_C < \beta I_B$  is called the "saturation region."


## $I_C$ - $V_{CE}$ characteristics

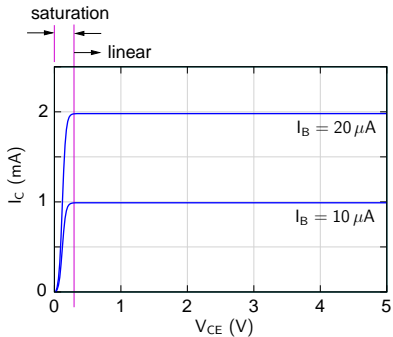

If  $I_B$  is doubled (from  $10 \mu\text{A}$  to  $20 \mu\text{A}$ ),  $I_C = \beta I_B$  changes by a factor of 2 in the linear region. Apart from that, there is no qualitative change in the  $I_C - V_{CE}$  plot.





## $I_C - V_{CE}$ characteristics

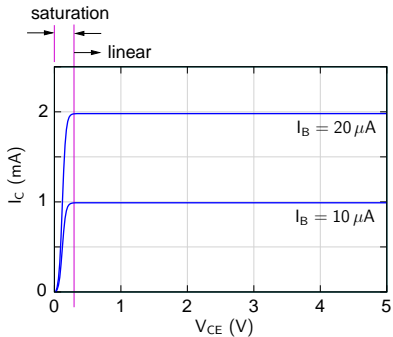

If  $I_B$  is doubled (from  $10 \mu\text{A}$  to  $20 \mu\text{A}$ ),  $I_C = \beta I_B$  changes by a factor of 2 in the linear region. Apart from that, there is no qualitative change in the  $I_C - V_{CE}$  plot.

Clearly, the  $I_C - V_{CE}$  behaviour of a BJT is not represented by a single curve but by a *family of curves*, known as the " $I_C - V_{CE}$  characteristics."



## $I_C - V_{CE}$ characteristics

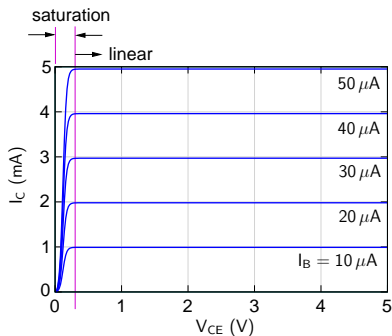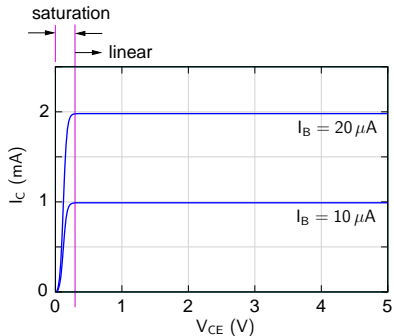

If  $I_B$  is doubled (from  $10 \mu A$  to  $20 \mu A$ ),  $I_C = \beta I_B$  changes by a factor of 2 in the linear region. Apart from that, there is no qualitative change in the  $I_C - V_{CE}$  plot.

Clearly, the  $I_C - V_{CE}$  behaviour of a BJT is not represented by a single curve but by a family of curves, known as the " $I_C - V_{CE}$  characteristics."

## $I_C - V_{CE}$ characteristics

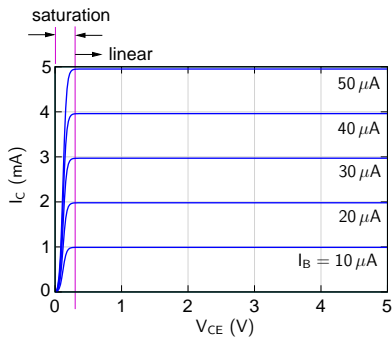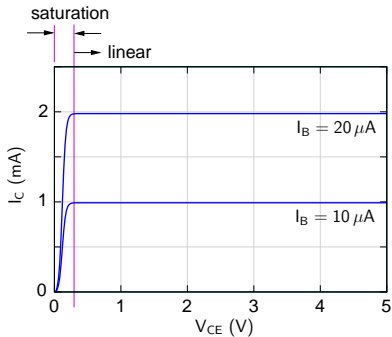


If  $I_B$  is doubled (from  $10 \mu\text{A}$  to  $20 \mu\text{A}$ ),  $I_C = \beta I_B$  changes by a factor of 2 in the linear region. Apart from that, there is no qualitative change in the  $I_C - V_{CE}$  plot.

Clearly, the  $I_C - V_{CE}$  behaviour of a BJT is not represented by a single curve but by a family of curves, known as the " $I_C - V_{CE}$  characteristics."


The  $I_E - V_{CB}$  and  $I_C - V_{BE}$  characteristics of a BJT are also useful in understanding BJT circuits.

## A simple BJT circuit (revisited)

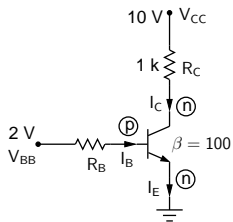

We are now in a position to explain what happens when  $R_B$  is decreased from 100 k to 10 k in the above circuit.


## A simple BJT circuit (revisited)

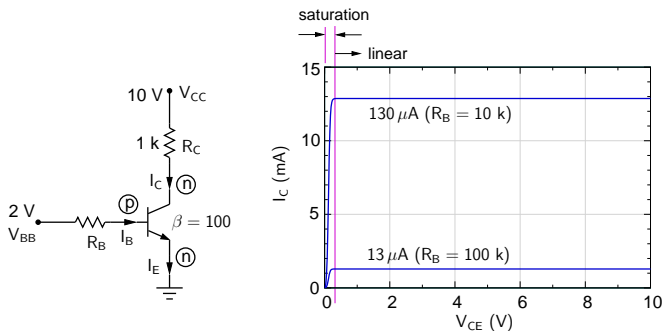

We are now in a position to explain what happens when  $R_B$  is decreased from 100 k to 10 k in the above circuit.

Let us plot  $I_C - V_{CE}$  curves for  $I_B \approx \frac{V_{BB} - 0.7 \text{ V}}{R_B}$  for the two values of  $R_B$ .

## A simple BJT circuit (revisited)

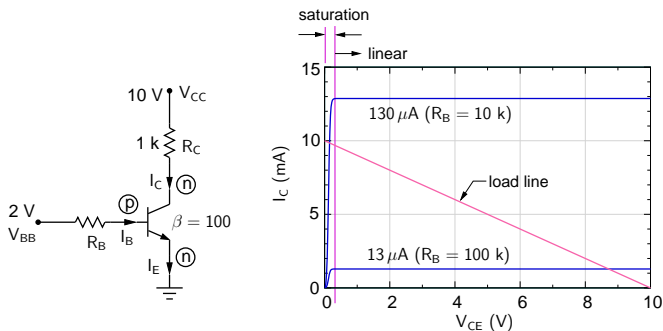


We are now in a position to explain what happens when  $R_B$  is decreased from 100 k to 10 k in the above circuit.

Let us plot  $I_C - V_{CE}$  curves for  $I_B \approx \frac{V_{BB} - 0.7 \text{ V}}{R_B}$  for the two values of  $R_B$ .

In addition to the BJT  $I_C - V_{CE}$  curve, the circuit variables must also satisfy the constraint,  $V_{CC} = V_{CE} + I_C R_C$ , a straight line in the  $I_C - V_{CE}$  plane.

## A simple BJT circuit (revisited)

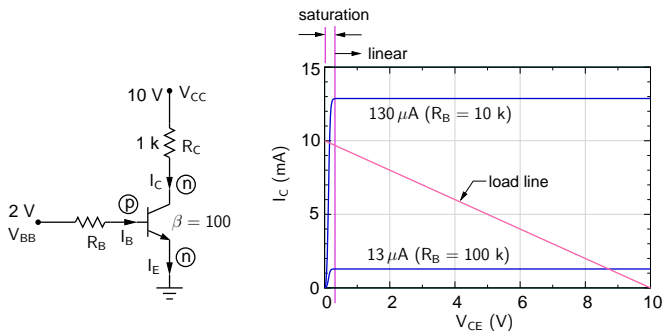

We are now in a position to explain what happens when  $R_B$  is decreased from 100 k to 10 k in the above circuit.

Let us plot  $I_C - V_{CE}$  curves for  $I_B \approx \frac{V_{BB} - 0.7 \text{ V}}{R_B}$  for the two values of  $R_B$ .

In addition to the BJT  $I_C - V_{CE}$  curve, the circuit variables must also satisfy the constraint,  $V_{CC} = V_{CE} + I_C R_C$ , a straight line in the  $I_C - V_{CE}$  plane.

The intersection of the load line and the BJT characteristics gives the solution for the circuit. For  $R_B = 10 \text{ k}$ , note that the BJT operates in the saturation region, leading to  $V_{CE} \approx 0.2 \text{ V}$ , and  $I_C = 9.8 \text{ mA}$ .