

EE101: Op Amp circuits (Part 6)




M. B. Patil

mbpatil@ee.iitb.ac.in

www.ee.iitb.ac.in/~sequel


Department of Electrical Engineering
Indian Institute of Technology Bombay

Sinusoidal oscillators

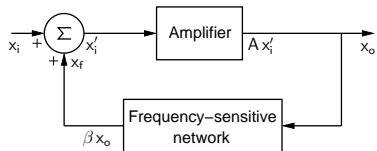

Consider an amplifier with feedback.


Sinusoidal oscillators

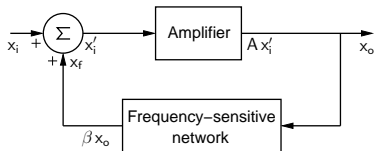

Consider an amplifier with feedback.

$$x_o = Ax_i' = A(x_i + x_f) = A(x_i + \beta x_o)$$


Sinusoidal oscillators

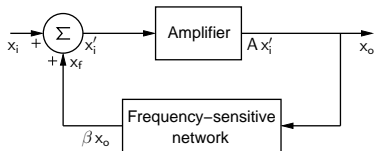

Consider an amplifier with feedback.

$$x_o = Ax'_i = A(x_i + x_f) = A(x_i + \beta x_o)$$
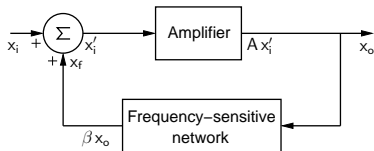
$$\rightarrow A_f \equiv \frac{x_o}{x_i} = \frac{A}{1 - A\beta}$$



Consider an amplifier with feedback.


$$x_o = Ax'_i = A(x_i + x_f) = A(x_i + \beta x_o)$$

$$\rightarrow A_f \equiv \frac{x_o}{x_i} = \frac{A}{1 - A\beta}$$

Since A and β will generally vary with ω , we re-write A_f as,

$$\rightarrow A_f(j\omega) = \frac{A(j\omega)}{1 - A(j\omega)\beta(j\omega)}$$

Sinusoidal oscillators

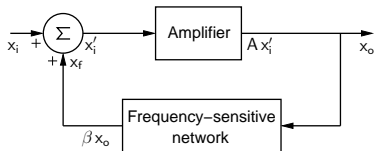

Consider an amplifier with feedback.

$$x_o = Ax'_i = A(x_i + x_f) = A(x_i + \beta x_o)$$


$$\rightarrow A_f \equiv \frac{x_o}{x_i} = \frac{A}{1 - A\beta}$$

Since A and β will generally vary with ω , we re-write A_f as,

$$\rightarrow A_f(j\omega) = \frac{A(j\omega)}{1 - A(j\omega)\beta(j\omega)}$$

As $A(j\omega)\beta(j\omega) \rightarrow 1$, $A_f(j\omega) \rightarrow \infty$, and we get a finite x_o even if $x_i = 0$.

Sinusoidal oscillators

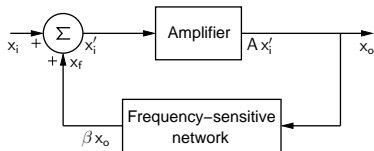

Consider an amplifier with feedback.

$$x_o = Ax'_i = A(x_i + x_f) = A(x_i + \beta x_o)$$

$$\rightarrow A_f \equiv \frac{x_o}{x_i} = \frac{A}{1 - A\beta}$$


Since A and β will generally vary with ω , we re-write A_f as,

$$\rightarrow A_f(j\omega) = \frac{A(j\omega)}{1 - A(j\omega)\beta(j\omega)}$$


As $A(j\omega)\beta(j\omega) \rightarrow 1$, $A_f(j\omega) \rightarrow \infty$, and we get a finite x_o even if $x_i = 0$.

In other words, we can remove x_i and still get a non-zero x_o . This is the basic principle behind sinusoidal oscillators.

Sinusoidal oscillators

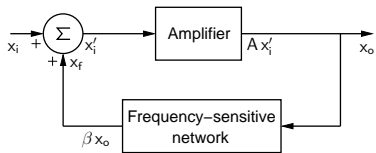


Sinusoidal oscillators

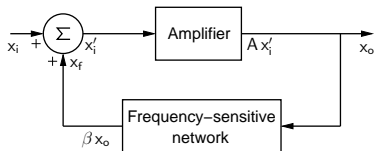


- * The condition, $A(j\omega)\beta(j\omega) = 1$, for a circuit to oscillate spontaneously (i.e., without any input), is known as the Barkhausen criterion.

Sinusoidal oscillators

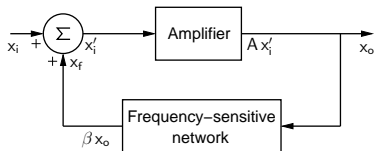


- * The condition, $A(j\omega)\beta(j\omega) = 1$, for a circuit to oscillate spontaneously (i.e., without any input), is known as the Barkhausen criterion.
- * For the circuit to oscillate at $\omega = \omega_0$, the β network is designed such that the Barkhausen criterion is satisfied only for ω_0 , i.e., all components except ω_0 get attenuated to zero.

Sinusoidal oscillators

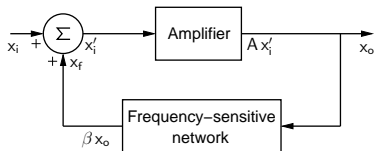


- * The condition, $A(j\omega)\beta(j\omega) = 1$, for a circuit to oscillate spontaneously (i.e., without any input), is known as the Barkhausen criterion.
- * For the circuit to oscillate at $\omega = \omega_0$, the β network is designed such that the Barkhausen criterion is satisfied only for ω_0 , i.e., all components except ω_0 get attenuated to zero.
- * The output x_o will therefore have a frequency ω_0 ($\omega_0/2\pi$ in Hz), but what about the amplitude?


Sinusoidal oscillators

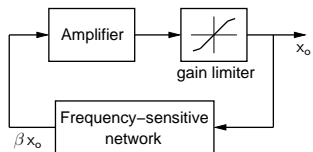


Sinusoidal oscillators

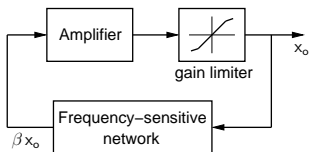

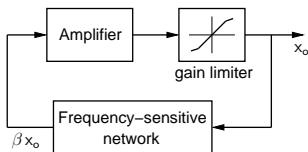- * A gain limiting mechanism is required to limit the amplitude of the oscillations.




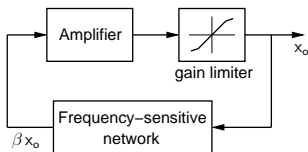- * A gain limiting mechanism is required to limit the amplitude of the oscillations.
- * Amplifier clipping can provide a gain limiter mechanism. For example, in an Op Amp, the output voltage is limited to $\pm V_{\text{sat}}$, and this serves to limit the gain as the magnitude of the output voltage increases.




- * A gain limiting mechanism is required to limit the amplitude of the oscillations.
- * Amplifier clipping can provide a gain limiter mechanism. For example, in an Op Amp, the output voltage is limited to $\pm V_{\text{sat}}$, and this serves to limit the gain as the magnitude of the output voltage increases.
- * For a more controlled output with low distortion, diode-resistor networks are used for gain limiting, as we shall see.

Sinusoidal oscillators

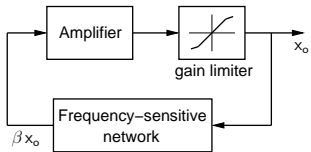


Sinusoidal oscillators

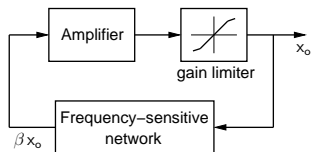


- * Up to about 100 kHz, an Op Amp based amplifier and a β network of resistors and capacitors can be used.

Sinusoidal oscillators

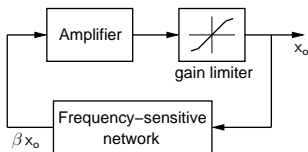



- * Up to about 100 kHz, an Op Amp based amplifier and a β network of resistors and capacitors can be used.
- * At higher frequencies, an Op Amp based amplifier is not suitable because of frequency response and slew rate limitations of Op Amps.

Sinusoidal oscillators


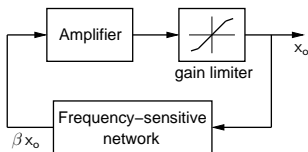


- * Up to about 100 kHz, an Op Amp based amplifier and a β network of resistors and capacitors can be used.
- * At higher frequencies, an Op Amp based amplifier is not suitable because of frequency response and slew rate limitations of Op Amps.
- * For high frequencies, transistor amplifiers are used, and LC tuned circuits or piezoelectric crystals are used in the β network.

Wien bridge oscillator

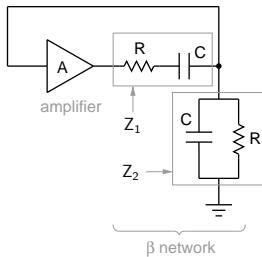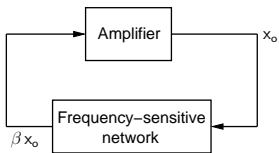


Wien bridge oscillator

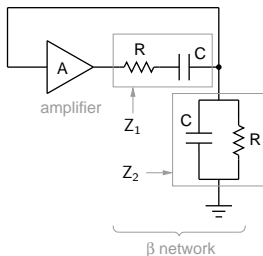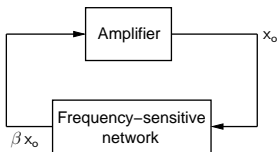

Assuming $R_{in} \rightarrow \infty$ for the amplifier, we get

$$A(s) \beta(s) = A \frac{Z_2}{Z_1 + Z_2} = A \frac{R \parallel (1/sC)}{R + (1/sC) + R \parallel (1/sC)} = A \frac{sRC}{(sRC)^2 + 3sRC + 1}$$

Wien bridge oscillator

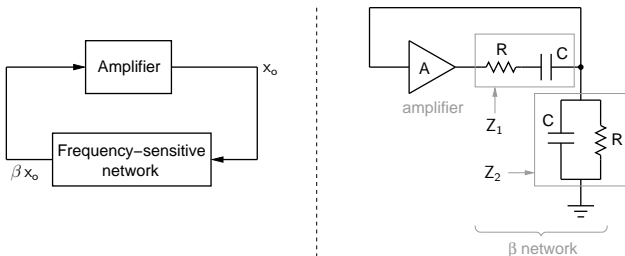



Assuming $R_{in} \rightarrow \infty$ for the amplifier, we get

$$A(s)\beta(s) = A \frac{Z_2}{Z_1 + Z_2} = A \frac{R \parallel (1/sC)}{R + (1/sC) + R \parallel (1/sC)} = A \frac{sRC}{(sRC)^2 + 3sRC + 1}$$

For $A\beta = 1$ (and with A equal to a real positive number),

$$\frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1} \text{ must be real and equal to } 1/A.$$

Wien bridge oscillator

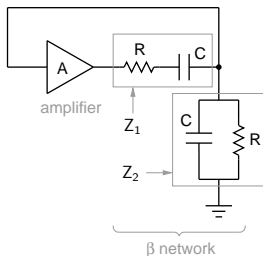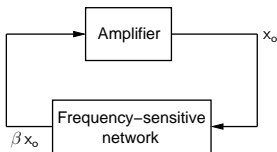

Assuming $R_{in} \rightarrow \infty$ for the amplifier, we get



$$A(s)\beta(s) = A \frac{Z_2}{Z_1 + Z_2} = A \frac{R \parallel (1/sC)}{R + (1/sC) + R \parallel (1/sC)} = A \frac{sRC}{(sRC)^2 + 3sRC + 1}$$

For $A\beta = 1$ (and with A equal to a real positive number),

$\frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1}$ must be real and equal to $1/A$.



$$\rightarrow \boxed{\omega = \frac{1}{RC}, A = 3}$$

Wien bridge oscillator

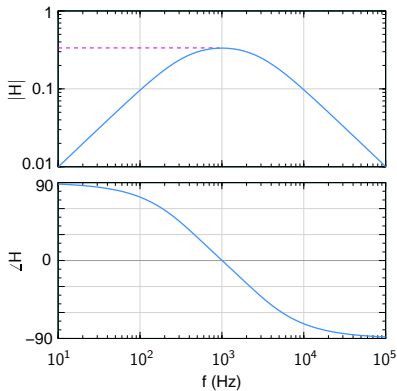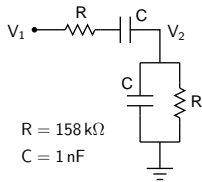

$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1}$$



Wien bridge oscillator

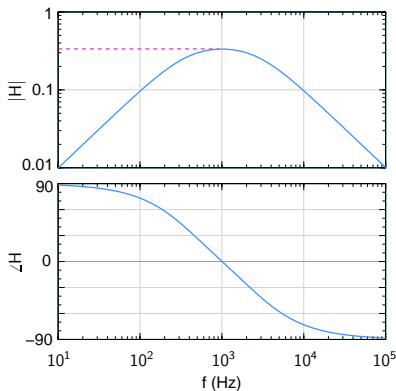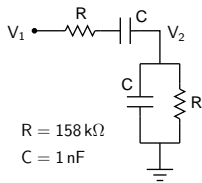

$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1}$$

Note that the condition $\angle H = 0$ is satisfied only at one frequency, $\omega_0 = 1/RC$, i.e., $f_0 = 1 \text{ kHz}$.
At this frequency, $|H| = 0.33$, i.e., $\beta(j\omega) = 1/3$.

Wien bridge oscillator

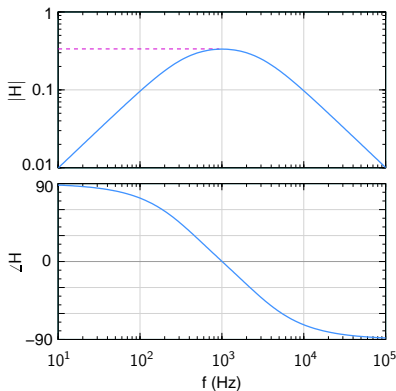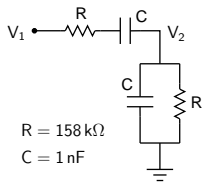



$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1}$$

Note that the condition $\angle H = 0$ is satisfied only at one frequency, $\omega_0 = 1/RC$, i.e., $f_0 = 1 \text{ kHz}$.

At this frequency, $|H| = 0.33$, i.e., $\beta(j\omega) = 1/3$.

For $A\beta = 1 \rightarrow A = 3$, as derived analytically.

Wien bridge oscillator

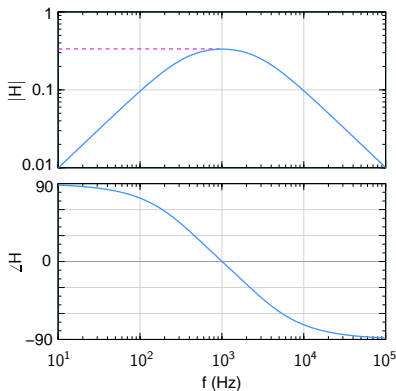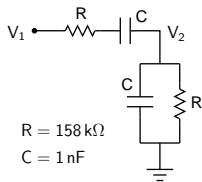

$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1}$$

Note that the condition $\angle H = 0$ is satisfied only at one frequency, $\omega_0 = 1/RC$, i.e., $f_0 = 1 \text{ kHz}$.


At this frequency, $|H| = 0.33$, i.e., $\beta(j\omega) = 1/3$.

For $A\beta = 1 \rightarrow A = 3$, as derived analytically.

SEQUEL file: ee101_osc.1.sqproj


Wien bridge oscillator

Block diagram

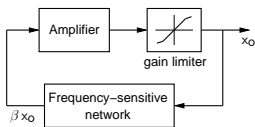


Ref.: S. Franco, "Design with Op Amps and analog ICs"
SEQUEL file: wien_osc_1.sqproj

Implementation

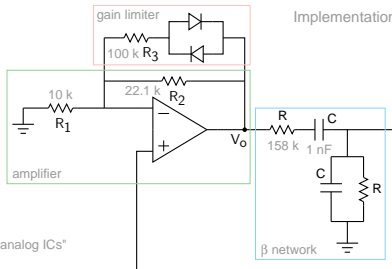


Output voltage

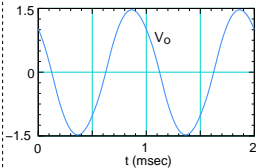


Wien bridge oscillator

Block diagram

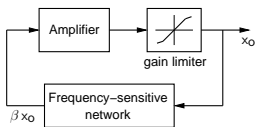


Ref.: S. Franco, "Design with Op Amps and analog ICs"
SEQUEL file: wien_osc_1.sqproj

Implementation

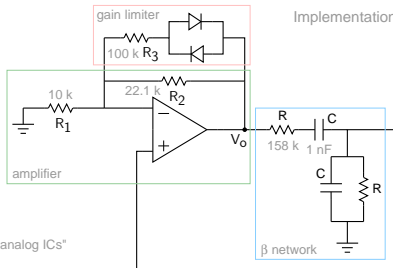


Output voltage

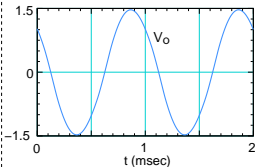

$$* \omega_0 = \frac{1}{RC} = \frac{1}{(158\text{ k}) \times (1\text{ nF})} \rightarrow f_0 = 1\text{ kHz.}$$


Wien bridge oscillator

Block diagram

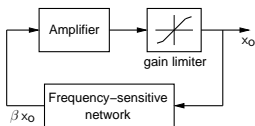


Ref.: S. Franco, "Design with Op Amps and analog ICs"

SEQUEL file: wien_osc_1.sqproj

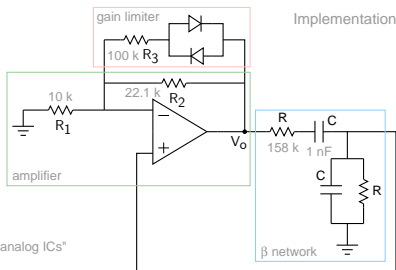

Implementation

Output voltage

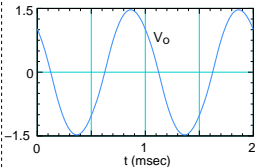


$$* \omega_0 = \frac{1}{RC} = \frac{1}{(158\text{ k}) \times (1\text{ nF})} \rightarrow f_0 = 1\text{ kHz.}$$

$$* \text{ Since the amplifier gain is required to be } A = 3, \text{ we must have } 1 + \frac{R_2}{R_1} = 3 \rightarrow R_2 = 2R_1.$$


Wien bridge oscillator

Block diagram

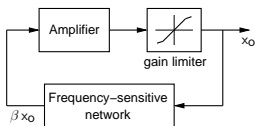


Ref.: S. Franco, "Design with Op Amps and analog ICs"

SEQUEL file: wien_osc_1.sqproj

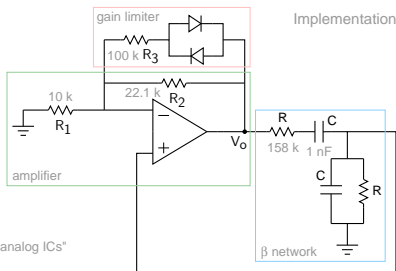

Implementation

Output voltage

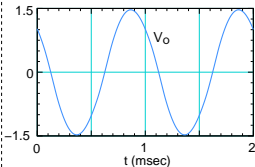


$$* \omega_0 = \frac{1}{RC} = \frac{1}{(158\text{ k}) \times (1\text{ nF})} \rightarrow f_0 = 1\text{ kHz.}$$

$$* \text{ Since the amplifier gain is required to be } A = 3, \text{ we must have } 1 + \frac{R_2}{R_1} = 3 \rightarrow R_2 = 2R_1.$$

* For gain limiting, diodes have been used. With one of the two diodes conducting, $R_2 \rightarrow R_2 \parallel R_3$, and the gain reduces.

Wien bridge oscillator

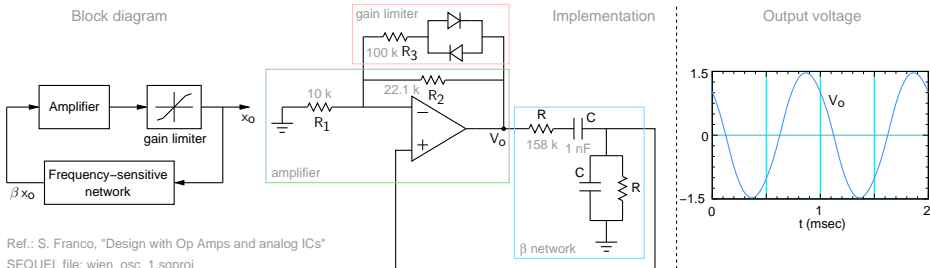


Ref.: S. Franco, "Design with Op Amps and analog ICs"

SEQUEL file: wien_osc_1.sqproj


- * $\omega_0 = \frac{1}{RC} = \frac{1}{(158 \text{ k}) \times (1 \text{ nF})} \rightarrow f_0 = 1 \text{ kHz}.$
- * Since the amplifier gain is required to be $A = 3$, we must have $1 + \frac{R_2}{R_1} = 3 \rightarrow R_2 = 2 R_1.$
- * For gain limiting, diodes have been used. With one of the two diodes conducting, $R_2 \rightarrow R_2 \parallel R_3$, and the gain reduces.
- * Note that there was no need to consider loading of the β network by the amplifier because of the large input resistance of the Op Amp. That is why β could be computed independently.

Phase-shift oscillator

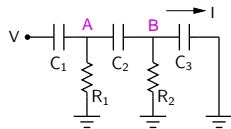

SEQUEL file: ee101_osc_4.sqproj


Phase-shift oscillator

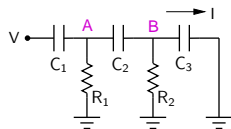

SEQUEL file: ee101_osc_4.sqproj

Let $R_1 = R_2 = R = 10 \text{ k}$, $G = 1/R$, and $C_1 = C_2 = C_3 = C = 16 \text{ nF}$.

Phase-shift oscillator

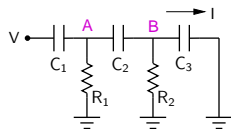

SEQUEL file: ee101_osc_4.sqproj


Let $R_1 = R_2 = R = 10\text{ k}$, $G = 1/R$, and $C_1 = C_2 = C_3 = C = 16\text{ nF}$.

Using nodal analysis,

$$sC(V_A - V) + GV_A + sC(V_A - V_B) = 0 \quad (1)$$

$$sC(V_B - V_A) + GV_B + sCV_B = 0 \quad (2)$$

Phase-shift oscillator

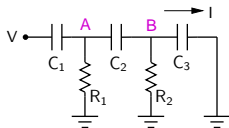

SEQUEL file: ee101_osc_4.sqproj

Let $R_1 = R_2 = R = 10\text{ k}$, $G = 1/R$, and $C_1 = C_2 = C_3 = C = 16\text{ nF}$.

Using nodal analysis,


$$sC(V_A - V) + GV_A + sC(V_A - V_B) = 0 \quad (1)$$

$$sC(V_B - V_A) + GV_B + sCV_B = 0 \quad (2)$$


Solving (1) and (2),

$$I = \frac{1}{R} \frac{(sRC)^3}{3(sRC)^2 + 4sRC + 1} V.$$

Phase-shift oscillator

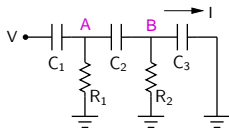

SEQUEL file: ee101_osc_4.sqproj

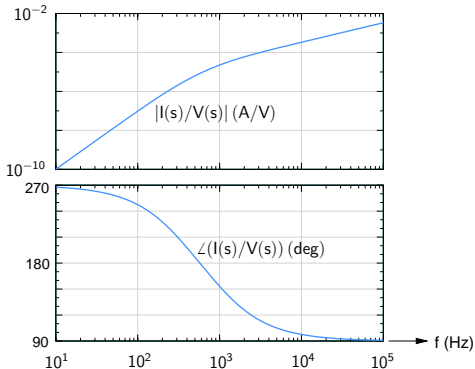

Let $R_1 = R_2 = R = 10 \text{ k}$, $G = 1/R$, and $C_1 = C_2 = C_3 = C = 16 \text{ nF}$.

Using nodal analysis,


$$sC(V_A - V) + GV_A + sC(V_A - V_B) = 0 \quad (1)$$

$$sC(V_B - V_A) + GV_B + sCV_B = 0 \quad (2)$$


Solving (1) and (2),

$$I = \frac{1}{R} \frac{(sRC)^3}{3(sRC)^2 + 4sRC + 1} V.$$

Phase-shift oscillator

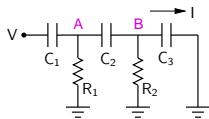


SEQUEL file: ee101_osc_4.sqproj

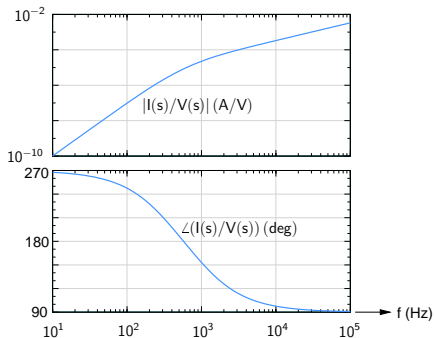


($R_1 = R_2 = R = 10\text{ k}$, and $C_1 = C_2 = C_3 = C = 16\text{ nF}$.)

$$\beta(j\omega) = \frac{I(j\omega)}{V(j\omega)} = \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$

Phase-shift oscillator

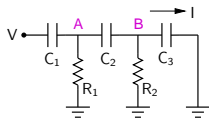

SEQUEL file: ee101_osc_4.sqproj

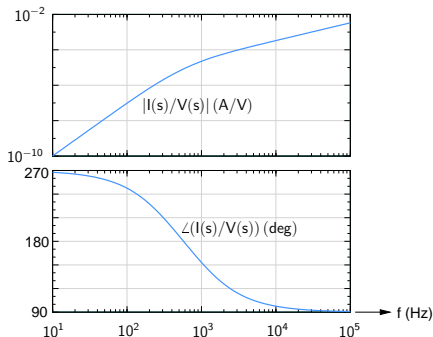


($R_1 = R_2 = R = 10 \text{ k}$, and $C_1 = C_2 = C_3 = C = 16 \text{ nF}$.)

$$\beta(j\omega) = \frac{I(j\omega)}{V(j\omega)} = \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$


For $\beta(j\omega)$ to be a real number, the denominator must be purely imaginary.

$$\rightarrow 3(\omega RC)^2 + 1 = 0, \text{ i.e., } 3(\omega RC)^2 = 1 \rightarrow \omega \equiv \omega_0 = \frac{1}{\sqrt{3}} \frac{1}{RC} \rightarrow f_0 = 574 \text{ Hz.}$$

Phase-shift oscillator

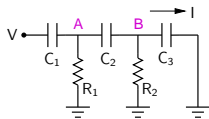

SEQUEL file: ee101_osc_4.sqproj

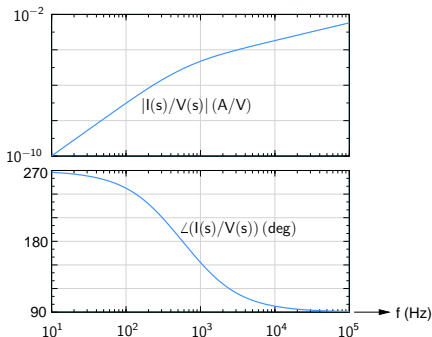

($R_1 = R_2 = R = 10 \text{ k}$, and $C_1 = C_2 = C_3 = C = 16 \text{ nF}$.)

$$\beta(j\omega) = \frac{I(j\omega)}{V(j\omega)} = \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$


For $\beta(j\omega)$ to be a real number, the denominator must be purely imaginary.

$$\rightarrow 3(\omega RC)^2 + 1 = 0, \text{ i.e., } 3(\omega RC)^2 = 1 \rightarrow \omega \equiv \omega_0 = \frac{1}{\sqrt{3}} \frac{1}{RC} \rightarrow f_0 = 574 \text{ Hz.}$$

Note that, at $\omega = \omega_0$,


$$\beta(j\omega_0) = \frac{1}{R} \frac{(j/\sqrt{3})^3}{4j/\sqrt{3}} = -\frac{1}{12R} = -8.33 \times 10^{-6}.$$

Phase-shift oscillator

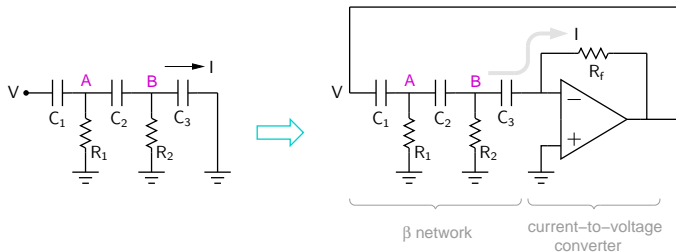

Note that the functioning of the β network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the Op Amp.


Phase-shift oscillator

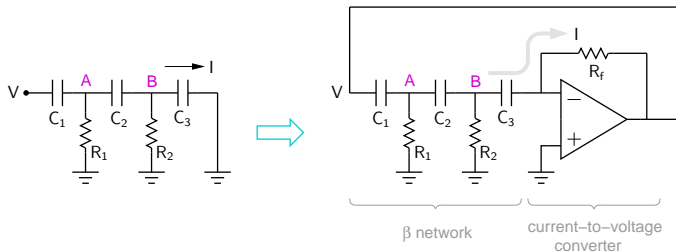

Note that the functioning of the β network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the Op Amp.

$$V(j\omega) = -R_f I(j\omega) \rightarrow A\beta(j\omega) = -R_f \frac{I(j\omega)}{V(j\omega)} = -\frac{R_f}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$

Phase-shift oscillator

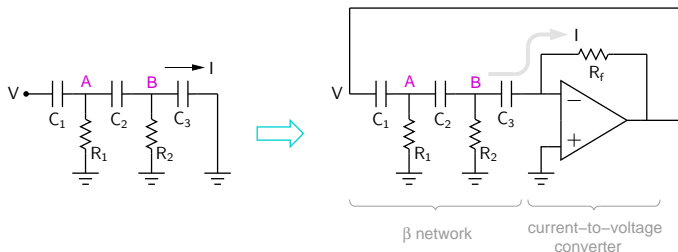


Note that the functioning of the β network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the Op Amp.

$$V(j\omega) = -R_f I(j\omega) \rightarrow A\beta(j\omega) = -R_f \frac{I(j\omega)}{V(j\omega)} = -\frac{R_f}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$

As seen before, at $\omega = \omega_0 = \frac{1}{\sqrt{3} RC}$, we have $\frac{I(j\omega)}{V(j\omega)} = -\frac{1}{12R}$.

Phase-shift oscillator

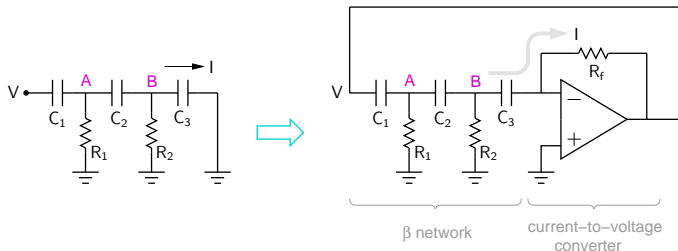


Note that the functioning of the β network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the Op Amp.

$$V(j\omega) = -R_f I(j\omega) \rightarrow A\beta(j\omega) = -R_f \frac{I(j\omega)}{V(j\omega)} = -\frac{R_f}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$

As seen before, at $\omega = \omega_0 = \frac{1}{\sqrt{3} RC}$, we have $\frac{I(j\omega)}{V(j\omega)} = -\frac{1}{12R}$.

For the circuit to oscillate, we need $A\beta = 1 \rightarrow R_f(1/12R) = 1$, i.e., $R_f = 12R$

Phase-shift oscillator

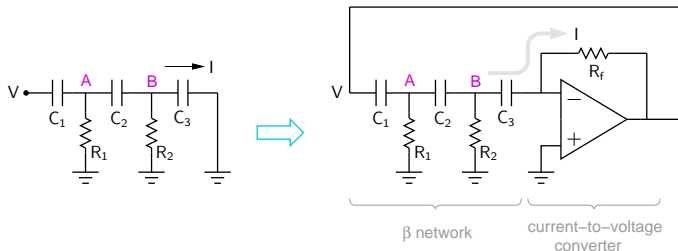

Note that the functioning of the β network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the Op Amp.

$$V(j\omega) = -R_f I(j\omega) \rightarrow A\beta(j\omega) = -R_f \frac{I(j\omega)}{V(j\omega)} = -\frac{R_f}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$


As seen before, at $\omega = \omega_0 = \frac{1}{\sqrt{3} RC}$, we have $\frac{I(j\omega)}{V(j\omega)} = -\frac{1}{12R}$.

For the circuit to oscillate, we need $A\beta = 1 \rightarrow R_f(1/12R) = 1$, i.e., $R_f = 12R$

In addition, we employ a gain limiter circuit to complete the oscillator design.


Phase-shift oscillator

Block diagram

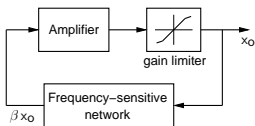


Ref.: Sedra and Smith, "Microelectronic circuits"
SEQUEL file: phase_shift_osc_1.sqproj

Implementation

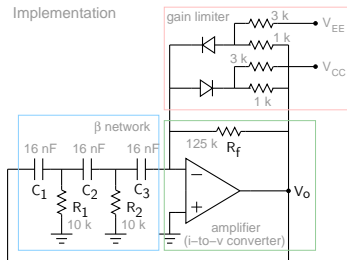


Output voltage

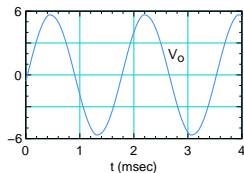


$$\omega_0 = \frac{1}{\sqrt{3}} \frac{1}{RC} \rightarrow f_0 = 574 \text{ Hz}, T = 1.74 \text{ ms}.$$

Inverting amplifier, revisited

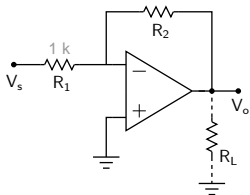

SEQUEL file: inv_amp_ac.sqproj


Inverting amplifier, revisited

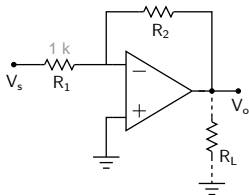

SEQUEL file: inv_amp_ac.sqproj

- * As seen earlier, $A_V = -R_2/R_1 \rightarrow |A_V|$ should be independent of the signal frequency.


Inverting amplifier, revisited

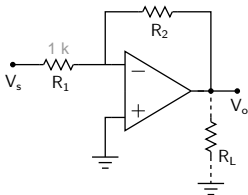


SEQUEL file: inv_amp_ac.sqproj

- * As seen earlier, $A_V = -R_2/R_1 \rightarrow |A_V|$ should be independent of the signal frequency.
- * However, a measurement with a real Op Amp will show that $|A_V|$ starts reducing at higher frequencies.

Inverting amplifier, revisited

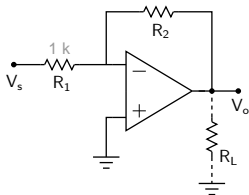


SEQUEL file: inv_amp_ac.sqproj

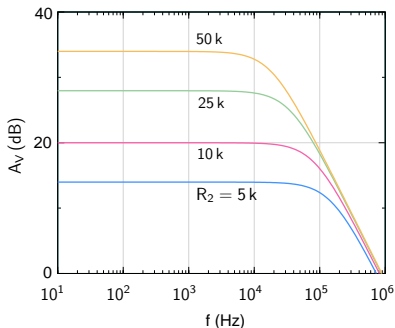


- * As seen earlier, $A_V = -R_2/R_1 \rightarrow |A_V|$ should be independent of the signal frequency.
- * However, a measurement with a real Op Amp will show that $|A_V|$ starts reducing at higher frequencies.

Inverting amplifier, revisited

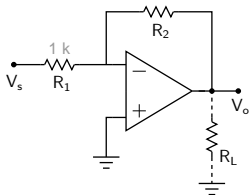


SEQUEL file: inv_amp_ac.sqproj

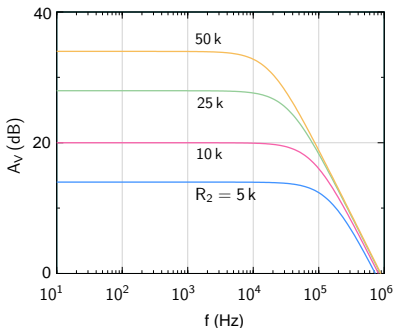


- * As seen earlier, $A_V = -R_2/R_1 \rightarrow |A_V|$ should be independent of the signal frequency.
- * However, a measurement with a real Op Amp will show that $|A_V|$ starts reducing at higher frequencies.
- * If $|A_V|$ is increased, the gain “roll-off” starts at lower frequencies.

Inverting amplifier, revisited


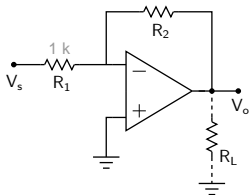


SEQUEL file: inv_amp_ac.sqproj

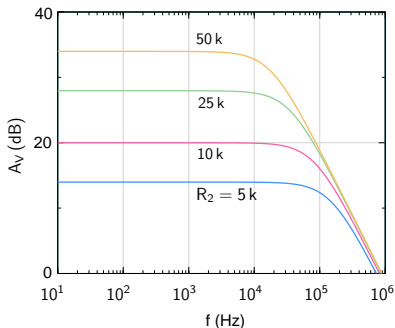



- * As seen earlier, $A_V = -R_2/R_1 \rightarrow |A_V|$ should be independent of the signal frequency.
- * However, a measurement with a real Op Amp will show that $|A_V|$ starts reducing at higher frequencies.
- * If $|A_V|$ is increased, the gain “roll-off” starts at lower frequencies.
- * This behaviour has to do with the frequency response of the Op Amp which we have not considered so far.

Frequency response of Op Amp 741

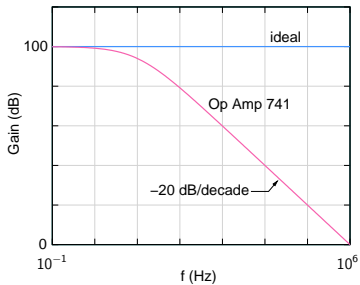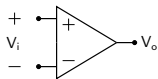

The gain of the 741 Op Amp starts falling at rather low frequencies, with $f_c \simeq 10$ Hz!



Frequency response of Op Amp 741

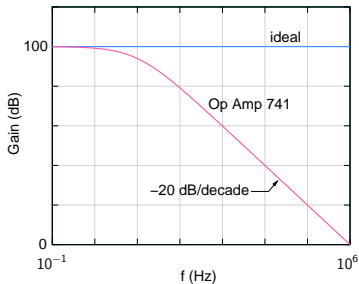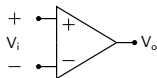

The gain of the 741 Op Amp starts falling at rather low frequencies, with $f_c \simeq 10$ Hz!

The 741 Op Amp (and many others) are *designed* with this feature to ensure that, in typical amplifier applications, the overall circuit is stable (and not oscillatory).

Frequency response of Op Amp 741

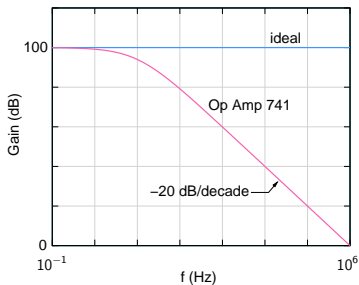
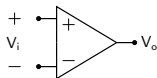


The gain of the 741 Op Amp starts falling at rather low frequencies, with $f_c \simeq 10$ Hz!

The 741 Op Amp (and many others) are *designed* with this feature to ensure that, in typical amplifier applications, the overall circuit is stable (and not oscillatory).

In other words, the Op Amp has been *internally compensated* for stability.

Frequency response of Op Amp 741

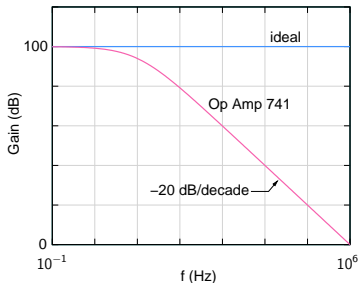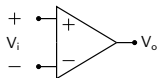

The gain of the 741 Op Amp starts falling at rather low frequencies, with $f_c \simeq 10$ Hz!

The 741 Op Amp (and many others) are *designed* with this feature to ensure that, in typical amplifier applications, the overall circuit is stable (and not oscillatory).



In other words, the Op Amp has been *internally compensated* for stability.

The gain of the 741 Op Amp can be represented by,

$$A(s) = \frac{A_0}{1 + s/\omega_c},$$

with $A_0 \approx 10^5$ (i.e., 100 dB), $\omega_c \approx 2\pi \times 10$ rad/s.



Frequency response of Op Amp 741

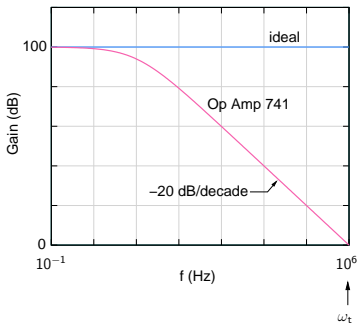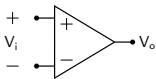

$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_c}$$

$$\text{For } \omega \gg \omega_c, \text{ we have } A(j\omega) \approx \frac{A_0}{j\omega/\omega_c}$$

Frequency response of Op Amp 741

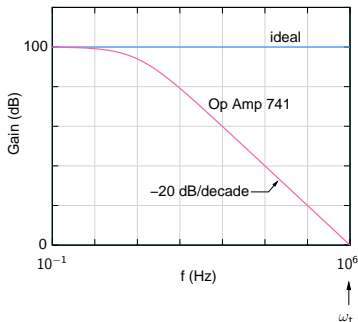
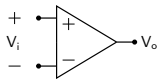


$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_c}$$

For $\omega \gg \omega_c$, we have $A(j\omega) \approx \frac{A_0}{j\omega/\omega_c}$.

$|A(j\omega)|$ becomes 1 when $A_0 = \omega/\omega_c$, i.e., $\omega = A_0\omega_c$.

Frequency response of Op Amp 741

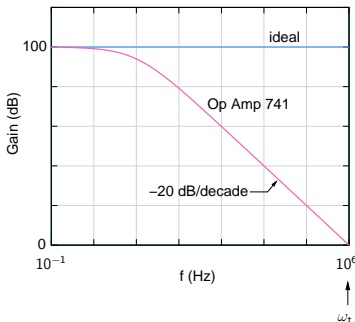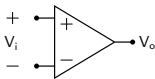

$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_c}$$



For $\omega \gg \omega_c$, we have $A(j\omega) \approx \frac{A_0}{j\omega/\omega_c}$.

$|A(j\omega)|$ becomes 1 when $A_0 = \omega/\omega_c$, i.e., $\omega = A_0\omega_c$.

This frequency, $\omega_t = A_0\omega_c$, is called the unity-gain frequency.

For the 741 Op Amp, $f_t = A_0f_c \approx 10^5 \times 10 = 10^6$ Hz.

Frequency response of Op Amp 741

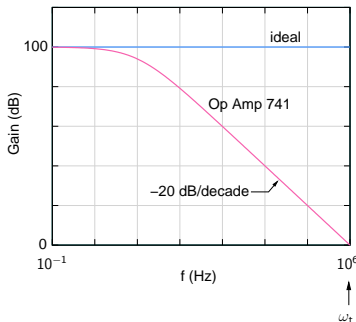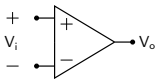

$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_c}$$

$$\text{For } \omega \gg \omega_c, \text{ we have } A(j\omega) \approx \frac{A_0}{j\omega/\omega_c}$$




$|A(j\omega)|$ becomes 1 when $A_0 = \omega/\omega_c$, i.e., $\omega = A_0\omega_c$.

This frequency, $\omega_t = A_0\omega_c$, is called the unity-gain frequency.


For the 741 Op Amp, $f_t = A_0f_c \approx 10^5 \times 10 = 10^6$ Hz.

Let us see how the frequency response of the 741 Op Amp affects the gain of an inverting amplifier.

Inverting amplifier, revisited

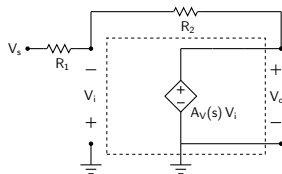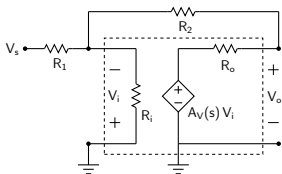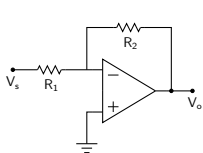


Inverting amplifier, revisited

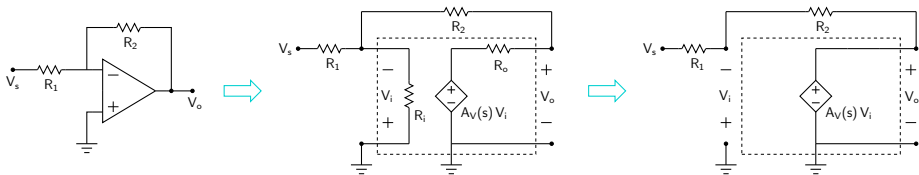

Assuming R_i to be large and R_o to be small, we get

$$-V_i(s) = V_s(s) \frac{R_2}{R_1 + R_2} + V_o(s) \frac{R_1}{R_1 + R_2}.$$

Inverting amplifier, revisited

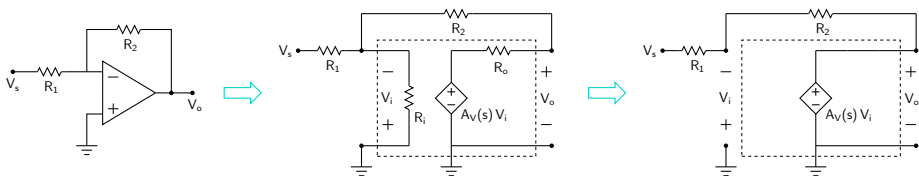


Assuming R_i to be large and R_o to be small, we get

$$-V_i(s) = V_s(s) \frac{R_2}{R_1 + R_2} + V_o(s) \frac{R_1}{R_1 + R_2}.$$

Using $V_o(s) = A_V(s) V_i(s)$,

$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{\left[1 + \left(\frac{R_1 + R_2}{R_1} \right) \frac{1}{A_0} \right] + \left(\frac{R_1 + R_2}{R_1 A_0} \right) \frac{s}{\omega_c}}$$

Inverting amplifier, revisited

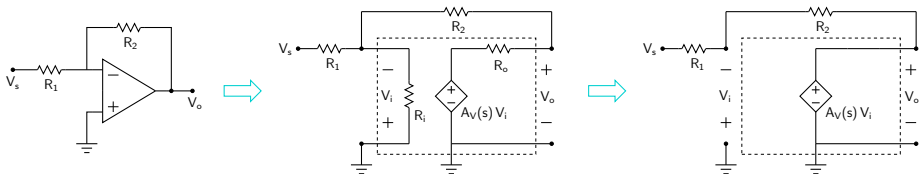


Assuming R_i to be large and R_o to be small, we get

$$-V_i(s) = V_s(s) \frac{R_2}{R_1 + R_2} + V_o(s) \frac{R_1}{R_1 + R_2}.$$

Using $V_o(s) = A_V(s) V_i(s)$,


$$\begin{aligned} \frac{V_o(s)}{V_s(s)} &= -\frac{R_2}{R_1} \frac{1}{\left[1 + \left(\frac{R_1 + R_2}{R_1}\right) \frac{1}{A_0}\right] + \left(\frac{R_1 + R_2}{R_1 A_0}\right) \frac{s}{\omega_c}} \\ &\approx -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c}, \quad \text{with } \omega'_c = \frac{\omega_c A_0}{1 + R_2/R_1} = \frac{\omega_t}{1 + R_2/R_1}. \end{aligned}$$

Inverting amplifier, revisited

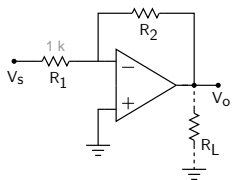

SEQUEL file: inv_amp_ac.sqproj


Inverting amplifier, revisited

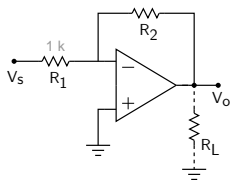

SEQUEL file: inv_amp_ac.sqproj

$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

Inverting amplifier, revisited

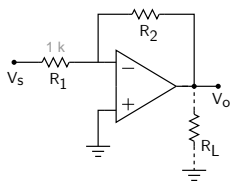


| R_2 | gain (dB) | f_c' (kHz) |
|-------|-----------|--------------|
| 5 k | 14 | 167 |
| | | |
| | | |
| | | |

SEQUEL file: inv_amp_ac.sqproj


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

Inverting amplifier, revisited

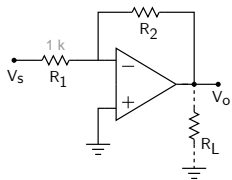


| R_2 | gain (dB) | f_c' (kHz) |
|-------|-----------|--------------|
| 5 k | 14 | 167 |
| | | |
| | | |
| | | |

SEQUEL file: inv_amp_ac.sqproj

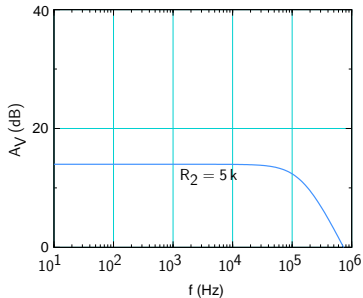


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

Inverting amplifier, revisited

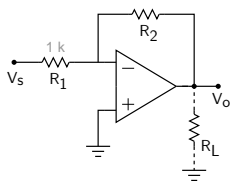


| R_2 | gain (dB) | f_c' (kHz) |
|-------|-----------|--------------|
| 5 k | 14 | 167 |
| 10 k | 20 | 91 |
| | | |
| | | |

SEQUEL file: inv_amp_ac.sqproj

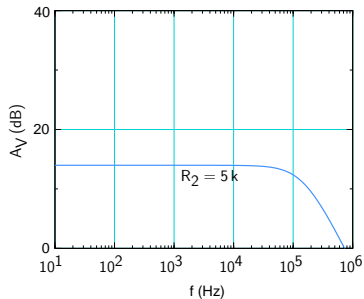


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

Inverting amplifier, revisited

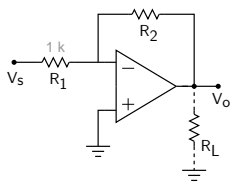


| R_2 | gain (dB) | f_c' (kHz) |
|-------|-----------|--------------|
| 5 k | 14 | 167 |
| 10 k | 20 | 91 |
| | | |
| | | |

SEQUEL file: inv_amp_ac.sqproj

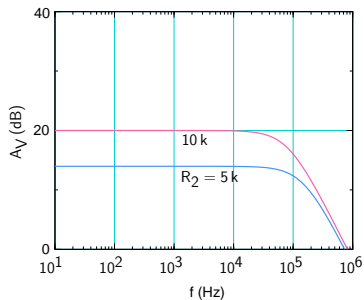


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

Inverting amplifier, revisited

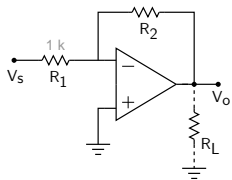


| R_2 | gain (dB) | f_c' (kHz) |
|-------|-----------|--------------|
| 5 k | 14 | 167 |
| 10 k | 20 | 91 |
| 25 k | 28 | 38 |
| | | |

SEQUEL file: inv_amp_ac.sqproj

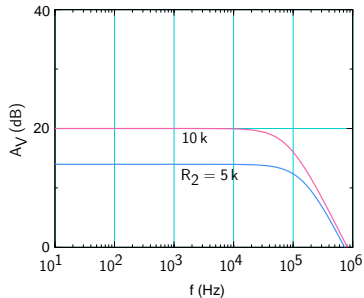


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega_c'} \quad \omega_c' = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

Inverting amplifier, revisited

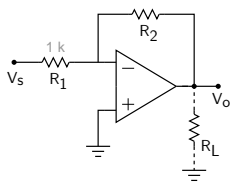


| R_2 | gain (dB) | f_c' (kHz) |
|-------|-----------|--------------|
| 5 k | 14 | 167 |
| 10 k | 20 | 91 |
| 25 k | 28 | 38 |
| | | |

SEQUEL file: inv_amp_ac.sqproj

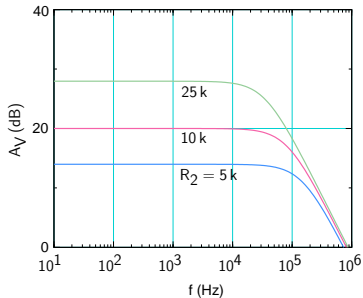


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

Inverting amplifier, revisited

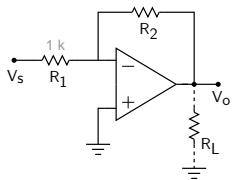


| R_2 | gain (dB) | f_c' (kHz) |
|-------|-----------|--------------|
| 5 k | 14 | 167 |
| 10 k | 20 | 91 |
| 25 k | 28 | 38 |
| 50 k | 34 | 19.6 |

SEQUEL file: inv_amp_ac.sqproj

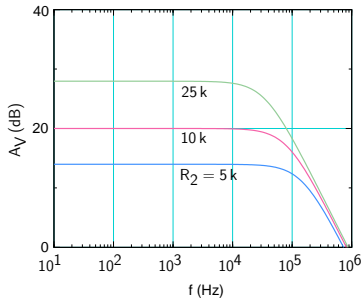


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

Inverting amplifier, revisited

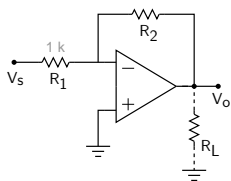

| R_2 | gain (dB) | f_c' (kHz) |
|-------|-----------|--------------|
| 5 k | 14 | 167 |
| 10 k | 20 | 91 |
| 25 k | 28 | 38 |
| 50 k | 34 | 19.6 |

SEQUEL file: inv_amp_ac.sqproj

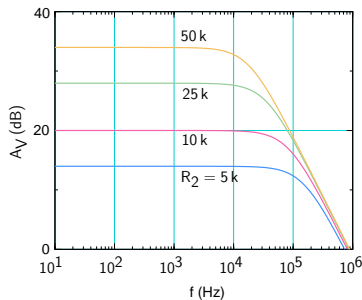

$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$