

# EE101: RLC Circuits (with DC sources)

---




**M. B. Patil**


[mbpatil@ee.iitb.ac.in](mailto:mbpatil@ee.iitb.ac.in)

Department of Electrical Engineering  
Indian Institute of Technology Bombay

# Series $RLC$ circuit

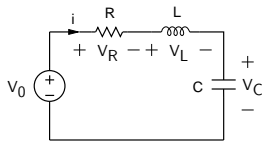


## Series $RLC$ circuit

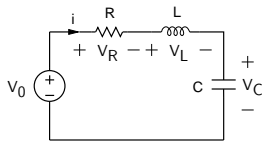

$$\text{KVL: } V_R + V_L + V_C = V_0 \Rightarrow iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_0$$

## Series $RLC$ circuit

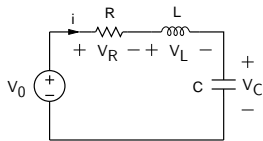


$$\text{KVL: } V_R + V_L + V_C = V_0 \Rightarrow iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_0$$

Differentiating w. r. t.  $t$ , we get,

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i = 0.$$

## Series $RLC$ circuit

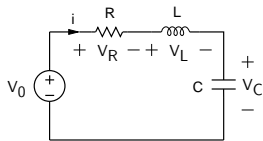

$$\text{KVL: } V_R + V_L + V_C = V_0 \Rightarrow iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_0$$


Differentiating w. r. t.  $t$ , we get,

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i = 0.$$


$$\text{i.e., } \frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0,$$

a second-order ODE with constant coefficients.

# Parallel $RLC$ circuit

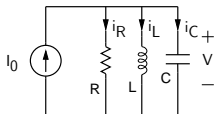


## Parallel $RLC$ circuit

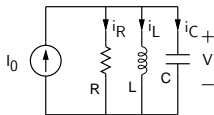

$$\text{KCL: } i_R + i_L + i_C = i_0 \Rightarrow \frac{1}{R} V + \frac{1}{L} \int V dt + C \frac{dV}{dt} = i_0$$

## Parallel $RLC$ circuit

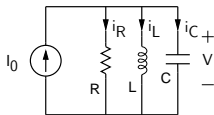


$$\text{KCL: } i_R + i_L + i_C = i_0 \Rightarrow \frac{1}{R} V + \frac{1}{L} \int V dt + C \frac{dV}{dt} = i_0$$

Differentiating w. r. t.  $t$ , we get,

$$\frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V + C \frac{d^2V}{dt^2} = 0.$$

## Parallel $RLC$ circuit

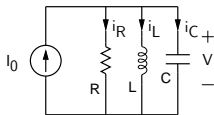

$$\text{KCL: } i_R + i_L + i_C = i_0 \Rightarrow \frac{1}{R} V + \frac{1}{L} \int V dt + C \frac{dV}{dt} = i_0$$



Differentiating w. r. t.  $t$ , we get,

$$\frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V + C \frac{d^2V}{dt^2} = 0.$$


$$\text{i.e., } \frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0,$$

a second-order ODE with constant coefficients.

# Series/Parallel RLC circuits

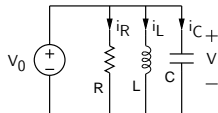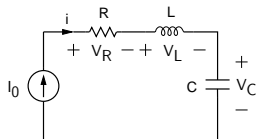


## Series/Parallel RLC circuits

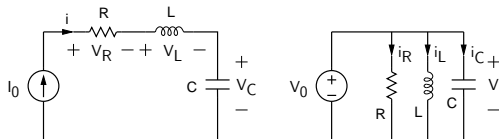

- \* A series RLC circuit driven by a constant current source is trivial to analyze.


## Series/Parallel RLC circuits

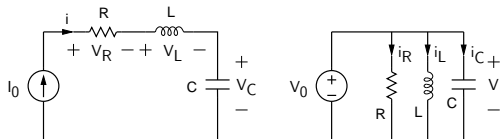

- \* A series RLC circuit driven by a constant current source is trivial to analyze. Since the current through each element is known, the voltage can be found in a straightforward manner.

$$V_R = iR, \quad V_L = L \frac{di}{dt}, \quad V_C = \frac{1}{C} \int i dt.$$

## Series/Parallel RLC circuits

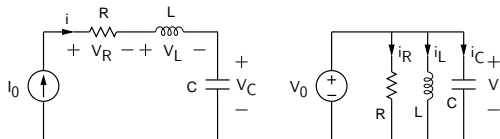


- \* A series RLC circuit driven by a constant current source is trivial to analyze. Since the current through each element is known, the voltage can be found in a straightforward manner.

$$V_R = iR, \quad V_L = L \frac{di}{dt}, \quad V_C = \frac{1}{C} \int i dt.$$

- \* A parallel RLC circuit driven by a constant voltage source is trivial to analyze.

## Series/Parallel RLC circuits

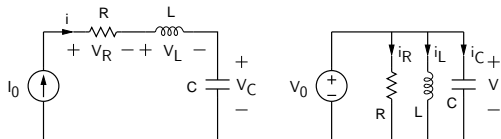


- \* A series RLC circuit driven by a constant current source is trivial to analyze. Since the current through each element is known, the voltage can be found in a straightforward manner.

$$V_R = iR, \quad V_L = L \frac{di}{dt}, \quad V_C = \frac{1}{C} \int i dt.$$

- \* A parallel RLC circuit driven by a constant voltage source is trivial to analyze. Since the voltage across each element is known, the current can be found in a straightforward manner.

$$i_R = V/R, \quad i_C = C \frac{dV}{dt}, \quad i_L = \frac{1}{L} \int V dt.$$

## Series/Parallel $RLC$ circuits

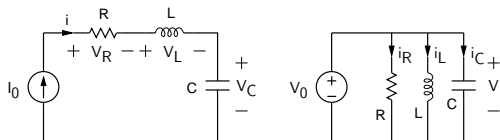

- \* A series  $RLC$  circuit driven by a constant current source is trivial to analyze. Since the current through each element is known, the voltage can be found in a straightforward manner.

$$V_R = iR, \quad V_L = L \frac{di}{dt}, \quad V_C = \frac{1}{C} \int i dt.$$

- \* A parallel  $RLC$  circuit driven by a constant voltage source is trivial to analyze. Since the voltage across each element is known, the current can be found in a straightforward manner.


$$i_R = V/R, \quad i_C = C \frac{dV}{dt}, \quad i_L = \frac{1}{L} \int V dt.$$

- \* The above equations hold even if the applied voltage or current is not constant, and the variables of interest can still be easily obtained without solving a differential equation.


A general  $RLC$  circuit (with one inductor and one capacitor) also leads to a second-order ODE. As an example, consider the following circuit:
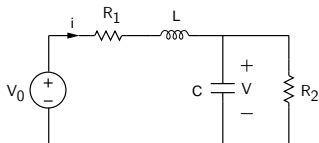
## Series/Parallel $RLC$ circuits

A general  $RLC$  circuit (with one inductor and one capacitor) also leads to a second-order ODE. As an example, consider the following circuit:



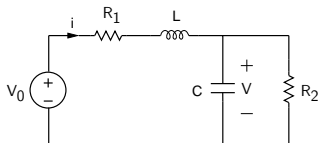
A general  $RLC$  circuit (with one inductor and one capacitor) also leads to a second-order ODE. As an example, consider the following circuit:



$$V_0 = R_1 i + L \frac{di}{dt} + V \quad (1)$$

$$i = C \frac{dV}{dt} + \frac{1}{R_2} V \quad (2)$$

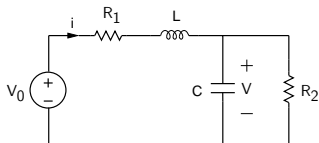A general *RLC* circuit (with one inductor and one capacitor) also leads to a second-order ODE. As an example, consider the following circuit:



$$V_0 = R_1 i + L \frac{di}{dt} + V \quad (1)$$

$$i = C \frac{dV}{dt} + \frac{1}{R_2} V \quad (2)$$

Substituting (2) in (1), we get

$$V_0 = R_1 [CV' + V/R_2] + L [CV'' + V'/R_2] + V, \quad (3)$$

$$V'' [LC] + V' [R_1 C + L/R_2] + V [1 + R_1/R_2] = V_0. \quad (4)$$

Consider the second-order ODE with constant coefficients,

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = K \text{ (constant).}$$

Consider the second-order ODE with constant coefficients,

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = K \text{ (constant).}$$

The general solution  $y(t)$  can be written as,

$$y(t) = y^{(h)}(t) + y^{(p)}(t),$$

where  $y^{(h)}(t)$  is the solution of the homogeneous equation,

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = 0,$$

and  $y^{(p)}(t)$  is a particular solution.

Consider the second-order ODE with constant coefficients,

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = K \text{ (constant)}.$$

The general solution  $y(t)$  can be written as,

$$y(t) = y^{(h)}(t) + y^{(p)}(t),$$

where  $y^{(h)}(t)$  is the solution of the homogeneous equation,

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = 0,$$

and  $y^{(p)}(t)$  is a particular solution.

Since  $K = \text{constant}$ , a particular solution is simply  $y^{(p)}(t) = K/b$ .

Consider the second-order ODE with constant coefficients,

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = K \text{ (constant).}$$

The general solution  $y(t)$  can be written as,

$$y(t) = y^{(h)}(t) + y^{(p)}(t),$$

where  $y^{(h)}(t)$  is the solution of the homogeneous equation,

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = 0,$$

and  $y^{(p)}(t)$  is a particular solution.

Since  $K = \text{constant}$ , a particular solution is simply  $y^{(p)}(t) = K/b$ .

In the context of *RLC* circuits,  $y^{(p)}(t)$  is the steady-state value of the variable of interest, i.e.,

$$y^{(p)} = \lim_{t \rightarrow \infty} y(t),$$

which can be often found by inspection.

For the homogeneous equation,

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = 0,$$

we first find the roots of the associated *characteristic equation*,

$$r^2 + ar + b = 0.$$

Let the roots be  $r_1$  and  $r_2$ . We have the following possibilities:

For the homogeneous equation,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = 0,$$

we first find the roots of the associated *characteristic equation*,

$$r^2 + a r + b = 0.$$

Let the roots be  $r_1$  and  $r_2$ . We have the following possibilities:

- \*  $r_1, r_2$  are real,  $r_1 \neq r_2$  (“overdamped”)

$$y^{(h)}(t) = C_1 \exp(r_1 t) + C_2 \exp(r_2 t).$$

For the homogeneous equation,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = 0,$$

we first find the roots of the associated *characteristic equation*,

$$r^2 + a r + b = 0.$$

Let the roots be  $r_1$  and  $r_2$ . We have the following possibilities:

- \*  $r_1, r_2$  are real,  $r_1 \neq r_2$  (“overdamped”)

$$y^{(h)}(t) = C_1 \exp(r_1 t) + C_2 \exp(r_2 t).$$

- \*  $r_1, r_2$  are complex,  $r_{1,2} = \alpha \pm j\omega$  (“underdamped”)

$$y^{(h)}(t) = \exp(\alpha t) [C_1 \cos(\omega t) + C_2 \sin(\omega t)].$$

For the homogeneous equation,

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = 0,$$

we first find the roots of the associated *characteristic equation*,

$$r^2 + ar + b = 0.$$

Let the roots be  $r_1$  and  $r_2$ . We have the following possibilities:

- \*  $r_1, r_2$  are real,  $r_1 \neq r_2$  (“overdamped”)

$$y^{(h)}(t) = C_1 \exp(r_1 t) + C_2 \exp(r_2 t).$$


- \*  $r_1, r_2$  are complex,  $r_{1,2} = \alpha \pm j\omega$  (“underdamped”)

$$y^{(h)}(t) = \exp(\alpha t) [C_1 \cos(\omega t) + C_2 \sin(\omega t)].$$

- \*  $r_1 = r_2 = \alpha$  (“critically damped”)

$$y^{(h)}(t) = \exp(\alpha t) [C_1 t + C_2].$$

## Parallel $RLC$ circuit

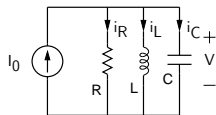


$$R=10\ \Omega$$

$$C=1\ \mu\text{F}$$

$$L=0.44\ \text{mH}$$

$$I_0 = 100\ \text{mA}$$

## Parallel RLC circuit

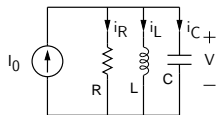

$$R=10\ \Omega$$

$$C=1\ \mu\text{F}$$


$$L=0.44\ \text{mH}$$

$$I_0 = 100\ \text{mA}$$

$$i_L(0^-) = 0\ \text{A} \Rightarrow i_L(0^+) = 0\ \text{A}.$$

$$V(0^-) = 0\ \text{V} \Rightarrow V(0^+) = 0\ \text{V}.$$

## Parallel $RLC$ circuit

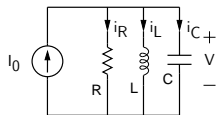

$$R=10\ \Omega$$

$$C=1\ \mu\text{F}$$

$$L=0.44\ \text{mH}$$


$$i_0 = 100\ \text{mA}$$

$$i_L(0^-) = 0\ \text{A} \Rightarrow i_L(0^+) = 0\ \text{A}.$$

$$V(0^-) = 0\ \text{V} \Rightarrow V(0^+) = 0\ \text{V}.$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \quad (\text{as derived earlier})$$

## Parallel RLC circuit

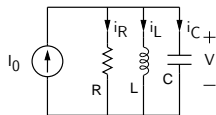

$$R=10\ \Omega$$

$$C=1\ \mu\text{F}$$

$$L=0.44\ \text{mH}$$

$$I_0 = 100\ \text{mA}$$

$$i_L(0^-) = 0\ \text{A} \Rightarrow i_L(0^+) = 0\ \text{A}.$$


$$V(0^-) = 0\ \text{V} \Rightarrow V(0^+) = 0\ \text{V}.$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \quad (\text{as derived earlier})$$

The roots of the characteristic equation are (show this):

$$r_1 = -0.65 \times 10^5\ \text{s}^{-1}, \quad r_2 = -0.35 \times 10^5\ \text{s}^{-1}.$$

## Parallel RLC circuit

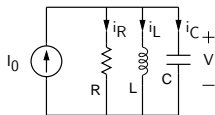

$$R=10\ \Omega$$

$$C=1\ \mu\text{F}$$

$$L=0.44\ \text{mH}$$

$$I_0 = 100\ \text{mA}$$

$$i_L(0^-) = 0\ \text{A} \Rightarrow i_L(0^+) = 0\ \text{A}.$$

$$V(0^-) = 0\ \text{V} \Rightarrow V(0^+) = 0\ \text{V}.$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \quad (\text{as derived earlier})$$


The roots of the characteristic equation are (show this):

$$r_1 = -0.65 \times 10^5\ \text{s}^{-1}, \quad r_2 = -0.35 \times 10^5\ \text{s}^{-1}.$$

The general expression for  $V(t)$  is,

$$V(t) = A \exp(r_1 t) + B \exp(r_2 t) + V(\infty),$$

## Parallel RLC circuit

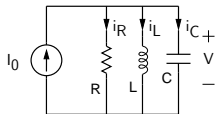

$$R=10\ \Omega$$

$$C=1\ \mu\text{F}$$

$$L=0.44\ \text{mH}$$

$$I_0 = 100\ \text{mA}$$

$$i_L(0^-) = 0\ \text{A} \Rightarrow i_L(0^+) = 0\ \text{A}.$$

$$V(0^-) = 0\ \text{V} \Rightarrow V(0^+) = 0\ \text{V}.$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \quad (\text{as derived earlier})$$

The roots of the characteristic equation are (show this):

$$r_1 = -0.65 \times 10^5\ \text{s}^{-1}, \quad r_2 = -0.35 \times 10^5\ \text{s}^{-1}.$$

The general expression for  $V(t)$  is,

$$V(t) = A \exp(r_1 t) + B \exp(r_2 t) + V(\infty),$$

$$\text{i.e., } V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2) + V(\infty),$$

where  $\tau_1 = -1/r_1 = 15.4\ \mu\text{s}$ ,  $\tau_2 = -1/r_2 = 28.6\ \mu\text{s}$ .

## Parallel $RLC$ circuit

$$\text{As } t \rightarrow \infty, V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V.}$$

## Parallel $RLC$ circuit

As  $t \rightarrow \infty$ ,  $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$ .

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2)$ ,

## Parallel $RLC$ circuit

As  $t \rightarrow \infty$ ,  $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$ .

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2)$ ,

Since  $V(0^+) = 0 \text{ V}$ , we have,

$$A + B = 0. \tag{1}$$

## Parallel $RLC$ circuit

As  $t \rightarrow \infty$ ,  $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$ .

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2)$ ,

Since  $V(0^+) = 0 \text{ V}$ , we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is  $i_L(0^+) = 0 \text{ A}$ , which can be used to obtain  $\frac{dV}{dt}(0^+)$ .

## Parallel $RLC$ circuit

As  $t \rightarrow \infty$ ,  $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$ .

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2)$ ,

Since  $V(0^+) = 0 \text{ V}$ , we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is  $i_L(0^+) = 0 \text{ A}$ , which can be used to obtain  $\frac{dV}{dt}(0^+)$ .

$i_L(0^+) = I_0 - \frac{1}{R} V(0^+) - C \frac{dV}{dt}(0^+) = 0 \text{ A}$ , which gives

## Parallel $RLC$ circuit

As  $t \rightarrow \infty$ ,  $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$ .

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2)$ ,

Since  $V(0^+) = 0 \text{ V}$ , we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is  $i_L(0^+) = 0 \text{ A}$ , which can be used to obtain  $\frac{dV}{dt}(0^+)$ .

$i_L(0^+) = I_0 - \frac{1}{R} V(0^+) - C \frac{dV}{dt}(0^+) = 0 \text{ A}$ , which gives

$$(A/\tau_1) + (B/\tau_2) = -I_0/C. \quad (2)$$

## Parallel $RLC$ circuit

As  $t \rightarrow \infty$ ,  $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$ .

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2)$ ,

Since  $V(0^+) = 0 \text{ V}$ , we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is  $i_L(0^+) = 0 \text{ A}$ , which can be used to obtain  $\frac{dV}{dt}(0^+)$ .

$i_L(0^+) = I_0 - \frac{1}{R} V(0^+) - C \frac{dV}{dt}(0^+) = 0 \text{ A}$ , which gives

$$(A/\tau_1) + (B/\tau_2) = -I_0/C. \quad (2)$$

From (1) and (2), we get the values of  $A$  and  $B$ , and

$$V(t) = -3.3 [\exp(-t/\tau_1) - \exp(-t/\tau_2)] \text{ V}. \quad (3)$$

(SEQUEL file: ee101\_r1c\_1.sqproj)

## Parallel RLC circuit

As  $t \rightarrow \infty$ ,  $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$ .

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2)$ ,

Since  $V(0^+) = 0 \text{ V}$ , we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is  $i_L(0^+) = 0 \text{ A}$ , which can be used to obtain  $\frac{dV}{dt}(0^+)$ .


$i_L(0^+) = I_0 - \frac{1}{R} V(0^+) - C \frac{dV}{dt}(0^+) = 0 \text{ A}$ , which gives

$$(A/\tau_1) + (B/\tau_2) = -I_0/C. \quad (2)$$



From (1) and (2), we get the values of  $A$  and  $B$ , and

$$V(t) = -3.3 [\exp(-t/\tau_1) - \exp(-t/\tau_2)] \text{ V}. \quad (3)$$


(SEQUEL file: ee101\_rlc\_1.sqproj)

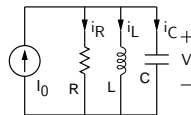

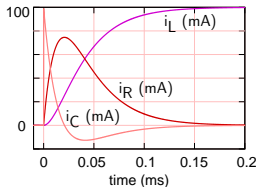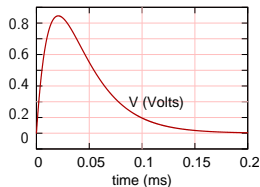
$R=10 \Omega$   
 $C=1 \mu\text{F}$   
 $L=0.44 \text{ mH}$   
 $I_0 = 100 \text{ mA}$




# Series $RLC$ circuit: home work

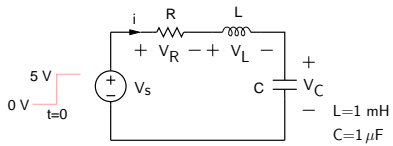


## Series $RLC$ circuit: home work

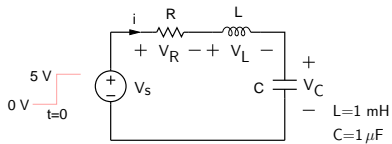

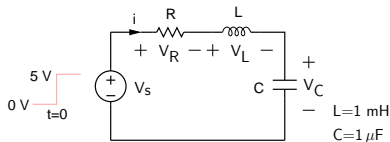
(a) Show that the condition for critically damped response is  $R = 63.2\text{ }\Omega$ .



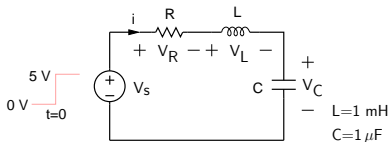- (a) Show that the condition for critically damped response is  $R = 63.2 \Omega$ .
- (b) For  $R = 20 \Omega$ , derive expressions for  $i(t)$  and  $V_L(t)$  for  $t > 0$  (Assume that  $V_C(0^-) = 0 \text{ V}$  and  $i_L(0^-) = 0 \text{ A}$ ). Plot them versus time.




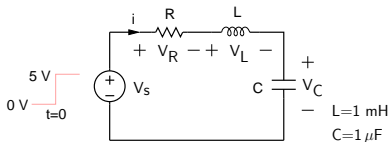- Show that the condition for critically damped response is  $R = 63.2 \Omega$ .
- For  $R = 20 \Omega$ , derive expressions for  $i(t)$  and  $V_L(t)$  for  $t > 0$  (Assume that  $V_C(0^-) = 0V$  and  $i_L(0^-) = 0A$ ). Plot them versus time.
- Repeat (b) for  $R = 100 \Omega$ .



- Show that the condition for critically damped response is  $R = 63.2\ \Omega$ .
- For  $R = 20\ \Omega$ , derive expressions for  $i(t)$  and  $V_L(t)$  for  $t > 0$  (Assume that  $V_C(0^-) = 0\text{ V}$  and  $i_L(0^-) = 0\text{ A}$ ). Plot them versus time.
- Repeat (b) for  $R = 100\ \Omega$ .
- Compare your results with the following plots.  
(SEQUEL file: ee101\_r1c\_2.sqproj)

## Series RLC circuit: home work

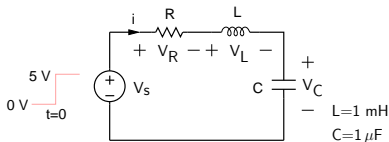

- Show that the condition for critically damped response is  $R = 63.2 \Omega$ .
- For  $R = 20 \Omega$ , derive expressions for  $i(t)$  and  $V_L(t)$  for  $t > 0$  (Assume that  $V_C(0^-) = 0 \text{ V}$  and  $i_L(0^-) = 0 \text{ A}$ ). Plot them versus time.
- Repeat (b) for  $R = 100 \Omega$ .
- Compare your results with the following plots.  
(SEQUEL file: ee101\_r1c\_2.sqproj)

