

Diode Circuits: Part 2





M. B. Patil

mbpatil@ee.iitb.ac.in

www.ee.iitb.ac.in/~sequel

Department of Electrical Engineering
Indian Institute of Technology Bombay

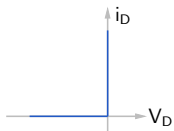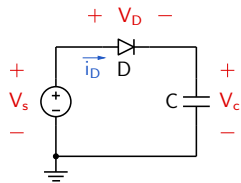Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$






$$V_{on} = 0\text{ V}$$

$$R_{on} \rightarrow 0\ \Omega$$



$$R_{off} \rightarrow \infty\ \Omega$$

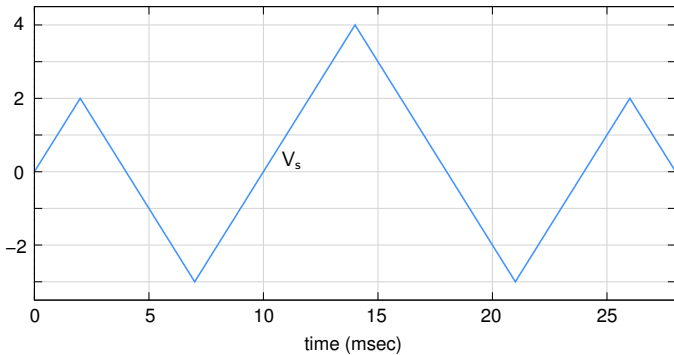

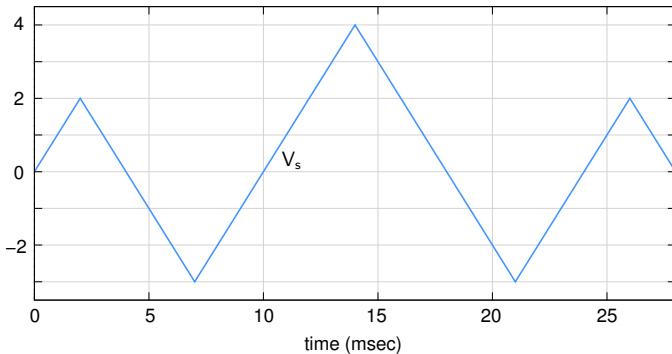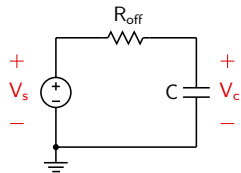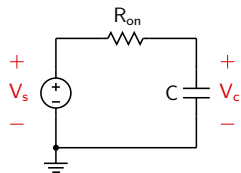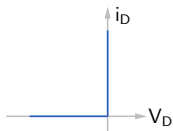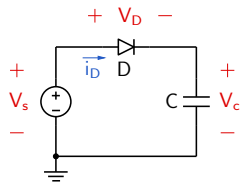Peak detector (with $V_{on} = 0\text{ V}$)



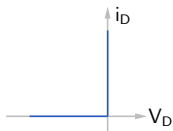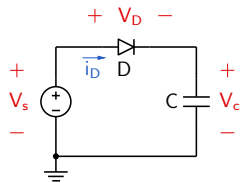Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

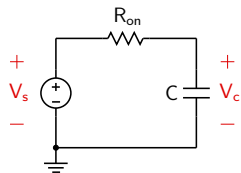


$$V_s > V_c$$

$$\tau = R_{on}C$$


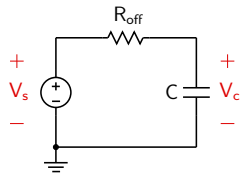


$$V_s < V_c$$

$$\tau = R_{off}C$$

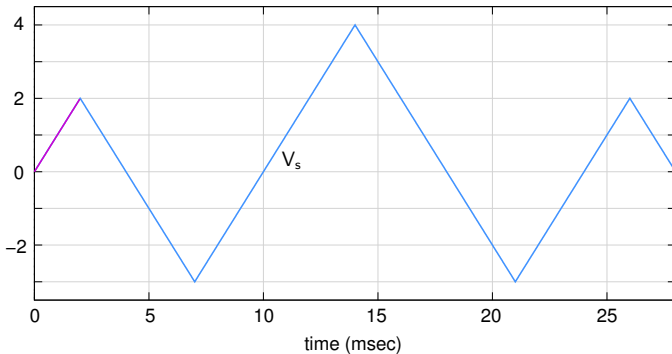

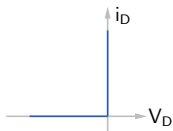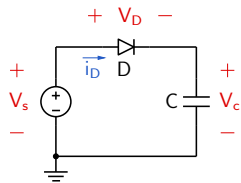Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

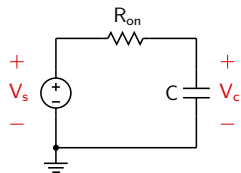


$$V_s > V_c$$

$$\tau = R_{on}C$$


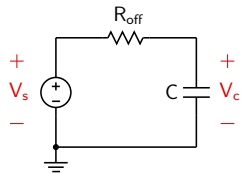


$$V_s < V_c$$

$$\tau = R_{off}C$$

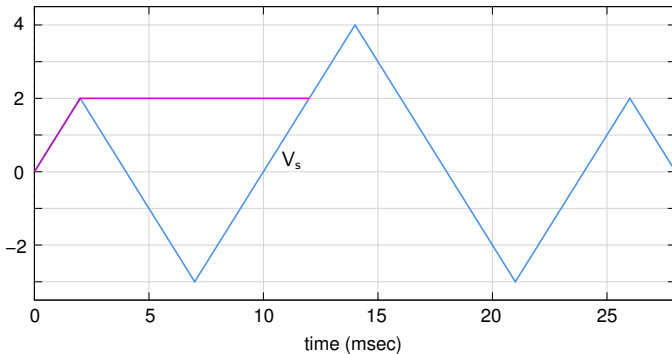

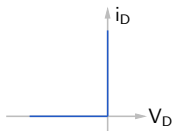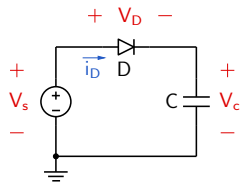Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

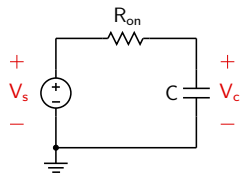


$$V_s > V_c$$

$$\tau = R_{on}C$$





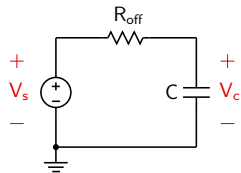


$$V_s < V_c$$



$$\tau = R_{off}C$$

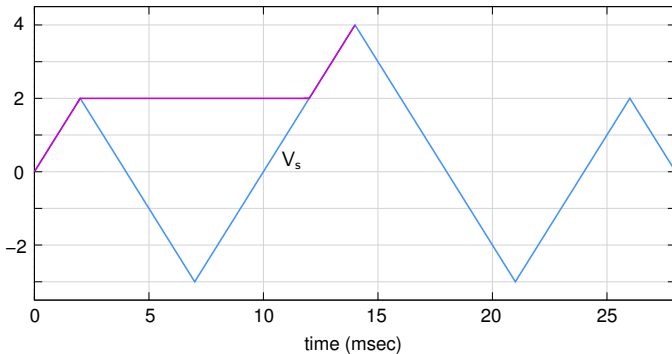

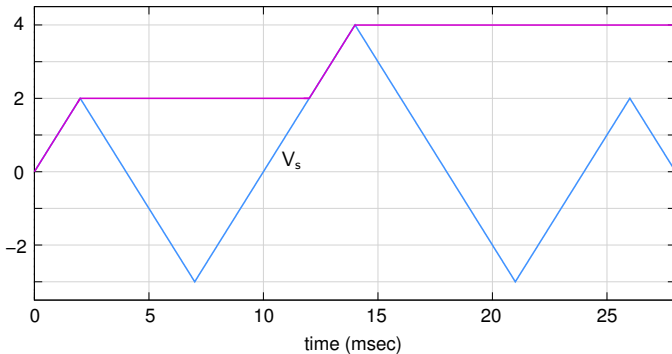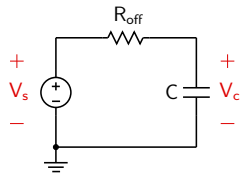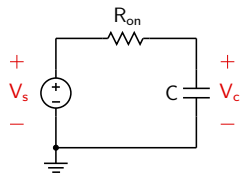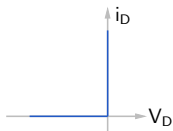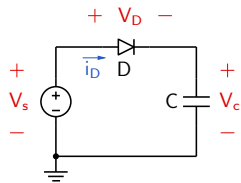Peak detector (with $V_{on} = 0\text{ V}$)



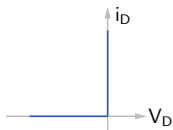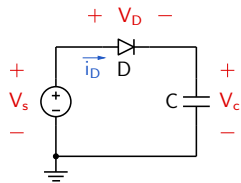Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

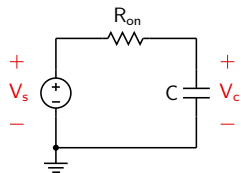


$$V_s > V_c$$

$$\tau = R_{on}C$$


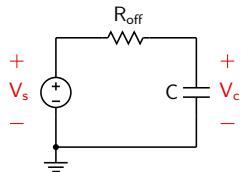


$$V_s < V_c$$

$$\tau = R_{off}C$$

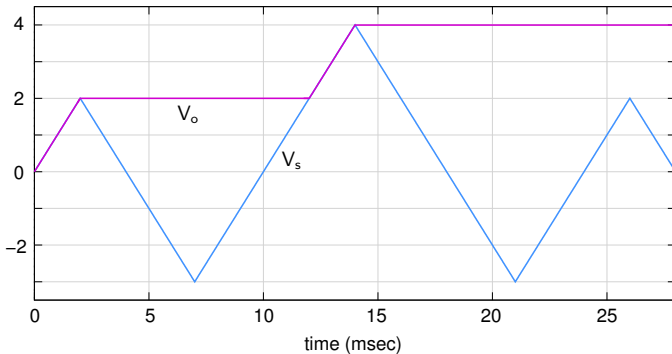

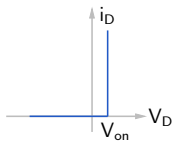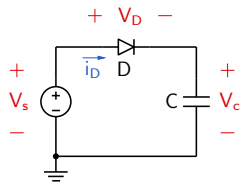Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$



$$V_{on} = 0.7\text{ V}$$

$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

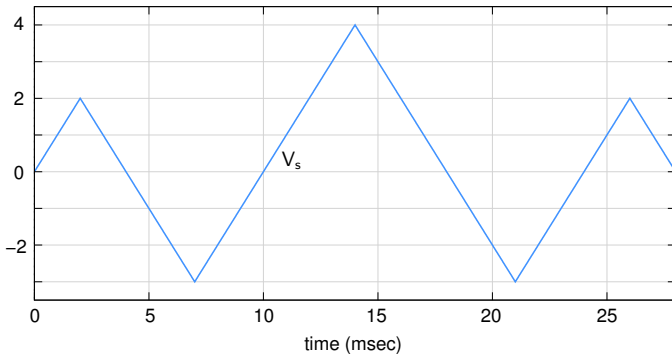

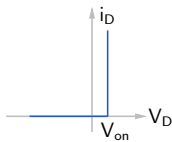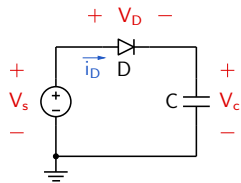Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

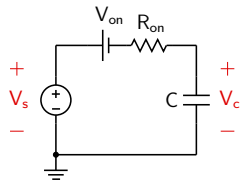


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


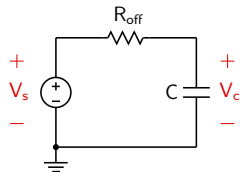


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

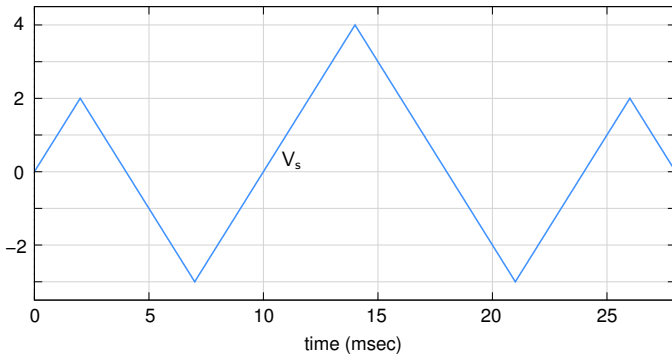

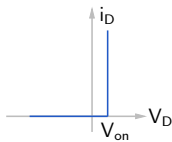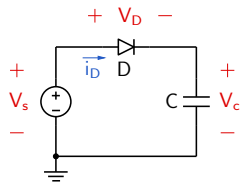Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

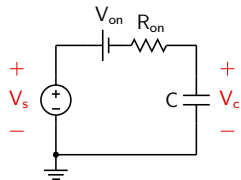


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


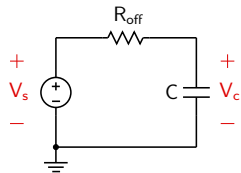


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

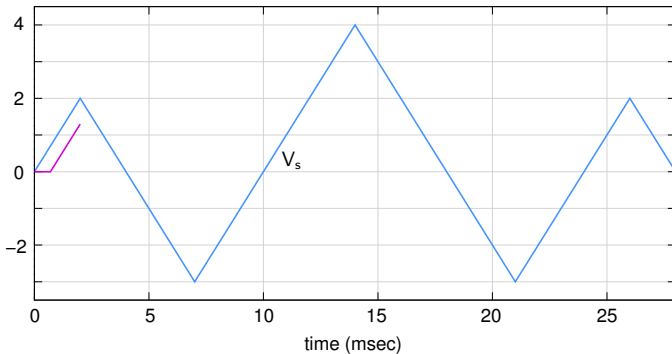

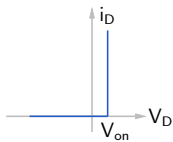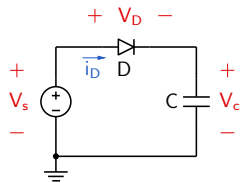Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

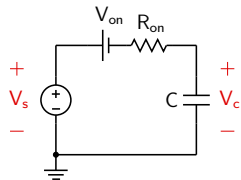


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


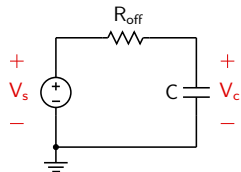


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

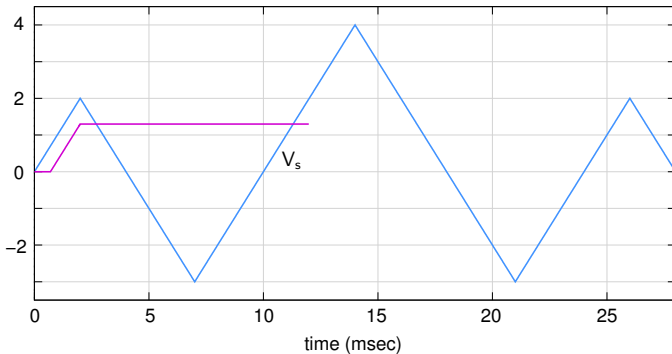

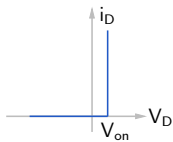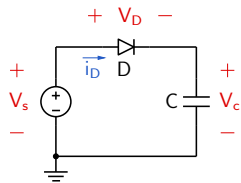Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

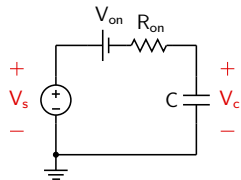


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


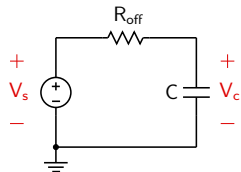


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

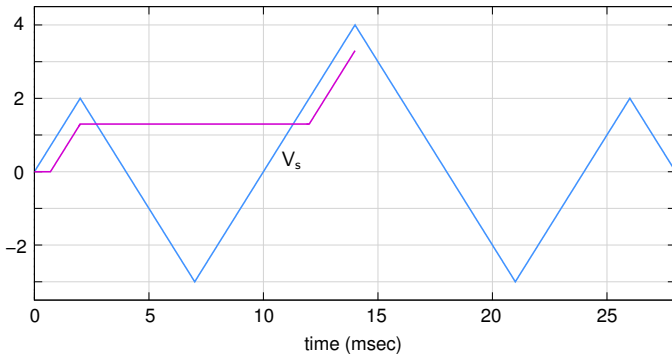

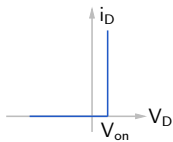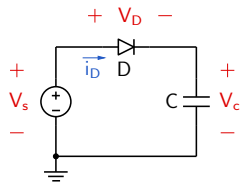Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

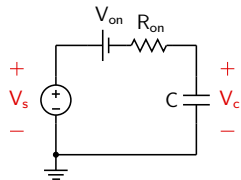


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


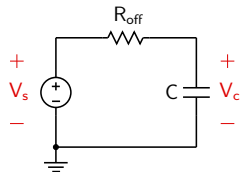


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

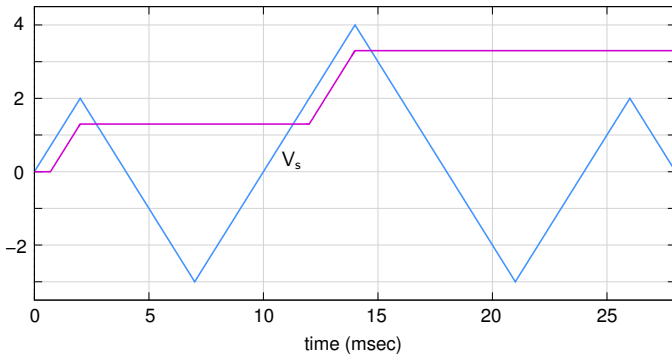

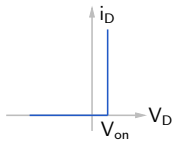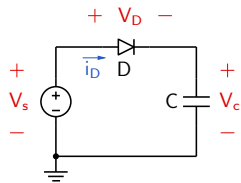Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

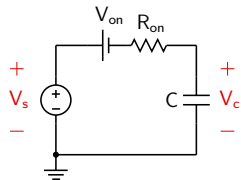


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$

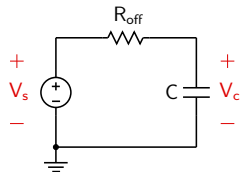


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

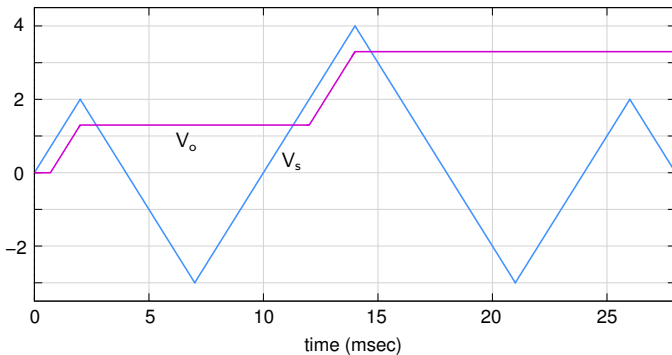


Clamper circuits

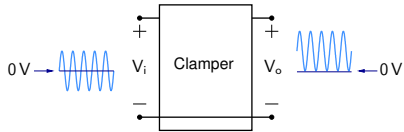


- * A clamper circuit provides a “level shift.” (The shape of the input signal is not altered.)

Clamper circuits

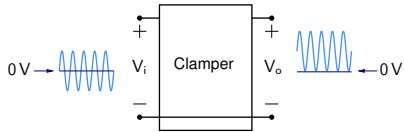



- * A clamper circuit provides a “level shift.” (The shape of the input signal is not altered.)
- * The shift could be positive or negative.

Clamper circuits

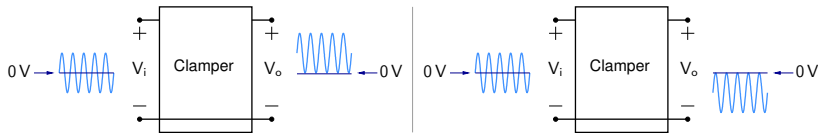

- * A clamper circuit provides a “level shift.” (The shape of the input signal is not altered.)
- * The shift could be positive or negative.

Clamper circuits

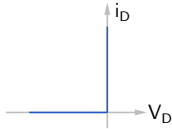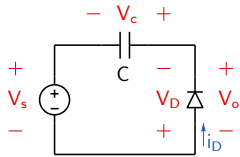


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$



$$V_{on} = 0 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

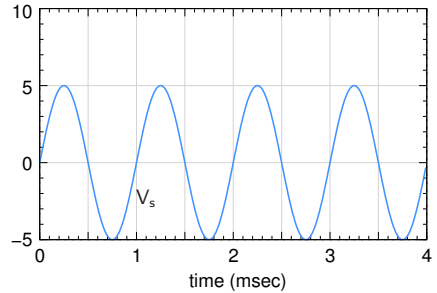

Clamper circuits

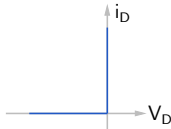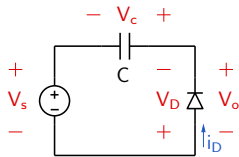


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

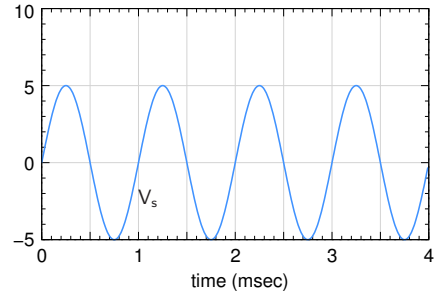

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.

Clamper circuits

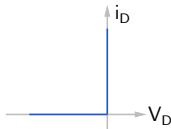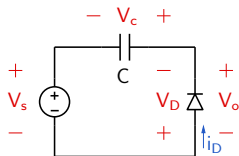


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

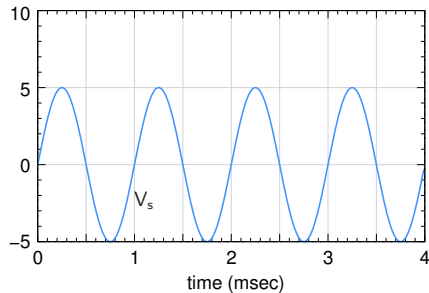

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.

Clamper circuits

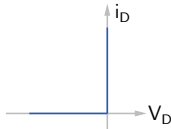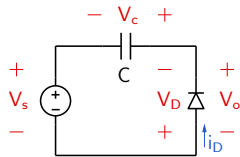


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

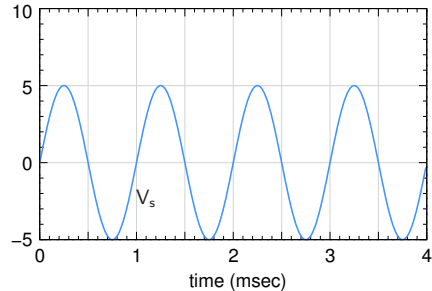

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

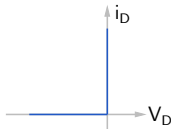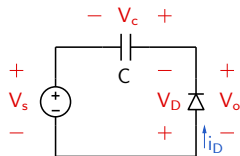


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

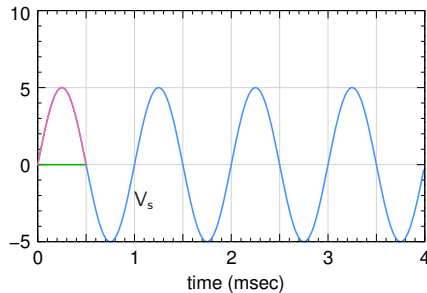

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

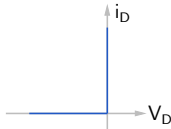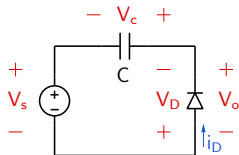


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

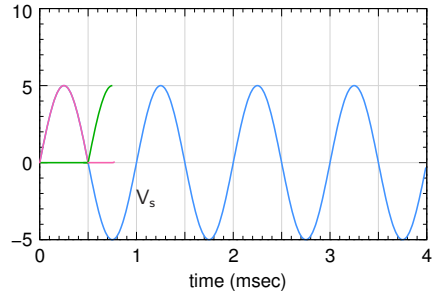

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

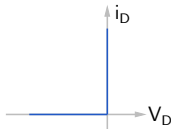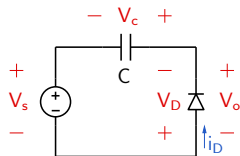


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

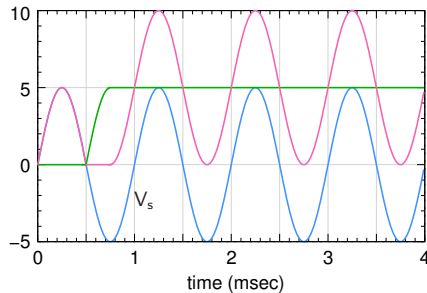

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

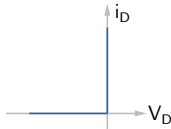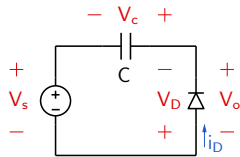


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

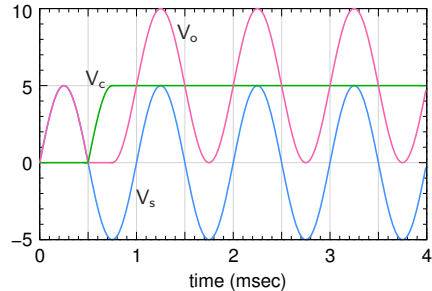

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

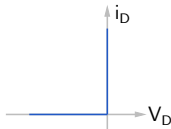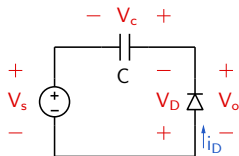


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

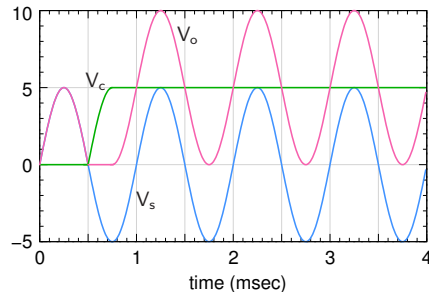

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.
- * Note that we are generally interested only in the steady-state behaviour and not in the transient at the beginning.

Clamper circuits

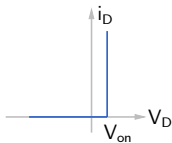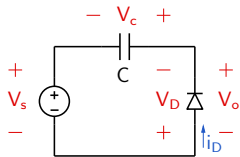


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$



$$V_{on} = 0.7 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

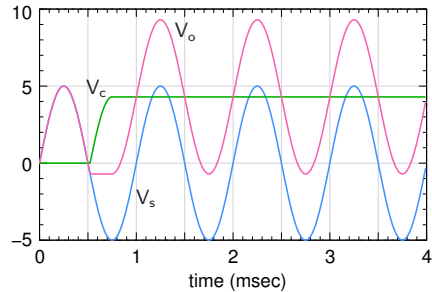

Clamper circuits

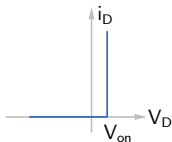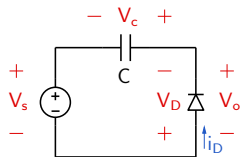


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$


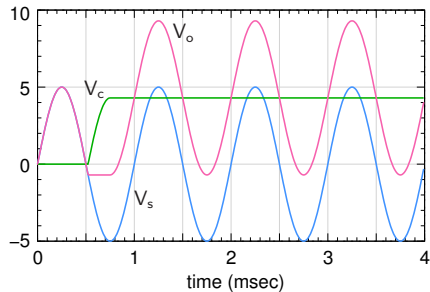


* When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit).

In this phase,

$$V_c + V_s + V_{on} = 0 \rightarrow V_c = -V_s - V_{on}.$$

Clamper circuits

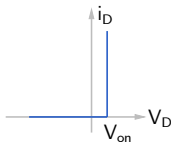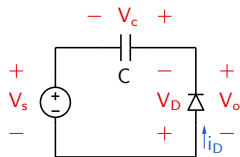


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

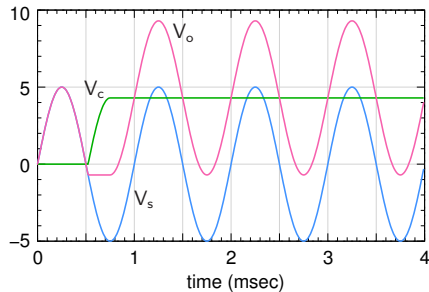

- * When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit).
In this phase,
 $V_c + V_s + V_{on} = 0 \rightarrow V_c = -V_s - V_{on}$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.

Clamper circuits

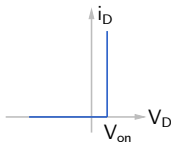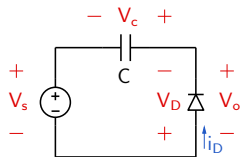


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

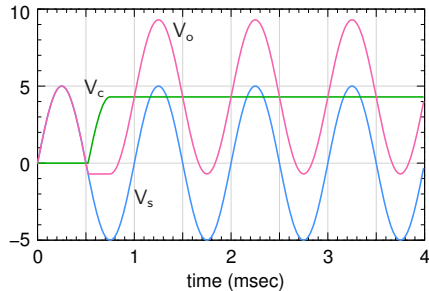

- * When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit). In this phase,
 $V_c + V_s + V_{on} = 0 \rightarrow V_c = -V_s - V_{on}$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value ($V_m - V_{on}$), it cannot change any more. We then have
 $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m - V_{on}$. In this case, V_o gets clamped at -0.7 V .

Clamper circuits

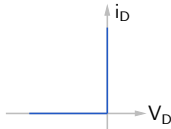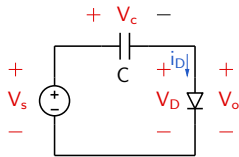


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$



$$V_{on} = 0 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

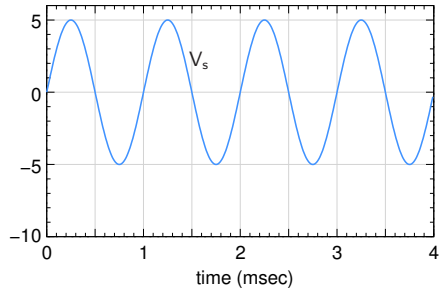

Clamper circuits

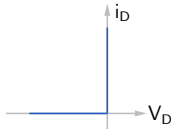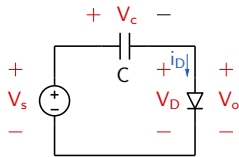


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

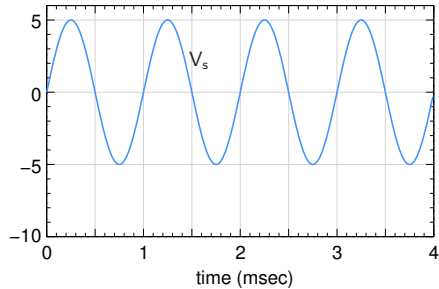

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.

Clamper circuits

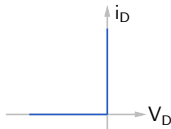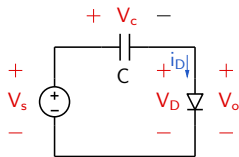


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

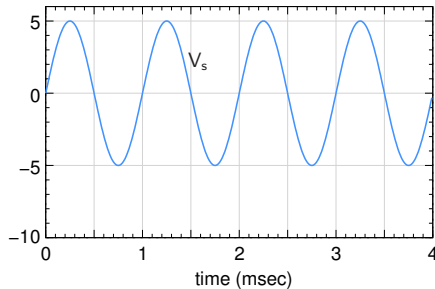

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.

Clamper circuits

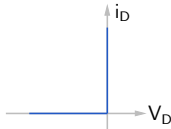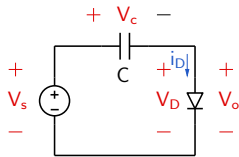


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

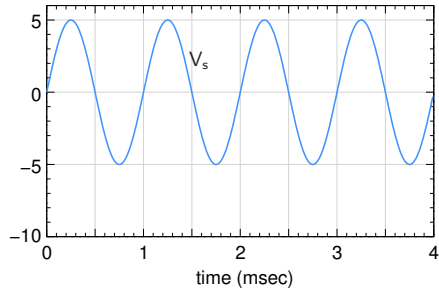

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m$, i.e., a negative level shift.

Clamper circuits

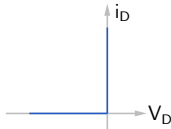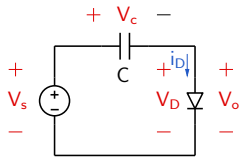


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

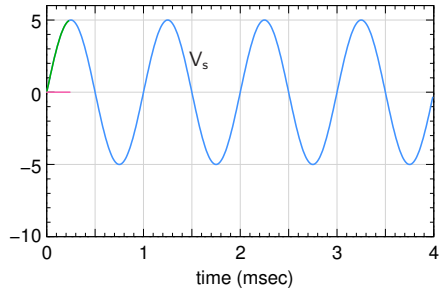

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m$, i.e., a negative level shift.

Clamper circuits

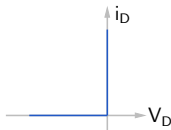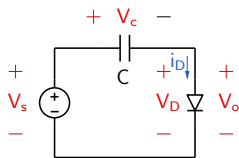


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

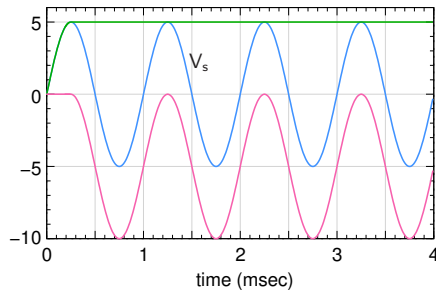

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m$, i.e., a negative level shift.

Clamper circuits

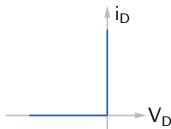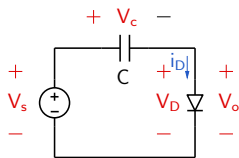


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

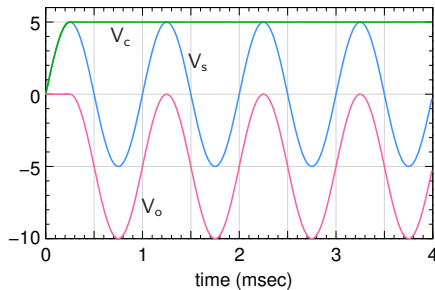

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m$, i.e., a negative level shift.

Clamper circuits

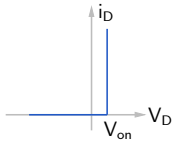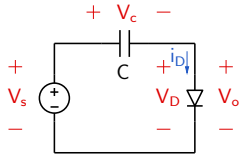


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$



$$V_{on} = 0.7 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

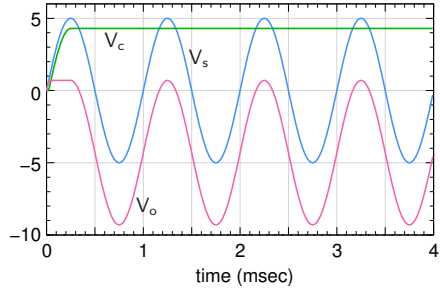

Clamper circuits

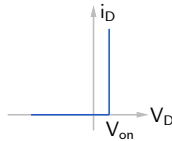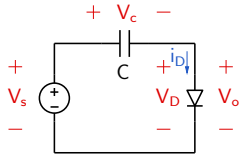


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$


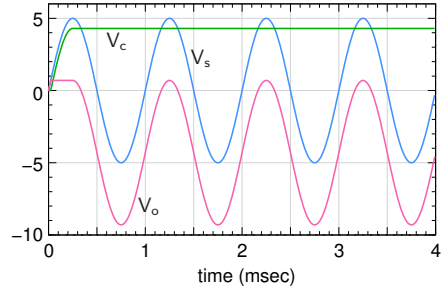


* When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit).

In this phase,

$$V_c + V_{on} - V_s = 0 \rightarrow V_c = V_s - V_{on}.$$

Clamper circuits

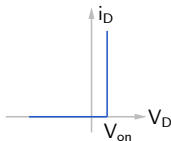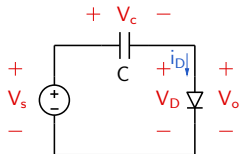


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

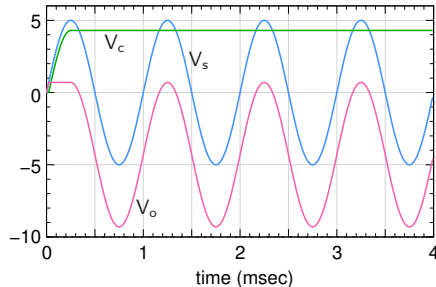

- * When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit). In this phase,
 $V_c + V_{on} - V_s = 0 \rightarrow V_c = V_s - V_{on}$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.

Clamper circuits

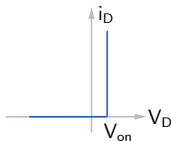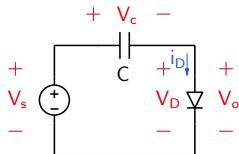


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$


$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

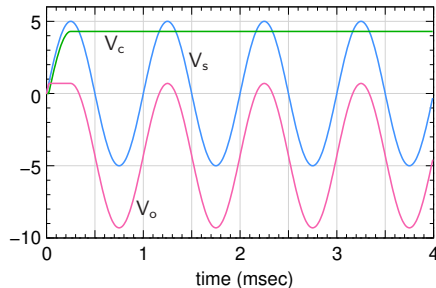


- * When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit). In this phase,
 $V_c + V_{on} - V_s = 0 \rightarrow V_c = V_s - V_{on}$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value ($V_m - V_{on}$), it cannot change any more. We then have $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m + V_{on}$. In this case, V_o gets clamped at 0.7 V .

Voltage doubler (peak-to-peak detector)

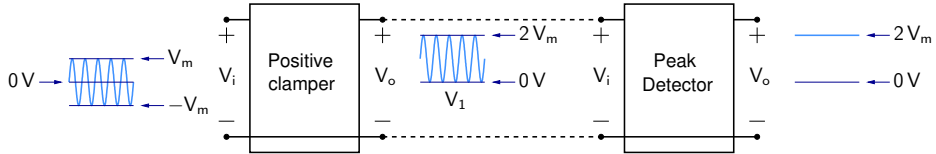


Voltage doubler (peak-to-peak detector)

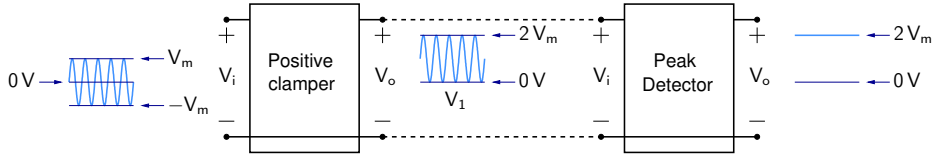


* Input voltage: $-V_m$ to V_m

Voltage doubler (peak-to-peak detector)

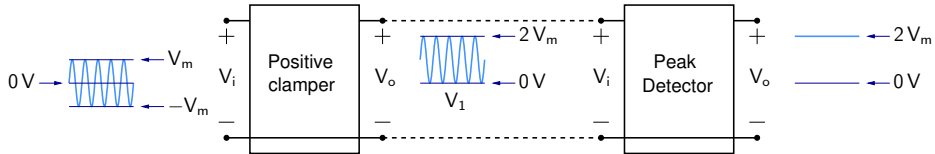



- * Input voltage: $-V_m$ to V_m
- * Output of positive clamper (V_1): 0 to $2V_m$

Voltage doubler (peak-to-peak detector)



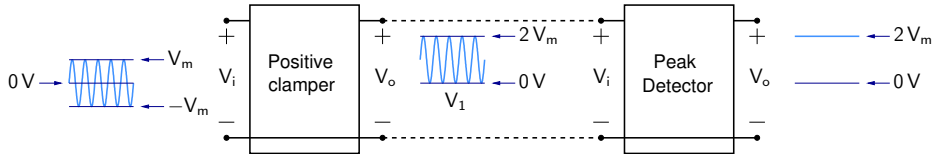


- * Input voltage: $-V_m$ to V_m
- * Output of positive clamper (V_1): 0 to $2V_m$
- * The peak detector detects the peak of $V_1(t)$, i.e., $2V_m$ (dc).




Voltage doubler (peak-to-peak detector)

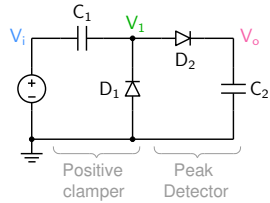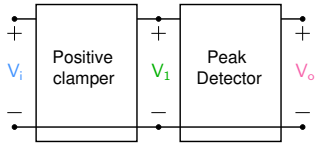



Voltage doubler (peak-to-peak detector)

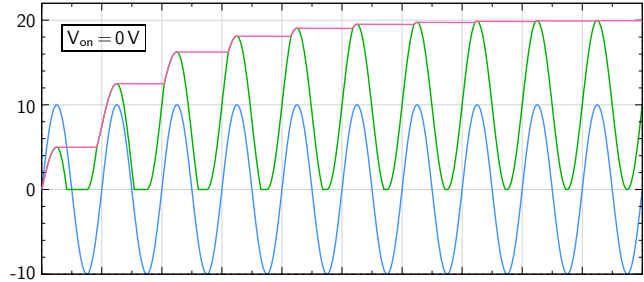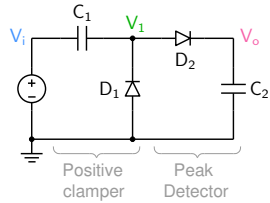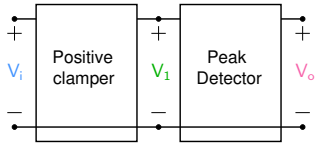


Voltage doubler (peak-to-peak detector)

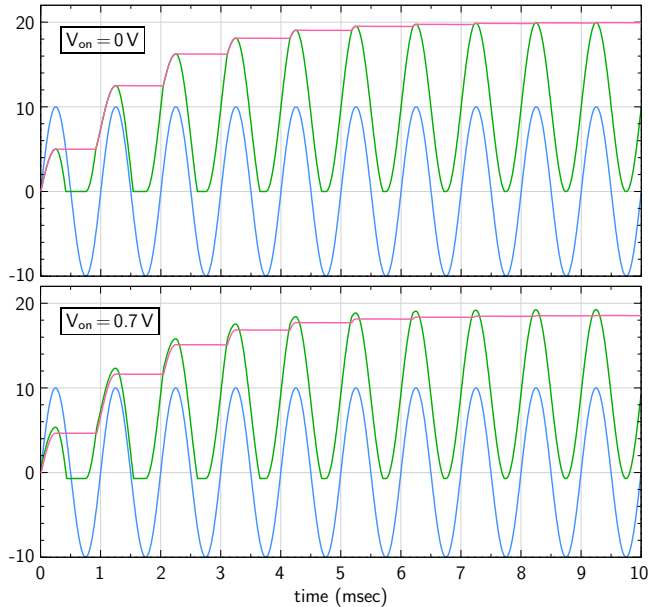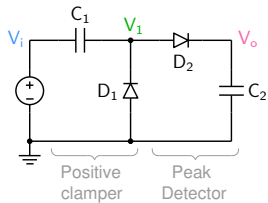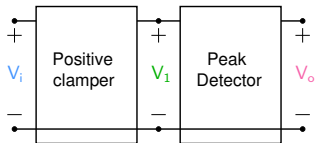


Voltage doubler (peak-to-peak detector)

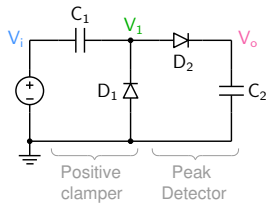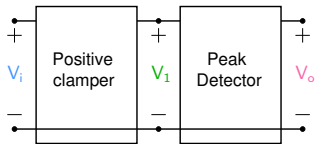


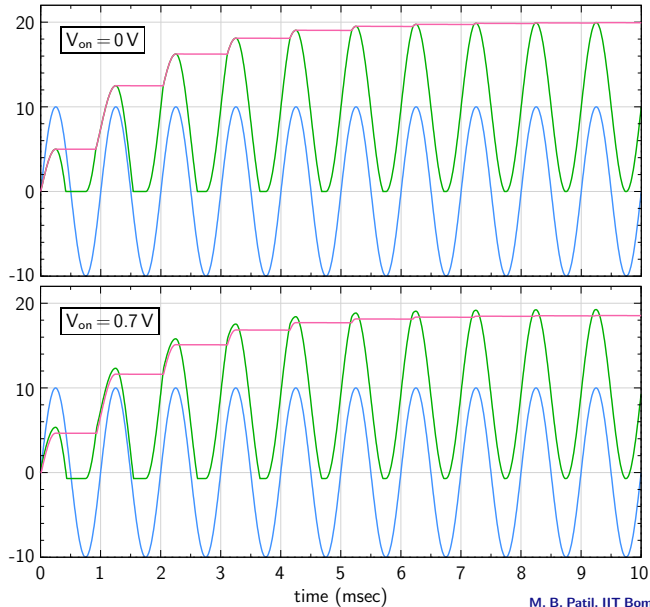
SEQUEL file: ee101_voltage_doubler.sqproj




Diode circuit example

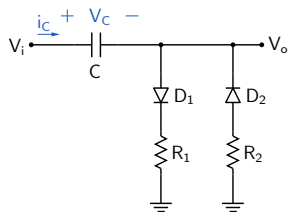

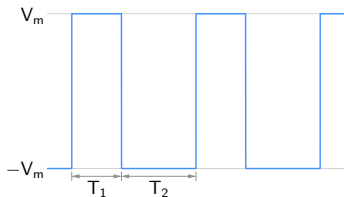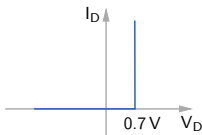Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.





Diode circuit example


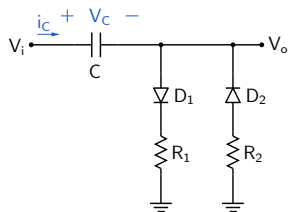


Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.

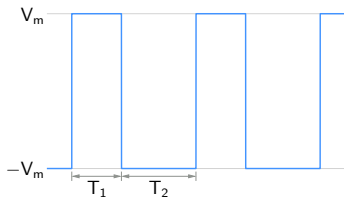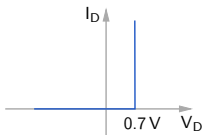* Charging time constant $\tau_1 = R_1 C$.




Diode circuit example

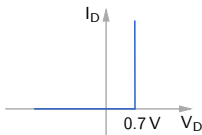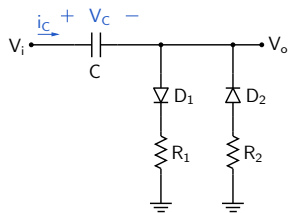


Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.

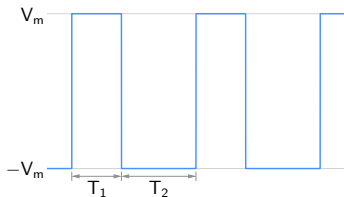- * Charging time constant $\tau_1 = R_1 C$.
- * Discharging time constant $\tau_2 = R_2 C$.




Diode circuit example

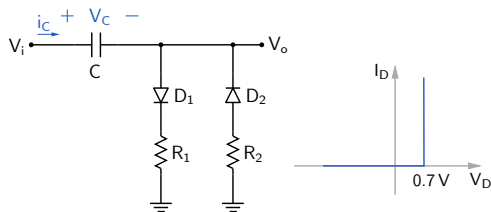


Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.

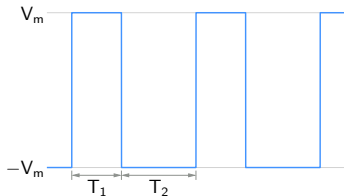- * Charging time constant $\tau_1 = R_1 C$.
- * Discharging time constant $\tau_2 = R_2 C$.
- * Since $\tau_1 \gg T$ and $\tau_2 \gg T$, we expect V_C to be nearly constant in steady state, i.e., $V_C(t) \approx \text{constant} \equiv V_C^0$.




Diode circuit example

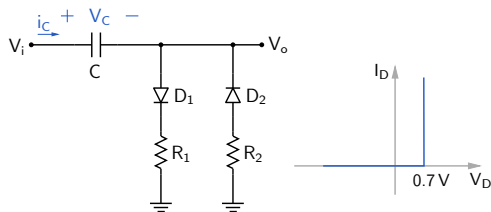


Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.

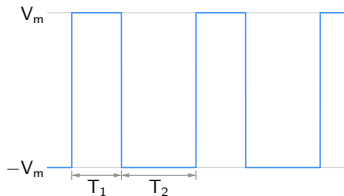- * Charging time constant $\tau_1 = R_1 C$.
- * Discharging time constant $\tau_2 = R_2 C$.
- * Since $\tau_1 \gg T$ and $\tau_2 \gg T$, we expect V_C to be nearly constant in steady state, i.e., $V_C(t) \approx \text{constant} \equiv V_C^0$.
- * $V_o(t) = V_i(t) - V_C(t) \approx V_i(t) - V_C^0$.




Diode circuit example




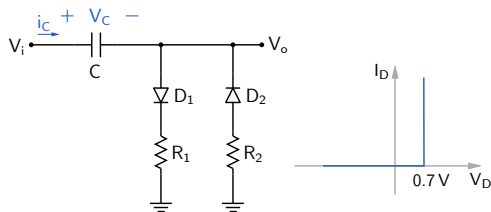







Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.




- * Charging time constant $\tau_1 = R_1 C$.
- * Discharging time constant $\tau_2 = R_2 C$.
- * Since $\tau_1 \gg T$ and $\tau_2 \gg T$, we expect V_C to be nearly constant in steady state, i.e., $V_C(t) \approx \text{constant} \equiv V_C^0$.
- * $V_o(t) = V_i(t) - V_C(t) \approx V_i(t) - V_C^0$.

Let us look at an example.



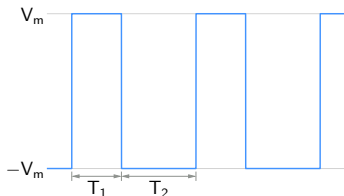


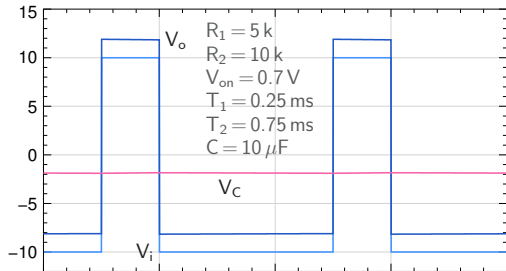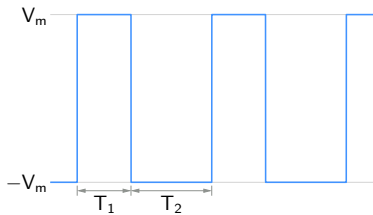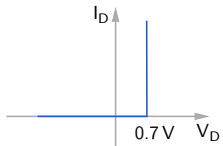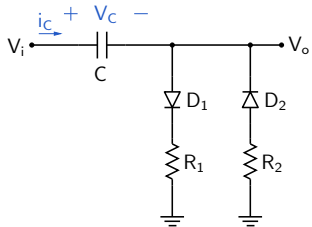

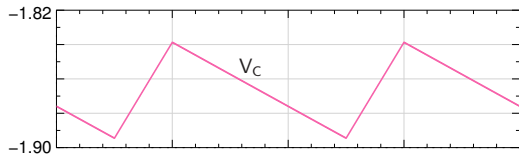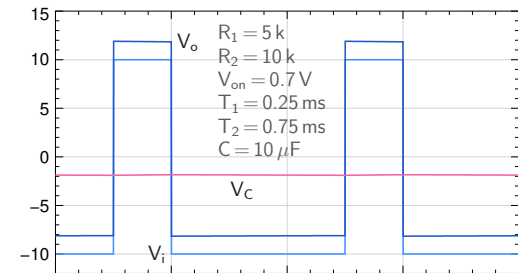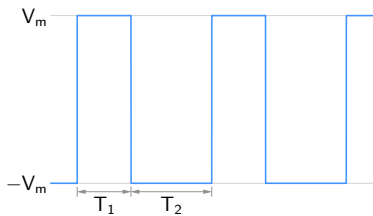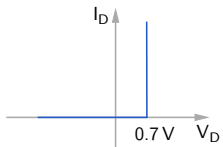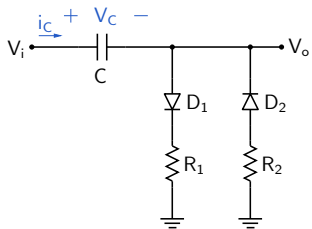


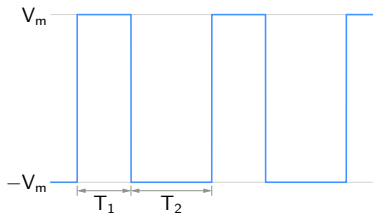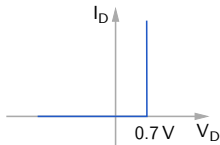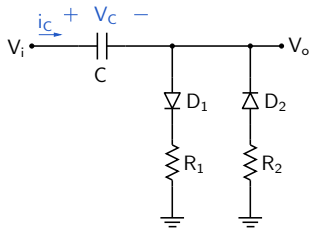

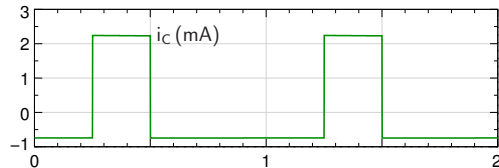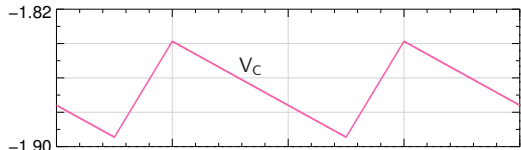
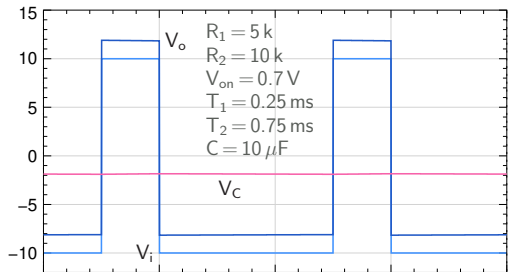
SEQUEL file:
ee101_diode_circuit_13.sqproj





Time (msec)

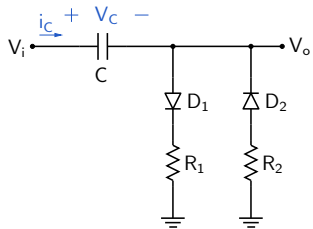


Charge conservation:

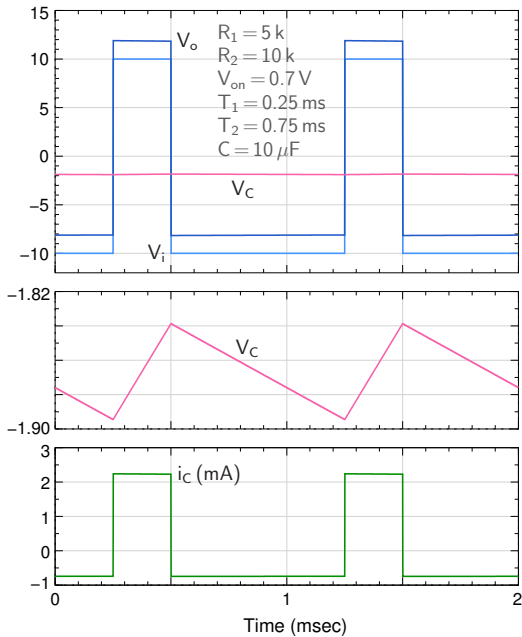
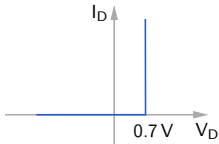


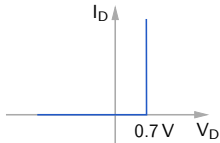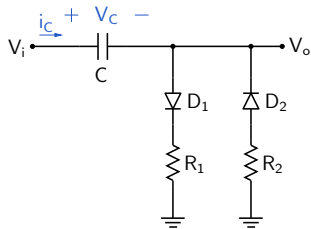

Charge conservation:
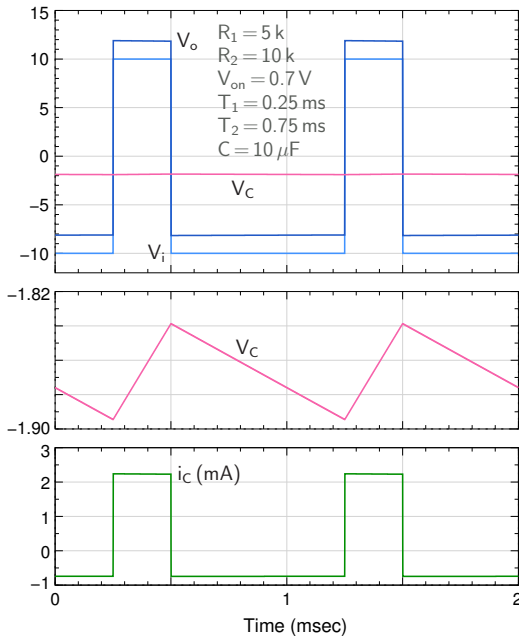
$$\Delta Q = \int_0^T i_C dt = \int_0^{T_1} i_C dt + \int_{T_1}^{T_1+T_2} i_C dt = 0.$$




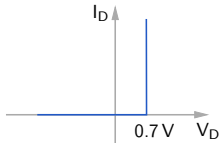
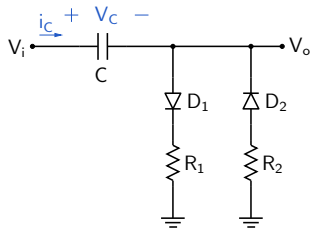


Charge conservation:

$$\Delta Q = \int_0^T i_C dt = \int_0^{T_1} i_C dt + \int_{T_1}^{T_1+T_2} i_C dt = 0.$$
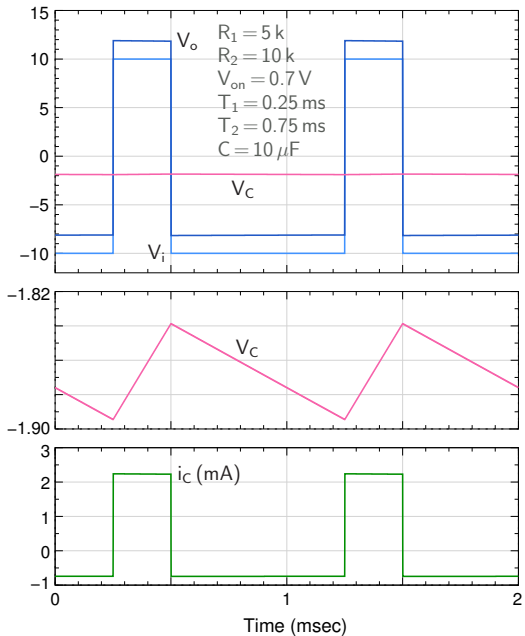
$$T_1 \left(\frac{V_m - V_C - V_{on}}{R_1} \right) - T_2 \left(\frac{0 - (-V_m - V_C) - V_{on}}{R_2} \right) = 0.$$



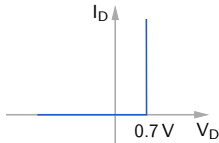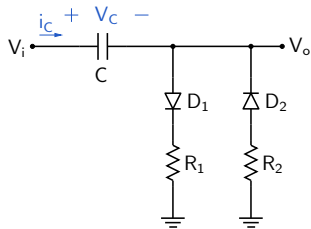




Charge conservation:

$$\Delta Q = \int_0^T i_C dt = \int_0^{T_1} i_C dt + \int_{T_1}^{T_1+T_2} i_C dt = 0.$$

$$T_1 \left(\frac{V_m - V_C - V_{on}}{R_1} \right) - T_2 \left(\frac{0 - (-V_m - V_C) - V_{on}}{R_2} \right) = 0.$$
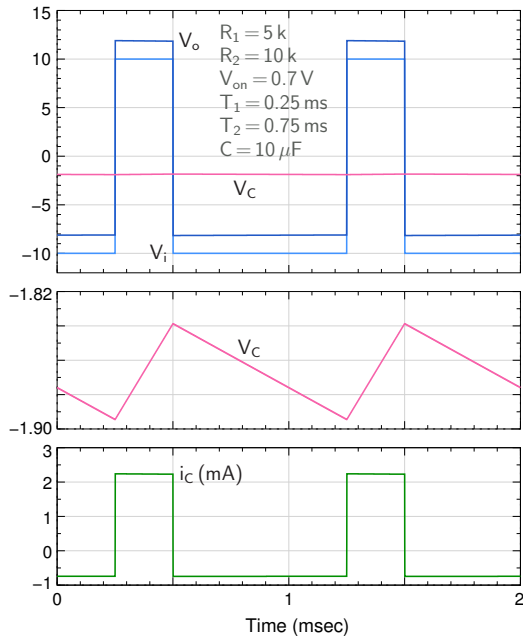
$$\left(\frac{T_1}{R_1} - \frac{T_2}{R_2} \right) (V_m - V_{on}) = V_C \left(\frac{T_1}{R_1} + \frac{T_2}{R_2} \right).$$



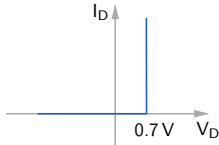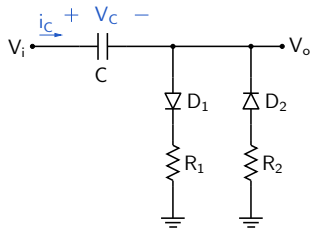


Charge conservation:

$$\Delta Q = \int_0^T i_C dt = \int_0^{T_1} i_C dt + \int_{T_1}^{T_1+T_2} i_C dt = 0.$$

$$T_1 \left(\frac{V_m - V_C - V_{on}}{R_1} \right) - T_2 \left(\frac{0 - (-V_m - V_C) - V_{on}}{R_2} \right) = 0.$$

$$\left(\frac{T_1}{R_1} - \frac{T_2}{R_2} \right) (V_m - V_{on}) = V_C \left(\frac{T_1}{R_1} + \frac{T_2}{R_2} \right).$$

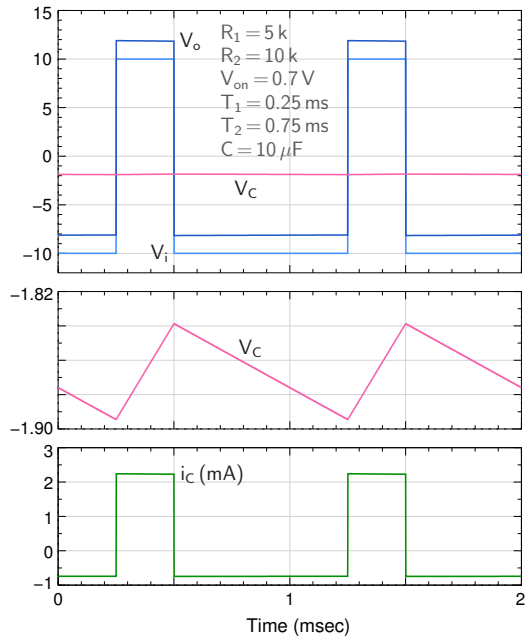
$$\rightarrow V_C = \frac{\left(\frac{T_1}{R_1} - \frac{T_2}{R_2} \right)}{\left(\frac{T_1}{R_1} + \frac{T_2}{R_2} \right)} (V_m - V_{on}) = -1.86 \text{ V}.$$



- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

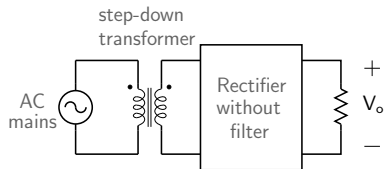


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

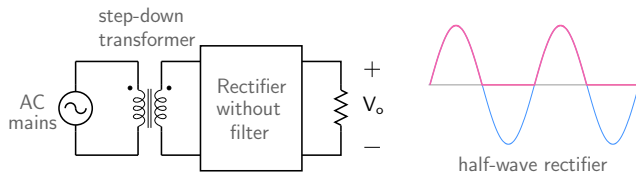



- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

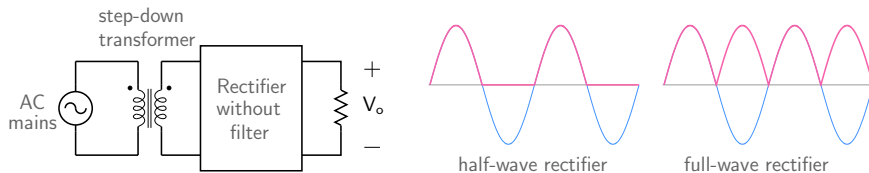


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

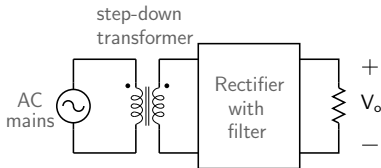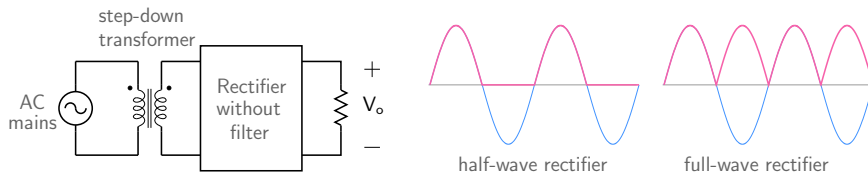


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

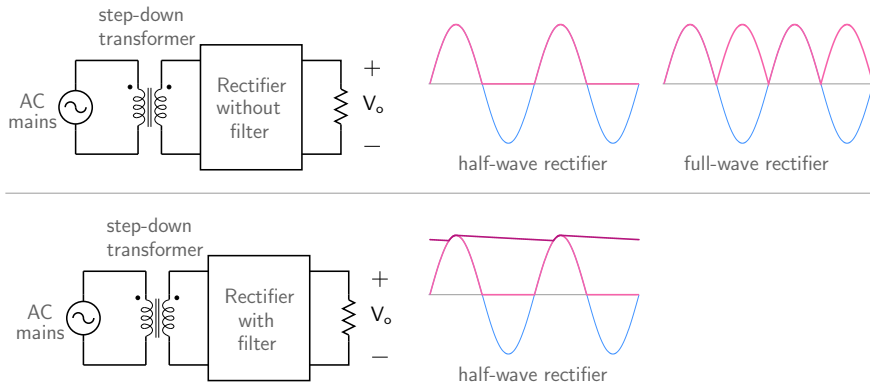


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

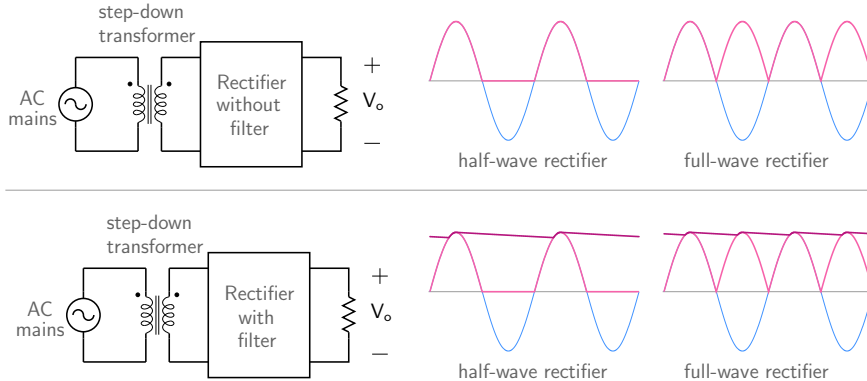




- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers



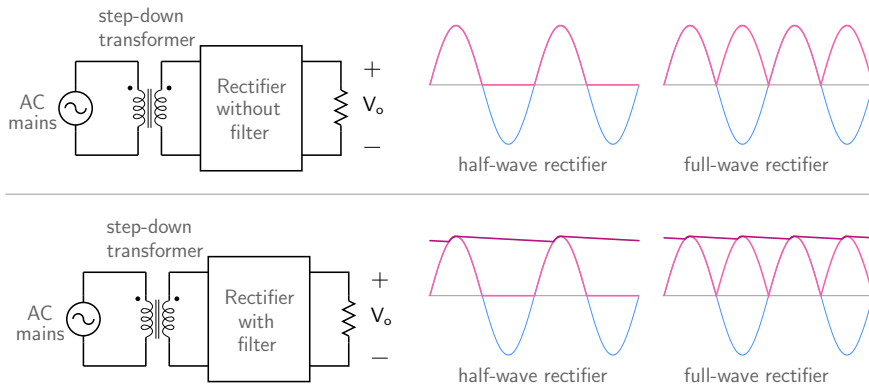


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains → step-down transformer → DC voltage OR
AC mains → DC voltage → lower DC voltage
- * A voltage regulator would be typically used to remove the ripple riding on the DC output.

Half-wave rectifier without filter

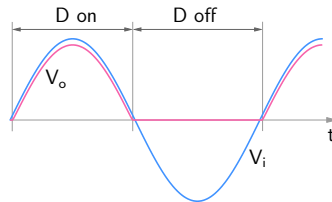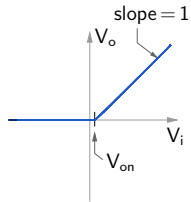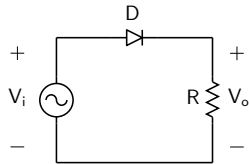


Half-wave rectifier without filter

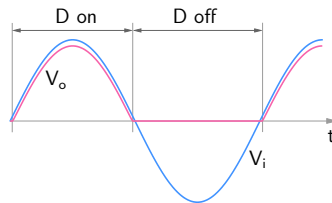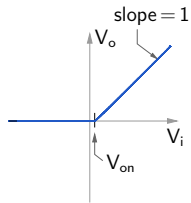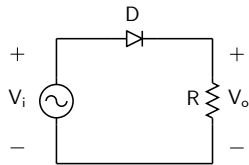


* D conducts only if $V_i > V_{on}$, and in that case $V_o = V_i - V_{on}$, a straight line with slope = 1.

Half-wave rectifier without filter


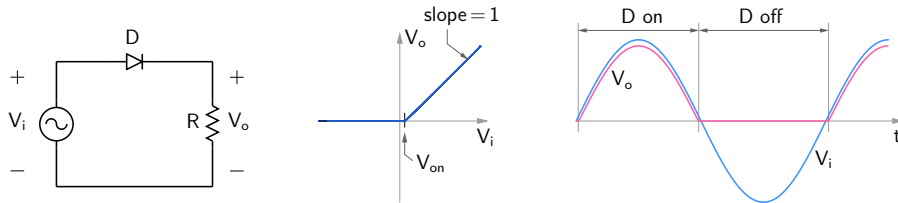


- * D conducts only if $V_i > V_{on}$, and in that case $V_o = V_i - V_{on}$, a straight line with slope = 1.
- * If $V_i < V_{on}$, D does not conduct $\rightarrow V_o = 0$.


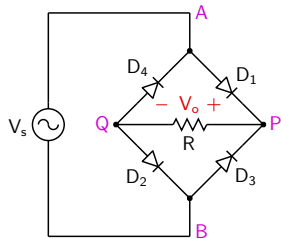
Full-wave (bridge) rectifier without filter




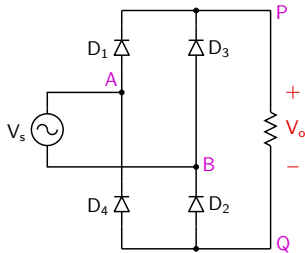
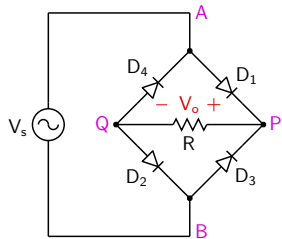
Full-wave (bridge) rectifier without filter





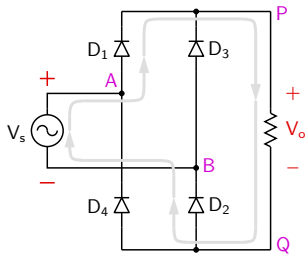
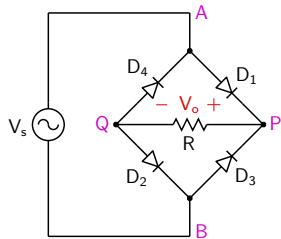
Full-wave (bridge) rectifier without filter



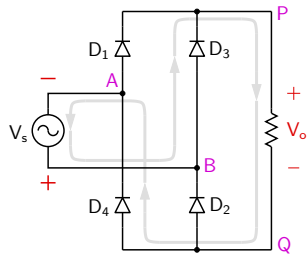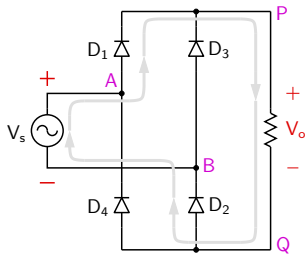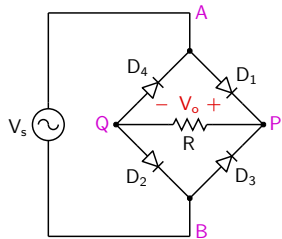
Full-wave (bridge) rectifier without filter



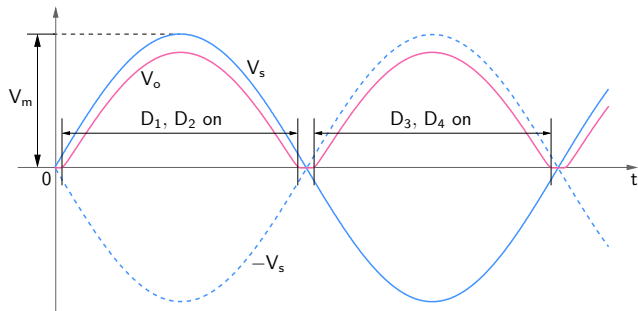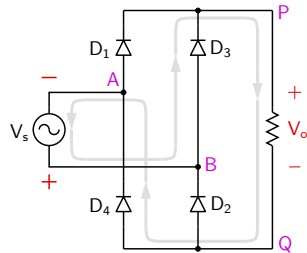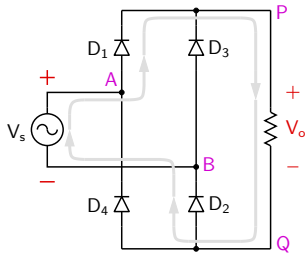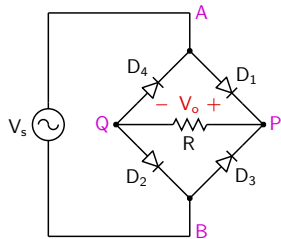
Full-wave (bridge) rectifier without filter



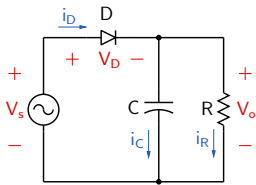Half-wave rectifier with capacitor filter




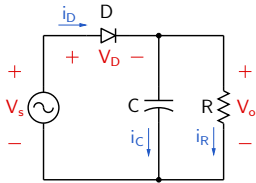Half-wave rectifier with capacitor filter




- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.

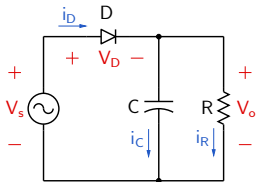
Half-wave rectifier with capacitor filter



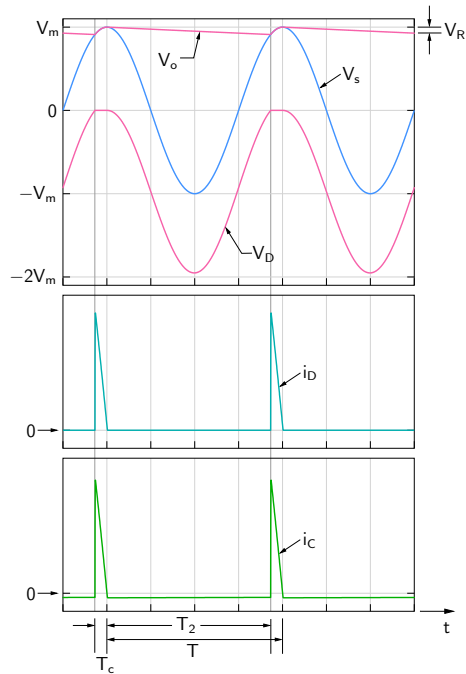
- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.



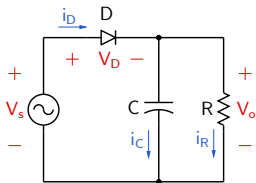
Half-wave rectifier with capacitor filter



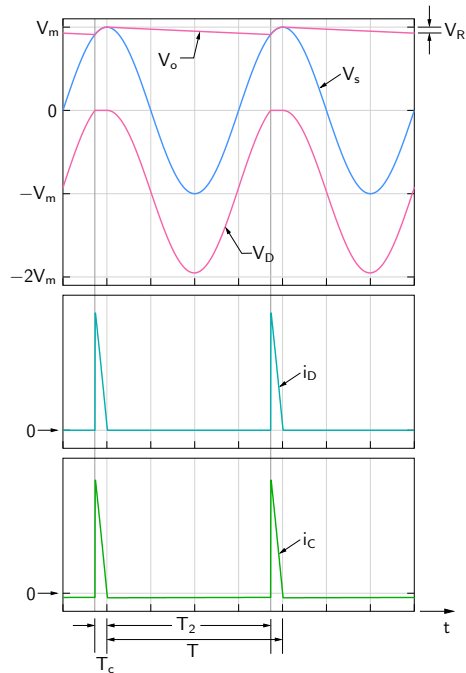
- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"



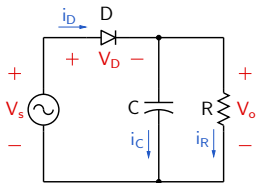
Half-wave rectifier with capacitor filter



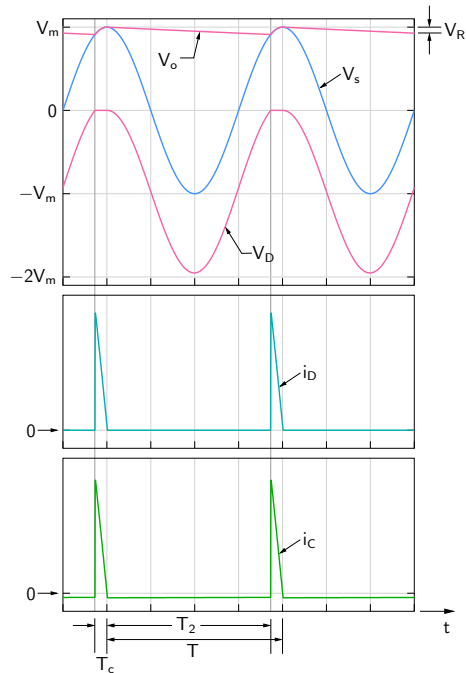
- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"
- * The peak diode current is much larger than the average load current.



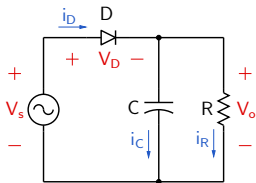
Half-wave rectifier with capacitor filter




- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"
- * The peak diode current is much larger than the average load current.
- * $V_D(t) = V_s(t) - V_o(t) \approx V_s(t) - V_m$
 \rightarrow The maximum reverse bias ("Peak Inverse Voltage" or PIV) across the diode is $2 V_m$.

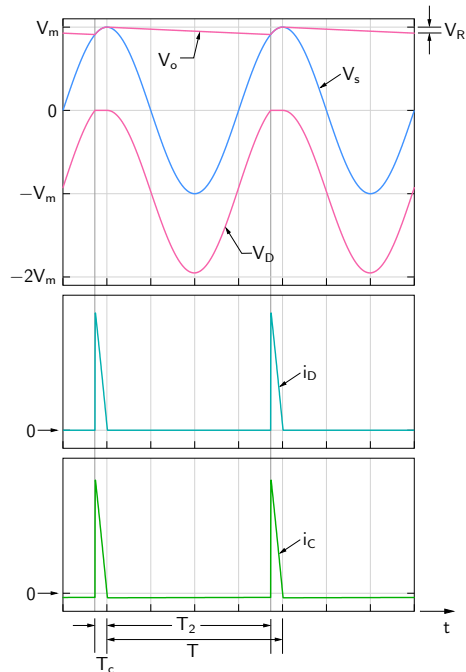

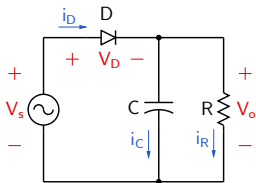
Half-wave rectifier with capacitor filter




- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"
- * The peak diode current is much larger than the average load current.
- * $V_D(t) = V_s(t) - V_o(t) \approx V_s(t) - V_m$
 \rightarrow The maximum reverse bias ("Peak Inverse Voltage" or PIV) across the diode is $2V_m$.
- * With $V_{on} = 0.7\text{ V}$, the plots are slightly different.

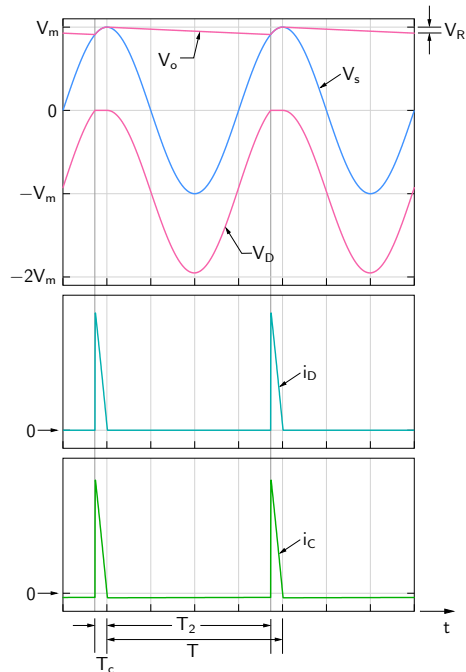

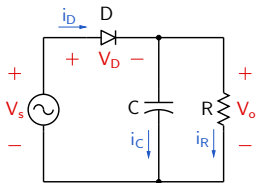
Half-wave rectifier with capacitor filter




- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"
- * The peak diode current is much larger than the average load current.
- * $V_D(t) = V_s(t) - V_o(t) \approx V_s(t) - V_m$
 \rightarrow The maximum reverse bias ("Peak Inverse Voltage" or PIV) across the diode is $2 V_m$.
- * With $V_{on} = 0.7 \text{ V}$, the plots are slightly different.

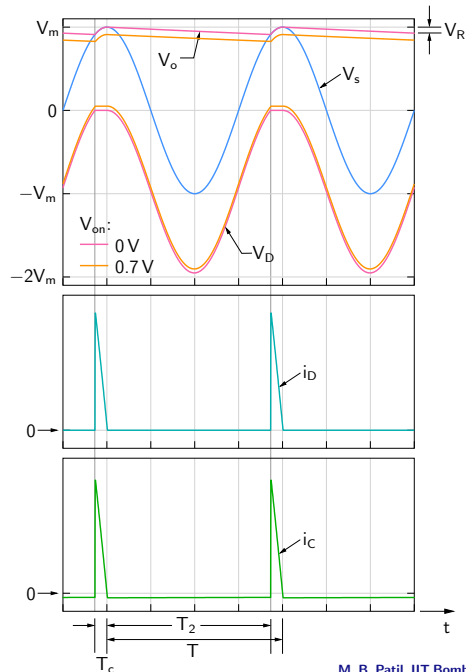

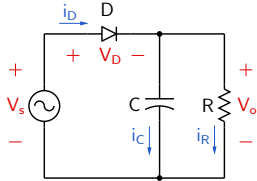
Half-wave rectifier with capacitor filter



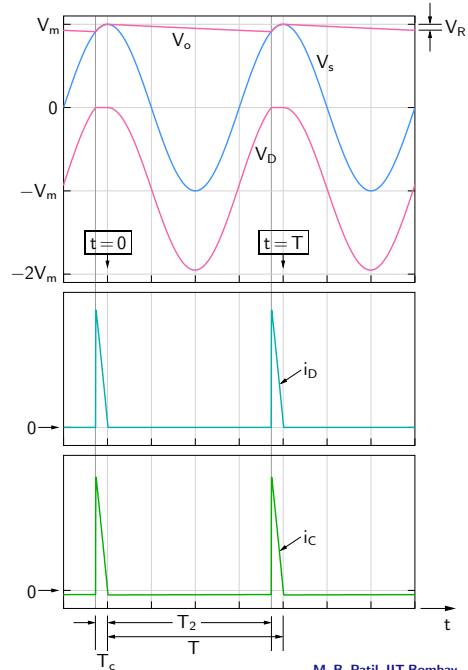$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)



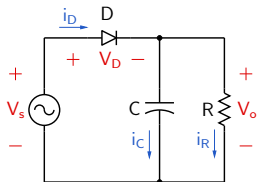Half-wave rectifier with capacitor filter




$V_m = 16 \text{ V}$, $f = 50 \text{ Hz}$, $R = 100 \Omega$. For a ripple voltage $V_R = 2 \text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0 \text{ V}$.)


(a) Filter Capacitance

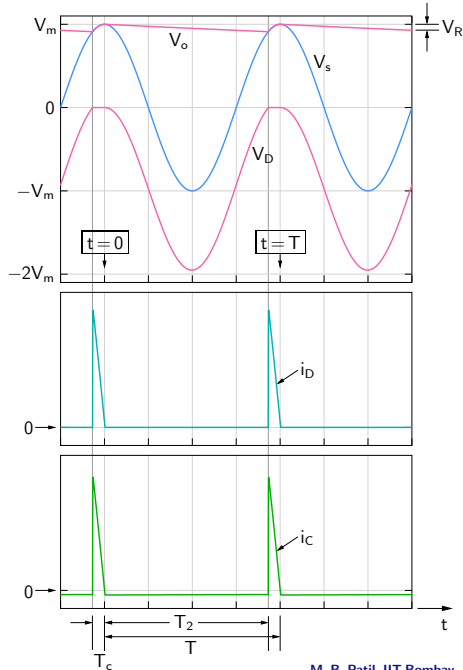1. In the discharge phase,

$$V_o(t) = V_m e^{-t/\tau} \approx V_m \left(1 - \frac{t}{\tau} \right).$$



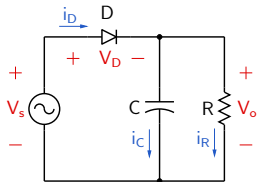Half-wave rectifier with capacitor filter



$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)

(a) Filter Capacitance


1. In the discharge phase,

$$V_o(t) = V_m e^{-t/\tau} \approx V_m \left(1 - \frac{t}{\tau}\right).$$



The drop in $V_o(t)$ is given by the second term.

Using $T_2 \approx T$,

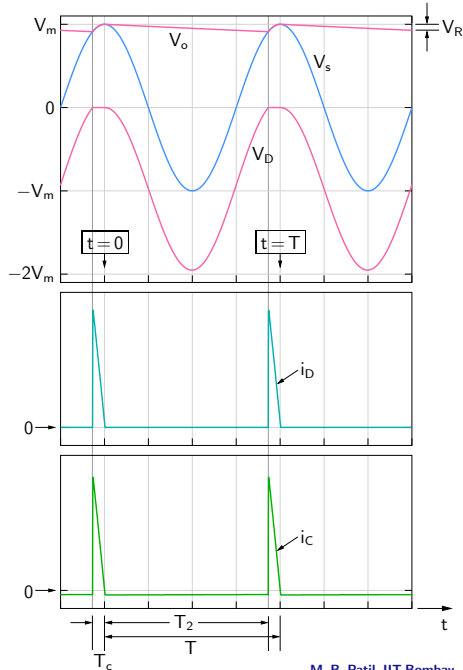
$$V_R = V_m \frac{T}{\tau} = V_m \frac{T}{RC}.$$



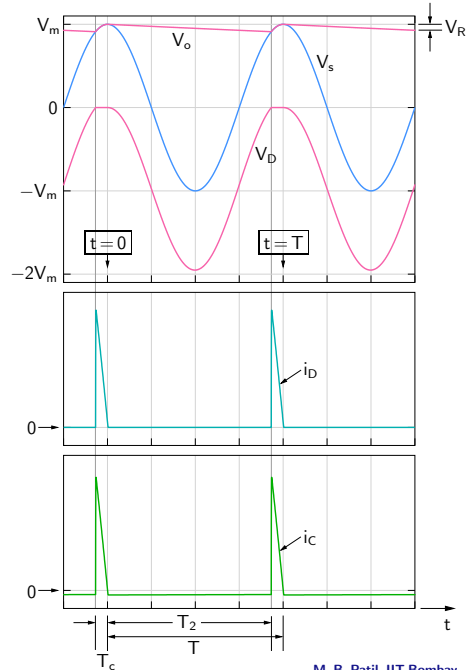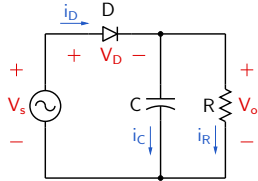Half-wave rectifier with capacitor filter



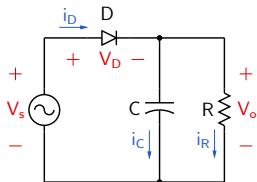
Half-wave rectifier with capacitor filter




(a) Filter capacitance

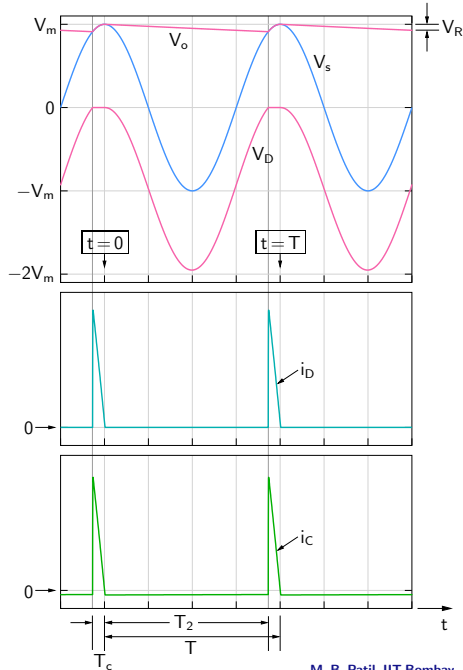2. Assuming $i_C = i_R = \frac{V_o}{R} \approx \frac{V_m}{R}$ in the discharge phase, we get

$$i_C = \frac{V_m}{R} = C \frac{\Delta V_o}{\Delta t} \approx C \frac{V_R}{T} \rightarrow V_R = V_m \frac{T}{RC}.$$



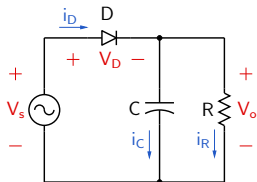Half-wave rectifier with capacitor filter




(a) Filter capacitance

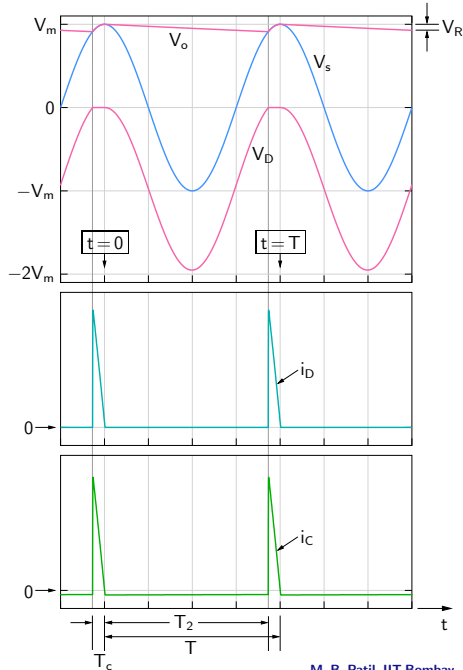
2. Assuming $i_C = i_R = \frac{V_o}{R} \approx \frac{V_m}{R}$ in the discharge phase, we get

$$i_C = \frac{V_m}{R} = C \frac{\Delta V_o}{\Delta t} \approx C \frac{V_R}{T} \rightarrow V_R = V_m \frac{T}{RC}.$$


$$\rightarrow C = \frac{V_m}{V_R} \frac{T}{R} = \frac{16 \text{ V}}{2 \text{ V}} \frac{20 \text{ ms}}{100 \Omega} = 1600 \mu\text{F}.$$



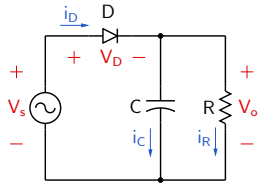
Half-wave rectifier with capacitor filter



(b) Average diode current

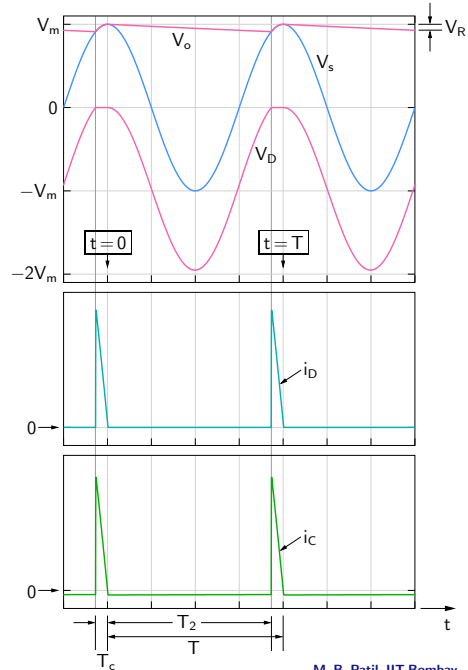

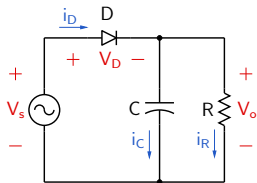
Half-wave rectifier with capacitor filter



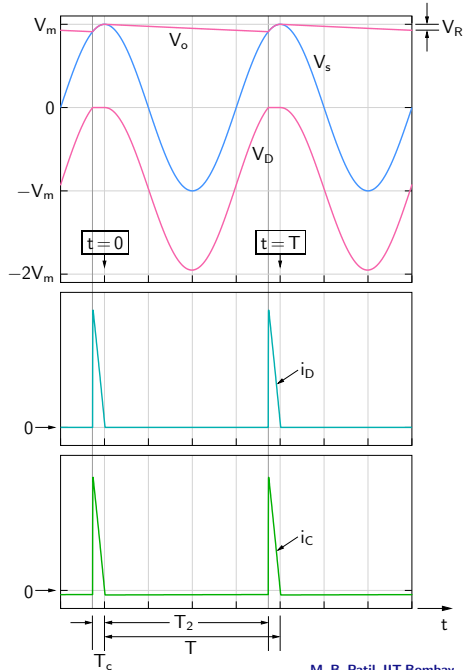
(b) Average diode current

Using charge balance,

$$\int_{T-T_c}^T (i_D - i_R) dt = \int_0^{T-T_c} i_R dt$$



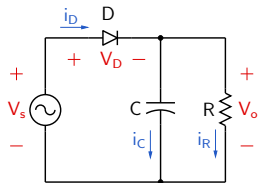Half-wave rectifier with capacitor filter




(b) Average diode current


Using charge balance,

$$\int_{T-T_c}^T (i_D - i_R) dt = \int_0^{T-T_c} i_R dt$$
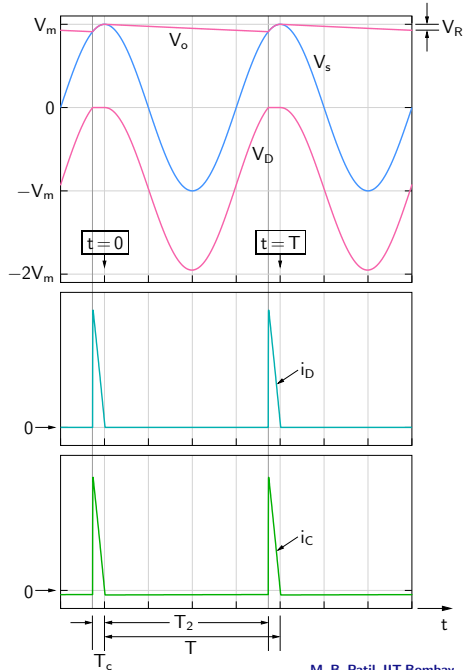
$$\rightarrow \int_{T-T_c}^T i_D dt = \int_0^{T-T_c} i_R dt.$$



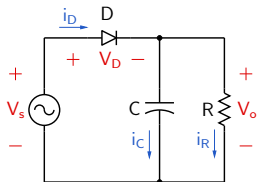Half-wave rectifier with capacitor filter




(b) Average diode current

Using charge balance,


$$\int_{T-T_c}^T (i_D - i_R) dt = \int_0^{T-T_c} i_R dt$$

$$\rightarrow \int_{T-T_c}^T i_D dt = \int_0^{T-T_c} i_R dt.$$
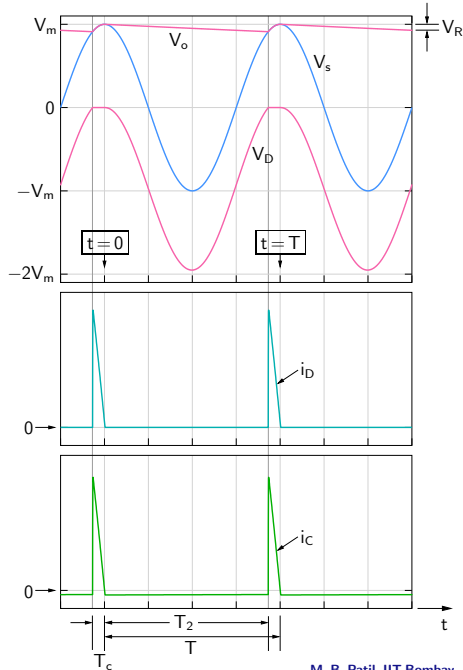
$$\begin{aligned} i_D^{av} &= \frac{1}{T} \int_0^T i_D dt = \frac{1}{T} \int_{T-T_c}^T i_D dt \\ &= \frac{1}{T} \int_0^{T-T_c} i_R dt \approx \frac{V_m}{R}. \end{aligned}$$



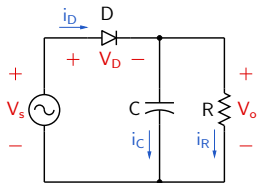Half-wave rectifier with capacitor filter



(b) Average diode current


Using charge balance,


$$\int_{T-T_c}^T (i_D - i_R) dt = \int_0^{T-T_c} i_R dt$$

$$\rightarrow \int_{T-T_c}^T i_D dt = \int_0^{T-T_c} i_R dt.$$


$$\begin{aligned} i_D^{av} &= \frac{1}{T} \int_0^T i_D dt = \frac{1}{T} \int_{T-T_c}^T i_D dt \\ &= \frac{1}{T} \int_0^{T-T_c} i_R dt \approx \frac{V_m}{R}. \end{aligned}$$

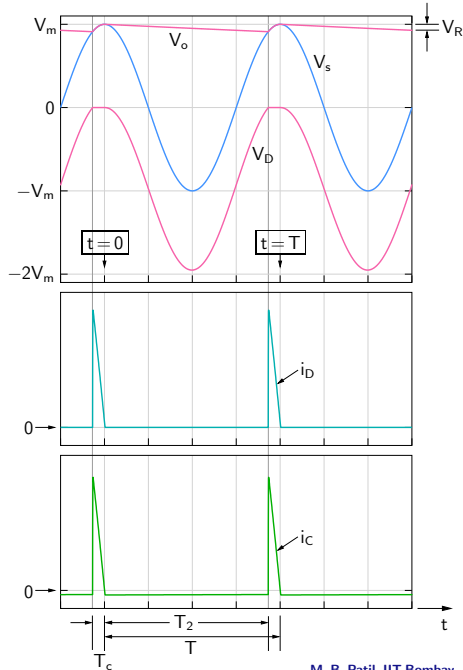
$$i_D^{av} \approx \frac{16 \text{ V}}{100 \Omega} = 160 \text{ mA}.$$



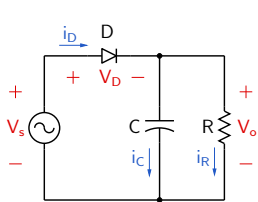


(b) Peak diode current

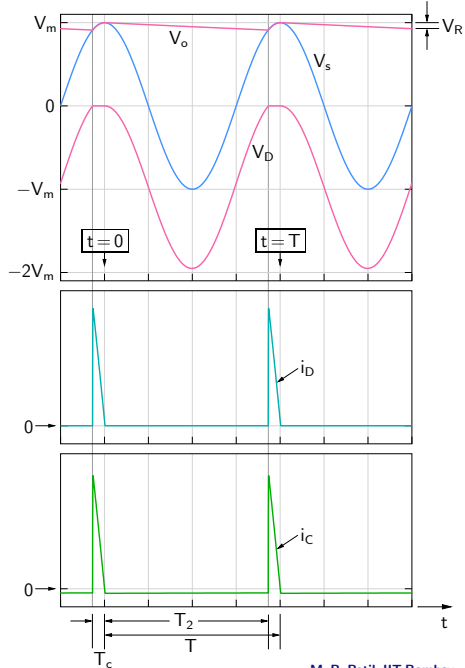


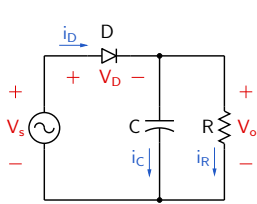

(b) Peak diode current


$$i_D^{\text{peak}} = C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} + \frac{V_m}{R}$$

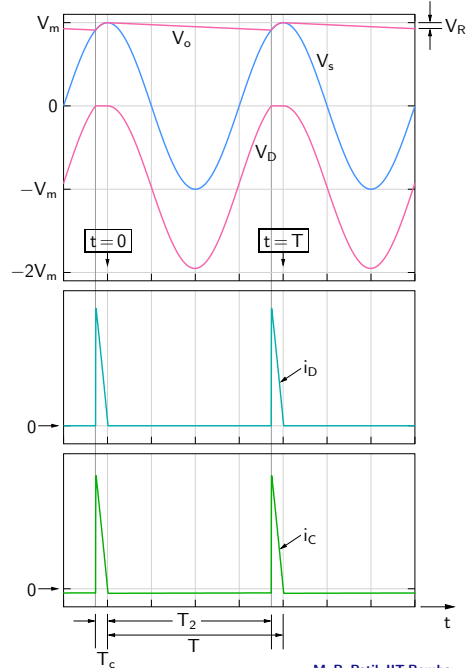


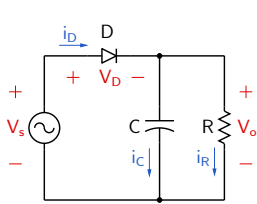

(b) Peak diode current

$$\begin{aligned}
 i_D^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_c) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_c + 0.16
 \end{aligned}$$

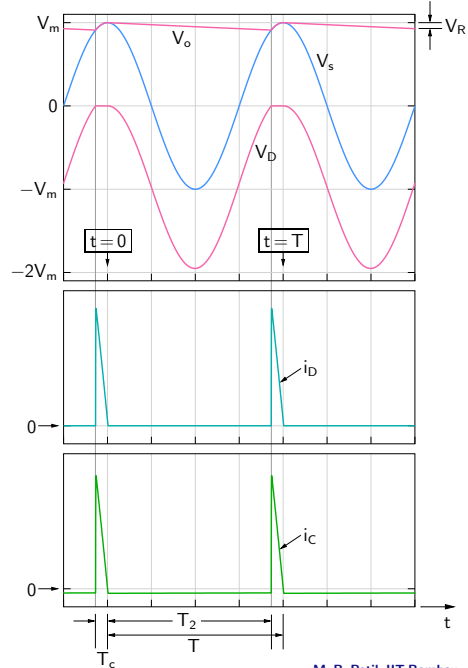

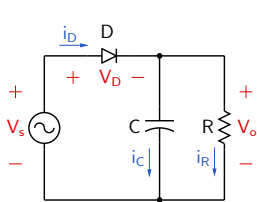



(b) Peak diode current

$$\begin{aligned}
 i_D^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_c) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_c + 0.16
 \end{aligned}$$

$$V_m \cos(-\omega T_c) = V_m - V_R, \text{ giving}$$
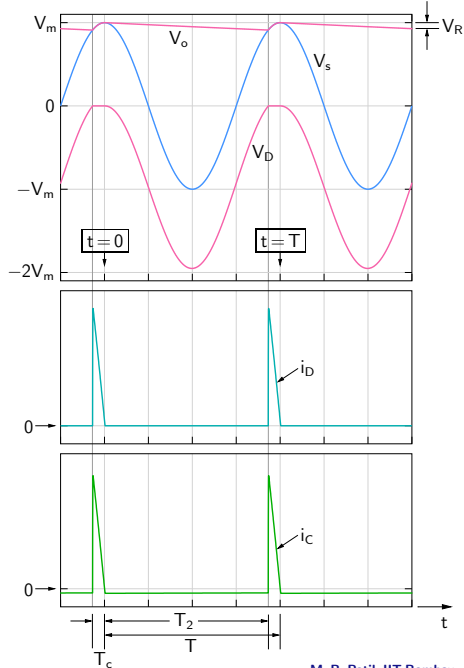
$$\omega T_c = \cos^{-1} \left(1 - \frac{V_R}{V_m} \right) = \cos^{-1} \left(1 - \frac{2}{16} \right) = 29^\circ.$$



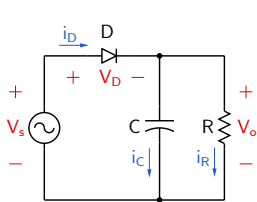


(b) Peak diode current


$$\begin{aligned}
 i_D^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_c) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_c + 0.16
 \end{aligned}$$

$$V_m \cos(-\omega T_c) = V_m - V_R, \text{ giving}$$


$$\omega T_c = \cos^{-1} \left(1 - \frac{V_R}{V_m} \right) = \cos^{-1} \left(1 - \frac{2}{16} \right) = 29^\circ.$$

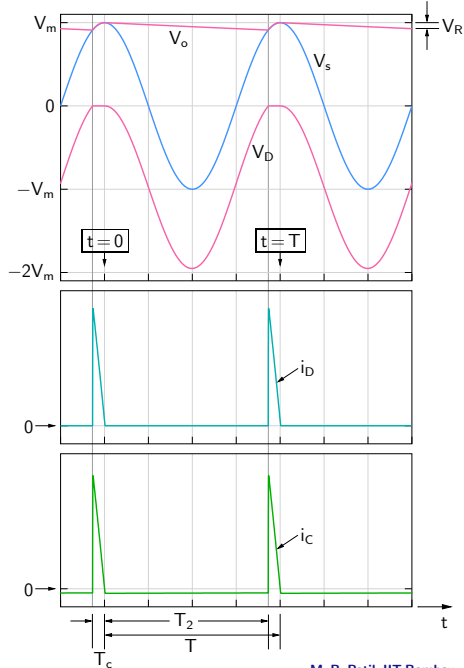
$$\begin{aligned}
 i_D^{\text{peak}} &= 2\pi \times 50 \times 1600 \times 10^{-6} \times 16 \times \sin 29^\circ + 0.16 \\
 &= 3.89 + 0.16 = 4.05 \text{ A.}
 \end{aligned}$$



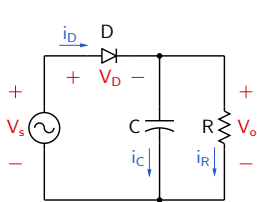

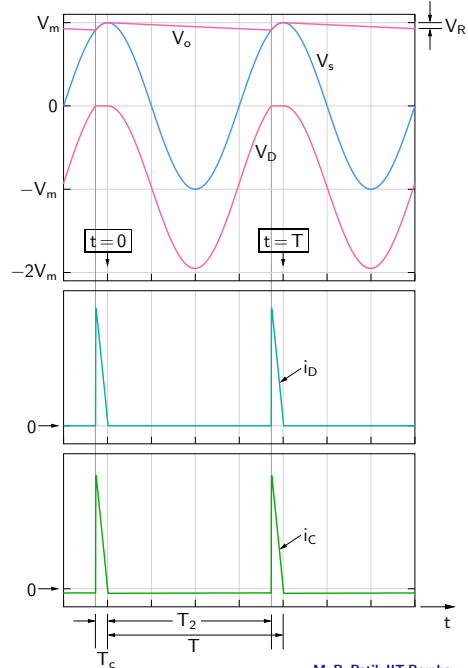
(b) Peak diode current: analytic expression




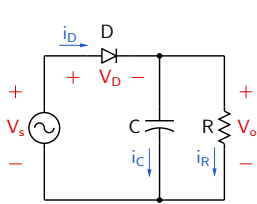

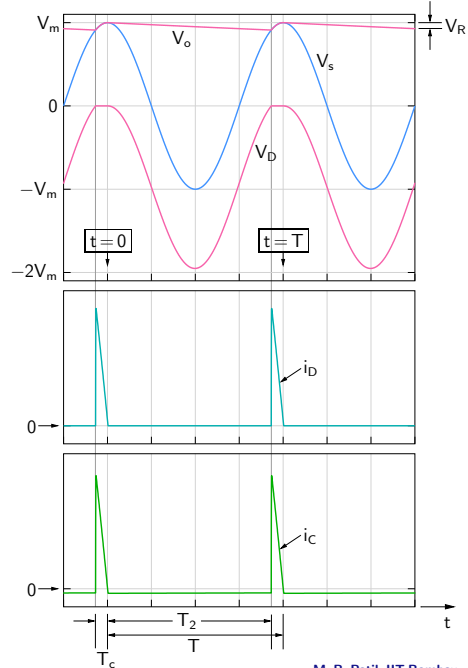(b) Peak diode current: analytic expression

$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$




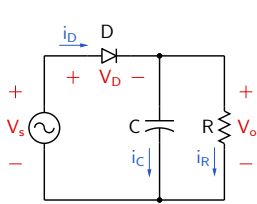


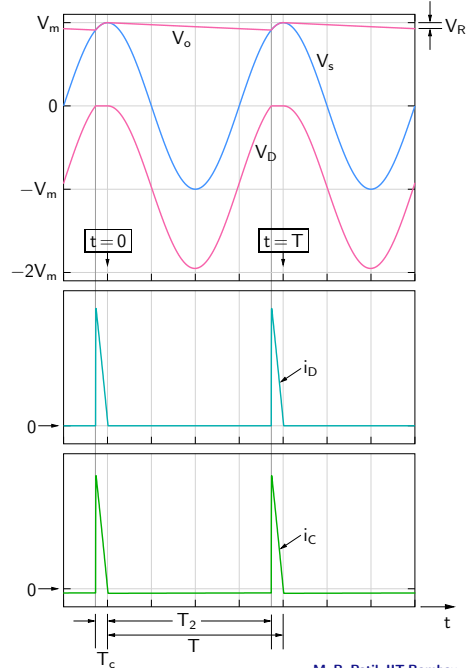(b) Peak diode current: analytic expression

$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$

$$\begin{aligned} \sin \omega T_c &= \sqrt{1 - \cos^2 \omega T_c} = \sqrt{1 - (1 - x)^2} \\ &= \sqrt{1 - (1 - 2x + x^2)} \approx \sqrt{2x} = \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$



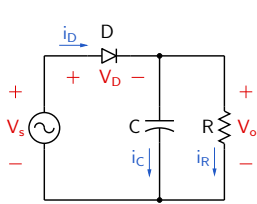



(b) Peak diode current: analytic expression

$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$

$$\begin{aligned} \sin \omega T_c &= \sqrt{1 - \cos^2 \omega T_c} = \sqrt{1 - (1 - x)^2} \\ &= \sqrt{1 - (1 - 2x + x^2)} \approx \sqrt{2x} = \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

$$\begin{aligned} i_D^{\text{peak}} &= i_R + C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} \\ &= i_R + \omega C V_m \sin \omega T_c \\ &= i_R + \omega C V_m \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

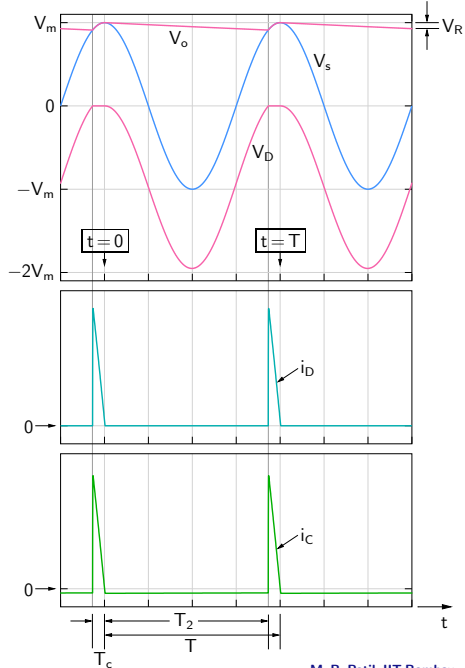

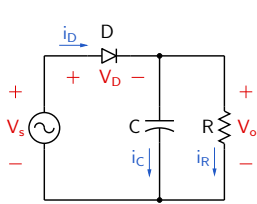


(b) Peak diode current: analytic expression


$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$

$$\begin{aligned} \sin \omega T_c &= \sqrt{1 - \cos^2 \omega T_c} = \sqrt{1 - (1 - x)^2} \\ &= \sqrt{1 - (1 - 2x + x^2)} \approx \sqrt{2x} = \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

$$\begin{aligned} i_D^{\text{peak}} &= i_R + C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} \\ &= i_R + \omega C V_m \sin \omega T_c \\ &= i_R + \omega C V_m \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

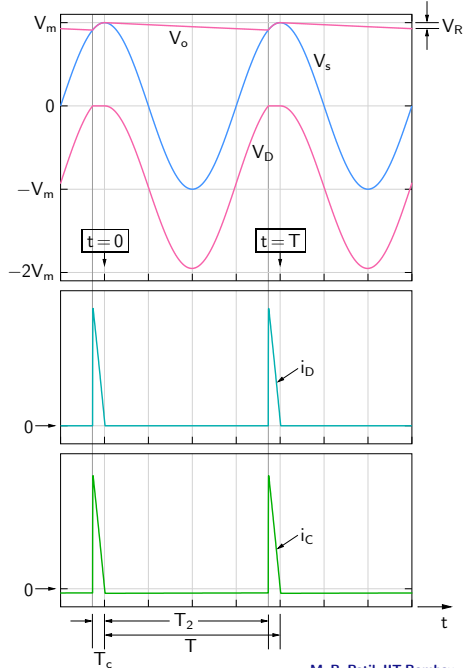(c) Maximum reverse bias $\approx 2 V_m = 32 \text{ V}$.



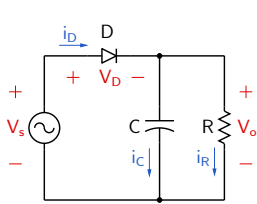

(b) Peak diode current: analytic expression


$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$

$$\begin{aligned} \sin \omega T_c &= \sqrt{1 - \cos^2 \omega T_c} = \sqrt{1 - (1 - x)^2} \\ &= \sqrt{1 - (1 - 2x + x^2)} \approx \sqrt{2x} = \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$




$$\begin{aligned} i_D^{\text{peak}} &= i_R + C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} \\ &= i_R + \omega C V_m \sin \omega T_c \\ &= i_R + \omega C V_m \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

(c) Maximum reverse bias $\approx 2 V_m = 32 \text{ V}$.


SEQUEL file: ee101_half_rectifier.sqproj

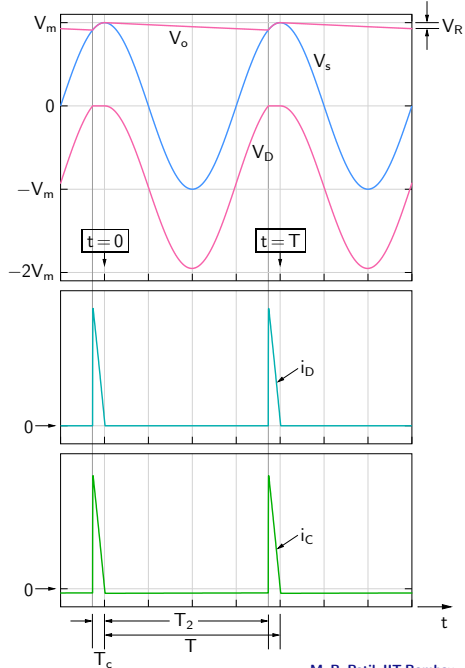

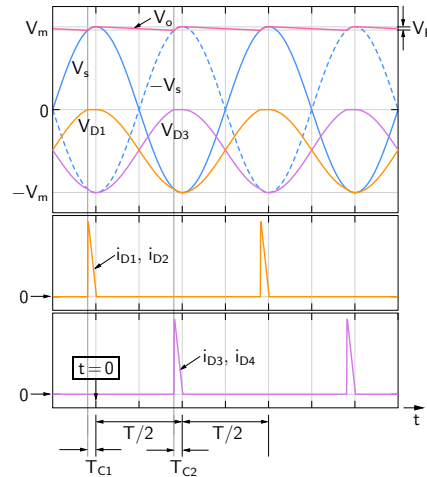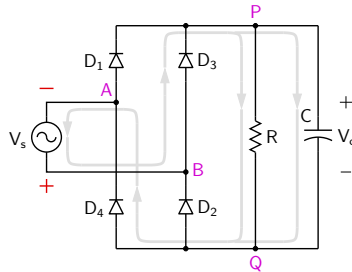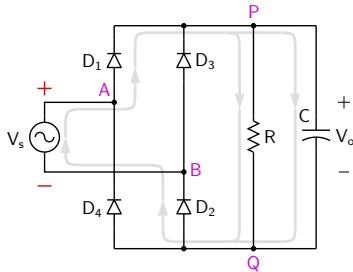
Full-wave (bridge) rectifier with capacitor filter



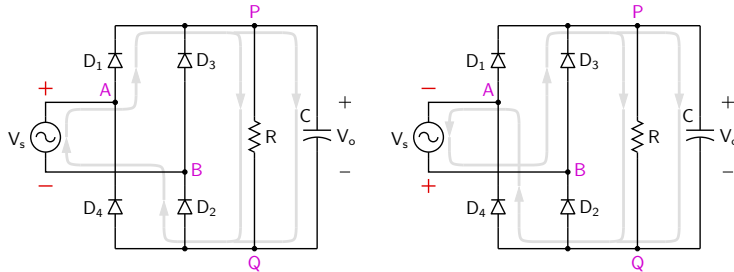
Full-wave (bridge) rectifier with capacitor filter



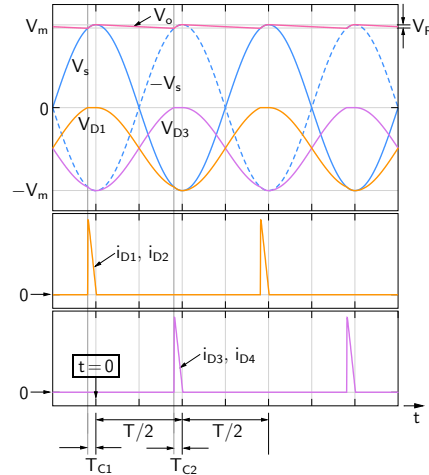
- * As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.



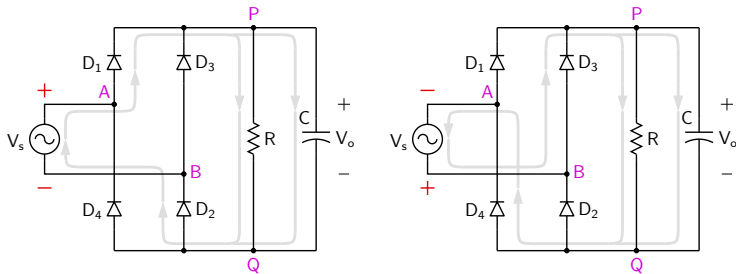
Full-wave (bridge) rectifier with capacitor filter



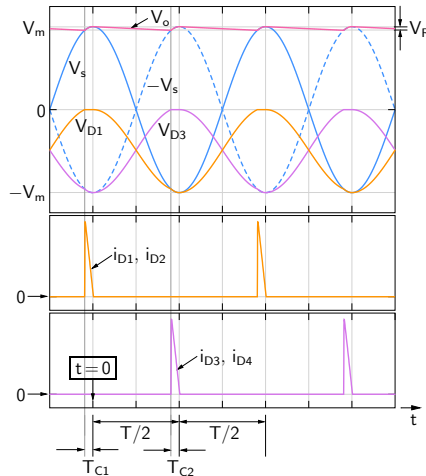
- * As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.
- * Charging through D_1, D_2 takes place when $V_o(t)$ falls below $V_s(t)$.



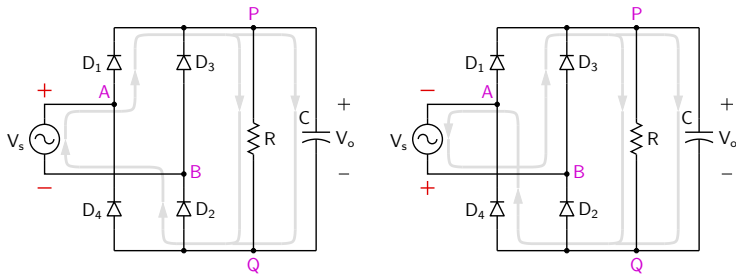
Full-wave (bridge) rectifier with capacitor filter



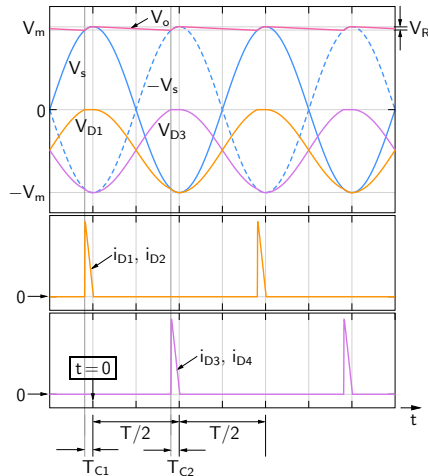
- * As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.
- * Charging through D_1, D_2 takes place when $V_o(t)$ falls below $V_s(t)$.
- * Charging through D_3, D_4 takes place when $V_o(t)$ falls below $-V_s(t)$.



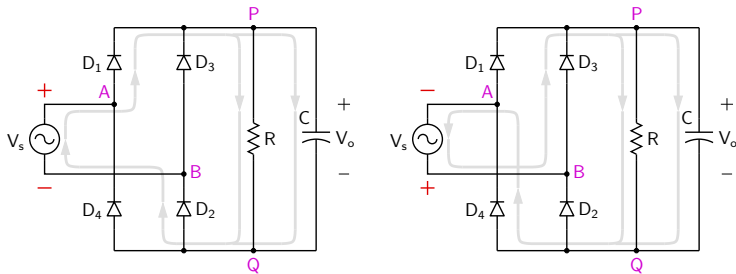
Full-wave (bridge) rectifier with capacitor filter



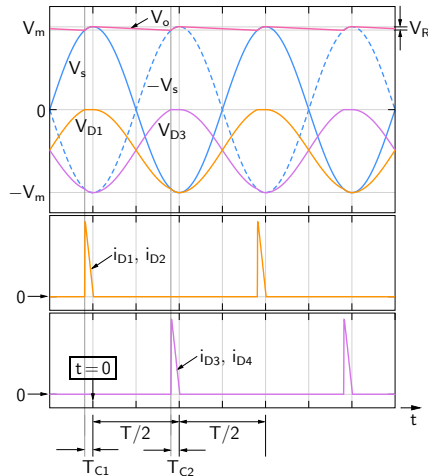
- * As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.
- * Charging through D_1, D_2 takes place when $V_o(t)$ falls below $V_s(t)$.
- * Charging through D_3, D_4 takes place when $V_o(t)$ falls below $-V_s(t)$.
- * The discharging interval is typically much longer than the charging intervals (T_{C1} and T_{C2}).



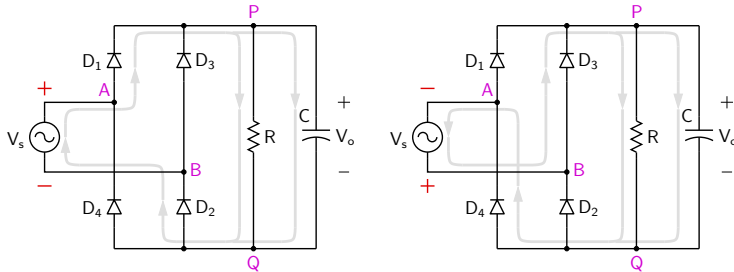
Full-wave (bridge) rectifier with capacitor filter




- * As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.
- * Charging through D_1, D_2 takes place when $V_o(t)$ falls below $V_s(t)$.
- * Charging through D_3, D_4 takes place when $V_o(t)$ falls below $-V_s(t)$.
- * The discharging interval is typically much longer than the charging intervals (T_{C1} and T_{C2}).
- * The maximum reverse bias across any of the diodes is V_m .

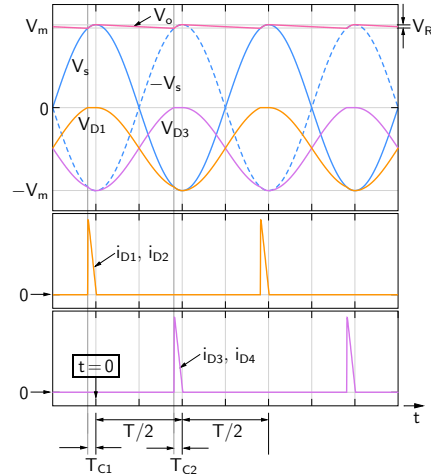

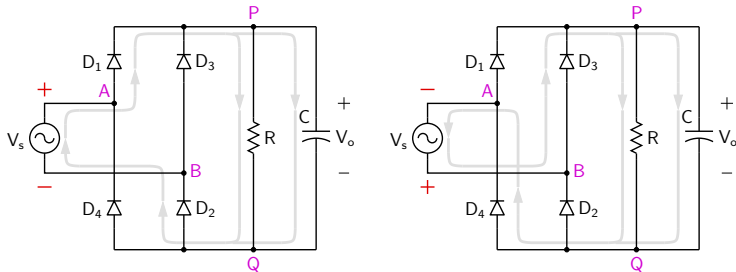
Full-wave rectifier with capacitor filter



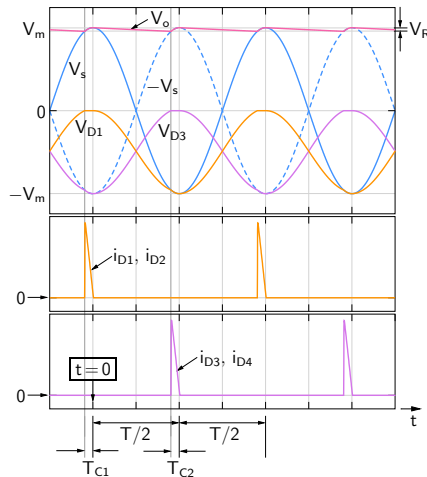$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)




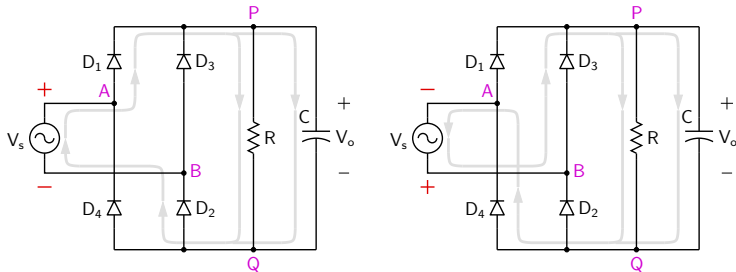Full-wave rectifier with capacitor filter




$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)

(a) filter capacitance:

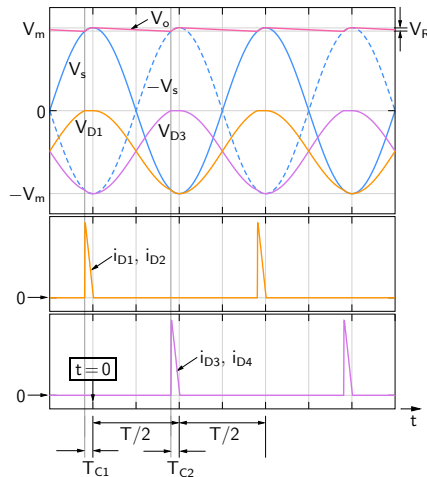

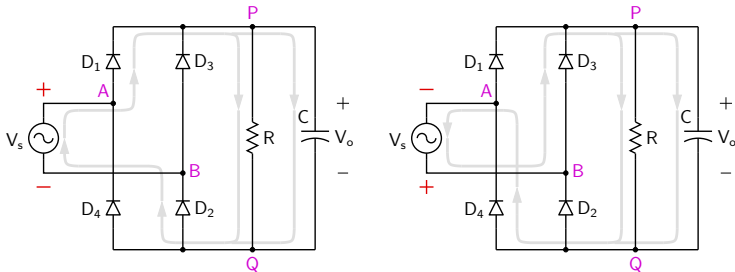Full-wave rectifier with capacitor filter




$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)

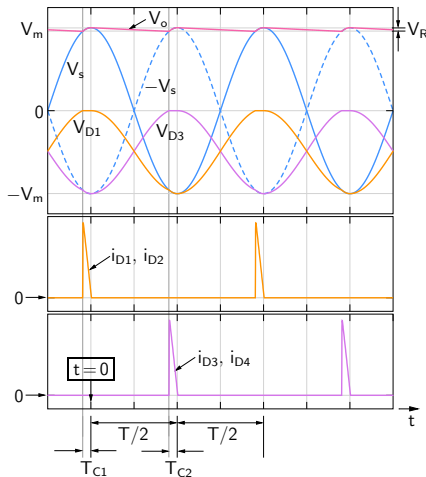
(a) filter capacitance:

Assuming $i_C = i_R = \frac{V_o}{R} \approx \frac{V_m}{R}$ in the discharge phase, we get

$$i_C = \frac{V_m}{R} = C \frac{\Delta V_o}{\Delta t} \approx C \frac{V_R}{T/2} \rightarrow V_R = V_m \frac{T}{2RC}.$$



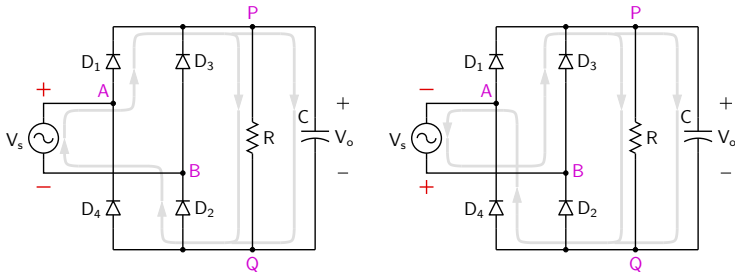Full-wave rectifier with capacitor filter




$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)

(a) filter capacitance:


Assuming $i_C = i_R = \frac{V_o}{R} \approx \frac{V_m}{R}$ in the discharge phase, we get

$$i_C = \frac{V_m}{R} = C \frac{\Delta V_o}{\Delta t} \approx C \frac{V_R}{T/2} \rightarrow V_R = V_m \frac{T}{2RC}.$$

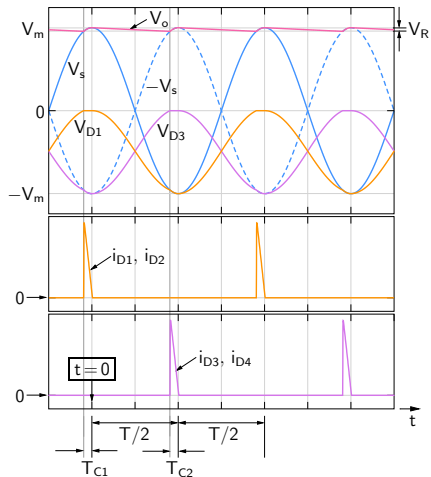
$$\rightarrow C = \frac{1}{2} \frac{V_m}{V_R} \frac{T}{R} = \frac{1}{2} \frac{16\text{ V}}{2\text{ V}} \frac{20\text{ ms}}{100\ \Omega} = 800\ \mu\text{F}.$$



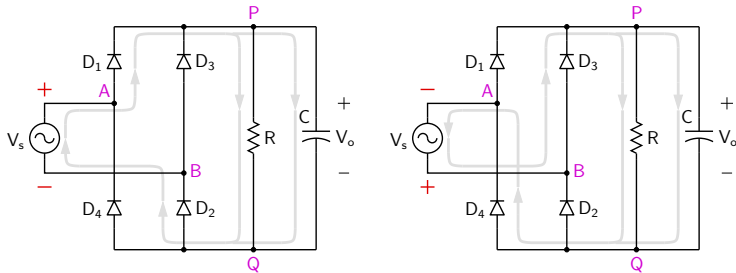
Full-wave rectifier with capacitor filter



(b) Average diode current

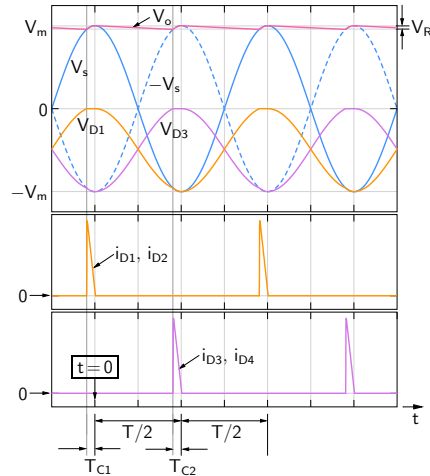


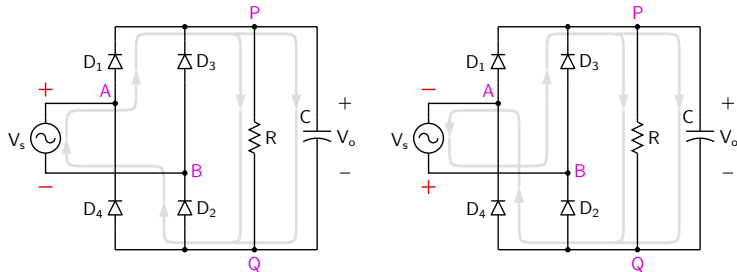Full-wave rectifier with capacitor filter




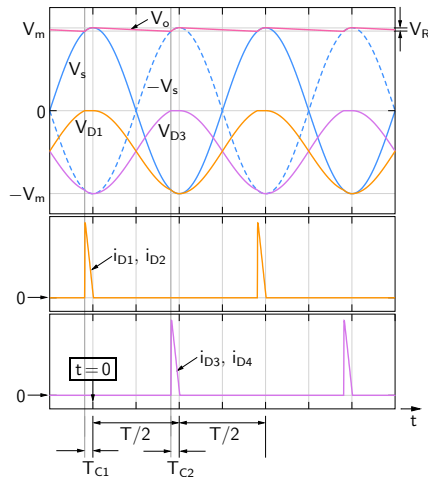(b) Average diode current

Half of the charge lost by the capacitor is supplied by i_{D1} ($= i_{D2}$), and the other half by i_{D3} ($= i_{D4}$).



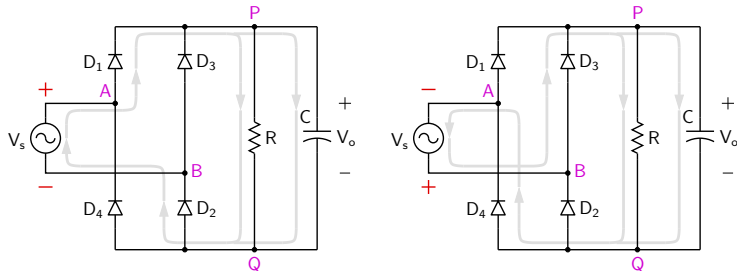
Full-wave rectifier with capacitor filter



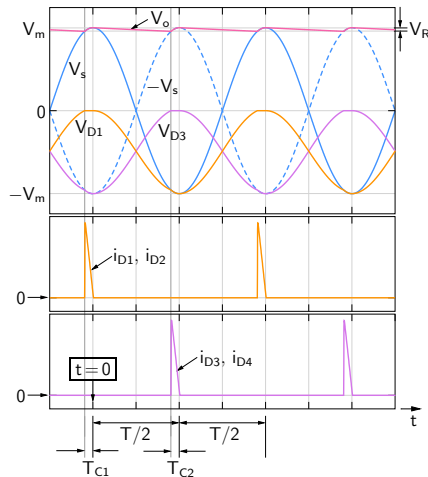
(b) Average diode current

Half of the charge lost by the capacitor is supplied by i_{D1} ($= i_{D2}$), and the other half by i_{D3} ($= i_{D4}$).

$$i_D^{av} = \frac{1}{T} \times \frac{1}{2} \times (\text{Charge lost in one cycle})$$



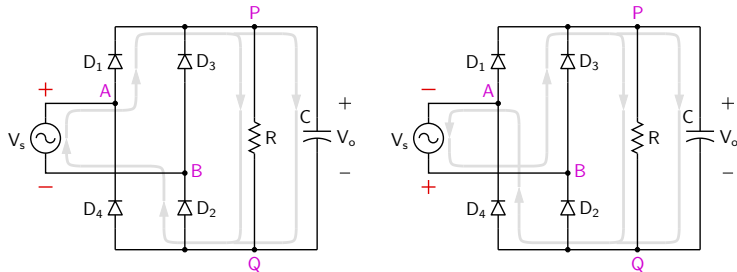Full-wave rectifier with capacitor filter




(b) Average diode current



Half of the charge lost by the capacitor is supplied by i_{D1} ($= i_{D2}$), and the other half by i_{D3} ($= i_{D4}$).

$$i_D^{av} = \frac{1}{T} \times \frac{1}{2} \times (\text{Charge lost in one cycle})$$

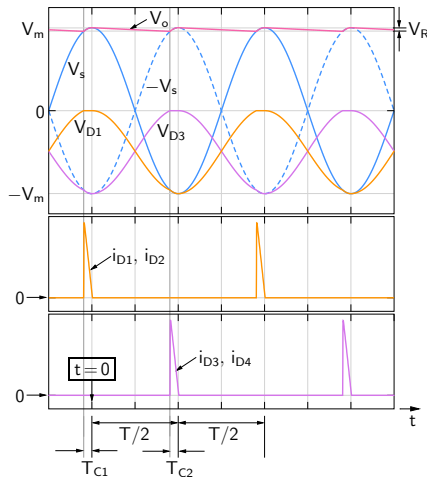
$$\approx \frac{1}{T} \times \frac{1}{2} \times \left(\frac{V_m}{R} \times T \right) = \frac{V_m}{2R} = \frac{16 \text{ V}}{2 \times 100 \Omega} = 80 \text{ mA}.$$



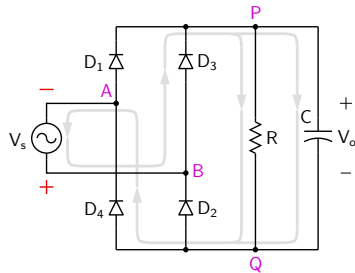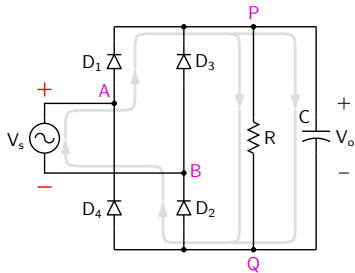
Full-wave rectifier with capacitor filter



(b) Peak diode current

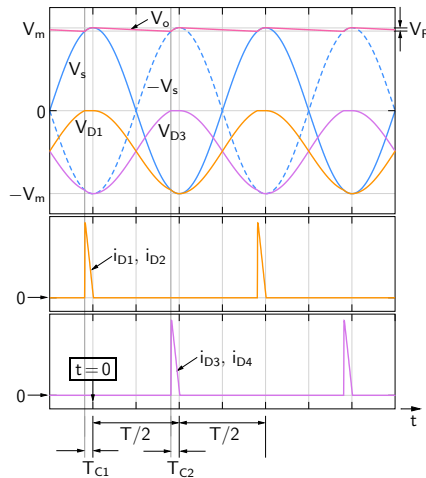


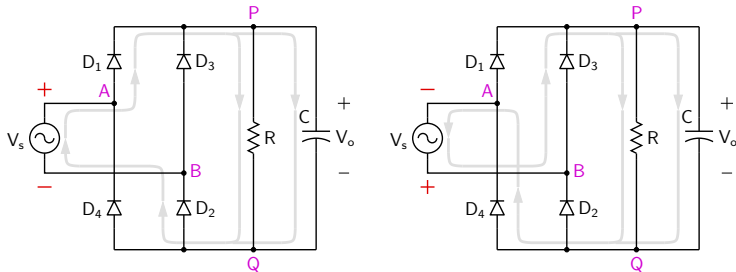Full-wave rectifier with capacitor filter




(b) Peak diode current

$$\begin{aligned}
 i_{D1}^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_{C1}} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_{C1}) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_{C1} + 0.16
 \end{aligned}$$

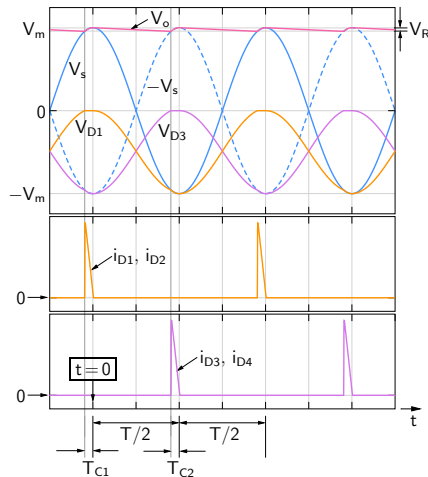


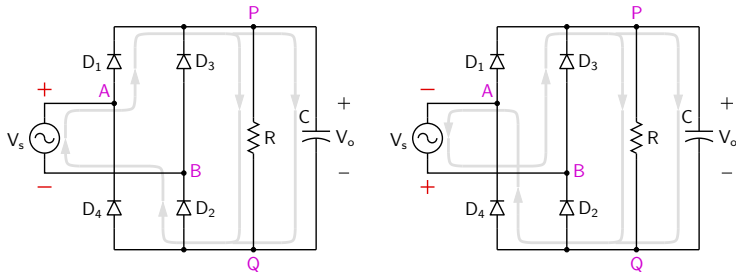Full-wave rectifier with capacitor filter




(b) Peak diode current

$$\begin{aligned}
 i_{D1}^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_{C1}} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_{C1}) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_{C1} + 0.16 \\
 \omega T_{C1} &= \cos^{-1} \left(1 - \frac{V_R}{V_m} \right) = \cos^{-1} \left(1 - \frac{2}{16} \right) = 29^\circ.
 \end{aligned}$$

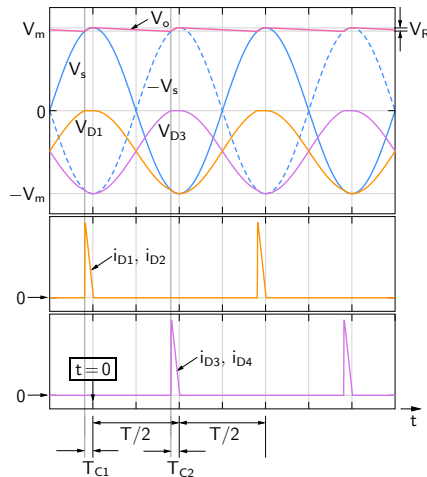

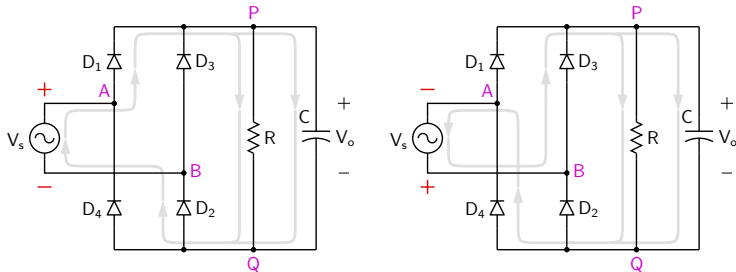Full-wave rectifier with capacitor filter




(b) Peak diode current


$$\begin{aligned}
 i_{D1}^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_{C1}} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_{C1}) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_{C1} + 0.16
 \end{aligned}$$

$$\omega T_{C1} = \cos^{-1} \left(1 - \frac{V_R}{V_m} \right) = \cos^{-1} \left(1 - \frac{2}{16} \right) = 29^\circ.$$

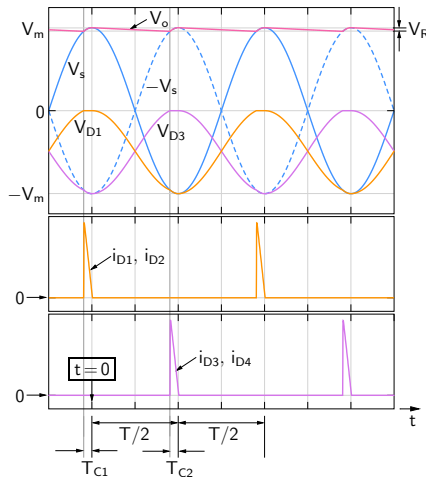
$$\begin{aligned}
 i_{D1}^{\text{peak}} &= 2\pi \times 50 \times 800 \times 10^{-6} \times 16 \times \sin 29^\circ + 0.16 \\
 &= 1.95 + 0.16 = 2.1 \text{ A}.
 \end{aligned}$$



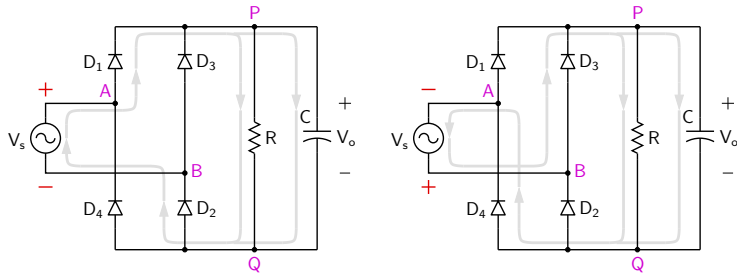
Full-wave rectifier with capacitor filter



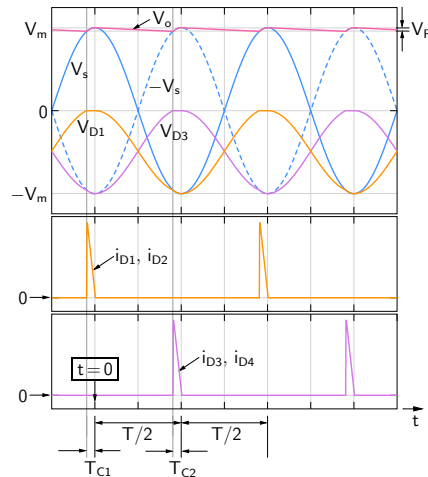(c) Maximum reverse bias = $V_m = 16\text{ V}$.




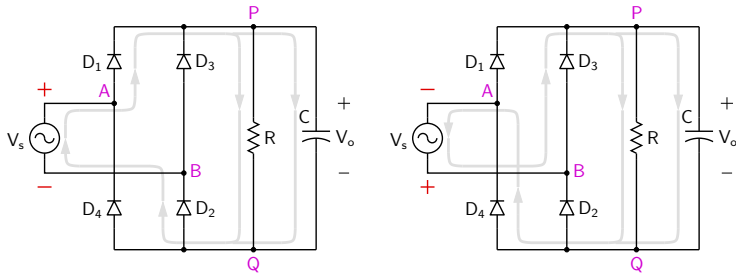Full-wave rectifier with capacitor filter



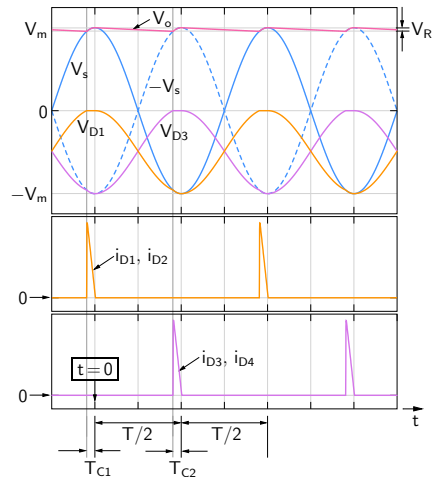(c) Maximum reverse bias = $V_m = 16\text{ V}$.

SEQUEL file: [diode_rectifier_4.sqproj](#)



Comparison of half-wave and full-wave (bridge) rectifiers with capacitive filter

For the same source voltage ($V_m \sin \omega t$), load (R), and ripple voltage (V_R), compare the half-wave and full-wave rectifiers.

Comparison of half-wave and full-wave (bridge) rectifiers with capacitive filter

For the same source voltage ($V_m \sin \omega t$), load (R), and ripple voltage (V_R), compare the half-wave and full-wave rectifiers.

Parameter	Half-wave	Full-wave
Number of diodes	1	4
Filter capacitance	C	$C/2$
Average diode current	i_D^{av}	$i_D^{\text{av}}/2$
Peak diode current	i_D^{peak}	$i_D^{\text{peak}}/2$
Maximum reverse voltage	$2 V_m$	V_m