

Automatic Test Pattern Generation - II

Virendra Singh

Associate Professor

Computer Architecture and Dependable Systems Lab

Dept. of Electrical Engineering

Indian Institute of Technology Bombay

viren@ee.iitb.ac.in



EE 709: Testing & Verification of VLSI Circuits

Lecture – 12 (Jan 30, 2012)

ATPG - Algorithmic

❖ Path Sensitization Method

- Fault Sensitization
- Fault Propagation
- Line Justification

❖ Path Sensitization Algorithms

- D- Algorithm (Roth)
- PODEM (P. Goel)
- FAN (Fujiwara)
- SOCRATES (Schultz)
- SPIRIT (Emil & Fujiwara)

Common Concept

- ❖ Fault Activation problem \rightarrow a LJ Problem
- ❖ The Fault Propagation problem \rightarrow
 1. Select a FP path to PO \rightarrow Decision
 2. Once the path is selected \rightarrow a set of LJ problems
- ❖ The LJ Problems \rightarrow Decisions or Implications



To justify $c = 1 \rightarrow a = 1, b = 1$ (Implication)

To justify $c = 0 \rightarrow a = 0$ or $b = 0$ (Decision)

- ❖ Incorrect decision \rightarrow Backtrack \rightarrow Another decision


D-Algorithm

Roth (IBM) - 1966

- Fundamental concepts invented:
 - First complete ATPG algorithm
 - **D-Calculus** (5 valued logic)
 - Implications – forward and backward
 - Implication stack
 - **Backtrack**
 - Test Search Space

Singular Cover Example

 - Minimal set of logic signal assignments to show *essential prime implicants of Karnaugh map*



Gate	Inputs	Output	Gate	Inputs	Output
AND	A B	d	NOR	d e	F
1	0 X	0	1	1 X	0
2	X 0	0	2	X 1	0
3	1 1	1	3	0 0	1

D-Cube

- Collapsed truth table entry to characterize logic
- Use Roth's 5-valued algebra
- Can change all D's to \overline{D} 's and $\overline{\overline{D}}$'s to D's (do both)
- **AND gate:**

	<i>A</i>	<i>B</i>	<i>d</i>
Rows 1 & 3	D	1	D
Reverse inputs	1	D	D
And two cubes	\overline{D}	\overline{D}	\overline{D}
Interchange D and \overline{D}	D	\overline{D}	\overline{D}
	$\overline{1}$	D	\overline{D}
	D	1	D

D-Cube Operation of D-Intersection

- ψ – undefined (same as ϕ)
- μ or λ – requires inversion of \mathbf{D} and $\overline{\mathbf{D}}$
- ***D-intersection***: $\mathbf{0} \cap \mathbf{0} = \mathbf{0} \cap \mathbf{X} = \mathbf{X} \cap \mathbf{0} = \mathbf{0}$
 $\mathbf{1} \cap \mathbf{1} = \mathbf{1} \cap \mathbf{X} = \mathbf{X} \cap \mathbf{1} = \mathbf{1}$
 $\mathbf{X} \cap \mathbf{X} = \mathbf{X}$

- ***D-containment*** –
**Cube a contains
 Cube b if b is a
 subset of a**

\cap	0	1	X	D	$\overline{\mathbf{D}}$
0	0	ϕ	0	ψ	ψ
1	ϕ	1	1	ψ	ψ
X	0	1	X	D	$\overline{\mathbf{D}}$
$\overline{\mathbf{D}}$	ψ	ψ	$\overline{\mathbf{D}}$	μ	λ
\mathbf{D}	ψ	ψ	\mathbf{D}	λ	μ

Primitive D-Cube of Failure

- Models circuit faults:
 - *Stuck-at-0*
 - *Stuck-at-1*
 - *Bridging fault* (short circuit)
 - Arbitrary change in logic function
- AND Output sa0: “1 1 \overline{D} ”
- AND Output sa1: “0 X \overline{D} ”
“X 0 \overline{D} ”
- Wire sa0: “D”
- *Propagation D-cube* – models conditions under which fault effect propagates through gate

Implication Procedure

1. Model fault with appropriate *primitive D-cube of failure* (**PDF**)
 2. Select *propagation D-cubes* to propagate fault effect to a circuit output (**D-drive procedure**)
 3. Select *singular cover cubes* to justify internal circuit signals (**Consistency procedure**)
- ❖ Put signal assignments in *test cube*
 - ❖ Regrettably, cubes are selected very arbitrarily by D-ALG

D-Algorithm – Top Level

1. Number all circuit lines in increasing level order from PIs to POs;
2. Select a primitive D-cube of the fault to be the *test cube*;
 - Put logic outputs with inputs labeled as D (\bar{D}) onto the *D-frontier*;
3. *D-drive* ();
4. *Consistency* ();
5. return ();

D-Algorithm – *D-drive*

```
while (untried fault effects on D-frontier)
  select next untried D-frontier gate for propagation;
  while (untried fault effect fanouts exist)
    select next untried fault effect fanout;
    generate next untried propagation D-cube;
    D-intersect selected cube with test cube;
    if (intersection fails or is undefined) continue;
    if (all propagation D-cubes tried & failed) break;
    if (intersection succeeded)
      add propagation D-cube to test cube -- recreate D-frontier;
      Find all forward & backward implications of assignment;
      save D-frontier, algorithm state, test cube, fanouts, fault;
      break;
    else if (intersection fails & D and  $\bar{D}$  in test cube) Backtrack ();
    else if (intersection fails) break;
  if (all fault effects unpropagatable) Backtrack ();
```


D-Algorithm - Consistency

g = coordinates of test cube with 1's & 0's;
if (g is only PIs) **fault testable & stop**;
for (each unjustified signal in g)
 Select highest # unjustified signal \underline{z} in g , not a PI;
 if (inputs to gate z are both D and \overline{D}) break;
 while (untried singular covers of gate z)
 select next untried singular cover;
 if (no more singular covers)
 If (no more stack choices) **fault untestable & stop**;
 else if (untried alternatives in *Consistency*)
 pop implication stack -- try alternate assignment;
 else
 Backtrack ();
 D-drive ();
 If (singular cover D-intersects with z) delete z from g , add inputs to
 singular cover to g , *find all forward and backward implications*
 of new assignment, and break;
 If (intersection fails) mark singular cover as failed;


Backtrack

if (PO exists with fault effect) *Consistency* ();
else pop prior implication stack setting to try
 alternate assignment;
if (no untried choices in implication stack)
 fault untestable & stop;
else return;


D-Algorithm

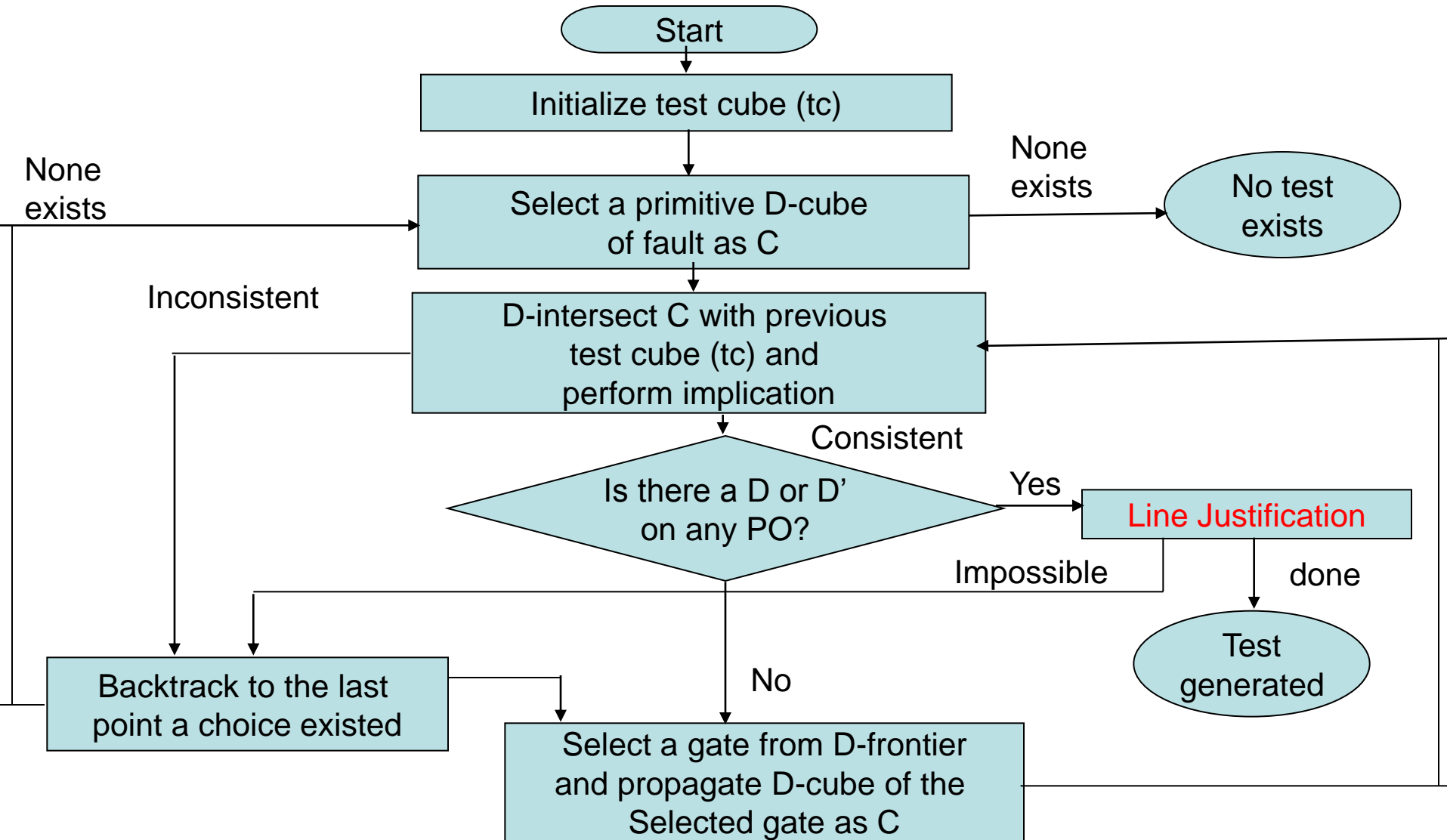

D-Algo (Line Justification)

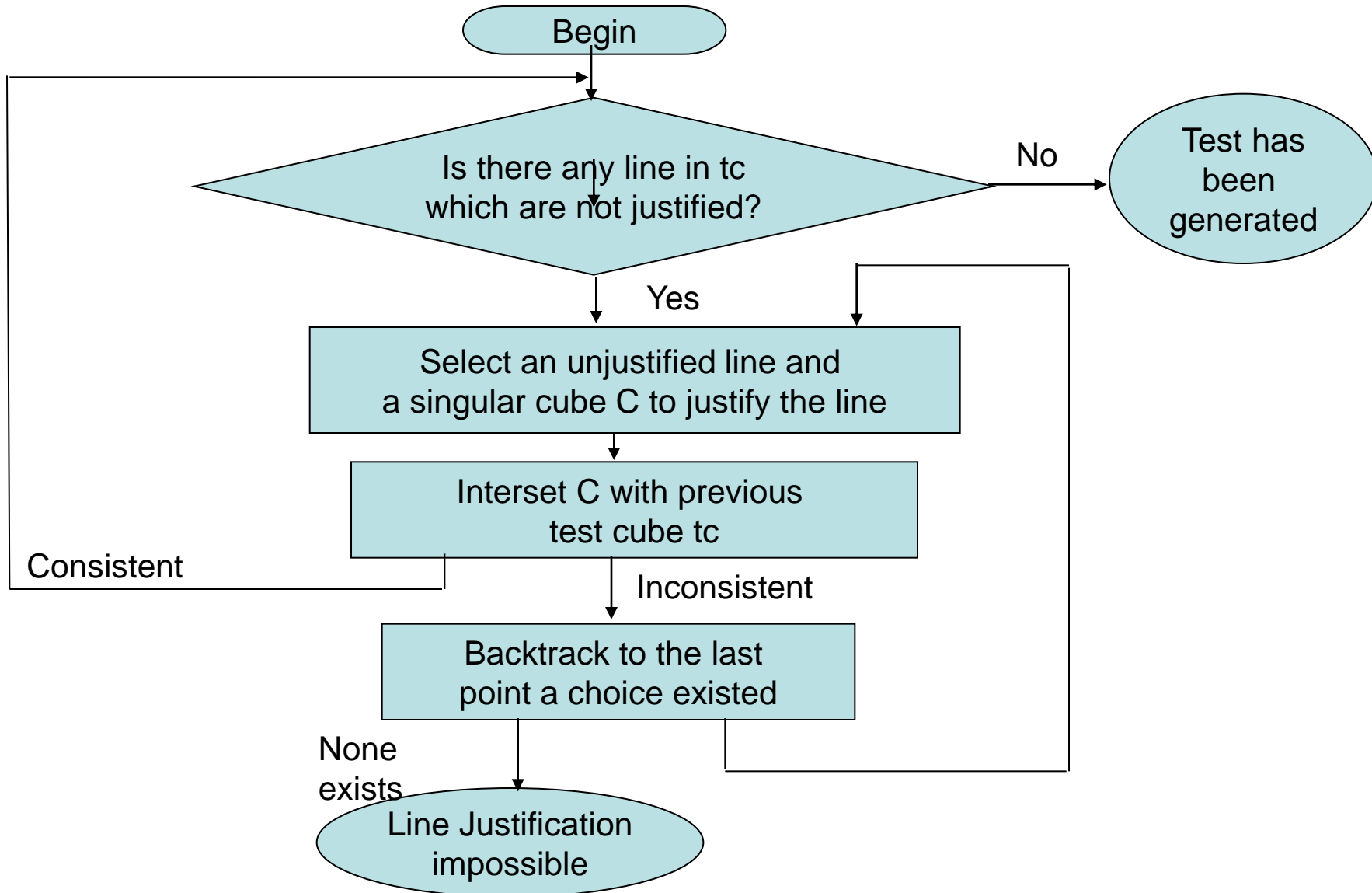

Circuit Example 1

 

Inputs			Output
A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Singular Cover & D-Cubes

A	B	C	d	e	F
1 0	1 0 1 0	 1 0	1 0 0 1 0	 0 1 1 1 0	 0 0 1
D 1 D	1 D D D 1 D	 1 D D	D D D D D D D D	 D D D D D D D D	 D D D D D D D D

- *Singular cover* – Used for justifying lines

- *Propagation D-cubes* – Conditions under which difference between good/failing machines propagates


Steps for Fault d sa0

Step	A	B	C	d	e	F	Cube type
1	1	1		D			PDF of AND gate
2				D	0	\overline{D}	Prop. D-cube for NOR
3		1	1		0		Sing. Cover of NAND


9 - V Algorithm (Muth)

- Logic values $\{0/0, 1/1, 0/1, 1/0, 0/u, 1/u, u/0, u/1, u/u\}$
 - $0/u = \{0, D'\}$, $1/u = \{D, 1\}$, $u/0 = \{0, D\}$, $u/1 = \{D', 1\}$
 - $u/u = \{0, 1, D, D'\}$
- Reduces amount of search done in multiple path sensitization – **D- Algo**

9 - V Algorithm

 


9 - V Algorithm

 

9-V Algorithm: Value Comp

Decision	Implication	Comments			
	$a=0$ $h=1$ $b=1$ $c=1$ $g=D$ $i=u/1$ $k=u/1$ $m=u/1$	Activate the fault Unique D-drive	$l=u/1$ $j=u/1$	$n=D$ $f?u/0$ $f=1$ $f?0$ $e?u/0$ $e=1$ $e?0$ $k=D$ $m=D$	Propagate via n
$d=1$	$i=D$ $d?0$ $n=1/u$	Propagate via i			

9-V Algorithm: Value Comp

 

Path Oriented DEcision Making (PODEM)

P. Goel, IBM, 1981

Motivation

- **IBM introduced semiconductor DRAM memory into its mainframes – late 1970's**
- **Memory had error correction and translation circuits – improved reliability**
 - **D-ALG unable to test these circuits**
 - ❖ **Search too undirected**
 - ❖ **Large XOR-gate trees**
 - ❖ **Must set all external inputs to define output**
 - **Needed a better ATPG tool**


PODEM

- **New concepts introduced:**
 - **Expand binary decision tree only around primary inputs**
 - **Use *X-PATH-CHECK* to test whether *D-frontier* still there**
 - ***Objectives* -- bring ATPG closer to propagating D (D') to PO**
 - ***Backtracing***

PODEM High-Level Flow


1. Assign binary value to unassigned PI
2. Determine implications of all PIs
3. Test Generated? If so, **done**.
4. Test possible with more assigned PIs? If maybe, go to Step 1
5. Is there untried combination of values on assigned PIs? If not, **exit: untestable fault**
6. Set untried combination of values on assigned PIs using objectives and backtrace. Then, go to Step 2

PODEM-Algorithm

 


PODEM

Ex: Objective = (F, 1).

 


The first time of backtracing

 


The second time of backtracing

D-Algorithm : Example

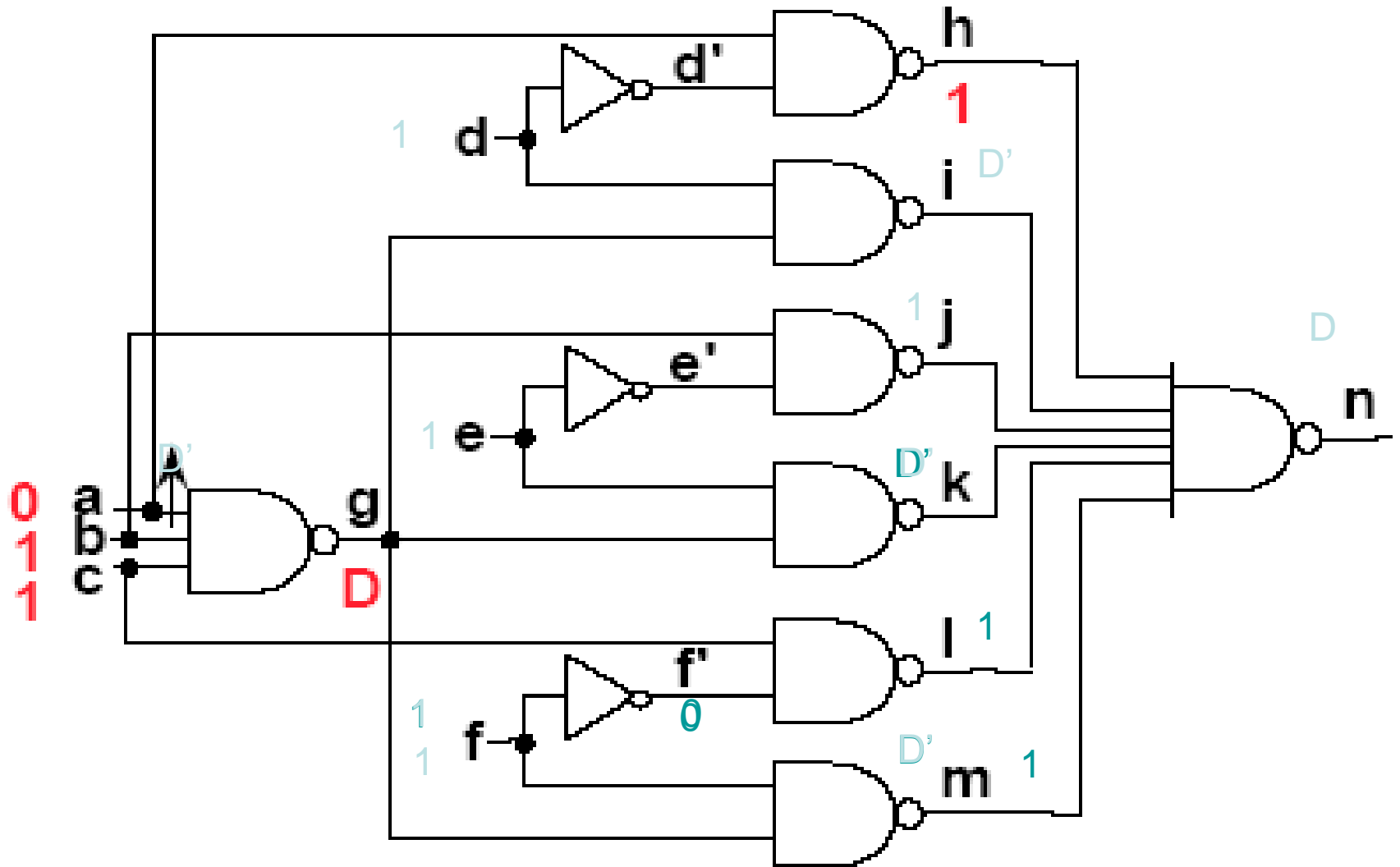


PODEM : Example

 

PODEM : Value Comp

Objective	PI assignment	Implications	D-frontier	Comments
a=0	a=0	h=1	g	
b=1	b=1		g	
c=1	c=1	g=D	i,k,m	
d=1	d=1	d?0 i=D	k,m,n	
k=1	e=0	e?1 j=0 k=1 n=1	m	x-path check fail !!
	e=1	e?0 j=1 k=D	m,n	reversal
l=1	f=1	f?0 l=1 m=D n=D		

PODEM : Decision Tree

 

Thank You

