

Sequential Equivalence Checking - I

Virendra Singh

Associate Professor

Computer Architecture and Dependable Systems Lab.

Dept. of Electrical Engineering
Indian Institute of Technology
Bombay

viren@ee.iitb.ac.in



EE 709: Testing & Verification of VLSI Circuits


Lecture – 14 (Feb 02, 2012)

Functional Equivalence

- If BDD can be constructed for each circuit
 - represent each circuit as *shared* (multi-output) BDD
 - ❖ **use the same variable ordering !**
 - BDDs of both circuits must be *identical*
- If BDDs are too large
 - cannot construct BDD, memory problem
 - use partitioned BDD method
 - decompose circuit into smaller pieces, each as BDD
 - check equivalence of internal points

Functional Decomposition

 
- Decompose each function into *functional* blocks
 - represent each block as a BDD (*partitioned BDD* method)
 - **define cut-points** (z)
 - verify equivalence of blocks at cut-points
 - starting at primary inputs



Cut-Points Resolution Problem


- If *all pairs* of cut-points (z_1, z_2) are equivalent
 - so are the two functions, F, G
- If *intermediate* functions (f_2, g_2) are not equivalent
 - the functions (F, G) may still be equivalent
 - this is called **false negative**

 - Why do we have false negative ?
 - functions are represented in terms of *intermediate* variables
 - to prove/disprove equivalence must represent the functions in terms of *primary inputs* (BDD composition)



Cut-Point Resolution – Theory

 - Let $f_1(x)=g_1(x) \quad \forall x$
 - if $f_2(z,y) \equiv g_2(z,y), \quad \forall z,y$ then $f_2(f_1(x),y) \equiv g_2(f_1(x),y) \Rightarrow F \equiv G$
 - if $f_2(z,y) \neq g_2(z,y), \quad \forall z,y \quad \not\Rightarrow \quad f_2(f_1(x),y) \neq g_2(f_1(x),y) \not\Rightarrow F \neq G$




We cannot say if $F \equiv G$ or not

- *False negative*
 - two functions are equivalent, but the verification algorithm declares them as different.


Cut-Point Resolution

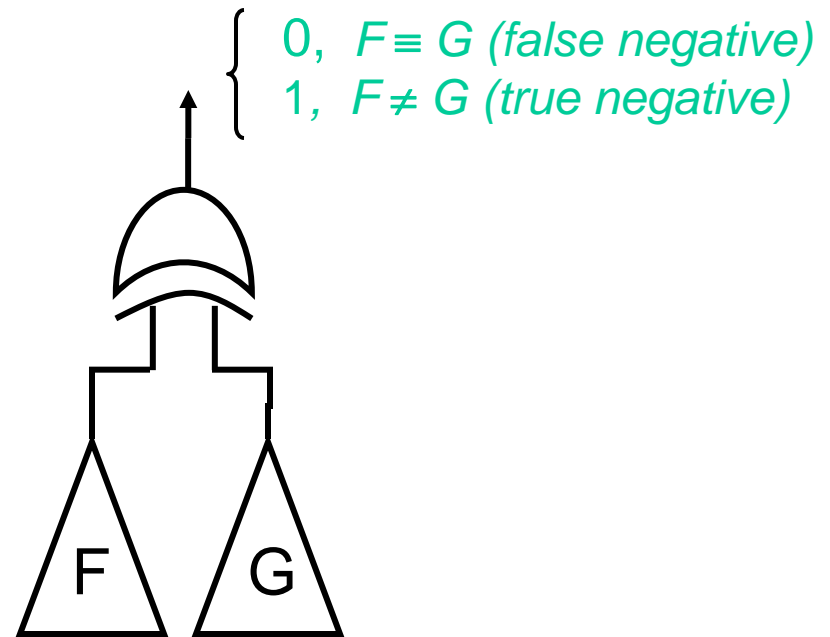- How to verify if negative is *false* or *true* ?
- **Procedure 1:** create a miter (XOR) between two potentially equivalent nodes/functions
 - perform ATPG test for *stuck-at 0*
 - find test pattern to prove $F \neq G$
 - efficient for true negative
 - (gives *test vector*, a proof)
 - inefficient when there is no test



Cut-Point Resolution

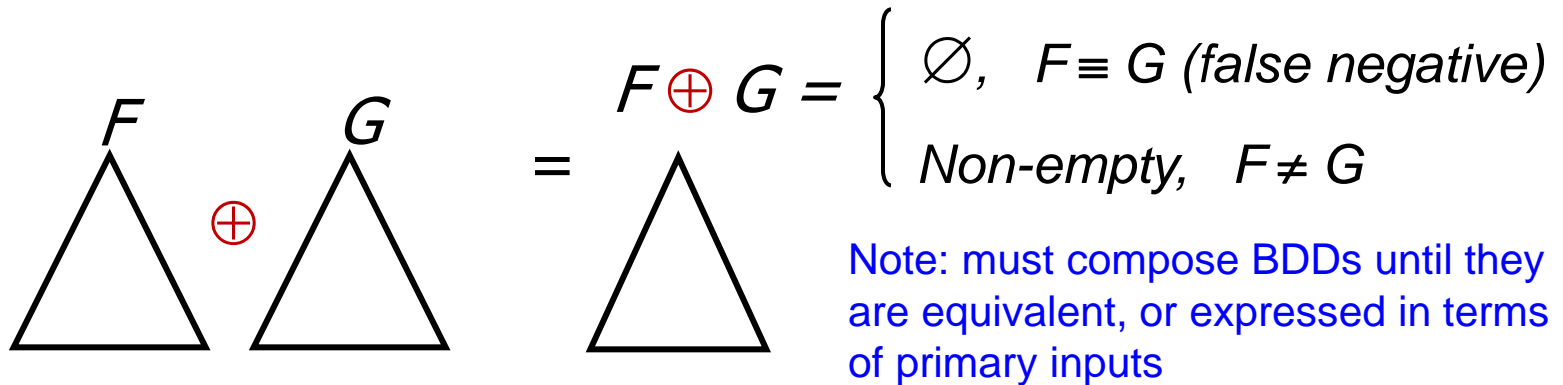
- Procedure 2: **create a BDD for $F \oplus G$**
 - perform satisfiability analysis (SAT) of the BDD
 - if BDD for $F \oplus G = \emptyset$, problem is *not* satisfiable, *false negative*
 - BDD for $F \oplus G \neq \emptyset$, problem is satisfiable, *true negative*



- the SAT solution, if exists, provides a *test vector* (proof of non-equivalence) – as in ATPG
- unlike the ATPG technique, it is effective for false negative (the BDD is empty!)

Sequential Equivalence Checking

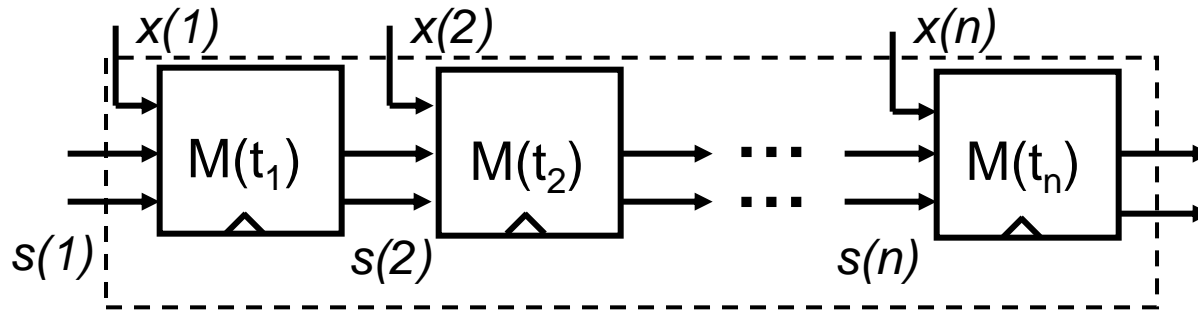- Represent each sequential circuit as an FSM
 - verify if two FSMs are equivalent
- Approach 1: Reduction to *combinational* circuit
 - unroll FSM over n time frames (flatten the design)




Combinational logic: $F(x(1,2, \dots n), s(1,2, \dots n))$

- check equivalence of the resulting combinational circuits
- problem: the resulting circuit can be too large to handle

Sequential Verification

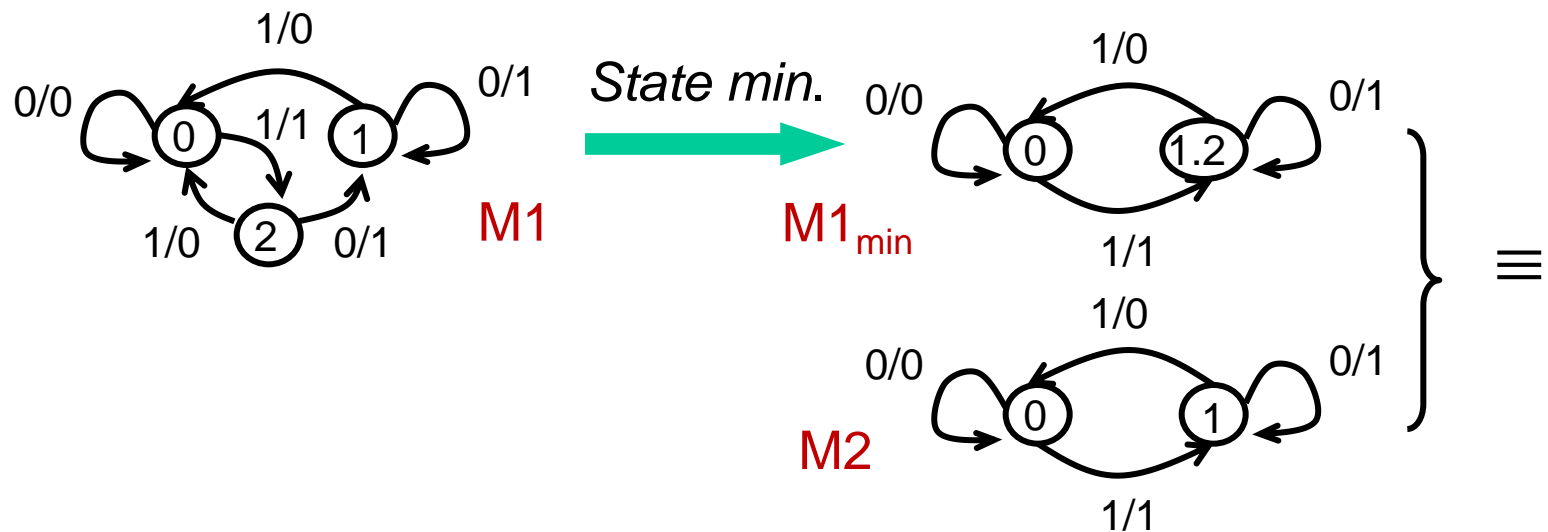- Approach 2: **Based on isomorphism of state transition graphs**
 - two machines M1, M2 are *equivalent* if their state transition graphs (STGs) are *isomorphic*
 - perform **state minimization** of each machine
 - check if STG(M1) and STG(M2) are isomorphic



State Minimization

X-Successor – If an input sequence X takes a machine from state S_i to state S_j , then S_j is said to be the X -successor of S_i

Strongly connected:- If for every pair of states (S_i, S_j) of a machine M there exists an input sequence which takes M from state S_i to S_j , then M is said to be strongly connected

State Equivalence

- Two states S_i and S_j of machine M are **distinguishable** if and only if there exists at least one finite input sequence which, when applied to M , causes different output sequences, depending on whether S_i or S_j is the initial state
- The sequence which distinguishes these states is called a **distinguishing sequence of the pair (S_i, S_j)**
- If there exists for pair (S_i, S_j) a distinguishing sequence of length k , the states in (S_i, S_j) are said to be **k -distinguishable**

State Equivalence

Machine M1

PS	NS, z	
	X = 0	X = 1
A	E, 0	D, 1
B	F, 0	D, 0
C	E, 0	B, 1
D	F, 0	B, 0
E	C, 0	F, 1
F	B, 0	C, 0

(A, B) – 1 Distinguishable

(A, E) – 3 Distinguishable

Seq - 111

k-equivalent – The states that are **not k-distinguishable** are said to be k-equivalent

Also *r-equivalent* $r < k$

State Equivalence

- States S_i and S_j of machine \mathbf{M} are said to be **equivalent** if and only if, **for every possible input sequence**, the same output sequence will be produced regardless of whether S_i or S_j is the initial state
- States that are k -equivalent for all $k < n-1$, are equivalent
- $S_i = S_j$, and $S_j = S_k$, then $S_i = S_k$

State Equivalence

- The set of states of a machine M can be partitioned into disjoint subsets, known as equivalence classes
- Two states are in the same equivalence class if and only if they are equivalent, and are in different classes if and only if they are distinguishable

Property: If S_i and S_j are equivalent states, their corresponding X -successors, for all X , are also equivalent

State Minimization Procedure

1. Partition the states of M into subsets s.t. all states in same subset are *1-equivalent*
2. Two states are 2-equivalent iff they are 1-equivalent and their I_i successors, for all possible I_i , are also 1-equivalent

PS	NS, z	
	X = 0	X = 1
A	E, 0	D, 1
B	F, 0	D, 0
C	E, 0	B, 1
D	F, 0	B, 0
E	C, 0	F, 1
F	B, 0	C, 0

$P_0 = (ABCDEF)$

$P_1 = (ACE), (BDF)$

$P_2 = (ACE), (BD), (F)$

$P_3 = (AC), (E), (BD), (F)$

$P_4 = (AC), (E), (BD), (F)$

Machine Equivalence

- Two machines M1, M2 are said to be equivalent if and only if, for every state in M1, there is corresponding equivalent state in M2
- If one machine can be obtained from the other by relabeling its states they are said to be **isomorphic** to each other

PS	NS, z	
	X = 0	X = 1
AC - α	$\beta, 0$	$\gamma, 1$
E - β	$\alpha, 0$	$\delta, 1$
BD - γ	$\delta, 0$	$\gamma, 0$
F - δ	$\gamma, 0$	$\alpha, 0$

State Equivalence - Example

Machine M2

PS	NS, z	
	X = 0	X = 1
A	E, 0	C, 0
B	C, 0	A, 0
C	B, 0	G, 0
D	G, 0	A, 0
E	F, 1	B, 0
F	E, 0	D, 0
G	D, 0	G, 0

P0 = (ABCDEFGG)

P1 = (ABCDFG) (E)

P2 = (AF) (BCDG) (E)



P3 = (AF) (BD) (CG) (E)

P4 = (A) (F) (BD) (CG) (E)

P5 = (A) (F) (BD) (CG) (E)

Reachability-Based Equivalence Checking

 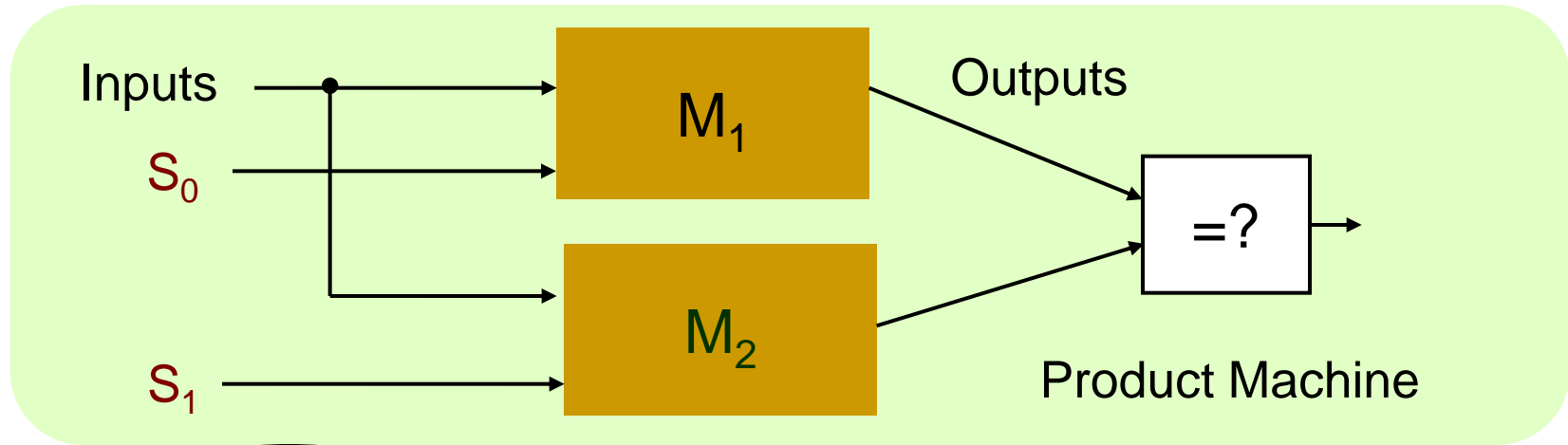
Approach 3: Symbolic Traversal Based Reachability Analysis



- Build product machine of M_1 and M_2
- Traverse state-space of product machine starting from reset states S_0, S_1
- Test equivalence of outputs in each state
- Can use any state-space traversal technique

Sequential Verification

- Symbolic FSM traversal of the product machine
- Given two FSMs: $M_1(X, S_1, \delta_1, \lambda_1, O_1)$,
 $M_2(X, S_2, \delta_2, \lambda_2, O_2)$
- Create a product FSM: $M = M_1 \times M_2$
 - traverse the states of M and check its output for each transition
 - the output $O(M) = 1$, if outputs $O_1 = O_2$
 - if all outputs of M are 1, M_1 and M_2 are *equivalent*
 - otherwise, an *error state* is reached
 - *error trace* is produced to show: $M_1 \neq M_2$

 


Product Machine - Construction

- Define the product machine $M(X, S, S^0, \delta, \lambda, O)$
 - states, $S = S_1 \times S_2$
 - next state function, $\delta(s, x) : (S_1 \times S_2) \times X \rightarrow (S_1 \times S_2)$
 - output function, $\lambda(s, x) : (S_1 \times S_2) \times X \rightarrow \{0,1\}$

$$O = \begin{cases} 1 & \text{if } O_1 = O_2 \\ 0 & \text{otherwise} \end{cases}$$
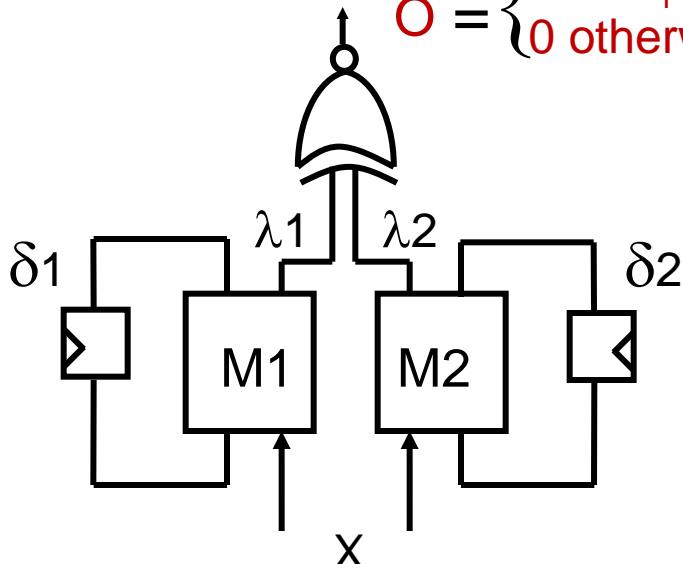
$$\lambda(s, x) = \lambda_1(s_1, x) \overline{\oplus} \lambda_2(s_2, x)$$



- Error trace (*distinguishing sequence*) that leads to an error state
 - sequence of inputs which produces 1 at the output of M
 - produces a state in M for which M1 and M2 give different outputs

FSM Traversal - Algorithm

- Traverse the product machine $M(X,S,\delta, \lambda,O)$
 - start at an initial state S_0
 - iteratively compute symbolic image $Img(S_0,R)$ (set of *next states*):

$$Img(S_0,R) = \exists_x \exists_s S_0(s) \bullet R(x,s,t)$$



$$R = \prod_i R_i = \prod_i (t_i \equiv \delta_i(s,x))$$

until an *error state* is reached


- transition relation R_i for each next state variable t_i can be computed as $t_i = (t \otimes \delta(s,x))$

(this is an alternative way to compute transition relation, when design is specified at gate level)



Construction of the Product FSM

  

 - For each pair of states, $s_1 \in M_1$, $s_2 \in M_2$
 - create a combined state $s = (s_1, s_2)$ of M
 - create transitions out of this state to other states of M
 - label the transitions (*input/output*) accordingly




FSM Traversal in Action

  

Initial states: $s_1=0$, $s_2=0$, $s=(0.0)$

State reached	Out(M)	
	x=0	x=1

 - $New^0 = (0.0)$ 1 1
- $New^1 = (1.1)$ 1 1
- $New^2 = (0.2)$ 1 1
- $New^3 = (1.0)$ 0 0



- **STOP** - backtrack to initial state to get *error trace*: $x=\{1,1,1,0\}$

Thank you

