

Yield and Fault Modeling

Virendra Singh

Associate Professor

Computer Architecture and Dependable Systems Lab

Dept. of Electrical Engineering

Indian Institute of Technology Bombay, Mumbai

viren@ee.iitb.ac.in



EE 709: Testing & Verification of VLSI Circuits

Lecture – 5 (Jan 16, 2012)


VLSI Chip Yield

- ❖ A manufacturing defect is a finite chip area with electrically malfunctioning circuitry caused by errors in the fabrication process.
- ❖ A chip with no manufacturing defect is called a good chip.
- ❖ Fraction (or percentage) of good chips produced in a manufacturing process is called the *yield*. Yield is denoted by symbol Y .
- ❖ Cost of a chip:

Cost of fabricating and testing a wafer

Yield x Number of chip sites on the wafer

Clustered VLSI Defects

 

Unclustered defects
Wafer yield = $12/22 = 0.55$

Clustered defects (VLSI)
Wafer yield = $17/22 = 0.77$

Yield Parameters

- Defect density (d) = Average number of defects per unit of chip area
- Chip area (A)
- Clustering parameter (α)
- Negative binomial distribution of defects,
 $p(x) = \text{Prob}(\text{number of defects on a chip} = x)$

$$p(x) = \frac{\Gamma(\alpha + x)}{x! \Gamma(\alpha)} \left(\frac{Ad}{\alpha} \right)^x \left(1 + \frac{Ad}{\alpha} \right)^{-\alpha - x}$$

where Γ is the gamma function

$\alpha = 0$, $p(x)$ is a delta function (maximum clustering)

$\alpha = \infty$, $p(x)$ is Poisson distribution (no clustering)

Yield Equation

$Y = \text{Prob (zero defect on a chip)} = p(0)$

$$Y = (1 + Ad / \alpha)^{- \alpha}$$

Example: $Ad = 1.0, \alpha = 0.5, Y = 0.58$

Unclustered defects: $\alpha = \infty, Y = e^{- Ad}$

Example: $Ad = 1.0, \alpha = \infty, Y = 0.37$

too pessimistic !

Defect Level or Reject Ratio

- ❖ *Defect level* (DL) is the ratio of faulty chips among the chips that pass tests.
- ❖ DL is measured as *parts per million* (ppm).
- ❖ DL is a measure of the effectiveness of tests.
- ❖ DL is a quantitative measure of the manufactured **product quality**. For commercial VLSI chips a DL greater than **500 ppm** is considered unacceptable.

Determination of DL

- ❖ From field return data: Chips failing in the field are returned to the manufacturer. The number of returned chips normalized to one million chips shipped is the DL.
- ❖ From test data: Fault coverage of tests and chip fallout rate are analyzed. A modified yield model is fitted to the fallout data to estimate the DL.

Modified Yield Equation

- **Three parameters:**
 - **Fault density, f = average number of stuck-at faults per unit chip area**
 - **Fault clustering parameter, β**
 - **Stuck-at fault coverage, T**

- **The modified yield equation:**

$$Y(T) = (1 + T Af / \beta)^{-\beta}$$

Assuming that tests with 100% fault coverage ($T=1.0$) remove all faulty chips,


$$Y = Y(1) = (1 + Af / \beta)^{-\beta}$$

Defect Level


$$DL(T) = \frac{Y(T) - Y(1)}{Y(T)}$$
$$= 1 - \frac{(\beta + TAf)^\beta}{(\beta + Af)^\beta}$$

Where T is the fault coverage of tests, Af is the average number of faults on the chip of area A , β is the fault clustering parameter. Af and β are determined by test data analysis.

Yield and Fault Coverage

 


Computed DL

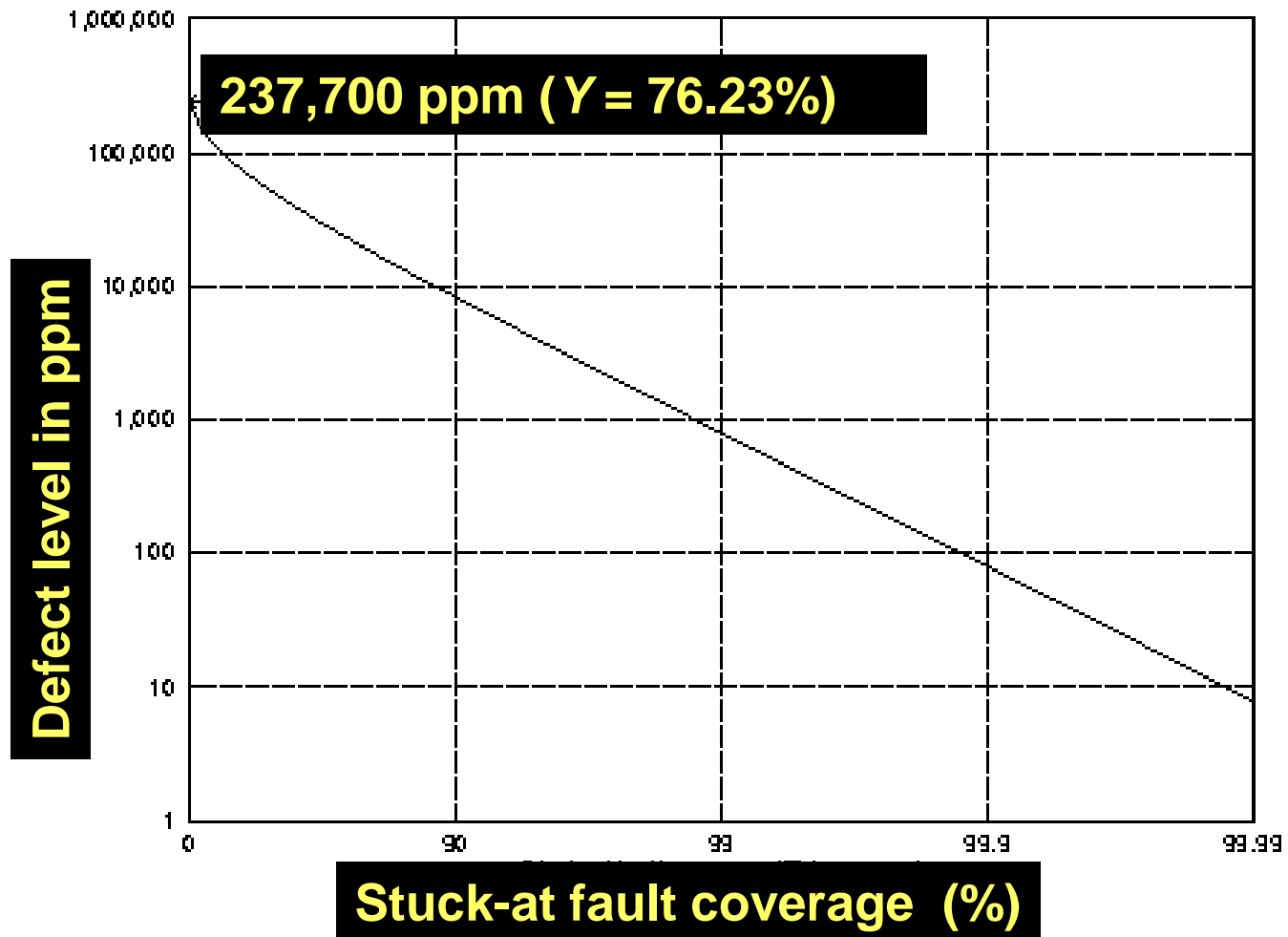


SEMATECH Chip (Courtesy: IBM)

Time to Market

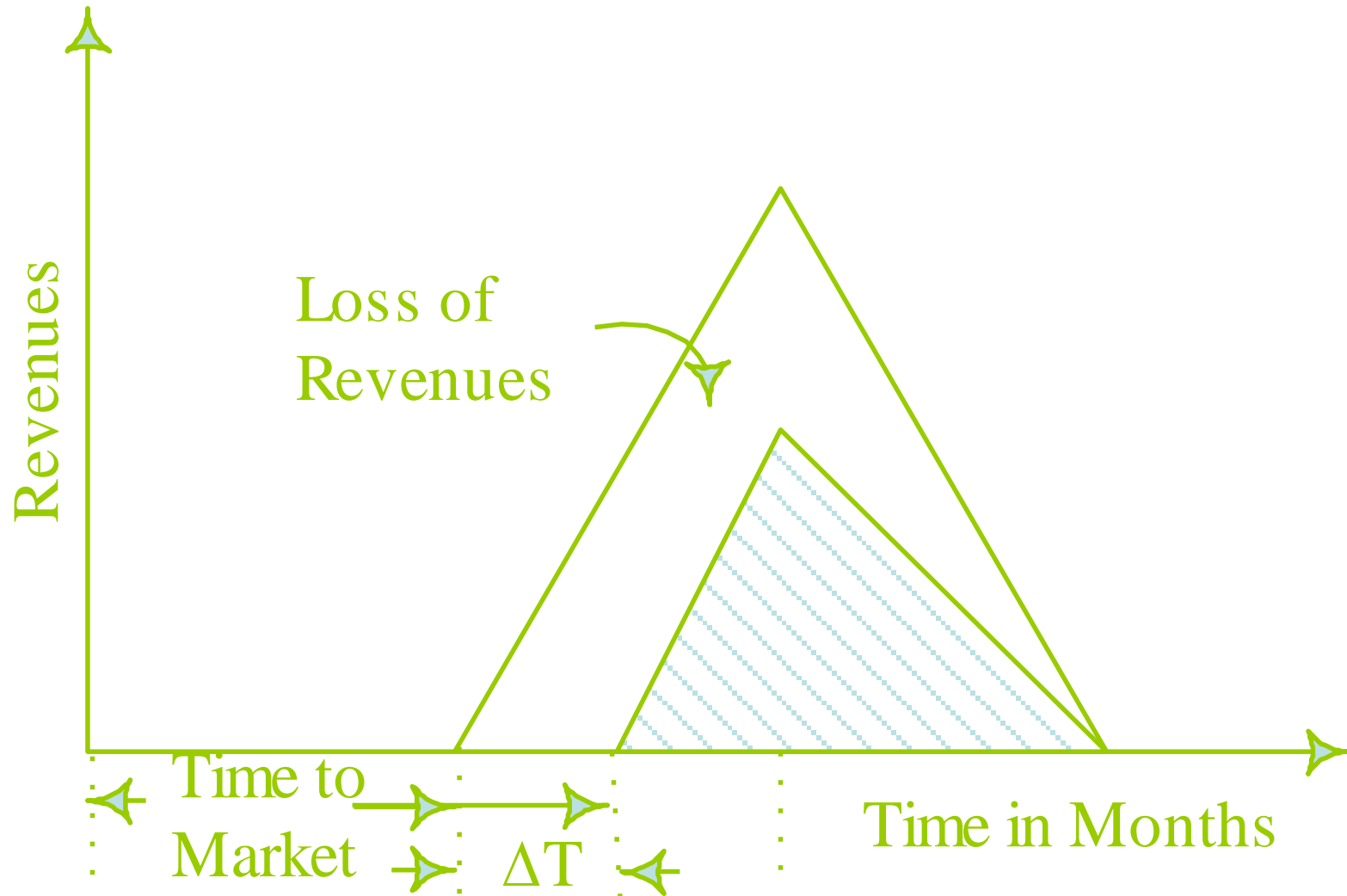

Failure Rate Vs Product Lifetime

 


Common Fault Models


- **Single stuck-at faults**
- **Transistor open and short faults**
- **Memory faults**
- **PLA faults (stuck-at, cross-point, bridging)**
- **Functional faults (processors)**
- **Delay faults (transition, path)**
- **Analog faults**

Single Stuck-at Fault

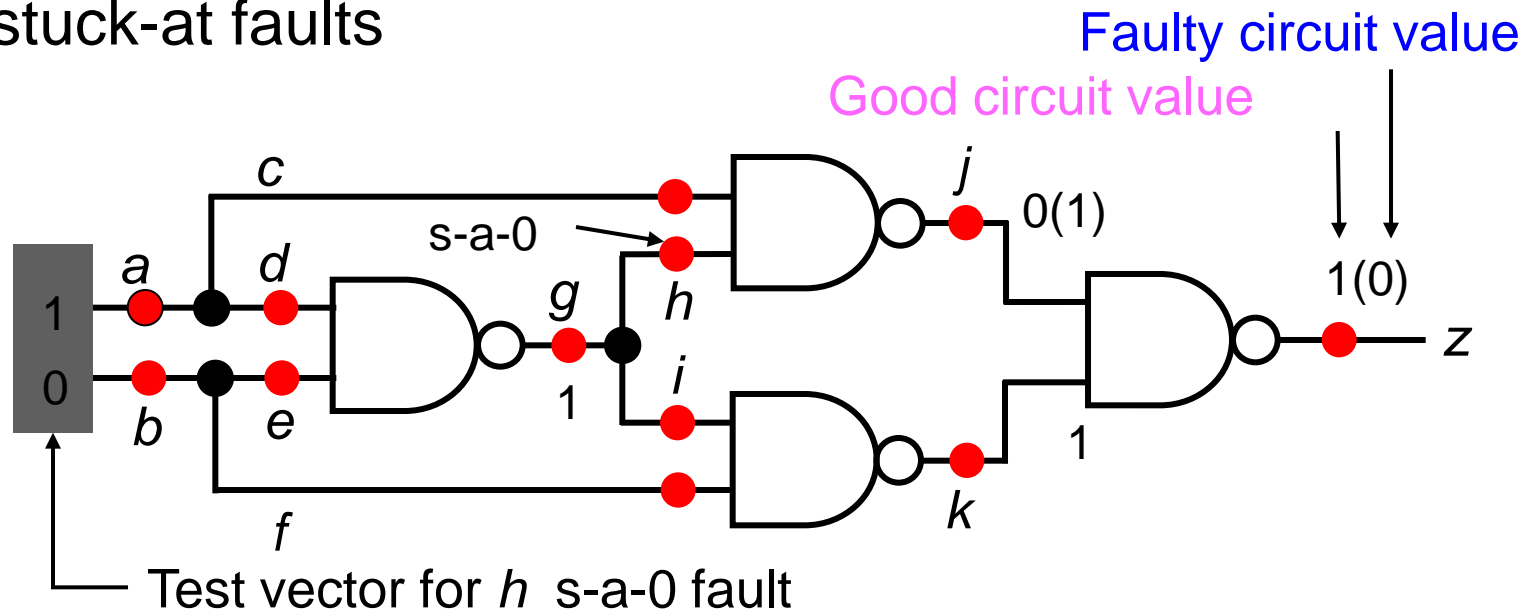- ❖ Three properties define a single stuck-at fault
 - Only one line is faulty
 - The faulty line is permanently set to 0 or 1
 - The fault can be at an input or output of a gate
- ❖ Example: XOR circuit has 12 fault sites (●) and 24 single stuck-at faults




SA Faults

 








Inputs AB	FF Response	Faulty Response					
		A/0	B/0	Z/0	A/1	B/1	Z/1
00	0	0	0	0	0	0	1
01	0	0	0	0	1	0	1
10	0	0	0	0	0	1	1
11	1	0	0	0	1	1	1

SA Faults

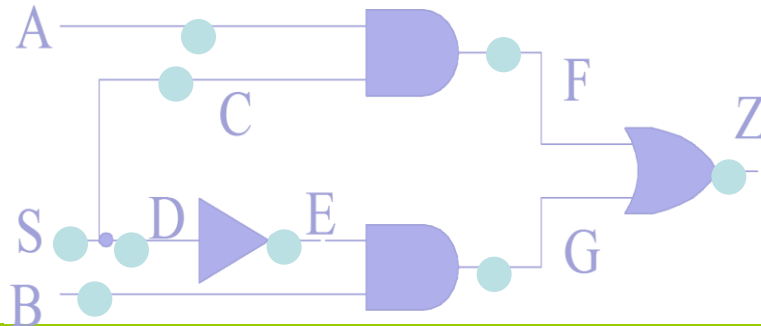


Inp SA	Response						
	FF	S/0	S/1	C/0	C/1	D/0	D/1
000	0	0	0	0	0	0	0
001	1	1	0	1	1	1	0
010	0	0	1	0	1	0	0
011	1	1	1	1	1	1	0
100	0	0	0	0	0	0	0
101	0	1	0	0	0	1	0
110	1	0	1	0	1	1	1
111	1	1	1	0	1	1	1

Equivalence Rules

  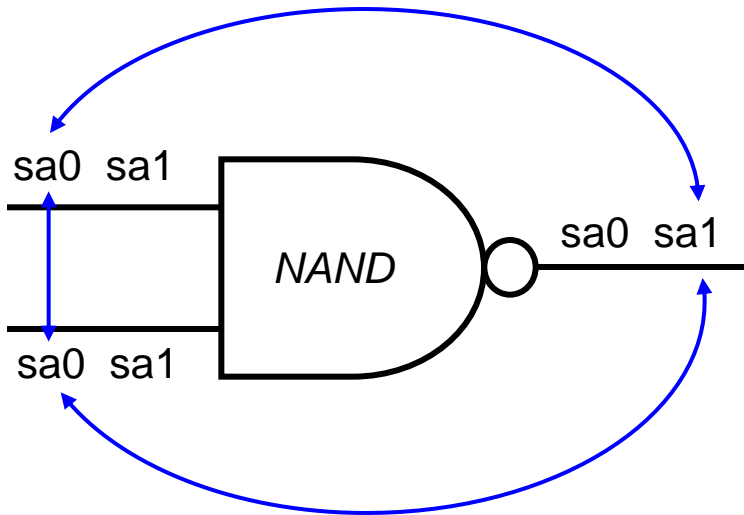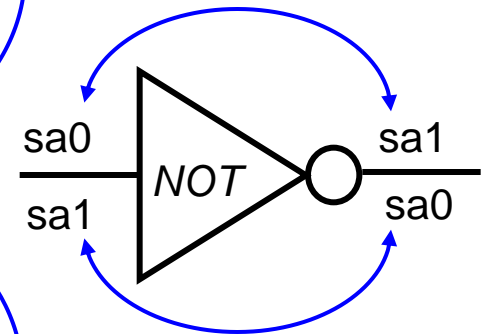 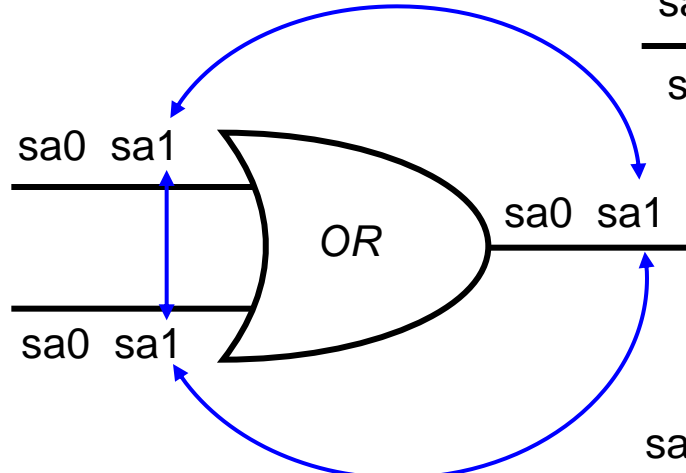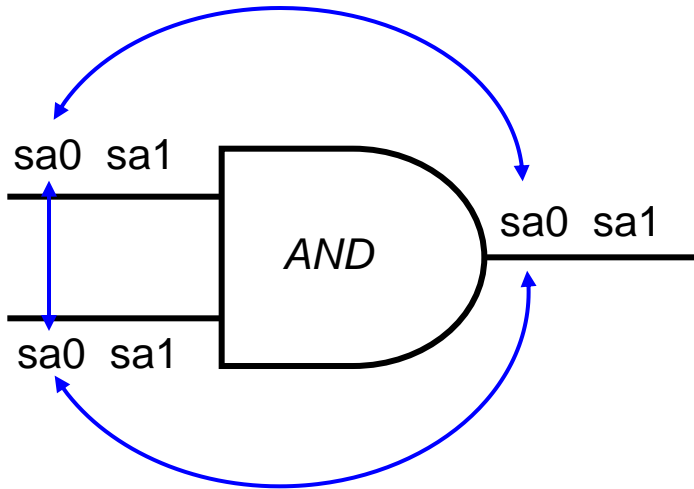


Equivalence Example

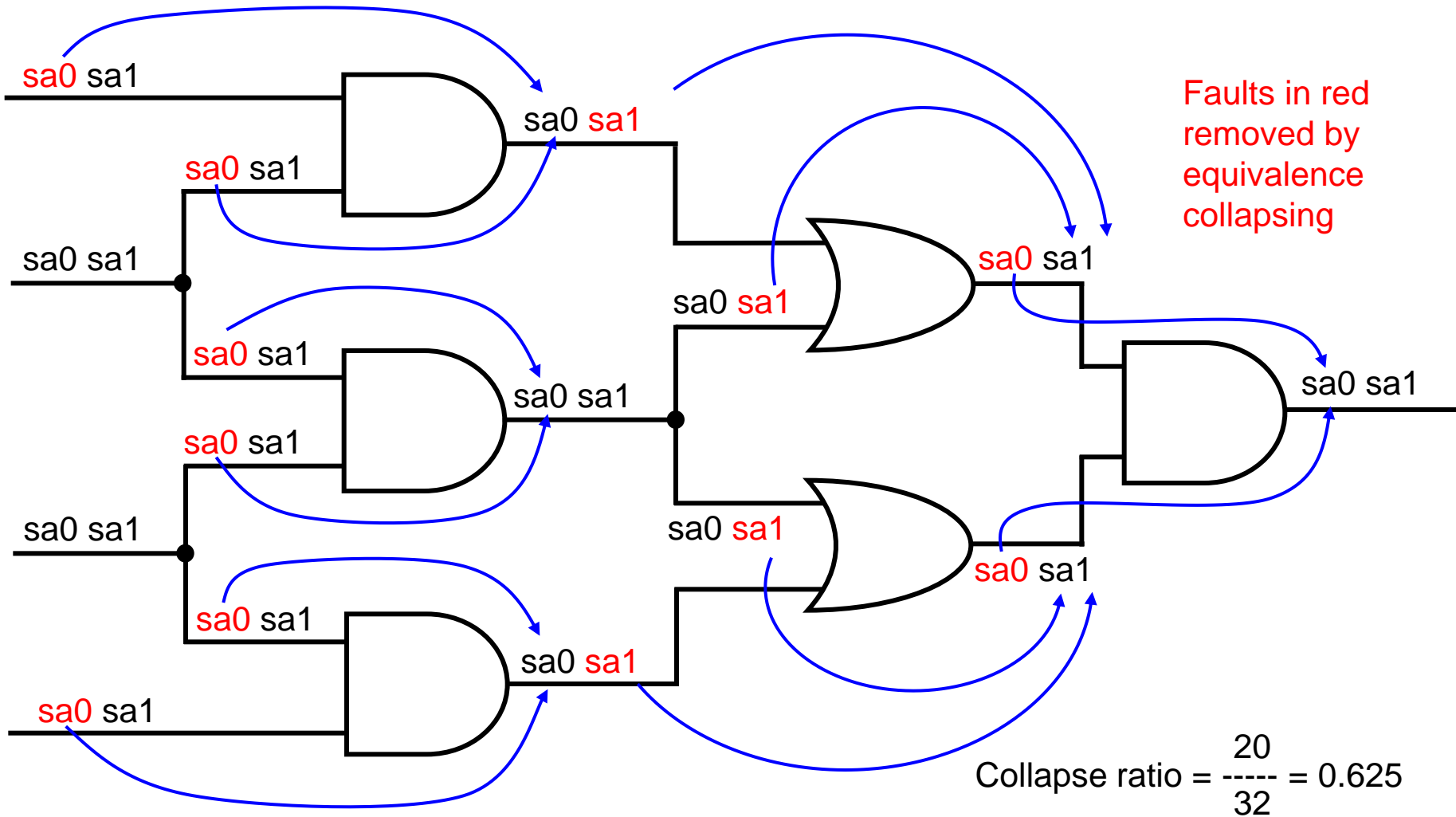

Fault Dominance


- ❖ If all tests of some fault $F1$ detect another fault $F2$, then $F2$ is said to dominate $F1$.
- ❖ Dominance fault collapsing: If fault $F2$ dominates $F1$, then $F2$ is removed from the fault list.
- ❖ When dominance fault collapsing is used, it is sufficient to consider only the input faults of Boolean gates.
- ❖ In a tree circuit (without fanouts) PI faults form a dominance collapsed fault set.
- ❖ **If two faults dominate each other then they are equivalent.**

Dominance Example

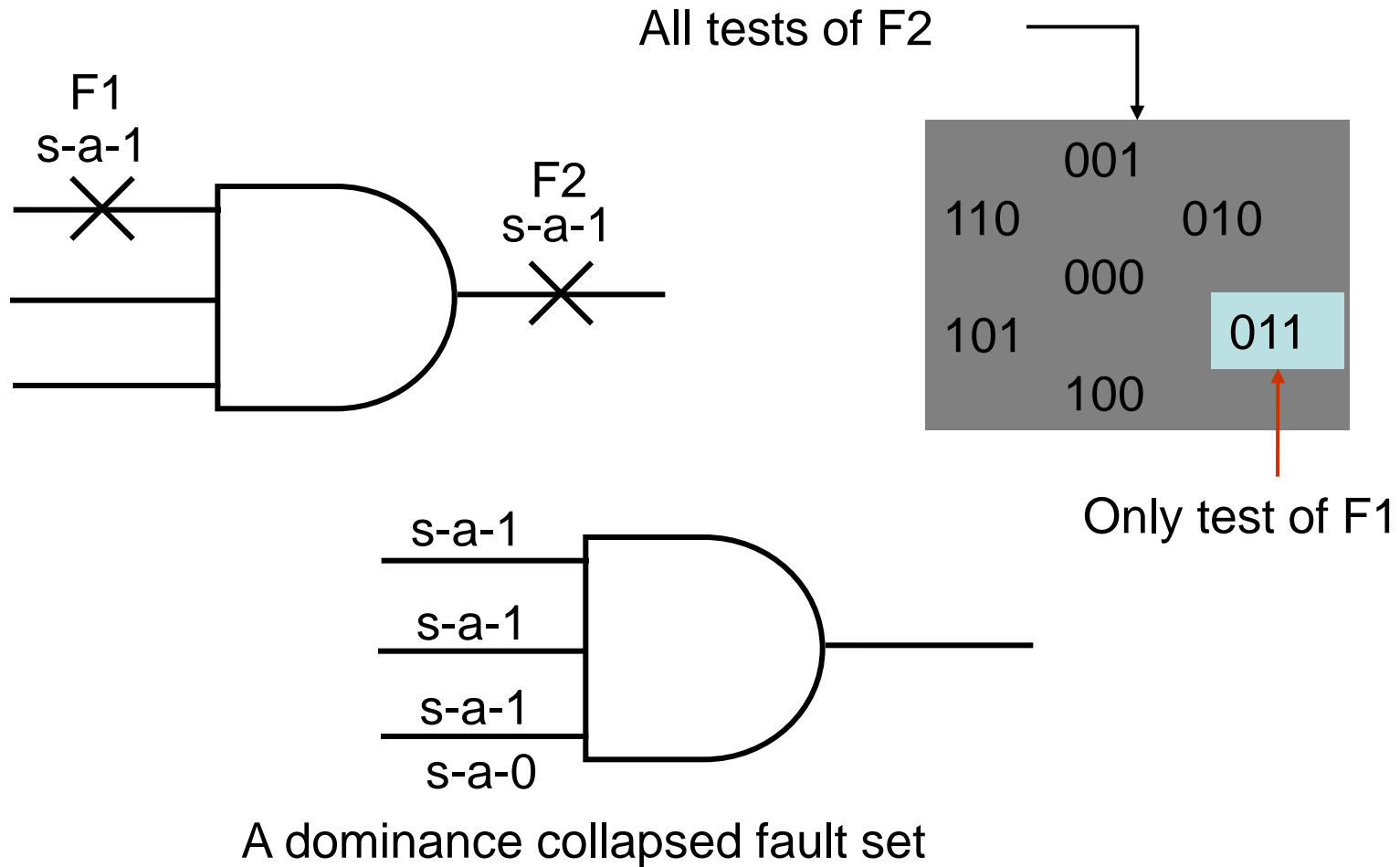

Checkpoints

 - ❖ Primary inputs and fanout branches of a combinational circuit are called *checkpoints*.
- ❖ Checkpoint theorem: A test set that detects all single (multiple) stuck-at faults on all checkpoints of a combinational circuit, also detects all single (multiple) stuck-at faults in that circuit.



Multiple Stuck-at Faults

- ❖ A multiple stuck-at fault means that any set of lines is stuck-at some combination of (0,1) values.
- ❖ The total number of single and multiple stuck-at faults in a circuit with k single fault sites is 3^k-1 .
- ❖ A single fault test can fail to detect the target fault if another fault is also present, however, such **masking** of one fault by another is rare.
- ❖ **Statistically, single fault tests cover a very large number of multiple faults.**

Transistor (Switch) Faults



- ❖ MOS transistor is considered an ideal switch and two types of faults are modeled:
 - Stuck-open -- a single transistor is permanently stuck in the open state.
 - Stuck-short -- a single transistor is permanently shorted irrespective of its gate voltage.
- ❖ Detection of a stuck-open fault requires two vectors.
- ❖ Detection of a stuck-short fault requires the measurement of quiescent current (I_{DDQ}).

Stuck-Open Example


Vector 1: test for A s-a-0
(Initialization vector)

Vector 2 (test for A s-a-1)

 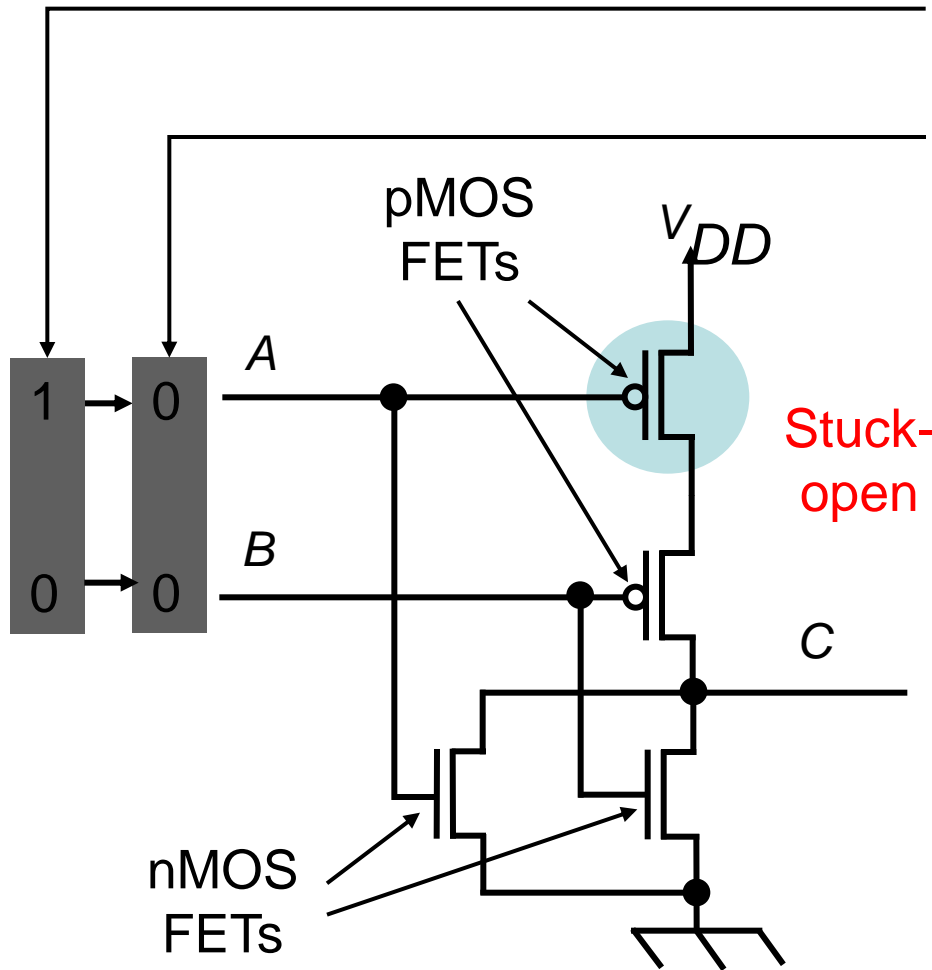*Two-vector s-op test
can be constructed by
ordering two s-at tests*



Stuck-Short Example

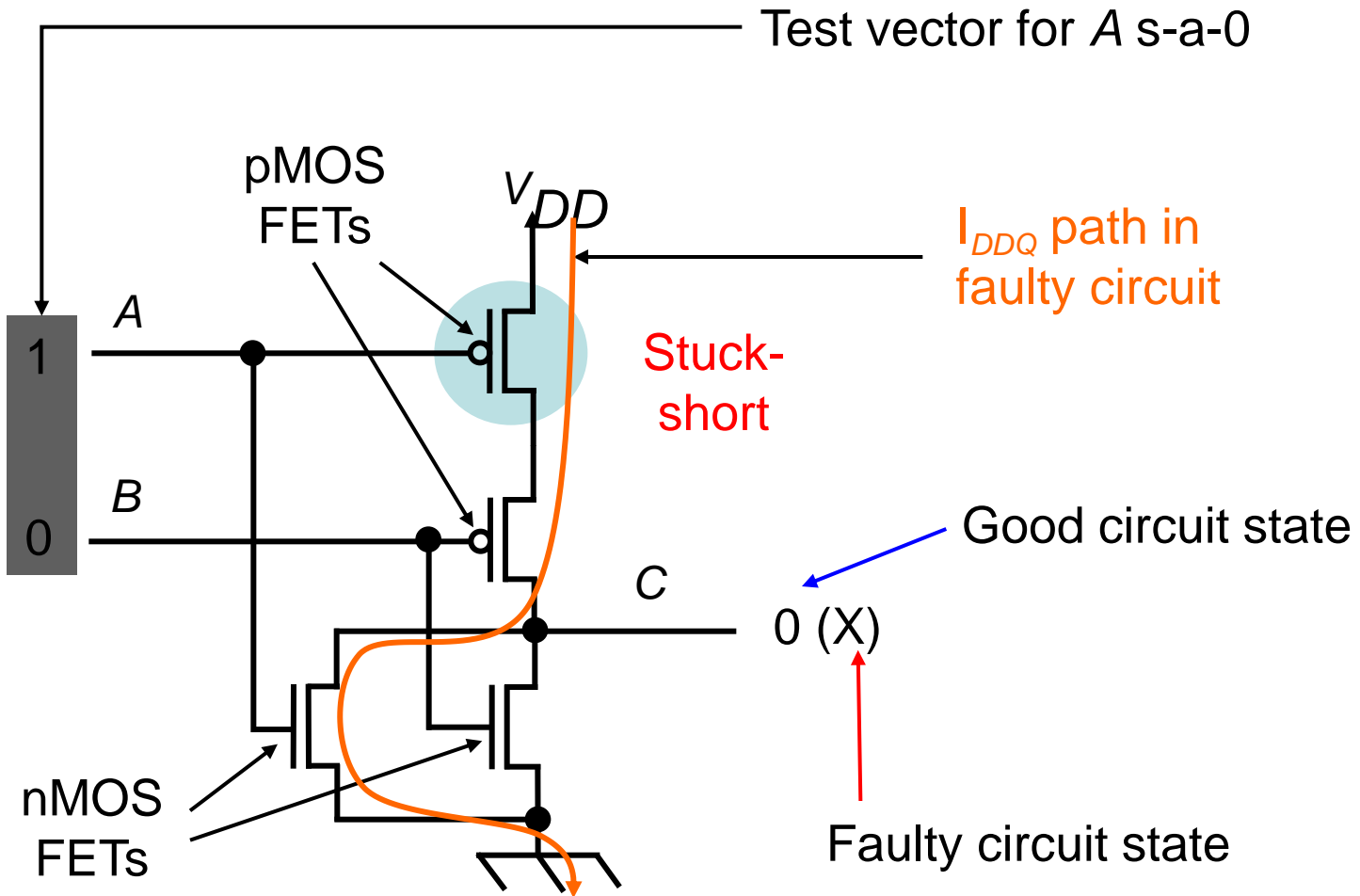

Fault Model - Summary

- Fault models are analyzable approximations of defects and are essential for a test methodology.
- For digital logic single stuck-at fault model offers best advantage of tools and experience.
- Many other faults (bridging, stuck-open and multiple stuck-at) are largely covered by stuck-at fault tests.
- Stuck-short and delay faults and technology-dependent faults require special tests.
- Memory and analog circuits need other specialized fault models and tests.

Thank You

