

Reduced Instruction Set Computer

Virendra Singh

Associate Professor

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering
Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: viren@ee.iitb.ac.in


Computer Organization & Architecture



Lecture 11 (09 April 2013)

CADSL

Processor Architecture

 


Where Does It All Begin?


- In a register called *program counter (PC)*.
- PC contains the memory address of the next instruction to be executed.
- In the beginning, PC contains the address of the memory location where the program begins.



Where is the Program?

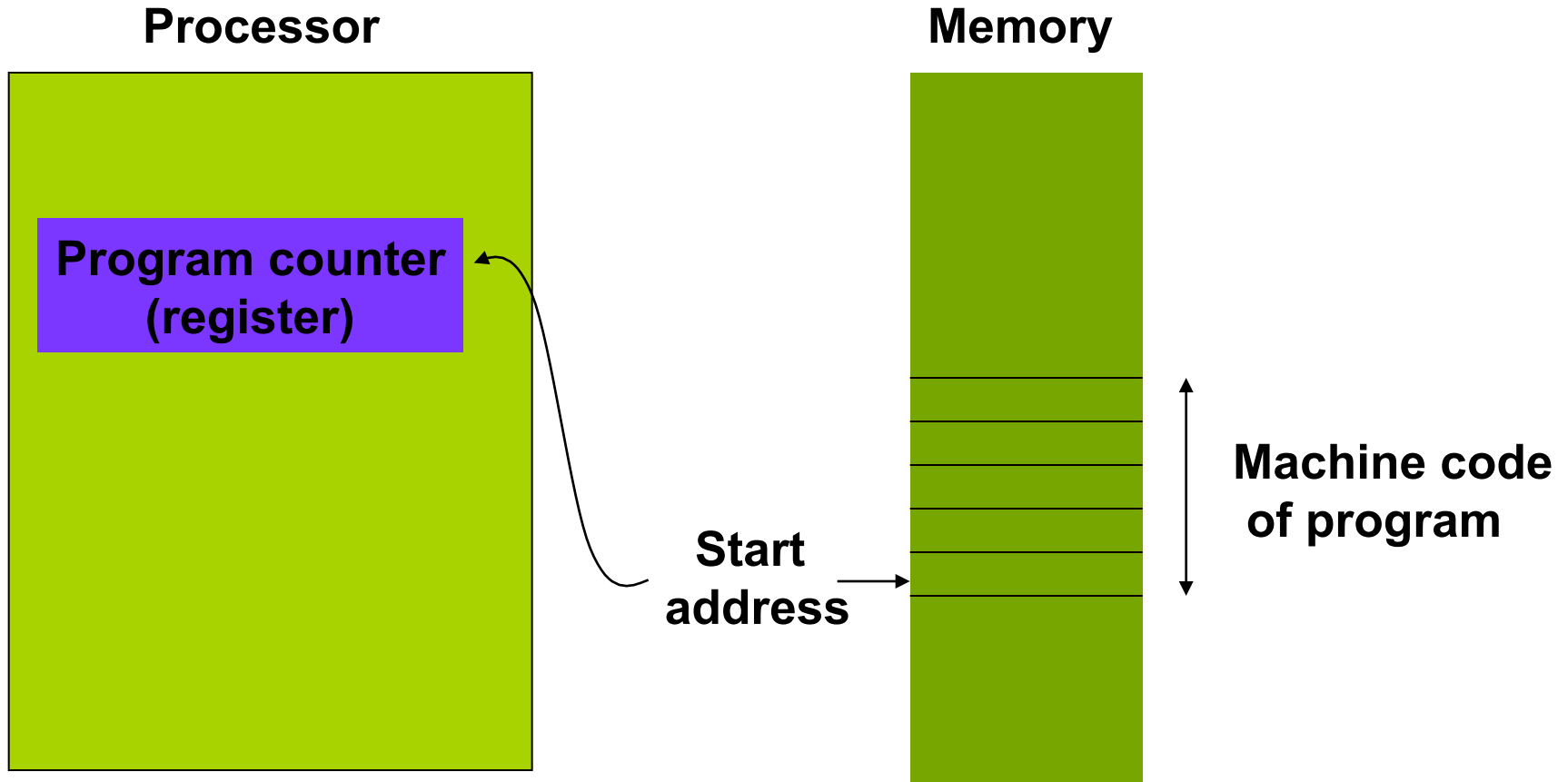

How Does It Run?

 


Datapath and Control


- Datapath: Memory, registers, adders, ALU, and communication buses. Each step (fetch, decode, execute) requires communication (data transfer) paths between memory, registers and ALU.
- Control: Datapath for each step is set up by control signals that set up dataflow directions on communication buses and select ALU and memory functions. Control signals are generated by a control unit consisting of one or more finite-state machines.



Datapath for Instruction Fetch

 

Register File: A Datapath Component

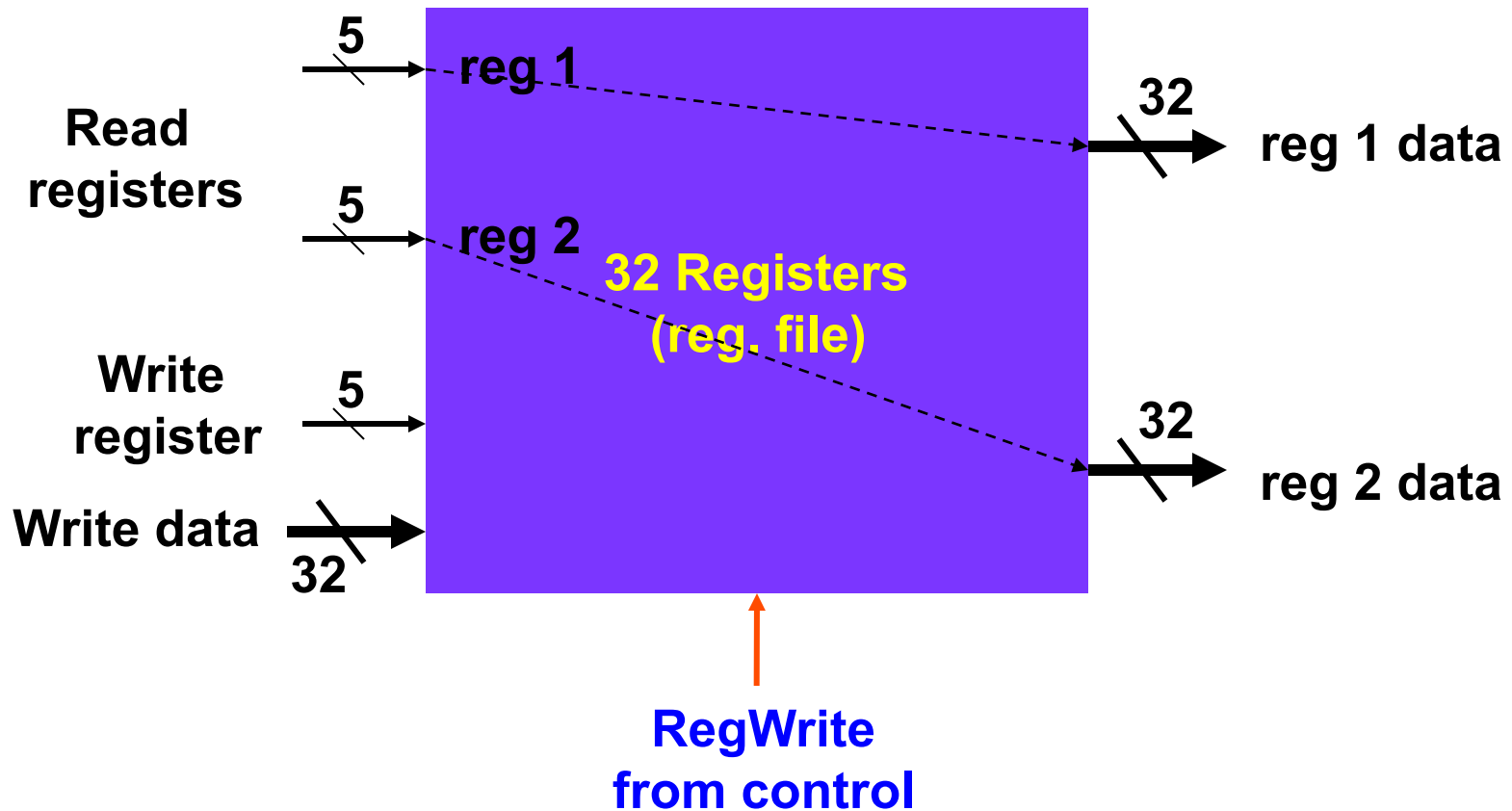

Multi-Operation ALU

Operation
select

ALU function

000

AND

001

OR

010


Add

110

Subtract

111

Set on less than

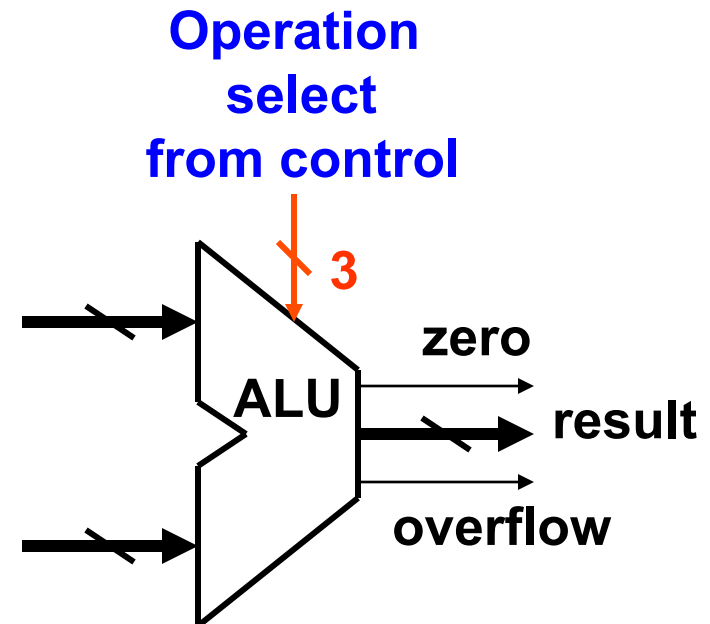

zero = 1, when all bits of result are 0



R-Type Instructions

- Also known as arithmetic-logical instructions

- **add, sub, slt**

- Example: add \$t0, \$s1, \$s2

- Machine instruction word

000000 10001 10010 01000 00000 100000

opcode \$s1 \$s2 \$t0 function


- Read two registers

- Write one register

- Opcode and function code go to control unit that generates RegWrite and ALU operation code.



Datapath for R-Type Instruction

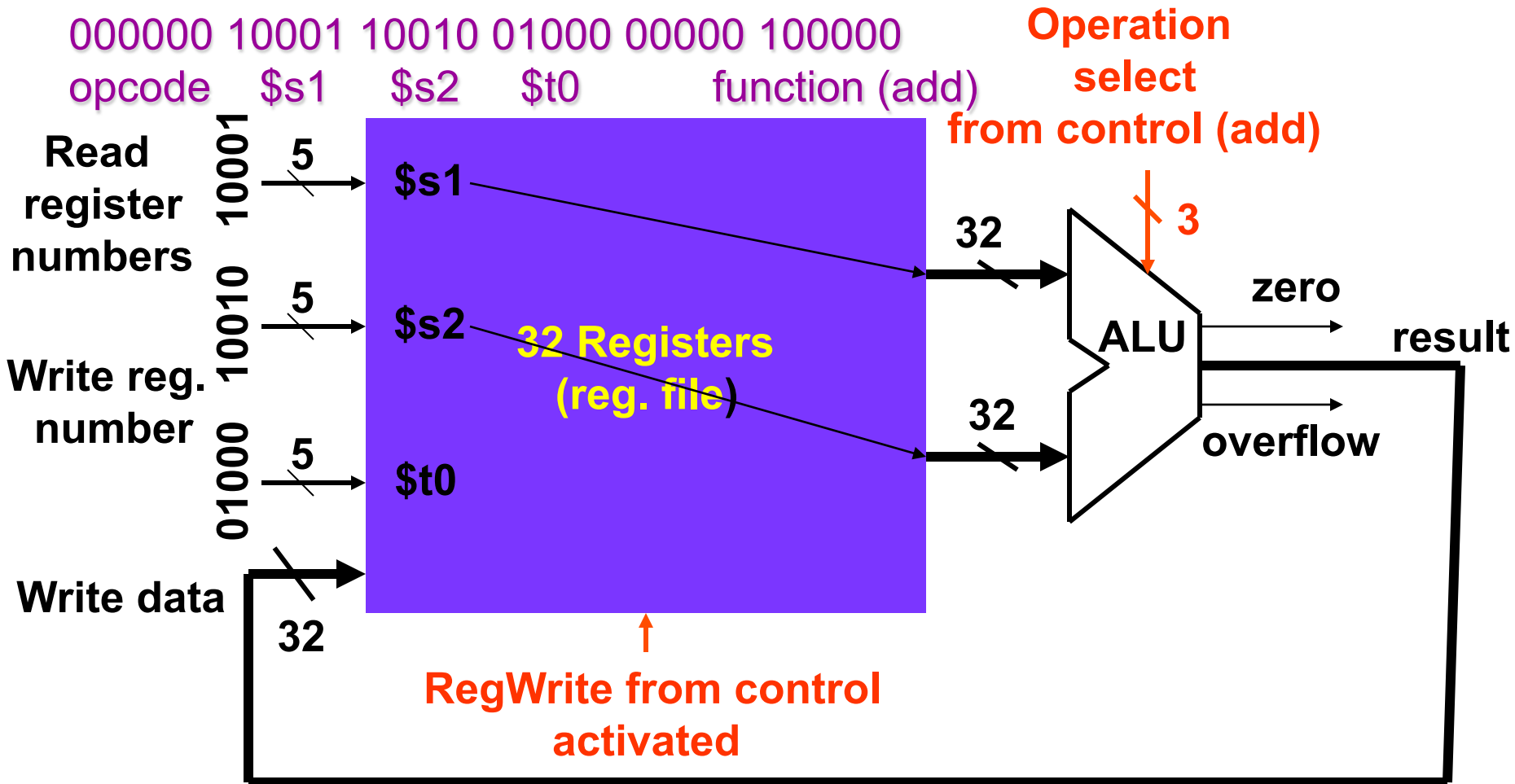

Load and Store Instructions

- I-type instructions
- lw \$t0, 1200 (\$t1) # incr. in bytes

100011 01001 01000 0000 0100 1011 0000

opcode \$t1 \$t0 1200

- sw \$t0, 1200 (\$t1) # incr. in bytes


101011 01001 01000 0000 0100 1011 0000

opcode \$t1 \$t0 1200




Datapath for lw Instruction

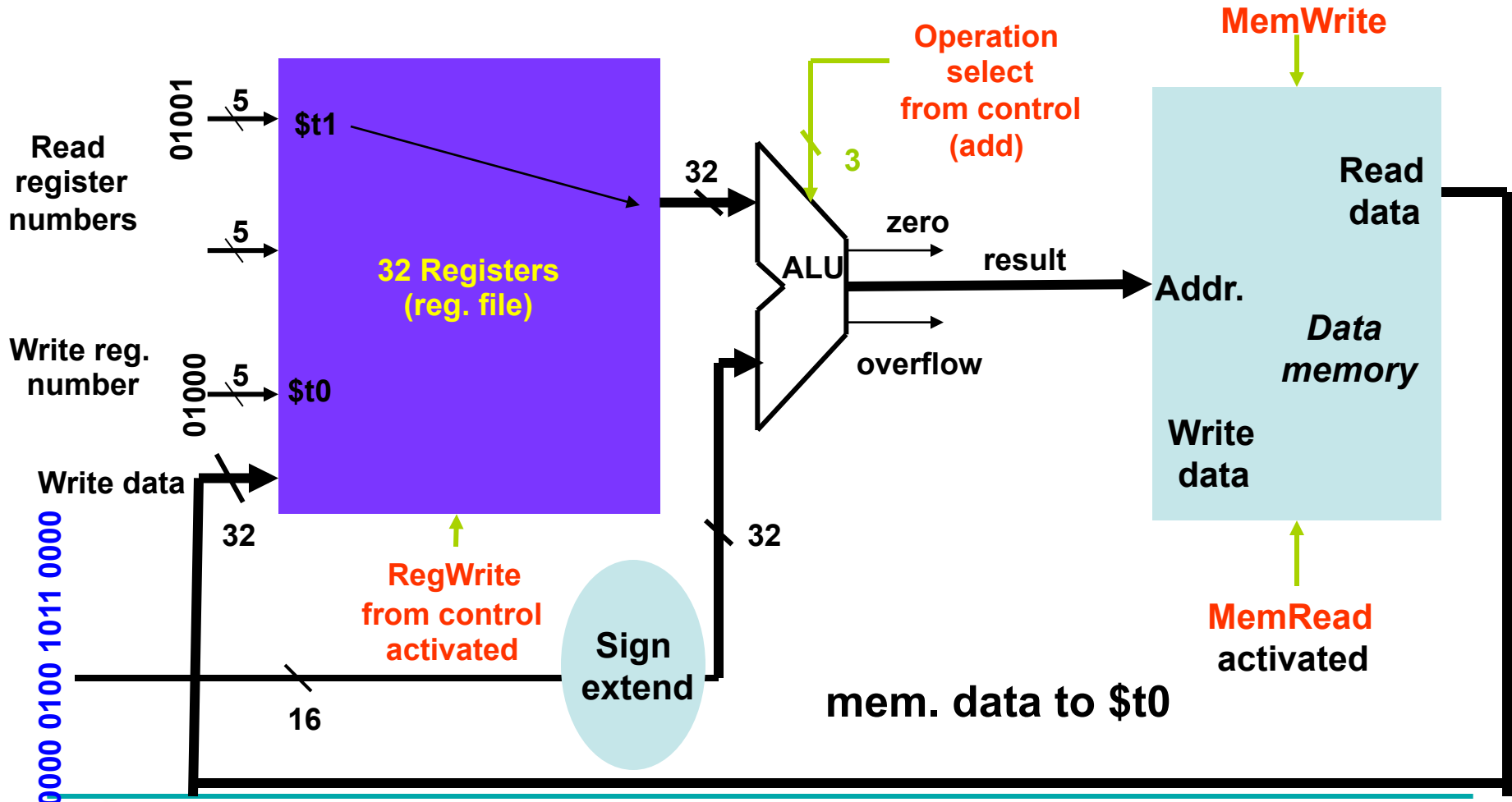100011 01001 01000 0000 0100 1011 0000
 opcode \$t1 \$t0 1200



Datapath for sw Instruction

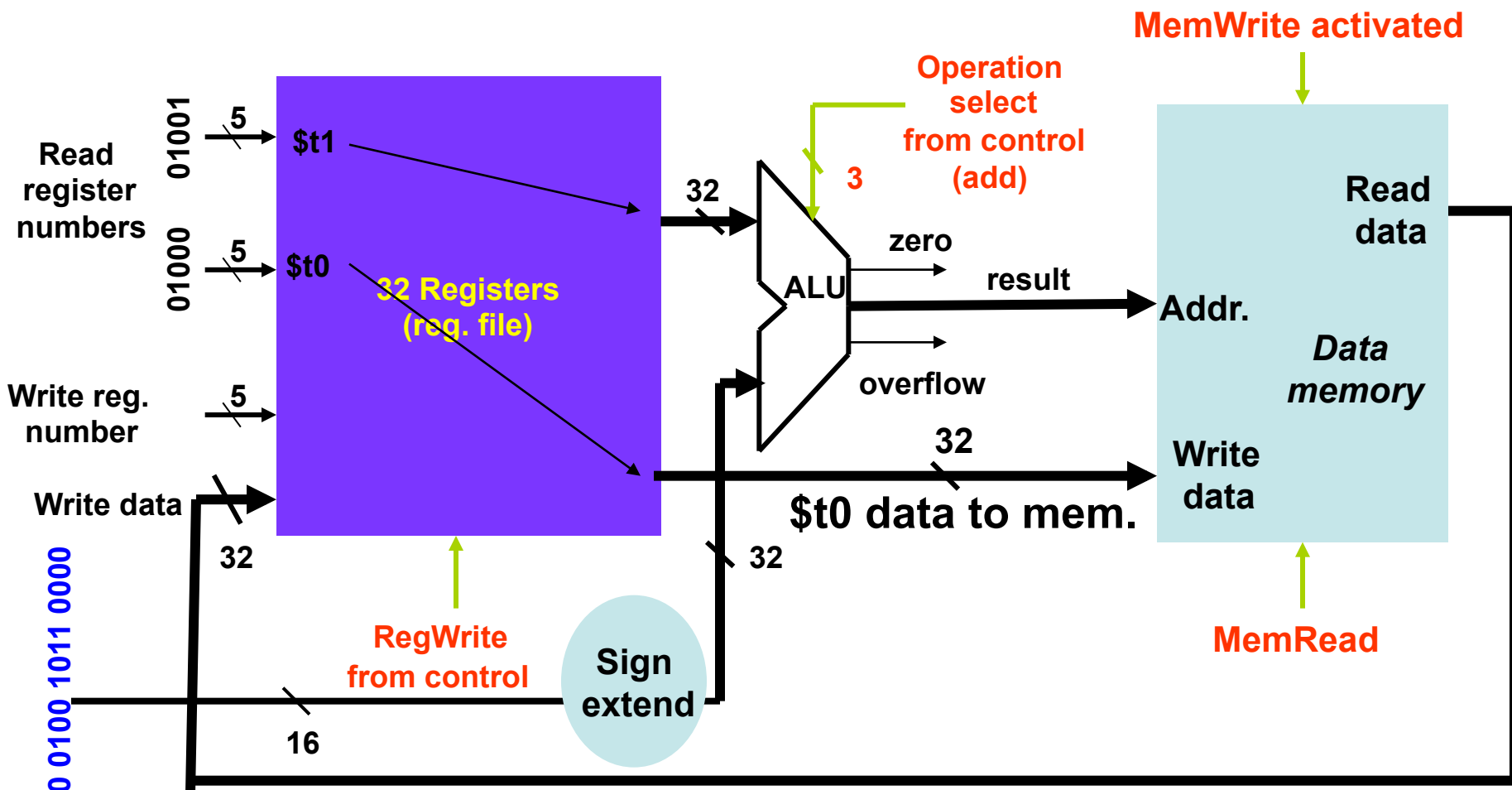101011 01001 01000 0000 0100 1011 0000
opcode \$t1 \$t0 1200



0000 0100 1011 0000



Branch Instruction (I-Type)

- beq $\$s1, \$s2, 25$ # if $\$s1 = \$s2$,
advance
PC through
instructions 25




16-bits

000100 10001 10010 0000 0000 0001 1001

Note: Can branch within $\pm 2^{15}$ words from the current instruction address in PC.




Datapath for beq Instruction

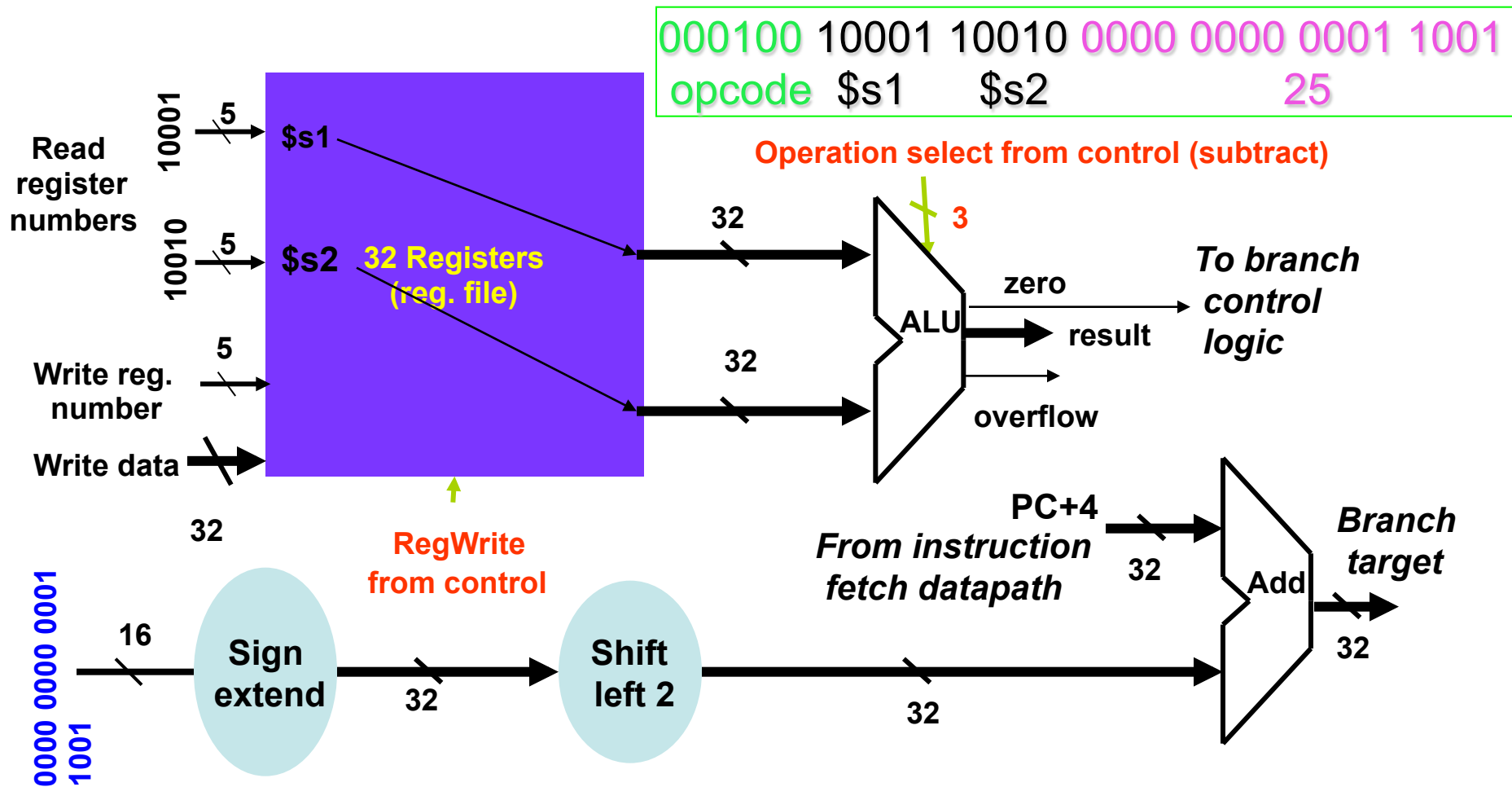



J-Type Instruction

- **j 2500** # jump to instruction 2,500

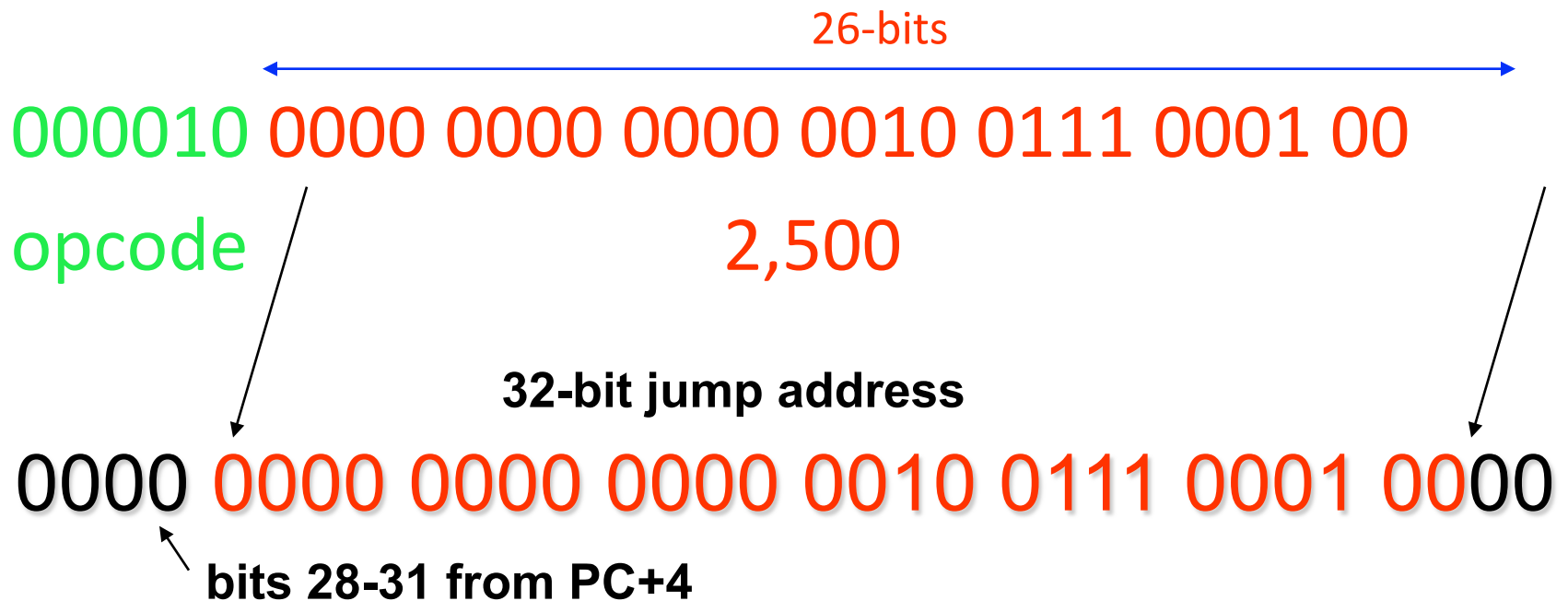

Datapath for Jump Instruction

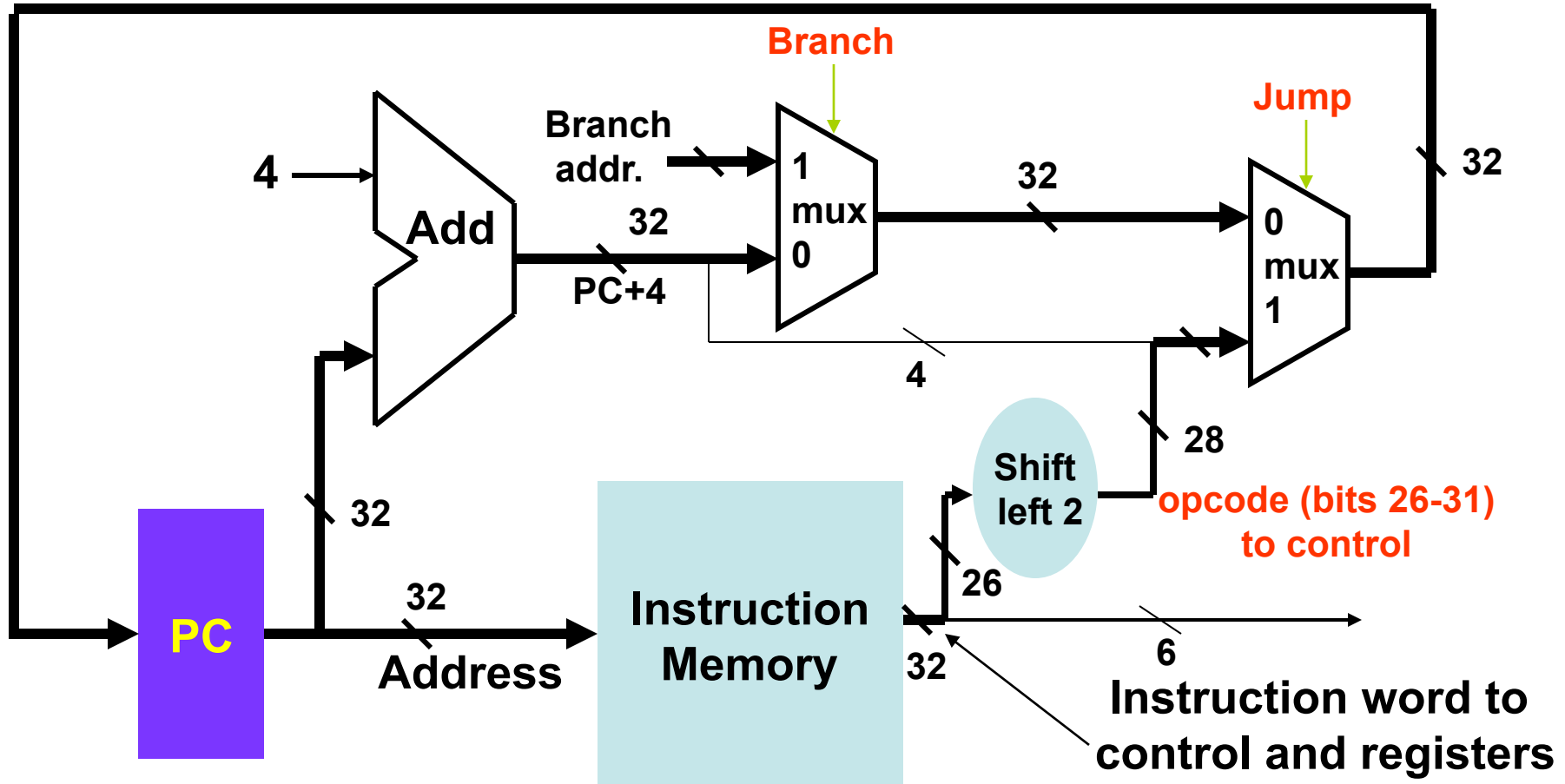


 

Combined Datapaths



Control Logic

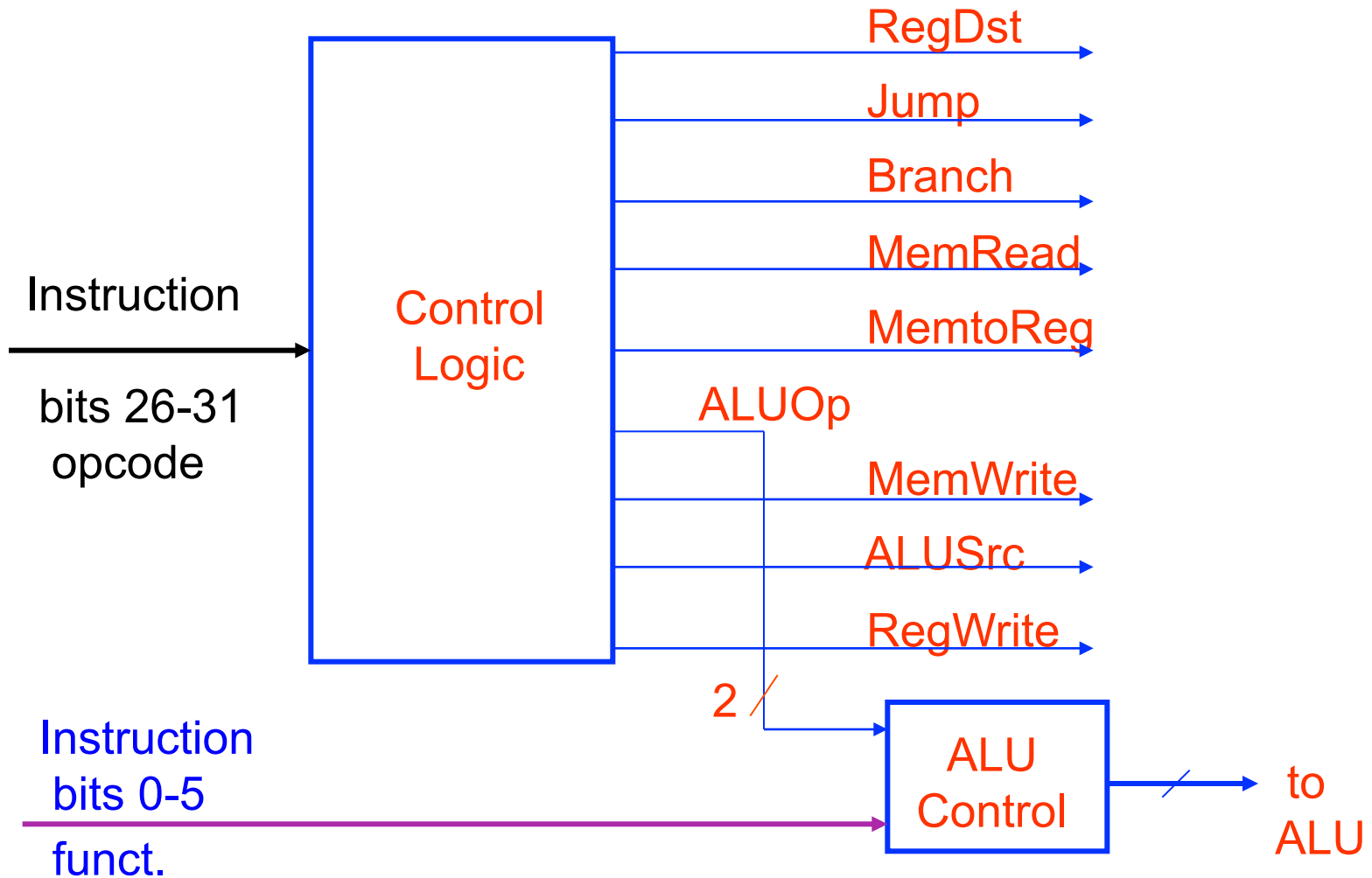

Control Logic: Truth Table

Instr type	Inputs: instr. opcode bits						Outputs: control signals									
	31	30	29	28	27	26	RegDst	Jump	ALUSrc	MemtoReg	RegWrite	MemRead	MemWrite	Branch	ALOp1	ALOp2
R	0	0	0	0	0	0	1	0	0	0	1	0	0	0	1	0
lw	1	0	0	0	1	1	0	0	1	1	1	1	0	0	0	0
sw	1	0	1	0	1	1	X	0	1	X	0	0	1	0	0	0
beq	0	0	0	1	0	0	X	0	0	X	0	0	0	1	0	1
j	0	0	0	0	1	0	X	1	X	X	X	X	X	X	X	X



How Long Does It Take?

- Assume control logic is fast and does not affect the critical timing. Major time delay components are ALU, memory read/write, and register read/write.
- Arithmetic-type (R-type)
 - Fetch (memory read) 2ns
 - Register read 1ns
 - ALU operation 2ns
 - Register write 1ns
 - **Total 6ns**



Time for lw and sw (I-Types)

- ALU (R-type) 6ns
- Load word (I-type)
 - Fetch (memory read) 2ns
 - Register read 1ns
 - ALU operation 2ns
 - Get data (mem. Read) 2ns
 - Register write 1ns
 - **Total 8ns**
- **Store word (no register write) 7ns**



Time for beq (I-Type)

- ALU (R-type) 6ns
- Load word (I-type) 8ns
- Store word (I-type) 7ns
- Branch on equal (I-type)
 - Fetch (memory read) 2ns
 - Register read 1ns
 - ALU operation 2ns
 - **Total 5ns**



Time for Jump (J-Type)

- ALU (R-type) 6ns
- Load word (I-type) 8ns
- Store word (I-type) 7ns
- Branch on equal (I-type) 5ns
- Jump (J-type)
 - Fetch (memory read) 2ns
 - **Total** 2ns



How Fast Can the Clock Be?

- If every instruction is executed in one clock cycle, then:
 - Clock period must be at least $8ns$ to perform the longest instruction, i.e., $1/w$.
 - This is a single cycle machine.
 - It is slower because many instructions take less than $8ns$ but are still allowed that much time.
- Method of speeding up: Use multicycle datapath.



Thank You

