

Motion Detector and Alarm System

Group No. : D1

Arun Kumar Meena (04d07041) <arun@ee.iitb.ac.in>

Prince Negi (04d07042) <prince@ee.iitb.ac.in>

Yogesh Kumar Meena (04d07043) <ykmeena@ee.iitb.ac.in>

Instructor: M.C. Chandorkar

Supervised By: D.K.Sharma

Abstract

The aim of this project is to make a system which can detect the break-in. When break-in is occur it will raise a alarm system. This system will also keep record of the time of break-ins and duration of break-ins, with the help of Real Time Clock generated by microcontroller. Data will be saved in the flash memory provided by microcontroller. Information about the break-ins will be displayed on the LCD screen.

1.Introduction.

Our aim is to develop a sensor pairs and alarm system which can detect the break-ins at the room windows. Our system will contain the Real Time Clock continuously displayed on LCD screen. With the help of this Real Time Clock, system will show the time of break-ins on LCD screen and ring the alarm.

In Later stage of this project USB interfacing will be done. That will transfer the data from microcontroller flash memory to a Computer. The power supply for this system will be taken

from the Mains AC supply. Further we will use battery back-up for system to keep functioning in case of power failure.

2. Block Diagram

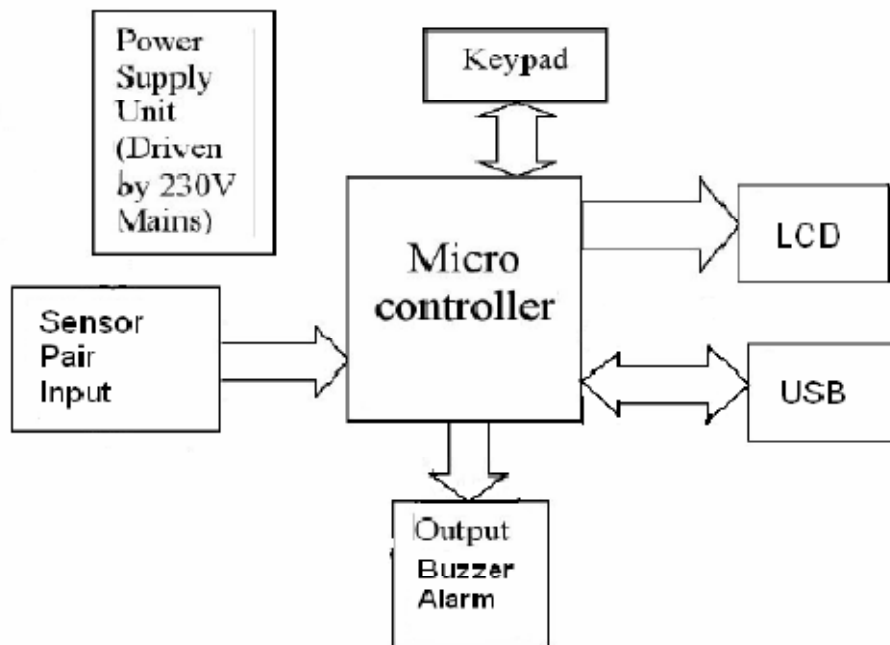


Fig. 1 Block Diagram

2.1 Microcontroller

In this project we are using AT89C52 microcontroller. This microcontroller developed by Atmel family, compatible with 8051 microcontrollers. It's a low-voltage, high performance CMOS 8-bit microcontroller with 8k bytes of flash programmable and erasable read only memory(PEROM).The architecture combined with Three-level Program Memory Lock and low power Idle and power-down modes. This device features a 256 x 8 bit internal RAM, 32 programmable I/O lines and three 16-bit Timer/Counters.

Typical application of this microcontroller includes the sensor system. It takes the analog signals and converts them in digital form. The timers make the configuration very ideal to industrial applications.

2.2 Keypad

In this project we are using 4x4 matrix keypad for taking the user inputs. User can feed the date, month, year and time. Also user can see the data saved in flash memory using this keypad.

2.3 LCD

In this project we are using a LCD, which can show 16 characters x 2 lines on the screen.

This will be enough for our project, as we have to show only date and time of break-in at the same time.

2.4 Sensor Pairs

A laser and photodiode is used as a sensor pairs for this project. To amplify the signal across photodiode we are used BC-547 a NPN transistor. The laser used will be enough powerful to cover the range of window. The laser is fed by square wave generated by microcontroller. The output of Photodiode is fed back to microcontroller to detect the break-in.

2.5 Buzzer Alarm

In the case of break-in (determined by microcontroller) a signal generated by microcontroller and 1 KHz frequency generated by 555 timer will be fed to AND gate (7408). The output of AND gate will be given to the LM 386 (Audio Amplifier), that will raise the alarm system.

2.6 Power Supply

To supply the current to microcontroller, sensor pairs and alarm system we have used a 220-12V transformer with the rated current of 0.5 Amp. The Ac supply from the transformer is regulated by a bridge-rectifier and filter circuit. The system requires one voltage levels; 5V supply to sensor pairs, buzzer circuit, LCD and microcontroller.

3. Software

3.1 Sensor Pairs input and output

To feed the frequency input to laser we are generating the 40Hz frequency with the help of microcontroller timers. For this purpose we used timer one. The input for the sensor pairs is given on the port 2.

The output from the photo diode is given back on the port2. By comparing the off time/On time of both signal microcontroller will be able to detect the break-in.

3.2 Keypad and real Time Clock

The initial time is fed to the real time clock using the keypad. With the help of programming we are able to save year, month, date, hour, minutes and seconds in the 16-bit registers. The real time clock will be updated by receiving the 1 sec timer interrupt. Other registers can be used for other temporary storage and data transfer.

3.3 LCD

LCD is programmed in such a way that it can display the information about the break-ins in terms of time of last break-in.

3.4 Flash Memory Storage

At the time of break-in information regarding the break-in is also stored, which can be seen later using keypad and LCD. This data also can be transferred to a Computer using USB interfacing.

4. Hardware

4.1 Power Supply

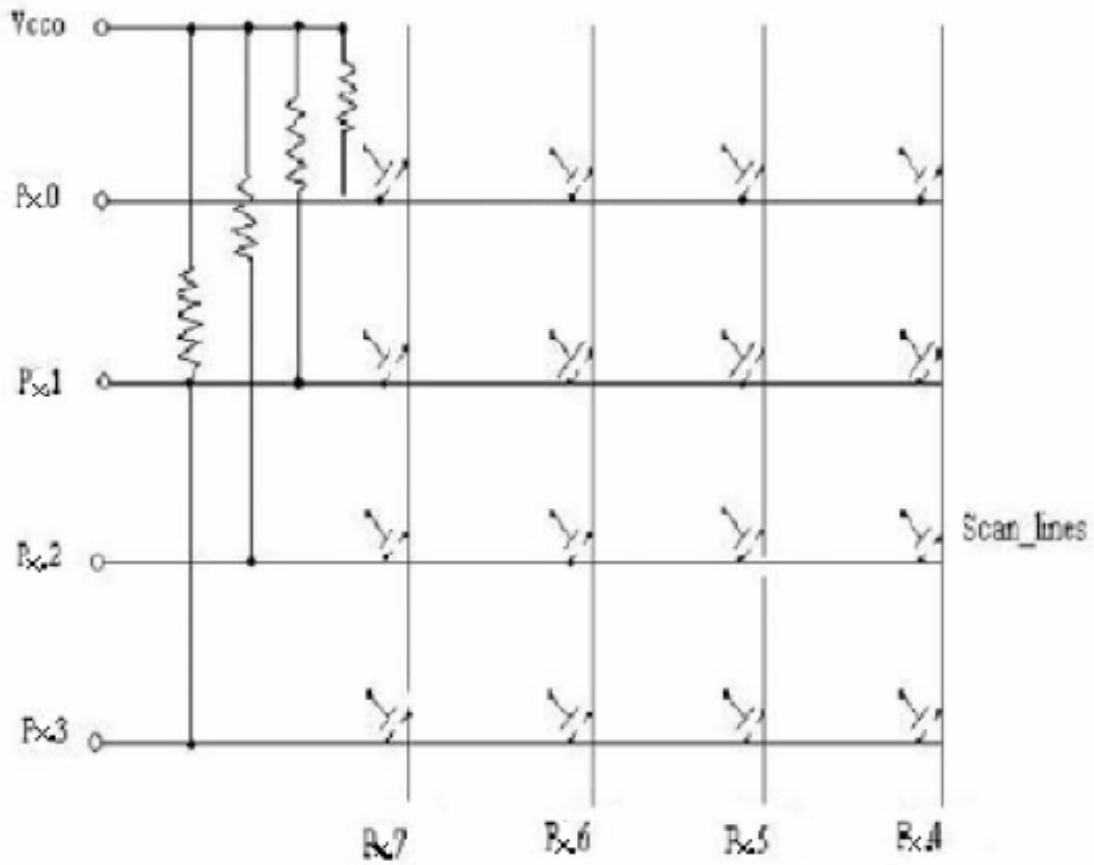


Fig. 3 4x4 Keypad

4.3 Laser (transmitter)

The square wave input to the laser is given by microcontroller. With the help of this input laser radiates the visible pointed light. The circuit diagram is given below.

4.4 Photo diode (Receiver)

The Photodiode will receive the light signal from the laser. To amplify the photodiode signal we used NPN transistor. The output of this transistor is going back to microcontroller. The circuit diagram is given below.

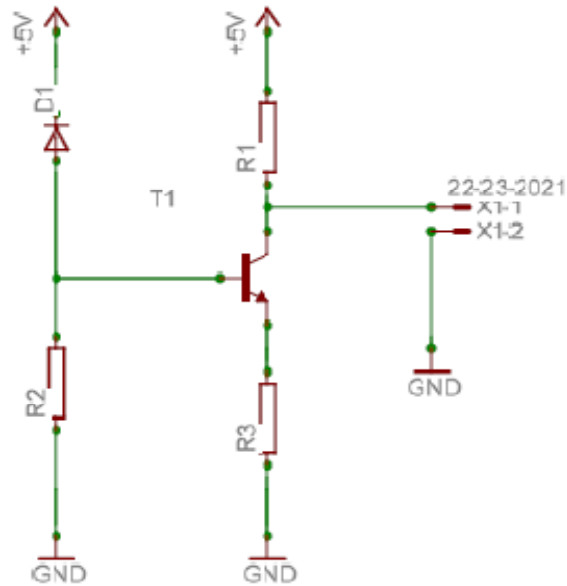


Fig. 5 Photo Diode and NPN Transistor

4.5 Microcontroller

The 40-pin dip diagram of microcontroller AT89C52 is given below.

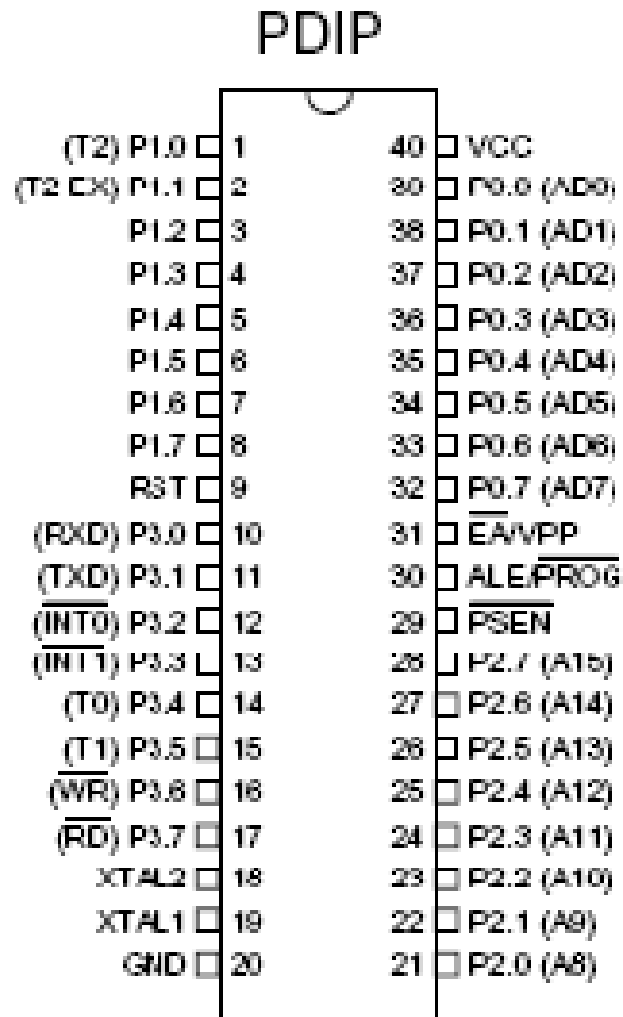


Fig. 6 Pin diagram of 89C52 Microcontroller

4.5 Buzzer Circuit

A signal given by microcontroller and frequency generated by 555 Timer will be fed to AND gate and output of AND gate will given to LM 386, that will raise the alarm system.

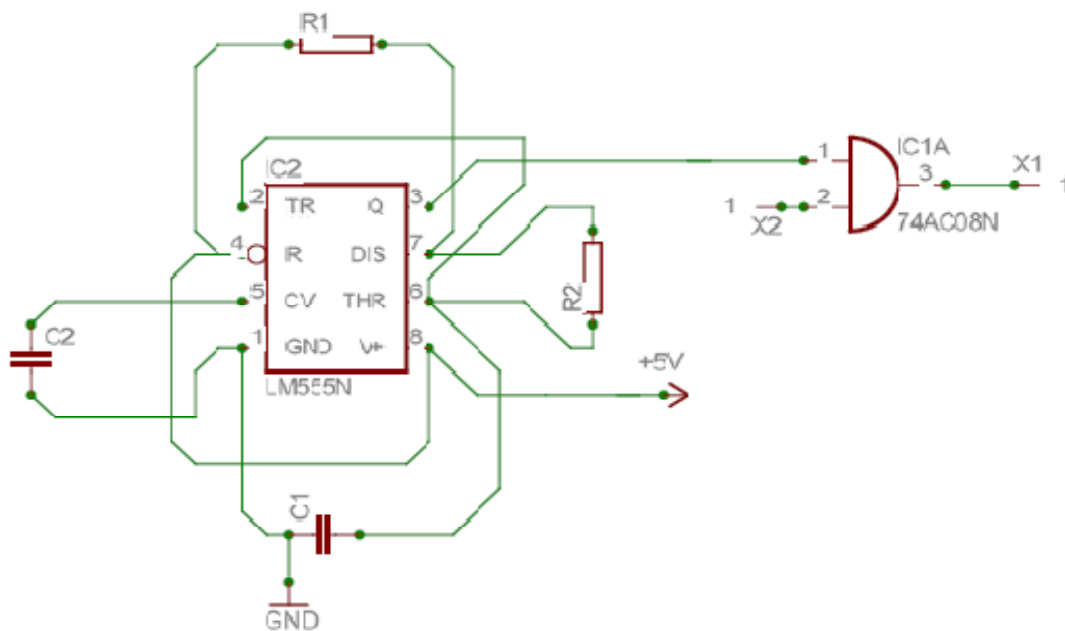


Fig. 7 555 Timer and AND gate

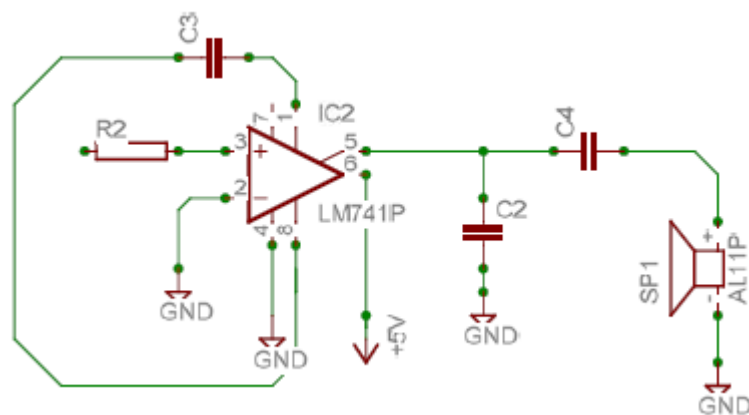


Fig. 8 LM386 and speaker

5. Work done so far

5.1 We have made the sensor pairs using Laser-Photodiode combination.

5.2 Buzzer circuit is done with the help of LM386 and other capacitor and resistors.

5.3 The software part of Real Time Clock, Square wave generation, break-in detection code has been checked.

5.4 At this time we are able to show the last break-in time with the help of Real-Time Clock on LCD screen.

5.5 Instead of 4x4 matrix keypad, we are using 4 switches to set the Hours, Minutes, Seconds and to check the last break-in time.

6. Remaining Work

6.1 Keypad interfacing with the microcontroller will be done.

6.3 In the later stage of this project USB interfacing with a Computer will be done.

7. Acknowledgements

We would like to acknowledge the immense help given by Prof. D.K.Sharma, Prof.M.C.Chandorkar and Mr. V.K. Tandon, which helped out us from various problems encountered during this project. Along with this we would like to thanks the lab assistance, TAs and other senior students.

8. References

(a) Atmel , AT89C52 Data Sheets

(b) A.S Sedra Smith and K.C.kamath, *Microelectronics circuit*, Fourth Edition (1982), New York, Oxford University Press, 2003.

(C) EE Department,IIT Bombay (electronics design Lab webpage) ,
<http://sharada.e.iitb.ac.in/~edlab>