


Control & Computing group, EE, IITB




22nd Feb 2022

This lecture: a glimpse of inter-relations between

- # Kirchhoff's current laws, # Kirchhoff's voltage laws (for planar/more-general circuits?)
- Tellegen's theorem: topology of circuit (already) implies conservation of power
- \searrow Laplacian matrix L: window to a world of graph theory
 - Hairy ball theorem: (in)ability to 'smoothly comb' hair on a fully haired ball
 - Euler's formula (convex polyhedron): #Faces - #Edges + #Vertices = 2 (or more generally (for toruses)?)
 - Types of equilibrium points (and their index) (on a sphere/other 'manifolds')

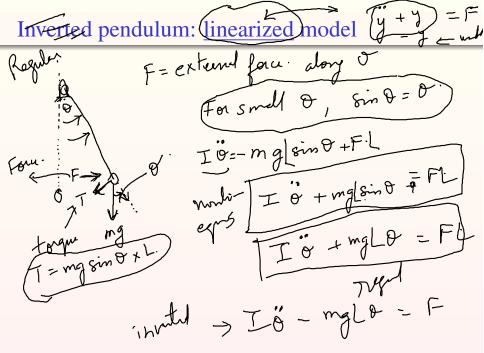

EE113: Related topics

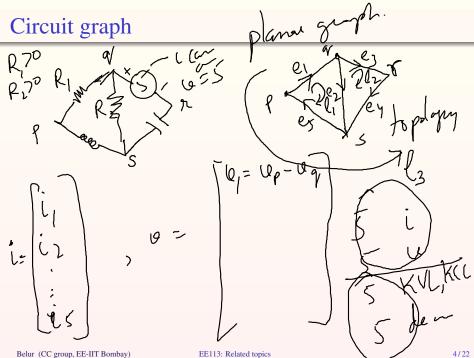


https://www.tutorialspoint.com/network%5Ftheory/network%5Ftheory%5Ftopology%5Fmatrices.htm

- Consider the graph: assign edge directions (in any way)
- Assign currents as positive along the edge
- Assign voltage-drops as positive along the current
- If an edge e_n is a resistor, then $v_n i_n > 0$: thus 'load convention'
- Construct 'node edge incidence matrix' A and loop edge 'comprisal' matrix B (which loop contains which edges)


For the same topology (and same orientations of the edges): Situation 1: put for each edge: any device: measure currents: vector i Situation 2: put each edge any device: measure voltages: vector v Then: (Tellegen's weak form): $v^{T} = 0 = \mathcal{O}_{1} i_{1} + \mathcal{O}_{2} i_{2}$ Strong form: dimension of all possible v's + all possible i's = number of edges vrance, independent (linear) (Voltage-vectors 'complement' the current vectors): after removing (shrinking) 'redundant' rows within A, and after removing (shrinking) 'redundant' rows within B is nonsingular, and (4 $AB^{T} = 0$

Easier to see in an example

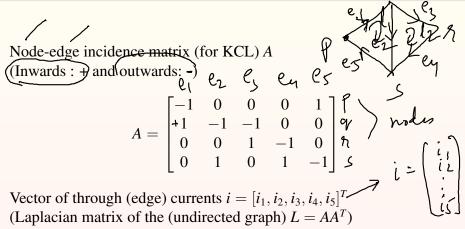



L gives number of (spanning) trees: Kirchhoff's matrix tree theorem

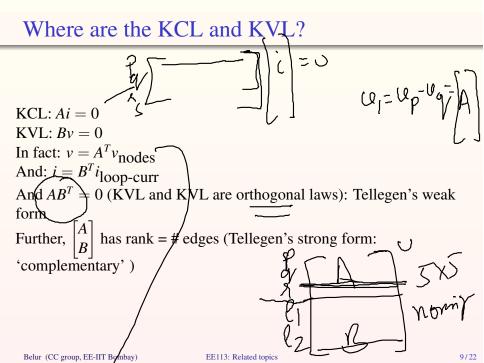
Loop-edge 'occurrence' matrix (KVL) (except outerm) Loops: choose clockwise (for convenience) Does an edge 'occur' in that loop? (aligned along loop : + and opposite: -) $B = \begin{bmatrix} 1 & 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 1 & 0 \\ -1 & 0 & -1 & -1 & -1 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \\ -1 \end{bmatrix}$ Vector of voltage drops (along edges) $(= [v_1, v_2, v_3, v_4, v_5]^T$ 6: un





٧ N 0 10

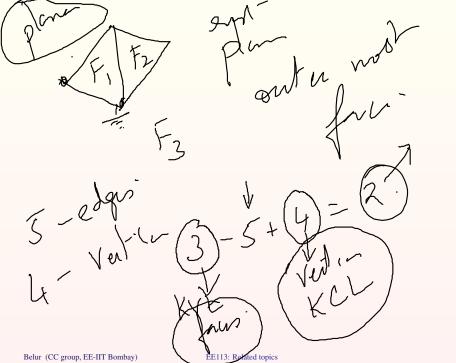


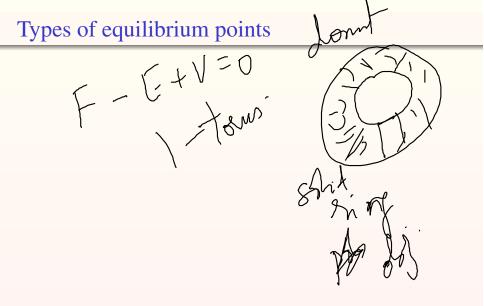

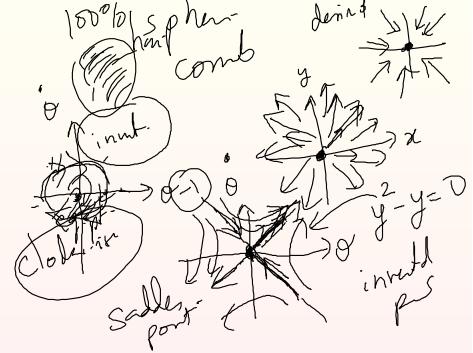

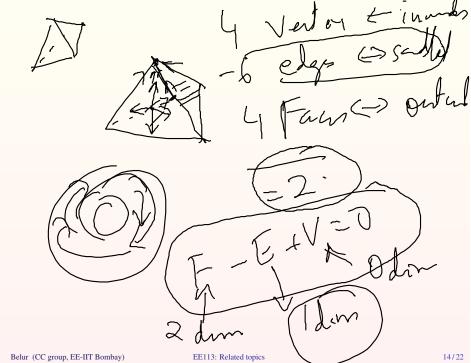

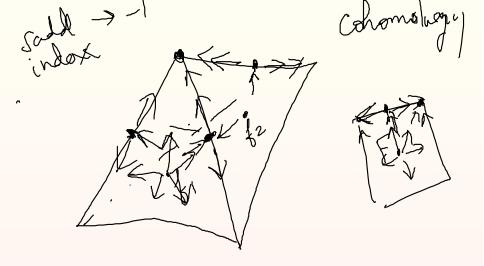


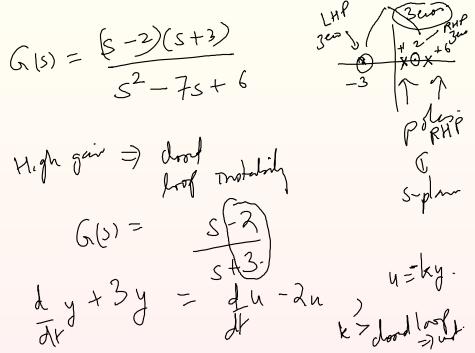


EE113: Related topics

18/22

Hairy ball theorem

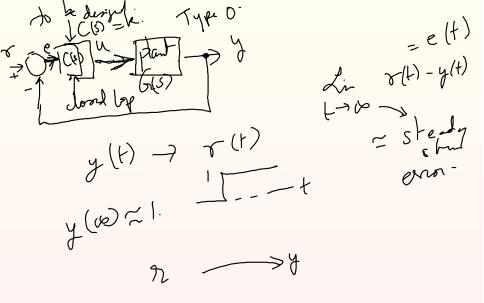

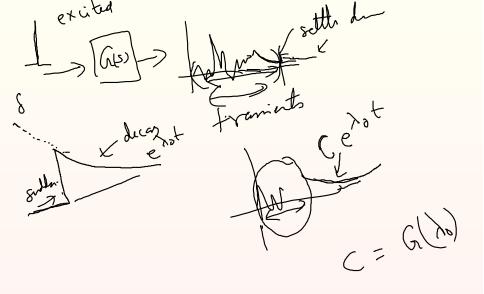

Tutorial on Thursday: will send problems today

= gim han (21S) \leq 111

Belur (CC group, EE-IIT Bombay)

EE113: Related topics