

Lecture 2 Module 1


- Inverse Laplace Transforms.
 - Response types depending on pole location.
-

An improper transfer function corresponds to an acausal system.

$$\underline{\dot{x}(t) + 2x(t) = \delta(t)}, \quad \underline{t > 0^-} \quad \underline{x(0^-) = 1}$$

classical method

$$\underline{t > 0^+}$$

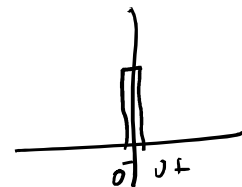

$$\begin{aligned} \dot{x}(t) + 2x(t) &= 0 \\ \Rightarrow x(t) &= x(0^+) e^{-2t} \\ &= 2 e^{-2t} \end{aligned}$$

$$\begin{aligned} x(0^+) - x(0^-) &= \int_{0^-}^{0^+} \delta(t) dt \\ &= \underline{1} \end{aligned}$$

$$x(0^+) = 2$$

$$\int_{0^+}^{\infty} f(t) e^{-st} dt = \mathcal{L}_+ [f(t)]$$

$$\dot{x} + 2x = \delta(t)$$

$$sX(s) - x(0^+) + 2X(s) = 0$$

$$X(s) = \frac{x(0^+)}{s+2} \Rightarrow ?$$

$$\int_{0^-}^{\infty} f(t) e^{-st} dt$$

$$\begin{aligned} sX(s) - x(0^-) + 2X(s) &= 1 \\ \Rightarrow X(s) &= \frac{1}{s+2} + \frac{x(0^-)}{s+2} \\ &= \frac{2}{s+2} = 2e^{-2t} \end{aligned}$$

$$y(t) = \int_{-\infty}^{\infty} h(\tau) u(t-\tau) d\tau$$

Suppose $u(t) = e^{\alpha t} \quad \alpha \in \mathbb{C}.$

$$y(t) = \int_{-\infty}^{\infty} h(\tau) e^{-\alpha \tau} \cdot \underline{e^{\alpha t}} d\tau = e^{\alpha t} \int_{-\infty}^{\infty} h(\tau) e^{-\alpha \tau} d\tau$$

For causality,

$$h(t) = 0 \quad t < 0$$

$$y(t) = e^{\alpha t} \int_{0^-}^{\infty} h(\tau) e^{-\alpha \tau} d\tau = e^{\alpha t} H(\alpha)$$

$$= e^{\alpha t} \underline{\hat{H}(\alpha)} \quad |\hat{H}(\alpha)| = M$$

$$\Phi = \angle \hat{H}(\alpha)$$

$$M \angle \Phi$$

$$\dot{x} + 2x = e^{\alpha t}$$

$$\text{Let } x(t) = H(\alpha) \cdot e^{\alpha t}$$

$$\alpha H(\alpha) e^{\alpha t} + 2H(\alpha) e^{\alpha t} = e^{\alpha t}$$

$$\Rightarrow H(\alpha) = \frac{1}{\alpha + 2}$$

$$H(s) = \frac{1}{s + 2}$$

$$h(t) = \mathcal{L}^{-1}[H(s)] = e^{-2t} \cdot 1(t)$$

- $F(s) = \int_{0^-}^{\infty} f(t) e^{-st} dt = \mathcal{L}[f(t)]$

$$\bar{F}(s) = \int_{0^-}^{\infty} e^{at} f(t) \cdot e^{-st} dt = F(s-a) \quad (\text{Ex})$$

$$\Rightarrow \mathcal{L}[e^{at} f(t)] = F(s-a). \quad - (i)$$

- $I_k = \int_{0^-}^{\infty} t^k e^{-st} dt = \left. \frac{t^k e^{-st}}{-s} \right|_{t=0^-}^{t \rightarrow \infty} - \int_{0^-}^{\infty} \frac{k t^{k-1} e^{-st}}{-s} dt, \quad k \in \mathbb{Z}_+$

$$= \frac{k}{s} I_{k-1}$$

$$I_0 = \frac{1}{s}$$

$$I_1 = \frac{1}{s^2}, \quad I_2 = \frac{2}{s^3}, \quad I_k = \frac{k!}{s^{k+1}} \quad - (ii)$$

$$G(s) = \frac{N(s)}{\prod_{i=1}^k (s - p_i)^{r_{p_i}}}$$

p_i are k distinct complex nos.

$$\deg(D(s)) = \sum_{i=1}^k r_{p_i}$$

$$G(s) = \sum_{i=1}^k \left(\sum_{d_i=1}^{r_{p_i}} \frac{A_{i,d_i}}{(s - p_i)^{d_i}} \right)$$

$$A_{i,d_i} \in \mathbb{C}$$

$$\Downarrow$$

$$\frac{A_{i,d_i} t^{d_i-1} e^{p_i t}}{d_i!}$$

$$G(s) = \frac{s}{s^2 + 3s + 2} = \frac{s}{(s+1)(s+2)}$$

$$= \frac{k_1}{s+1} + \frac{k_2}{s+2}$$

$$\frac{s}{(s+1)(s+2)} = \frac{k_1}{s+1} + \frac{k_2}{s+2}$$

$$s = k_1(s+2) + k_2(s+1) \quad \forall s$$

$$k_1 + k_2 = 1 \quad ; \quad 2k_1 + k_2 = 0$$

$$s = -1, \quad s = -2$$

$$k_1 = -1$$

$$k_2 = 2$$

$$Ax = b$$

$$A = \begin{bmatrix} \triangle \end{bmatrix}$$

$$A = \begin{bmatrix} \square \end{bmatrix}$$

$$\lim_{s \rightarrow -1} (s+1) G(s) = k_1$$

$$\lim_{s \rightarrow -2} (s+2) G(s) = k_2$$

$$\ddot{x} + 2\dot{x} + x = 0$$

$$\dot{x}(0) = b \quad x(0) = a.$$

$$s^2 X(s) - s x(0) - \dot{x}(0) + 2s X(s) - 2x(0) + X(s) = 0$$

$$\Rightarrow X(s) = \frac{as + (2a+b)}{(s+1)^2}$$

$$X(s) = \frac{A_1}{s+1} + \frac{A_2}{(s+1)^2}$$

$$as + (2a+b)$$

$$= A_2 + A_1(s+1)$$

$$A_2 + A_1 = 2a+b$$

$$A_1 = a$$

$$A_2 = a+b$$

$$X(s) = \frac{a}{s+1} + \frac{a+b}{(s+1)^2}$$

$$x(t) = a e^{-t} + (a+b) t e^{-t}$$

$$X(s) = \frac{A_1}{s+1} + \frac{A_2}{(s+1)^2}$$

$$\lim_{s \rightarrow -1} (s+1)^2 X(s) = \lim_{s \rightarrow -1} 2s A_1 + A_2$$

$$\frac{A_1}{(s+1)} + \frac{A_2}{(s+1)^2} = a s + (2a+b)$$

$$A_2 + A_1(s+1) = a s + (2a+b) \Rightarrow A_1 = a$$

Complex poles

$$\frac{5s+2}{(s+a)^2 + b^2} =$$

$$a, b > 0$$

$$\frac{A + j\bar{A}}{s+a + jb}$$

$$+ \frac{B + j\bar{B}}{s+a - jb}$$

$$A, \bar{A}, B, \bar{B} \in \mathbb{R}$$

$$p, \zeta \in \mathbb{R}$$

Ex

$$(A + j\bar{A})^* = (B + j\bar{B})$$

$$(A + j\bar{A})(s+a - jb) + (B + j\bar{B})(s+a + jb) = ps + \zeta$$

$$\left. \begin{array}{l} \bar{A} = -\bar{B} \\ A = B \end{array} \right\} \textcircled{\text{EV}}$$

$$z_1 e^{p_1 t} + z_2 e^{p_2 t}$$

$$z_1, z_2, p_1, p_2 \in \mathbb{C}$$

$$e^{\alpha t} \cos \beta t \quad e^{\alpha t} \sin \beta t$$

$$\mathcal{L}^{-1} \left[\frac{z_1}{s - p_1} \right] = z_1 e^{p_1 t}$$

$$\mathcal{L}^{-1} \left[\frac{z_1^*}{s - p_1^*} \right] = z_1^* e^{p_1^* t}$$

$$\begin{aligned} & z_1 e^{\alpha t} e^{j\beta t} + z_1^* e^{\alpha t} e^{-j\beta t} \\ &= \left[(a + jb) e^{j\beta t} + (a - jb) e^{-j\beta t} \right] e^{\alpha t} \\ &= \left[2a \left[\frac{e^{j\beta t} + e^{-j\beta t}}{2} \right] + 2b \left[\frac{e^{j\beta t} - e^{-j\beta t}}{2j} \right] \right] e^{\alpha t} \end{aligned}$$

$$\mathcal{L}^{-1}\left[\frac{\omega}{s^2 + \omega^2}\right] = \sin \omega t$$

$$\mathcal{L}^{-1}\left[\frac{s}{s^2 + \omega^2}\right] = \cos \omega t$$

$$\mathcal{L}^{-1}\left[\frac{\omega}{(s+a)^2 + \omega^2}\right] = e^{-at} \sin \omega t$$

$$e^{-at} \cos \omega t$$

$$G(s) = \frac{3}{s(s^2 + 2s + 5)} = \frac{k_1}{s} + \frac{k_2 s + k_3}{(s^2 + 2s + 5)}$$

$$\lim_{s \rightarrow 0} s G(s) = k_1 = 3/5, \quad 3 = \left(k_2 + 3/5\right)s^2 + \left(k_3 + \frac{6}{5}\right)s + 3$$

$$G(s) = \frac{N(s)}{D(s)} e^{-s\tau}$$

$$\int_{\delta^-}^{\infty} f(t-\tau) e^{-st} dt = e^{-s\tau} F(s)$$

$$F(s) = \mathcal{L}[f(t)]$$

$$G(s) = \frac{2s e^{-2s} + 3s e^{-5s}}{(s+2)(s+3)(s+4)}$$

Ex

$$= e^{-2s} \left[\frac{A}{(s+2)} + \frac{B}{s+3} + \frac{C}{s+4} \right] + e^{-5s} \left[\frac{D}{s+2} + \frac{E}{s+3} + \frac{F}{s+4} \right]$$

② Take a transfer fn with repeated complex poles.
and see which method is easier.


$$G(s) = \frac{7s + 8}{[s^2 + 5s + 20]^2}$$

$$\boxed{A_2 = 5}$$



$$\frac{7s + 8}{(s + 2)^2(s + 1)} = \frac{A}{(s + 2)^2} + \frac{B}{(s + 1)} + \frac{C}{s + 2}$$

$$\sum z_i e^{p_i t}$$


LHP

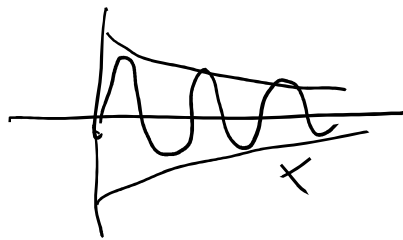

$\text{Im}(s)$

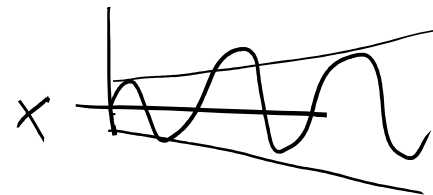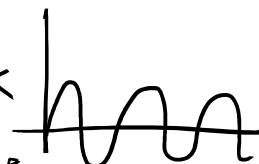

RHP

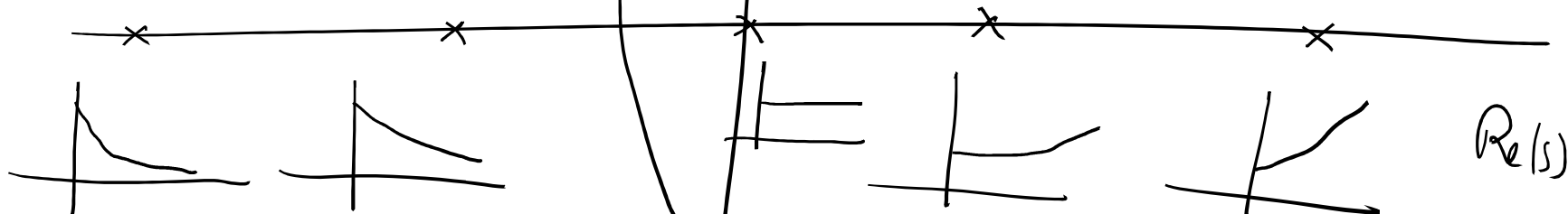

stable

x


unstable

$$t^k e^{-\alpha t} \downarrow \alpha > 0$$

⊕ Additional practice problems (Inverse Laplace Transforms).

- $\frac{2s+3}{s^2+3s+2}$
- $\frac{s+2}{(s+1)^2}$
- $\frac{1}{s^2+2s+10}$
- $\frac{2s^2+3s+2}{(s+1)^3}$
- $\frac{s+2}{(s+1)^2(s+3)}$
- $\frac{s(1+e^{-2s}+e^{-7s})+e^{-2s}}{s(s+6)}$

• Analysis of electrical ccts. Module 2

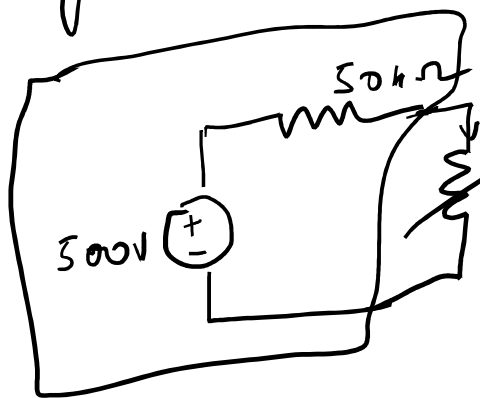

Current Source.

$$10\Omega < R_L < 50\Omega$$


KCL, KVL



$$v = Ri \rightarrow V(s) = R I(s)$$


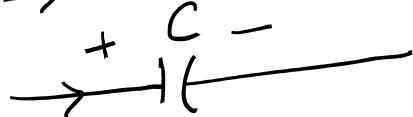
$$v = L \frac{di}{dt} \rightarrow V(s) = sL I(s)$$



$$v = \frac{1}{C} \int i dt \rightarrow V(s) = \frac{1}{sC} I(s)$$

$$\mathcal{L} \left[\int_0^t f(\tau) d\tau \right] = \underbrace{\int_0^{\infty} \underbrace{f(\tau)}_u \underbrace{e^{-st}}_{dv} d\tau}_{\substack{\text{by parts} \\ \text{let } u = \int_0^t f(\tau) d\tau \\ dv = e^{-st}}} = \frac{1}{s} F(s) \quad F(s) = \mathcal{L}[f(t)]$$

$$V(s) = \boxed{R} I(s)$$

$$V(s) = \boxed{sL} I(s)$$


$$V(s) = \boxed{\frac{1}{sC}} I(s)$$

KVL

$$\text{KCL} \left\{ \begin{array}{l} I(s) = \frac{V(s)}{R} \\ I(s) = \frac{V(s)}{sL} \\ I(s) = sC V(s) \end{array} \right. \quad \left[\begin{array}{c} \frac{1}{R} \\ \frac{1}{sL} \\ \frac{1}{sC} \end{array} \right]$$

$$\int u dv = uv - \int v du$$


series ckt.

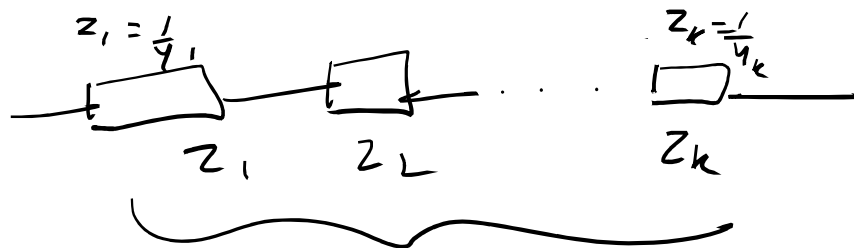

$$Z_{eq} = \sum_{i=1}^k Z_i$$





$$Y_{eq} = \frac{1}{\sum_{i=1}^k \frac{1}{y_i}}$$

|| ckt

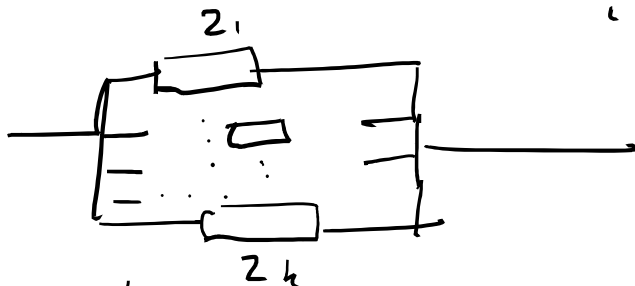

$$Y_{eq} = \sum_{i=1}^k Y_i$$
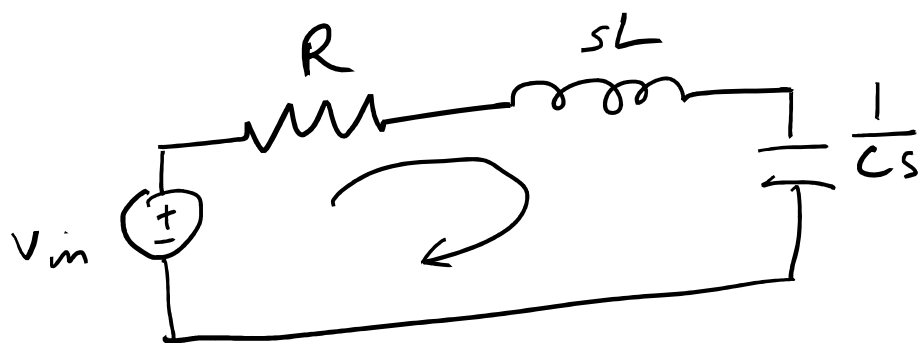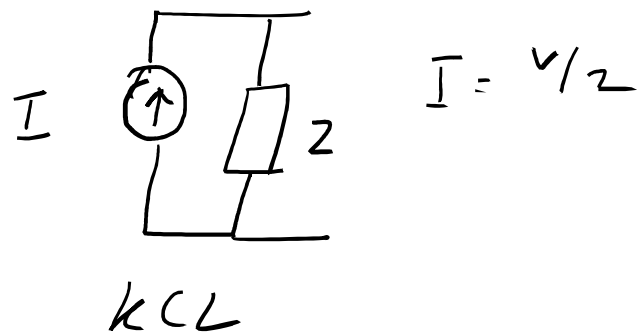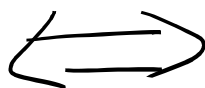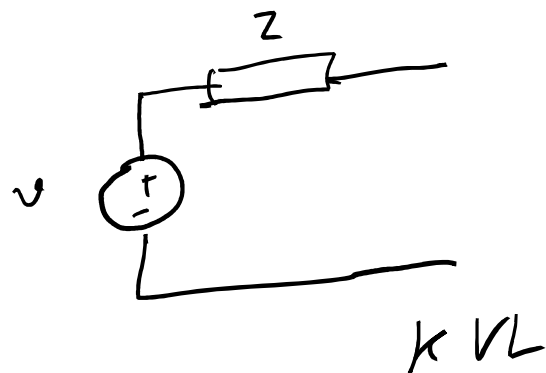
$$Z_{eq} = \frac{1}{\sum_{i=1}^k \frac{1}{z_i}}$$



$$I(s) \left[R + \frac{1}{sC} + sL \right] = V_{in}(s)$$

$$\Rightarrow \frac{Cs}{LCs^2 + RCs + 1} = \frac{I(s)}{V_{in}(s)}$$

$$\Rightarrow \frac{I(s)}{V_{in}(s)} = \frac{s/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Suppose R is negligibly small.

Additionally consider $V_a(s) = \frac{1}{s}$


$$I(s) = \frac{1/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$i(t) = \mathcal{L}^{-1}[I(s)] = \mathcal{L}^{-1}\left[\frac{1/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}}\right]$$

$$i(t) = \mathcal{L}^{-1}\left[\frac{\frac{1/L}{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}}}{\left(s + \frac{R}{2L}\right)^2 + \left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}\right)^2}\right]$$

$$= \frac{1}{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}} \cdot e^{-\frac{Rt}{2L}} \sin\left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} t\right)$$

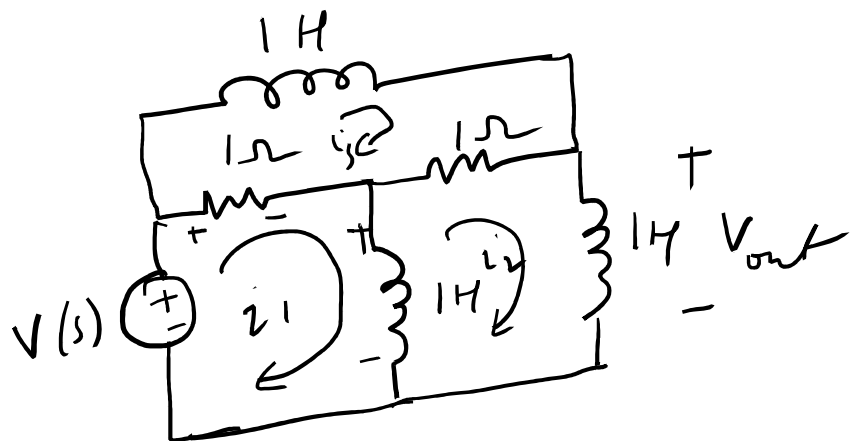study RL & RC circuits response to a const. voltage.



$$1H \rightarrow s$$

$$1\Omega \rightarrow 1$$

$$V(s)$$

$$\begin{vmatrix} s+1 & -1 & -1 \\ -1 & 2s+1 & -1 \\ -1 & -1 & s+2 \end{vmatrix} = s(s^2 + 5s + 2) \quad \text{(ii)}$$


obtain $\frac{V_{out}(s)}{V(s)}$

$$\begin{aligned} V(s) &= [I_1(s) - I_2(s)]s + [I_1(s) - I_3(s)] \\ &= (s+1)I_1 - 1I_2 - I_3 \quad \text{(i)} \end{aligned}$$

$$\begin{aligned} 0 &= (I_2 - I_3) + s(I_2) \\ &\quad + s[I_2 - I_1] \end{aligned}$$

$$\Rightarrow -sI_1 + (s+1)I_2 - I_3 = 0 \quad \text{(ii)}$$
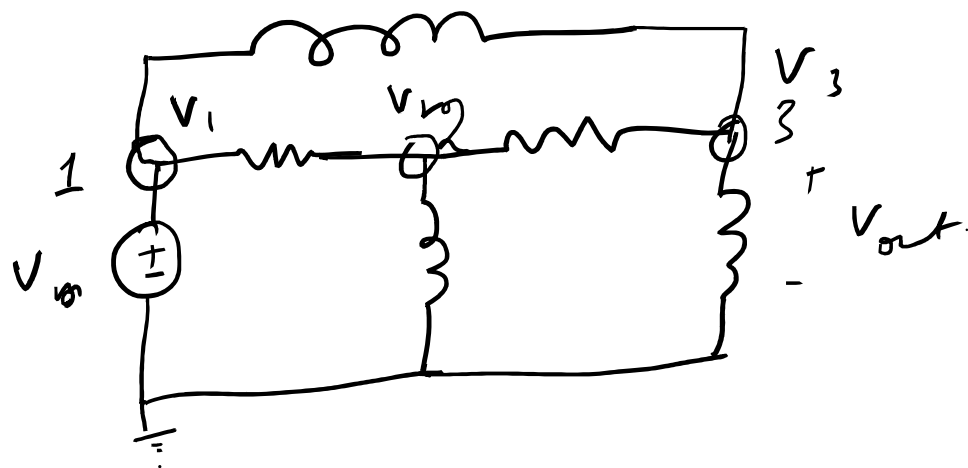
$$\begin{aligned} V(s)(s^2 + 2s + 1) \quad \frac{I_2(s)}{V(s)} &= \frac{s^2 + 2s + 1}{s(s^2 + 5s + 2)} = -I_1 - I_2 + (s+2)I_3 \quad \text{(iii)} \\ \Rightarrow V_{out}/V_{in} &= \frac{s^2 + 2s + 1}{s^2 + 5s + 2} \end{aligned}$$



For application of KCL
you can merge together
elements in parallel.

$$\begin{cases} V_1 = V_{in} \\ V_2 \left(\frac{1}{1} + \frac{1}{1} + \frac{1}{s} \right) - V_1 \left(\frac{1}{1} \right) - V_3 \left(\frac{1}{1} \right) = 0 \\ V_3 \left(\frac{1}{s} + \frac{1}{s} + \frac{1}{1} \right) - \frac{1}{1} V_2 - \frac{1}{s} V_1 = 0 \end{cases}$$


$$\frac{(V_2 - V_1)}{1} + \frac{V_2 - V_3}{1} + \frac{V_2}{s} = 0 \quad (2)$$

$$\frac{V_3}{s} + \frac{V_3 - V_2}{1} + \frac{V_3 - V_1}{s} = 0 \quad (3)$$


$V_3 = V_{out}$
(E1) Verify the tf using KCL
For application of KVL
you can merge together
elements in series.

$$V_1 = V_{in} \rightarrow (1)$$


Twin T det

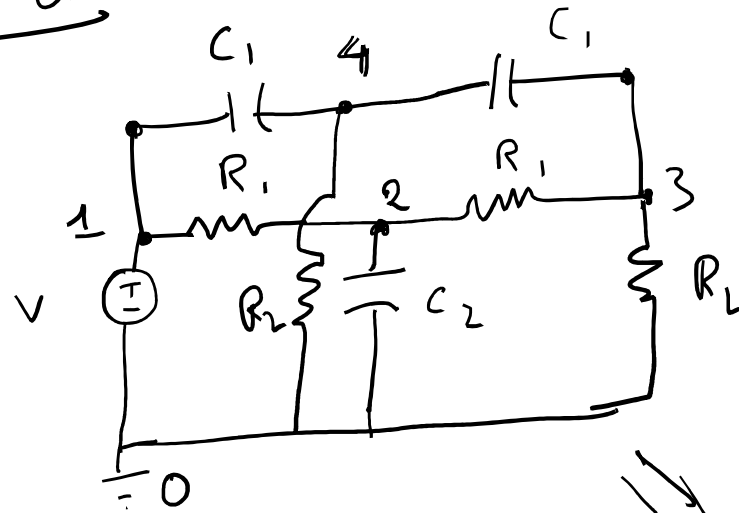


Graph theoretical
method

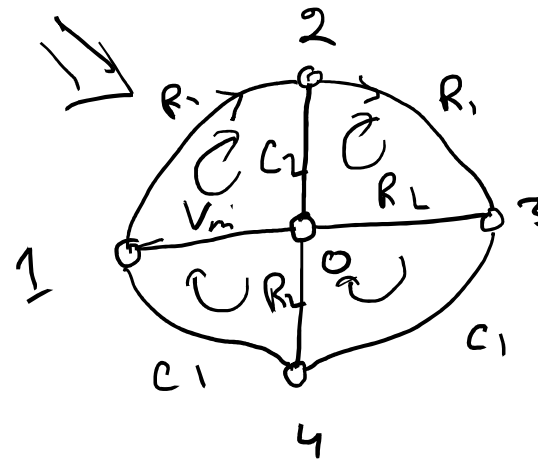


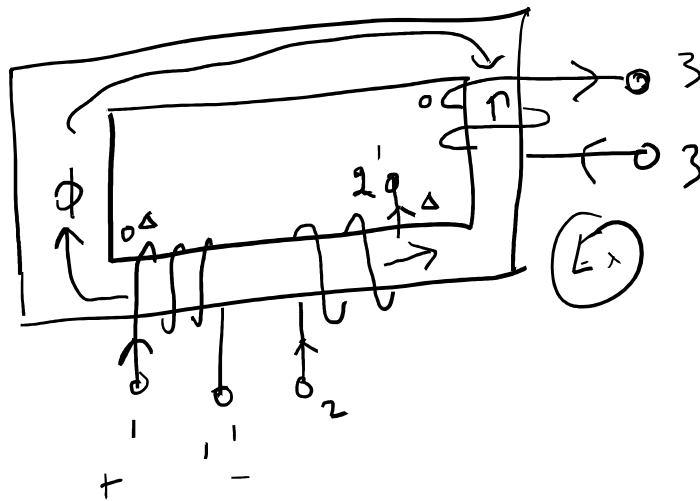- Module 3
- Ckts with Mutual Inductance
 - OPAMPs & their transfer fns



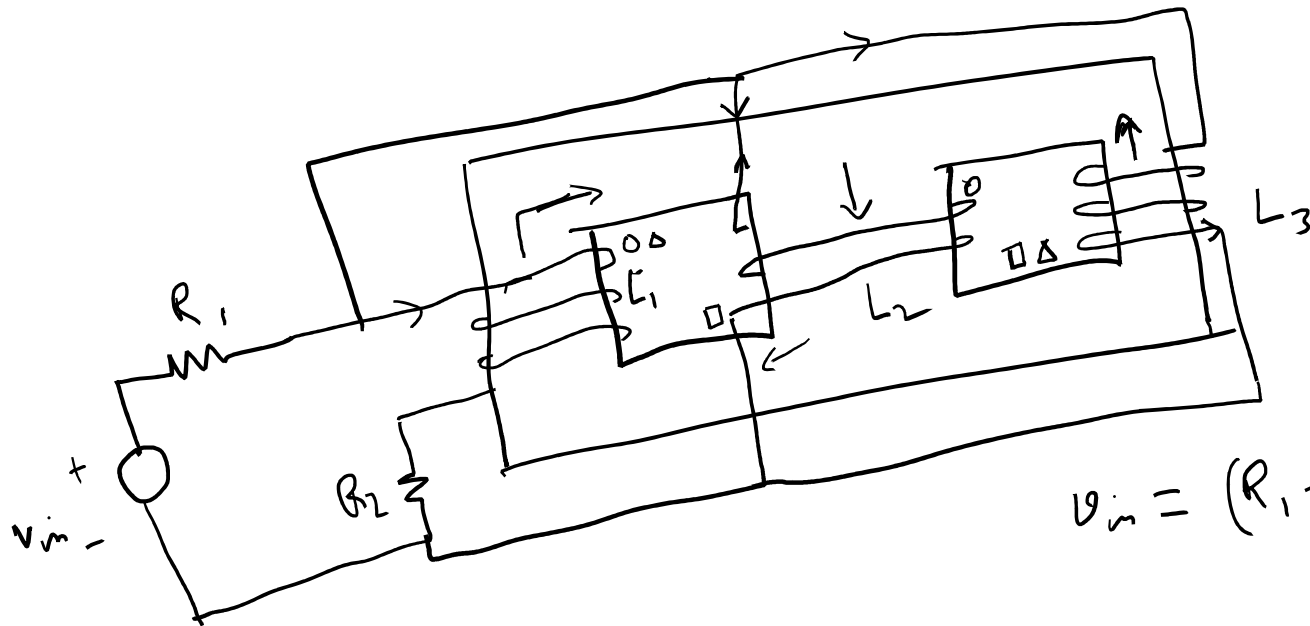
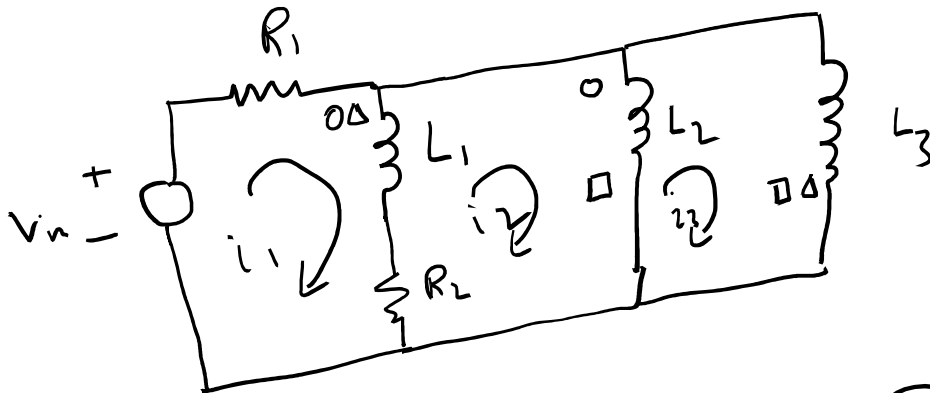
$$\begin{aligned}
 V_m = & (R_1 + R_2 + sL_1) \bar{I}_1 \\
 & - (sL_1 + R_2) \bar{I}_2 \\
 & + sM_{12} (\bar{I}_2 - \bar{I}_3) \\
 & - sM_{13} \bar{I}_3 \quad \text{--- (1)}
 \end{aligned}$$




(E+)

$$\begin{aligned}
 & -sM_{12} (\bar{I}_2 - \bar{I}_3) \\
 & -sM_{21} (\bar{I}_2 - \bar{I}_1) \quad \text{(2)} \\
 & sM_{13} \quad sM_{23} \quad \text{--- (3)}
 \end{aligned}$$

OP Amps


Differential Amplifiers

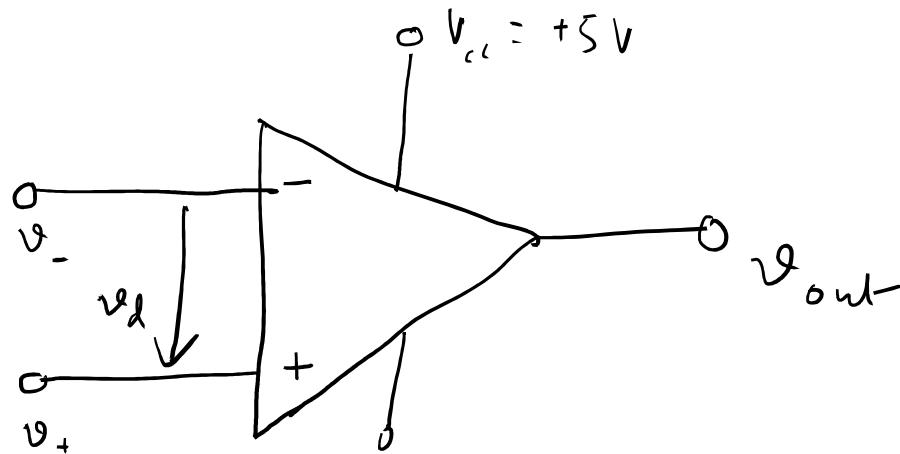

$$v_d = v_+ - v_- \quad (i)$$

$$v_{out} = A v_d \quad (ii)$$

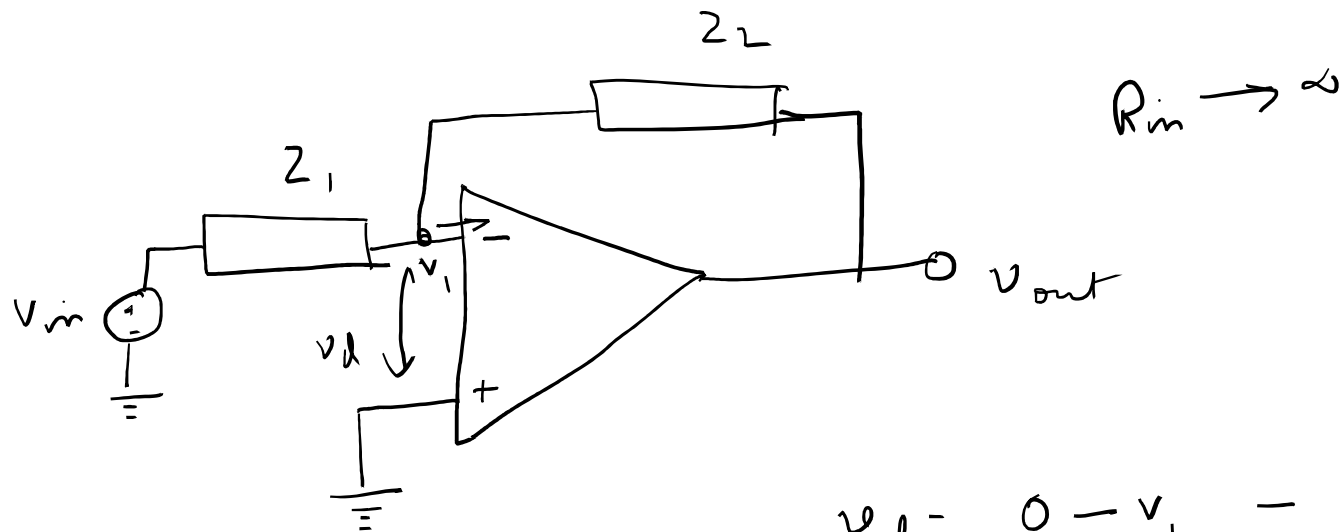- Infinite i/p impedance
- Zero o/p impedance.
- $A \rightarrow \infty$



$$\frac{v_{in} - 0}{Z_1} + \frac{v_{out} - 0}{Z_2} = 0$$


$$\frac{v_{out}}{v_{in}} = - \frac{Z_2}{Z_1}$$

$$v_d = 0 - v_1 \quad \text{--- (1)}$$

$$v_{out} = A v_d \quad \text{--- (2)}$$

$$= - A v_1$$
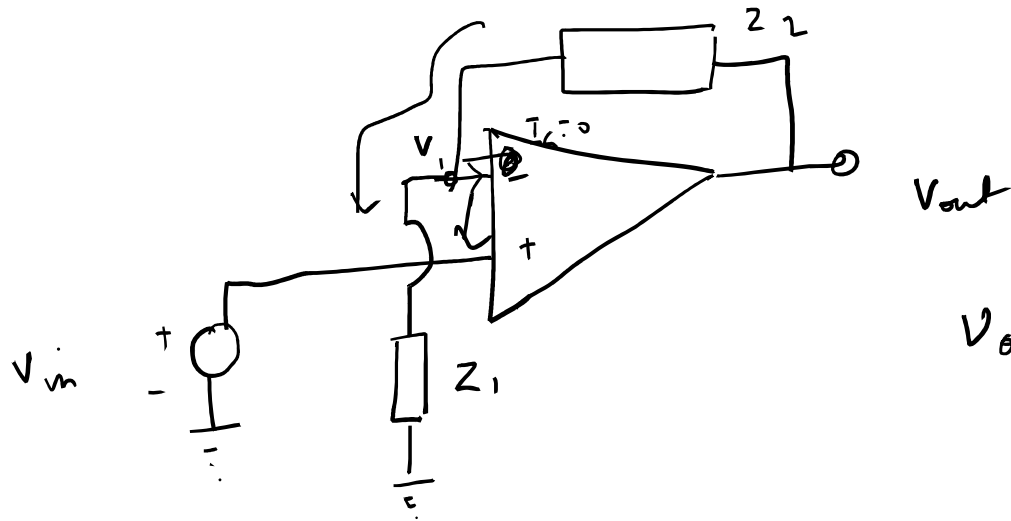
$$v_1 = - \frac{v_{out}}{A} \rightarrow 0 \quad \text{Virtual short.}$$



$$V_{out} = A v_d$$

$$= A (V_{in} - V_1) \quad (1)$$

$$\frac{V_{out} Z_1}{Z_1 + Z_2} = V_1$$


$$V_{out} = \left(\frac{Z_1 + Z_2}{Z_1} \right) V_1$$

$$= \left(\frac{Z_1 + Z_2}{Z_1} \right) V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{Z_1 + Z_2}{Z_1} = 1 + \frac{Z_2}{Z_1}$$

$$V_{in} - V_1 = \frac{V_{out}}{A} \rightarrow 0$$

$$V_{in} = V_1$$

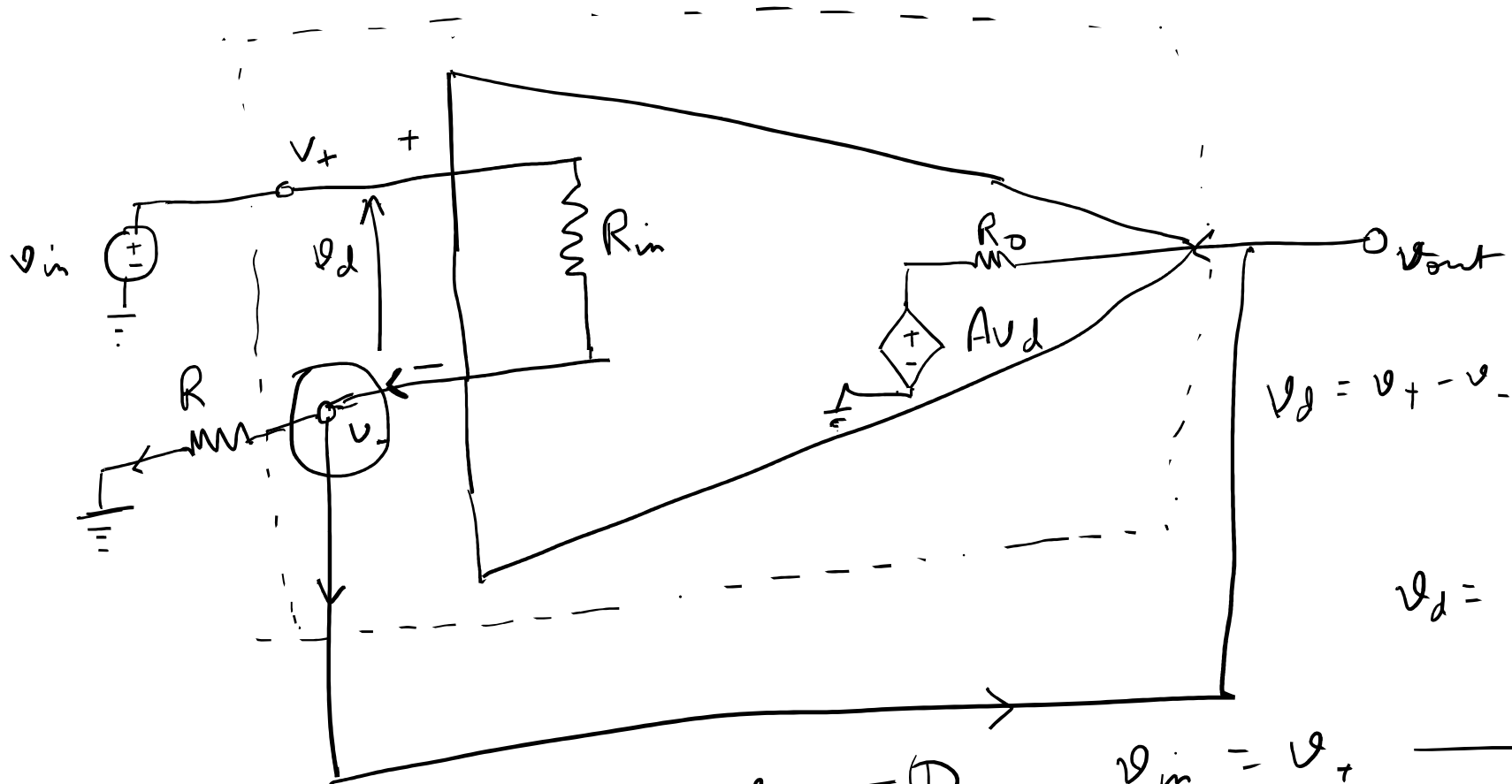

$$v_{out} = v_- \quad \text{--- (1)}$$

$$v_{in} = v_+ \quad \text{--- (2)}$$

$$\frac{v_+ - v_-}{R_{in}} = \frac{v_-}{R} + \frac{v_{out} - A(v_+ - v_-)}{R_o}$$

$$\frac{v_{out} - A(v_+ - v_-)}{R_o}$$

$$v_o \left[\frac{1}{R} + \frac{1}{R_o} + \frac{A}{R_o} + \frac{1}{R_{in}} \right] = v_{in} \left[\frac{1}{R_{in}} + \frac{A}{R_o} \right]$$


$$\frac{v_o}{v_{in}} = \frac{\frac{1}{R_{in}} + \frac{A}{R_o}}{\frac{1}{R} + \frac{1}{R_o} + \frac{A}{R_o} + \frac{1}{R_{in}}}$$

- (i) $A \rightarrow \infty$
- (ii) $R_o \rightarrow 0$
- (iii) $R_{in} \rightarrow \infty$


(Ex)

Goal $\frac{v_o}{v_{in}} = 1$


Ex

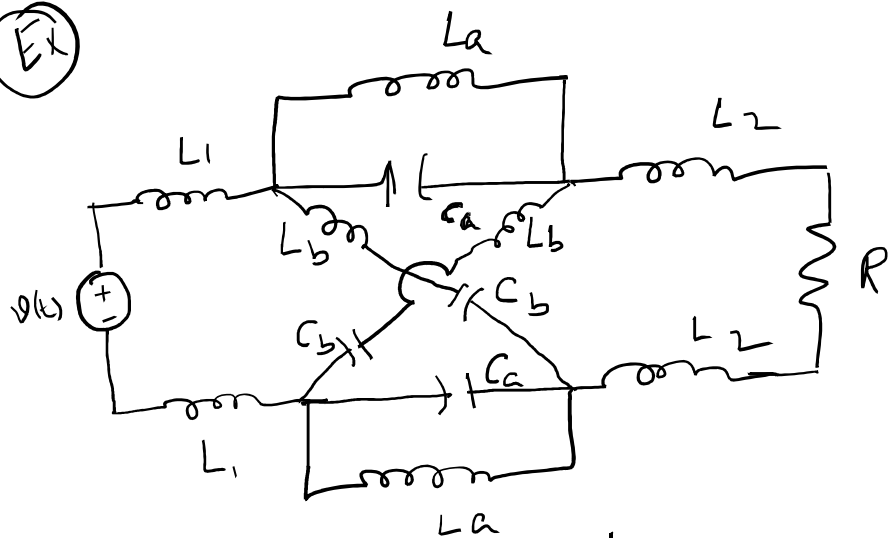

Apply KVL to write the eqn

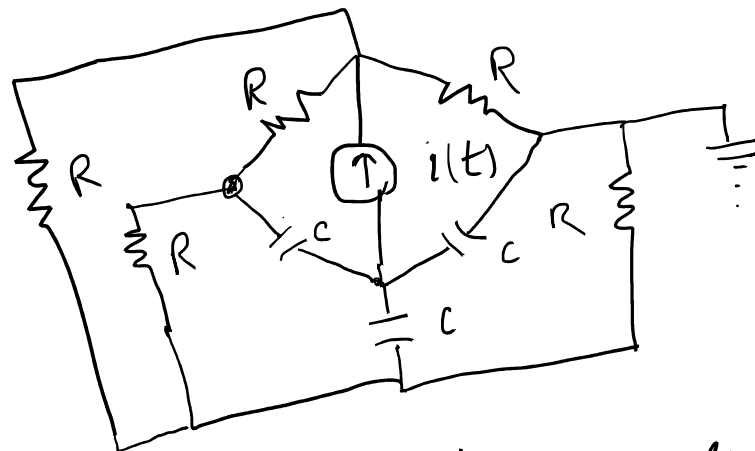


Apply KCL to write the eqn.

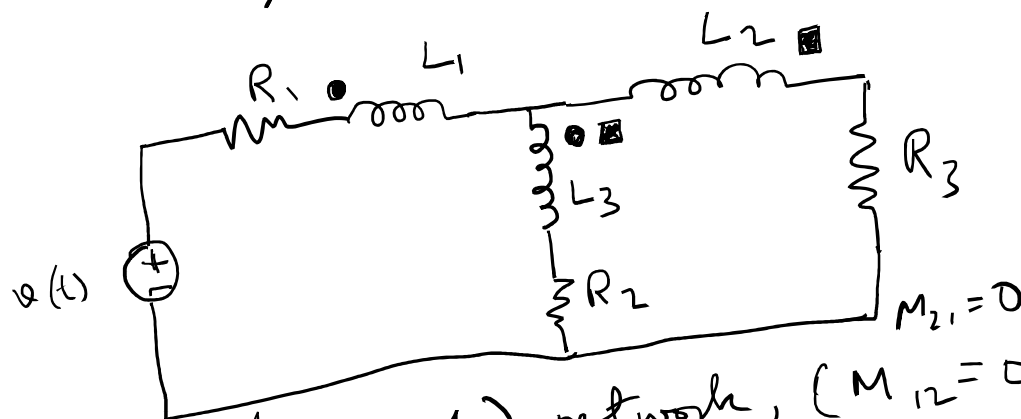

For the magnetically coupled network, ($M_{12} = 0$), formulate loop eqns using KVL.

Ex world

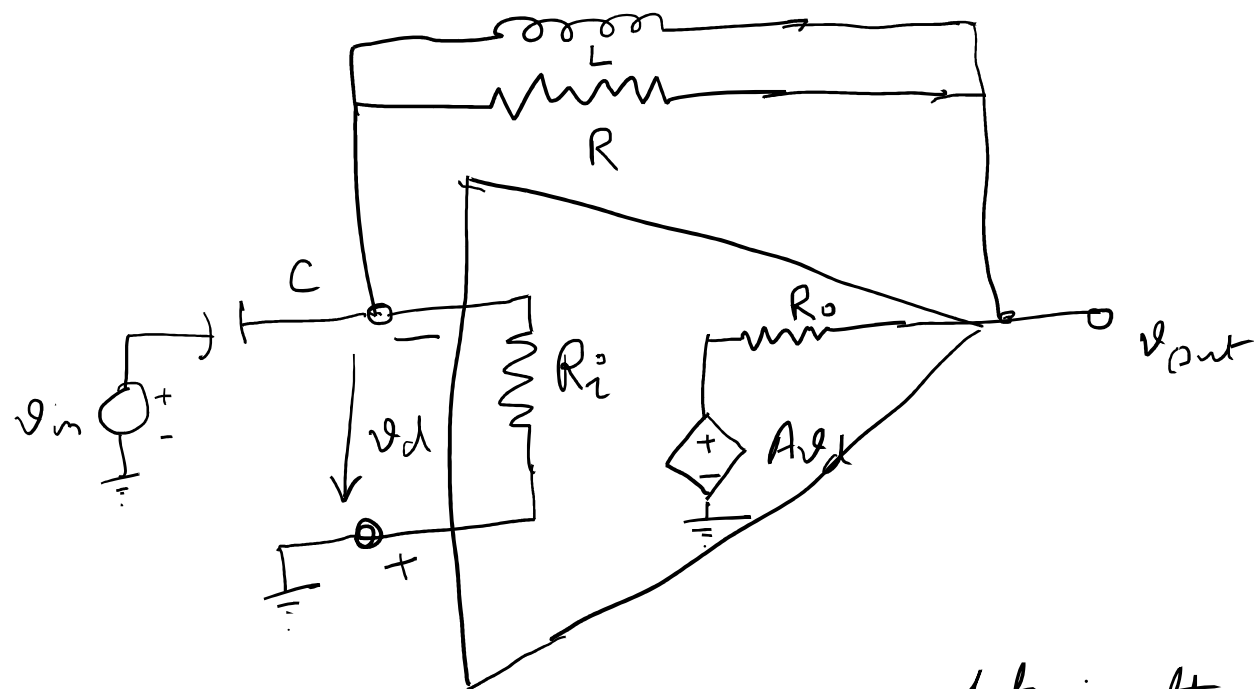

For the non-ideal OP Amp, obtain the t.f. $\frac{V_{out}(s)}{V_{in}(s)}$.

Test the effects of $A \rightarrow \infty$, $R_o \rightarrow 0$ & $R_i \rightarrow \infty$ individually, and together.