Transformer

# Transformer :

Machine to transform levels of voltage and current but not power or volt-ampere.


### From ampere's law:



CoreWinding

 $N_1 = no.$  of turns of the coil  $i_m = current$  in the coil

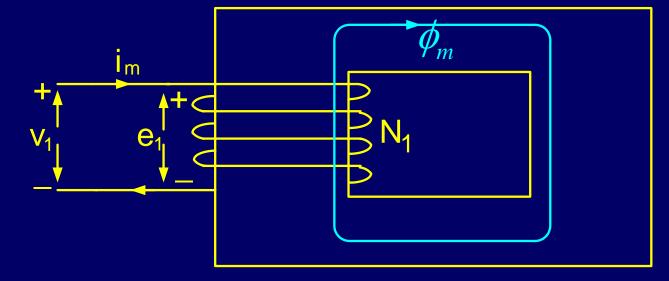Direction of flux given by right hand thumb rule




### From Faraday's law:

$$v_1 = e_1 = N_1 \frac{d\phi_m}{dt}$$


Magnitude of core flux is determined by the induced voltage and hence applied voltage in case of an ideal transformer.

 $=\frac{N_1 i_m}{\text{reluctance}}$ 

For an ideal transformer,  $i_m = 0$ 

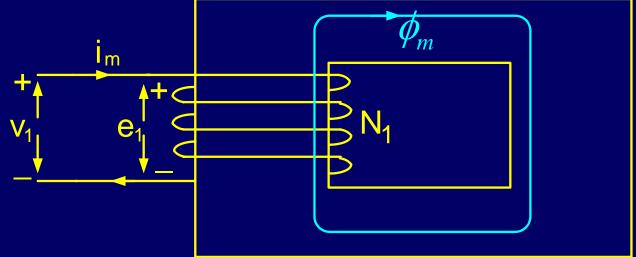

## Voltage induced in winding 2

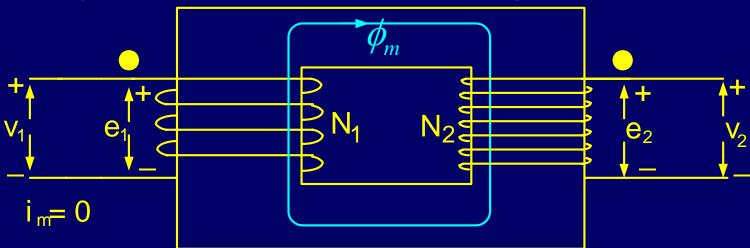


Ideal transformer: Recluctance of core material is zero

$$v_1 = e_1 = N_1 \frac{d\phi_m}{dt}$$


$$v_2 = e_2 = N_2 \frac{d\phi_m}{dt}$$

Polarity of induced voltage is given by Lenz's law : "dotted" terminals gets ' similar polarity

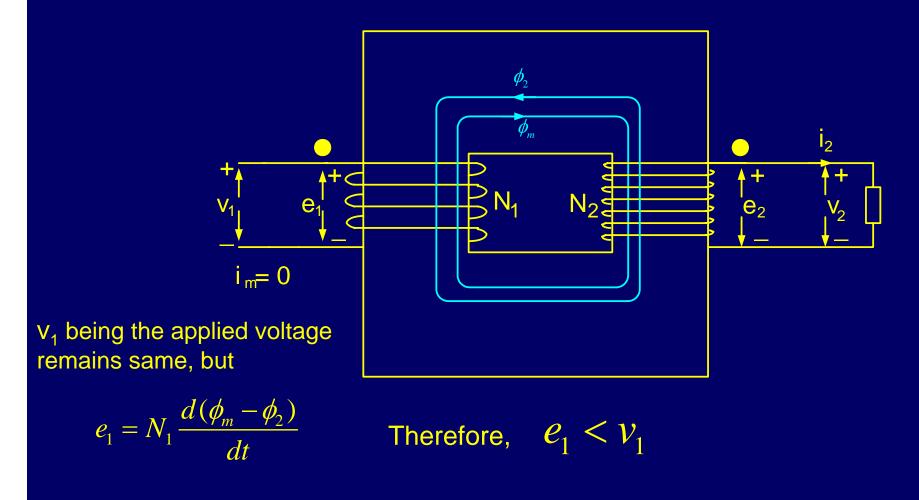
$$\frac{v_1}{v_2} = \frac{e_1}{e_2} = \frac{N_1}{N_2}$$



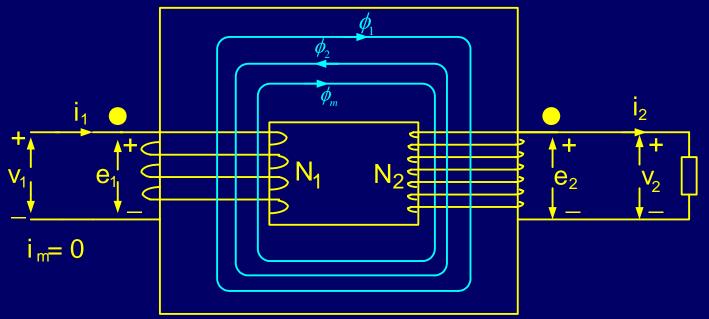Hence a current  $i_1$  flows from v1 to "dot" terminal of winding 1. Flow of current  $i_1$  in N<sub>1</sub> sets a flux  $\phi_1$  in the core



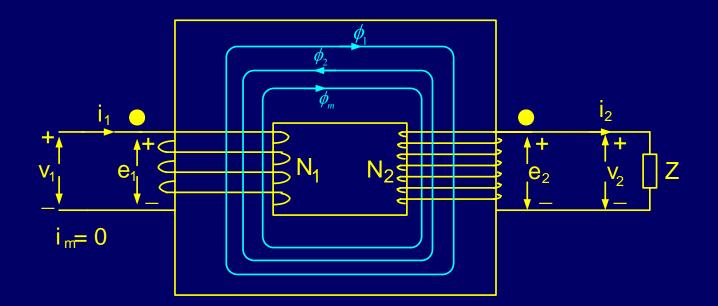Steady state will reach when,  $\phi_1 = \phi_2$  Therefore at steady state  $\phi_1 = \frac{N_1 i_1}{\text{reluctance}}$   $\phi_2 = \frac{N_2 i_2}{\text{reluctance}}$   $N_1 i_1 = N_2 i_2$  $\frac{i_1 = N_2}{N_2}$ 




 $\frac{v_1}{v_2} = \frac{e_1}{e_2} = \frac{V_1}{V_2} = \frac{N_1}{N_2}$  $\frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{e_2}{e_1} = \frac{v_2}{v_1}$ 

Therefore,

 $v_1 i_1 = v_2 i_2$  $e_1 i_1 = e_2 i_2$ 

Volt-amperes at both the sides are same

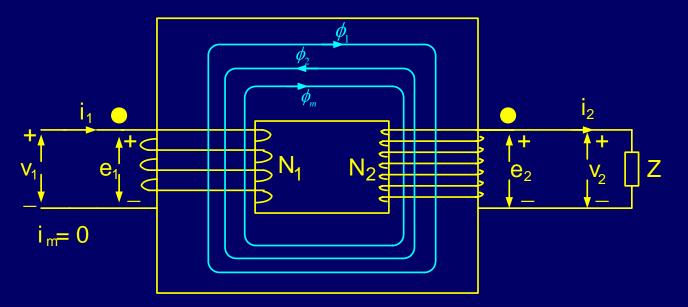

Impedance seen by winding-1,

$$Z = \frac{v_2}{i_2} = \frac{e_2}{i_2}$$

Impedance seen by winding-2,

$$Z' = \frac{v_1}{i_1} = \frac{\frac{N_1 v_2}{N_2}}{\frac{N_2 i_2}{N_1}} = \left(\frac{N_1}{N_2}\right)^2 \frac{v_2}{i_2} = \left(\frac{N_1}{N_2}\right)^2 Z$$