

Question 1) For the circuit in picture,

- what is the minimum number of mesh (or loop) equations required to find all branch currents in the circuit. Arrange the mesh equations in a matrix form.
- What is the minimum number of node equations required to solve for all voltages across the components of the circuit. Arrange the node equations in a matrix form.
- Which method (mesh or node) do you think is more computationally efficient for this circuit.

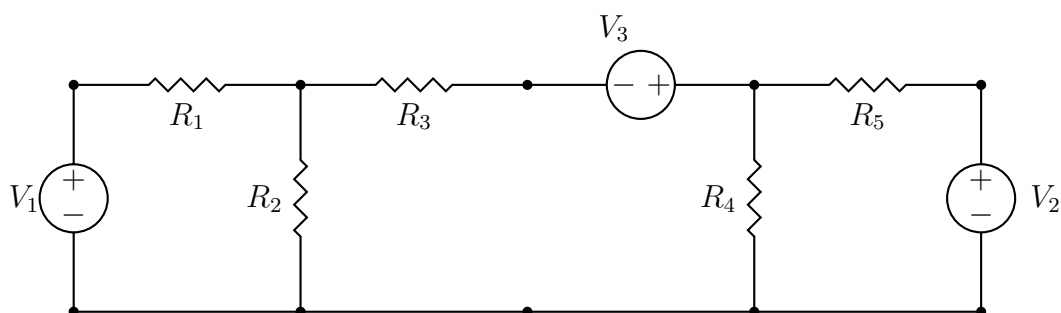


Figure 1: Circuit for Question 1

Question 2) Let the current through resistor R_j be i_j . Find the values of i_j in the circuit shown below.

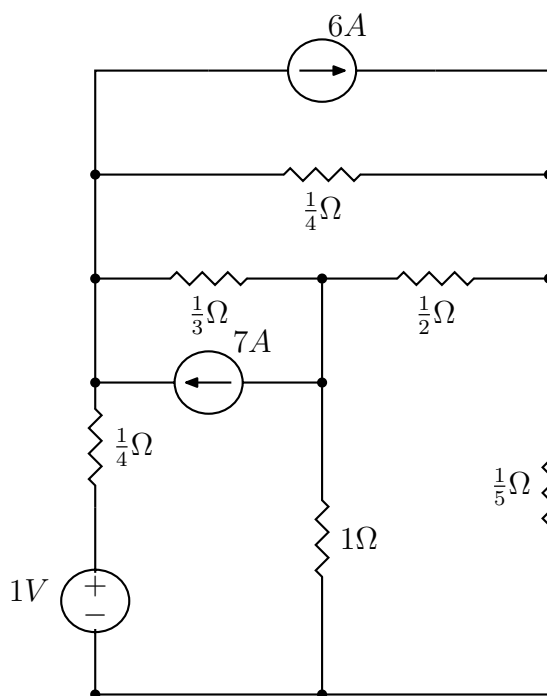


Figure 2: Circuit for Question 2

Question 3) In Figure 3, find the current i through the 2Ω resistor using loop analysis.



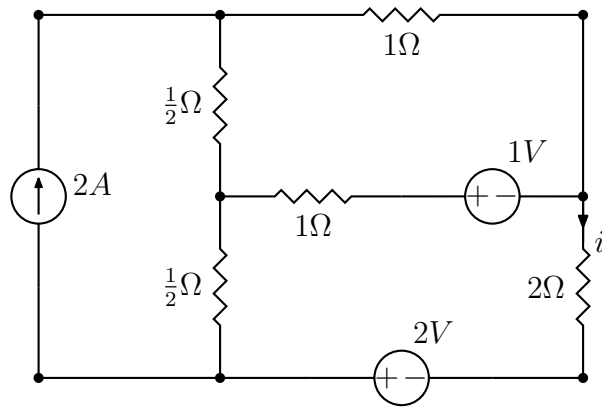


Figure 3: Circuit for Question 3


Question 4) Find the voltage gain, i.e. $\frac{v_o}{v_{in}}$ from the circuit below.

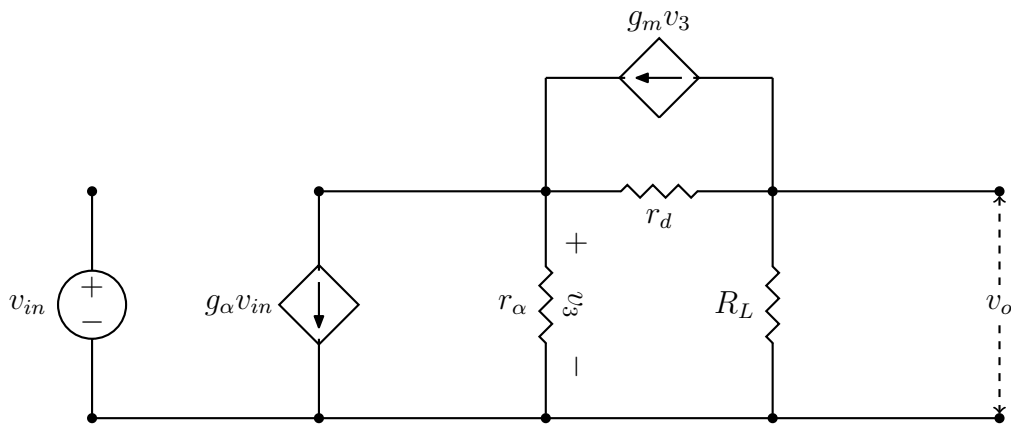

Question 5) Determine the currents that flow in each resistor using superposition theorem.

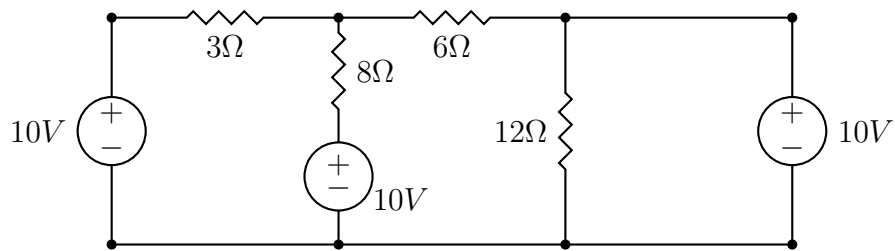

Question 6) Determine i and v using superposition theorem.

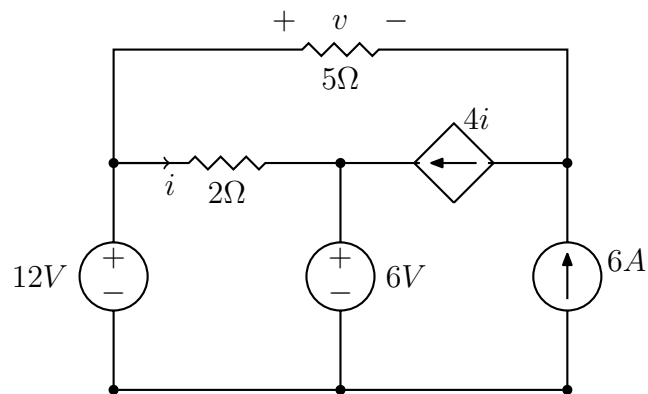

Question 7) Solve the problem in Question 2 using mesh analysis(if you have used node analysis there).