

Indian Institute of Technology Bombay

Dept of Electrical Engineering

Handout 7

EE 101 Electrical & Electronic Circuits

Tutorial 5

Aug 19, 2011

Question 1) Which of the following series RLC circuits are (i) under-damped, (ii) critically damped and (iii) over-damped? The capacitors and inductors were de-energized at $t < 0$. If a step voltage of $2V$ ($v = 0$ for $t < 0$ and $v = 2V$ for $t \geq 0$) is applied to the circuits, determine the current in each case.

1. $R = 4\Omega, L = 2H, C = \frac{1}{2}F$
2. $R = 2\Omega, L = 1H, C = \frac{1}{2}F$
3. $R = 5\Omega, L = 3H, C = \frac{1}{3}F$

Question 2) The initial conditions are zero for the circuit in Figure 2. A step voltage of V_{in} Volts is applied at time $t = 7s$. This means that the applied voltage is zero before time $7s$ and the level changes to V_{in} there after. You are required to find the voltage $v_c(t)$ across the capacitor.

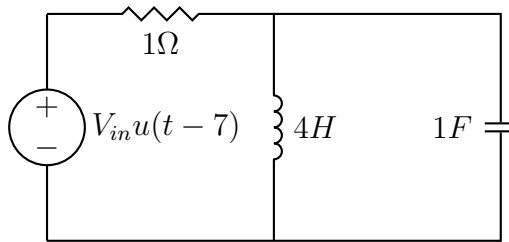


Figure 2

Hint: This can be solved faster, if you know the current solution of the series RLC circuit. In particular, this circuit is in some sense a dual of the RLC circuit we extensively discussed in class.

Question 3) The switch in Figure 3 is closed at time $t = 0$.

1. What is the voltage across the capacitor at $t = 0$.
2. What are the values of $i_1(t)$ and $i_2(t)$.

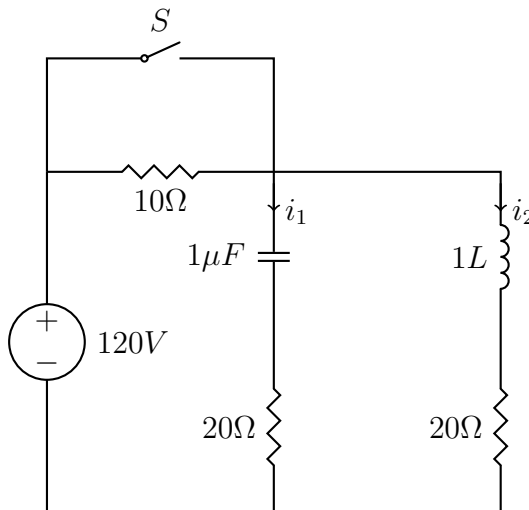


Figure 3.

Question 4) The switch in Figure 4 is at position a for a long time. At $t = 5 : 00pm$ today, the switch was moved to position b . Find the voltage $v_c(t)$ across the capacitor for all time.

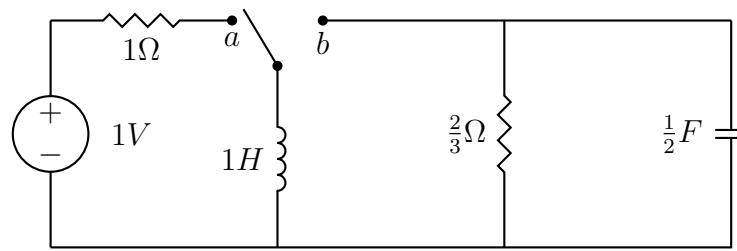


Figure 4

Question 5) Find $v_1(t)$ and $v_2(t)$ if the voltage is $6(1 - u(t))$. (This is to compensate for Problem 5 of Tutorial 4, where a switch was present, which renders the circuit currents to zero after time zero. So you can ignore Problem 5 from Tutorial 4).

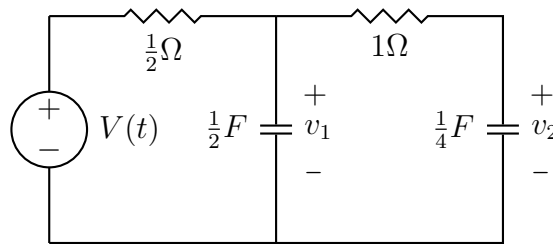


Figure 5

Question 6) Find $v(t)$ and $i(t)$ if the input $V(t) = 12(1 - u(t))$.

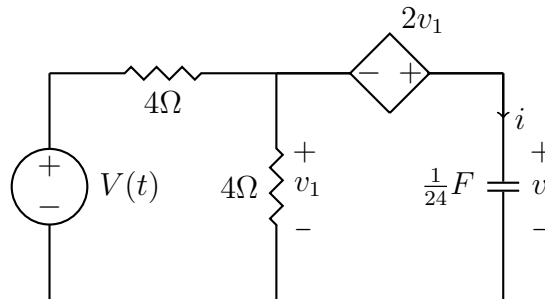


Figure 6

Question 7) If $K_1 = -3$, find the voltage across the capacitor $v_c(t)$.

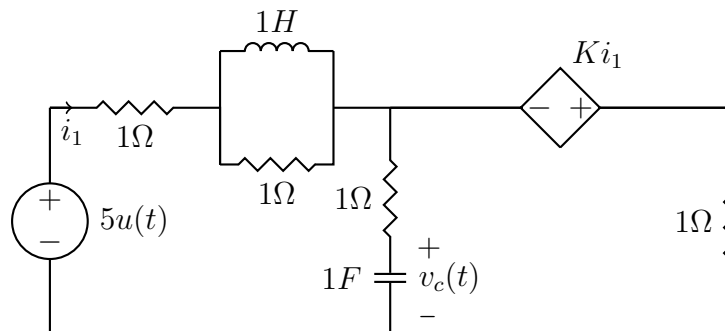


Figure 7