

Indian Institute of Technology Bombay  
Dept of Electrical Engineering

**Handout 8**  
Tutorial 6

**EE 101 Electrical & Electronic Circuits**  
Aug 26, 2011

**Question 1)** Let an input of  $V(t) = 240 \sin(\omega_0 t + \frac{\pi}{4})$  Volts is applied as input to the circuit below. At what value of  $\omega_0$  will the voltage sinusoid  $v_R(t)$  achieve the minimal amplitude. (Recall that amplitude of a sine wave is the maximal level it can take, i.e.  $\alpha$  in  $\alpha \sin(\omega t)$  )

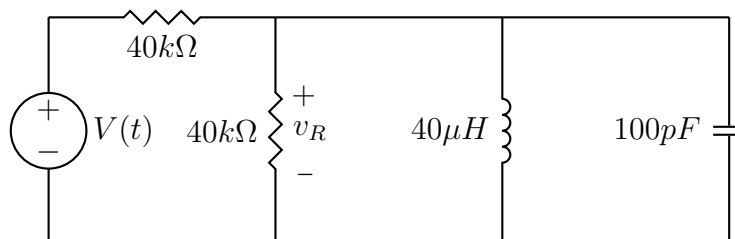


Figure 1

Can you justify the term **resonant frequency**, for the  $\omega_0$  you found in the question above.

**Question 2)** Find the voltage across the inductor if  $V(t) = e^{-5t} \cos(4t - 30^{\text{deg}})u(t)$  Volts.

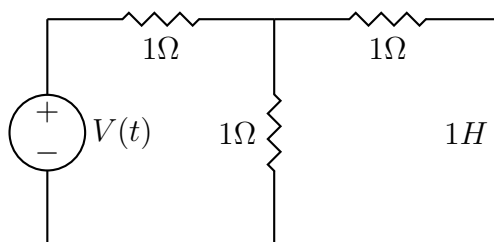


Figure 2

**Question 3)** If  $V(t) = 10 \cos(2t - \frac{\pi}{3})$ , find the Thevenin equivalent between A and B.

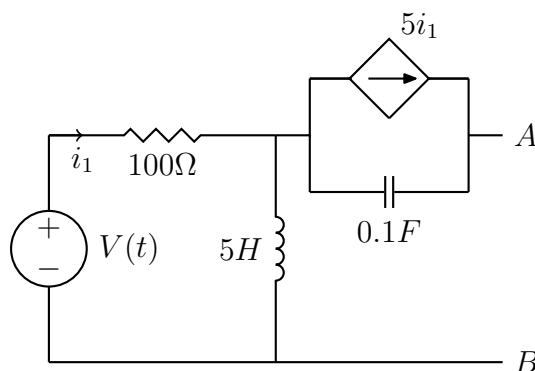


Figure 3

**Question 4)** In Figure 4, let  $V(t) = 24\sqrt{2}\cos(2t)$  Volts. Find the voltage across terminals  $A$  and  $B$ .

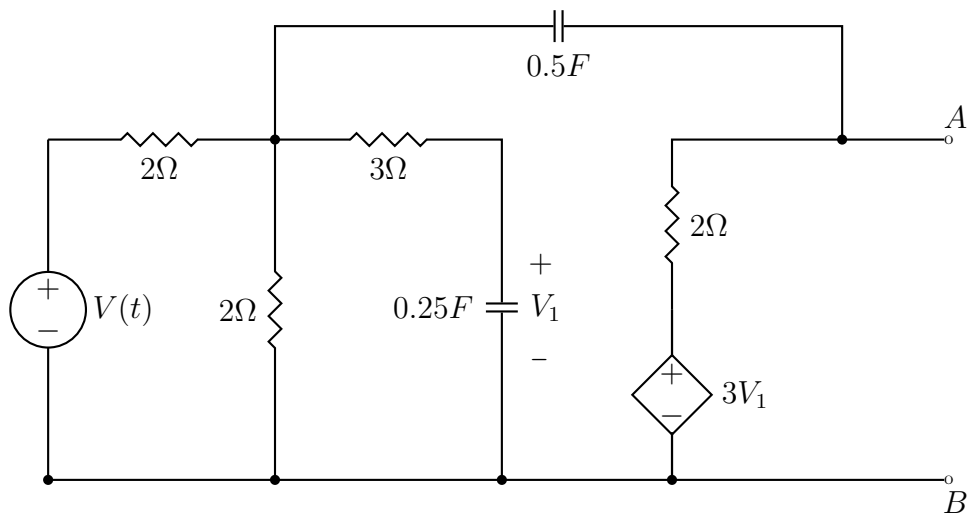


Figure 4

**Question 5)** If  $V_1(t) = \cos 4t$  and  $V_2(t) = 2 \sin 8t$ , find the current through the capacitor.

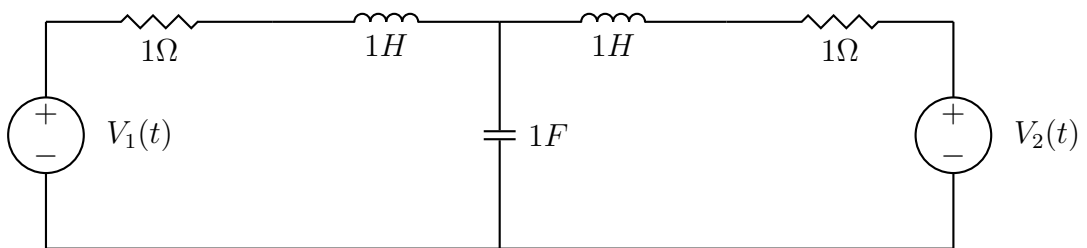


Figure 5