

Design of a Gm-C filter of very low trans-conductance & highly resistant to out-of-band Electromagnetic Interferences

Presented by

Snehasish Roychowdhury



Department of Electrical Engineering,

IIT Bombay

Application: G_m -C filter of few Hz cut-off

▪ Bio-Medical applications:

- Pulse rate of a human body is 72 pulses/min on average.
- Hence, to isolate and detect our pulses from environmental noises in electronic systems, low pass filters of cut-off frequency in Hz is needed.
- This is how we can reduce the out of band noises and interferences by low pass filtering.

Cut-off frequency of G_m-C filter

- $(v_{in} - v_{out}) * G_m = I_{out}$

Again,

- $v_{out} = I_{out} * \left(\frac{1}{sC_{load}}\right)$


Hence, $(v_{in} - v_{out}) * G_m = sC_{load}v_{out}$

- $v_{in} * G_m = (sC_{load} + G_m) * v_{out}$

- $\frac{v_{out}}{v_{in}} = \frac{1}{1 + \frac{sC_{load}}{G_m}}$

- Hence, DC gain= 0dB

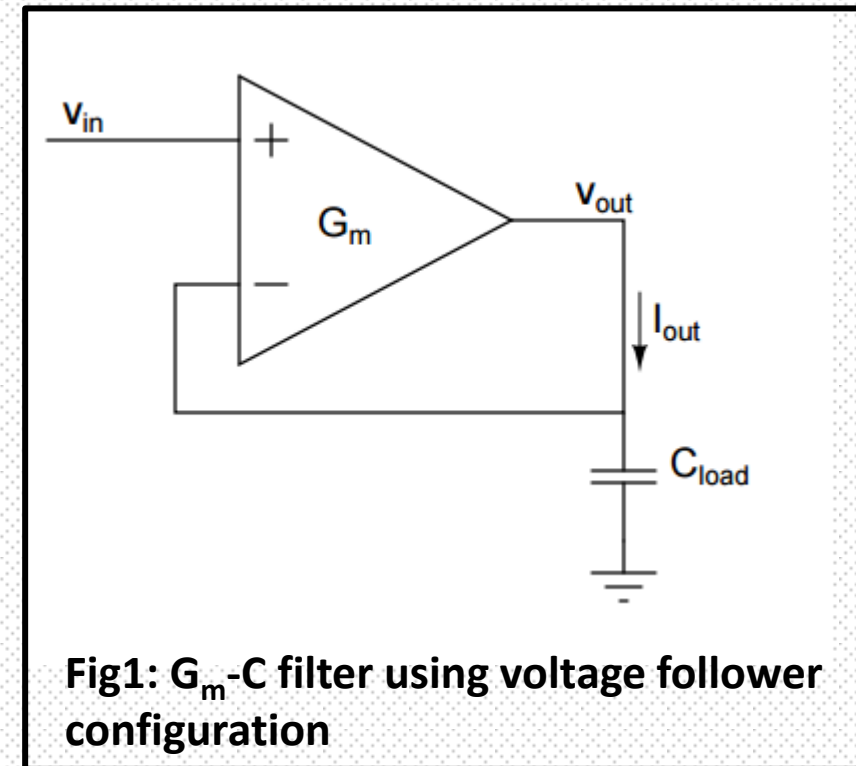- Cut-off frequency of the filter is : $\frac{G_m}{2\pi C_{load}}$ Hz



Block diagram of G_m -C filter

□ Cut-off freq = $\frac{G_m}{2\pi C_{load}}$

□ For 70Hz, $C_{load} = 1\text{pF}$,


$G_m = 0.47\text{nA/V}$.

$$G_m = \frac{i_{out}}{v_{id}} = \frac{i_{out}}{v_{im}} * \text{Attn. factor} \left(\frac{1}{k}\right)$$

□ Voltage attenuator at input stage reduces G_m

□ 2nd stage **Trans-conductor**: Input: v_{im} (voltage), output: I_{out} (current)

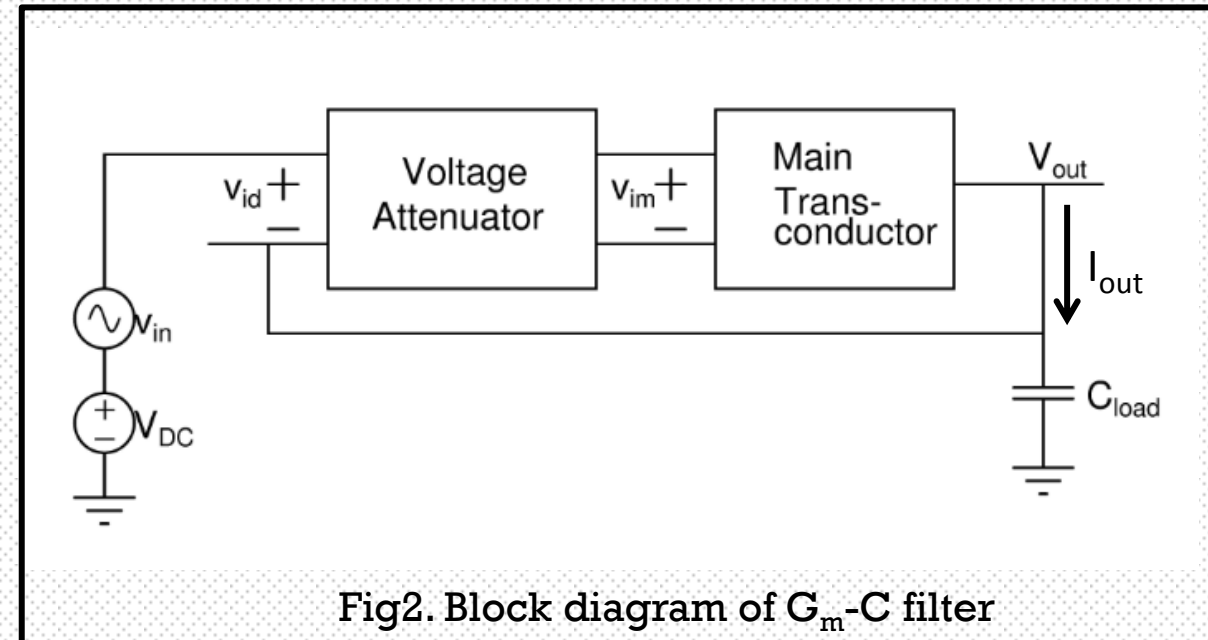□ All transistors in G_m -C filter are in **sub-threshold** region.



Cross-coupled trans-conductor design:

$$I_{o1} = I_1 + I_3 \text{ \& } I_{o2} = I_2 + I_4$$

$$\frac{I_1}{I_2} = \frac{\exp\left(\frac{v_{ss1}-v_{m1}}{nV_T}\right)}{\exp\left(\frac{v_{ss1}-v_{m2}}{nV_T}\right)} = \exp\left(\frac{-v_{im}}{nV_T}\right)$$

$$\frac{I_3}{I_4} = \frac{\exp\left(\frac{v_{ss2}-v_{m2}}{nV_T}\right)}{\exp\left(\frac{v_{ss2}-v_{m1}}{nV_T}\right)} = \exp\left(\frac{v_{im}}{nV_T}\right)$$

Now,

$$\frac{I_1 - I_2}{I_1 + I_2} = \frac{\exp\left(\frac{-v_{im}}{nV_T}\right) - 1}{\exp\left(\frac{-v_{im}}{nV_T}\right) + 1} = \frac{\exp\left(\frac{-v_{im}}{2nV_T}\right) - \exp\left(\frac{v_{im}}{2nV_T}\right)}{\exp\left(\frac{-v_{im}}{2nV_T}\right) + \exp\left(\frac{v_{im}}{2nV_T}\right)} = -\tanh\left(\frac{v_{im}}{2nV_T}\right)$$

$$\Rightarrow I_1 - I_2 = -I_{ss1} \tanh\left(\frac{v_{im}}{2nV_T}\right)$$

$$\Rightarrow I_3 - I_4 = I_{ss2} \tanh\left(\frac{v_{im}}{2nV_T}\right)$$

$$\Rightarrow I_{od} = I_{o1} - I_{o2} = (I_{ss2} - I_{ss1}) \tanh\left(\frac{v_{im}}{2nV_T}\right) \dots\dots (1)$$

Inputs of the trans-conductor: v_{m1} & v_{m2}

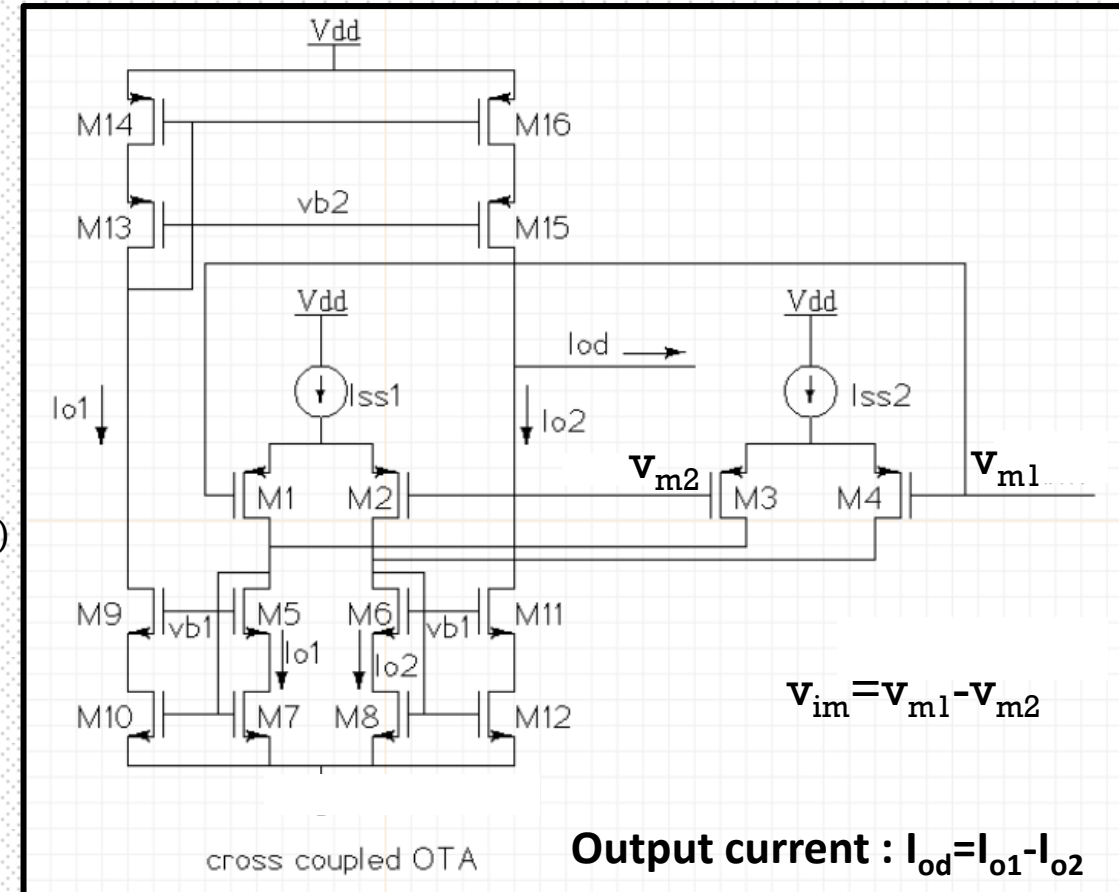


Fig3. Cross-coupled Trans-conductor

Voltage attenuator design:

□ DC Analysis:

Assume all g_m 's & I_{bias} 's are equal. Hence,

$$I_1 = I_3 = I_5 \quad \& \quad I_2 = I_4 = I_6$$

Now, for DC analysis, $V_1 = V_2$

By symmetry,

$$V_a = V_b = V_c \quad \&$$

$$V_1 = V_{m1} = V_{m2} = V_2 \quad \dots\dots\dots (2)$$

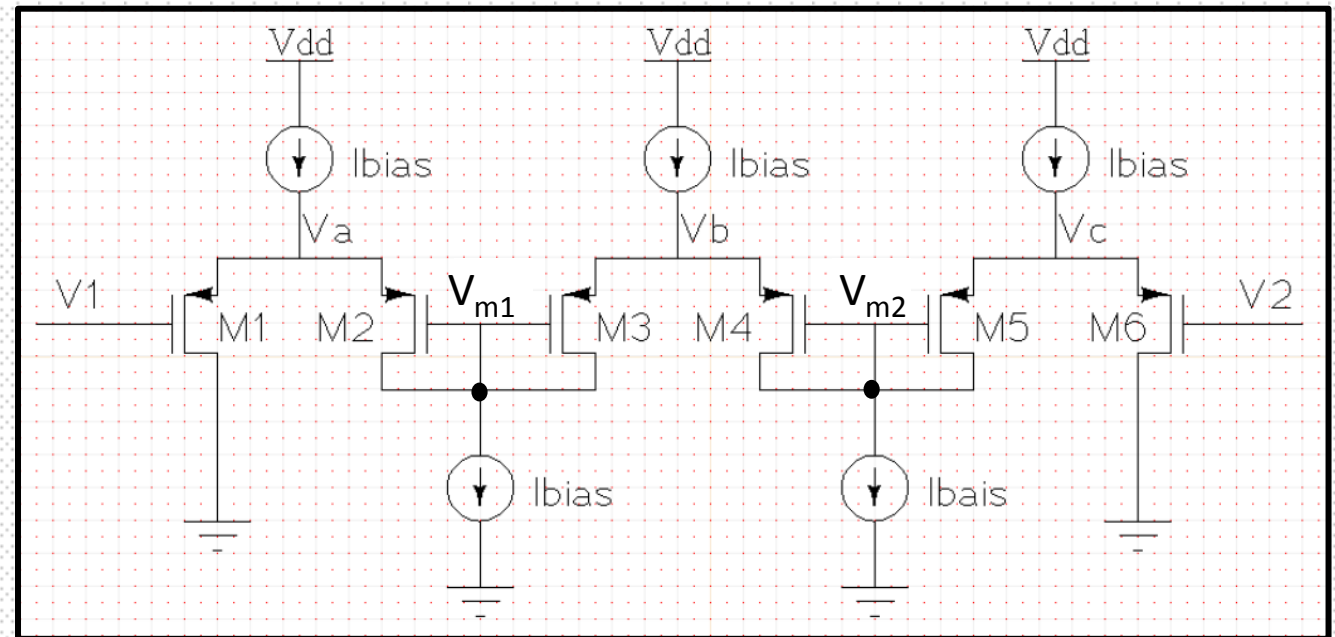


Fig4. Normal voltage attenuator

Fig ref: Sawigun, C.; Pal, D.; Demosthenous, A., "A wide-input linear range sub-threshold transconductor for sub-Hz filtering," in Circuits and Systems (ISCAS), Proceedings of 2010 IEEE International Symposium on , vol., no., pp.1567-1570,2010

Voltage attenuator design (Ctd.)

□ Small signal Analysis:

Assumed all g_m 's are equal.

$$\Rightarrow (v_a - v_1) + (v_c - v_2) = 0$$

$$\& \frac{g_m}{4} (v_a - v_c) = g_m (v_c - v_2)$$

$$\Rightarrow (v_a - v_b) = \frac{2}{3} (v_1 - v_2) \dots\dots (3)$$

$$\text{Again, } \frac{g_m}{4} (v_a - v_c) = g_m (v_a - v_{m1}) = g_m (v_{m2} - v_c)$$

$$\text{By solving: } v_{m1} - v_{m2} = \frac{v_a - v_b}{2} \dots\dots\dots (4)$$

$$\text{From (3) \& (4), } v_{m1} - v_{m2} = v_{im} = \frac{v_1 - v_2}{3} = \frac{v_{id}}{k} \dots\dots\dots (5)$$

Attenuation factor for one stage attenuator = $(1/k)$.

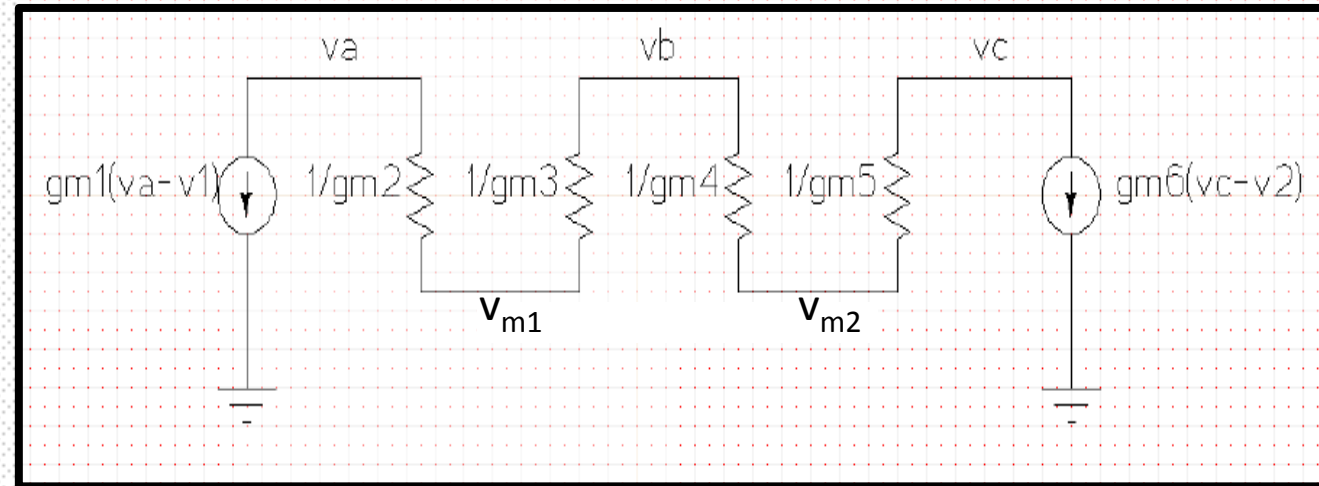



Fig5. ac equivalent of voltage attenuator

Overall trans-conductor

From (1) & (5),

$$I_{od} = (I_{SS2} - I_{SS1}) \tanh\left(\frac{v_{id}}{2knV_T}\right) \&$$
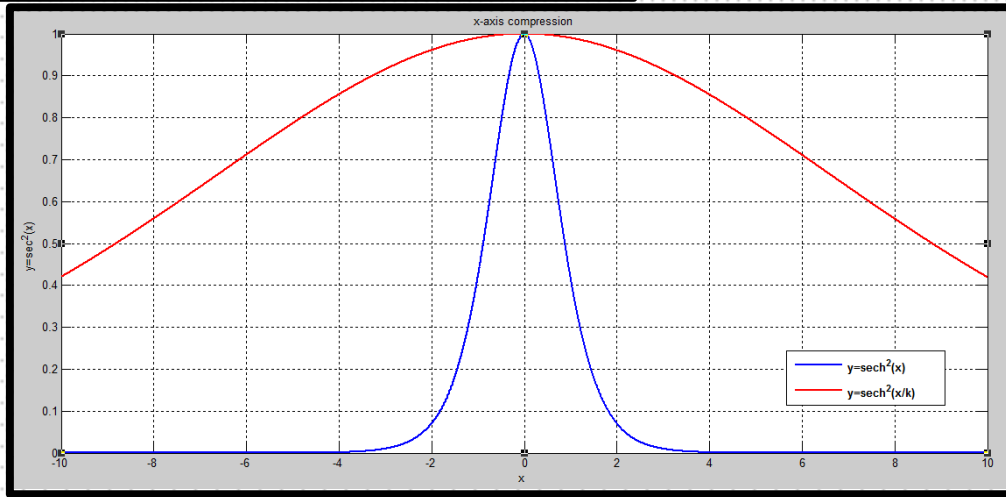
$$G_m = \frac{(I_{SS2} - I_{SS1})}{2knV_T} \operatorname{sech}^2\left(\frac{v_{id}}{2knV_T}\right) \dots (6)$$



- Voltage Attenuator takes role in x-axis compression too.
- Cross-coupled trans-conductor reduces G_m .
- From Simulation: $I_{SS1} = 4nA, I_{SS2} = 5.23nA, k = 3$
- From eqn(6): $G_m \approx 0.47nA/V$. From simulation, G_m has almost constant value: $0.4637nS$ upto $140mVpp$.

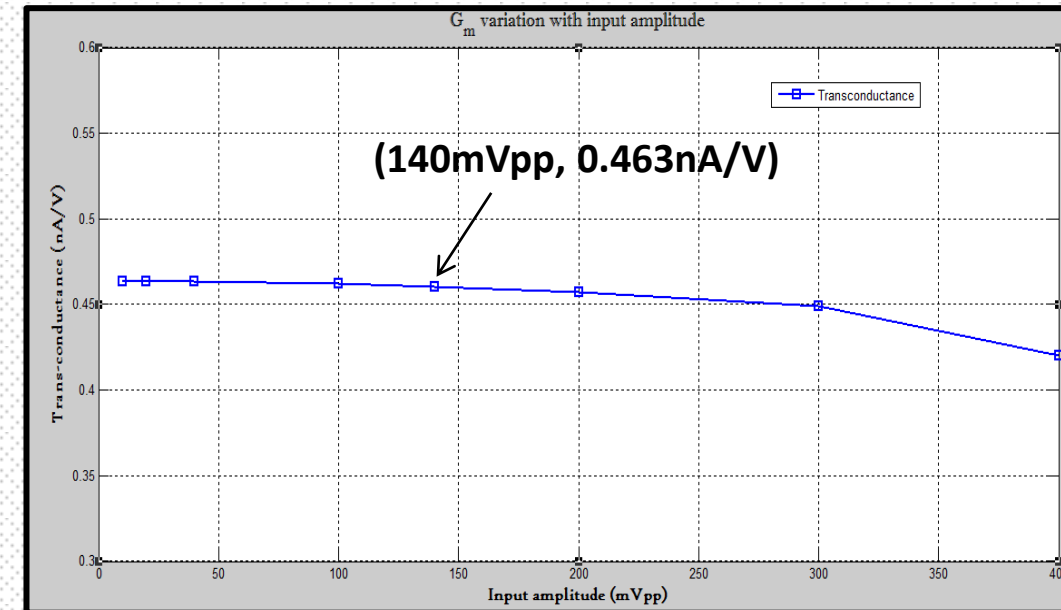
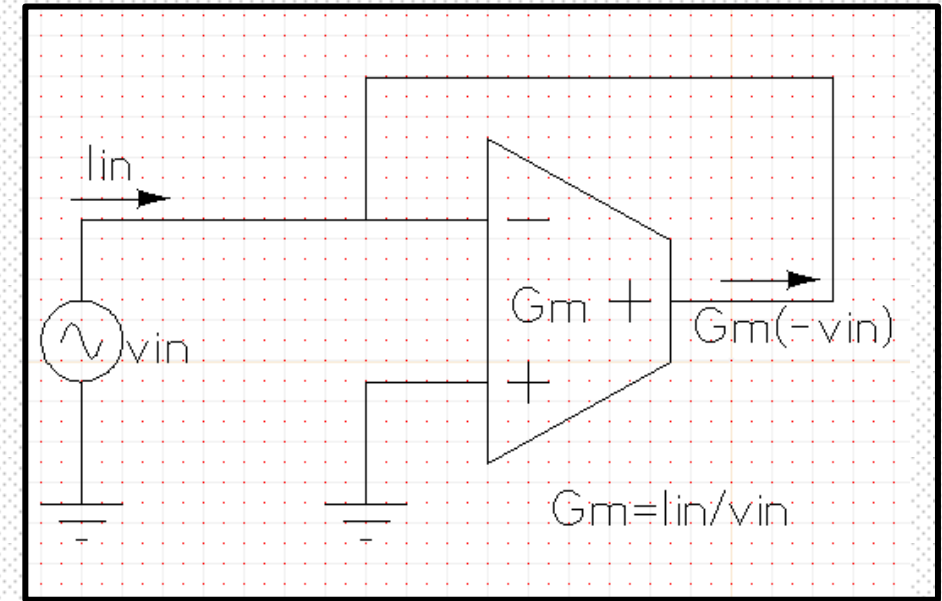


Fig6. G_m variation with input amplitude

1st order G_m-C filter response

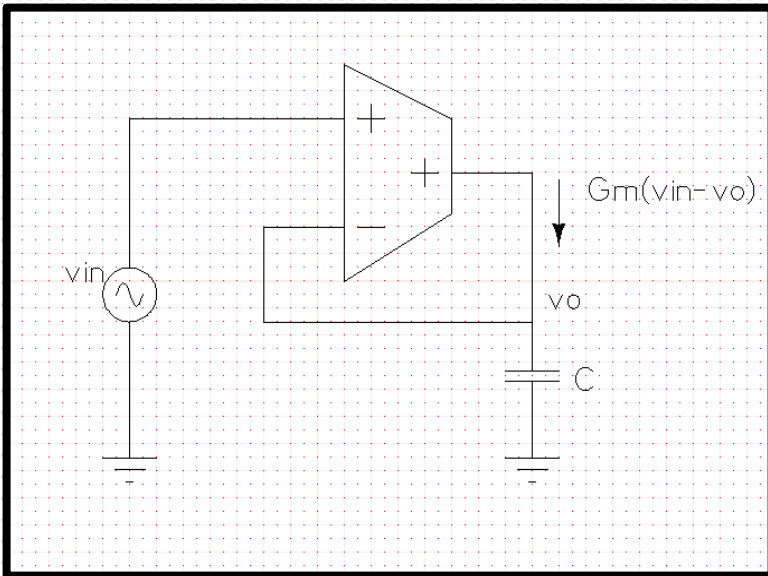


Fig7. Closed loop G_m-C filter

$$\text{Cut-off frequency, } f_o = \frac{g_m}{2\pi C_{Load}}$$

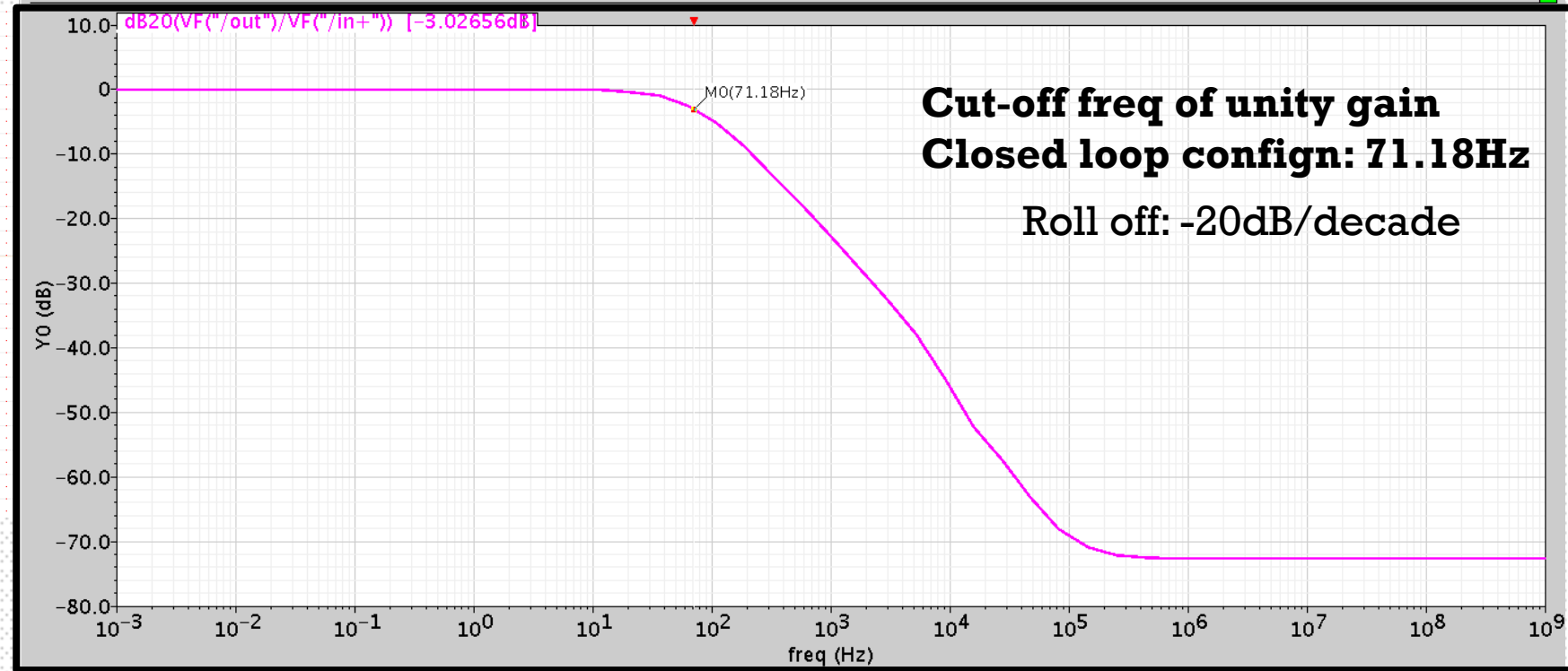


Fig8. ac response of the G_m-C filter

For G_m=0.463 nA/V , C_{load}=1pF , Theoretically cut-off frequency, f_o=70.53Hz.

HF linearity issue (coherent sampling)

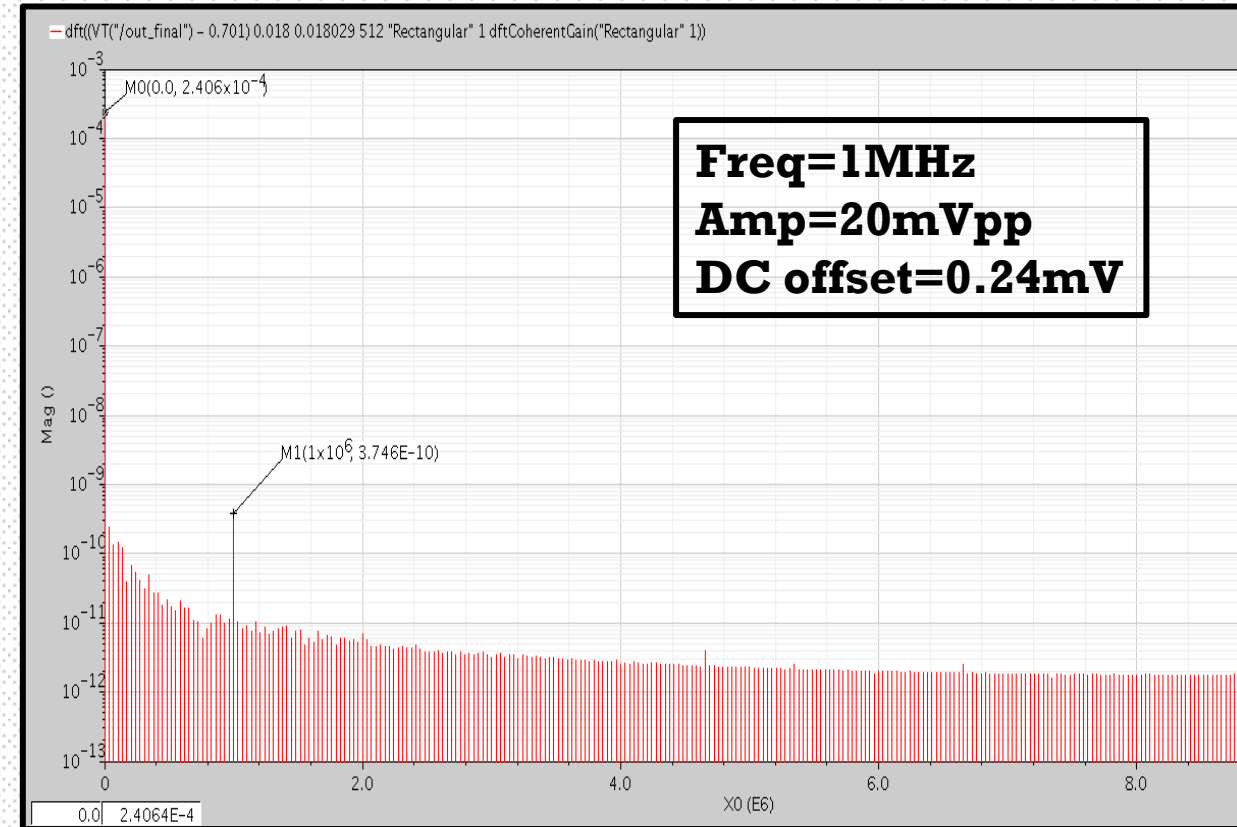
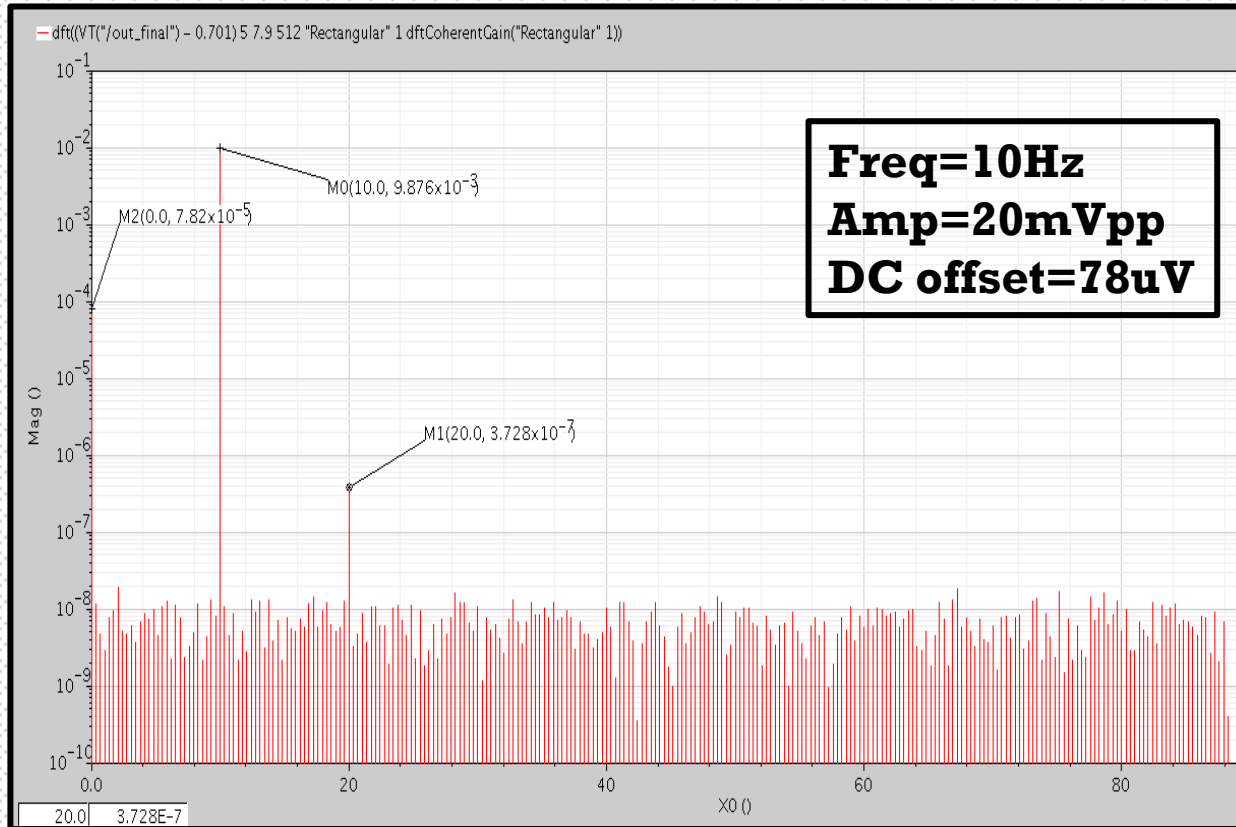


Fig10 : FFT Analysis (Log Magnitude vs frequency) with coherent sampling $N_{\text{WINDOW}}=29$, $N_{\text{RECOED}}=512$

High frequency Interferences

- Input stage offset is critical, as it is amplified at the output stage. So, we want to reduce offset at input stage, Voltage Attenuator.

- Unity gain configuration at high frequency

$$V_{out} = V_b = V_{DC}$$

Hence, CM interference,

$$v_{cm} = \frac{v_a + v_b}{2} = V_{DC} + \frac{v_{emi}}{2}$$

$$v_{dm} = v_a - v_b = v_{emi}$$


- It behaves like open loop

With both CM & DM

Interferences. DM inter-

ference can't be avoided.

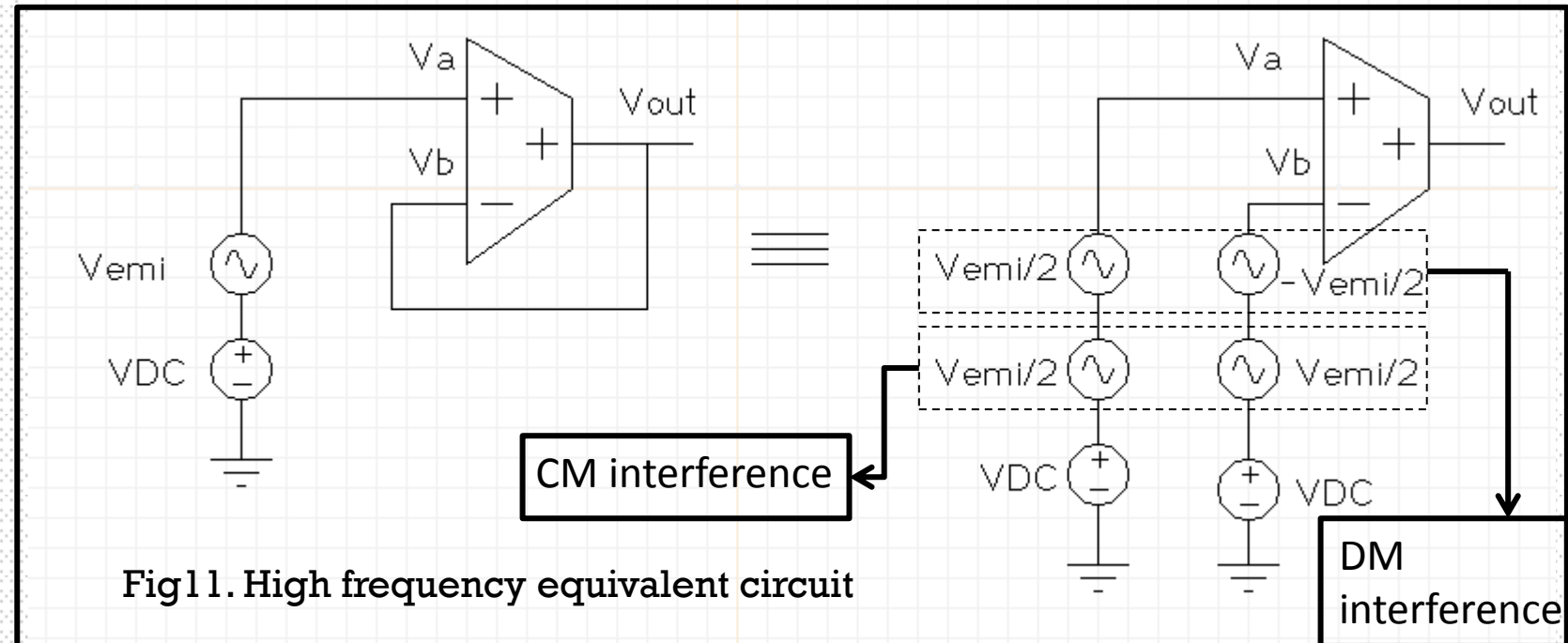- CM interference effect at output can be made zero by proper biasing technique.



CM & DM Interferences



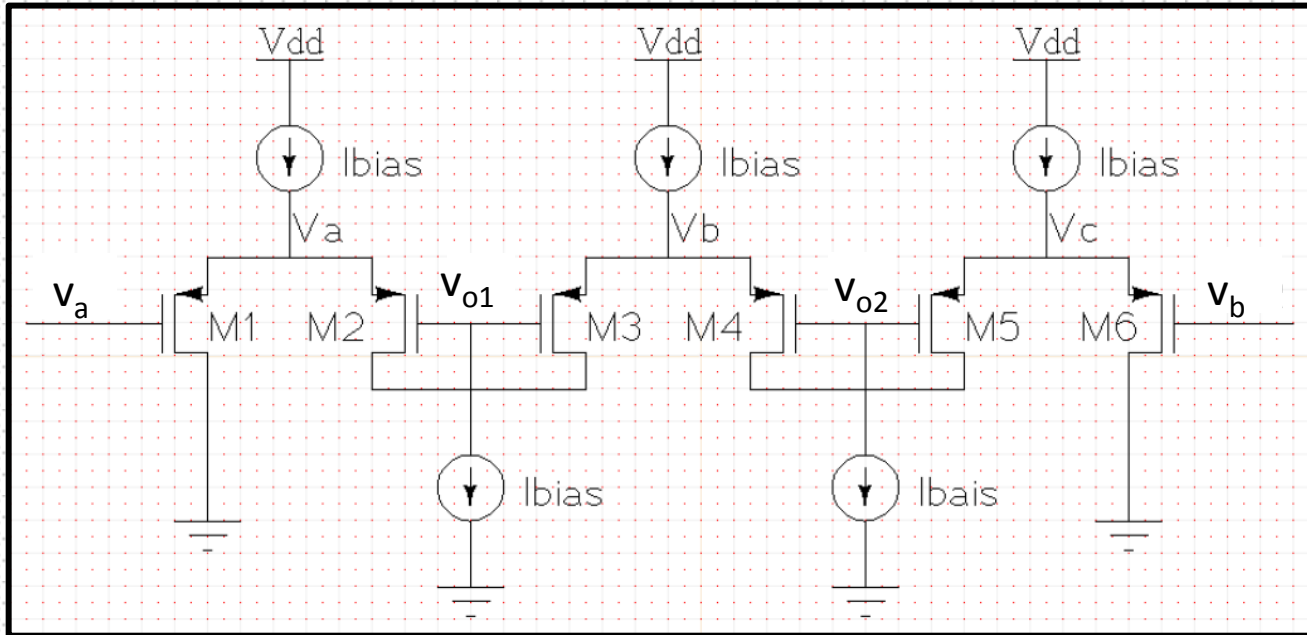


Fig12: Voltage attenuator

- $H_{cm} = \left. \frac{v_{o1,cm}}{v_{cm}} \right|_{v_{dm}=0}$
- $H_{dm} = \left. \frac{v_{o1,dm}}{v_{dm}/2} \right|_{v_{cm}=0}$
- Hence, $v_{o1} = H_{cm}v_{cm} + H_d v_d$
& $v_{o2} = H_{cm}v_{cm} - H_d v_d$

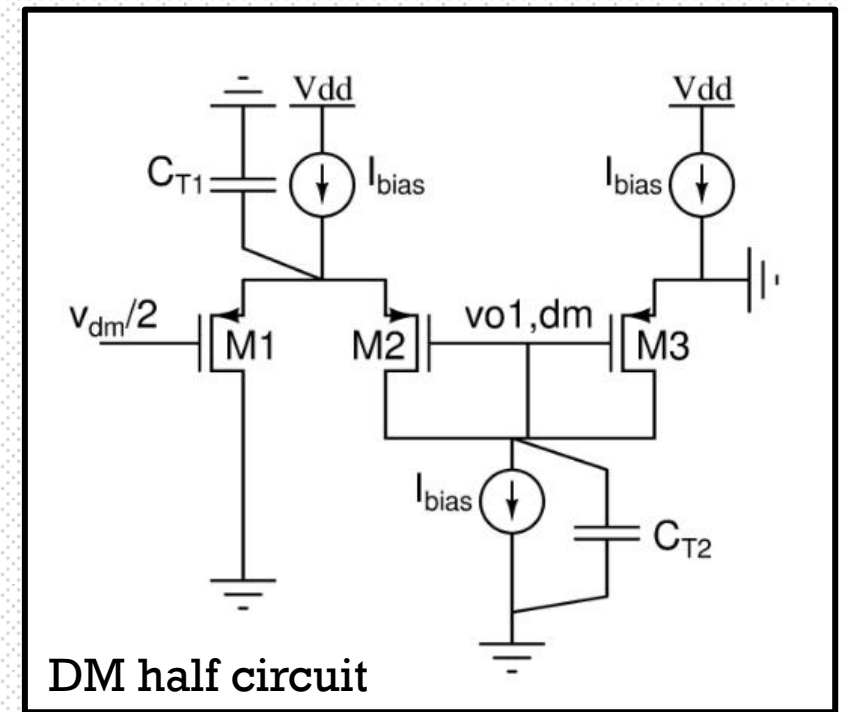

DM half circuit

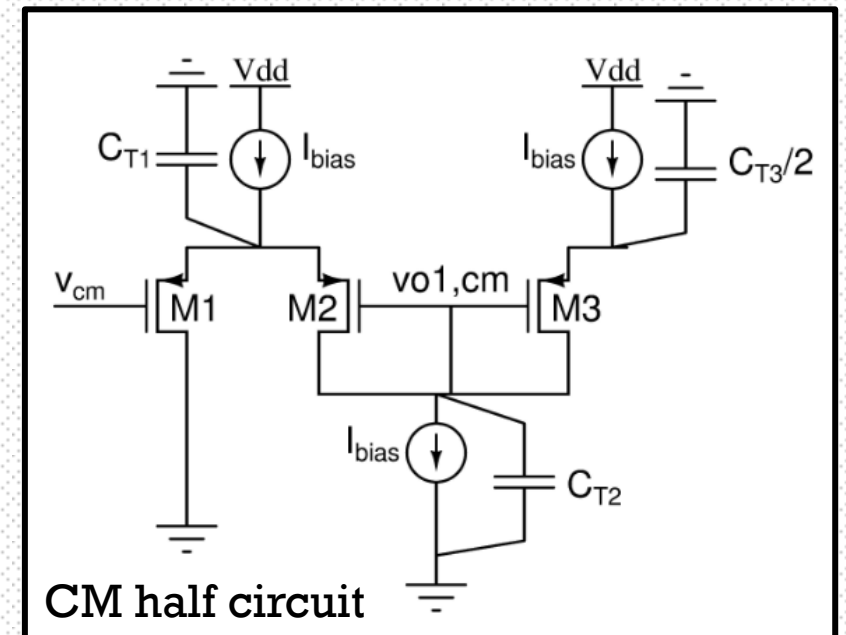

CM half circuit

Offset issues in front end Attenuator

Let, $x = A \sin(\omega t)$

For 2nd order harmonics at output:

$$x^2 = A^2 \sin^2(\omega t) = \frac{A^2}{2} (1 - \cos(2\omega t))$$

Hence, 2nd order harmonics give DC offset that can't be removed by low-pass filtering.


Offset 1 :

due to second order term : $a_2(H_{cm}v_{cm} + H_d v_d)^2$,

Offset 2 :

due to second order term : $a_2(H_{cm}v_{cm} - H_d v_d)^2$,

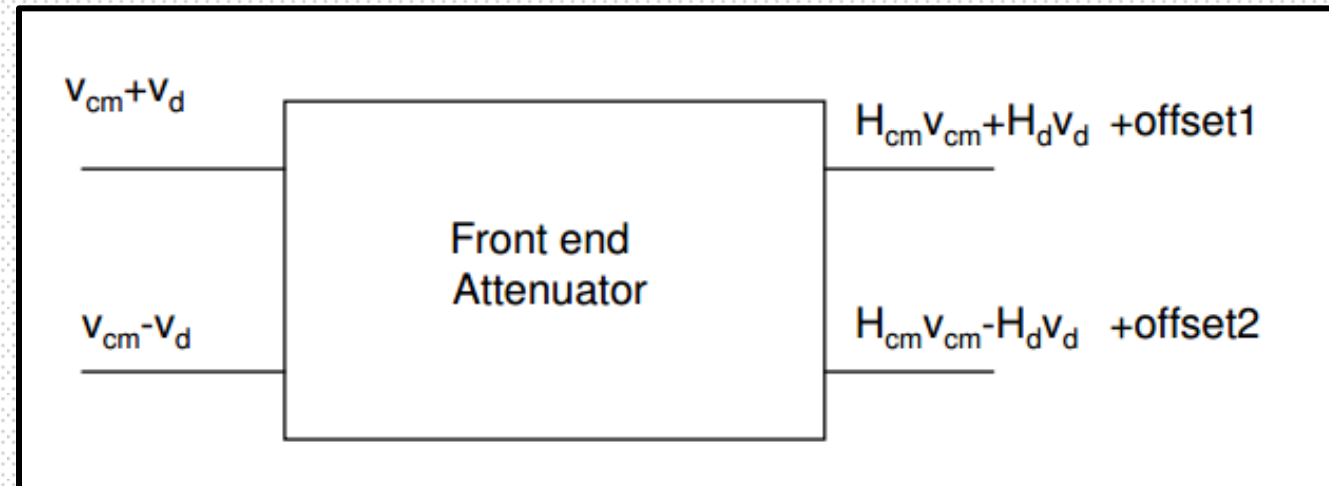Hence, Offset 1 & Offset 2 are significantly different values from each other.



Offset issues in front end Attenuator


- This offset will increase further in second stage, where differential input is amplified by a high gain factor.
- Let, net output $v_{out} = G * \{(\text{Offset1} - \text{Offset2}) + 2H_d v_d\}$, **G: gain of second stage= high**
- Draws huge offset at output.
- Hence, elimination of offset at the 1st stage is important.

Offset 1 :

due to : $a_2(H_{cm}v_{cm} + H_d v_d)^2$,

Offset 2 :

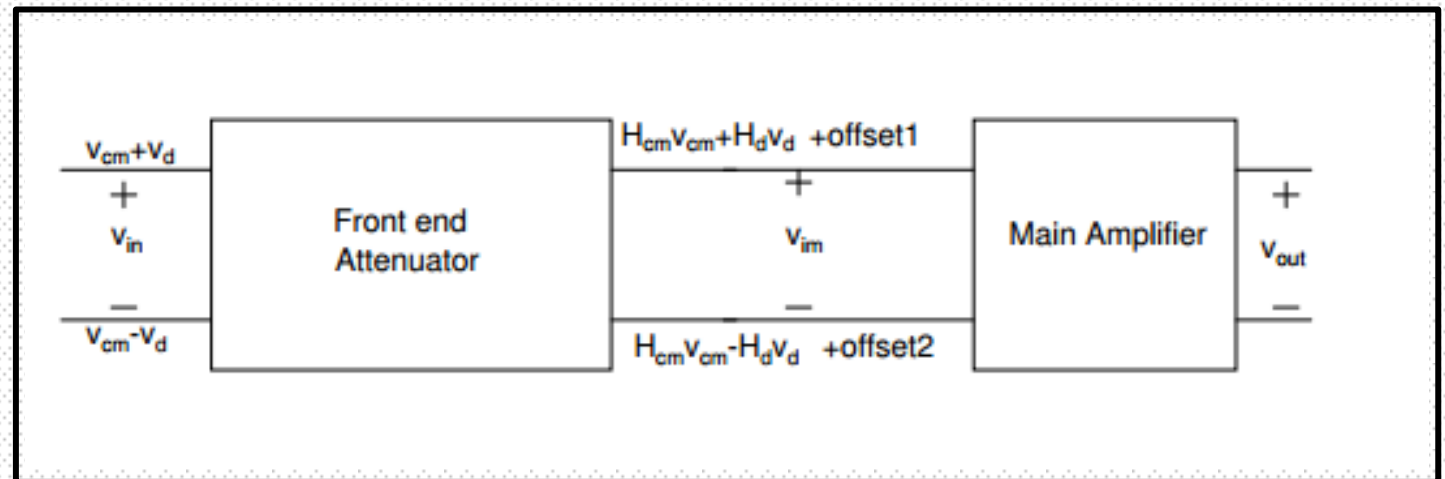due to : $a_2(H_{cm}v_{cm} - H_d v_d)^2$,



Solution : as $H_d \neq 0$, we can make $H_{cm} = 0$ for **Offset1 = Offset 2.**

By this, v_{out} gets rid of any DC offset.

Reduce CM interference:

Outputs of attenuator: $v_{o1} = H_{cm} v_c = v_{o2} = v_o$ (say) {as $v_{dm}=0$ here}

KCL at node s_1 (7), v_{o1} (8), s_2 (9):

$$(sC_{gs1} + g_m)(v_c - v_{s1}) + (g_m + sC_{gs2})(v_o - v_{s1}) = sC_{T1}v_{s1} \quad (7)$$

$$(g_m + sC_{gs2})(v_o - v_{s1}) + (g_m + sC_{gs3})(v_o - v_{s2}) + sC_{T2}v_o = 0 \quad (8)$$



$$(g_m + sC_{gs3})v_o = v_{s2}(g_m + s(C_{gs3} + C_{T3})) \quad (9)$$

From (9), find v_{s2} & Put in (8):

$$v_{s1} = \frac{v_{o1} \left(2g_m + s(C_{gs2} + C_{gs3} + C_{T2}) - \frac{(g_m + sC_{gs3})^2}{g_m + s(C_{gs3} + C_{T3})} \right)}{(g_m + sC_{gs2})}$$

$$\text{Put } v_{s1} \text{ in (7): } H_{cm} = \frac{v_{o1}}{v_{cm}} = \frac{(sC_{gs1})}{(g_m + sC_{gs2}) - \frac{2g_m + s(C_{T1} + C_{gs1} + C_{gs2})}{(g_m + sC_{gs2})} \left\{ 2g_m + s(C_{gs2} + C_{gs3} + C_{T2}) - \frac{(g_m + sC_{gs3})^2}{g_m + s(C_{gs3} + C_{T3})} \right\}}$$

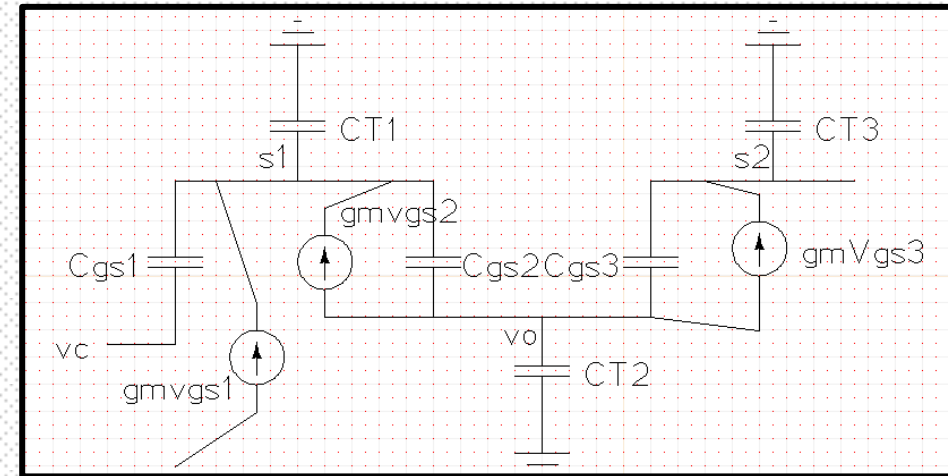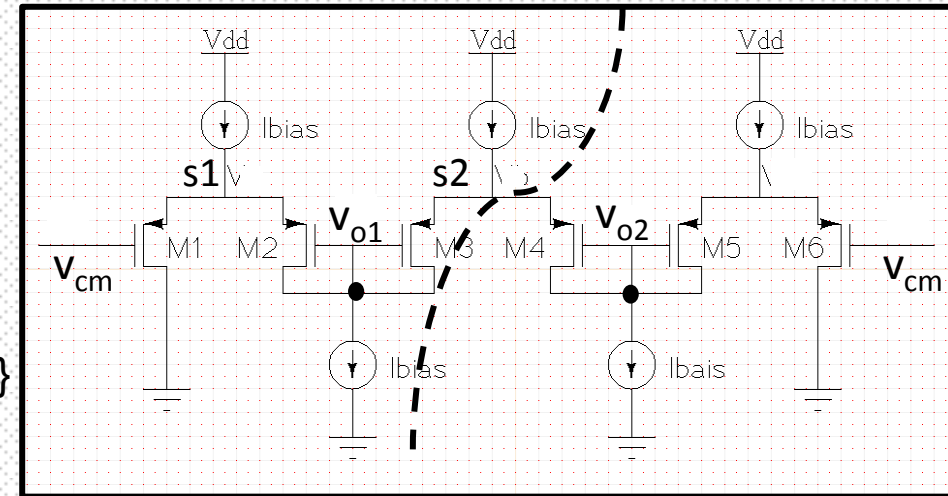- **Observation:** H_{cm} decreases if C_{T1} & C_{T3} decreases. We want to minimize C_{T1} & C_{T3} .
- $C_{T1} = C_{db} + C_{sb1} + C_{sb2}$, $C_{T3} = C_{sb3} + C_{db}/2$



Reduction of CM interference(Ctd.)

- $C_{T1} = C_{db} + C_{sb1} + C_{sb2}$, $C_{T3} = C_{sb3} + C_{db}/2$
- We want $C_{sb} = 0$, but in twin-tub CMOS process, shorting S to B causes high **well capacitance (C_{GND})** at source.
- Hence, one auxiliary pair source node(V_{s1}) is connected to bulk of main pair. This is **Source-buffered structure**.
- $C_{sb1} + C_{sb2}$ sees almost same potential across it. Though these two potentials are not exactly equal, but voltage across $C_{sb1} + C_{sb2}$ is very small, causing it to be virtually shorted.
- In advantage, S & B of main pair are decoupled.

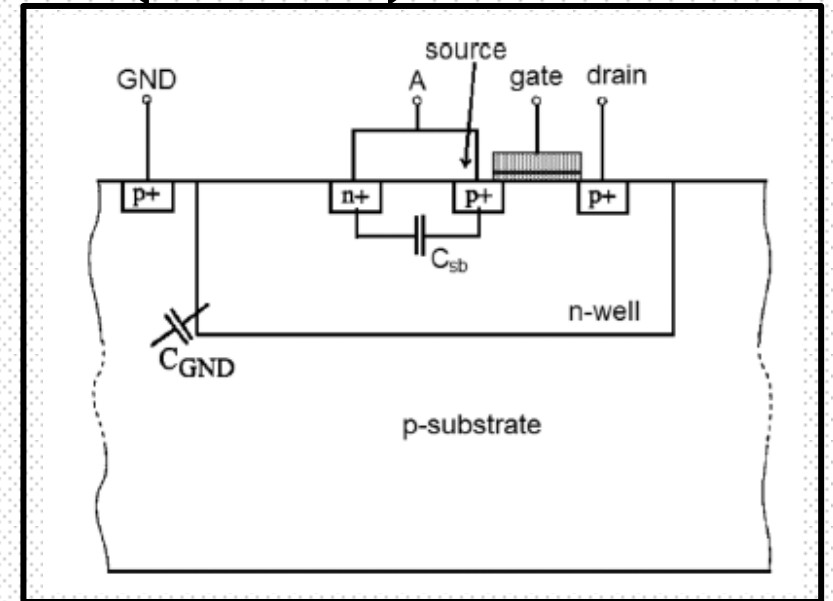


Fig14: vertical p-MOS, Fig15: Source-buffering

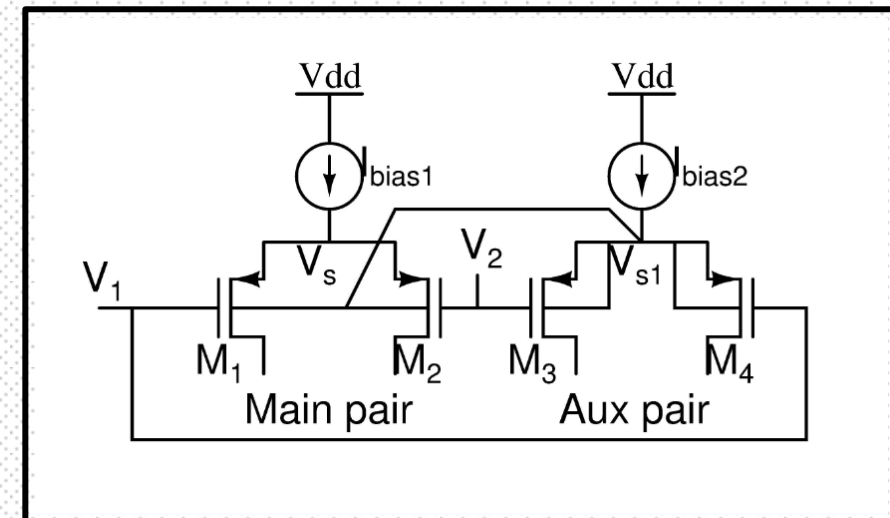


Fig14 Ref: Jingjing Yu; Amer, A.; Sanchez-Sinencio, E., "Electromagnetic Interference Resisting Operational Amplifier," in *Circuits and Systems I: Regular Papers, IEEE Transactions on* , vol.61, no.7, pp.1917-1927, July 2014

Calculation for CMTF (H_{cm})

Applying KCL at A,B,C,D,E,X nodes, we get six equations.

By solving these equations, we get:

$$H_{cm}(\infty) = \left(\frac{v_x}{v_1} \right) = \frac{\alpha_2 \gamma_1 - \alpha_1 \gamma_2}{\alpha_1 \beta_2 - \alpha_2 \beta_1}$$

Here, $\alpha_1, \alpha_2, \beta_1, \beta_2, \gamma_1, \gamma_2$ are constant values at very high Frequency, coming from parasitic capacitances & C_1 .

By making , $H_{cm}(\infty)=0$, we find a quadratic equation of C_1 .

By solving the equation , ($C_1 = C_{gs1} + C_{ext}$) we find:

$$C_{ext} = 95fF$$

Adding this amount of external capacitance will make $H_{cm} = 0$ at very high frequency.


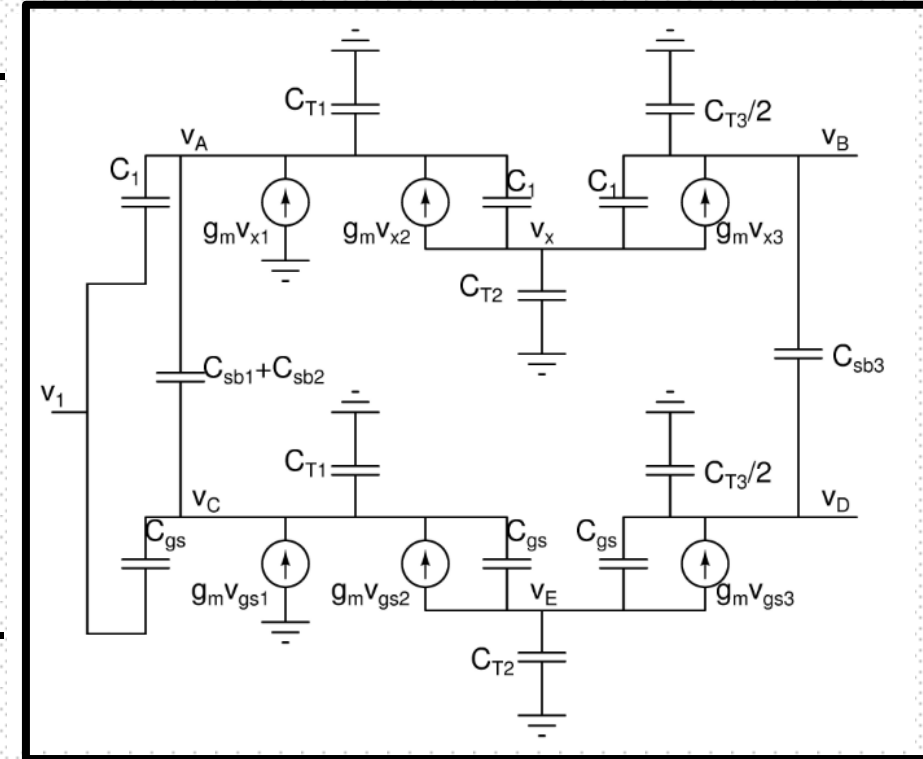


Fig18: ac equivalent model of Half Circuit for Common mode inputs



Comparison I (100mVpp)

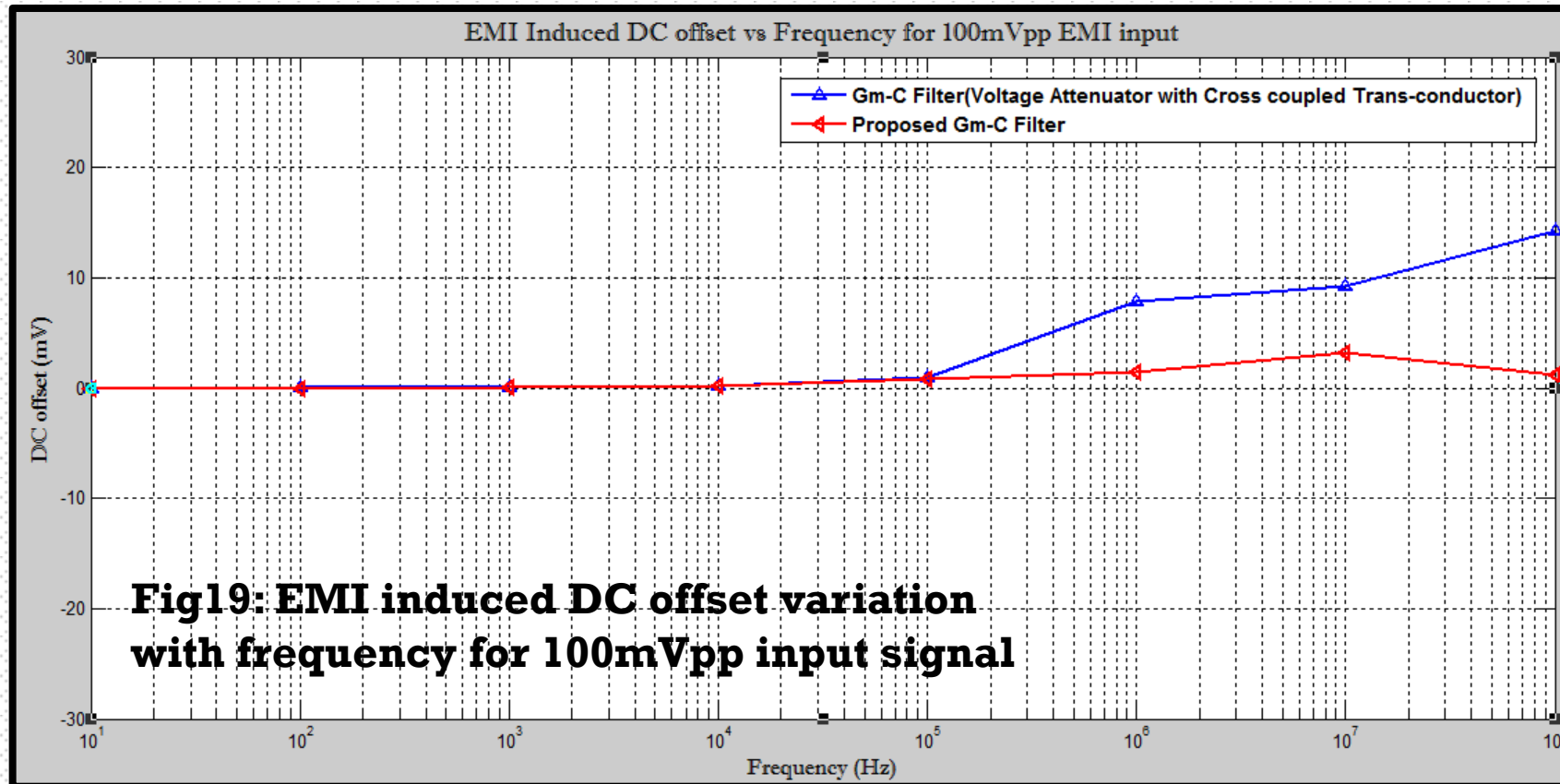

- Upto 100KHz, offsets are almost same as parasitic effect comes at high frequencies.
- Upto 100KHz, EMI induced Offset is very low (~uV). This proves good linearity of the filter at low frequency.
- Proposed Gm-C filter shows small offset even at high freq due to its immunity to CM interference.
- Acc to calculation, offset will reach zero at infinite frequency


- In frequency range [10Hz-100MHz], Maximum EMI induced offset (Magnitude): (i) Voltage attenuator with cross-coupled transconductor based G_m -C filter:: **1.996%** (ii) Proposed G_m -C filter:: **0.459%**

Comparison II (FFT: 50mVpp, 1MHz)

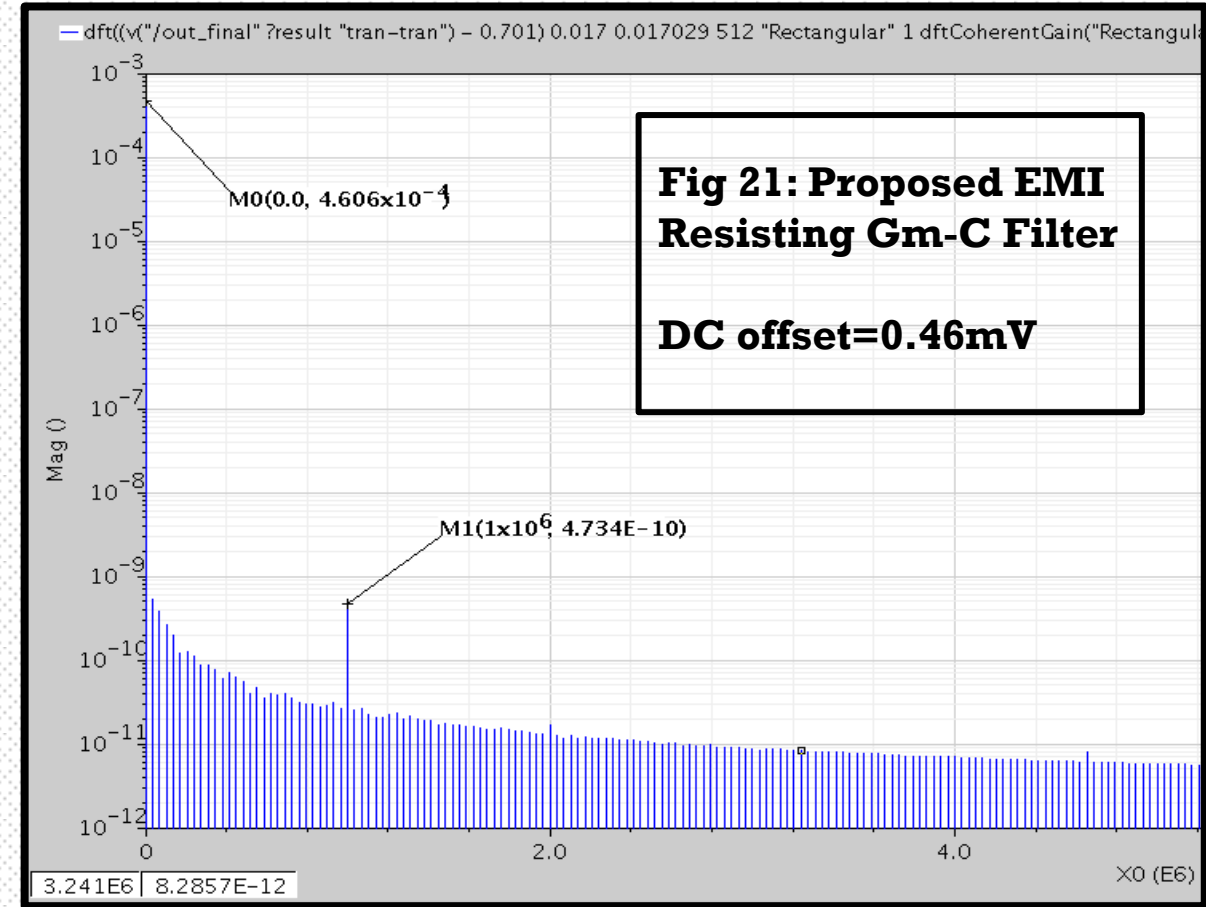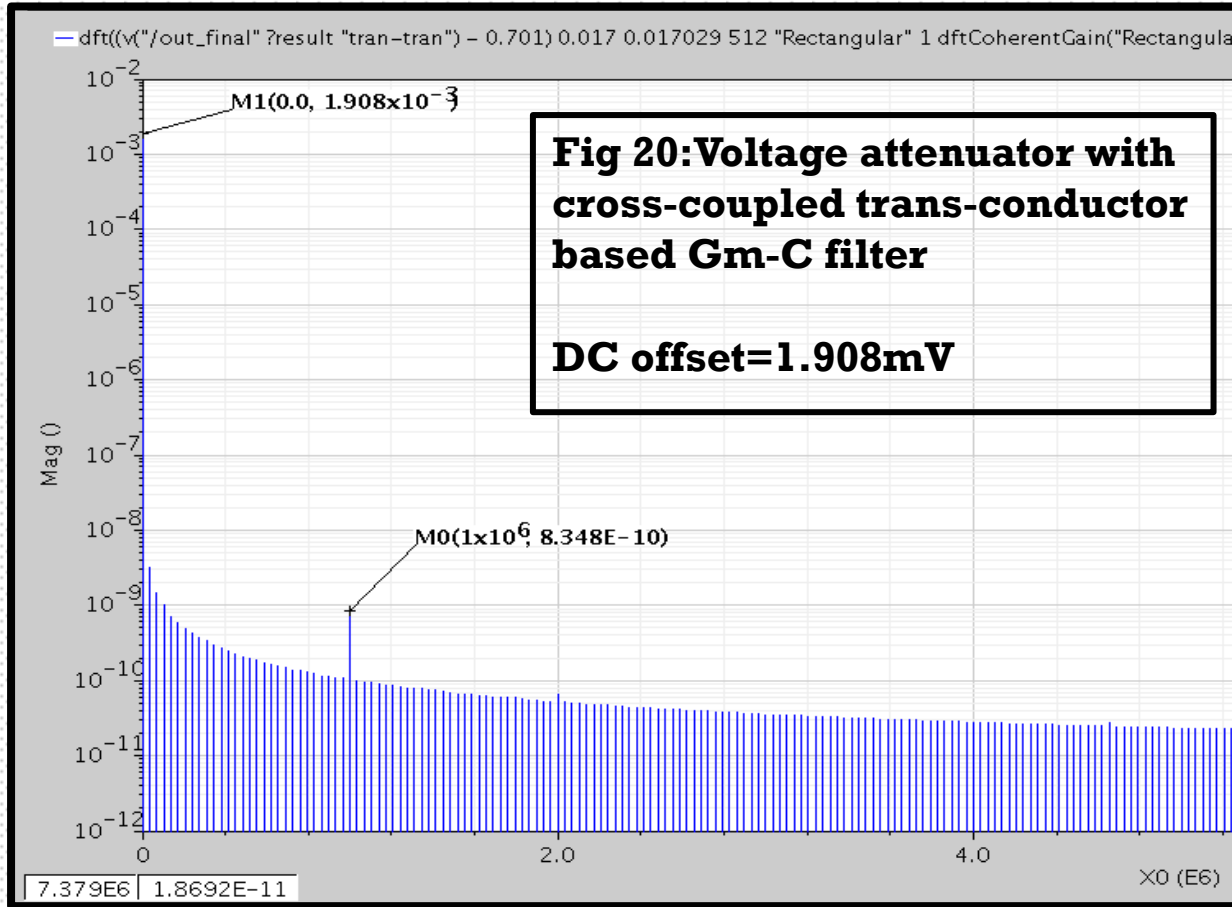

Coherent sampling: $f_{in}=1\text{MHz}$, $N_{WINDOW}=29$, $N_{RECORD}=512$: irreducible. DC Offset is reduced in EMI resisting filter.

Comparison III (1MHz)

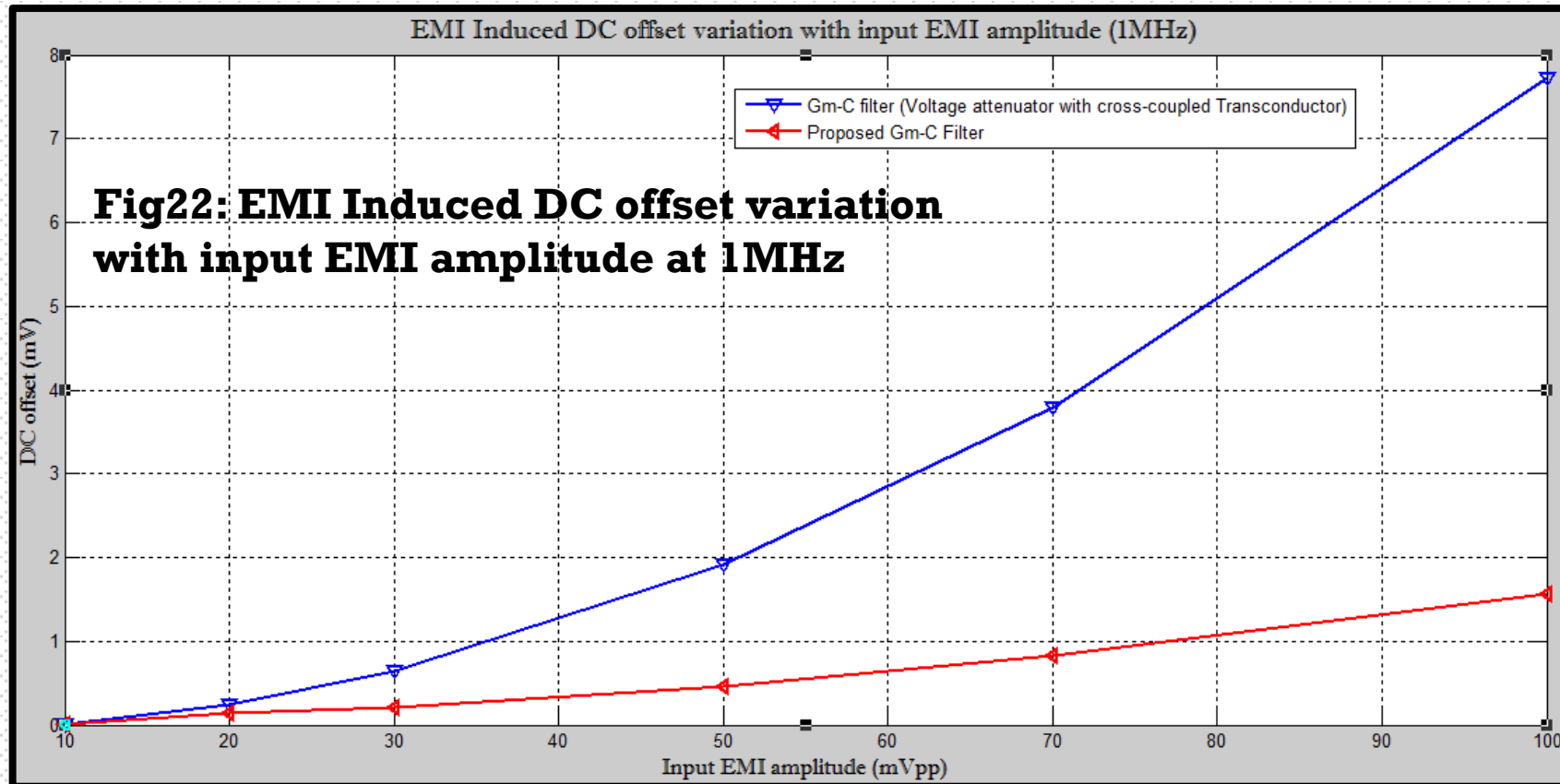

- For non-linearity of the filter at high frequency, DC offset is high. Let, $v_{in} = A \sin(\omega t)$. ie. $v_{in}^2 = \frac{A^2}{2} (1 - \cos(\omega t))$. This DC Offset is high when amplitude is high as seen in figure.
- But, by making $H_{cm}(\infty) = 0$, we are reducing non-linearity of the filter at high frequency.
- This is why at $f \gg GBW$ ($f = 1\text{MHz}$ here), this proposed filter is much immune to Electromagnetic Interference. (CM interference precisely)

With input amplitude, EMI induced DC offset increases. Rate of increment is less in proposed Filter.

Conclusion

▪ **Advantage:**

- For out-of band EMI frequencies, when parasitic capacitances come in picture, **EMI induced DC offset** becomes a challenging issue. Hence, This approach for EMI resisting highly linear sub-kilohertz G_m -C filter is noble in this field.

▪ **Disadvantage:**

- Added power dissipation
- Transistor area increment

THANK YOU

Source buffering

- We want to make $H_{cm}=0$ & accordingly we'll choose C_1
- KCL at node C(10),E(11),D(12):

$$(sC_{gs} + g_{m1})(v_1 + v_E - 2v_A - 2v_{bs1}) = sC_{T1}v_A + s(C_{bs1} + C_{T1})v_{bs1} \quad .(10)$$

$$(2v_E - v_D - v_C)(sC_{gs} + g_{m1}) + sC_{T2}v_E = 0 \quad .(11)$$

$$(v_E - v_B - v_{bs2})(sC_{gs} + g_{m1}) = s \frac{C_{bs2} + C_{T3}}{2} v_{bs2} + s \frac{C_{T3}}{2} v_B \quad .(12)$$

Solving (11) & (12) to omit v_E :

$$\left[\left[g_m + s \left\{ C_{gs} + \frac{C_{sb2} + C_{T3}}{2} \right\} \right] \left[2g_m + s(2C_{gs2} + C_{T2}) \right] - (g_m + sC_{gs})^2 \right] * (v_{bs2} + v_B) = (v_A + v_{bs1})(g_m + sC_{gs})^2 \quad (13)$$

Put v_E value from(12) in (10):

$$(sC_{gs} + g_{m1})v_1 + v_{bs2} \left[g_m + s \left\{ C_{gs} + \frac{C_{sb2} + C_{T3}}{2} \right\} \right] + v_B \left[g_m + s \left\{ C_{gs} + \frac{C_{T3}}{2} \right\} \right] = v_A \left[2g_m + s(2C_{gs} + C_{T1}) \right] + v_{bs1} \left[2g_m + s(2C_{gs} + C_{T1} + C_{sb1}) \right] \quad (14)$$

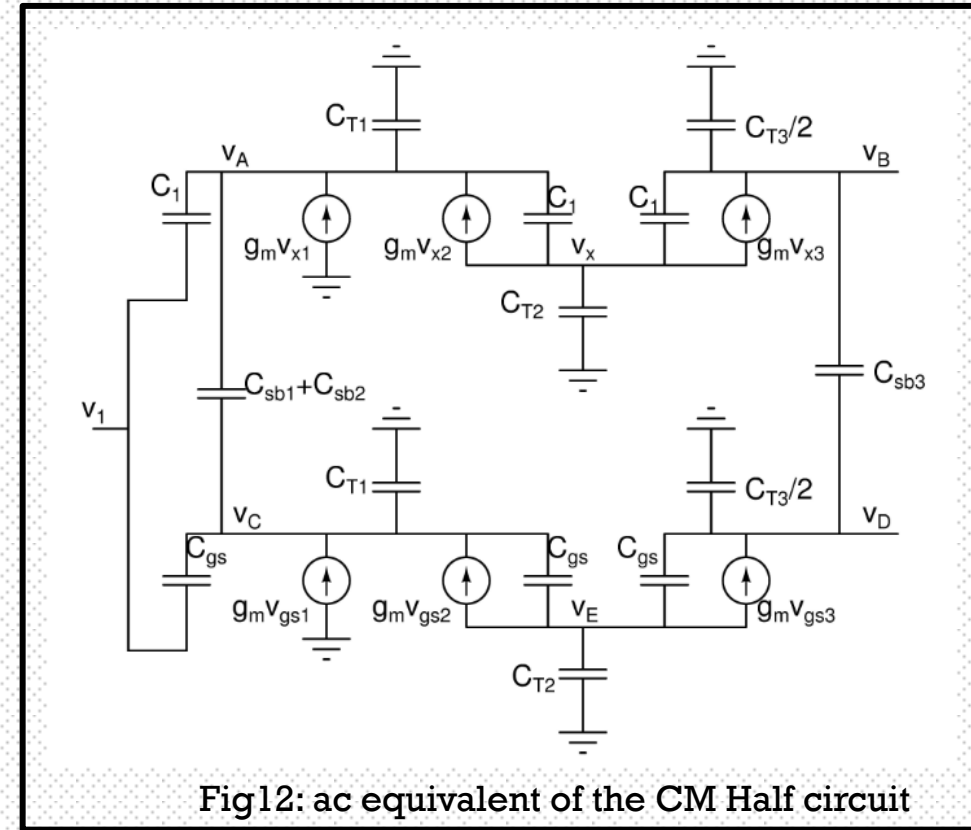


Fig12: ac equivalent of the CM Half circuit

Now, KCL at A(15), B(16), X(17):

$$(sC_1 + g_m)(v_1 + v_x) + (2g_{mb} + sC_{bs1})v_{bs1} = [2g_m + s(2C_1 + C_{T1})]v_A \quad \dots\dots\dots (15)$$

$$(sC_1 + g_m)v_x + \left(g_{mb1} + \frac{sC_{sb2}}{2}\right)v_{sb2} = \left(g_m + s\left(C_1 + \frac{C_{T3}}{2}\right)\right)v_B \quad \dots\dots\dots (16)$$

$$[2g_m + s(2C_1 + C_{T2})]v_x + g_{mb}(v_{bs1} + v_{bs2}) = (v_A + v_B)(g_m + sC_1) \quad \dots\dots\dots (17)$$

For minimizing, we assume:

$$M(v_{bs2} + v_B) = N(v_A + v_{bs1}) \quad \dots\dots\dots (13.a)$$

$$Pv_1 + Qv_{bs2} + Rv_B = Sv_A + Tv_{bs1} \quad \dots\dots\dots (14.a)$$

$$A(v_1 + v_x) + Bv_{bs1} = Cv_A \quad \dots\dots\dots (15.a)$$

$$Dv_x + Ev_{bs2} = Fv_B \quad \dots\dots\dots (16.a)$$

$$Gv_x + H(v_{bs1} + v_{bs2}) = I(v_A + v_B) \quad \dots\dots\dots (17.a)$$

Solving (13.a) & (14.a):

$$v_{bs2} = X_2v_1 + Y_2v_B + Z_2v_A \quad \text{where, } X_2 = \frac{NP}{(TM-NQ)}, Y_2 = \frac{-(S-T)}{(TM-NQ)}, Z_2 = \frac{-(TM-NR)}{(TM-NQ)} \quad \dots\dots\dots (18)$$

$$v_{bs1} = X_1v_1 + Y_1v_B + Z_1v_A \quad \text{where, } X_1 = \frac{MP}{(TM-NQ)}, Y_1 = \frac{M(R-Q)}{(TM-NQ)}, Z_1 = -\left[1 + \frac{M(S-T)}{(TM-NQ)}\right] \quad \dots\dots\dots (19)$$

$$M = \left[\left[g_m + s \left\{ C_{gs} + \frac{C_{sb2} + C_{T3}}{2} \right\} \right] [2g_m + s(2C_{gs2} + C_{T2})] - (g_m + sC_{gs})^2 \right],$$

$$N = (g_m + sC_{gs})^2$$

$$P = (sC_{gs} + g_{m1}), Q = \left[g_m + s \left\{ C_{gs} + \frac{C_{sb2} + C_{T3}}{2} \right\} \right], R = \left[g_m + s \left\{ C_{gs} + \frac{C_{T3}}{2} \right\} \right]$$

$$S = [2g_m + s(2C_{gs} + C_{T1})], T = [2g_m + s(2C_{gs} + C_{T1} + C_{sb1})],$$

$$A = (sC_1 + g_m), B = (2g_{mb} + sC_{bs1})$$

$$C = [2g_m + s(2C_1 + C_{T1})], D = (sC_1 + g_m), E = \left(g_{mb1} + \frac{sC_{sb2}}{2} \right),$$

$$F = \left(g_m + s \left(C_1 + \frac{C_{T3}}{2} \right) \right)$$

$$G = [2g_m + s(2C_1 + C_{T2})], H = g_{mb}, I = (g_m + sC_1)$$

At high frequency ($s \rightarrow \infty$), we find the following:

$$\begin{aligned}
 \blacksquare X_2 &= \frac{NP}{(TM-NQ)} = \frac{C_{gs}^3}{(2C_{gs}+C_{T1}+C_{sb1}) \left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right] - C_{gs}^2 \left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right)} \\
 \blacksquare Y_2 &= \frac{-N(S-T)}{(TM-NQ)} = \frac{C_{sb1} * C_{gs}^2}{(2C_{gs}+C_{T1}+C_{sb1}) \left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right] - C_{gs}^2 \left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right)} \\
 \blacksquare Z_2 &= \frac{-(TM-NR)}{(TM-NQ)} = \frac{C_{gs}^2 \left(C_{gs} + \frac{C_{T3}}{2} \right) - (2C_{gs}+C_{T1}+C_{sb1}) \left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right]}{(2C_{gs}+C_{T1}+C_{sb1}) \left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right] - C_{gs}^2 \left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right)} \\
 \blacksquare X_1 &= \frac{MP}{TM-NQ} = \frac{\left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right] C_{gs}}{(2C_{gs}+C_{T1}+C_{sb1}) \left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right] - C_{gs}^2 \left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right)} \\
 \blacksquare Y_1 &= \frac{M(R-Q)}{TM-NQ} = \frac{- \left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right] * \frac{C_{T3}}{2}}{(2C_{gs}+C_{T1}+C_{sb1}) \left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right] - C_{gs}^2 \left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right)} \\
 \blacksquare Z_1 &= \frac{M(S-T)}{TM-NQ} = \frac{\left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right] * C_{sb1}}{(2C_{gs}+C_{T1}+C_{sb1}) \left[\left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right) (2C_{gs}+C_{T2}) - C_{gs}^2 \right] - C_{gs}^2 \left(C_{gs} + \frac{C_{sb2}+C_{T3}}{2} \right)} - 1
 \end{aligned}$$

All terms are independent of C_1

Put equation(19) in (15.a): $v_1(A + BX_1) + BY_1v_B + Av_X = (C - BZ_1)v_A$

Put equation(18) in (16.a): $Dv_X + EX_2v_1 + EZ_2v_A = (F - EY_2)v_B$

▪ Put value of v_A from first equation in second equation: $\alpha_1v_B = \beta_1v_X + \gamma_1v_1$ (20)

where, $\alpha_1 = [(F - EY_2)(C - BZ_1) - EZ_2BY_1]$, $\beta_1 = (D(C - BZ_1) + EZ_2A)$, $\gamma_1 = \{EX_2(C - BZ_1) + EZ_2(A + BX_1)\}$

From (18) & (19), put values v_{bs1} & v_{bs2} in (17.a): $\alpha_2v_B = \beta_2v_X + \gamma_2v_1$ (21)

where, $\alpha_2 = \left[I + \frac{IBY_1}{C - BZ_1} - H(Y_1 + Y_2) - \frac{H(Z_1 + Z_2)BY_1}{C - BZ_1} \right]$, $\beta_2 = \left[G + \frac{AH(Z_1 + Z_2)}{C - BZ_1} - \frac{AI}{C - BZ_1} \right]$, $\gamma_2 = \left[H(X_1 + X_2) + \frac{H(Z_1 + Z_2)(A + BX_1)}{C - BZ_1} - \frac{(A + BX_1)I}{C - BZ_1} \right]$

From (20) & (21): $\left(\frac{\alpha_2}{\alpha_1} \right) (\beta_1v_X + \gamma_1v_1) = \beta_2v_X + \gamma_2v_1$

$$H_{cm} = \frac{\alpha_2\gamma_1 - \alpha_1\gamma_2}{\alpha_1\beta_2 - \alpha_2\beta_1}$$

For $H_{cm}=0$, we find: $\alpha_2\gamma_1 - \alpha_1\gamma_2=0$

$$\Rightarrow [I(C - BZ_1) + IBY_1 - H(Y_1 + Y_2)(C - BZ_1) - H(Z_1 + Z_2)BY_1] * [EX_2(C - BZ_1) + EZ_2(A + BX_1)] = [(F - EY_2)(C - BZ_1) - EZ_2BY_1] * [H(X_1 + X_2)(C - BZ_1) + H(Z_1 + Z_2)(A + BX_1) - (A + BX_1)I]$$

1st term: $[I(C - BZ_1) + IBY_1 - H(Y_1 + Y_2)(C - BZ_1) - H(Z_1 + Z_2)BY_1]$ divide numerator and denominator by [order of max(num, den) = 2], we'll find the term is simplified to: $[(C_1)((2C_1 + C_{T1}) - C_{bs1}Z_1) + C_1C_{bs1}Y_1]$

2nd term: $[EX_2(C - BZ_1) + EZ_2(A + BX_1)]$ divide numerator and denominator by s^2 gives:

$$\left[\frac{C_{sb2}}{2} X_2 ((2C_1 + C_{T1}) - C_{bs1}Z_1) + \frac{C_{sb2}}{2} Z_2 (C_1 + C_{bs1}X_1) \right]$$

3rd term: $[(F - EY_2)(C - BZ_1) - EZ_2BY_1]$ is simplified by dividing num & den by s^2 and put $s \rightarrow \infty$

$$: \left[\left(\left(C_1 + \frac{C_{T3}}{2} \right) - \left(\frac{C_{sb2}}{2} * Y_2 \right) \right) \left((2C_1 + C_{T1}) - (C_{bs1}Z_1) \right) \right] - \left(\frac{C_{sb2}}{2} \right) (C_{bs1})Z_2Y_1$$

4th term: $[H(X_1 + X_2)(C - BZ_1) + H(Z_1 + Z_2)(A + BX_1) - (A + BX_1)I]$ is simplified by dividing num & den by s^2 and put $s \rightarrow \infty$

$$: [-(C_1 + C_{bs1}X_1)(C_1)]$$

$$C_1^2(4X_2 + 2Z_2 - 2) + C_1 \left\{ \left((2C_{T1}X_2 - 2C_{bs1}Z_1X_2 + 2C_{bs1}X_1Z_2) + (C_{T1} - C_{bs1}Z_1 + C_{bs1}Y_1)(2X_2 + Z_2) \right) - (C_{T1} - C_{bs1}Z_1 - C_{bs1}Z_2Y_1 + 2C_{bs1}X_1) \right\} + C_{T1} - C_{bs1}Z_1 + C_{bs1}Y_1$$

$$C_{T1}X_2 - C_{bs1}Z_1X_2 + C_{bs1}X_1Z_2 - C_{bs1}X_1(C_{T1} - C_{bs1}Z_1 - C_{bs1}Z_2Y_1) = 0$$

This follows the form: $aC_1^2 + bC_1 + c = 0$

From DC simulation: $C_{gs}=7.05\text{fF}$, $C_{sb1}=17.14\text{fF}$, $C_{sb2}=17.02\text{fF}$, $C_{T1}=10.46\text{fF}$, $C_{T2}=10.47\text{fF}$, $C_{T3}=10.47\text{fF}$, $g_m=42.4\text{nA/V}$

Hence, putting the values in all equations, $a = -4.03$, $b = -2.53 * 10^{-15}$ & $c = 4.12 * 10^{-26}$

$$C_1 = - \frac{2.53 * 10^{-15} - \sqrt{(-2.53 * 10^{-15})^2 + 4 * 4.03 * 4.12 * 10^{-26}}}{2 * 4.03} = 100.79 \text{ fF}$$

▪ $C_1 = C_{gs} + C_{ext}$, Here, $C_{gs}=7.05\text{fF}$, $\Rightarrow C_{ext} = 93.74\text{fF}$

▪ We consider,

$$C_{ext} = 95\text{fF}$$

RETURN

Infinite frequency for 1st term:

1st term:

$$[I(C - BZ_1) + IBY_1 - H(Y_1 + Y_2)(C - BZ_1) - H(Z_1 + Z_2)BY_1]$$

$$= (g_m + sC_1)[2g_m + s(2C_1 + C_{T1}) - (2g_{mb} + sC_{bs1})Z_1 + (2g_{mb} + sC_{bs1})Y_1] \\ - [g_{mb}(Y_1 + Y_2)(2g_m + s(2C_1 + C_{T1}))] - [g_{mb}(Z_1 + Z_2)(2g_{mb} + sC_{bs1})Y_1]$$

The critical frequencies above which (at least 10 times) we are considering the approximation of $s \rightarrow \infty$ is valid:

$$(i) \frac{g_m}{C_1} = \frac{42.2n}{100.79f} = 67.48 \text{ KHz}$$

$$(ii) \frac{2g_m}{2C_1 + C_{T1}} = 64.27 \text{ KHz}$$

$$(iii) \frac{2g_{mb}}{C_{bs1}} = 74.9 \text{ KHz}$$

Infinite frequency for 2nd term:

2nd term:

$$[EX_2(C - BZ_1) + EZ_2(A + BX_1)]$$

$$= \left(g_{mb1} + \frac{sC_{bs2}}{2} \right) [X_2 \{ 2g_m + s(2C_1 + C_{T1}) - (2g_{mb} + sC_{bs1})Z_1 \} + Z_2 \{ (g_m + sC_1) + (2g_{mb} + sC_{bs1})X_1 \}]$$

The critical frequencies above which (at least 10 times) we are considering the approximation of $s \rightarrow \infty$ is valid:

$$(i) \frac{2g_m X_2 - 2g_{mb} Z_1}{(2C_1 + C_{T1})X_2 - C_{bs1}Z_1} = 71.33 \text{ KHz}$$

$$(ii) \frac{(g_m + 2g_{mb}X_1)}{C_1 + C_{bs1}X_1} = 67.16 \text{ KHz}$$

Infinite frequency for 3rd term:

3rd term:

$$[(F - EY_2)(C - BZ_1) - EZ_2BY_1]$$

$$= \left[\left\{ (g_m + g_{mb}Y_2) + s \left(C_1 + \frac{C_{T3}}{2} - \frac{C_{bs2}}{2} Y_2 \right) \right\} \{ (2g_m - 2g_{mb}) + s(2C_1 + C_{T1} - C_{bs1}Z_1) \} - Z_2Y_1(g_{mb} + \frac{sC_{bs2}}{2})(2g_{mb} + sC_{bs1}) \right]$$

The critical frequencies above which (at least 10 times) we are considering the approximation of $s \rightarrow \infty$ is valid:

$$(i) \frac{g_m + g_{mb}Y_2}{C_1 + \frac{C_{T3}}{2} - \frac{C_{bs2}}{2} Y_2} = 64.18 \text{ KHz}$$

$$(ii) \frac{2(g_m - g_{mb})}{2C_1 + C_{T1} - C_{bs1}Z_1} = 54.6 \text{ KHz}$$

Infinite frequency for 4th term:

4th term:

$$[H(X_1 + X_2)(C - BZ_1) + H(Z_1 + Z_2)(A + BX_1) - (A + BX_1)I]$$

$$= g_{mb}(X_1 + X_2)[2g_m + s(2C_1 + C_{T1}) - (2g_{mb} + sC_{bs1})Z_1] + g_{mb}(Z_1 + Z_2)[g_m + sC_1 + (2g_{mb} + sC_{bs1})X_1] - (g_m + sC_1)[g_m + sC_1 + (2g_{mb} + sC_{bs1})X_1]$$

The critical frequencies above which (at least 10 times) we are considering the approximation of $s \rightarrow \infty$ is valid:

$$(i) \frac{g_m + 2g_{mb}X_1}{C_1 + C_{bs1}X_1} = 67.16 \text{ KHz}$$

$$(ii) \frac{2(g_m - g_{mb}Z_1)}{2C_1 + C_{T1} - C_{bs1}Z_1} = 64.37 \text{ KHz}$$

- $M = \left[\left[g_m + s \left\{ C_{gs} + \frac{C_{sb2} + C_{T3}}{2} \right\} \right] \left[2g_m + s(2C_{gs2} + C_{T2}) \right] - (g_m + sC_{gs})^2 \right],$
- $N = (g_m + sC_{gs})^2, P = (sC_{gs} + g_{m1}),$
- $Q = \left[g_m + s \left\{ C_{gs} + \frac{C_{sb2} + C_{T3}}{2} \right\} \right], R = \left[g_m + s \left\{ C_{gs} + \frac{C_{T3}}{2} \right\} \right]$
- $S = [2g_m + s(2C_{gs} + C_{T1})], T = [2g_m + s(2C_{gs} + C_{T1} + C_{sb1})],$
- $A = (sC_1 + g_m), B = (2g_{mb} + sC_{bs1})$
- $C = [2g_m + s(2C_1 + C_{T1})], D = (sC_1 + g_m),$
- $E = \left(g_{mb1} + \frac{sC_{sb2}}{2} \right), F = \left(g_m + s \left(C_1 + \frac{C_{T3}}{2} \right) \right)$
- $G = [2g_m + s(2C_1 + C_{T2})], H = g_{mb}, I = (g_m + sC_1)$

$$X_2 = \frac{NP}{(TM-NQ)}, Y_2 = \frac{-N(S-T)}{(TM-NQ)}, Z_2 = \frac{-(TM-NR)}{(TM-NQ)}$$

$$X_1 = \frac{MP}{(TM-NQ)}, Y_1 = \frac{M(R-Q)}{(TM-NQ)}, Z_1 = - \left[1 + \frac{M(S-T)}{(TM-NQ)} \right]$$

For $X_{1,2}, Y_{1,2}, Z_{1,2}$, the frequencies above which we can consider $\rightarrow \infty$, are given as following:

- M,Q: (i) $\frac{g_m}{C_{gs} + \frac{C_{bs2} + C_{T3}}{2}} = 324.5KHz$
- (ii) $\frac{2g_m}{2C_{gs} + C_{T2}} = 549.3KHz$
- N,P: $\frac{g_m}{C_{gs}} = 957.2KHz$
- R: $\frac{2g_m}{2C_{gs} + C_{T3}} = 549.3KHz$
- T: $\frac{g_m}{C_{gs} + \frac{C_{T1} + C_{bs1}}{2}} < 549KHz$
- S: $\frac{2g_m}{2C_{gs} + C_{T1}} = 549.3KHz$

Conclusion:

All the terms are considered individually to find the frequency above which we can consider our assumption is valid. Ie H_{cm} is zero.

From all the terms above, we find highest frequency = 957.2 KHz. Hence, above almost 10 times, of it ie 9-10 MHz, we can Assume frequency to be infinite. All our assumptions are valid above this frequency. This is valid as 10MHz is considered typically in EMI frequency range.

Comparison (100mVpp)


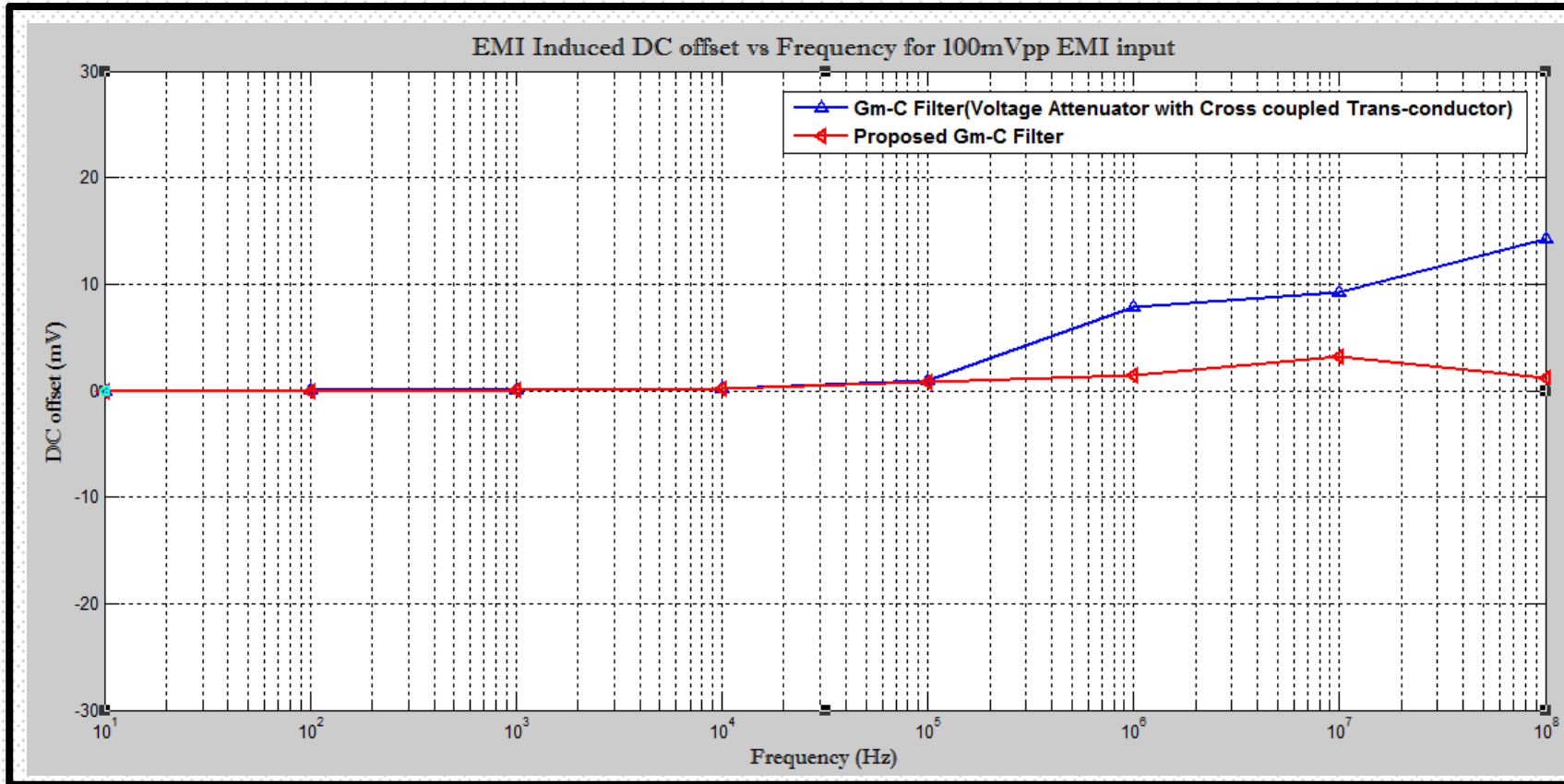


Fig19: EMI induced DC offset variation with frequency for 100mVpp input signal

▪ Here, we see the EMI Induced DC offset is reduced significantly for this proposed G_m -C filter compared to Uncompesated G_m -C filter From the frequency near 10MHz, which is considered to Be the minimum value of Infinty while calculating CMTF $H_{cm}(\infty)=0$.

- In frequency range [10Hz-100MHz], Maximum EMI induced offset (Magnitude): (i) Voltage attenuator with cross-coupled transconductor based G_m -C filter:: **1.996%** (ii) Proposed G_m -C filter:: **0.459%**

DC offset reduction at high frequency

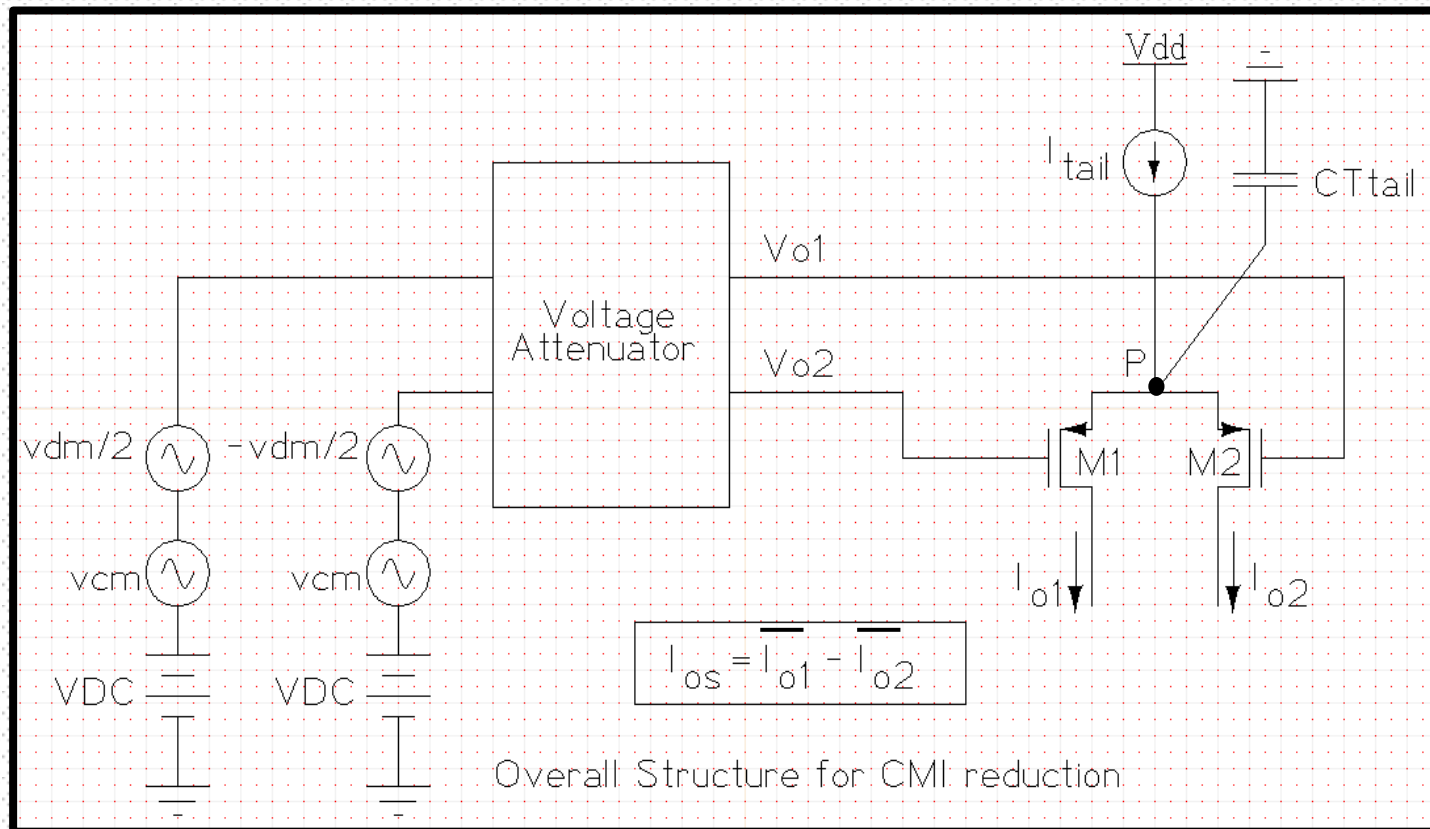

$$v_{o1} = H_{cm} v_{cm} + H_{dm} \frac{v_{dm}}{2} \quad \&$$

$$v_{o2} = H_{cm} v_{cm} - H_{dm} \frac{v_{dm}}{2}$$

$$\text{And, } V_{o1} = v_{o1} + V_{DC} \quad \& \quad V_{o2} = v_{o2} + V_{DC}$$

- CASE1:** If Common mode interference comes at attenuator output, then from equations above: $|v_{o1}| \neq |v_{o2}|$
 Unequal capacitive division occurs across gate-source of M1 & M2 due to $C_{T,tail}$ and as a result, $|v_{gs,M1}| \neq |v_{gs,M2}|$ ie finite offset current I_{OS} at output.
- CASE2:** Instead, if we make $H_{cm} = 0$ somehow, ie no CM Interference at attenuator output, $|v_{o1}| = |v_{o2}|$

In this case, P acts as virtual ground as second stage doesn't see any common mode input. ie $I_{os} = 0$. This is why we need to minimize H_{cm} of the first stage to reduce DC offset at output.