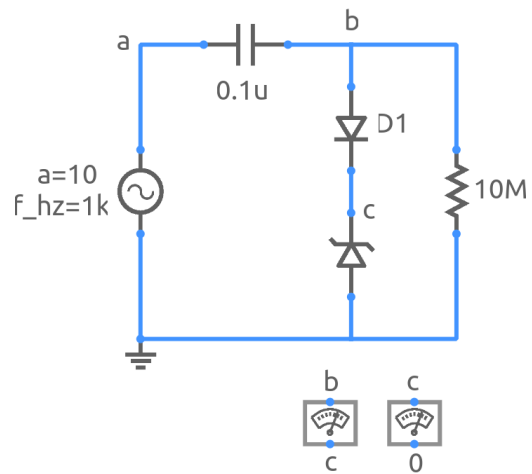


ee101\_diode\_circuit\_11a.sqproj



Observe the effect of R on the output voltage. Try 10k and 10M.