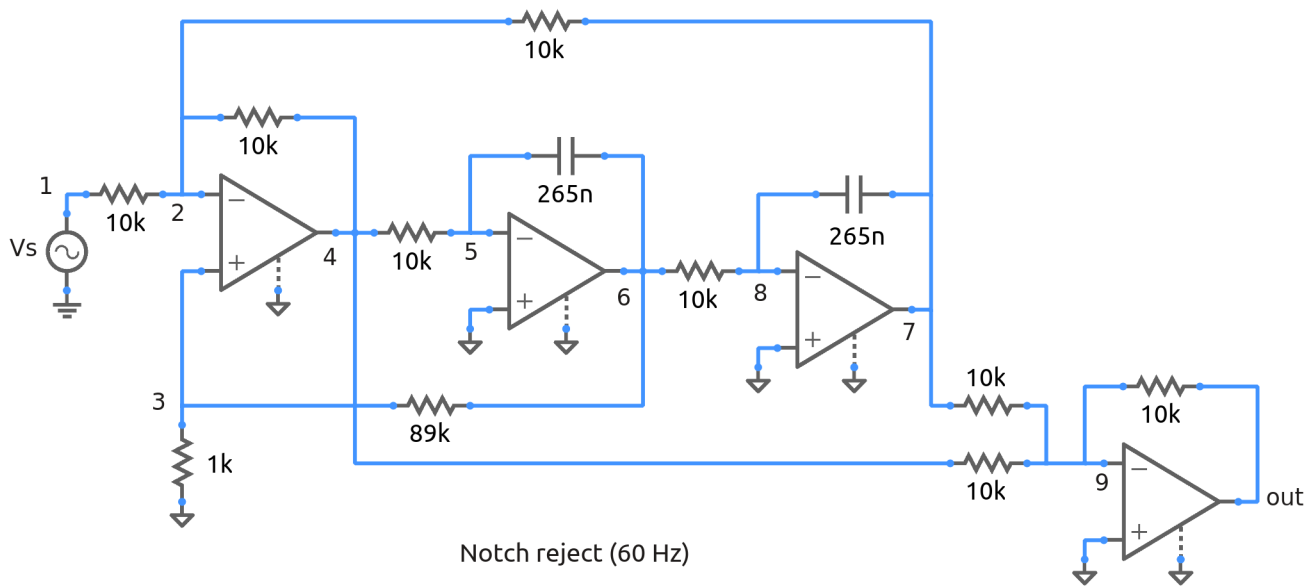


ee101\_op\_filter\_9.sqproj



Ref: J. M. Fiore: Op Amps and linear integrated circuits

## Exercise Set

1. Plot the magnitude frequency response (log-log plot), and comment on the type of this filter circuit.