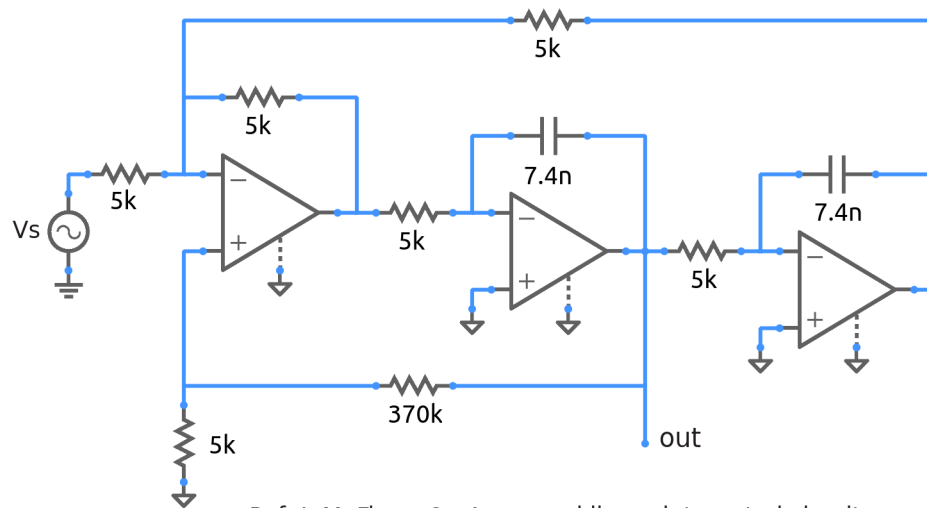


ee101\_op\_filter\_8.sqproj



Ref: J. M. Fiore: Op Amps and linear integrated circuits

## Exercise Set

1. Plot the magnitude frequency response (log-log plot), and comment on the type of this filter circuit.

## Reference

1. S. Franco, *Design with Operation Amplifiers and Analog Integrated Circuits*, McGraw-Hill, 1998.