

EE101: Digital circuits (Part 1)




M. B. Patil

mbpatil@ee.iitb.ac.in
www.ee.iitb.ac.in/~sequel

Department of Electrical Engineering
Indian Institute of Technology Bombay

Digital circuits

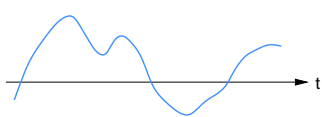


analog signal



digital signal

Digital circuits

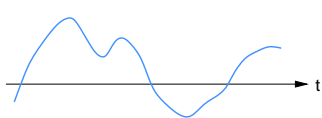


analog signal



digital signal

- * For an analog signal $x(t)$, the actual value (a real number) at a given time is important.

Digital circuits

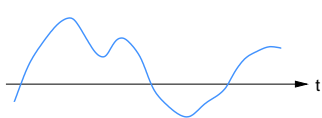


analog signal



digital signal

- * For an analog signal $x(t)$, the actual value (a real number) at a given time is important.
- * A digital signal, on the other hand, is “binary” in nature, i.e., it takes on only two values: low (0) or high (1).

Digital circuits

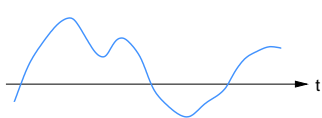


analog signal



digital signal

- * For an analog signal $x(t)$, the actual value (a real number) at a given time is important.
- * A digital signal, on the other hand, is “binary” in nature, i.e., it takes on only two values: low (0) or high (1).
- * Although we have shown 0 and 1 as constant levels, in reality, that is not required. Any value in the low (high) band will be interpreted as 0 (1) by digital circuits.

Digital circuits

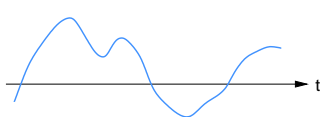



analog signal




digital signal

- * For an analog signal $x(t)$, the actual value (a real number) at a given time is important.
- * A digital signal, on the other hand, is “binary” in nature, i.e., it takes on only two values: low (0) or high (1).
- * Although we have shown 0 and 1 as constant levels, in reality, that is not required. Any value in the low (high) band will be interpreted as 0 (1) by digital circuits.
- * The definition of low and high bands depends on the technology used, such as TTL (Transistor-Transistor Logic), CMOS (Complementary MOS), ECL (Emitter-Coupled Logic), etc.

A simple digital circuit

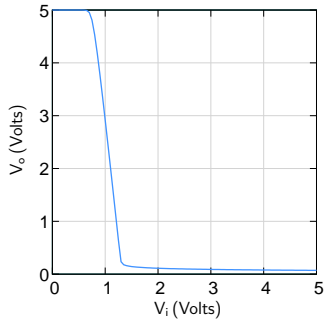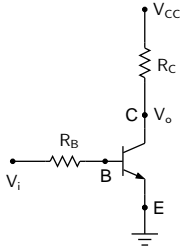


A simple digital circuit

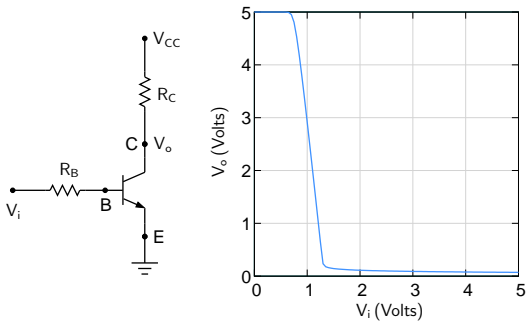


- * If V_i is low ("0"), V_o is high ("1").
- If V_i is high ("1"), V_o is low ("0").

A simple digital circuit

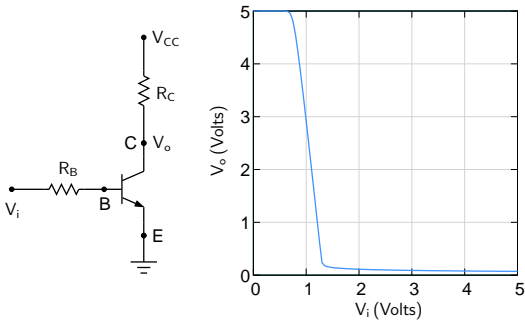


- * If V_i is low ("0"), V_o is high ("1").
If V_i is high ("1"), V_o is low ("0").
- * The circuit is called an "inverter" because it inverts the logic level of the input. If the input is 0, it makes the output 1, and vice versa.

A simple digital circuit

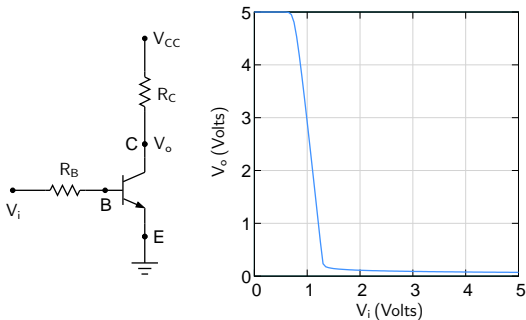


- * If V_i is low ("0"), V_o is high ("1").
If V_i is high ("1"), V_o is low ("0").
- * The circuit is called an "inverter" because it inverts the logic level of the input. If the input is 0, it makes the output 1, and vice versa.
- * Digital circuits are made using a variety of devices. The simple BJT inverter we have shown should only be considered as an illustrative circuit.

A simple digital circuit

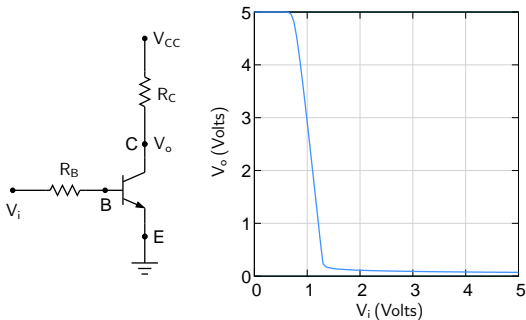


- * If V_i is low ("0"), V_o is high ("1").
If V_i is high ("1"), V_o is low ("0").
- * The circuit is called an "inverter" because it inverts the logic level of the input. If the input is 0, it makes the output 1, and vice versa.
- * Digital circuits are made using a variety of devices. The simple BJT inverter we have shown should only be considered as an illustrative circuit.
- * Most of the VLSI circuits today employ the MOS technology because of the high packing density and low power consumption it offers.

Digital circuits

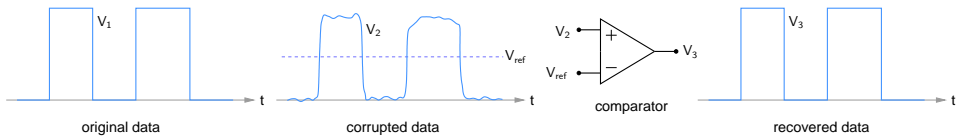


Digital circuits

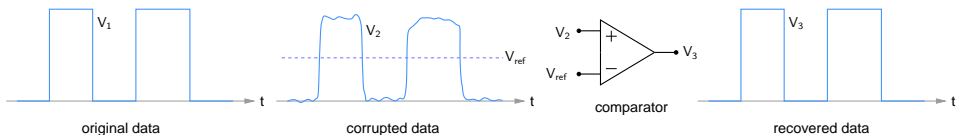


- * A major advantage of digital systems is that, even if the original data gets distorted (e.g., in transmitting through optical fibre or storing on a CD) due to noise, attenuation, etc., it can be retrieved easily.

Digital circuits

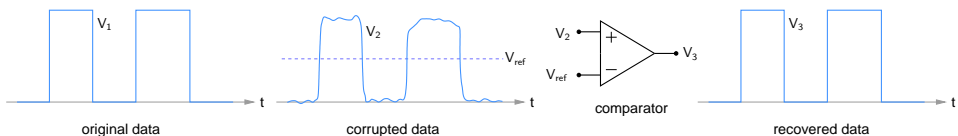


- * A major advantage of digital systems is that, even if the original data gets distorted (e.g., in transmitting through optical fibre or storing on a CD) due to noise, attenuation, etc., it can be retrieved easily.
- * There are several other benefits of using digital representation:

Digital circuits

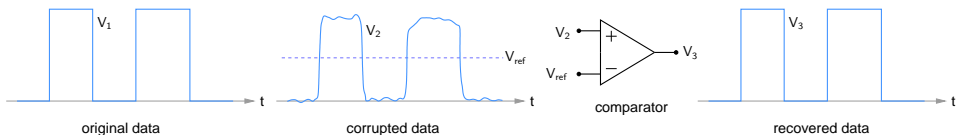


- * A major advantage of digital systems is that, even if the original data gets distorted (e.g., in transmitting through optical fibre or storing on a CD) due to noise, attenuation, etc., it can be retrieved easily.
- * There are several other benefits of using digital representation:
 - can use computers to process the data.

Digital circuits

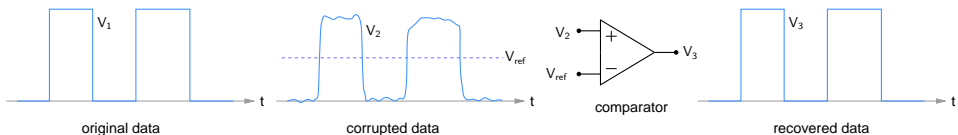

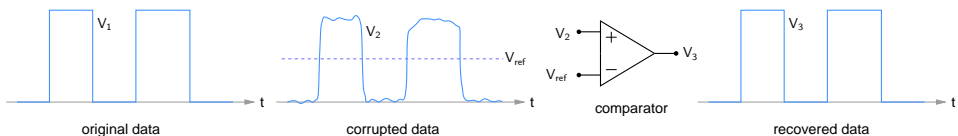- * A major advantage of digital systems is that, even if the original data gets distorted (e.g., in transmitting through optical fibre or storing on a CD) due to noise, attenuation, etc., it can be retrieved easily.
- * There are several other benefits of using digital representation:
 - can use computers to process the data.
 - can store in a variety of storage media.



- * A major advantage of digital systems is that, even if the original data gets distorted (e.g., in transmitting through optical fibre or storing on a CD) due to noise, attenuation, etc., it can be retrieved easily.
- * There are several other benefits of using digital representation:
 - can use computers to process the data.
 - can store in a variety of storage media.
 - can *program* the functionality. For example, the behaviour of a digital filter can be changed simply by changing its coefficients.

Operation

NOT

AND

OR

Gate

Truth table

Notation


Operation

NOT

AND

OR

Gate

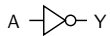

Truth table

A	Y
0	1
1	0

Notation

$$Y = \overline{A}$$

Logical operations


Operation

NOT

AND

OR

Gate

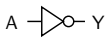

Truth table

A	Y
0	1
1	0

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Notation

$$Y = \bar{A}$$

$$Y = A \cdot B \\ = AB$$

Logical operations


Operation

NOT

AND

OR

Gate

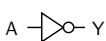

Truth table

A	Y
0	1
1	0

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Notation

$$Y = \bar{A}$$

$$Y = A \cdot B \\ = AB$$

$$Y = A + B$$

Operation

NAND

NOR

XOR

Gate

Truth table

Notation


Operation

NAND

NOR

XOR

Gate

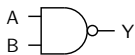

Truth table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Notation

$$Y = \overline{A \cdot B}$$
$$= \overline{AB}$$

Logical operations



Operation

NAND

NOR

XOR

Gate

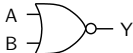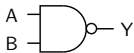

Truth table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Notation

$$Y = \overline{A \cdot B}$$
$$= \overline{AB}$$

$$Y = \overline{A + B}$$



Operation

NAND

NOR

XOR

Gate

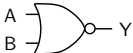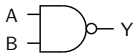

Truth table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Notation

$$Y = \overline{A \cdot B}$$

$$= \overline{AB}$$

$$Y = \overline{A + B}$$

$$Y = A \oplus B$$

$$= A\overline{B} + \overline{A}B$$

- * The AND operation is *commutative*.
→ $A \cdot B = B \cdot A$.

- * The AND operation is *commutative*.
 $\rightarrow A \cdot B = B \cdot A.$
- * The AND operation is *associative*.
 $\rightarrow (A \cdot B) \cdot C = A \cdot (B \cdot C).$

- * The AND operation is *commutative*.
→ $A \cdot B = B \cdot A$.
- * The AND operation is *associative*.
→ $(A \cdot B) \cdot C = A \cdot (B \cdot C)$.
- * The OR operation is *commutative*.
→ $A + B = B + A$.

- * The AND operation is *commutative*.
 $\rightarrow A \cdot B = B \cdot A.$
- * The AND operation is *associative*.
 $\rightarrow (A \cdot B) \cdot C = A \cdot (B \cdot C).$
- * The OR operation is *commutative*.
 $\rightarrow A + B = B + A.$
- * The OR operation is *associative*.
 $\rightarrow (A + B) + C = A + (B + C).$

Boolean algebra (George Boole, 1815-1864)

* Theorem: $\overline{\overline{A}} = A$.

Boolean algebra (George Boole, 1815-1864)

- * Theorem: $\overline{\overline{A}} = A$.

The theorem can be proved by constructing a truth table:

A	\overline{A}	$\overline{\overline{A}}$
0	1	0
1	0	1

- * Theorem: $\overline{\overline{A}} = A$.

The theorem can be proved by constructing a truth table:

A	\overline{A}	$\overline{\overline{A}}$
0	1	0
1	0	1

Therefore, for all possible values that A can take (i.e., 0 and 1), $\overline{\overline{A}}$ is the same as A .

$$\Rightarrow \overline{\overline{A}} = A.$$

Boolean algebra (George Boole, 1815-1864)

- * Theorem: $\overline{\overline{A}} = A$.

The theorem can be proved by constructing a truth table:

A	\overline{A}	$\overline{\overline{A}}$
0	1	0
1	0	1

Therefore, for all possible values that A can take (i.e., 0 and 1), $\overline{\overline{A}}$ is the same as A .

$$\Rightarrow \overline{\overline{A}} = A.$$

- * Similarly, the following theorems can be proved:

$$A + 0 = A \quad A \cdot 1 = A$$

$$A + 1 = 1 \quad A \cdot 0 = 0$$

$$A + A = A \quad A \cdot A = A$$

$$A + \overline{A} = 1 \quad A \cdot \overline{A} = 0$$

Boolean algebra (George Boole, 1815-1864)

- * Theorem: $\overline{\overline{A}} = A$.

The theorem can be proved by constructing a truth table:

A	\overline{A}	$\overline{\overline{A}}$
0	1	0
1	0	1

Therefore, for all possible values that A can take (i.e., 0 and 1), $\overline{\overline{A}}$ is the same as A .

$$\Rightarrow \overline{\overline{A}} = A.$$

- * Similarly, the following theorems can be proved:

$$A + 0 = A \quad A \cdot 1 = A$$

$$A + 1 = 1 \quad A \cdot 0 = 0$$

$$A + A = A \quad A \cdot A = A$$

$$A + \overline{A} = 1 \quad A \cdot \overline{A} = 0$$

Note the duality: ($+ \leftrightarrow \cdot$) and ($1 \leftrightarrow 0$).

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0								
0	1								
1	0								
1	1								

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0							
0	1	1							
1	0	1							
1	1	1							

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1						
0	1	1	0						
1	0	1	0						
1	1	1	0						

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1					
0	1	1	0	1					
1	0	1	0	0					
1	1	1	0	0					

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1				
0	1	1	0	1	0				
1	0	1	0	0	1				
1	1	1	0	0	0				

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1			
0	1	1	0	1	0	0			
1	0	1	0	0	1	0			
1	1	1	0	0	0	0			

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1	0		
0	1	1	0	1	0	0	0		
1	0	1	0	0	1	0	0		
1	1	1	0	0	0	0	1		

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1	0	1	
0	1	1	0	1	0	0	0	1	
1	0	1	0	0	1	0	0	1	
1	1	1	0	0	0	0	1	0	

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	1	0	0	1	0	0	1	1
1	1	1	0	0	0	0	1	0	0

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	1	0	0	1	0	0	1	1
1	1	1	0	0	0	0	1	0	0

* Comparing the truth tables for $\overline{A + B}$ and $\overline{A} \cdot \overline{B}$, we conclude that $\overline{A + B} = \overline{A} \cdot \overline{B}$.

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	1	0	0	1	0	0	1	1
1	1	1	0	0	0	0	1	0	0

- * Comparing the truth tables for $\overline{A + B}$ and $\overline{A} \overline{B}$, we conclude that $\overline{A + B} = \overline{A} \overline{B}$.
- * Similarly, $\overline{A \cdot B} = \overline{A} + \overline{B}$.

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	1	0	0	1	0	0	1	1
1	1	1	0	0	0	0	1	0	0

- * Comparing the truth tables for $\overline{A + B}$ and $\overline{A} \overline{B}$, we conclude that $\overline{A + B} = \overline{A} \overline{B}$.
- * Similarly, $\overline{A \cdot B} = \overline{A} + \overline{B}$.
- * Similar relations hold for more than two variables, e.g.,

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	1	0	0	1	0	0	1	1
1	1	1	0	0	0	0	1	0	0

- * Comparing the truth tables for $\overline{A + B}$ and $\overline{A} \overline{B}$, we conclude that $\overline{A + B} = \overline{A} \overline{B}$.
- * Similarly, $\overline{A \cdot B} = \overline{A} + \overline{B}$.
- * Similar relations hold for more than two variables, e.g.,
$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C},$$

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	1	0	0	1	0	0	1	1
1	1	1	0	0	0	0	1	0	0

- * Comparing the truth tables for $\overline{A + B}$ and $\overline{A} \cdot \overline{B}$, we conclude that $\overline{A + B} = \overline{A} \cdot \overline{B}$.
- * Similarly, $\overline{A \cdot B} = \overline{A} + \overline{B}$.
- * Similar relations hold for more than two variables, e.g.,

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C},$$

$$\overline{A + B + C + D} = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D},$$

De Morgan's theorems

A	B	$A + B$	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	1	0	0	1	0	0	1	1
1	1	1	0	0	0	0	1	0	0

- * Comparing the truth tables for $\overline{A + B}$ and $\overline{A} \cdot \overline{B}$, we conclude that $\overline{A + B} = \overline{A} \cdot \overline{B}$.
- * Similarly, $\overline{A \cdot B} = \overline{A} + \overline{B}$.
- * Similar relations hold for more than two variables, e.g.,

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C},$$

$$\overline{A + B + C + D} = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D},$$

$$\overline{(A + B) \cdot C} = \overline{(A + B)} + \overline{C}.$$

1. $A \cdot (B + C) = AB + AC.$

Distributive laws

1. $A \cdot (B + C) = AB + AC$.

A	B	C	$B + C$	$A \cdot (B + C)$	AB	AC	$AB + AC$
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

Distributive laws

1. $A \cdot (B + C) = AB + AC$.

A	B	C	$B + C$	$A \cdot (B + C)$	AB	AC	$AB + AC$
0	0	0	0				
0	0	1	1				
0	1	0	1				
0	1	1	1				
1	0	0	0				
1	0	1	1				
1	1	0	1				
1	1	1	1				

Distributive laws

1. $A \cdot (B + C) = AB + AC$.

A	B	C	$B + C$	$A \cdot (B + C)$	AB	AC	$AB + AC$
0	0	0	0	0			
0	0	1	1	0			
0	1	0	1	0			
0	1	1	1	0			
1	0	0	0	0			
1	0	1	1	1			
1	1	0	1	1			
1	1	1	1	1			

Distributive laws

1. $A \cdot (B + C) = AB + AC$.

A	B	C	$B + C$	$A \cdot (B + C)$	AB	AC	$AB + AC$
0	0	0	0	0	0		
0	0	1	1	0	0		
0	1	0	1	0	0		
0	1	1	1	0	0		
1	0	0	0	0	0		
1	0	1	1	1	0		
1	1	0	1	1	1		
1	1	1	1	1	1		

Distributive laws

1. $A \cdot (B + C) = AB + AC$.

A	B	C	$B + C$	$A \cdot (B + C)$	AB	AC	$AB + AC$
0	0	0	0	0	0	0	
0	0	1	1	0	0	0	
0	1	0	1	0	0	0	
0	1	1	1	0	0	0	
1	0	0	0	0	0	0	
1	0	1	1	1	0	1	
1	1	0	1	1	1	0	
1	1	1	1	1	1	1	

Distributive laws

1. $A \cdot (B + C) = AB + AC$.

A	B	C	$B + C$	$A \cdot (B + C)$	AB	AC	$AB + AC$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

Distributive laws

1. $A \cdot (B + C) = AB + AC$.

A	B	C	$B + C$	$A \cdot (B + C)$	AB	AC	$AB + AC$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1



$$2. A + B \cdot C = (A + B) \cdot (A + C).$$

2. $A + B \cdot C = (A + B) \cdot (A + C)$.

A	B	C	BC	$A + BC$	$A + B$	$A + C$	$(A + B)(A + C)$
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

2. $A + B \cdot C = (A + B) \cdot (A + C)$.

A	B	C	BC	$A + BC$	$A + B$	$A + C$	$(A + B)(A + C)$
0	0	0	0				
0	0	1	0				
0	1	0	0				
0	1	1	1				
1	0	0	0				
1	0	1	0				
1	1	0	0				
1	1	1	1				

2. $A + B \cdot C = (A + B) \cdot (A + C)$.

A	B	C	BC	$A + BC$	$A + B$	$A + C$	$(A + B)(A + C)$
0	0	0	0	0			
0	0	1	0	0			
0	1	0	0	0			
0	1	1	1	1			
1	0	0	0	1			
1	0	1	0	1			
1	1	0	0	1			
1	1	1	1	1			

2. $A + B \cdot C = (A + B) \cdot (A + C)$.

A	B	C	BC	A + BC	A + B	A + C	(A + B)(A + C)
0	0	0	0	0	0		
0	0	1	0	0	0		
0	1	0	0	0	1		
0	1	1	1	1	1		
1	0	0	0	1	1		
1	0	1	0	1	1		
1	1	0	0	1	1		
1	1	1	1	1	1		

$$2. A + B \cdot C = (A + B) \cdot (A + C).$$

A	B	C	$B \cdot C$	$A + B \cdot C$	$A + B$	$A + C$	$(A + B)(A + C)$
0	0	0	0	0	0	0	
0	0	1	0	0	0	1	
0	1	0	0	0	1	0	
0	1	1	1	1	1	1	
1	0	0	0	1	1	1	
1	0	1	0	1	1	1	
1	1	0	0	1	1	1	
1	1	1	1	1	1	1	

$$2. A + B \cdot C = (A + B) \cdot (A + C).$$

A	B	C	BC	$A + BC$	$A + B$	$A + C$	$(A + B)(A + C)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

$$2. A + B \cdot C = (A + B) \cdot (A + C).$$

A	B	C	BC	$A + BC$	$A + B$	$A + C$	$(A + B)(A + C)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1



* $A + AB = A$.

To prove this theorem, we can follow two approaches:

* $A + AB = A$.

To prove this theorem, we can follow two approaches:

- (a) Construct truth tables for LHS and RHS for all possible input combinations, and show that they are the same.

* $A + AB = A$.

To prove this theorem, we can follow two approaches:

- (a) Construct truth tables for LHS and RHS for all possible input combinations, and show that they are the same.
- (b) Use identities and theorems stated earlier to show that LHS=RHS.

* $A + AB = A$.

To prove this theorem, we can follow two approaches:

- Construct truth tables for LHS and RHS for all possible input combinations, and show that they are the same.
- Use identities and theorems stated earlier to show that LHS=RHS.

$$\begin{aligned} A + AB &= A \cdot 1 + A \cdot B \\ &= A \cdot (1 + B) \\ &= A \cdot (1) \\ &= A \end{aligned}$$

* $A + AB = A$.

To prove this theorem, we can follow two approaches:

- (a) Construct truth tables for LHS and RHS for all possible input combinations, and show that they are the same.
- (b) Use identities and theorems stated earlier to show that LHS=RHS.

$$\begin{aligned}A + AB &= A \cdot 1 + A \cdot B \\ &= A \cdot (1 + B) \\ &= A \cdot (1) \\ &= A\end{aligned}$$

* $A \cdot (A + B) = A$.

* $A + AB = A$.

To prove this theorem, we can follow two approaches:

- Construct truth tables for LHS and RHS for all possible input combinations, and show that they are the same.
- Use identities and theorems stated earlier to show that LHS=RHS.

$$\begin{aligned}A + AB &= A \cdot 1 + A \cdot B \\ &= A \cdot (1 + B) \\ &= A \cdot (1) \\ &= A\end{aligned}$$

* $A \cdot (A + B) = A$.

Proof:
$$\begin{aligned}A \cdot (A + B) &= A \cdot A + A \cdot B \\ &= A + AB \\ &= A\end{aligned}$$

Duality

$$A + AB = A \iff A \cdot (A + B) = A.$$

Note the duality between OR and AND.

Duality

$$A + AB = A \iff A \cdot (A + B) = A.$$

Note the duality between OR and AND.

Dual of $A + AB$ (LHS): $AB \rightarrow A + B$
 $A + AB \rightarrow A \cdot (A + B).$

Duality

$$A + AB = A \iff A \cdot (A + B) = A.$$

Note the duality between OR and AND.

$$\begin{aligned} \text{Dual of } A + AB \text{ (LHS): } & AB \rightarrow A + B \\ & A + AB \rightarrow A \cdot (A + B). \end{aligned}$$

Dual of A (RHS) = A (since there are no operations involved).

Duality

$$A + AB = A \iff A \cdot (A + B) = A.$$

Note the duality between OR and AND.

$$\begin{aligned} \text{Dual of } A + AB \text{ (LHS): } & AB \rightarrow A + B \\ & A + AB \rightarrow A \cdot (A + B). \end{aligned}$$

Dual of A (RHS) = A (since there are no operations involved).

$$\Rightarrow A \cdot (A + B) = A.$$

Duality

$$A + AB = A \iff A \cdot (A + B) = A.$$

Note the duality between OR and AND.

$$\begin{aligned} \text{Dual of } A + AB \text{ (LHS): } & AB \rightarrow A + B \\ & A + AB \rightarrow A \cdot (A + B). \end{aligned}$$

Dual of A (RHS) = A (since there are no operations involved).

$$\Rightarrow A \cdot (A + B) = A.$$

Similarly, consider $A + \bar{A} = 1$, with $(+ \leftrightarrow \cdot)$ and $(1 \leftrightarrow 0)$.

Duality

$$A + AB = A \iff A \cdot (A + B) = A.$$

Note the duality between OR and AND.

$$\begin{aligned} \text{Dual of } A + AB \text{ (LHS): } & AB \rightarrow A + B \\ & A + AB \rightarrow A \cdot (A + B). \end{aligned}$$

Dual of A (RHS) = A (since there are no operations involved).

$$\Rightarrow A \cdot (A + B) = A.$$

Similarly, consider $A + \bar{A} = 1$, with $(+ \leftrightarrow \cdot)$ and $(1 \leftrightarrow 0)$.

$$\text{Dual of LHS} = A \cdot \bar{A}.$$

Duality

$$A + AB = A \iff A \cdot (A + B) = A.$$

Note the duality between OR and AND.

$$\begin{aligned} \text{Dual of } A + AB \text{ (LHS): } & AB \rightarrow A + B \\ & A + AB \rightarrow A \cdot (A + B). \end{aligned}$$

Dual of A (RHS) = A (since there are no operations involved).

$$\Rightarrow A \cdot (A + B) = A.$$

Similarly, consider $A + \bar{A} = 1$, with $(+ \leftrightarrow \cdot)$ and $(1 \leftrightarrow 0)$.

$$\text{Dual of LHS} = A \cdot \bar{A}.$$

$$\text{Dual of RHS} = 0.$$

Duality

$$A + AB = A \iff A \cdot (A + B) = A.$$

Note the duality between OR and AND.

$$\begin{aligned} \text{Dual of } A + AB \text{ (LHS): } & AB \rightarrow A + B \\ & A + AB \rightarrow A \cdot (A + B). \end{aligned}$$

Dual of A (RHS) = A (since there are no operations involved).

$$\Rightarrow A \cdot (A + B) = A.$$

Similarly, consider $A + \bar{A} = 1$, with $(+ \leftrightarrow \cdot)$ and $(1 \leftrightarrow 0)$.

$$\text{Dual of LHS} = A \cdot \bar{A}.$$

$$\text{Dual of RHS} = 0.$$

$$\Rightarrow A \cdot \bar{A} = 0.$$

$$* A + \overline{A}B = A + B.$$

* $A + \bar{A}B = A + B.$

Proof: $A + \bar{A}B = (A + \bar{A}) \cdot (A + B)$ (by distributive law)
 $= 1 \cdot (A + B)$
 $= A + B$

Dual theorem: $A \cdot (\bar{A} + B) = AB.$

$$* A + \bar{A}B = A + B.$$

$$\begin{aligned} \text{Proof: } A + \bar{A}B &= (A + \bar{A}) \cdot (A + B) && \text{(by distributive law)} \\ &= 1 \cdot (A + B) \\ &= A + B \end{aligned}$$

$$\text{Dual theorem: } A \cdot (\bar{A} + B) = AB.$$

$$* AB + A\bar{B} = A.$$

* $A + \bar{A}B = A + B.$

Proof: $A + \bar{A}B = (A + \bar{A}) \cdot (A + B)$ (by distributive law)
 $= 1 \cdot (A + B)$
 $= A + B$

Dual theorem: $A \cdot (\bar{A} + B) = AB.$

* $AB + A\bar{B} = A.$

Proof: $AB + A\bar{B} = A \cdot (B + \bar{B})$ (by distributive law)
 $= A \cdot 1$
 $= A$

Dual theorem: $(A + B) \cdot (A + \bar{B}) = A.$

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.
- (b) Tedulkar does not score a century AND Warne fails (to get wickets).

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.
- (b) Tedulkar does not score a century AND Warne fails (to get wickets).
- (c) Tedulkar does not score a century AND Sehwag scores a century.

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.
- (b) Tendulkar does not score a century AND Warne fails (to get wickets).
- (c) Tendulkar does not score a century AND Sehwag scores a century.

Let $T \equiv$ Tendulkar scores a century.

$S \equiv$ Sehwag scores a century.

$W \equiv$ Warne fails.

$I \equiv$ India wins.

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.
- (b) Tedulkar does not score a century AND Warne fails (to get wickets).
- (c) Tedulkar does not score a century AND Sehwag scores a century.

Let $T \equiv$ Tendulkar scores a century.

$S \equiv$ Sehwag scores a century.

$W \equiv$ Warne fails.

$I \equiv$ India wins.

$$I = T + \bar{T}W + \bar{T}S$$

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.
- (b) Tedulkar does not score a century AND Warne fails (to get wickets).
- (c) Tedulkar does not score a century AND Sehwag scores a century.

Let $T \equiv$ Tendulkar scores a century.

$S \equiv$ Sehwag scores a century.

$W \equiv$ Warne fails.

$I \equiv$ India wins.

$$\begin{aligned} I &= T + \bar{T}W + \bar{T}S \\ &= T + T + \bar{T}W + \bar{T}S \end{aligned}$$

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.
- (b) Tendulkar does not score a century AND Warne fails (to get wickets).
- (c) Tendulkar does not score a century AND Sehwag scores a century.

Let $T \equiv$ Tendulkar scores a century.

$S \equiv$ Sehwag scores a century.

$W \equiv$ Warne fails.

$I \equiv$ India wins.

$$\begin{aligned} I &= T + \bar{T}W + \bar{T}S \\ &= T + T + \bar{T}W + \bar{T}S \\ &= (T + \bar{T}W) + (T + \bar{T}S) \end{aligned}$$

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.
- (b) Tedulkar does not score a century AND Warne fails (to get wickets).
- (c) Tedulkar does not score a century AND Sehwag scores a century.

Let $T \equiv$ Tendulkar scores a century.

$S \equiv$ Sehwag scores a century.

$W \equiv$ Warne fails.

$I \equiv$ India wins.

$$\begin{aligned} I &= T + \bar{T}W + \bar{T}S \\ &= T + T + \bar{T}W + \bar{T}S \\ &= (T + \bar{T}W) + (T + \bar{T}S) \\ &= (T + \bar{T}) \cdot (T + W) + (T + \bar{T}) \cdot (T + S) \end{aligned}$$

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.
- (b) Tedulkar does not score a century AND Warne fails (to get wickets).
- (c) Tedulkar does not score a century AND Sehwag scores a century.

Let $T \equiv$ Tendulkar scores a century.

$S \equiv$ Sehwag scores a century.

$W \equiv$ Warne fails.

$I \equiv$ India wins.

$$\begin{aligned} I &= T + \bar{T}W + \bar{T}S \\ &= T + T + \bar{T}W + \bar{T}S \\ &= (T + \bar{T}W) + (T + \bar{T}S) \\ &= (T + \bar{T}) \cdot (T + W) + (T + \bar{T}) \cdot (T + S) \\ &= T + W + T + S \\ &= T + W + S \end{aligned}$$

A game of words

In an India-Australia match, India will win if one or more of the following conditions are met:

- (a) Tendulkar scores a century.
- (b) Tendulkar does not score a century AND Warne fails (to get wickets).
- (c) Tendulkar does not score a century AND Sehwag scores a century.

Let $T \equiv$ Tendulkar scores a century.

$S \equiv$ Sehwag scores a century.

$W \equiv$ Warne fails.

$I \equiv$ India wins.

$$\begin{aligned} I &= T + \bar{T}W + \bar{T}S \\ &= T + T + \bar{T}W + \bar{T}S \\ &= (T + \bar{T}W) + (T + \bar{T}S) \\ &= (T + \bar{T}) \cdot (T + W) + (T + \bar{T}) \cdot (T + S) \\ &= T + W + T + S \\ &= T + W + S \end{aligned}$$

i.e., India will win if one or more of the following hold:

- (a) Tendulkar strikes, (b) Warne fails, (c) Sehwag strikes.

Logical functions in standard forms

Consider a function X of three variables A , B , C :

$$\begin{aligned} X &= \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + AB\overline{C} \\ &\equiv X_1 + X_2 + X_3 + X_4 \end{aligned}$$

Logical functions in standard forms

Consider a function X of three variables A, B, C :

$$\begin{aligned} X &= \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C} \\ &\equiv X_1 + X_2 + X_3 + X_4 \end{aligned}$$

This form is called the “sum of products” form (“sum” corresponding to OR and “product” corresponding to AND).

Logical functions in standard forms

Consider a function X of three variables A, B, C :

$$\begin{aligned} X &= \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + AB\overline{C} \\ &\equiv X_1 + X_2 + X_3 + X_4 \end{aligned}$$

This form is called the “sum of products” form (“sum” corresponding to OR and “product” corresponding to AND).

We can construct the truth table for X in a systematic manner:

Logical functions in standard forms

Consider a function X of three variables A, B, C :

$$\begin{aligned} X &= \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C} \\ &\equiv X_1 + X_2 + X_3 + X_4 \end{aligned}$$

This form is called the “sum of products” form (“sum” corresponding to OR and “product” corresponding to AND).

We can construct the truth table for X in a systematic manner:

- (1) Enumerate all possible combinations of A, B, C .
Since each of A, B, C can take two values (0 or 1), we have 2^3 possibilities.

Logical functions in standard forms

Consider a function X of three variables A , B , C :

$$\begin{aligned} X &= \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C} \\ &\equiv X_1 + X_2 + X_3 + X_4 \end{aligned}$$

This form is called the “sum of products” form (“sum” corresponding to OR and “product” corresponding to AND).

We can construct the truth table for X in a systematic manner:

- (1) Enumerate all possible combinations of A , B , C .
Since each of A , B , C can take two values (0 or 1), we have 2^3 possibilities.
- (2) Tabulate $X_1 = \bar{A}B\bar{C}$, etc. Note that X_1 is 1 only if $\bar{A} = B = \bar{C} = 1$ (i.e., $A = 0$, $B = 1$, $C = 0$), and 0 otherwise.

Logical functions in standard forms

Consider a function X of three variables A, B, C :

$$\begin{aligned} X &= \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C} \\ &\equiv X_1 + X_2 + X_3 + X_4 \end{aligned}$$

This form is called the “sum of products” form (“sum” corresponding to OR and “product” corresponding to AND).

We can construct the truth table for X in a systematic manner:

- (1) Enumerate all possible combinations of A, B, C .
Since each of A, B, C can take two values (0 or 1), we have 2^3 possibilities.
- (2) Tabulate $X_1 = \bar{A}B\bar{C}$, etc. Note that X_1 is 1 only if $\bar{A} = B = \bar{C} = 1$ (i.e., $A = 0, B = 1, C = 0$), and 0 otherwise.
- (3) Since $X = X_1 + X_2 + X_3 + X_4$,
 X is 1 if any of X_1, X_2, X_3, X_4 is 1; else X is 0.
→ tabulate X .

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + AB\overline{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0					
0	0	1					
0	1	0	1				
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + AB\overline{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0	0				
0	0	1	0				
0	1	0	1				
0	1	1	0				
1	0	0	0				
1	0	1	0				
1	1	0	0				
1	1	1	0				

"Sum of products" form

$$X = X_1 + X_2 + X_3 + X_4 = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0	0				
0	0	1	0				
0	1	0	1				
0	1	1	0	1			
1	0	0	0				
1	0	1	0				
1	1	0	0				
1	1	1	0				

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0	0	0			
0	0	1	0	0			
0	1	0	1	0			
0	1	1	0	1			
1	0	0	0	0			
1	0	1	0	0			
1	1	0	0	0			
1	1	1	0	0			

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0	0	0			
0	0	1	0	0			
0	1	0	1	0			
0	1	1	0	1			
1	0	0	0	0	1		
1	0	1	0	0			
1	1	0	0	0			
1	1	1	0	0			

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0	0	0	0		
0	0	1	0	0	0		
0	1	0	1	0	0		
0	1	1	0	1	0		
1	0	0	0	0	1		
1	0	1	0	0	0		
1	1	0	0	0	0		
1	1	1	0	0	0		

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0	0	0	0		
0	0	1	0	0	0		
0	1	0	1	0	0		
0	1	1	0	1	0		
1	0	0	0	0	1		
1	0	1	0	0	0		
1	1	0	0	0	0	1	
1	1	1	0	0	0		

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0	0	0	0	0	
0	0	1	0	0	0	0	
0	1	0	1	0	0	0	
0	1	1	0	1	0	0	
1	0	0	0	0	1	0	
1	0	1	0	0	0	0	
1	1	0	0	0	0	1	
1	1	1	0	0	0	0	

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0	0	0	0	0	
0	0	1	0	0	0	0	
0	1	0	1	0	0	0	1
0	1	1	0	1	0	0	1
1	0	0	0	0	1	0	1
1	0	1	0	0	0	0	
1	1	0	0	0	0	1	1
1	1	1	0	0	0	0	

“Sum of products” form

$$X = X_1 + X_2 + X_3 + X_4 = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	X ₁	X ₂	X ₃	X ₄	X
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	1	0	0	1
1	0	0	0	0	1	0	1
1	0	1	0	0	0	0	0
1	1	0	0	0	0	1	1
1	1	1	0	0	0	0	0

Logical functions in standard forms

Consider a function Y of three variables A, B, C :

$$Y = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$
$$\equiv Y_1 \cdot Y_2 \cdot Y_3 \cdot Y_4$$

Logical functions in standard forms

Consider a function Y of three variables A, B, C :

$$Y = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$
$$\equiv Y_1 \cdot Y_2 \cdot Y_3 \cdot Y_4$$

This form is called the “product of sums” form (“sum” corresponding to OR and “product” corresponding to AND).

Logical functions in standard forms

Consider a function Y of three variables A, B, C :

$$Y = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$
$$\equiv Y_1 \cdot Y_2 \cdot Y_3 \cdot Y_4$$

This form is called the “product of sums” form (“sum” corresponding to OR and “product” corresponding to AND).

We can construct the truth table for Y in a systematic manner:

Logical functions in standard forms

Consider a function Y of three variables A, B, C :

$$Y = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$
$$\equiv Y_1 \cdot Y_2 \cdot Y_3 \cdot Y_4$$

This form is called the “product of sums” form (“sum” corresponding to OR and “product” corresponding to AND).

We can construct the truth table for Y in a systematic manner:

- (1) Enumerate all possible combinations of A, B, C .
Since each of A, B, C can take two values (0 or 1), we have 2^3 possibilities.

Logical functions in standard forms

Consider a function Y of three variables A, B, C :

$$Y = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$
$$\equiv Y_1 \cdot Y_2 \cdot Y_3 \cdot Y_4$$

This form is called the “product of sums” form (“sum” corresponding to OR and “product” corresponding to AND).

We can construct the truth table for Y in a systematic manner:

- (1) Enumerate all possible combinations of A, B, C .
Since each of A, B, C can take two values (0 or 1), we have 2^3 possibilities.
- (2) Tabulate $Y_1 = A + B + C$, etc. Note that Y_1 is 0 only if $A = B = C = 0$; Y_1 is 1 otherwise.

Logical functions in standard forms

Consider a function Y of three variables A, B, C :

$$Y = (A + B + C) \cdot (A + B + \bar{C}) \cdot (\bar{A} + B + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C})$$
$$\equiv Y_1 \cdot Y_2 \cdot Y_3 \cdot Y_4$$

This form is called the “product of sums” form (“sum” corresponding to OR and “product” corresponding to AND).

We can construct the truth table for Y in a systematic manner:

- (1) Enumerate all possible combinations of A, B, C .
Since each of A, B, C can take two values (0 or 1), we have 2^3 possibilities.
- (2) Tabulate $Y_1 = A + B + C$, etc. Note that Y_1 is 0 only if $A = B = C = 0$; Y_1 is 1 otherwise.
- (3) Since $Y = Y_1 Y_2 Y_3 Y_4$,
 Y is 0 if any of Y_1, Y_2, Y_3, Y_4 is 0; else Y is 1.
→ tabulate Y .

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0				
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0				
0	0	1	1				
0	1	0	1				
0	1	1	1				
1	0	0	1				
1	0	1	1				
1	1	0	1				
1	1	1	1				

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0				
0	0	1	1	0			
0	1	0	1				
0	1	1	1				
1	0	0	1				
1	0	1	1				
1	1	0	1				
1	1	1	1				

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0	1			
0	0	1	1	0			
0	1	0	1	1			
0	1	1	1	1			
1	0	0	1	1			
1	0	1	1	1			
1	1	0	1	1			
1	1	1	1	1			

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0	1			
0	0	1	1	0			
0	1	0	1	1			
0	1	1	1	1			
1	0	0	1	1			
1	0	1	1	1	0		
1	1	0	1	1			
1	1	1	1	1			

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0	1	1		
0	0	1	1	0	1		
0	1	0	1	1	1		
0	1	1	1	1	1		
1	0	0	1	1	1		
1	0	1	1	1	0		
1	1	0	1	1	1		
1	1	1	1	1	1		

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0	1	1		
0	0	1	1	0	1		
0	1	0	1	1	1		
0	1	1	1	1	1		
1	0	0	1	1	1		
1	0	1	1	1	0		
1	1	0	1	1	1		
1	1	1	1	1	1	0	

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0	1	1	1	
0	0	1	1	0	1	1	
0	1	0	1	1	1	1	
0	1	1	1	1	1	1	
1	0	0	1	1	1	1	
1	0	1	1	1	0	1	
1	1	0	1	1	1	1	
1	1	1	1	1	1	0	

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0	1	1	1	0
0	0	1	1	0	1	1	0
0	1	0	1	1	1	1	
0	1	1	1	1	1	1	
1	0	0	1	1	1	1	
1	0	1	1	1	0	1	0
1	1	0	1	1	1	1	
1	1	1	1	1	1	0	0

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0	1	1	1	0
0	0	1	1	0	1	1	0
0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1
1	0	1	1	1	0	1	0
1	1	0	1	1	1	1	1
1	1	1	1	1	1	0	0

“Product of sums” form

$$Y = Y_1 Y_2 Y_3 Y_4 = (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

A	B	C	Y ₁	Y ₂	Y ₃	Y ₄	Y
0	0	0	0	1	1	1	0
0	0	1	1	0	1	1	0
0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1
1	0	1	1	1	0	1	0
1	1	0	1	1	1	1	1
1	1	1	1	1	1	0	0

Note that Y is identical to X (seen two slides back). This is an example of how the same function can be written in two seemingly different forms (in this case, the sum-of-products form and the product-of-sums form).

Standard sum-of-products form

Consider a function X of three variables A, B, C :

$$X = AB\bar{C} + \bar{A}BC + \bar{A}\bar{B}\bar{C}$$

Standard sum-of-products form

Consider a function X of three variables A , B , C :

$$X = AB\bar{C} + \bar{A}BC + \bar{A}\bar{B}\bar{C}$$

This form is called the *standard* sum-of-products form, and each individual term (consisting of all three variables) is called a “minterm.”

Standard sum-of-products form

Consider a function X of three variables A , B , C :

$$X = AB\bar{C} + \bar{A}BC + \bar{A}\bar{B}\bar{C}$$

This form is called the *standard* sum-of-products form, and each individual term (consisting of all three variables) is called a “minterm.”

In the truth table for X , the numbers of 1s is the same as the number of minterms, as we have seen in an example.

Standard sum-of-products form

Consider a function X of three variables A , B , C :

$$X = AB\bar{C} + \bar{A}BC + \bar{A}B\bar{C}$$

This form is called the *standard* sum-of-products form, and each individual term (consisting of all three variables) is called a “minterm.”

In the truth table for X , the numbers of 1s is the same as the number of minterms, as we have seen in an example.

X can be rewritten as,

$$\begin{aligned} X &= AB\bar{C} + \bar{A}B(C + \bar{C}) \\ &= AB\bar{C} + \bar{A}B. \end{aligned}$$

Standard sum-of-products form

Consider a function X of three variables A , B , C :

$$X = AB\bar{C} + \bar{A}BC + \bar{A}B\bar{C}$$

This form is called the *standard* sum-of-products form, and each individual term (consisting of all three variables) is called a “minterm.”

In the truth table for X , the numbers of 1s is the same as the number of minterms, as we have seen in an example.

X can be rewritten as,

$$\begin{aligned} X &= AB\bar{C} + \bar{A}B(C + \bar{C}) \\ &= AB\bar{C} + \bar{A}B. \end{aligned}$$

This is also a sum-of-products form, but not the standard one.

Standard product-of-sums form

Consider a function X of three variables A, B, C :

$$X = (A + B + C)(\bar{A} + B + C)(\bar{A} + \bar{B} + C)$$

Standard product-of-sums form

Consider a function X of three variables A, B, C :

$$X = (A + B + C)(\bar{A} + B + C)(\bar{A} + \bar{B} + C)$$

This form is called the *standard* product-of-sums form, and each individual term (consisting of all three variables) is called a “maxterm.”

Standard product-of-sums form

Consider a function X of three variables A , B , C :

$$X = (A + B + C)(\bar{A} + B + C)(\bar{A} + \bar{B} + C)$$

This form is called the *standard* product-of-sums form, and each individual term (consisting of all three variables) is called a “maxterm.”

In the truth table for X , the numbers of 0s is the same as the number of maxterms, as we have seen in an example.

Standard product-of-sums form

Consider a function X of three variables A , B , C :

$$X = (A + B + C)(\bar{A} + B + C)(\bar{A} + \bar{B} + C)$$

This form is called the *standard* product-of-sums form, and each individual term (consisting of all three variables) is called a “maxterm.”

In the truth table for X , the numbers of 0s is the same as the number of maxterms, as we have seen in an example.

X can be rewritten as,

$$\begin{aligned} X &= (A + B + C)(\bar{A} + B + C)(\bar{A} + \bar{B} + C) \\ &= (A + B + C)(\bar{A} + C + B)(\bar{A} + C + \bar{B}) \\ &= (A + B + C)(\bar{A} + C + B\bar{B}) \\ &= (A + B + C)(\bar{A} + C). \end{aligned}$$

Standard product-of-sums form

Consider a function X of three variables A, B, C :

$$X = (A + B + C)(\bar{A} + B + C)(\bar{A} + \bar{B} + C)$$

This form is called the *standard* product-of-sums form, and each individual term (consisting of all three variables) is called a “maxterm.”

In the truth table for X , the numbers of 0s is the same as the number of maxterms, as we have seen in an example.

X can be rewritten as,

$$\begin{aligned} X &= (A + B + C)(\bar{A} + B + C)(\bar{A} + \bar{B} + C) \\ &= (A + B + C)(\bar{A} + C + B)(\bar{A} + C + \bar{B}) \\ &= (A + B + C)(\bar{A} + C + B\bar{B}) \\ &= (A + B + C)(\bar{A} + C). \end{aligned}$$

This is also a product-of-sums form, but not the standard one.

The “don't care” condition

I want to design a box (with inputs A , B , C , and output S) which will help in scheduling my appointments.

$A \equiv$ I am in town, and the time slot being suggested for the appointment is free.

$B \equiv$ My favourite player is scheduled to play a match (which I can watch on TV).

$C \equiv$ The appointment is crucial for my business.

$S \equiv$ Schedule the appointment.

The “don't care” condition

I want to design a box (with inputs A , B , C , and output S) which will help in scheduling my appointments.

$A \equiv$ I am in town, and the time slot being suggested for the appointment is free.

$B \equiv$ My favourite player is scheduled to play a match (which I can watch on TV).

$C \equiv$ The appointment is crucial for my business.

$S \equiv$ Schedule the appointment.

The following truth table summarizes the expected functioning of the box.

A	B	C	S
0	X	X	0
1	0	X	1
1	1	0	0
1	1	1	1

The “don't care” condition

I want to design a box (with inputs A , B , C , and output S) which will help in scheduling my appointments.

$A \equiv$ I am in town, and the time slot being suggested for the appointment is free.

$B \equiv$ My favourite player is scheduled to play a match (which I can watch on TV).

$C \equiv$ The appointment is crucial for my business.

$S \equiv$ Schedule the appointment.

The following truth table summarizes the expected functioning of the box.

A	B	C	S
0	X	X	0
1	0	X	1
1	1	0	0
1	1	1	1

Note that we have a new entity called X in the truth table.

The “don't care” condition

I want to design a box (with inputs A , B , C , and output S) which will help in scheduling my appointments.

$A \equiv$ I am in town, and the time slot being suggested for the appointment is free.

$B \equiv$ My favourite player is scheduled to play a match (which I can watch on TV).

$C \equiv$ The appointment is crucial for my business.

$S \equiv$ Schedule the appointment.

The following truth table summarizes the expected functioning of the box.

A	B	C	S
0	X	X	0
1	0	X	1
1	1	0	0
1	1	1	1

Note that we have a new entity called X in the truth table.

X can be 0 or 1 (it does not matter) and is therefore called the “don't care” condition.

The “don't care” condition

I want to design a box (with inputs A , B , C , and output S) which will help in scheduling my appointments.

$A \equiv$ I am in town, and the time slot being suggested for the appointment is free.

$B \equiv$ My favourite player is scheduled to play a match (which I can watch on TV).

$C \equiv$ The appointment is crucial for my business.

$S \equiv$ Schedule the appointment.

The following truth table summarizes the expected functioning of the box.

A	B	C	S
0	X	X	0
1	0	X	1
1	1	0	0
1	1	1	1

Note that we have a new entity called X in the truth table.

X can be 0 or 1 (it does not matter) and is therefore called the “don't care” condition.

Don't care conditions can often be used to get a more efficient implementation of a logical function.