

EE101: Op Amp circuits (Part 1)



M. B. Patil

mbpatil@ee.iitb.ac.in
www.ee.iitb.ac.in/~sequel

Department of Electrical Engineering
Indian Institute of Technology Bombay

- * The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.

- * The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- * The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.

- * The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- * The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.
- * The characteristics of an Op Amp are nearly ideal \rightarrow Op Amp circuits can be expected to perform as per theoretical design in most cases.

- * The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- * The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.
- * The characteristics of an Op Amp are nearly ideal → Op Amp circuits can be expected to perform as per theoretical design in most cases.
- * Amplifiers built with Op Amps work with DC input voltages as well → useful in sensor applications (e.g., temperature, pressure)

Op Amps: introduction


- * The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- * The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.
- * The characteristics of an Op Amp are nearly ideal → Op Amp circuits can be expected to perform as per theoretical design in most cases.
- * Amplifiers built with Op Amps work with DC input voltages as well → useful in sensor applications (e.g., temperature, pressure)
- * The user can generally carry out circuit design without a thorough knowledge of the intricate details (next slide) of an Op Amp. This makes the design process simple.

Op Amps: introduction




- * The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- * The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.
- * The characteristics of an Op Amp are nearly ideal → Op Amp circuits can be expected to perform as per theoretical design in most cases.
- * Amplifiers built with Op Amps work with DC input voltages as well → useful in sensor applications (e.g., temperature, pressure)
- * The user can generally carry out circuit design without a thorough knowledge of the intricate details (next slide) of an Op Amp. This makes the design process simple.
- * However, as Einstein has said, we should “make everything as simple as possible, but not simpler.” → need to know where the ideal world ends, and the real one begins.

Op Amp 741


Actual circuit

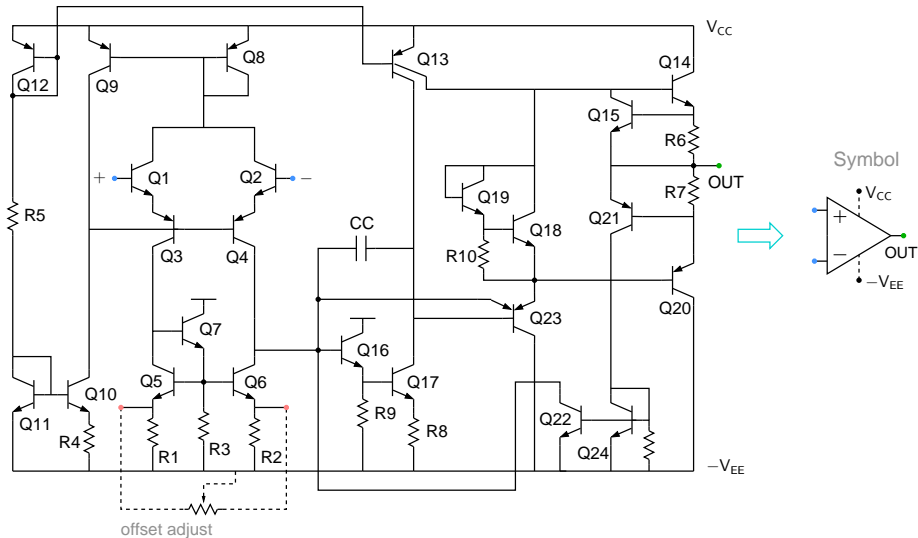

Op Amp: equivalent circuit

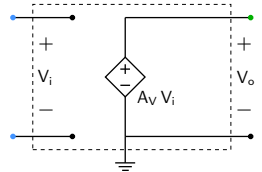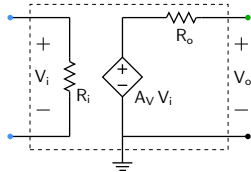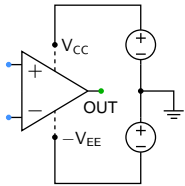


Op Amp: equivalent circuit

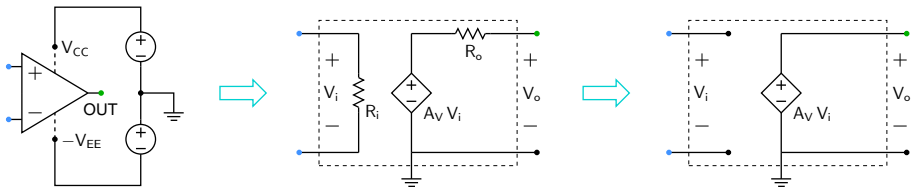


- * The external resistances (\sim a few $k\Omega$) are generally much larger than R_o and much smaller than $R_i \rightarrow$ we can assume $R_i \rightarrow \infty$, $R_o \rightarrow 0$ without significantly affecting the analysis.

Op Amp: equivalent circuit

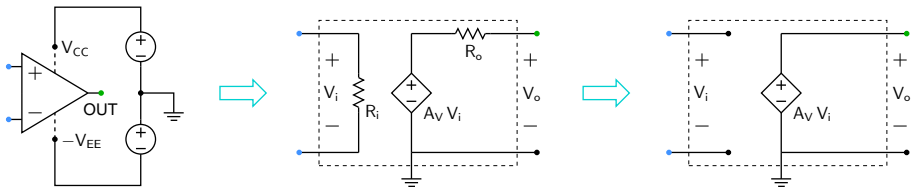

- * The external resistances (\sim a few $k\Omega$) are generally much larger than R_o and much smaller than $R_i \rightarrow$ we can assume $R_i \rightarrow \infty$, $R_o \rightarrow 0$ without significantly affecting the analysis.
- * V_{CC} and $-V_{EE}$ ($\sim \pm 5 V$ to $\pm 15 V$) must be supplied; an Op Amp will not work without them!


Op Amp: equivalent circuit

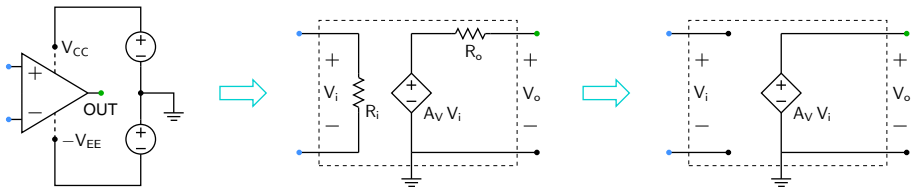

- * The external resistances (\sim a few $k\Omega$) are generally much larger than R_o and much smaller than $R_i \rightarrow$ we can assume $R_i \rightarrow \infty$, $R_o \rightarrow 0$ without significantly affecting the analysis.
- * V_{CC} and $-V_{EE}$ ($\sim \pm 5 V$ to $\pm 15 V$) must be supplied; an Op Amp will not work without them!

In Op Amp circuits, the supply voltages are often not shown explicitly.

Op Amp: equivalent circuit



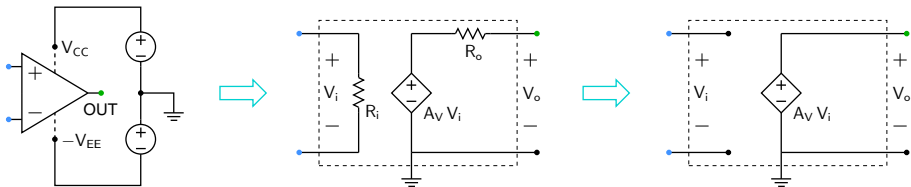


- * The external resistances (\sim a few $k\Omega$) are generally much larger than R_o and much smaller than $R_i \rightarrow$ we can assume $R_i \rightarrow \infty$, $R_o \rightarrow 0$ without significantly affecting the analysis.
- * V_{CC} and $-V_{EE}$ ($\sim \pm 5 V$ to $\pm 15 V$) must be supplied; an Op Amp will not work without them!




In Op Amp circuits, the supply voltages are often not shown explicitly.

Parameter	Ideal Op Amp	741
A_V	∞	10^5 (100 dB)
R_i	∞	2 M Ω
R_o	0	75 Ω

Op Amp: equivalent circuit

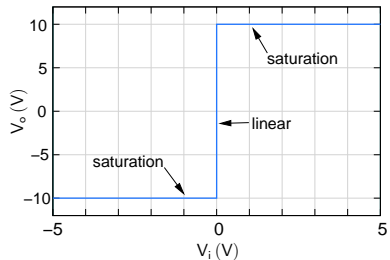
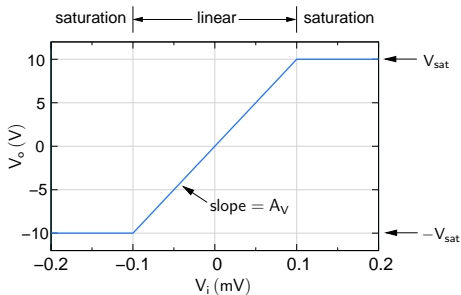
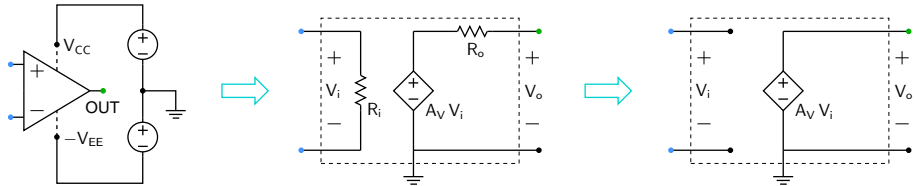


Op Amp: equivalent circuit

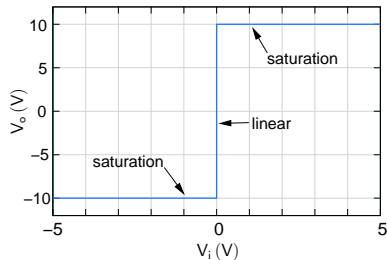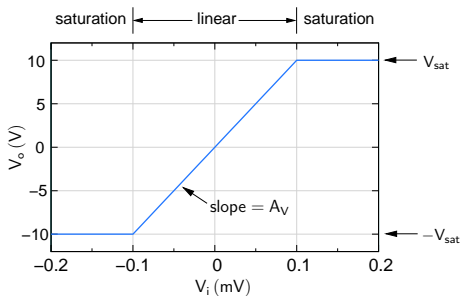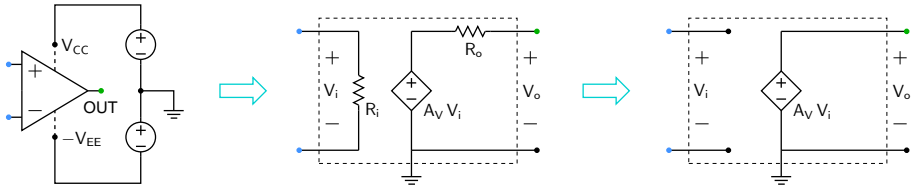




* The output voltage V_o is limited to $\pm V_{sat}$, where $V_{sat} \sim 1.5$ V less than V_{CC} .

Op Amp: equivalent circuit

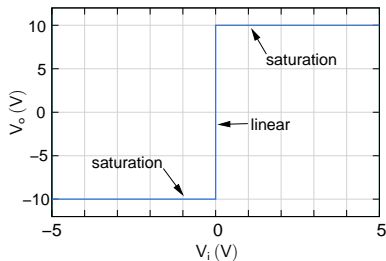
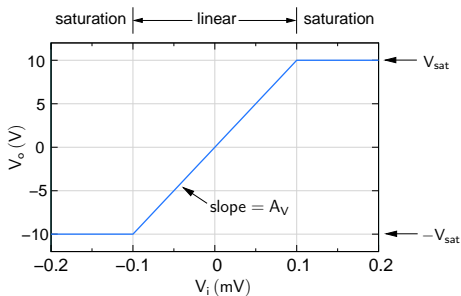
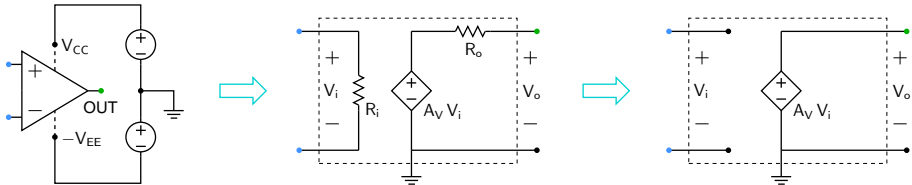


- * The output voltage V_o is limited to $\pm V_{sat}$, where $V_{sat} \sim 1.5$ V less than V_{CC} .
- * For $-V_{sat} < V_o < V_{sat}$, $V_i = V_+ - V_- = V_o/A_V$, which is very small $\rightarrow V_+$ and V_- are *virtually* the same.

Op Amp circuits

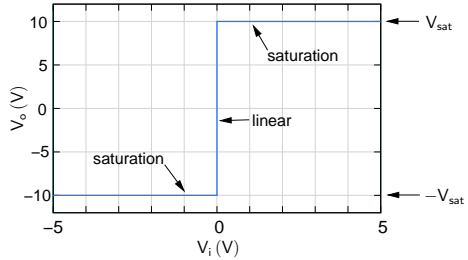
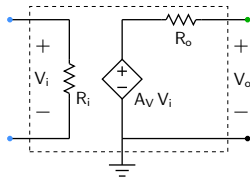
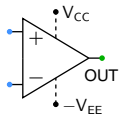


Op Amp circuits

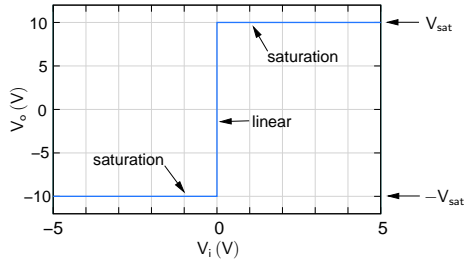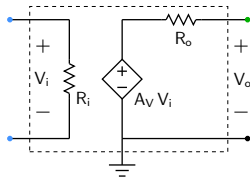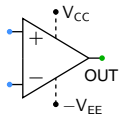




* Broadly, Op Amp circuits can be divided into two categories:

Op Amp circuits

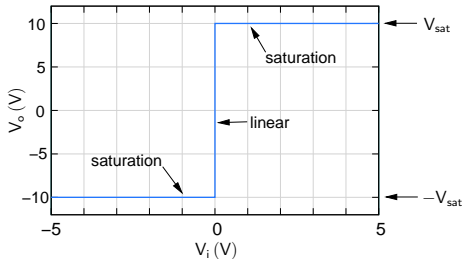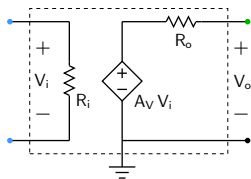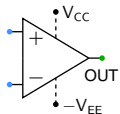

- * Broadly, Op Amp circuits can be divided into two categories:
 - Op Amp operating in the linear region




Op Amp circuits

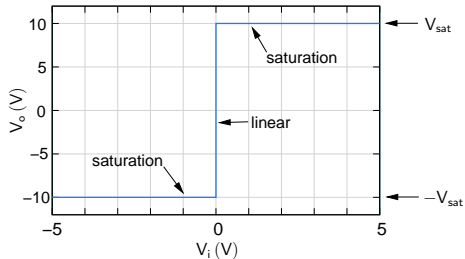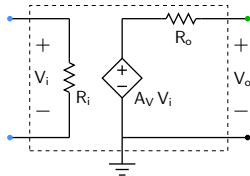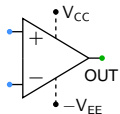

* Broadly, Op Amp circuits can be divided into two categories:




- Op Amp operating in the linear region
- Op Amp operating in the saturation region

Op Amp circuits

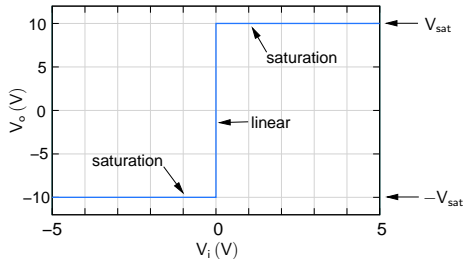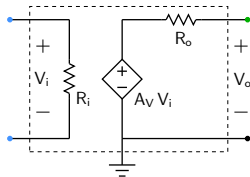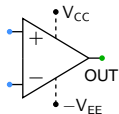




- * Broadly, Op Amp circuits can be divided into two categories:
 - Op Amp operating in the linear region
 - Op Amp operating in the saturation region
- * Whether an Op Amp in a given circuit will operate in linear or saturation region depends on

Op Amp circuits

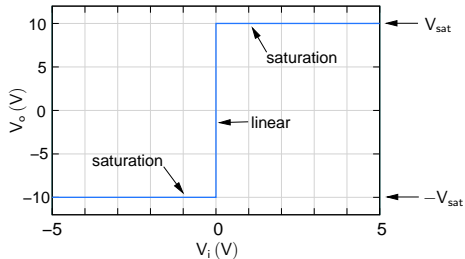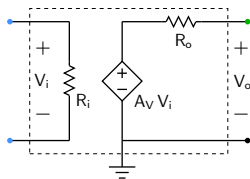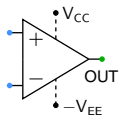




- * Broadly, Op Amp circuits can be divided into two categories:
 - Op Amp operating in the linear region
 - Op Amp operating in the saturation region
- * Whether an Op Amp in a given circuit will operate in linear or saturation region depends on
 - input voltage magnitude

Op Amp circuits

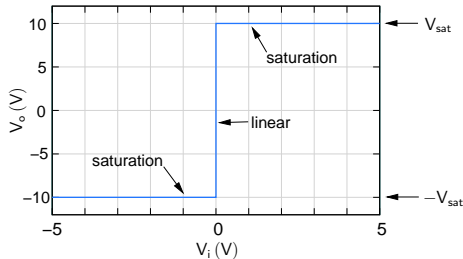
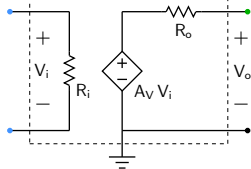
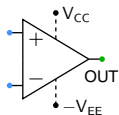


- * Broadly, Op Amp circuits can be divided into two categories:
 - Op Amp operating in the linear region
 - Op Amp operating in the saturation region
- * Whether an Op Amp in a given circuit will operate in linear or saturation region depends on
 - input voltage magnitude
 - type of feedback (negative or positive)
(We will take a qualitative look at feedback later.)

Op Amp circuits (linear region)

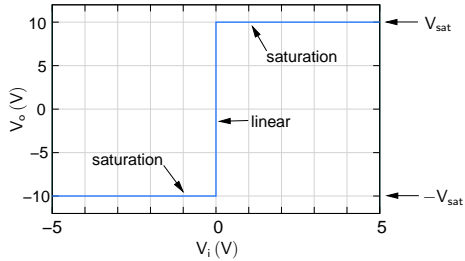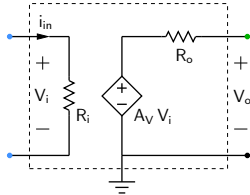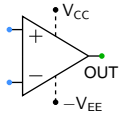

Op Amp circuits (linear region)

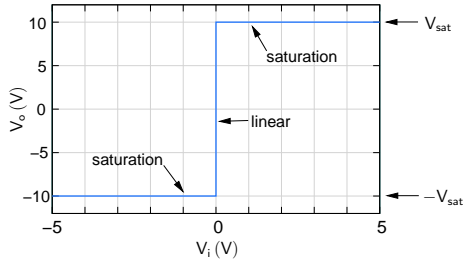
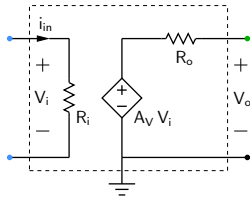
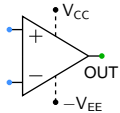


In the linear region,

* $V_+ - V_- = V_o/A_V$, which is very small

$$\rightarrow \boxed{V_+ \approx V_-}$$

Op Amp circuits (linear region)

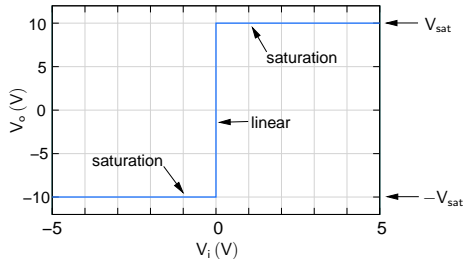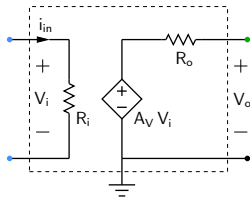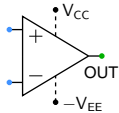

In the linear region,




- * $V_+ - V_- = V_o/A_V$, which is very small

$$\rightarrow V_+ \approx V_-$$

- * Since R_i is typically much larger than other resistances in the circuit, we can assume $R_i \rightarrow \infty$.

$$\rightarrow i_{in} \approx 0$$

Op Amp circuits (linear region)

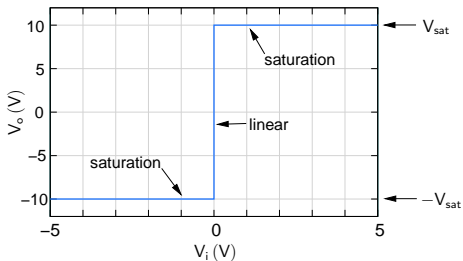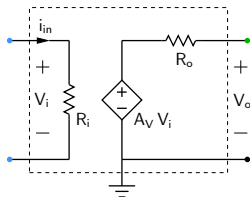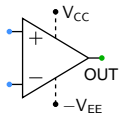

In the linear region,

- * $V_+ - V_- = V_o/A_V$, which is very small


$$\rightarrow V_+ \approx V_-$$

- * Since R_i is typically much larger than other resistances in the circuit, we can assume $R_i \rightarrow \infty$.


$$\rightarrow i_{in} \approx 0$$

These two “golden rules” enable us to understand several Op Amp circuits.

Op Amp circuits (linear region)

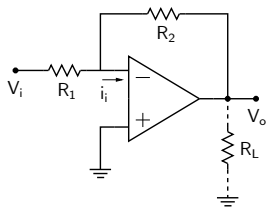


Op Amp circuits (linear region)

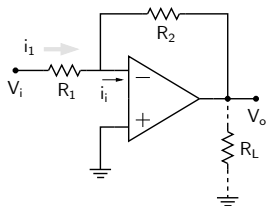

Since $V_+ \approx V_-$, $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$.

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Op Amp circuits (linear region)

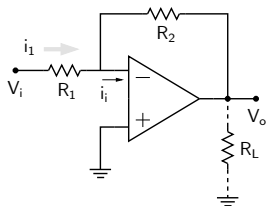


Since $V_+ \approx V_-$, $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$.

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since i_i (current entering the Op Amp) is zero, i_1 goes through R_2 .

Op Amp circuits (linear region)

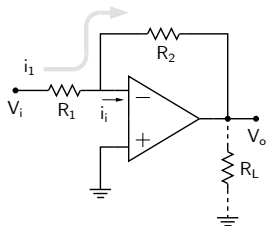


Since $V_+ \approx V_-$, $V_- \approx 0\text{ V} \rightarrow i_i = (V_i - 0)/R = V_i/R$.

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since i_i (current entering the Op Amp) is zero, i_1 goes through R_2 .

Op Amp circuits (linear region)

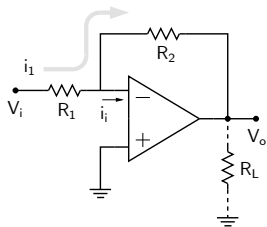


Since $V_+ \approx V_-$, $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$.

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since i_i (current entering the Op Amp) is zero, i_1 goes through R_2 .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left(\frac{V_i}{R_1}\right) R_2 = -\left(\frac{R_2}{R_1}\right) V_i.$$

Op Amp circuits (linear region)

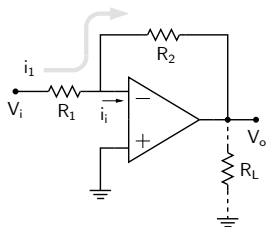

Since $V_+ \approx V_-$, $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$.


(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since i_i (current entering the Op Amp) is zero, i_1 goes through R_2 .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left(\frac{V_i}{R_1}\right) R_2 = -\left(\frac{R_2}{R_1}\right) V_i.$$

The circuit is called an “inverting amplifier.”

Op Amp circuits (linear region)

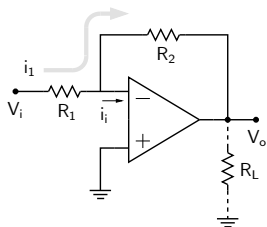

Since $V_+ \approx V_-$, $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$.

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)


Since i_i (current entering the Op Amp) is zero, i_1 goes through R_2 .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left(\frac{V_i}{R_1}\right) R_2 = -\left(\frac{R_2}{R_1}\right) V_i.$$

The circuit is called an “inverting amplifier.”

Where does the current go?

Op Amp circuits (linear region)

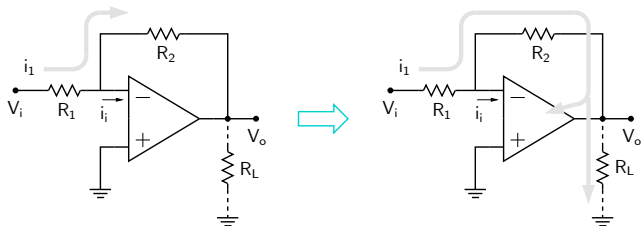

Since $V_+ \approx V_-$, $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$.

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)



Since i_i (current entering the Op Amp) is zero, i_1 goes through R_2 .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left(\frac{V_i}{R_1}\right) R_2 = -\left(\frac{R_2}{R_1}\right) V_i.$$



The circuit is called an “inverting amplifier.”

Where does the current go?

Op Amp circuits: inverting amplifier

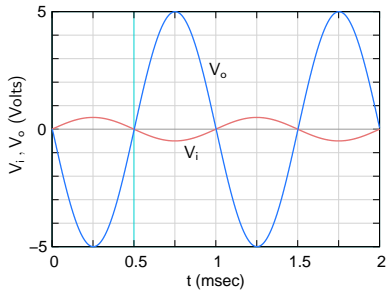
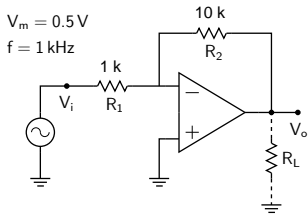


Op Amp circuits: inverting amplifier

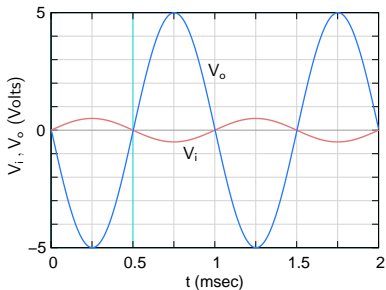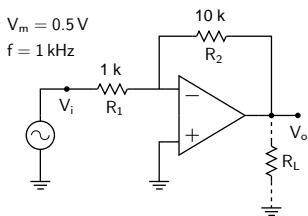



- * The gain of the inverting amplifier is $-R_2/R_1$. It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the Op Amp which is $\sim 10^5$).

Op Amp circuits: inverting amplifier

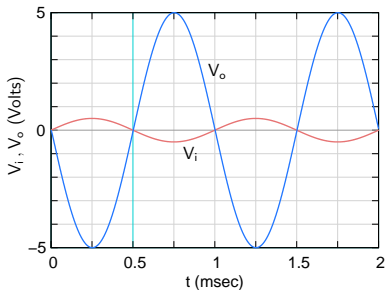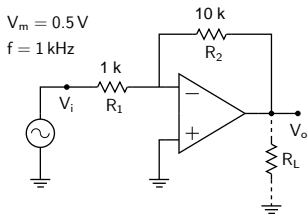



- * The gain of the inverting amplifier is $-R_2/R_1$. It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the Op Amp which is $\sim 10^5$).
- * The gain can be adjusted simply by changing R_1 or R_2 !

Op Amp circuits: inverting amplifier

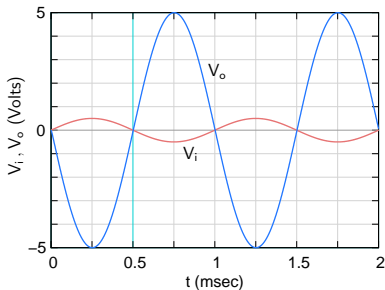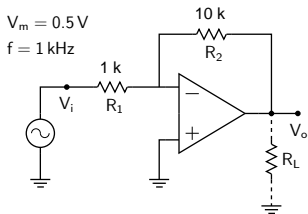

- * The gain of the inverting amplifier is $-R_2/R_1$. It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the Op Amp which is $\sim 10^5$).
- * The gain can be adjusted simply by changing R_1 or R_2 !
- * For the common-emitter amplifier, on the other hand, the gain $-g_m (R_C \parallel R_L)$ depends on how the BJT is biased (since g_m depends on I_C).



Op Amp circuits: inverting amplifier

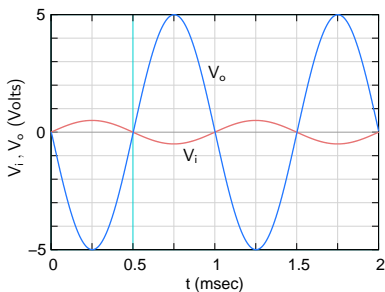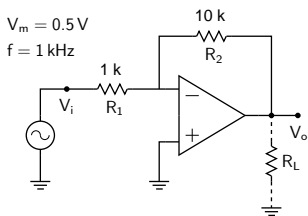



- * The gain of the inverting amplifier is $-R_2/R_1$. It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the Op Amp which is $\sim 10^5$).
- * The gain can be adjusted simply by changing R_1 or R_2 !
- * For the common-emitter amplifier, on the other hand, the gain $-g_m (R_C \parallel R_L)$ depends on how the BJT is biased (since g_m depends on I_C).

(SEQUEL file: ee101_inv_amp_1.sqproj)

Op Amp circuits: inverting amplifier

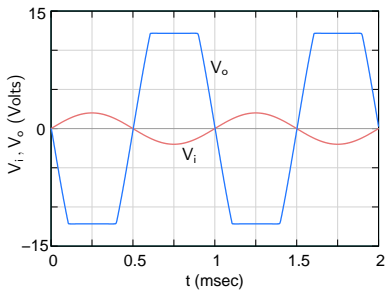
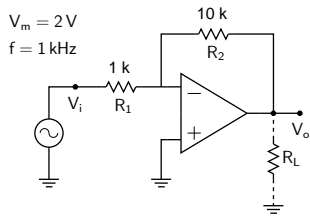


Op Amp circuits: inverting amplifier

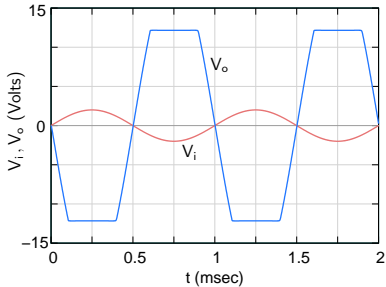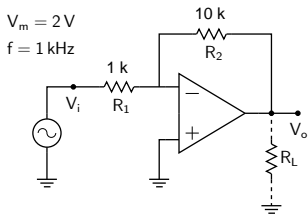



* The output voltage is limited to $\pm V_{\text{sat}}$.

Op Amp circuits: inverting amplifier

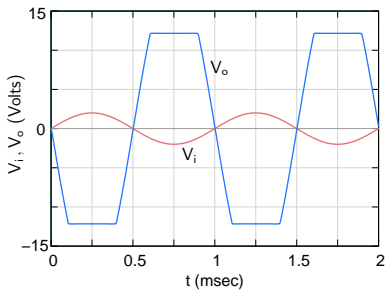
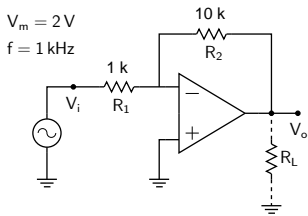


- * The output voltage is limited to $\pm V_{sat}$.
- * V_{sat} is $\sim 1.5\text{ V}$ less than the supply voltage V_{CC} .

Op Amp circuits: inverting amplifier

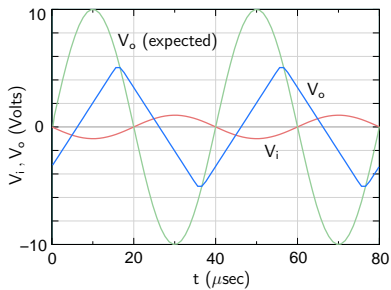
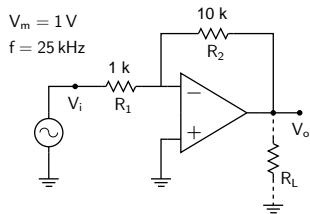


Op Amp circuits: inverting amplifier

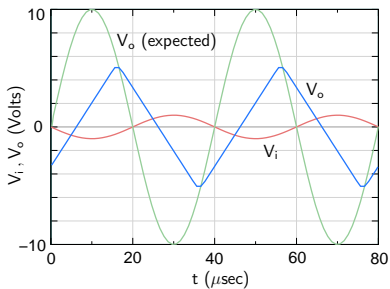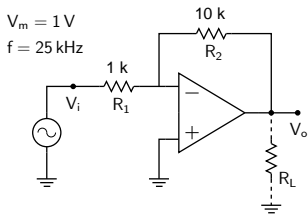



- * If the signal frequency is too high, a practical Op Amp cannot keep up with the input due to its “slew rate” limitation.

Op Amp circuits: inverting amplifier

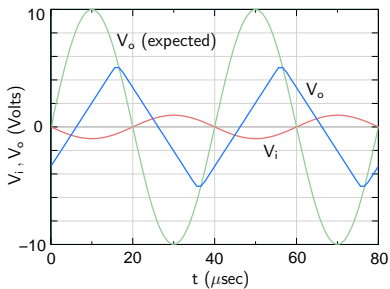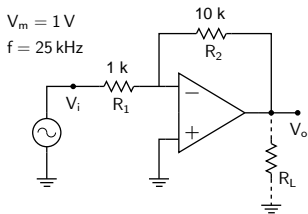



- * If the signal frequency is too high, a practical Op Amp cannot keep up with the input due to its “slew rate” limitation.
- * The slew rate of an Op Amp is the maximum rate at which the Op Amp output can rise (or fall).

Op Amp circuits: inverting amplifier

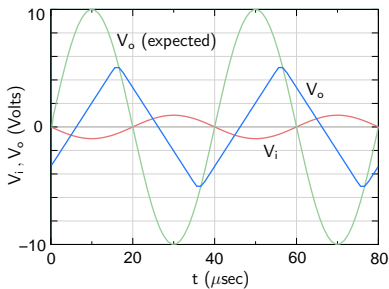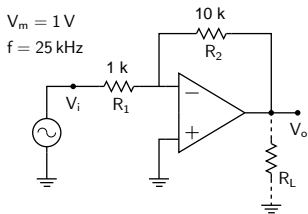

- * If the signal frequency is too high, a practical Op Amp cannot keep up with the input due to its “slew rate” limitation.
- * The slew rate of an Op Amp is the maximum rate at which the Op Amp output can rise (or fall).
- * For the 741, the slew rate is $0.5\text{ V}/\mu\text{sec}$.


Op Amp circuits: inverting amplifier

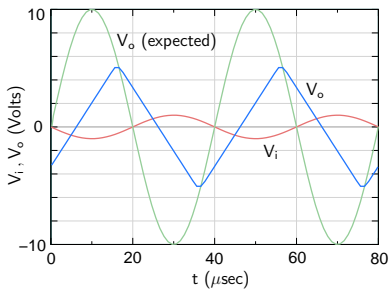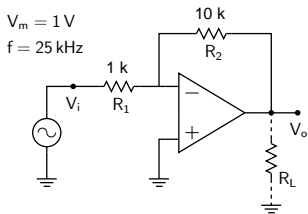


- * If the signal frequency is too high, a practical Op Amp cannot keep up with the input due to its “slew rate” limitation.
- * The slew rate of an Op Amp is the maximum rate at which the Op Amp output can rise (or fall).
- * For the 741, the slew rate is $0.5\text{ V}/\mu\text{sec}$.

(SEQUEL file: ee101_inv_amp_2.sqproj)

Op Amp circuits: inverting amplifier

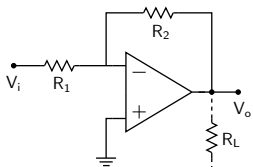



Circuit 1

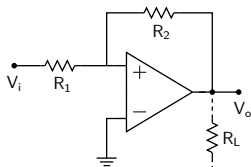

Circuit 2

What if the + (non-inverting) and - (inverting) inputs of the Op Amp are interchanged?



Op Amp circuits: inverting amplifier

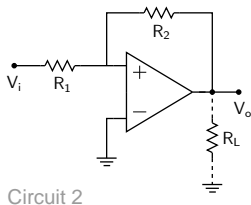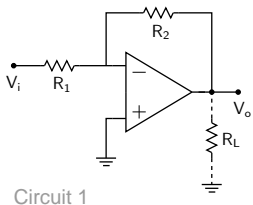

What if the + (non-inverting) and - (inverting) inputs of the Op Amp are interchanged?

Our previous analysis would once again give us $V_o = -\frac{R_2}{R_1} V_i$.

Op Amp circuits: inverting amplifier

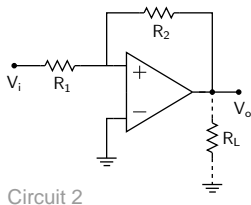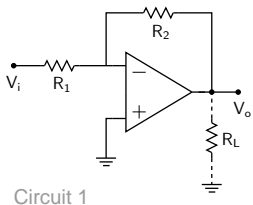



What if the + (non-inverting) and - (inverting) inputs of the Op Amp are interchanged?

Our previous analysis would once again give us $V_o = -\frac{R_2}{R_1} V_i$.

However, from Circuit 1 to Circuit 2, the nature of the feedback changes from negative to positive.

→ Our assumption that the Op Amp is working in the linear region does not hold for Circuit 2, and $V_o = -\frac{R_2}{R_1} V_i$ does not apply any more.

Op Amp circuits: inverting amplifier

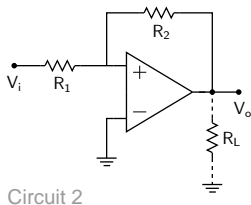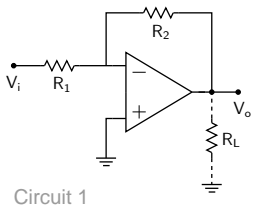

What if the + (non-inverting) and - (inverting) inputs of the Op Amp are interchanged?


Our previous analysis would once again give us $V_o = -\frac{R_2}{R_1} V_i$.

However, from Circuit 1 to Circuit 2, the nature of the feedback changes from negative to positive.

→ Our assumption that the Op Amp is working in the linear region does not hold for Circuit 2, and $V_o = -\frac{R_2}{R_1} V_i$ does not apply any more.


(Circuit 2 is also useful, and we will discuss it later.)

Op Amp circuits (linear region)

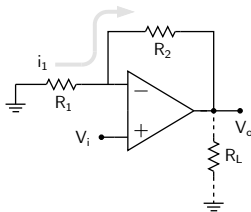

* $V_+ \approx V_- = V_i$


Op Amp circuits (linear region)

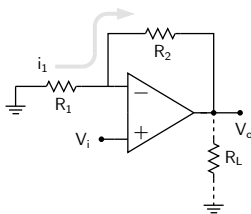

$$* V_+ \approx V_- = V_i$$

$$\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1 .$$

Op Amp circuits (linear region)

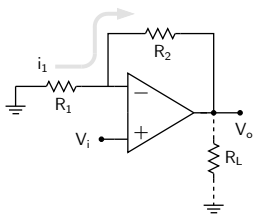


$$* V_+ \approx V_- = V_i$$

$$\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1 .$$


$$* V_o = V_+ - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right) .$$

Op Amp circuits (linear region)

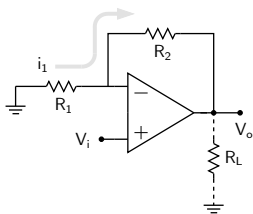


- * $V_+ \approx V_- = V_i$
 $\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1$.
- * $V_o = V_+ - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right)$.
- * This circuit is known as the “non-inverting amplifier.”

Op Amp circuits (linear region)


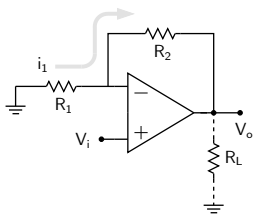


- * $V_+ \approx V_- = V_i$
 $\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1$.
- * $V_o = V_+ - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right)$.
- * This circuit is known as the “non-inverting amplifier.”
- * Again, interchanging + and - changes the nature of the feedback from negative to positive, and the circuit operation becomes completely different.


Inverting or non-inverting?

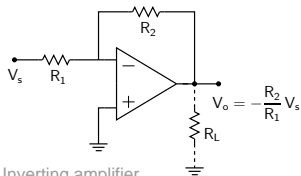

Inverting amplifier

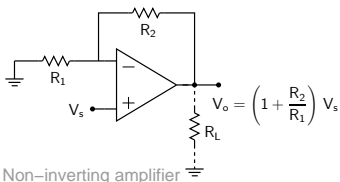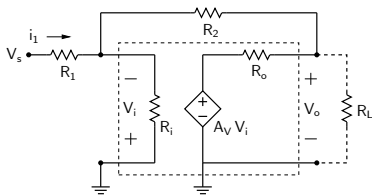


Non-inverting amplifier


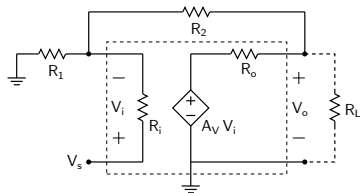


- * If the sign of the output voltage is not a concern, which configuration should be preferred?


Inverting or non-inverting?

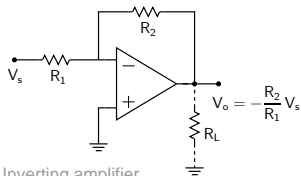

Inverting amplifier

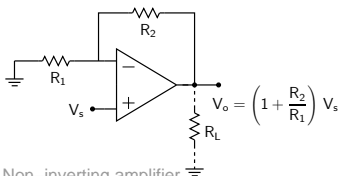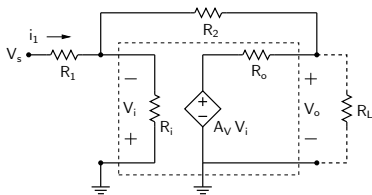


Non-inverting amplifier


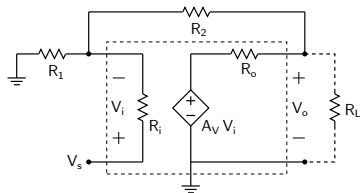


- * If the sign of the output voltage is not a concern, which configuration should be preferred?
- * For the inverting amplifier, since $V_- \approx 0\text{ V}$, $i_1 = V_s/R_1 \rightarrow R_{in} = V_s/i_1 = R_1$.


Inverting or non-inverting?

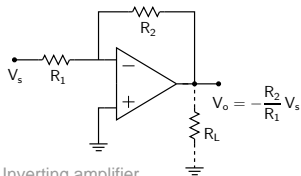

Inverting amplifier

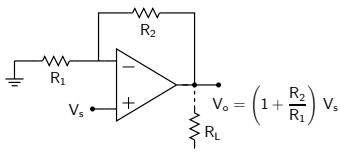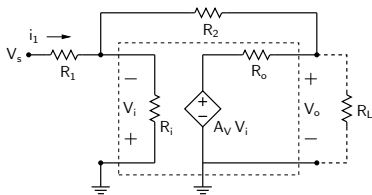


Non-inverting amplifier

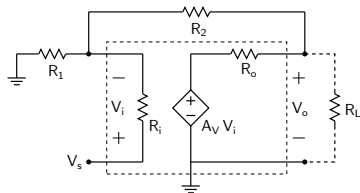


- * If the sign of the output voltage is not a concern, which configuration should be preferred?
 - * For the inverting amplifier, since $V_- \approx 0\text{ V}$, $i_1 = V_s/R_1 \rightarrow R_{in} = V_s/i_1 = R_1$.
 - * For the non-inverting amplifier, $R_{in} \sim R_i$ of the Op Amp, which is a few $\text{M}\Omega$.
- Non-inverting amplifier is better if a large R_{in} is required.

Non-inverting amplifier

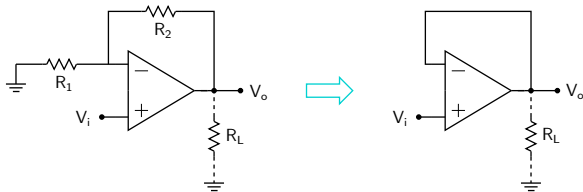

Consider $R_1 \rightarrow \infty$, $R_2 \rightarrow 0$.


Non-inverting amplifier

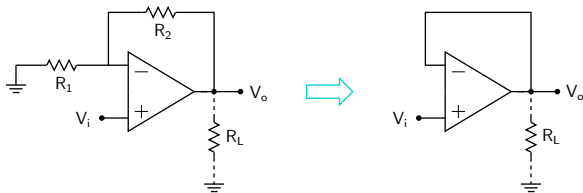

Consider $R_1 \rightarrow \infty$, $R_2 \rightarrow 0$.

$$\frac{V_o}{V_i} \rightarrow 1 + \frac{R_2}{R_1} \rightarrow 1, \text{ i.e., } V_o = V_i.$$

Non-inverting amplifier

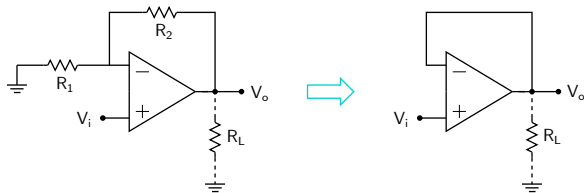


Consider $R_1 \rightarrow \infty$, $R_2 \rightarrow 0$.

$$\frac{V_o}{V_i} \rightarrow 1 + \frac{R_2}{R_1} \rightarrow 1, \text{ i.e., } V_o = V_i.$$

This circuit is known as unity-gain amplifier/voltage follower/buffer.

Non-inverting amplifier

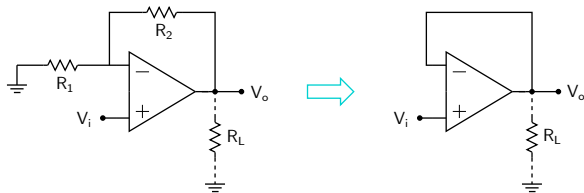


Consider $R_1 \rightarrow \infty$, $R_2 \rightarrow 0$.

$$\frac{V_o}{V_i} \rightarrow 1 + \frac{R_2}{R_1} \rightarrow 1, \text{ i.e., } V_o = V_i.$$

This circuit is known as unity-gain amplifier/voltage follower/buffer.


What has been achieved?

Loading effects

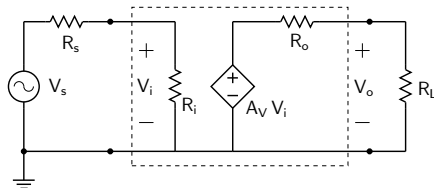

Consider an amplifier of gain A_V . We would like to have $V_o = A_V V_s$.

Loading effects

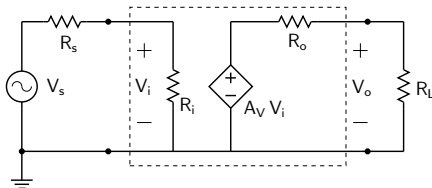


Consider an amplifier of gain A_V . We would like to have $V_o = A_V V_s$.

However, the actual output voltage is,

$$V_o = \frac{R_L}{R_o + R_L} \times A_V V_i = A_V \times \frac{R_L}{R_o + R_L} \times \frac{R_i}{R_i + R_s} V_s.$$

Loading effects

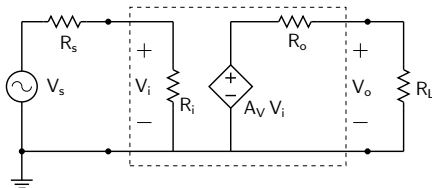


Consider an amplifier of gain A_V . We would like to have $V_o = A_V V_s$.

However, the actual output voltage is,

$$V_o = \frac{R_L}{R_o + R_L} \times A_V V_i = A_V \times \frac{R_L}{R_o + R_L} \times \frac{R_i}{R_i + R_s} V_s.$$

To obtain the desired V_o , we need $R_i \rightarrow \infty$ and $R_o \rightarrow 0$.

Loading effects

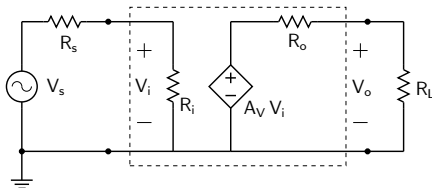

Consider an amplifier of gain A_V . We would like to have $V_o = A_V V_s$.


However, the actual output voltage is,

$$V_o = \frac{R_L}{R_o + R_L} \times A_V V_i = A_V \times \frac{R_L}{R_o + R_L} \times \frac{R_i}{R_i + R_s} V_s.$$

To obtain the desired V_o , we need $R_i \rightarrow \infty$ and $R_o \rightarrow 0$.


The buffer (voltage follower) provides this feature (next slide).

Op Amp buffer

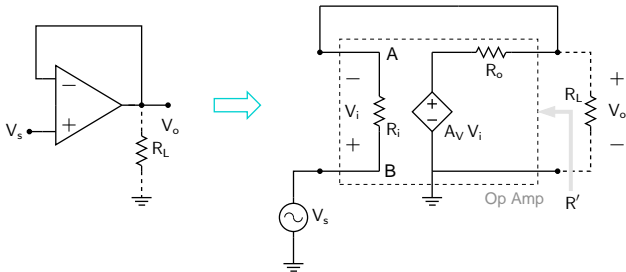


- * The current drawn from the source (V_s) is small (since R_i of the Op Amp is large) \rightarrow the buffer has a large input resistance.

Op Amp buffer

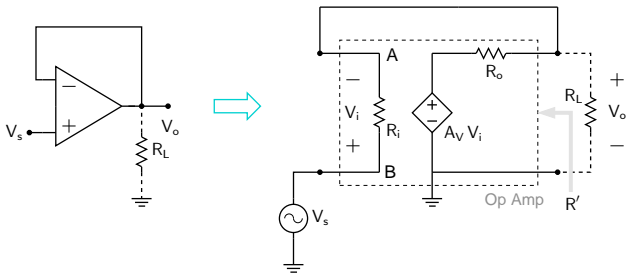


- * The current drawn from the source (V_s) is small (since R_i of the Op Amp is large) \rightarrow the buffer has a large input resistance.
- * As we have seen earlier, A_V is large $\rightarrow V_i \approx 0 V \rightarrow V_A = V_B = V_s$.

Op Amp buffer

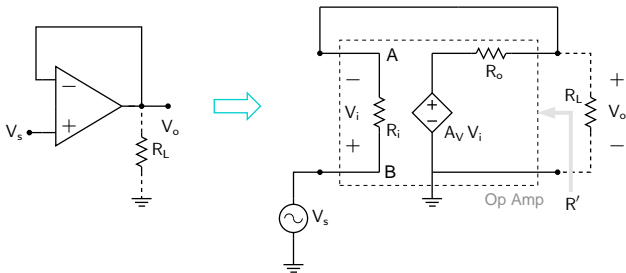


- * The current drawn from the source (V_s) is small (since R_i of the Op Amp is large) \rightarrow the buffer has a large input resistance.
- * As we have seen earlier, A_V is large $\rightarrow V_i \approx 0 V \rightarrow V_A = V_B = V_s$.
- * The resistance seen by R_L is $R' \approx R_o$, which is small \rightarrow the buffer has a small output resistance. (To find R' , deactivate the input voltage source (V_s) $\rightarrow A_V V_i = 0 V$.)

Op Amp buffer

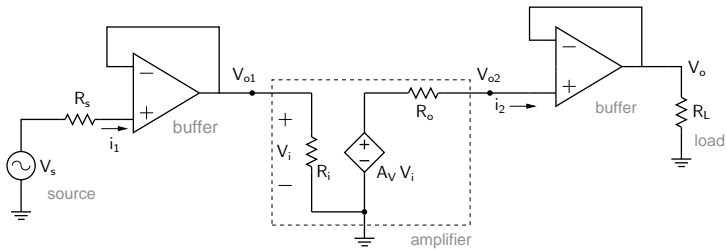


Op Amp buffer

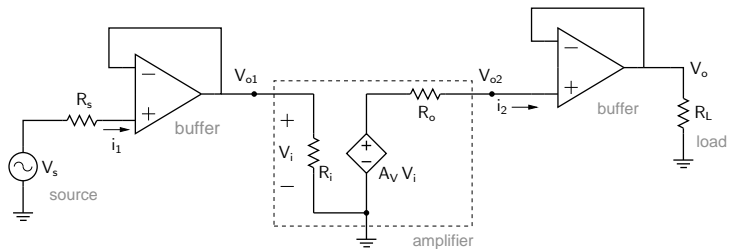


Since the buffer has a large input resistance, $i_1 \approx 0 A$,
and V_+ (on the source side) = $V_s \rightarrow V_{o1} = V_s$.

Op Amp buffer

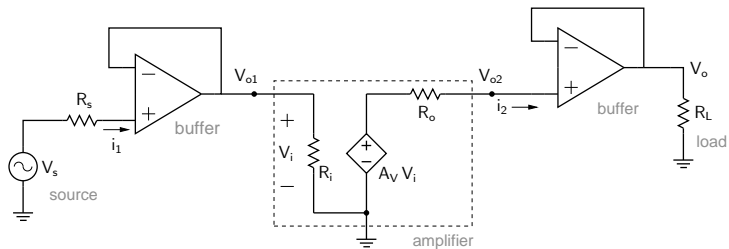

Since the buffer has a large input resistance, $i_1 \approx 0 A$,
and V_+ (on the source side) = $V_s \rightarrow V_{o1} = V_s$.
Similarly, $i_2 \approx 0 A$, and $V_{o2} = A_V V_s$.

Op Amp buffer

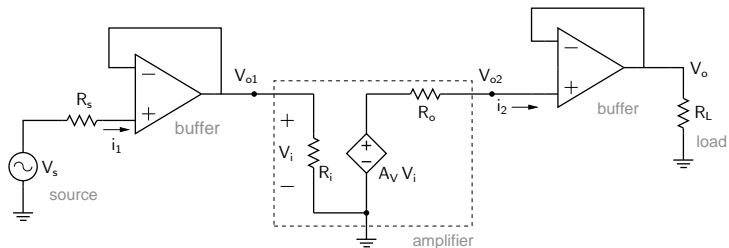


Since the buffer has a large input resistance, $i_1 \approx 0 A$,
and V_+ (on the source side) $= V_s \rightarrow V_{o1} = V_s$.


Similarly, $i_2 \approx 0 A$, and $V_{o2} = A_V V_s$.

Finally, $V_o = V_{o2} = A_V V_s$, as desired, *irresepective* of R_S and R_L .

Op Amp circuits (linear region)

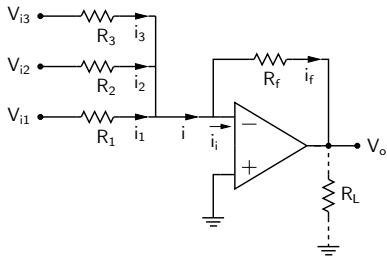


Op Amp circuits (linear region)

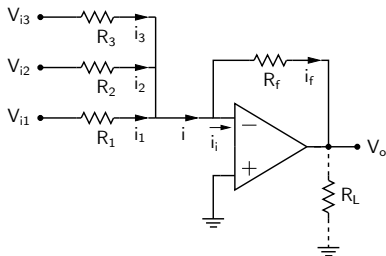

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$


Op Amp circuits (linear region)

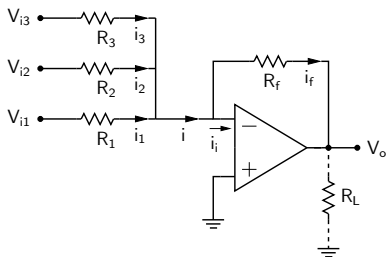

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

Op Amp circuits (linear region)

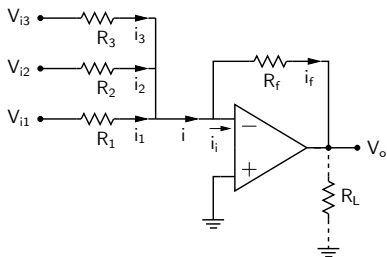


$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

Because of the large input resistance of the Op Amp, $i_i \approx 0 \rightarrow i_f = i$, which gives,

Op Amp circuits (linear region)

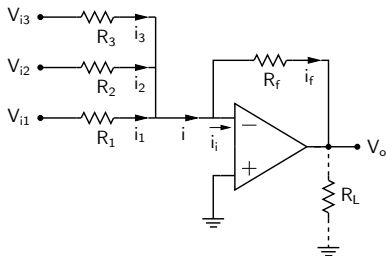

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$


$$i = i_1 + i_2 + i_3 = \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

Because of the large input resistance of the Op Amp, $i_i \approx 0 \rightarrow i_f = i$, which gives,

$$V_o = V_- - i_f R_f = 0 - \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right) R_f = - \left(\frac{R_f}{R_1} V_{i1} + \frac{R_f}{R_2} V_{i2} + \frac{R_f}{R_3} V_{i3} \right),$$

i.e., V_o is a *weighted sum* of V_{i1} , V_{i2} , V_{i3} .

Op Amp circuits (linear region)

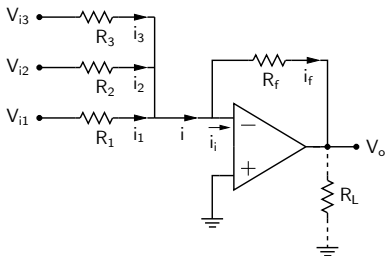

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

Because of the large input resistance of the Op Amp, $i_i \approx 0 \rightarrow i_f = i$, which gives,


$$V_o = V_- - i_f R_f = 0 - \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right) R_f = - \left(\frac{R_f}{R_1} V_{i1} + \frac{R_f}{R_2} V_{i2} + \frac{R_f}{R_3} V_{i3} \right),$$

i.e., V_o is a *weighted sum* of V_{i1} , V_{i2} , V_{i3} .

If $R_1 = R_2 = R_3 = R$, the circuit acts as a summer, giving

$$V_o = -K (V_{i1} + V_{i2} + V_{i3}) \quad \text{with } K = R_f/R.$$

Summer example

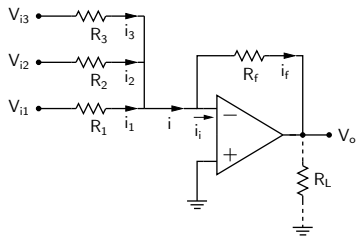


$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$


$$R_f = 2 \text{ k}\Omega$$

$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$

SEQUEL file: ee101_summer.sqproj

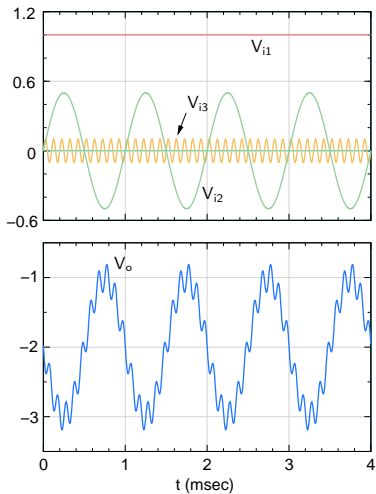

Summer example

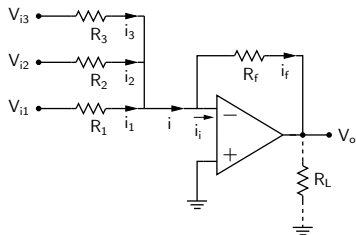


$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$

$$R_f = 2 \text{ k}\Omega$$


$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$

SEQUEL file: ee101_summer.sqproj

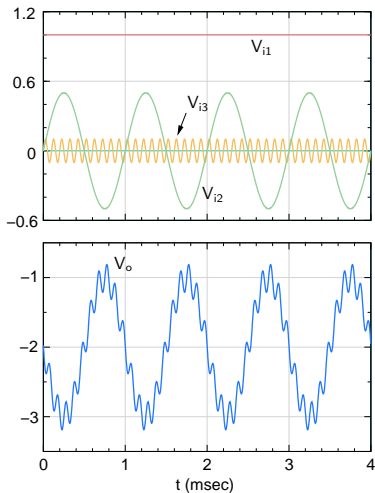

- * Note that the summer also works with DC inputs. This is true about the inverting and non-inverting amplifiers as well.

Summer example

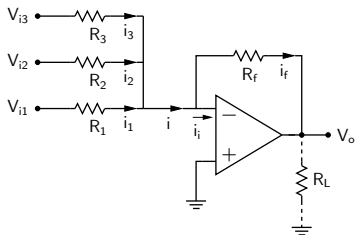


$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$

$$R_f = 2 \text{ k}\Omega$$

$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$

SEQUEL file: ee101_summer.sqproj

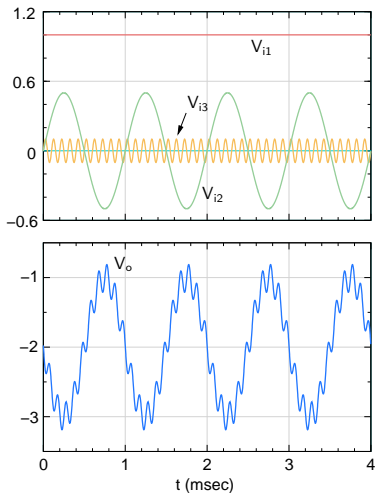

- * Note that the summer also works with DC inputs. This is true about the inverting and non-inverting amplifiers as well.
- * Op Amps make life simpler! Think of adding voltages in any other way.