

## Op-Amp Circuits: Part 2

---




M. B. Patil


[mbpatil@ee.iitb.ac.in](mailto:mbpatil@ee.iitb.ac.in)

[www.ee.iitb.ac.in/~sequel](http://www.ee.iitb.ac.in/~sequel)

Department of Electrical Engineering  
Indian Institute of Technology Bombay

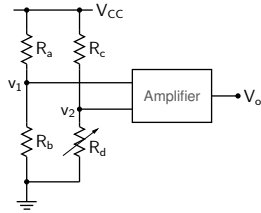
## Common-mode and differential-mode voltages



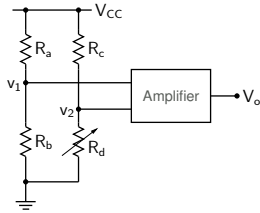

Consider a bridge circuit for sensing temperature, pressure, etc., with  $R_a = R_b = R_c = R$ .

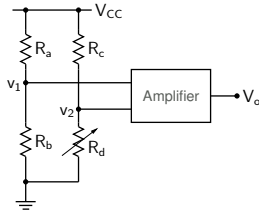
$R_d = R + \Delta R$  varies with the quantity to be measured. Typically,  $\Delta R$  is a small fraction of  $R$ .



Consider a bridge circuit for sensing temperature, pressure, etc., with  $R_a = R_b = R_c = R$ .

$R_d = R + \Delta R$  varies with the quantity to be measured. Typically,  $\Delta R$  is a small fraction of  $R$ .

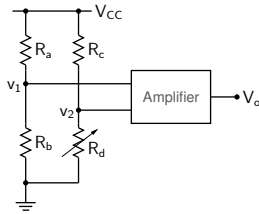The bridge converts  $\Delta R$  to a signal voltage which can then be suitably amplified and used for display or control.




Consider a bridge circuit for sensing temperature, pressure, etc., with  $R_a = R_b = R_c = R$ .

$R_d = R + \Delta R$  varies with the quantity to be measured. Typically,  $\Delta R$  is a small fraction of  $R$ .

The bridge converts  $\Delta R$  to a signal voltage which can then be suitably amplified and used for display or control.

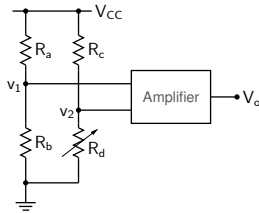Assuming that the amplifier has a large input resistance,




Consider a bridge circuit for sensing temperature, pressure, etc., with  $R_a = R_b = R_c = R$ .

$R_d = R + \Delta R$  varies with the quantity to be measured. Typically,  $\Delta R$  is a small fraction of  $R$ .

The bridge converts  $\Delta R$  to a signal voltage which can then be suitably amplified and used for display or control.

Assuming that the amplifier has a large input resistance,
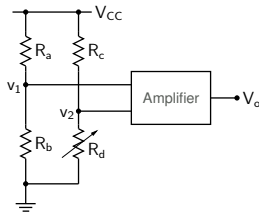
$$v_1 = \frac{R}{R + R} V_{CC} = \frac{1}{2} V_{CC}.$$



Consider a bridge circuit for sensing temperature, pressure, etc., with  $R_a = R_b = R_c = R$ .

$R_d = R + \Delta R$  varies with the quantity to be measured. Typically,  $\Delta R$  is a small fraction of  $R$ .


The bridge converts  $\Delta R$  to a signal voltage which can then be suitably amplified and used for display or control.

Assuming that the amplifier has a large input resistance,

$$v_1 = \frac{R}{R + R} V_{CC} = \frac{1}{2} V_{CC}.$$

$$v_2 = \frac{(R + \Delta R)}{R + (R + \Delta R)} V_{CC} = \frac{1}{2} \frac{1 + x}{1 + x/2} V_{CC} \approx \frac{1}{2} (1 + x) (1 - x/2) V_{CC} = \frac{1}{2} (1 + x/2) V_{CC},$$

where  $x = \Delta R/R$ .

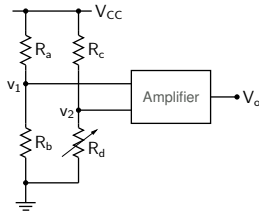

Consider a bridge circuit for sensing temperature, pressure, etc., with  $R_a = R_b = R_c = R$ .

$R_d = R + \Delta R$  varies with the quantity to be measured. Typically,  $\Delta R$  is a small fraction of  $R$ .

The bridge converts  $\Delta R$  to a signal voltage which can then be suitably amplified and used for display or control.

Assuming that the amplifier has a large input resistance,

$$v_1 = \frac{R}{R + R} V_{CC} = \frac{1}{2} V_{CC} .$$

$$v_2 = \frac{(R + \Delta R)}{R + (R + \Delta R)} V_{CC} = \frac{1}{2} \frac{1 + x}{1 + x/2} V_{CC} \approx \frac{1}{2} (1 + x) (1 - x/2) V_{CC} = \frac{1}{2} (1 + x/2) V_{CC} ,$$

where  $x = \Delta R/R$ .


For example, with  $V_{CC} = 15 \text{ V}$ ,  $R = 1 \text{ k}$ ,  $\Delta R = 0.01 \text{ k}$ ,

$$v_1 = 7.5 \text{ V} ,$$

$$v_2 = 7.5 + 0.0375 \text{ V} .$$



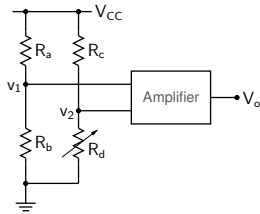
## Common-mode and differential-mode voltages




$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$
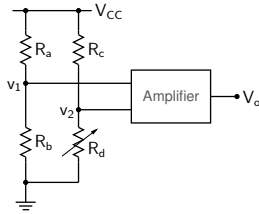
## Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

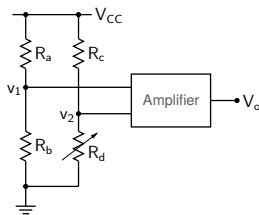The amplifier should only amplify  $v_2 - v_1 = 0.0375 \text{ V}$  (since that is the signal arising from  $\Delta R$ ).



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$


The amplifier should only amplify  $v_2 - v_1 = 0.0375 \text{ V}$  (since that is the signal arising from  $\Delta R$ ).

Definitions:

Given  $v_1$  and  $v_2$ ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$
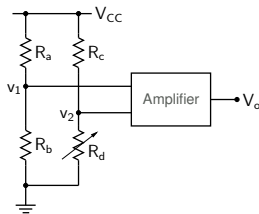
$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify  $v_2 - v_1 = 0.0375 \text{ V}$  (since that is the signal arising from  $\Delta R$ ).

Definitions:


Given  $v_1$  and  $v_2$ ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$

$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$

$v_1$  and  $v_2$  can be rewritten as,
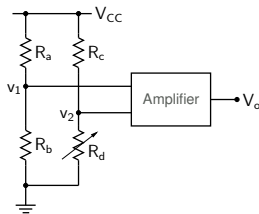
$$v_1 = v_c - v_d/2, \quad v_2 = v_c + v_d/2.$$



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify  $v_2 - v_1 = 0.0375 \text{ V}$  (since that is the signal arising from  $\Delta R$ ).

Definitions:

Given  $v_1$  and  $v_2$ ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$


$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$

$v_1$  and  $v_2$  can be rewritten as,

$$v_1 = v_c - v_d/2, \quad v_2 = v_c + v_d/2.$$

In the above example,  $v_c \approx 7.5 \text{ V}$ ,  $v_d = 37.5 \text{ mV}$ .
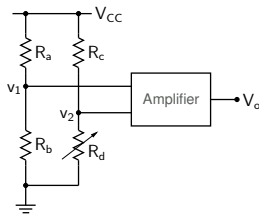
## Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify  $v_2 - v_1 = 0.0375 \text{ V}$  (since that is the signal arising from  $\Delta R$ ).

Definitions:

Given  $v_1$  and  $v_2$ ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$

$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$


$v_1$  and  $v_2$  can be rewritten as,

$$v_1 = v_c - v_d/2, \quad v_2 = v_c + v_d/2.$$


In the above example,  $v_c \approx 7.5 \text{ V}$ ,  $v_d = 37.5 \text{ mV}$ .

Note that the common-mode voltage is quite large compared to the differential-mode voltage.

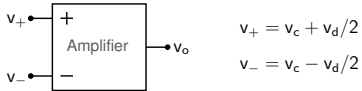This is a common situation in transducer circuits.



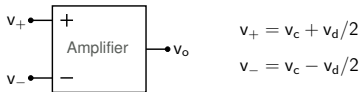An ideal amplifier would only amplify the difference  $(v_+ - v_-)$ , giving  $v_o = A_d (v_+ - v_-) = A_d v_d$ , where  $A_d$  is called the “differential gain” or simply the gain ( $A_V$ ).



An ideal amplifier would only amplify the difference ( $v_+ - v_-$ ), giving

$$v_o = A_d (v_+ - v_-) = A_d v_d,$$


where  $A_d$  is called the “differential gain” or simply the gain ( $A_V$ ).

In practice, the output can also have a common-mode component:

$$v_o = A_d v_d + A_c v_c,$$

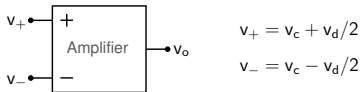where  $A_c$  is called the “common-mode gain”.





An ideal amplifier would only amplify the difference ( $v_+ - v_-$ ), giving

$$v_o = A_d (v_+ - v_-) = A_d v_d,$$

where  $A_d$  is called the “differential gain” or simply the gain ( $A_V$ ).

In practice, the output can also have a common-mode component:


$$v_o = A_d v_d + A_c v_c,$$

where  $A_c$  is called the “common-mode gain”.

The ability of an amplifier to *reject* the common-mode signal is given by the

Common-Mode Rejection Ratio (CMRR):

$$\text{CMRR} = \frac{A_d}{A_c}$$

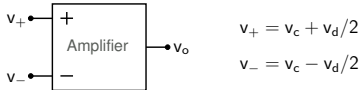

An ideal amplifier would only amplify the difference  $(v_+ - v_-)$ , giving

$$v_o = A_d (v_+ - v_-) = A_d v_d,$$

where  $A_d$  is called the “differential gain” or simply the gain ( $A_V$ ).

In practice, the output can also have a common-mode component:

$$v_o = A_d v_d + A_c v_c,$$

where  $A_c$  is called the “common-mode gain”.


The ability of an amplifier to *reject* the common-mode signal is given by the

Common-Mode Rejection Ratio (CMRR):


$$\text{CMRR} = \frac{A_d}{A_c}$$

For the 741 op-amp, the CMRR is 90 dB ( $\simeq 30,000$ ), which may be considered to be infinite in many applications. In such cases, mismatch between circuit components will determine the overall common-mode rejection performance of the circuit.

## Op-amp circuits (linear region)

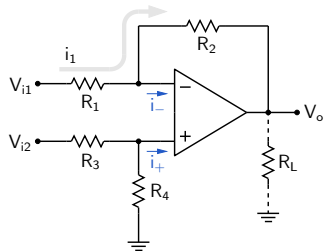


## Op-amp circuits (linear region)

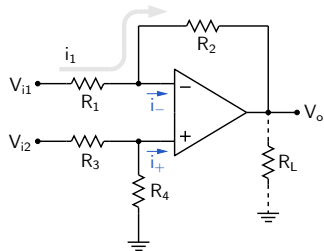

Method 1:

Large input resistance of op-amp  $\rightarrow i_+ = 0$ ,  $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$ .

## Op-amp circuits (linear region)

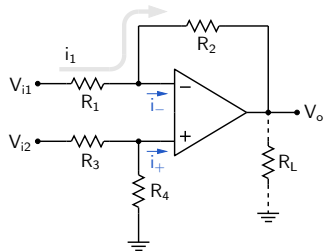


Method 1:

Large input resistance of op-amp  $\rightarrow i_+ = 0$ ,  $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$ .

Since  $V_+ - V_- \approx 0$ ,  $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$ .

## Op-amp circuits (linear region)

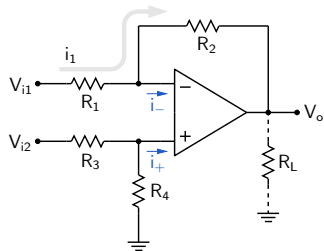


Method 1:

Large input resistance of op-amp  $\rightarrow i_+ = 0$ ,  $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$ .

Since  $V_+ - V_- \approx 0$ ,  $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$ .

$i_- \approx 0 \rightarrow V_o = V_- - i_1 R_2 \approx V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$ .

## Op-amp circuits (linear region)

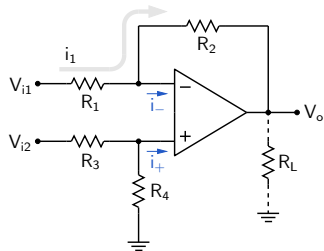

Method 1:

Large input resistance of op-amp  $\rightarrow i_+ = 0$ ,  $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$ .


Since  $V_+ - V_- \approx 0$ ,  $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$ .

$i_- \approx 0 \rightarrow V_o = V_- - i_1 R_2 \approx V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$ .

Substituting for  $V_+$  and selecting  $\frac{R_4}{R_3} = \frac{R_2}{R_1}$ , we get (show this)

$$V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1}).$$

## Op-amp circuits (linear region)

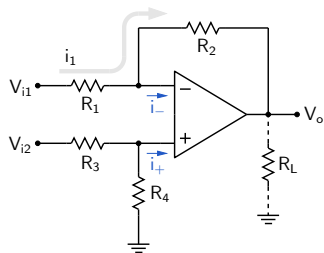

Method 1:

Large input resistance of op-amp  $\rightarrow i_+ = 0$ ,  $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$ .

Since  $V_+ - V_- \approx 0$ ,  $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$ .

$i_- \approx 0 \rightarrow V_o = V_- - i_1 R_2 \approx V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$ .




Substituting for  $V_+$  and selecting  $\frac{R_4}{R_3} = \frac{R_2}{R_1}$ , we get (show this)

$$V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1}).$$

The circuit is a "difference amplifier."






## Difference amplifier

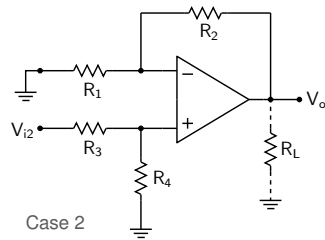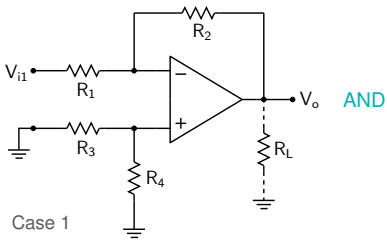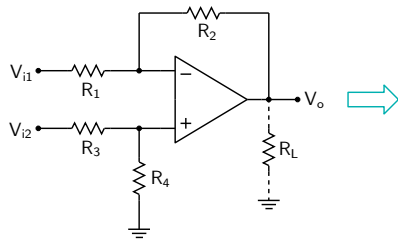

### Method 2:

Since the op-amp is operating in the linear region, we can use superposition:

## Difference amplifier

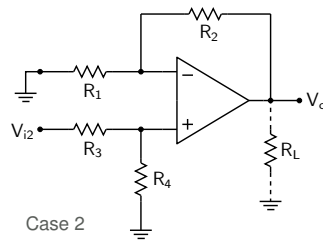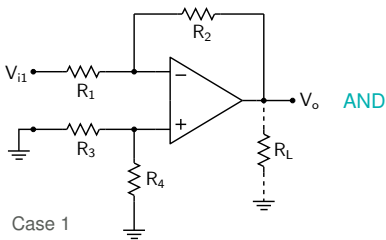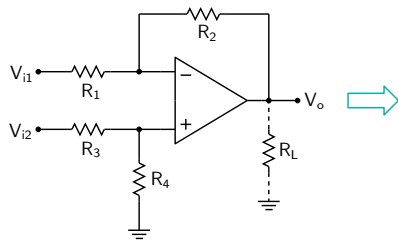


### Method 2:

Since the op-amp is operating in the linear region, we can use superposition:

Case 1: Inverting amplifier (note that  $V_+ = 0\text{ V}$ ).

$$\rightarrow V_{o1} = -\frac{R_2}{R_1} V_{i1}.$$

## Difference amplifier

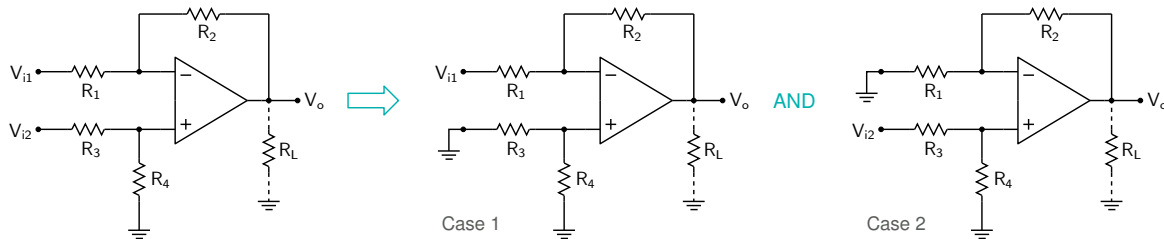

### Method 2:

Since the op-amp is operating in the linear region, we can use superposition:


Case 1: Inverting amplifier (note that  $V_+ = 0\text{ V}$ ).

$$\rightarrow V_{o1} = -\frac{R_2}{R_1} V_{i1}.$$

Case 2: Non-inverting amplifier, with  $V_i = \frac{R_4}{R_3 + R_4} V_{i2}$ .

$$\rightarrow V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2}.$$

## Difference amplifier

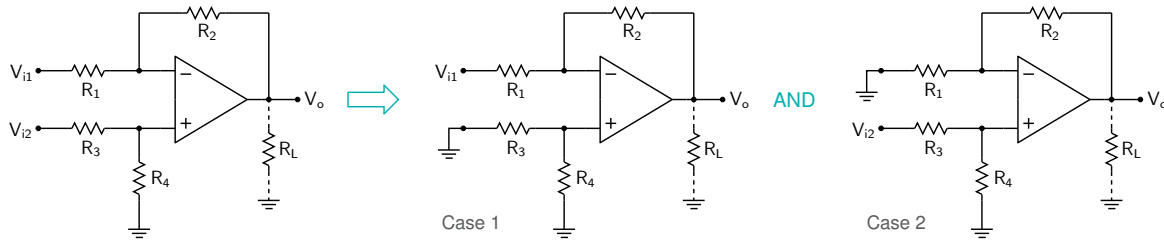

### Method 2:

Since the op-amp is operating in the linear region, we can use superposition:

Case 1: Inverting amplifier (note that  $V_+ = 0$  V).

$$\rightarrow V_{o1} = -\frac{R_2}{R_1} V_{i1}.$$


Case 2: Non-inverting amplifier, with  $V_i = \frac{R_4}{R_3 + R_4} V_{i2}$ .

$$\rightarrow V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2}.$$


The net result is,

$$V_o = V_{o1} + V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1} = \frac{R_2}{R_1} (V_{i2} - V_{i1}), \text{ if } \frac{R_4}{R_3} = \frac{R_2}{R_1}.$$

# Difference amplifier

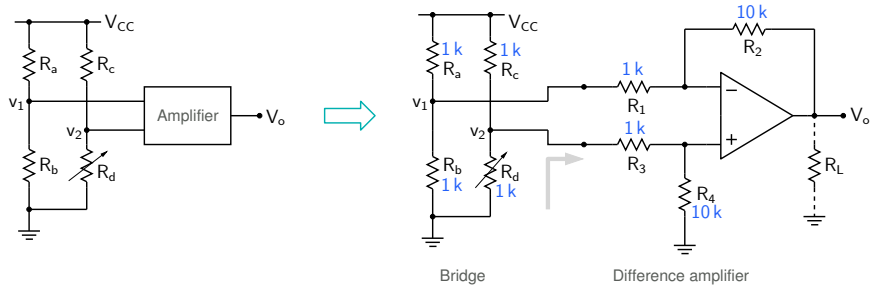


## Difference amplifier

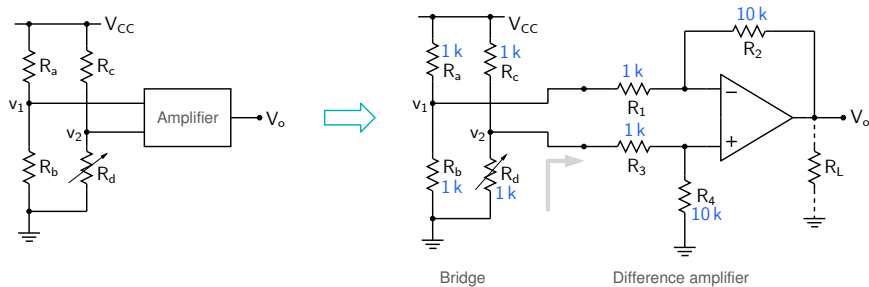

The resistance seen from  $v_2$  is  $(R_3 + R_4)$  which is small enough to cause  $v_2$  to change.  
This is not desirable.

# Difference amplifier

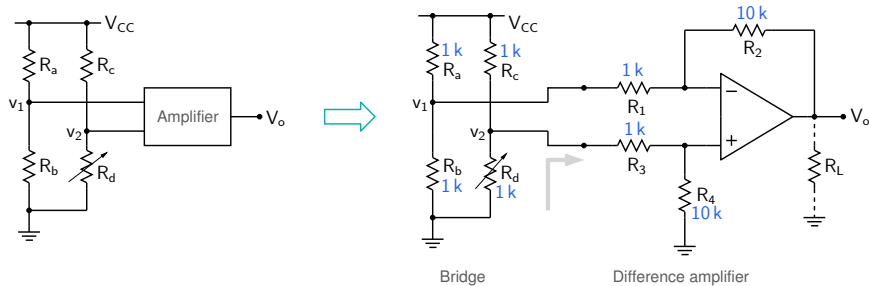


The resistance seen from  $v_2$  is  $(R_3 + R_4)$  which is small enough to cause  $v_2$  to change.

This is not desirable.

→ need to improve the input resistance of the difference amplifier.

# Difference amplifier

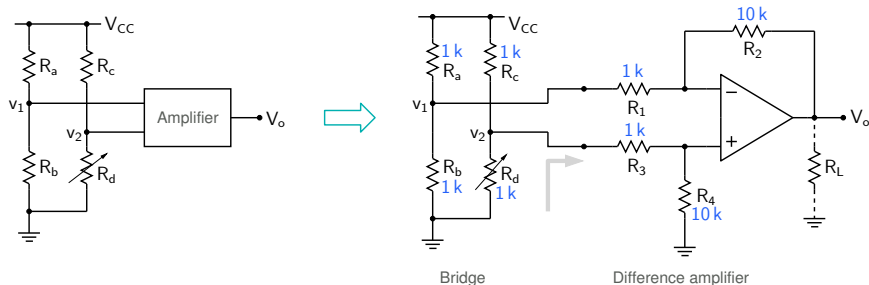

The resistance seen from  $v_2$  is  $(R_3 + R_4)$  which is small enough to cause  $v_2$  to change.


This is not desirable.

→ need to improve the input resistance of the difference amplifier.


We will discuss an improved difference amplifier later. Before we do that, let us discuss another problem with the above difference amplifier which can be important for some applications (next slide).



## Difference amplifier

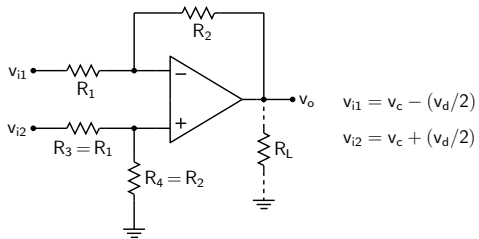


## Difference amplifier

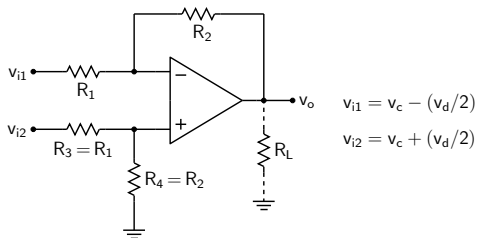

Consider the difference amplifier with  $R_3 = R_1$ ,  $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$ .

The output voltage depends only on the differential-mode signal  $(v_{i2} - v_{i1})$ ,  
i.e.,  $A_c$  (common-mode gain) = 0.

## Difference amplifier

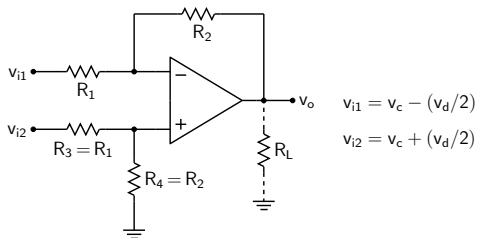


Consider the difference amplifier with  $R_3 = R_1$ ,  $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$ .

The output voltage depends only on the differential-mode signal  $(v_{i2} - v_{i1})$ ,  
i.e.,  $A_c$  (common-mode gain) = 0.

In practice,  $R_3$  and  $R_1$  may not be exactly equal. Let  $R_3 = R_1 + \Delta R$ .

## Difference amplifier

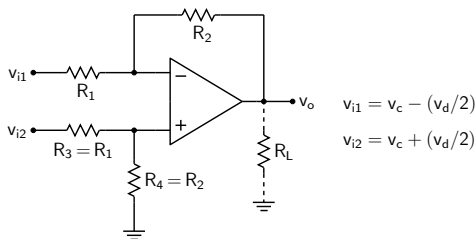


Consider the difference amplifier with  $R_3 = R_1$ ,  $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$ .

The output voltage depends only on the differential-mode signal  $(v_{i2} - v_{i1})$ ,  
i.e.,  $A_c$  (common-mode gain) = 0.

In practice,  $R_3$  and  $R_1$  may not be exactly equal. Let  $R_3 = R_1 + \Delta R$ .

$$\begin{aligned} v_o &= \frac{R_4}{R_3 + R_4} \left( 1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} = \frac{R_2}{R_1 + \Delta R + R_2} \left( 1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} \\ &\simeq \frac{R_2}{R_1} (v_d - x v_c), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this}) \end{aligned}$$

## Difference amplifier

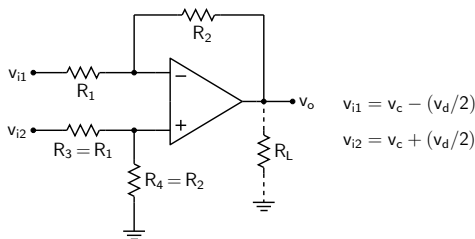

Consider the difference amplifier with  $R_3 = R_1$ ,  $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$ .


The output voltage depends only on the differential-mode signal  $(v_{i2} - v_{i1})$ ,  
i.e.,  $A_c$  (common-mode gain) = 0.

In practice,  $R_3$  and  $R_1$  may not be exactly equal. Let  $R_3 = R_1 + \Delta R$ .

$$\begin{aligned}
 v_o &= \frac{R_4}{R_3 + R_4} \left( 1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} = \frac{R_2}{R_1 + \Delta R + R_2} \left( 1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} \\
 &\simeq \frac{R_2}{R_1} (v_d - x v_c), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this})
 \end{aligned}$$

$$|A_c| = \frac{\Delta R}{R_1 + R_2} \frac{R_2}{R_1} \ll |A_d| = \frac{R_2}{R_1}.$$

## Difference amplifier

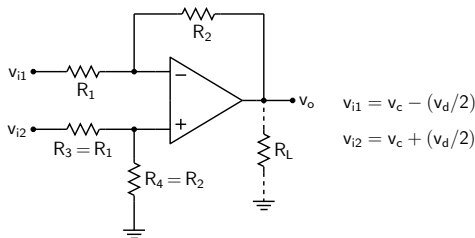

Consider the difference amplifier with  $R_3 = R_1$ ,  $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$ .


The output voltage depends only on the differential-mode signal  $(v_{i2} - v_{i1})$ ,  
i.e.,  $A_c$  (common-mode gain) = 0.

In practice,  $R_3$  and  $R_1$  may not be exactly equal. Let  $R_3 = R_1 + \Delta R$ .

$$\begin{aligned}
 v_o &= \frac{R_4}{R_3 + R_4} \left( 1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} = \frac{R_2}{R_1 + \Delta R + R_2} \left( 1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} \\
 &\simeq \frac{R_2}{R_1} (v_d - x v_c), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this})
 \end{aligned}$$


$|A_c| = \frac{\Delta R}{R_1 + R_2} \frac{R_2}{R_1} \ll |A_d| = \frac{R_2}{R_1}$ . However, since  $v_c$  can be large compared to  $v_d$ , the effect of  $A_c$  cannot be ignored.

## Difference amplifier

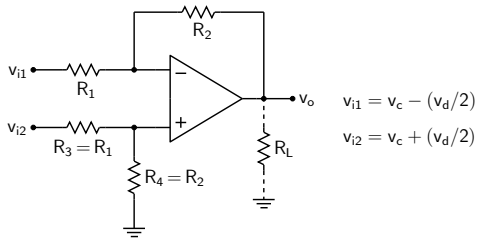

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

## Difference amplifier

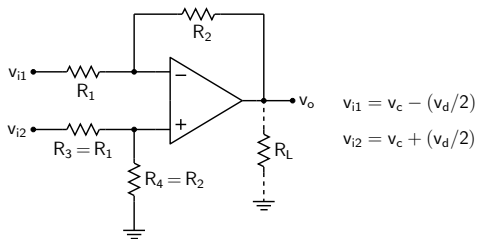


$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

In our earlier example,  $v_c = 7.5 \text{ V}$ ,  $v_d = 0.0375 \text{ V}$ .



## Difference amplifier

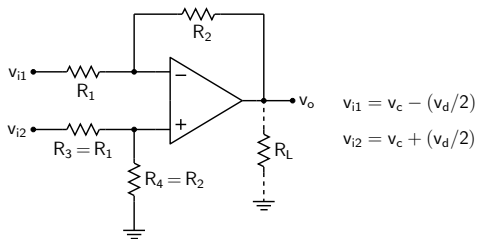


$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

In our earlier example,  $v_c = 7.5 \text{ V}$ ,  $v_d = 0.0375 \text{ V}$ .

With  $R_1 = 1 \text{ k}$ ,  $R_2 = 10 \text{ k}$ ,  $x = \frac{0.01 \text{ k}}{11 \text{ k}} = 0.00091 \rightarrow |A_c| = 0.00091 \frac{10 \text{ k}}{1 \text{ k}} = 0.0091$ ,  $|A_d| = \frac{10 \text{ k}}{1 \text{ k}} = 10$ .

$$|v_o^c| = |A_c v_c| = 0.0091 \times 7.5 = 0.068 \text{ V}.$$

## Difference amplifier

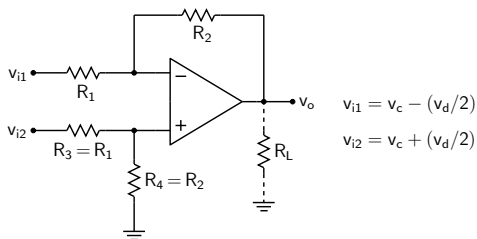

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$


In our earlier example,  $v_c = 7.5 \text{ V}$ ,  $v_d = 0.0375 \text{ V}$ .

$$\text{With } R_1 = 1 \text{ k}, R_2 = 10 \text{ k}, x = \frac{0.01 \text{ k}}{11 \text{ k}} = 0.00091 \rightarrow |A_c| = 0.00091 \frac{10 \text{ k}}{1 \text{ k}} = 0.0091, |A_d| = \frac{10 \text{ k}}{1 \text{ k}} = 10.$$

$$|v_o^c| = |A_c v_c| = 0.0091 \times 7.5 = 0.068 \text{ V}.$$

$$|v_o^d| = |A_d v_d| = 10 \times 0.0375 = 0.375 \text{ V}.$$

## Difference amplifier

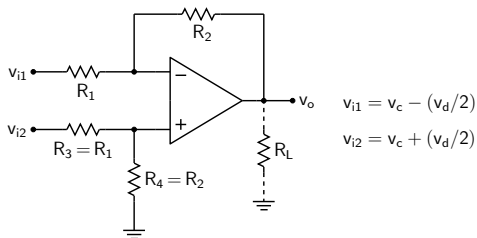

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

In our earlier example,  $v_c = 7.5 \text{ V}$ ,  $v_d = 0.0375 \text{ V}$ .

$$\text{With } R_1 = 1 \text{ k}, R_2 = 10 \text{ k}, x = \frac{0.01 \text{ k}}{11 \text{ k}} = 0.00091 \rightarrow |A_c| = 0.00091 \frac{10 \text{ k}}{1 \text{ k}} = 0.0091, |A_d| = \frac{10 \text{ k}}{1 \text{ k}} = 10.$$

$$|v_o^c| = |A_c v_c| = 0.0091 \times 7.5 = 0.068 \text{ V}.$$


$$|v_o^d| = |A_d v_d| = 10 \times 0.0375 = 0.375 \text{ V}.$$

The (spurious) common-mode contribution is substantial.

If we measure  $v_o$ , we will conclude that  $v_d = \frac{v_o}{A_d}$ , but in reality, it would be different.


→ need a circuit which will drastically reduce the common-mode component at the output.
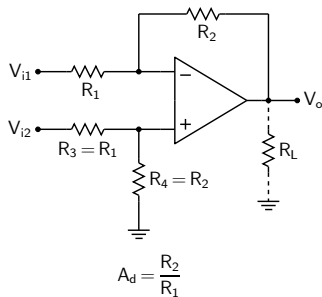
## Difference amplifier: resistance mismatch



$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$
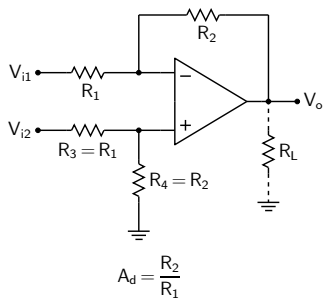
## Difference amplifier: resistance mismatch




$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$A_c = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1}$$
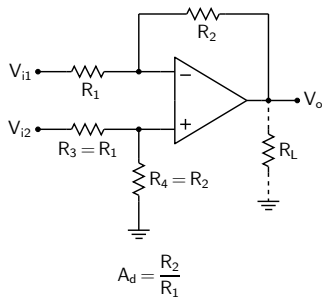
## Difference amplifier: resistance mismatch




$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$
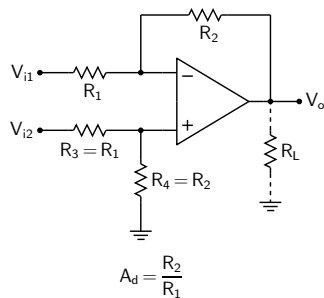
## Difference amplifier: resistance mismatch




$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

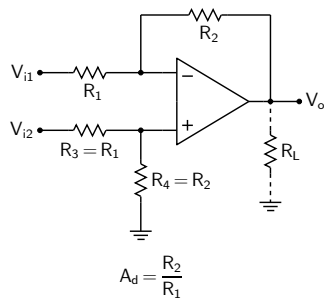Assume ideal op-amp with  $R_1 = R_1^0(1 + x_1)$ , etc. 1 % resistor  $\rightarrow x = 0.01$ .



$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$


$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

Assume ideal op-amp with  $R_1 = R_1^0(1 + x_1)$ , etc. 1 % resistor  $\rightarrow x = 0.01$ .
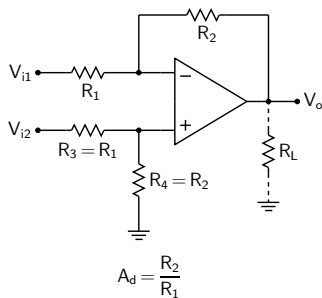
$$\rightarrow A_c = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2^0(1 + x_2)}{R_1^0(1 + x_1)} \times \frac{R_3^0(1 + x_3)}{R_4^0(1 + x_4)}\right).$$





$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$


$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

Assume ideal op-amp with  $R_1 = R_1^0(1 + x_1)$ , etc. 1% resistor  $\rightarrow x = 0.01$ .

$$\rightarrow A_c = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2^0(1 + x_2)}{R_1^0(1 + x_1)} \times \frac{R_3^0(1 + x_3)}{R_4^0(1 + x_4)}\right).$$

Using  $(1 + u_1)(1 + u_2) \approx 1 + u_1 + u_2$  if  $|u_1| \ll 1$ ,  $|u_2| \ll 1$ ,

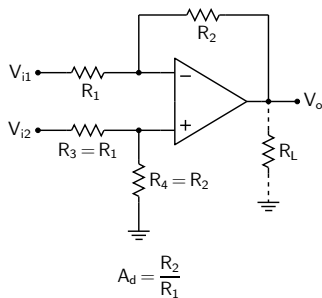

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$


$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

Assume ideal op-amp with  $R_1 = R_1^0(1 + x_1)$ , etc. 1% resistor  $\rightarrow x = 0.01$ .

$$\rightarrow A_c = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2^0(1 + x_2)}{R_1^0(1 + x_1)} \times \frac{R_3^0(1 + x_3)}{R_4^0(1 + x_4)}\right).$$

Using  $(1 + u_1)(1 + u_2) \approx 1 + u_1 + u_2$  if  $|u_1| \ll 1$ ,  $|u_2| \ll 1$ ,

and  $\frac{1}{1 + u} \approx 1 - u$  if  $|u| \ll 1$ ,

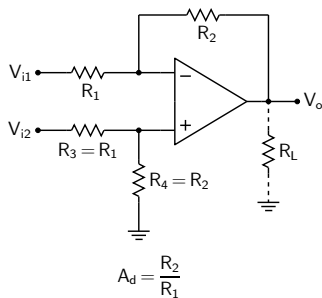

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

Assume ideal op-amp with  $R_1 = R_1^0(1 + x_1)$ , etc. 1% resistor  $\rightarrow x = 0.01$ .


$$\rightarrow A_c = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2^0(1 + x_2)}{R_1^0(1 + x_1)} \times \frac{R_3^0(1 + x_3)}{R_4^0(1 + x_4)}\right).$$

Using  $(1 + u_1)(1 + u_2) \approx 1 + u_1 + u_2$  if  $|u_1| \ll 1$ ,  $|u_2| \ll 1$ ,

and  $\frac{1}{1 + u} \approx 1 - u$  if  $|u| \ll 1$ ,


$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$
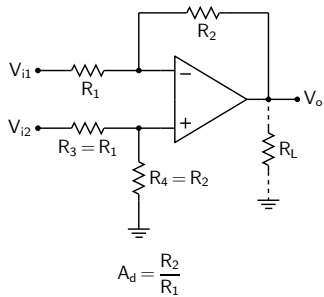
## Difference amplifier: resistance mismatch



$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

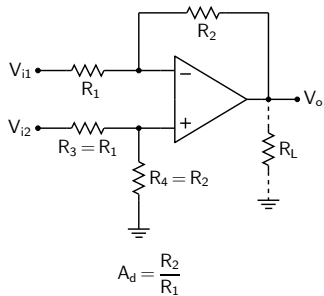
## Difference amplifier: resistance mismatch



$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$
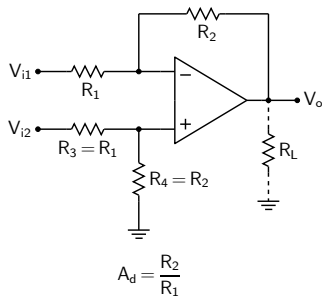
## Difference amplifier: resistance mismatch




$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$

$$(1) \quad R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$
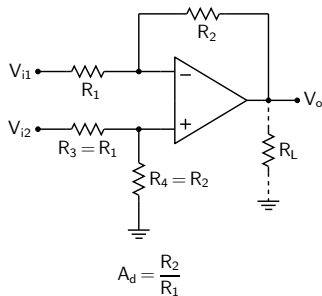
## Difference amplifier: resistance mismatch




$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$

$$(1) R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$

$$A_c = \frac{1}{2} (x_1 - x_2 - x_3 + x_4)$$
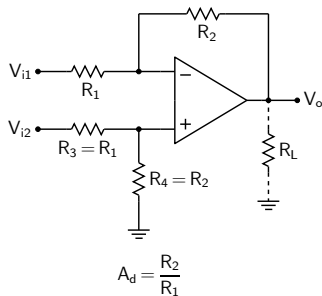
## Difference amplifier: resistance mismatch




$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$

$$(1) R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$
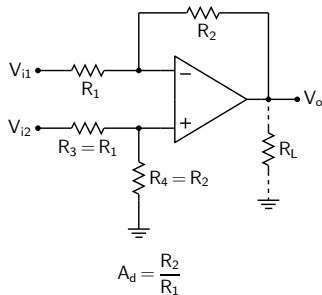
$$\begin{aligned} A_c &= \frac{1}{2} (x_1 - x_2 - x_3 + x_4) \\ &= \frac{1}{2} 4x = 2x \text{ (worst case)} \end{aligned}$$






$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$

$$(1) R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$

$$\begin{aligned} A_c &= \frac{1}{2} (x_1 - x_2 - x_3 + x_4) \\ &= \frac{1}{2} 4x = 2x \text{ (worst case)} \end{aligned}$$
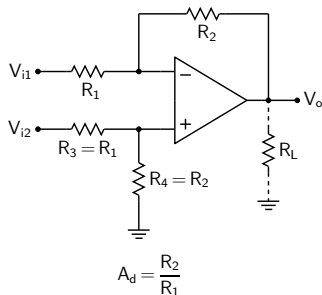
$$(2) R_1^0 \ll R_2^0 \text{ (i.e., } R_3^0 \ll R_4^0)$$



$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$


$$(1) R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$

$$\begin{aligned} A_c &= \frac{1}{2} (x_1 - x_2 - x_3 + x_4) \\ &= \frac{1}{2} 4x = 2x \text{ (worst case)} \end{aligned}$$


$$(2) R_1^0 \ll R_2^0 \text{ (i.e., } R_3^0 \ll R_4^0)$$

$$A_c = \frac{(R_4^0/R_3^0)}{1 + (R_4^0/R_3^0)} (x_1 - x_2 - x_3 + x_4) \approx 4x \text{ (worst case)}$$

## Improved difference amplifier

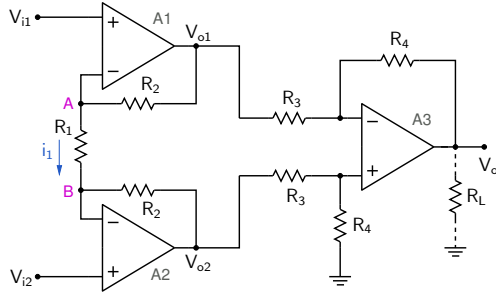


## Improved difference amplifier

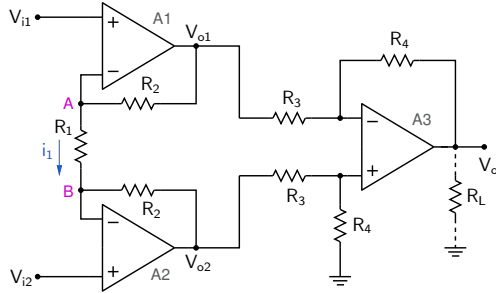

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$


## Improved difference amplifier

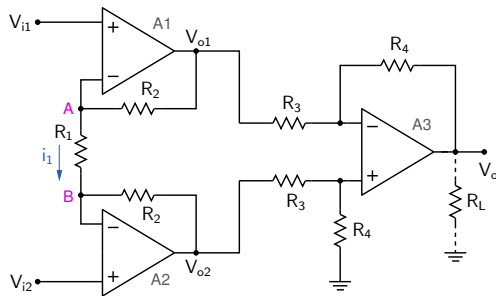

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2  $\Rightarrow$  the current through the two resistors marked  $R_2$  is also equal to  $i_1$ .


## Improved difference amplifier

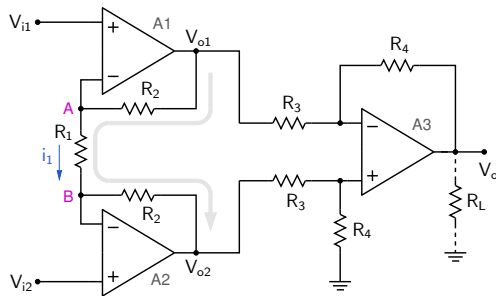

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2  $\Rightarrow$  the current through the two resistors marked  $R_2$  is also equal to  $i_1$ .

## Improved difference amplifier

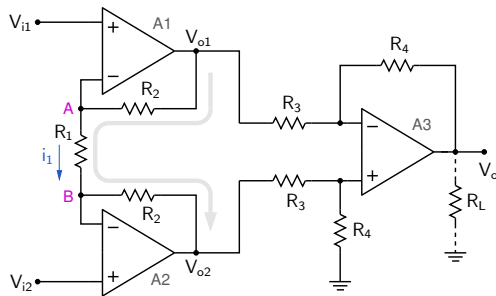


$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2  $\Rightarrow$  the current through the two resistors marked  $R_2$  is also equal to  $i_1$ .

$$V_{o1} - V_{o2} = i_1(R_1 + 2R_2) = \frac{1}{R_1} (V_{i1} - V_{i2}) (R_1 + 2R_2) = (V_{i1} - V_{i2}) \left( 1 + \frac{2R_2}{R_1} \right).$$

## Improved difference amplifier

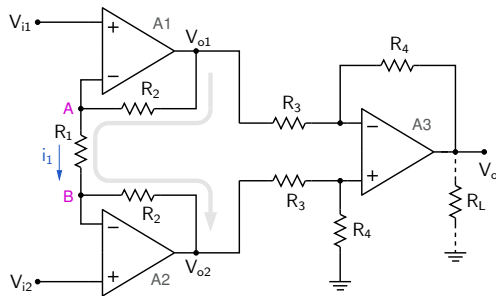

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$


Large input resistance of A1 and A2  $\Rightarrow$  the current through the two resistors marked  $R_2$  is also equal to  $i_1$ .

$$V_{o1} - V_{o2} = i_1(R_1 + 2R_2) = \frac{1}{R_1} (V_{i1} - V_{i2}) (R_1 + 2R_2) = (V_{i1} - V_{i2}) \left( 1 + \frac{2R_2}{R_1} \right).$$

$$\text{Finally, } V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1}) = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (V_{i2} - V_{i1}).$$



## Improved difference amplifier

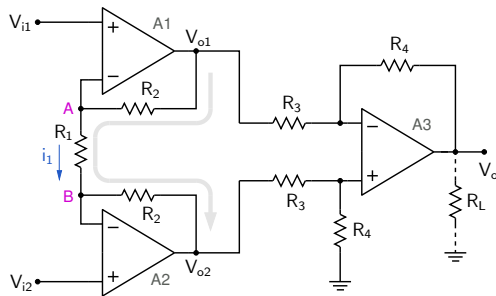

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$


Large input resistance of A1 and A2  $\Rightarrow$  the current through the two resistors marked  $R_2$  is also equal to  $i_1$ .

$$V_{o1} - V_{o2} = i_1(R_1 + 2R_2) = \frac{1}{R_1} (V_{i1} - V_{i2}) (R_1 + 2R_2) = (V_{i1} - V_{i2}) \left(1 + \frac{2R_2}{R_1}\right).$$


$$\text{Finally, } V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1}) = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right) (V_{i2} - V_{i1}).$$

This circuit is known as the “instrumentation amplifier.”

# Instrumentation amplifier

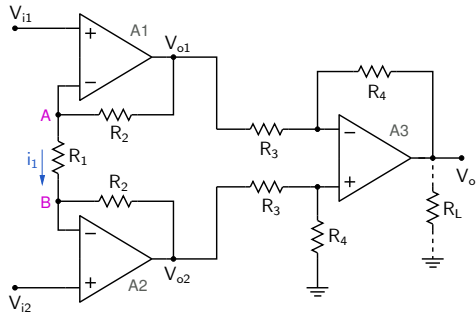


## Instrumentation amplifier

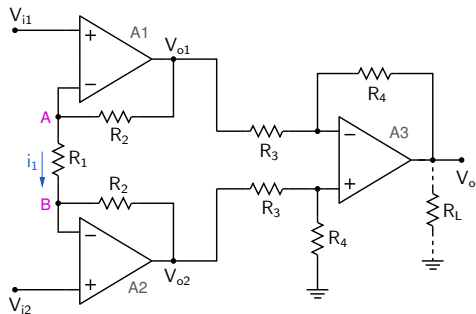


The input resistance seen from  $V_{i1}$  or  $V_{i2}$  is large (since an op-amp has a large input resistance).

## Instrumentation amplifier

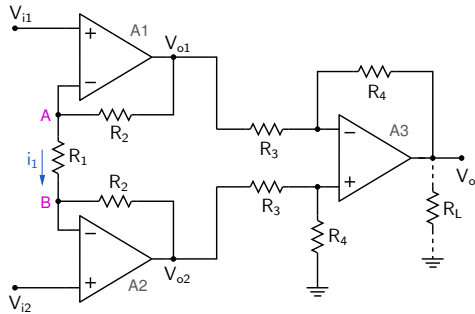


The input resistance seen from  $V_{i1}$  or  $V_{i2}$  is large (since an op-amp has a large input resistance).  
→ the amplifier will not “load” the preceding stage, a desirable feature.

## Instrumentation amplifier

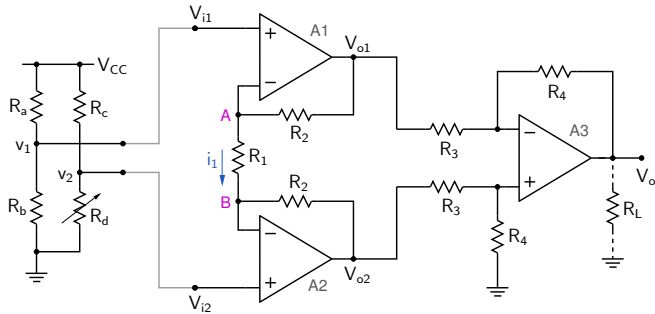

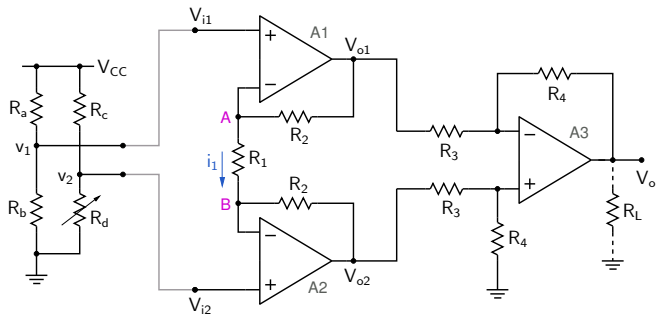The input resistance seen from  $V_{i1}$  or  $V_{i2}$  is large (since an op-amp has a large input resistance).  
→ the amplifier will not “load” the preceding stage, a desirable feature.




The input resistance seen from  $V_{i1}$  or  $V_{i2}$  is large (since an op-amp has a large input resistance).

→ the amplifier will not “load” the preceding stage, a desirable feature.

As a result, the voltages  $v_1$  and  $v_2$  in the bridge circuit will remain essentially the same when the bridge circuit is connected to the instrumentation amplifier.

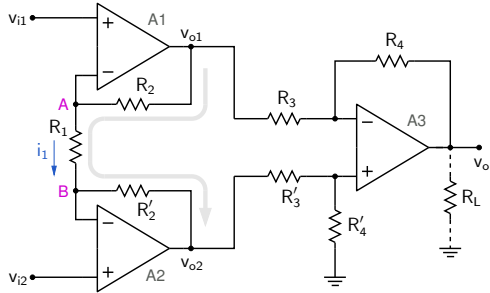
## Instrumentation amplifier: common-mode rejection



$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$
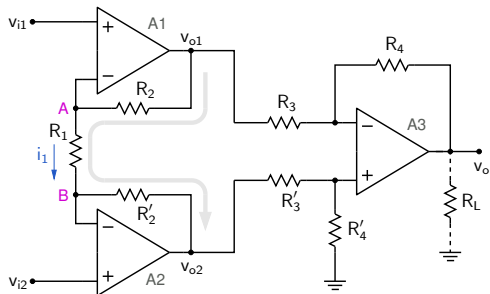
## Instrumentation amplifier: common-mode rejection




$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$

Note that  $v_{o1}$  serves as  $v_{i1}$  for the difference amplifier, and  $v_{o2}$  as  $v_{i2}$ . Let us find the differential-mode and common-mode components associated with  $v_{o1}$  and  $v_{o2}$ .
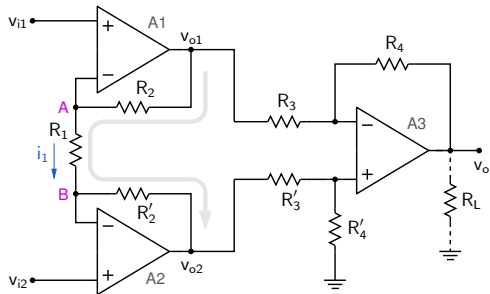
$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$






$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$

Note that  $v_{o1}$  serves as  $v_{i1}$  for the difference amplifier, and  $v_{o2}$  as  $v_{i2}$ . Let us find the differential-mode and common-mode components associated with  $v_{o1}$  and  $v_{o2}$ .

$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$
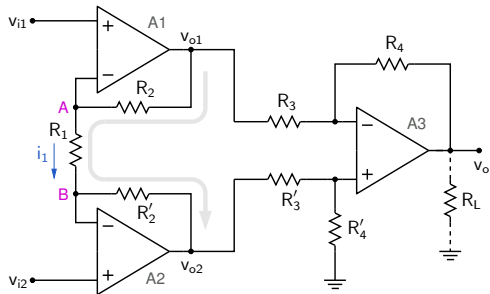
$$v'_{id} = (R_2 + R'_2 + R_1) \frac{1}{R_1} \left[ \left( v_c + \frac{v_d}{2} \right) - \left( v_c - \frac{v_d}{2} \right) \right] = \left( 1 + \frac{R_2 + R'_2}{R_1} \right) v_d.$$



$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$


Note that  $v_{o1}$  serves as  $v_{i1}$  for the difference amplifier, and  $v_{o2}$  as  $v_{i2}$ . Let us find the differential-mode and common-mode components associated with  $v_{o1}$  and  $v_{o2}$ .

$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$

$$v'_{id} = (R_2 + R'_2 + R_1) \frac{1}{R_1} \left[ \left( v_c + \frac{v_d}{2} \right) - \left( v_c - \frac{v_d}{2} \right) \right] = \left( 1 + \frac{R_2 + R'_2}{R_1} \right) v_d.$$

$$v'_{ic} = \frac{1}{2} \left[ \left( v_c - \frac{v_d}{2} \right) + i_1 R_2 + \left( v_c + \frac{v_d}{2} \right) - i_1 R'_2 \right] \approx v_c.$$
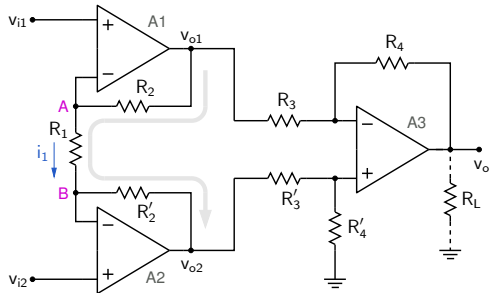
## Instrumentation amplifier: common-mode rejection



$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$


Note that  $v_{o1}$  serves as  $v_{i1}$  for the difference amplifier, and  $v_{o2}$  as  $v_{i2}$ . Let us find the differential-mode and common-mode components associated with  $v_{o1}$  and  $v_{o2}$ .

$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$

$$v'_{id} = (R_2 + R'_2 + R_1) \frac{1}{R_1} \left[ \left( v_c + \frac{v_d}{2} \right) - \left( v_c - \frac{v_d}{2} \right) \right] = \left( 1 + \frac{R_2 + R'_2}{R_1} \right) v_d.$$

$$v'_{ic} = \frac{1}{2} \left[ \left( v_c - \frac{v_d}{2} \right) + i_1 R_2 + \left( v_c + \frac{v_d}{2} \right) - i_1 R'_2 \right] \approx v_c.$$

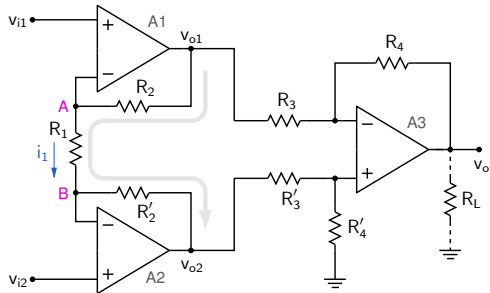→  $v_d$  has got amplified but not  $v_c$  → overall improvement in CMRR.



$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$

Note that  $v_{o1}$  serves as  $v_{i1}$  for the difference amplifier, and  $v_{o2}$  as  $v_{i2}$ . Let us find the differential-mode and common-mode components associated with  $v_{o1}$  and  $v_{o2}$ .

$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$

$$v'_{id} = (R_2 + R'_2 + R_1) \frac{1}{R_1} \left[ \left( v_c + \frac{v_d}{2} \right) - \left( v_c - \frac{v_d}{2} \right) \right] = \left( 1 + \frac{R_2 + R'_2}{R_1} \right) v_d.$$

$$v'_{ic} = \frac{1}{2} \left[ \left( v_c - \frac{v_d}{2} \right) + i_1 R_2 + \left( v_c + \frac{v_d}{2} \right) - i_1 R'_2 \right] \approx v_c.$$

→  $v_d$  has got amplified but not  $v_c$  → overall improvement in CMRR.


(Note that resistor mismatch in the second stage needs to be considered, but it will have a limited effect.)

Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.
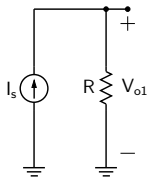
## Current-to-voltage conversion


Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.

Current-to-voltage conversion can be achieved by simply passing the current through a resistor:  $V_{o1} = I_s R$ .




Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.

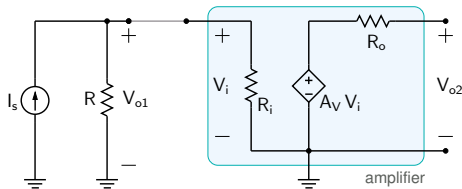Current-to-voltage conversion can be achieved by simply passing the current through a resistor:  $V_{o1} = I_s R$ .




However, this simple approach will not work if the next stage in the circuit (such as an amplifier) has a finite  $R_i$ , since it will modify  $V_{o1}$  to  $V_{o1} = I_s (R_i \parallel R)$ , which is not desirable.

## Current-to-voltage conversion

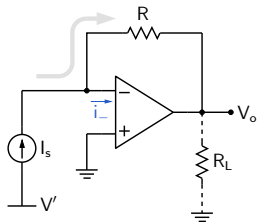




## Current-to-voltage conversion

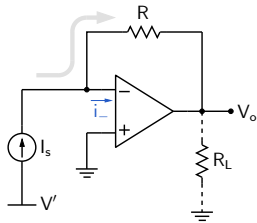

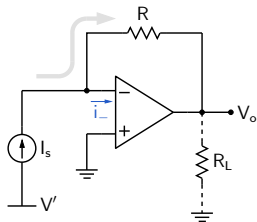
$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$



$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

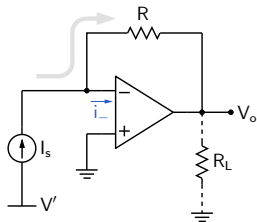
The output voltage is proportional to the source current, *irrespective* of the value of  $R_L$ , i.e., irrespective of the next stage.



$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of  $R_L$ , i.e., irrespective of the next stage.


Example: a photocurrent detector.

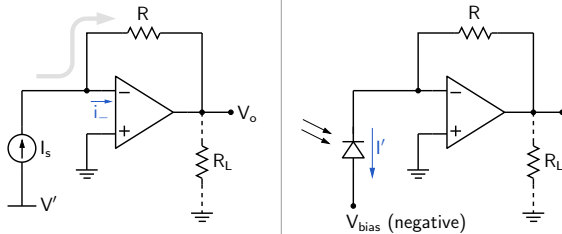

$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of  $R_L$ , i.e., irrespective of the next stage.

Example: a photocurrent detector.

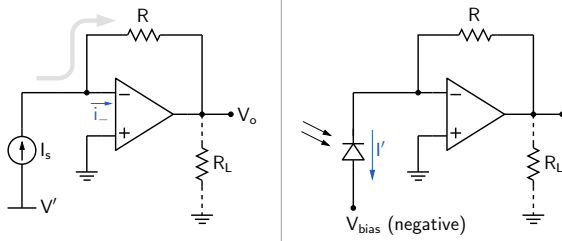


$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of  $R_L$ , i.e., irrespective of the next stage.


Example: a photocurrent detector.

$V_o = I' R$ . (Note: The diode is under a reverse bias, with  $V_n = 0 \text{ V}$  and  $V_p = V_{bias}$ .)

## Op-amp circuits (linear region)

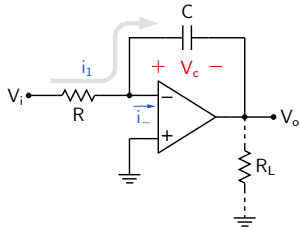


## Op-amp circuits (linear region)

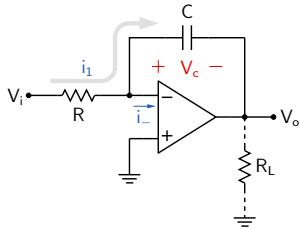

$$V_- \approx V_+ = 0\text{ V} \rightarrow i_1 = V_i/R.$$

## Op-amp circuits (linear region)

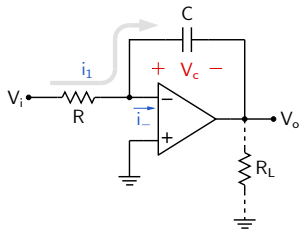


$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R.$$

Since  $i_- \approx 0$ , the current through the capacitor is  $i_1$ .

$$\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_i}{R}.$$



## Op-amp circuits (linear region)

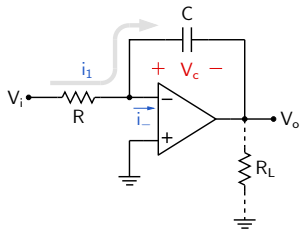


$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i/R.$$

Since  $i_- \approx 0$ , the current through the capacitor is  $i_1$ .

$$\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_i}{R}.$$

$$V_c = V_- - V_o = 0 - V_o = -V_o \rightarrow C \left( -\frac{dV_o}{dt} \right) = \frac{V_i}{R}$$

## Op-amp circuits (linear region)

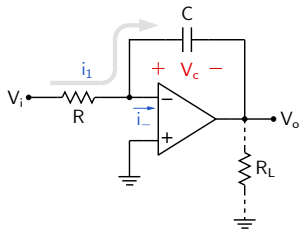

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R.$$

Since  $i_- \approx 0$ , the current through the capacitor is  $i_1$ .



$$\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_i}{R}.$$

$$V_c = V_- - V_o = 0 - V_o = -V_o \rightarrow C \left( -\frac{dV_o}{dt} \right) = \frac{V_i}{R}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$

The circuit works as an integrator.



# Integrator

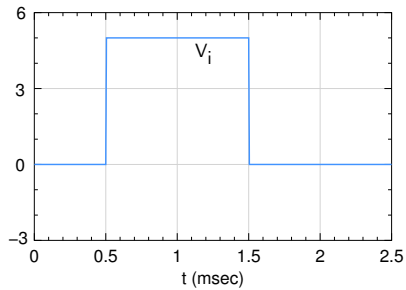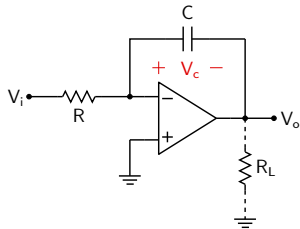

Given:  $R = 10 \text{ k}$ ,  $C = 0.2 \mu\text{F}$ .

If  $V_o = 0 \text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5 \text{ msec}$ ,  $t_1 = 1.5 \text{ msec}$ ).

# Integrator

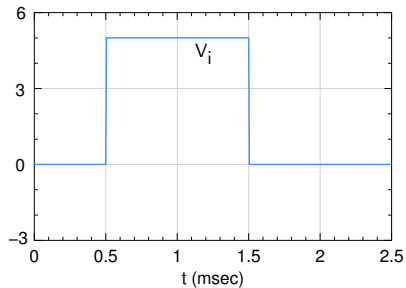
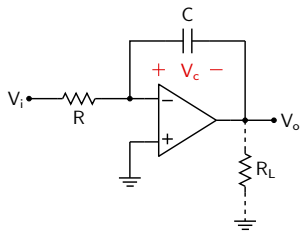


Given:  $R = 10\text{ k}$ ,  $C = 0.2\text{ }\mu\text{F}$ .

If  $V_o = 0\text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5\text{ msec}$ ,  $t_1 = 1.5\text{ msec}$ ).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

# Integrator

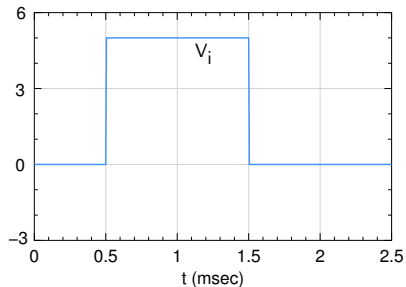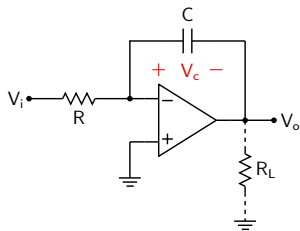



Given:  $R = 10\text{ k}$ ,  $C = 0.2\text{ }\mu\text{F}$ .

If  $V_o = 0\text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5\text{ msec}$ ,  $t_1 = 1.5\text{ msec}$ ).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

$$* \text{ For } t < t_0, V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$$

# Integrator

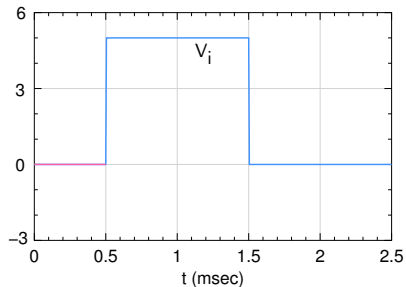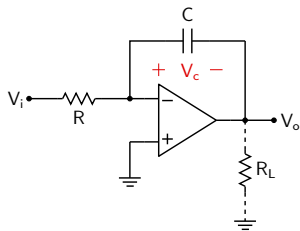



Given:  $R = 10\text{ k}$ ,  $C = 0.2\text{ }\mu\text{F}$ .

If  $V_o = 0\text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5\text{ msec}$ ,  $t_1 = 1.5\text{ msec}$ ).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

$$* \text{ For } t < t_0, V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$$

# Integrator

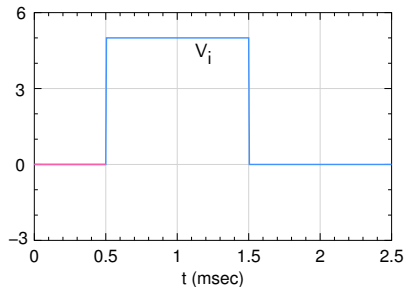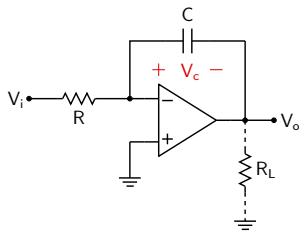

Given:  $R = 10\text{ k}$ ,  $C = 0.2\text{ }\mu\text{F}$ .



If  $V_o = 0\text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5\text{ msec}$ ,  $t_1 = 1.5\text{ msec}$ ).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

$$* \text{ For } t < t_0, V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$$

$$* \text{ For } t_0 < t < t_1, V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow \text{a straight line with a negative slope}$$

# Integrator

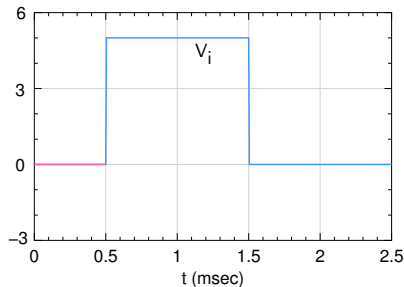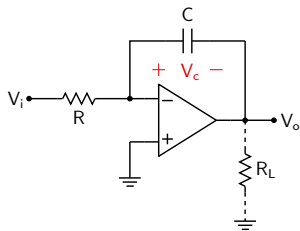

Given:  $R = 10\text{ k}$ ,  $C = 0.2\text{ }\mu\text{F}$ .

If  $V_o = 0\text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5\text{ msec}$ ,  $t_1 = 1.5\text{ msec}$ ).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$



\* For  $t < t_0$ ,  $V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$

\* For  $t_0 < t < t_1$ ,  $V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow$  a straight line with a negative slope

At  $t = t_1$ ,  $V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$



# Integrator

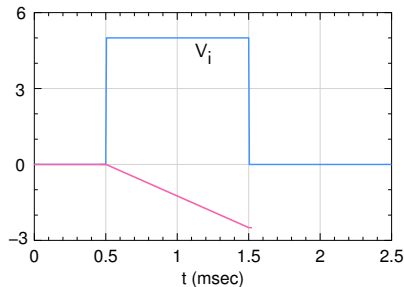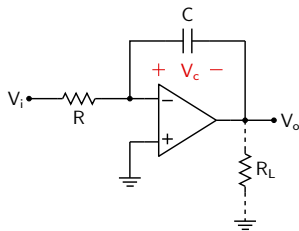

Given:  $R = 10\text{ k}$ ,  $C = 0.2\text{ }\mu\text{F}$ .

If  $V_o = 0\text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5\text{ msec}$ ,  $t_1 = 1.5\text{ msec}$ ).



$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

\* For  $t < t_0$ ,  $V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$

\* For  $t_0 < t < t_1$ ,  $V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow$  a straight line with a negative slope

At  $t = t_1$ ,  $V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$

# Integrator

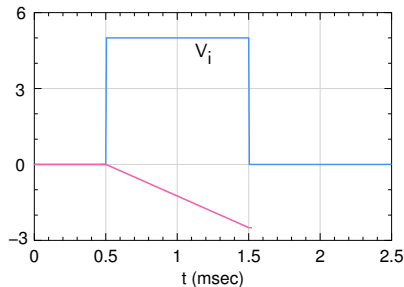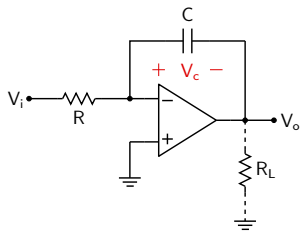

Given:  $R = 10\text{ k}$ ,  $C = 0.2\text{ }\mu\text{F}$ .

If  $V_o = 0\text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5\text{ msec}$ ,  $t_1 = 1.5\text{ msec}$ ).



$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

\* For  $t < t_0$ ,  $V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$

\* For  $t_0 < t < t_1$ ,  $V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow$  a straight line with a negative slope

$$\text{At } t = t_1, V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$$

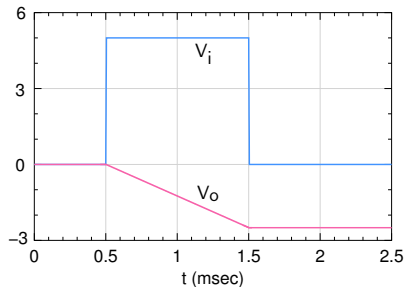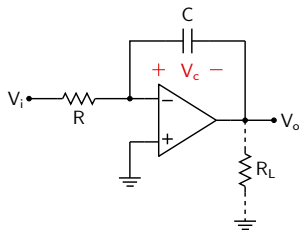\* For  $t > t_1$ ,  $V_o(t)$  remains constant since  $V_i = 0\text{ V}$ .



Given:  $R = 10\text{ k}$ ,  $C = 0.2\text{ }\mu\text{F}$ .

If  $V_o = 0\text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5\text{ msec}$ ,  $t_1 = 1.5\text{ msec}$ ).



$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

$$* \text{ For } t < t_0, V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$$

$$* \text{ For } t_0 < t < t_1, V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow \text{a straight line with a negative slope}$$

$$\text{At } t = t_1, V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$$
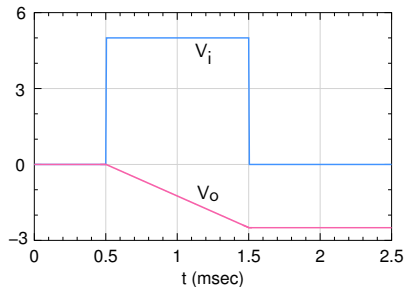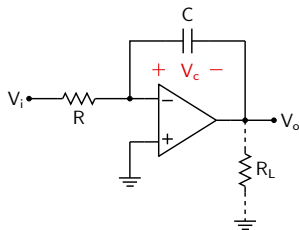
$$* \text{ For } t > t_1, V_o(t) \text{ remains constant since } V_i = 0\text{ V}.$$



Given:  $R = 10\text{ k}$ ,  $C = 0.2\text{ }\mu\text{F}$ .

If  $V_o = 0\text{ V}$  at  $t = 0$ , find  $V_o(t)$  (Let  $t_0 = 0.5\text{ msec}$ ,  $t_1 = 1.5\text{ msec}$ ).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

$$* \text{ For } t < t_0, V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$$



$$* \text{ For } t_0 < t < t_1, V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow \text{a straight line with a negative slope}$$

$$\text{At } t = t_1, V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$$



$$* \text{ For } t > t_1, V_o(t) \text{ remains constant since } V_i = 0\text{ V}.$$

SEQUEL file: ee101\_integrator\_1.sqproj



# Integrator

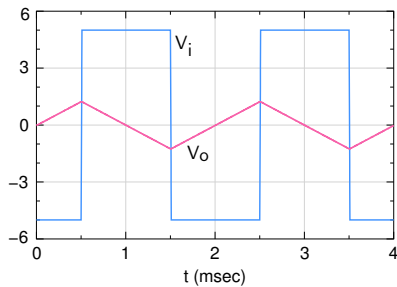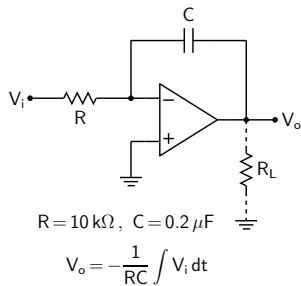

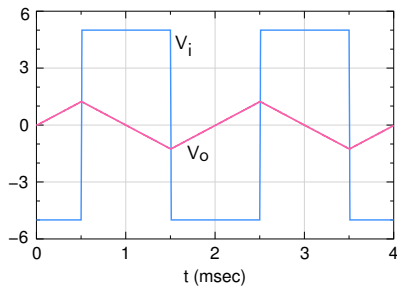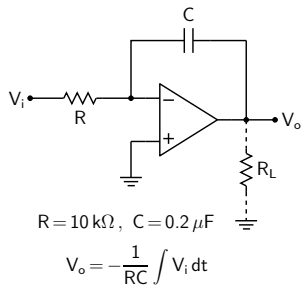\* An integrator can be used to convert a square wave to a triangle wave.



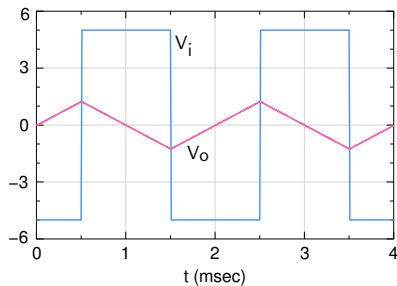
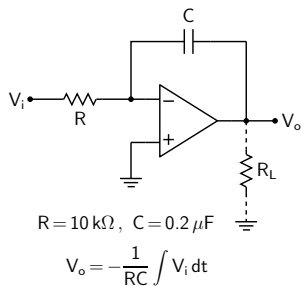
- \* An integrator can be used to convert a square wave to a triangle wave.
- \* In practice, the circuit needs a small modification, as discussed in the following.



- \* An integrator can be used to convert a square wave to a triangle wave.
- \* In practice, the circuit needs a small modification, as discussed in the following.





SEQUEL file: ee101\_integrator\_2.sqproj

## Practical op-amps: Offset voltage



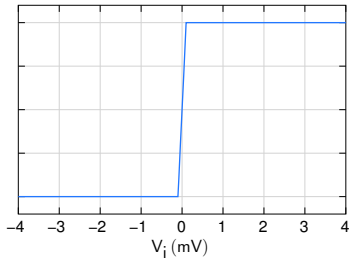
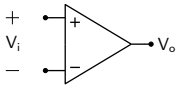




## Practical op-amps: Offset voltage

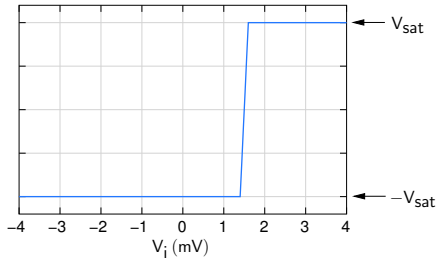
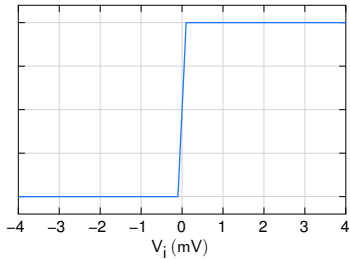
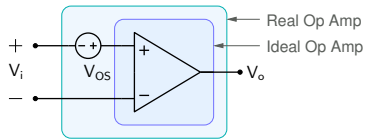
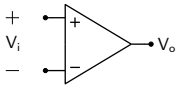


## Practical op-amps: Offset voltage

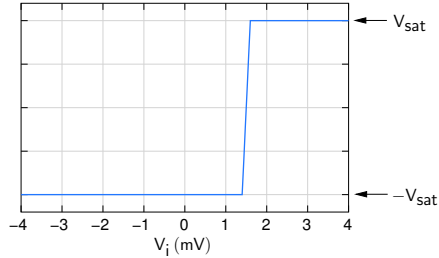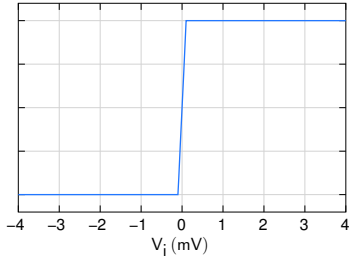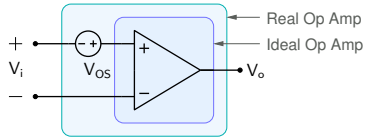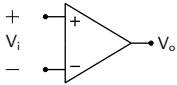

For the real op-amp,  $V_o = A_V((V_+ + V_{os}) - V_-)$ .





## Practical op-amps: Offset voltage

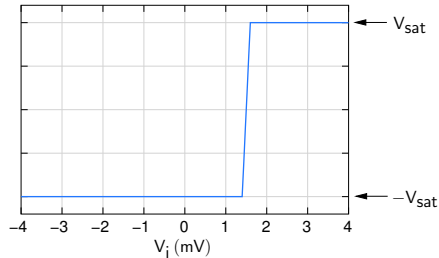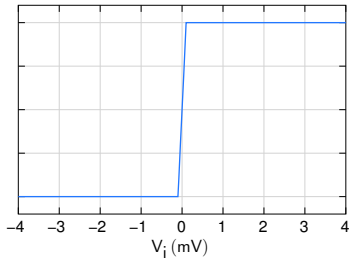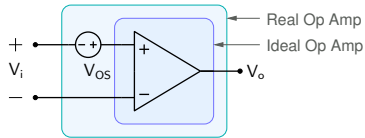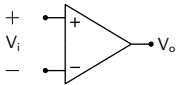

For the real op-amp,  $V_o = A_V((V_+ + V_{OS}) - V_-)$ .

For  $V_o = 0$  V,  $V_+ + V_{OS} - V_- = 0 \rightarrow V_i = V_+ - V_- = -V_{OS}$ .

## Practical op-amps: Offset voltage

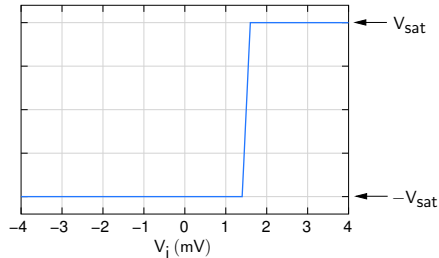
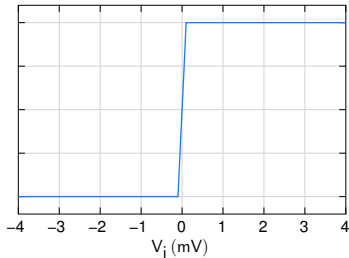
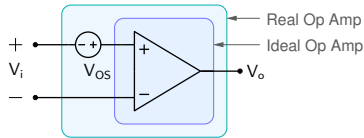
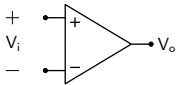


For the real op-amp,  $V_o = A_V((V_+ + V_{OS}) - V_-)$ .

For  $V_o = 0$  V,  $V_+ + V_{OS} - V_- = 0 \rightarrow V_i = V_+ - V_- = -V_{OS}$ .

$V_o$  versus  $V_i$  curve gets shifted (Note:  $V_{OS}$  is negative in the above example).

## Practical op-amps: Offset voltage

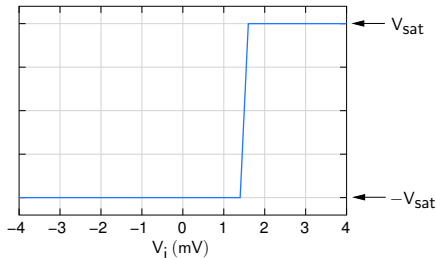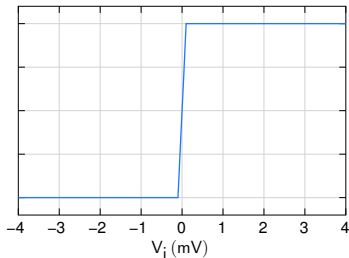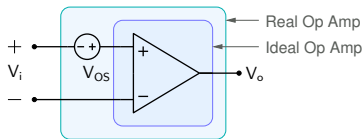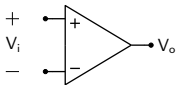


For the real op-amp,  $V_o = A_V((V_+ + V_{OS}) - V_-)$ .

For  $V_o = 0$  V,  $V_+ + V_{OS} - V_- = 0 \rightarrow V_i = V_+ - V_- = -V_{OS}$ .


$V_o$  versus  $V_i$  curve gets shifted (Note:  $V_{OS}$  is negative in the above example).

741:  $-6 \text{ mV} < V_{OS} < 6 \text{ mV}$ , OP-77:  $-50 \mu\text{V} < V_{OS} < 50 \mu\text{V}$ .
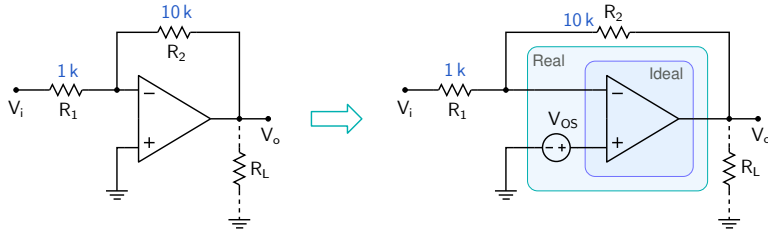
## Effect of $V_{OS}$ : inverting amplifier



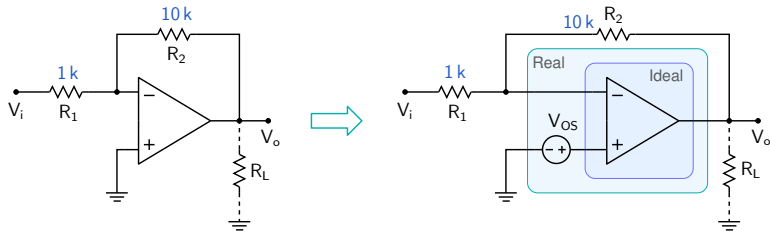
## Effect of $V_{OS}$ : inverting amplifier



By superposition,  $V_o = -\frac{R_2}{R_1} V_i + V_{OS} \left(1 + \frac{R_2}{R_1}\right).$
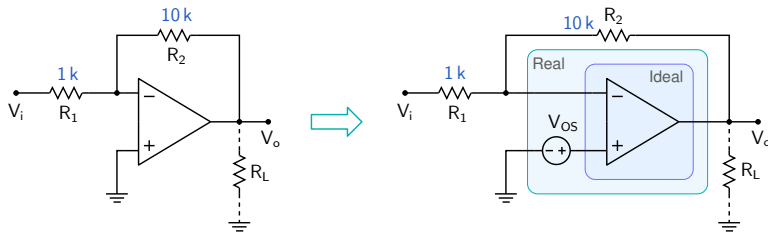
## Effect of $V_{OS}$ : inverting amplifier




By superposition,  $V_o = -\frac{R_2}{R_1} V_i + V_{OS} \left(1 + \frac{R_2}{R_1}\right)$ .

For  $V_{OS} = 2\text{ mV}$ , the contribution from  $V_{OS}$  to  $V_o$  is  $22\text{ mV}$ ,


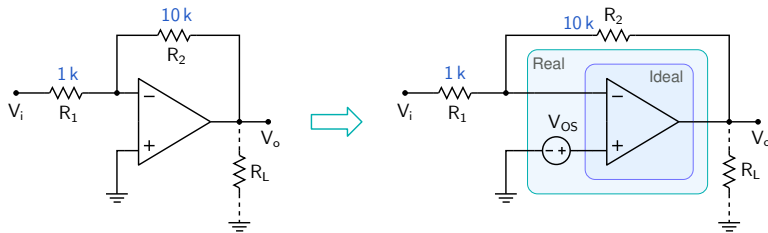
## Effect of $V_{OS}$ : inverting amplifier





By superposition,  $V_o = -\frac{R_2}{R_1} V_i + V_{OS} \left(1 + \frac{R_2}{R_1}\right)$ .

For  $V_{OS} = 2\text{ mV}$ , the contribution from  $V_{OS}$  to  $V_o$  is  $22\text{ mV}$ ,

i.e., a DC shift of  $22\text{ mV}$ .


## Effect of $V_{OS}$ : integrator

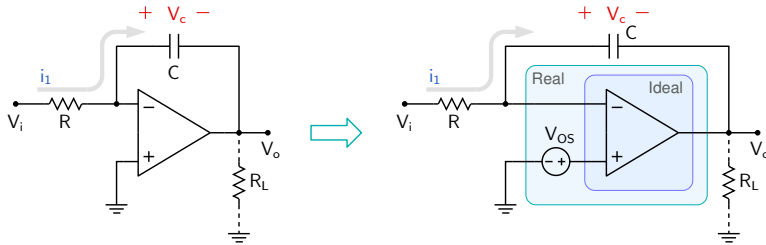

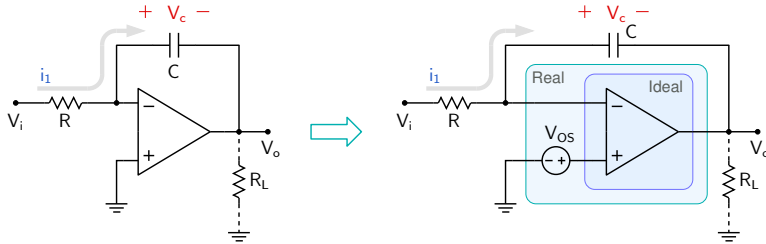

$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$


## Effect of $V_{OS}$ : integrator

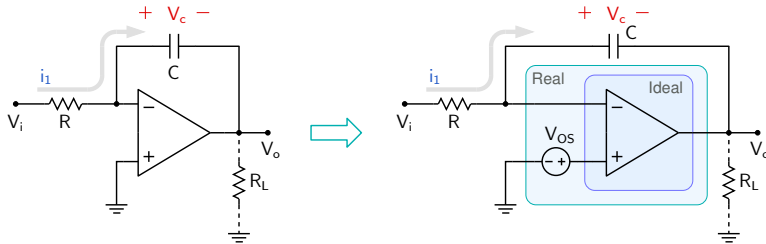

$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$

$$\text{i.e., } V_c = \frac{1}{RC} \int (V_i - V_{OS}) dt.$$

## Effect of $V_{OS}$ : integrator

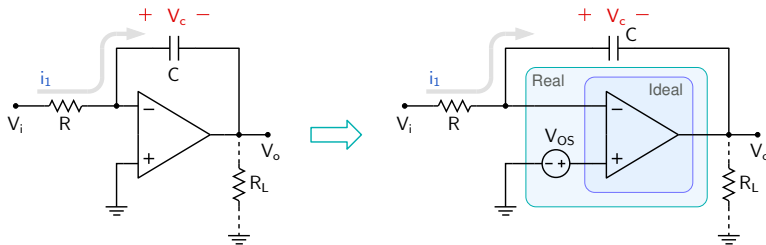


$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$

$$\text{i.e., } V_c = \frac{1}{RC} \int (V_i - V_{OS}) dt.$$

Even with  $V_i = 0$  V,  $V_c$  will keep rising or falling (depending on the sign of  $V_{OS}$ ).

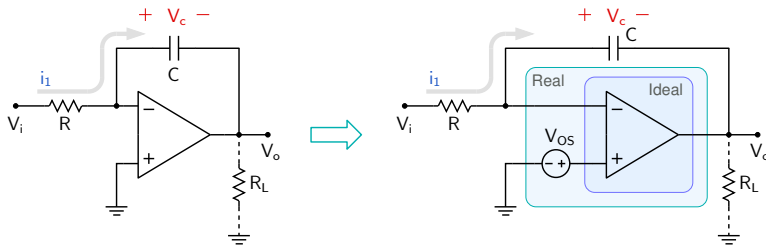Eventually, the Op Amp will be driven into saturation.



$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$



$$\text{i.e., } V_c = \frac{1}{RC} \int (V_i - V_{OS}) dt.$$


Even with  $V_i = 0$  V,  $V_c$  will keep rising or falling (depending on the sign of  $V_{OS}$ ).

Eventually, the Op Amp will be driven into saturation.


→ need to address this issue!
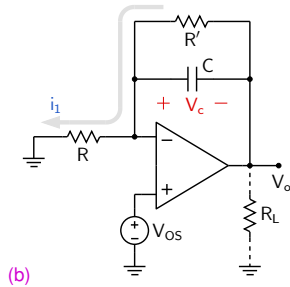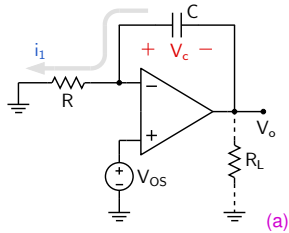
## Effect of $V_{OS}$ : integrator with $V_i = 0$



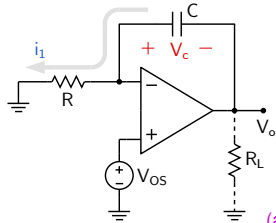

(a)

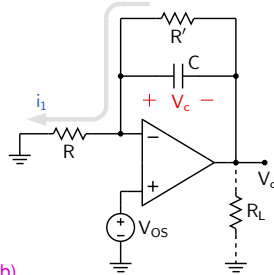


(b)


$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$
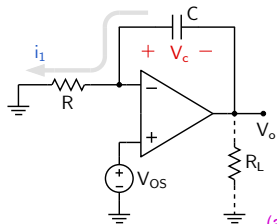
$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$





(a)

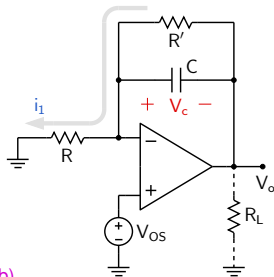


(b)

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$


$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$

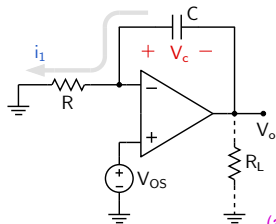(b) There is a DC path for the current.

$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$



(a)

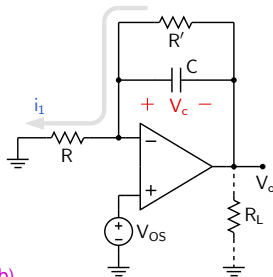

(b)

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$


$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$

(b) There is a DC path for the current.


$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$

$R'$  should be small enough to have a negligible effect on  $V_o$ .
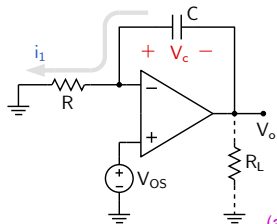
## Effect of $V_{OS}$ : integrator with $V_i = 0$



(a)

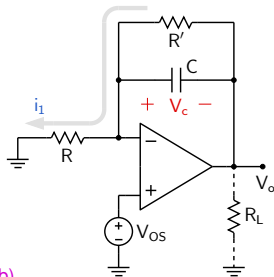

(b)

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$


$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$

(b) There is a DC path for the current.


$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$

$R'$  should be small enough to have a negligible effect on  $V_o$ .

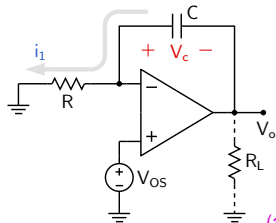However,  $R'$  must be large enough to ensure that the circuit still functions as an integrator.



(a)

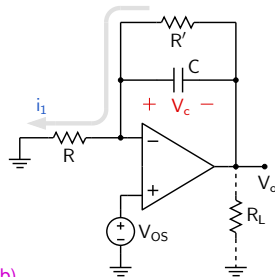

(b)

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$

$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$

(b) There is a DC path for the current.


$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$

$R'$  should be small enough to have a negligible effect on  $V_o$ .


However,  $R'$  must be large enough to ensure that the circuit still functions as an integrator.

$\rightarrow R' \gg 1/\omega C$  at the frequency of interest.

## Op-amp 741: offset null


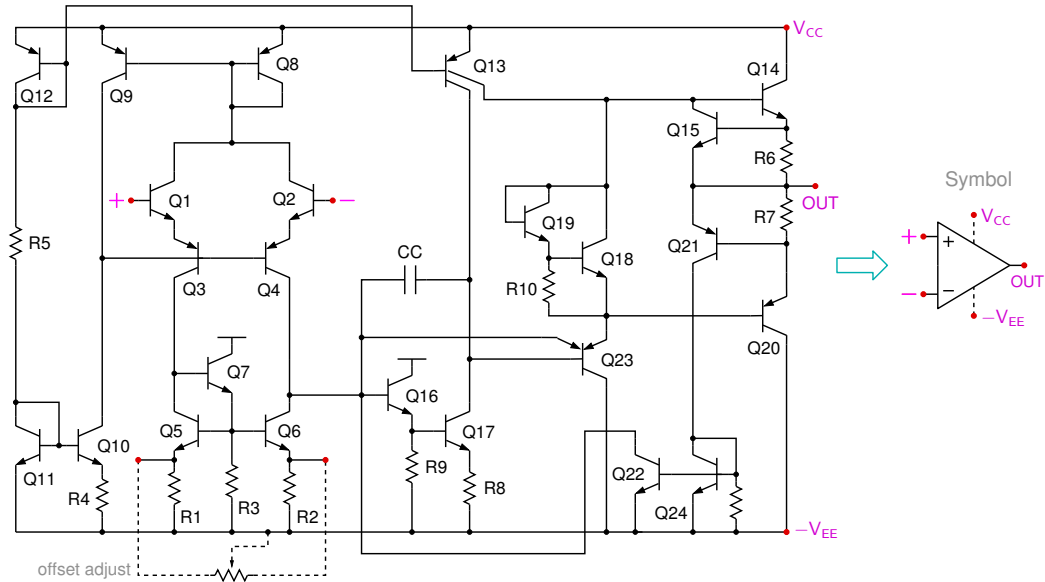


## Input bias currents

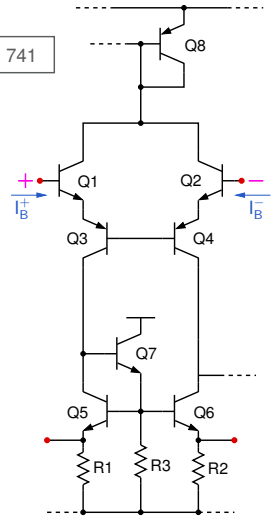



# Input bias currents

741

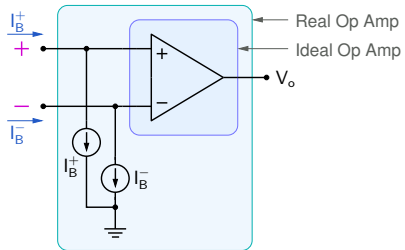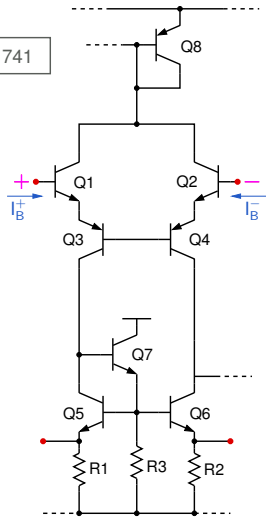

# Input bias currents

741

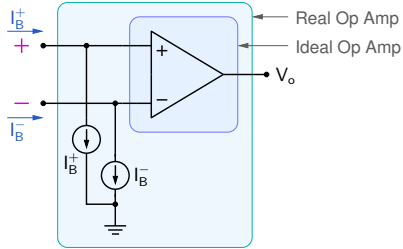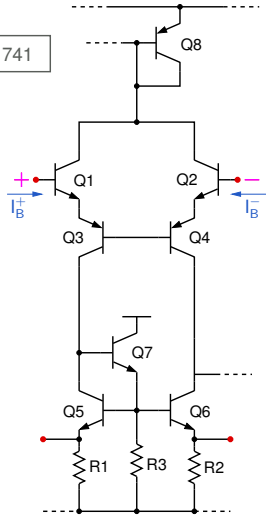



$I_B^+$  and  $I_B^-$  are generally not equal.

$|I_B^+ - I_B^-|$  : "offset current" ( $I_{OS}$ )

$(I_B^+ + I_B^-)/2$  : "bias current" ( $I_B$ )



# Input bias currents

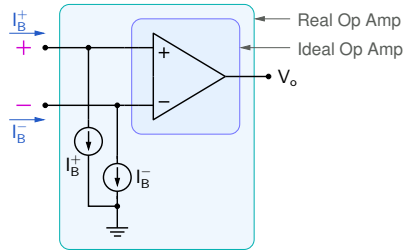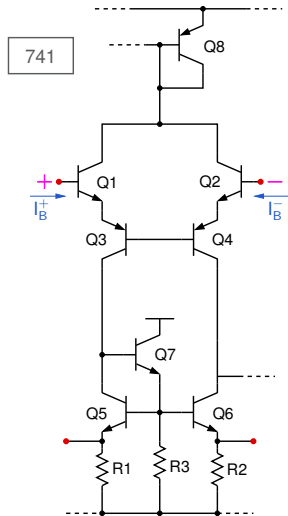


Typical values


Op-Amp	$I_B$	$I_{OS}$	$V_{OS}$	Type
741	80 nA	20 nA	1 mV	BJT input
OP77	1.2 nA	0.3 nA	$10 \mu V$	BJT input
411	50 pA	25 pA	0.8 mV	FET input

$I_B^+$  and  $I_B^-$  are generally not equal.  
 $|I_B^+ - I_B^-|$  : "offset current" ( $I_{OS}$ )  
 $(I_B^+ + I_B^-)/2$  : "bias current" ( $I_B$ )
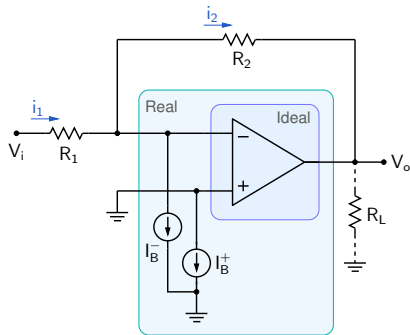
## Effect of bias currents: inverting amplifier



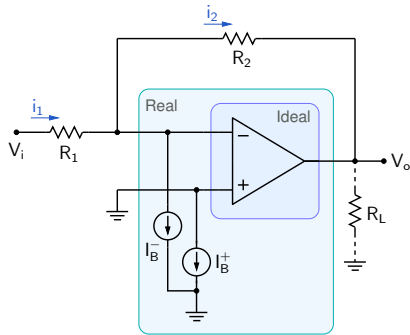
## Effect of bias currents: inverting amplifier



Assume that the op-amp is ideal in other respects (including  $V_{OS} = 0$  V).

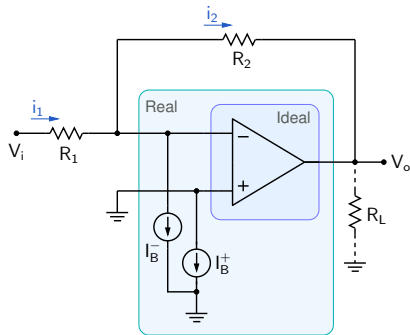
## Effect of bias currents: inverting amplifier



Assume that the op-amp is ideal in other respects (including  $V_{OS} = 0\text{ V}$ ).

$$V_- \approx V_+ = 0\text{ V} \rightarrow i_1 = V_i / R_1.$$
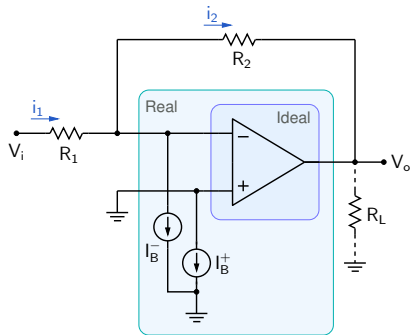
## Effect of bias currents: inverting amplifier




Assume that the op-amp is ideal in other respects (including  $V_{OS} = 0\text{ V}$ ).

$$V_- \approx V_+ = 0\text{ V} \rightarrow i_1 = V_i / R_1.$$

$$i_2 = i_1 - I_B^- \rightarrow V_o = V_- - i_2 R_2 = 0 - \left( \frac{V_i}{R_1} - I_B^- \right) R_2 = -\frac{R_2}{R_1} V_i + I_B^- R_2,$$
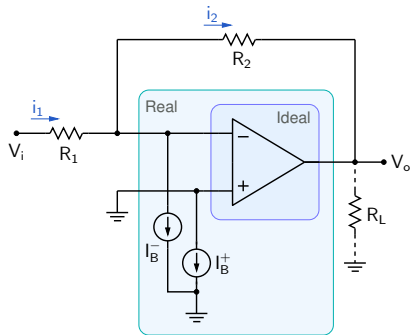
## Effect of bias currents: inverting amplifier



Assume that the op-amp is ideal in other respects (including  $V_{OS} = 0\text{ V}$ ).


$$V_- \approx V_+ = 0\text{ V} \rightarrow i_1 = V_i / R_1.$$

$$i_2 = i_1 - I_B^- \rightarrow V_o = V_- - i_2 R_2 = 0 - \left( \frac{V_i}{R_1} - I_B^- \right) R_2 = -\frac{R_2}{R_1} V_i + I_B^- R_2,$$


i.e., the bias current causes a DC shift in  $V_o$ .

$$\text{For } I_B^- = 80\text{ nA}, R_2 = 10\text{ k}, \Delta V_o = 0.8\text{ mV}.$$
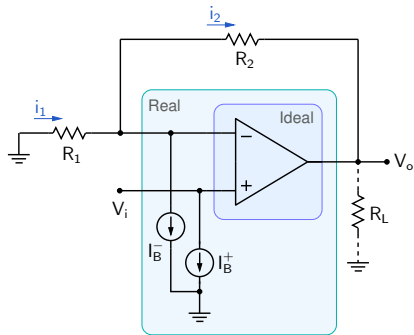
## Effect of bias currents: non-inverting amplifier



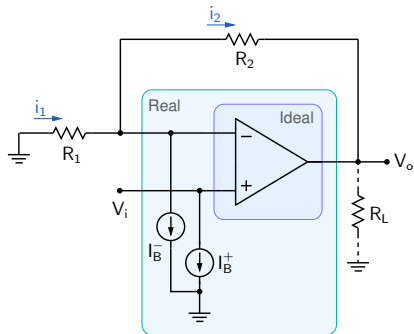
## Effect of bias currents: non-inverting amplifier



Assume that the op-amp is ideal in other respects (including  $V_{OS} = 0$  V).



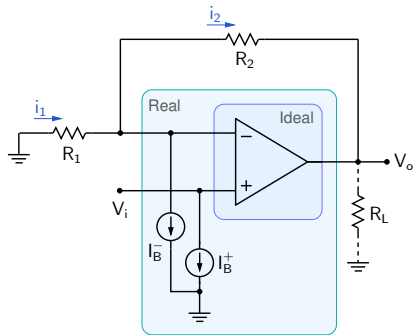
## Effect of bias currents: non-inverting amplifier



Assume that the op-amp is ideal in other respects (including  $V_{OS} = 0$  V).

$$V_- \approx V_+ = V_i \rightarrow i_1 = \frac{0 - V_i}{R_1} = -\frac{V_i}{R_1}.$$
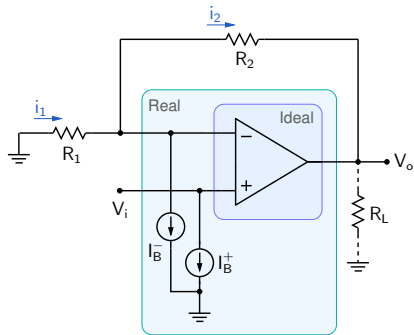
## Effect of bias currents: non-inverting amplifier




Assume that the op-amp is ideal in other respects (including  $V_{OS} = 0$  V).

$$V_- \approx V_+ = V_i \rightarrow i_1 = \frac{0 - V_i}{R_1} = -\frac{V_i}{R_1}.$$

$$i_2 = i_1 - I_B^- = -\frac{V_i}{R_1} - I_B^-.$$
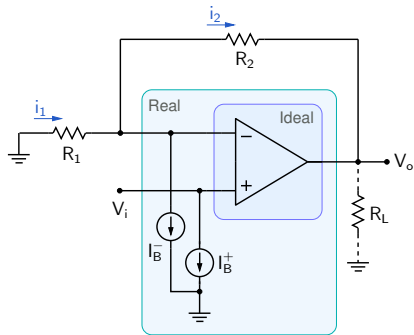
## Effect of bias currents: non-inverting amplifier



Assume that the op-amp is ideal in other respects (including  $V_{OS} = 0$  V).


$$V_- \approx V_+ = V_i \rightarrow i_1 = \frac{0 - V_i}{R_1} = -\frac{V_i}{R_1}.$$

$$i_2 = i_1 - I_B^- = -\frac{V_i}{R_1} - I_B^-.$$


$$V_o = V_- - i_2 R_2 = V_i - \left( -\frac{V_i}{R_1} - I_B^- \right) R_2 = V_i \left( 1 + \frac{R_2}{R_1} \right) + I_B^- R_2.$$

→ Again, a DC shift  $\Delta V_o$ .

## Effect of bias currents: integrator

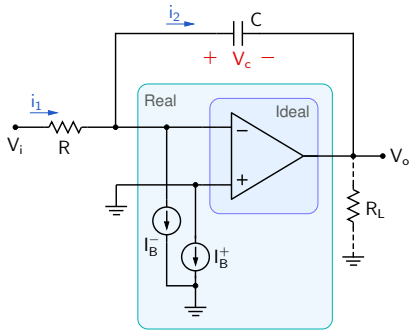


## Effect of bias currents: integrator

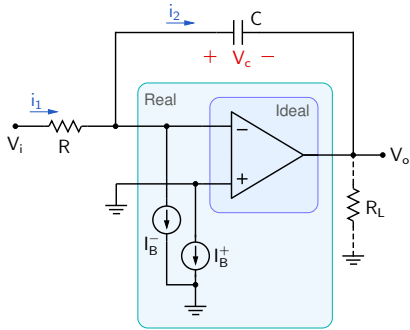

Even with  $V_i = 0$  V,  $V_c = \frac{1}{C} \int -I_B^- dt$  will drive the op-amp into saturation.


## Effect of bias currents: integrator

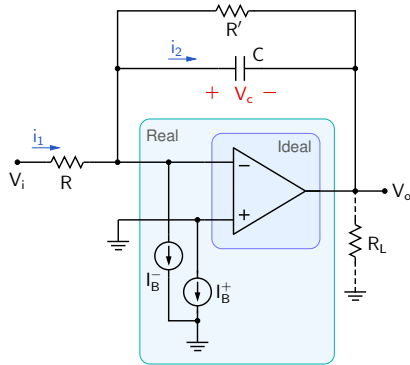

Even with  $V_i = 0$  V,  $V_c = \frac{1}{C} \int -I_B^- dt$  will drive the op-amp into saturation.

Connecting  $R'$  across  $C$  provides a DC path for the current, and results in a DC shift  $\Delta V_o = I_B^- R'$  at the output.

## Effect of bias currents: integrator

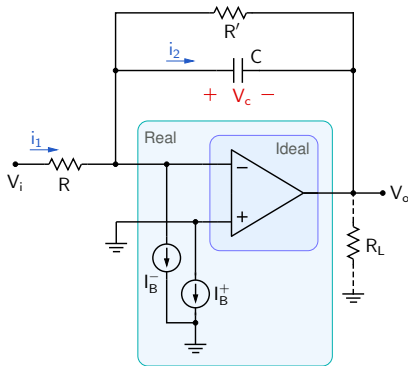


Even with  $V_i = 0$  V,  $V_c = \frac{1}{C} \int -I_B^- dt$  will drive the op-amp into saturation.

Connecting  $R'$  across  $C$  provides a DC path for the current, and results in a DC shift  $\Delta V_o = I_B^- R'$  at the output.

As we have discussed earlier,  $R'$  should be small enough to have a negligible effect on  $V_o$ .


However,  $R'$  must be large enough to ensure that the circuit still functions as an integrator.
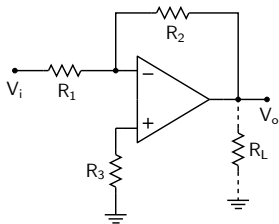
## Effect of bias currents: inverting amplifier







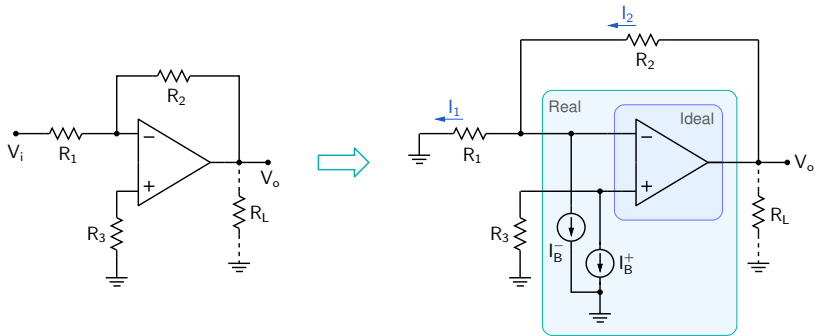
## Effect of bias currents: inverting amplifier


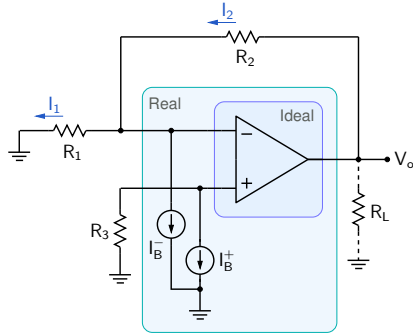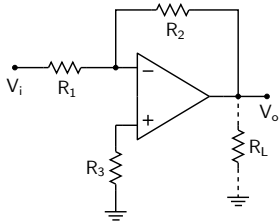
## Effect of bias currents: inverting amplifier



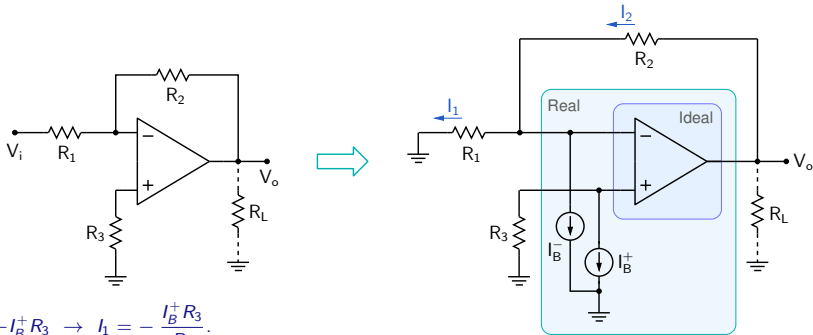
$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$



$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$

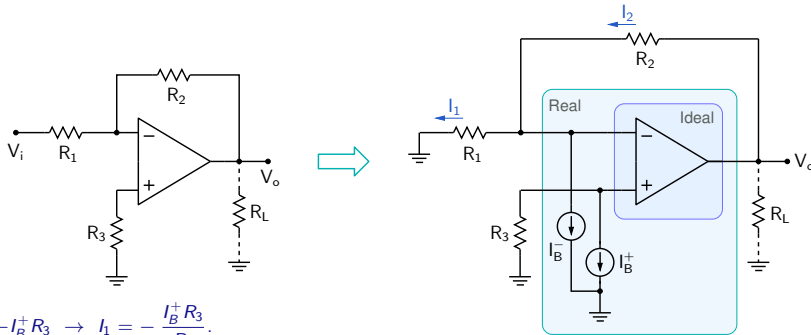
$$V_o = V_- + I_2 R_2 = -I_B^+ R_3 + R_2 \left( -\frac{I_B^+ R_3}{R_1} + I_B^- \right) = -\left( 1 + \frac{R_2}{R_1} \right) I_B^+ R_3 + I_B^- R_2.$$



$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$

$$V_o = V_- + I_2 R_2 = -I_B^+ R_3 + R_2 \left( -\frac{I_B^+ R_3}{R_1} + I_B^- \right) = -\left( 1 + \frac{R_2}{R_1} \right) I_B^+ R_3 + I_B^- R_2.$$
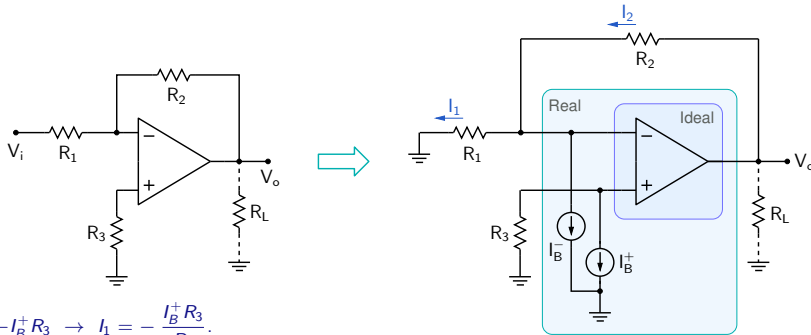
$$\text{Using } I_B = \frac{I_B^+ + I_B^-}{2}, I_{OS} = I_B^+ - I_B^-, \text{ i.e., } I_B^+ = I_B + \frac{I_{OS}}{2}, I_B^- = I_B - \frac{I_{OS}}{2}, \text{ we get}$$




$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$

$$V_o = V_- + I_2 R_2 = -I_B^+ R_3 + R_2 \left( -\frac{I_B^+ R_3}{R_1} + I_B^- \right) = -\left( 1 + \frac{R_2}{R_1} \right) I_B^+ R_3 + I_B^- R_2.$$

Using  $I_B = \frac{I_B^+ + I_B^-}{2}$ ,  $I_{OS} = I_B^+ - I_B^-$ , i.e.,  $I_B^+ = I_B + \frac{I_{OS}}{2}$ ,  $I_B^- = I_B - \frac{I_{OS}}{2}$ , we get
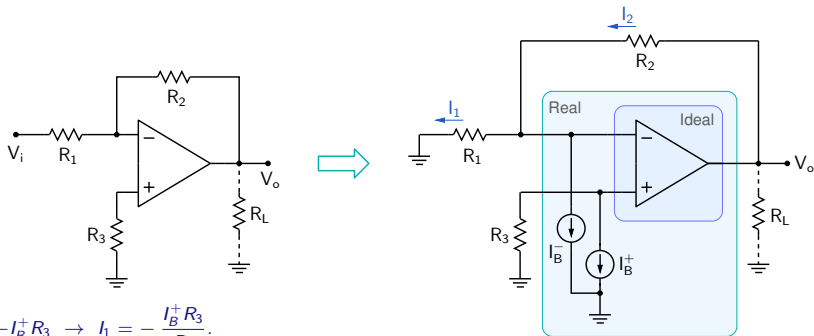
$$V_o = -R_3 \left( 1 + \frac{R_2}{R_1} \right) \left( I_B + \frac{I_{OS}}{2} \right) + R_2 \left( I_B - \frac{I_{OS}}{2} \right) = \left( 1 + \frac{R_2}{R_1} \right) \left\{ [(R_1 \parallel R_2) - R_3] I_B - [(R_1 \parallel R_2) + R_3] \frac{I_{OS}}{2} \right\}$$



$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$

$$V_o = V_- + I_2 R_2 = -I_B^+ R_3 + R_2 \left( -\frac{I_B^+ R_3}{R_1} + I_B^- \right) = -\left( 1 + \frac{R_2}{R_1} \right) I_B^+ R_3 + I_B^- R_2.$$

Using  $I_B = \frac{I_B^+ + I_B^-}{2}$ ,  $I_{OS} = I_B^+ - I_B^-$ , i.e.,  $I_B^+ = I_B + \frac{I_{OS}}{2}$ ,  $I_B^- = I_B - \frac{I_{OS}}{2}$ , we get

$$V_o = -R_3 \left( 1 + \frac{R_2}{R_1} \right) \left( I_B + \frac{I_{OS}}{2} \right) + R_2 \left( I_B - \frac{I_{OS}}{2} \right) = \left( 1 + \frac{R_2}{R_1} \right) \left\{ [(R_1 \parallel R_2) - R_3] I_B - [(R_1 \parallel R_2) + R_3] \frac{I_{OS}}{2} \right\}$$

The first term can be made zero if we select  $R_3 = R_1 \parallel R_2$ .

$\rightarrow V_o = -R_2 I_{OS}$  (Compare with  $V_o = R_2 I_B^-$  when  $R_3$  is not connected.)

- \* For the integrator,  $V_{OS}$  and  $I_B$  will lead to saturation unless a DC path (a resistor) is provided.

## Should we worry about $V_{OS}$ and $I_B$ ?

- \* For the integrator,  $V_{OS}$  and  $I_B$  will lead to saturation unless a DC path (a resistor) is provided.
- \* In AC applications (e.g., audio), the DC shift arising due to  $V_{OS}$  or  $I_B$  is of no consequence since a coupling capacitor will block it anyway.



## Should we worry about $V_{OS}$ and $I_B$ ?

- \* For the integrator,  $V_{OS}$  and  $I_B$  will lead to saturation unless a DC path (a resistor) is provided.
- \* In AC applications (e.g., audio), the DC shift arising due to  $V_{OS}$  or  $I_B$  is of no consequence since a coupling capacitor will block it anyway.
- \* A DC shift is a matter of concern when the output is expected to be a DC (or slowly varying) quantity, e.g., a temperature sensor or a strain gauge circuit.