

Op-Amp Circuits: Part 3



M. B. Patil



mbpatil@ee.iitb.ac.in

www.ee.iitb.ac.in/~sequel

Department of Electrical Engineering
Indian Institute of Technology Bombay



Introduction to filters

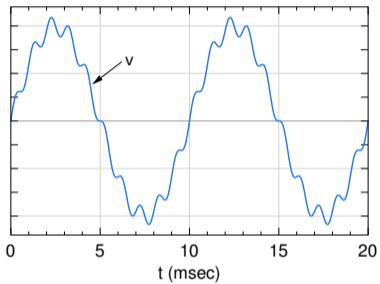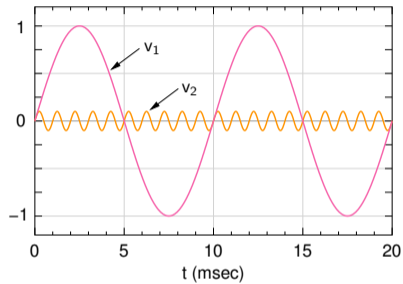Consider $v(t) = v_1(t) + v_2(t) = V_{m1} \sin \omega_1 t + V_{m2} \sin \omega_2 t$.



Introduction to filters


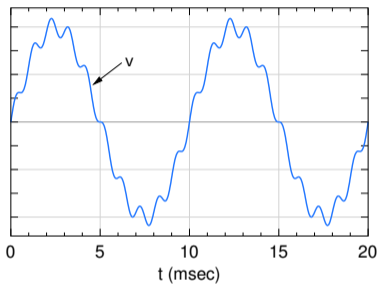
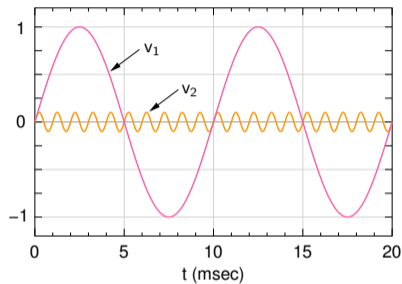
Consider $v(t) = v_1(t) + v_2(t) = V_{m1} \sin \omega_1 t + V_{m2} \sin \omega_2 t$.



A low-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the low-frequency component $v_1(t)$ and remove the high-frequency component $v_2(t)$.

Introduction to filters

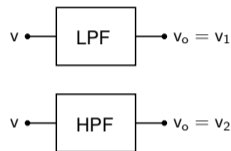
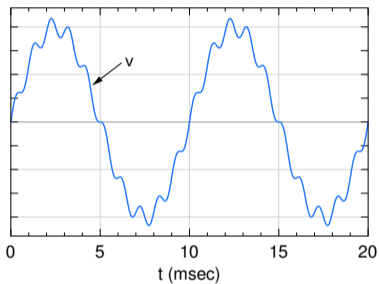
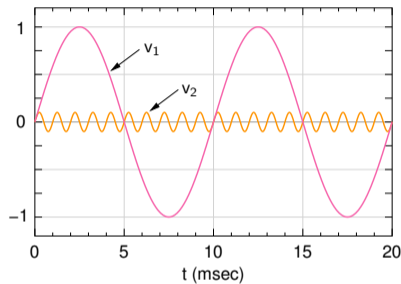
Consider $v(t) = v_1(t) + v_2(t) = V_{m1} \sin \omega_1 t + V_{m2} \sin \omega_2 t$.



A low-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the low-frequency component $v_1(t)$ and remove the high-frequency component $v_2(t)$.

A high-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the high-frequency component $v_2(t)$ and remove the low-frequency component $v_1(t)$.

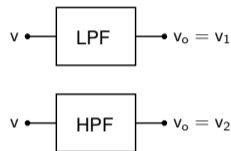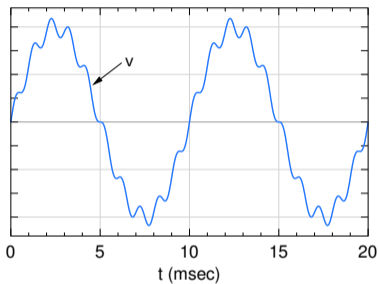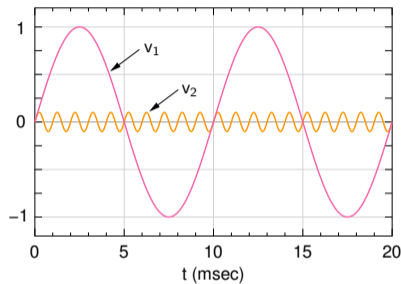Consider $v(t) = v_1(t) + v_2(t) = V_{m1} \sin \omega_1 t + V_{m2} \sin \omega_2 t$.





A low-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the low-frequency component $v_1(t)$ and remove the high-frequency component $v_2(t)$.

A high-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the high-frequency component $v_2(t)$ and remove the low-frequency component $v_1(t)$.




There are some other types of filters, as we will see.

Ideal low-pass filter

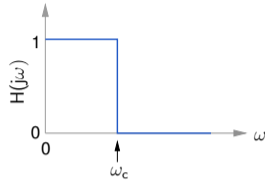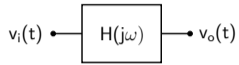




$$V_o(j\omega) = H(j\omega) V_i(j\omega).$$

Ideal low-pass filter

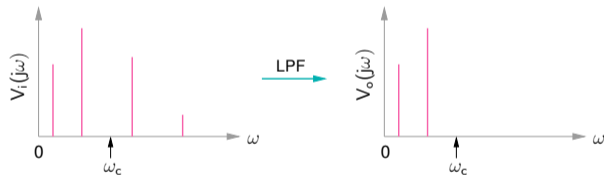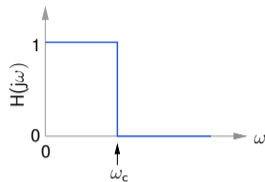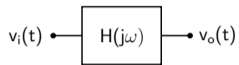

$$V_o(j\omega) = H(j\omega) V_i(j\omega).$$

Ideal low-pass filter

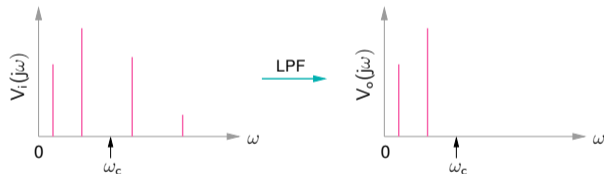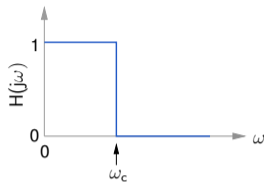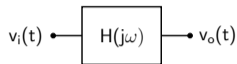


$$V_o(j\omega) = H(j\omega) V_i(j\omega).$$

All components with $\omega < \omega_c$ appear at the output without attenuation.



All components with $\omega > \omega_c$ get eliminated.

(Note that the ideal low-pass filter has $\angle H(j\omega) = 1$, i.e., $H(j\omega) = 1 + j0$.)




Ideal filters




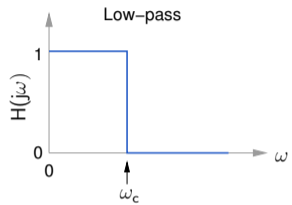


Ideal filters


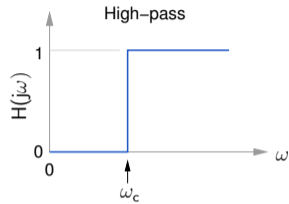
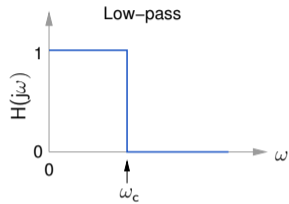


Ideal filters

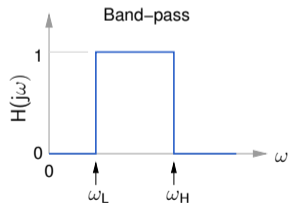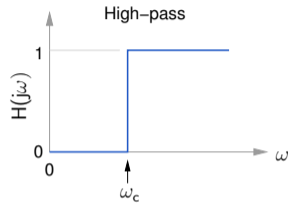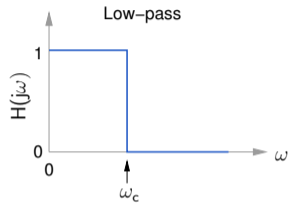


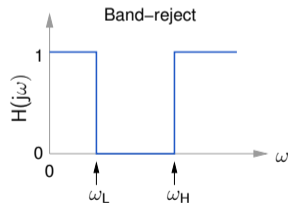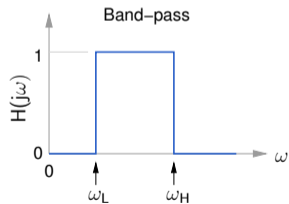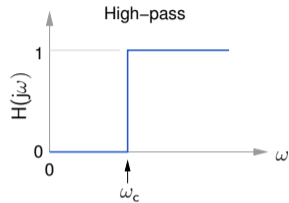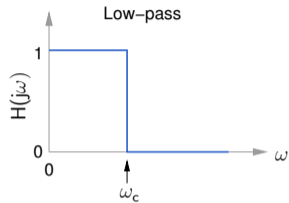


Ideal low-pass filter: example

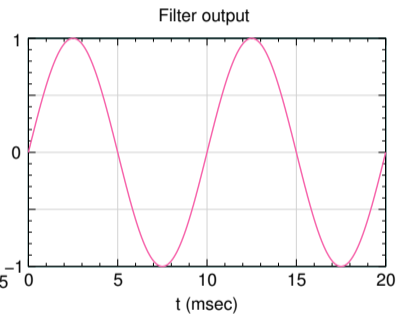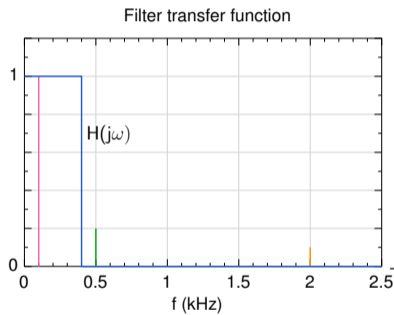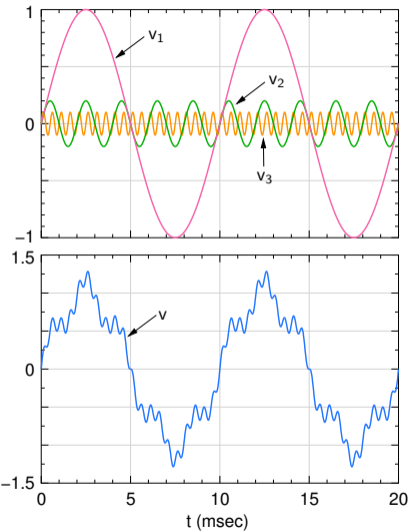


Ideal high-pass filter: example

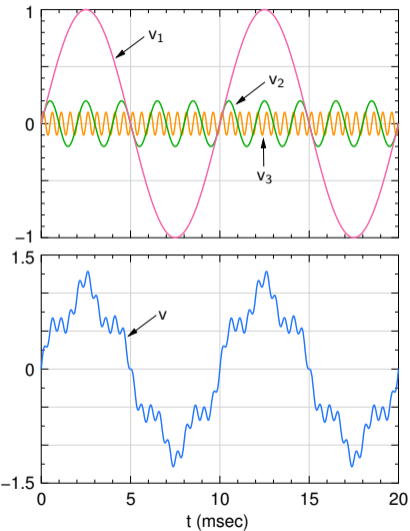


Filter transfer function

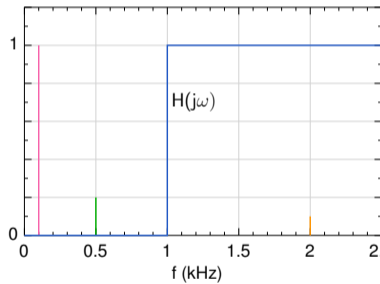


Filter output

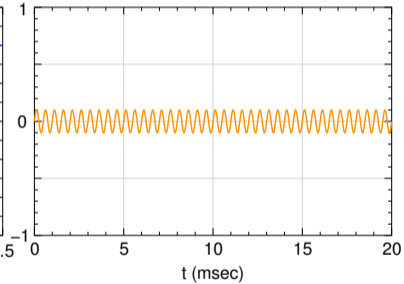


Ideal band-pass filter: example

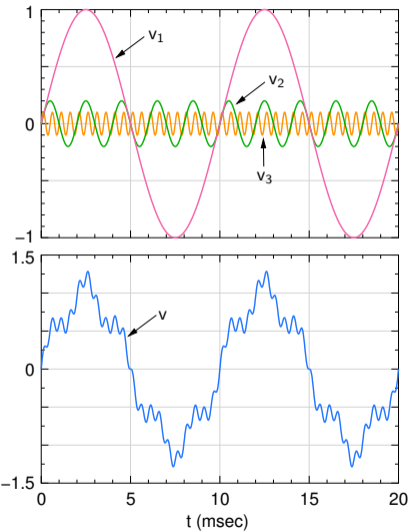



Filter transfer function

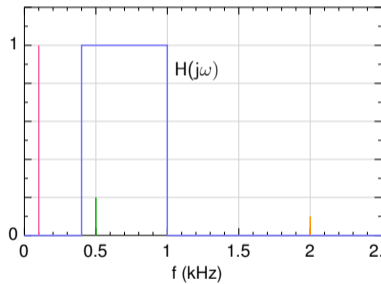

Filter output

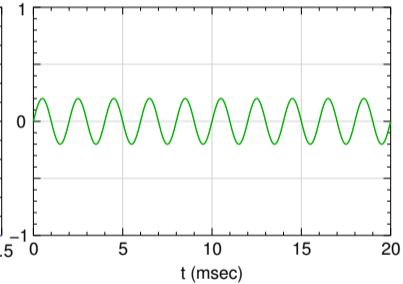

Ideal band-reject filter: example

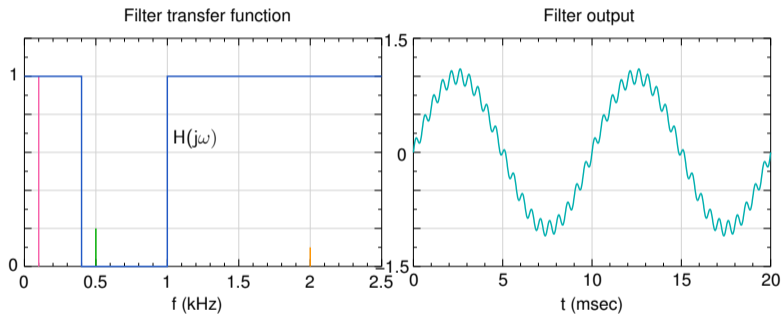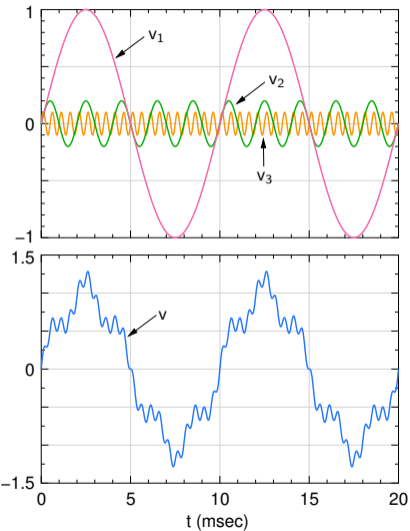

- * In practical filter circuits, the ideal filter response is approximated with a suitable $H(j\omega)$ that can be obtained with circuit elements. For example,

$$H(s) = \frac{1}{a_5s^5 + a_4s^4 + a_3s^3 + a_2s^2 + a_1s + a_0}$$

represents a 5th-order low-pass filter.

- * In practical filter circuits, the ideal filter response is approximated with a suitable $H(j\omega)$ that can be obtained with circuit elements. For example,

$$H(s) = \frac{1}{a_5s^5 + a_4s^4 + a_3s^3 + a_2s^2 + a_1s + a_0}$$

represents a 5th-order low-pass filter.

- * Some commonly used approximations (polynomials) are the Butterworth, Chebyshev, Bessel, and elliptic functions.



- * In practical filter circuits, the ideal filter response is approximated with a suitable $H(j\omega)$ that can be obtained with circuit elements. For example,

$$H(s) = \frac{1}{a_5s^5 + a_4s^4 + a_3s^3 + a_2s^2 + a_1s + a_0}$$


represents a 5th-order low-pass filter.

- * Some commonly used approximations (polynomials) are the Butterworth, Chebyshev, Bessel, and elliptic functions.
- * Coefficients for these filters are listed in filter handbooks. Also, programs for filter design are available on the internet.

Practical filters

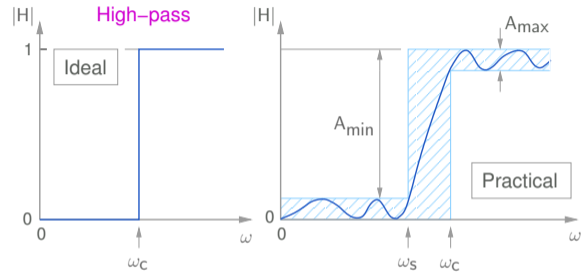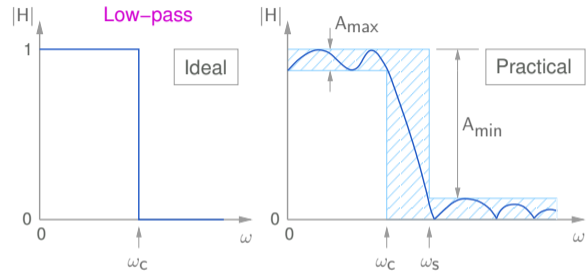


Practical filters

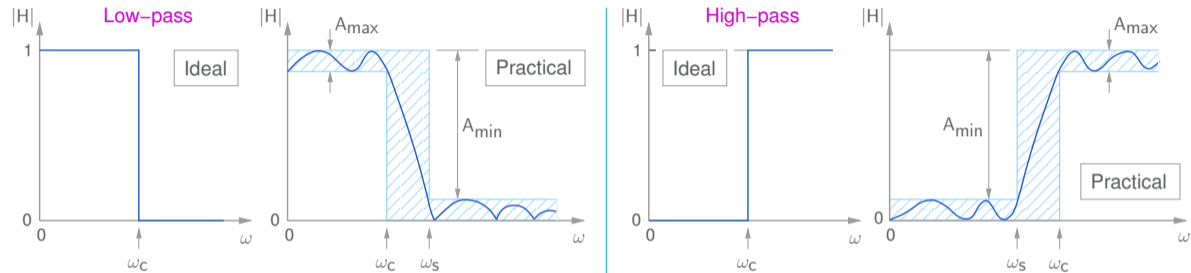


* A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.

Practical filters

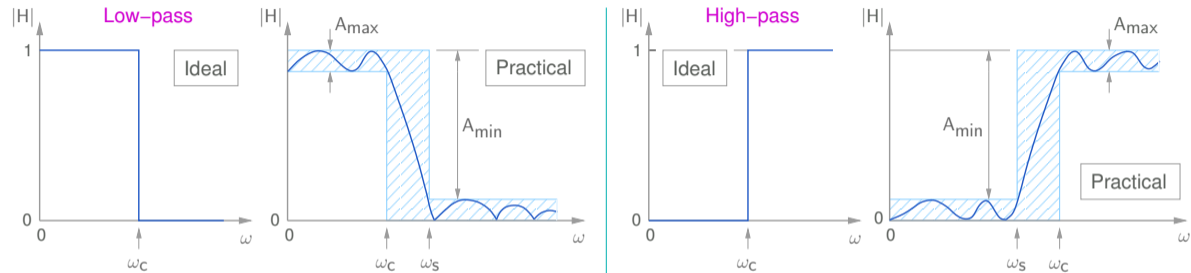


- * A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.
- * A_{\min} is the minimum attenuation to be provided by the filter, e.g., $A_{\min} = 60$ dB.


Practical filters

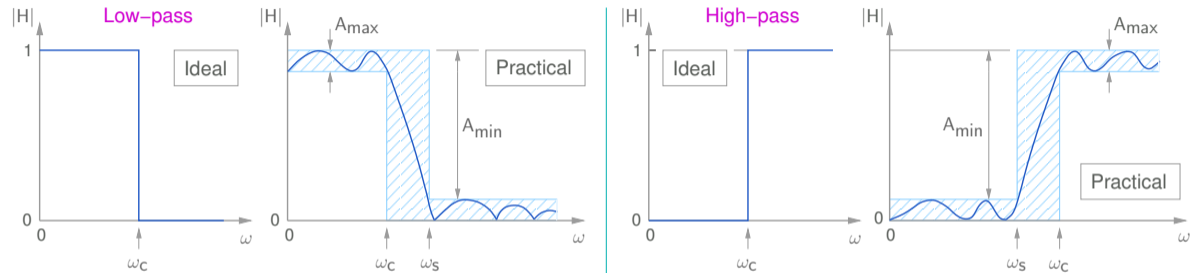

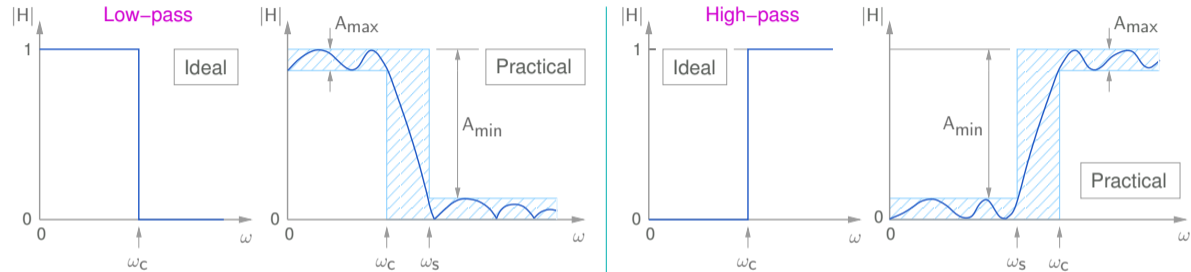- * A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.
- * A_{\min} is the minimum attenuation to be provided by the filter, e.g., $A_{\min} = 60$ dB.
- * ω_s : edge of the stop band.



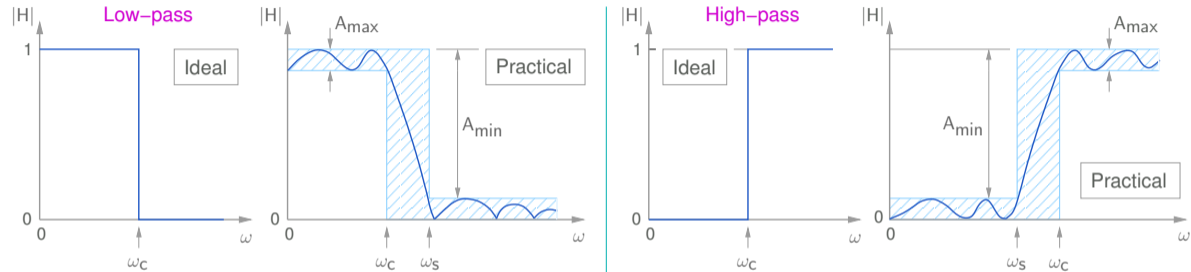- * A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.
- * A_{\min} is the minimum attenuation to be provided by the filter, e.g., $A_{\min} = 60$ dB.
- * ω_s : edge of the stop band.
- * ω_s/ω_c (for a low-pass filter): selectivity factor, a measure of the sharpness of the filter.



- * A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.
- * A_{\min} is the minimum attenuation to be provided by the filter, e.g., $A_{\min} = 60$ dB.
- * ω_s : edge of the stop band.
- * ω_s/ω_c (for a low-pass filter): selectivity factor, a measure of the sharpness of the filter.
- * $\omega_c < \omega < \omega_s$: transition band.

For a low-pass filter, $H(s) = \frac{1}{\sum_{i=0}^n a_i (s/\omega_c)^i}$.

Coefficients (a_i) for various types of filters are tabulated in handbooks. We now look at $|H(j\omega)|$ for two commonly used filters.

For a low-pass filter, $H(s) = \frac{1}{\sum_{i=0}^n a_i (s/\omega_c)^i}$.

Coefficients (a_i) for various types of filters are tabulated in handbooks. We now look at $|H(j\omega)|$ for two commonly used filters.

Butterworth filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 (\omega/\omega_c)^{2n}}}.$$

For a low-pass filter, $H(s) = \frac{1}{\sum_{i=0}^n a_i (s/\omega_c)^i}$.

Coefficients (a_i) for various types of filters are tabulated in handbooks. We now look at $|H(j\omega)|$ for two commonly used filters.

Butterworth filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 (\omega/\omega_c)^{2n}}}.$$

Chebyshev filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 C_n^2(\omega/\omega_c)}} \quad \text{where}$$

$$C_n(x) = \cos [n \cos^{-1}(x)] \quad \text{for } x \leq 1,$$

$$C_n(x) = \cosh [n \cosh^{-1}(x)] \quad \text{for } x \geq 1,$$

For a low-pass filter, $H(s) = \frac{1}{\sum_{i=0}^n a_i (s/\omega_c)^i}$.

Coefficients (a_i) for various types of filters are tabulated in handbooks. We now look at $|H(j\omega)|$ for two commonly used filters.

Butterworth filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 (\omega/\omega_c)^{2n}}}.$$

Chebyshev filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 C_n^2(\omega/\omega_c)}} \quad \text{where}$$



$$C_n(x) = \cos [n \cos^{-1}(x)] \quad \text{for } x \leq 1,$$

$$C_n(x) = \cosh [n \cosh^{-1}(x)] \quad \text{for } x \geq 1,$$



$H(s)$ for a high-pass filter can be obtained from $H(s)$ of the corresponding low-pass filter by $(s/\omega_c) \rightarrow (\omega_c/s)$.

Practical filters (low-pass)

Butterworth filters:

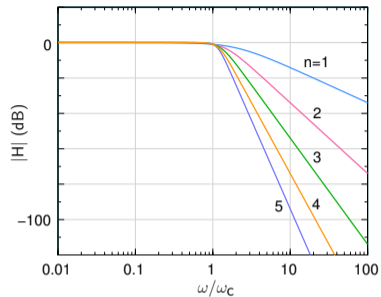
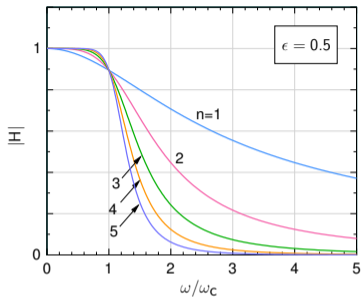


Chebyshev filters:

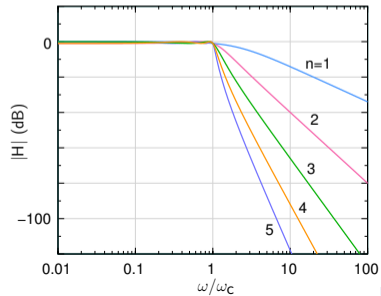
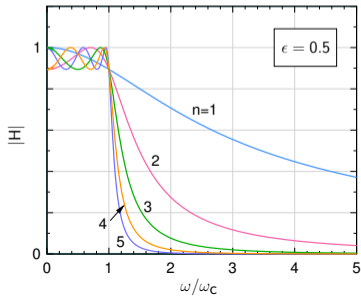


Practical filters (high-pass)


Butterworth filters:

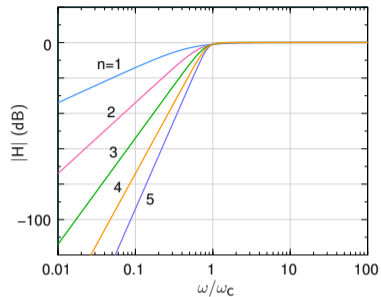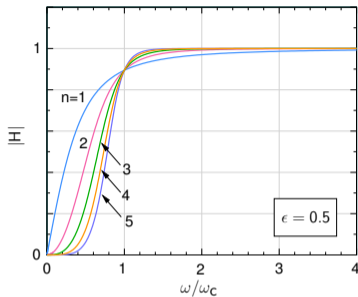


Chebyshev filters:

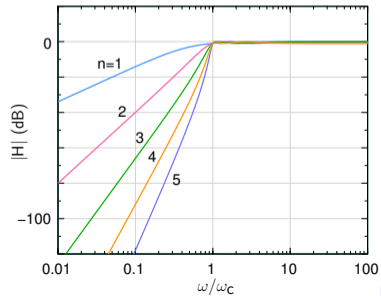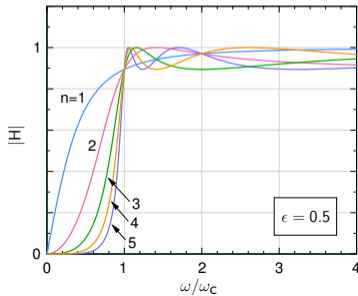

Passive filter example

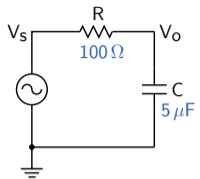


Passive filter example

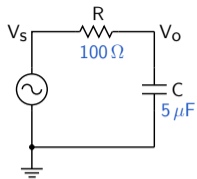

$$H(s) = \frac{(1/sC)}{R + (1/sC)} = \frac{1}{1 + (s/\omega_0)},$$

$$\text{with } \omega_0 = 1/RC \rightarrow f_0 = \omega_0/2\pi = 318\ \text{Hz}$$


(Low-pass filter)

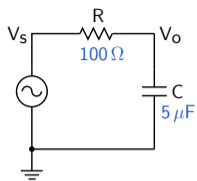

$$H(s) = \frac{(1/sC)}{R + (1/sC)} = \frac{1}{1 + (s/\omega_0)},$$


$$\text{with } \omega_0 = 1/RC \rightarrow f_0 = \omega_0/2\pi = 318\ \text{Hz}$$

(Low-pass filter)

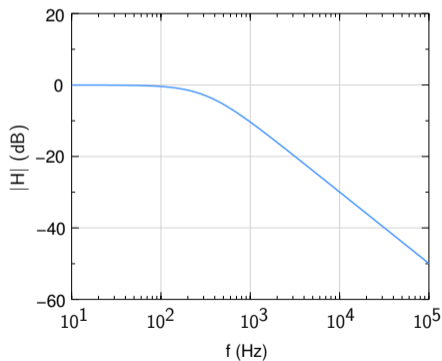


(SEQUEL file: ee101_rc_ac_2.sqproj)

Passive filter example

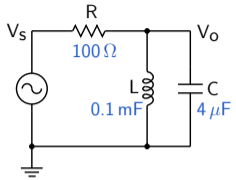

Passive filter example

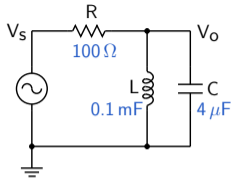


$$H(s) = \frac{(sL) \parallel (1/sC)}{R + (sL) \parallel (1/sC)} = \frac{s(L/R)}{1 + s(L/R) + s^2LC}$$

$$\text{with } \omega_0 = 1/\sqrt{LC} \rightarrow f_0 = \omega_0/2\pi = 7.96\ \text{kHz}$$

(Band-pass filter)


Passive filter example

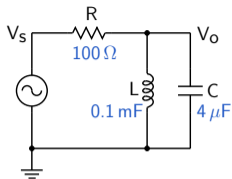

$$H(s) = \frac{(sL) \parallel (1/sC)}{R + (sL) \parallel (1/sC)} = \frac{s(L/R)}{1 + s(L/R) + s^2LC}$$

$$\text{with } \omega_0 = 1/\sqrt{LC} \rightarrow f_0 = \omega_0/2\pi = 7.96\ \text{kHz}$$

(Band-pass filter)

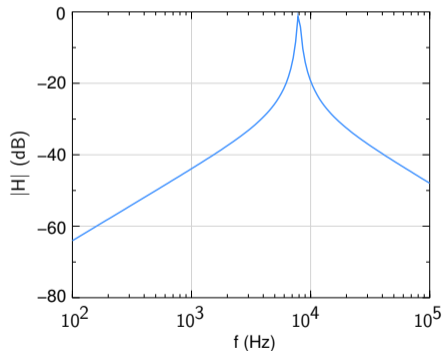

(SEQUEL file: ee101_rlc_3.sqproj)

- * Op-amp filters can be designed without using inductors. This is a significant advantage since inductors are bulky and expensive. Inductors also exhibit nonlinear behaviour (arising from the core properties) which is undesirable in a filter circuit.

Op-amp filters (“Active” filters)

- * Op-amp filters can be designed without using inductors. This is a significant advantage since inductors are bulky and expensive. Inductors also exhibit nonlinear behaviour (arising from the core properties) which is undesirable in a filter circuit.
- * With op-amps, a filter circuit can be designed with a pass-band gain.


Op-amp filters (“Active” filters)

- * Op-amp filters can be designed without using inductors. This is a significant advantage since inductors are bulky and expensive. Inductors also exhibit nonlinear behaviour (arising from the core properties) which is undesirable in a filter circuit.
- * With op-amps, a filter circuit can be designed with a pass-band gain.
- * Op-amp filters can be easily incorporated in an integrated circuit.


Op-amp filters (“Active” filters)

- * Op-amp filters can be designed without using inductors. This is a significant advantage since inductors are bulky and expensive. Inductors also exhibit nonlinear behaviour (arising from the core properties) which is undesirable in a filter circuit.
- * With op-amps, a filter circuit can be designed with a pass-band gain.
- * Op-amp filters can be easily incorporated in an integrated circuit.
- * However, there are situations in which passive filters are still used.
 - high frequencies at which op-amps do not have sufficient gain
 - high power which op-amps cannot handle

Op-amp filters: example

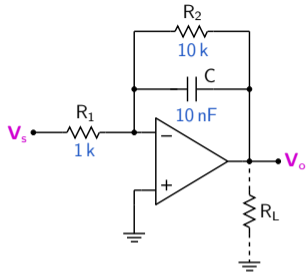

Op-amp filters: example

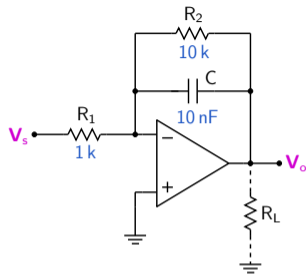


Op-amp filters are designed for op-amp operation in the linear region
→ Our analysis of the inverting amplifier applies, and we get,

$$\mathbf{V}_o = -\frac{R_2 \parallel (1/sC)}{R_1} \mathbf{V}_s \quad (\mathbf{V}_s \text{ and } \mathbf{V}_o \text{ are phasors})$$

$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$

Op-amp filters: example

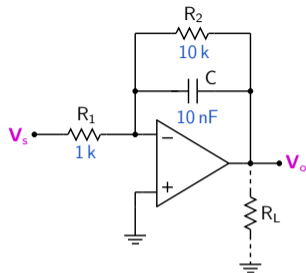



Op-amp filters are designed for op-amp operation in the linear region
→ Our analysis of the inverting amplifier applies, and we get,

$$\mathbf{V}_o = -\frac{R_2 \parallel (1/sC)}{R_1} \mathbf{V}_s \quad (\mathbf{V}_s \text{ and } \mathbf{V}_o \text{ are phasors})$$

$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$

This is a low-pass filter, with $\omega_0 = 1/R_2C$ (i.e., $f_0 = \omega_0/2\pi = 1.59 \text{ kHz}$).

Op-amp filters: example

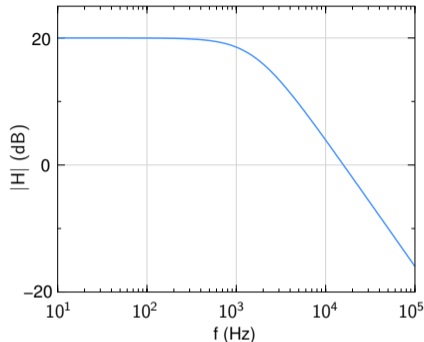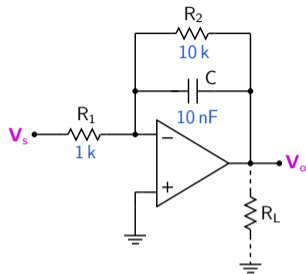

Op-amp filters are designed for op-amp operation in the linear region



→ Our analysis of the inverting amplifier applies, and we get,

$$\mathbf{V}_o = -\frac{R_2 \parallel (1/sC)}{R_1} \mathbf{V}_s \quad (\mathbf{V}_s \text{ and } \mathbf{V}_o \text{ are phasors})$$

$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$

This is a low-pass filter, with $\omega_0 = 1/R_2C$ (i.e., $f_0 = \omega_0/2\pi = 1.59 \text{ kHz}$).

Op-amp filters: example

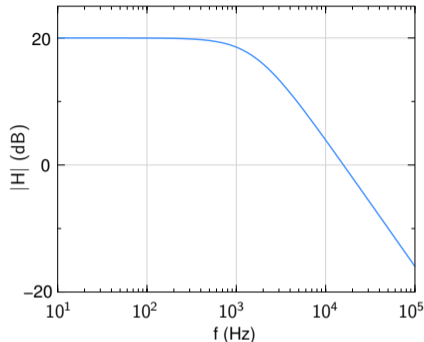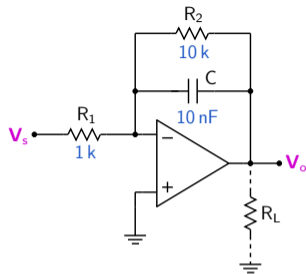

Op-amp filters are designed for op-amp operation in the linear region

→ Our analysis of the inverting amplifier applies, and we get,


$$\mathbf{V}_o = -\frac{R_2 \parallel (1/sC)}{R_1} \mathbf{V}_s \quad (\mathbf{V}_s \text{ and } \mathbf{V}_o \text{ are phasors})$$

$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$


This is a low-pass filter, with $\omega_0 = 1/R_2C$ (i.e., $f_0 = \omega_0/2\pi = 1.59 \text{ kHz}$).

(SEQUEL file: ee101_op_filter_1.sqproj)

Op-amp filters: example

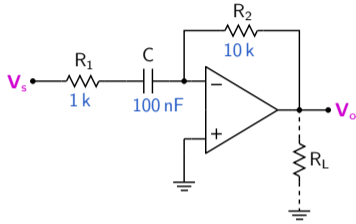


Op-amp filters: example

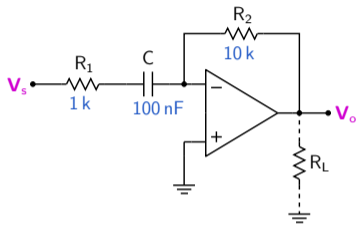

$$H(s) = -\frac{R_2}{R_1 + (1/sC)} = -\frac{sR_2C}{1 + sR_1C}.$$



Op-amp filters: example

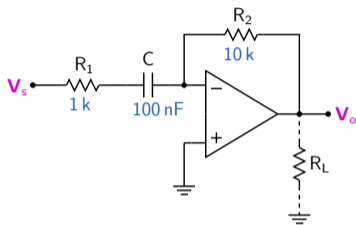

$$H(s) = -\frac{R_2}{R_1 + (1/sC)} = -\frac{sR_2C}{1 + sR_1C}.$$



This is a high-pass filter, with $\omega_0 = 1/R_1C$ (i.e., $f_0 = \omega_0/2\pi = 1.59\text{ kHz}$).

Op-amp filters: example

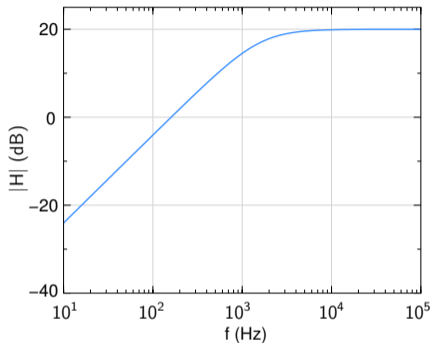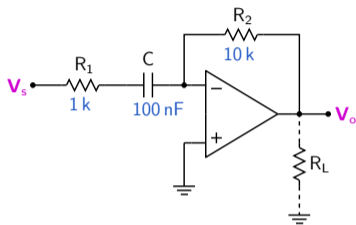

$$H(s) = -\frac{R_2}{R_1 + (1/sC)} = -\frac{sR_2C}{1 + sR_1C}.$$

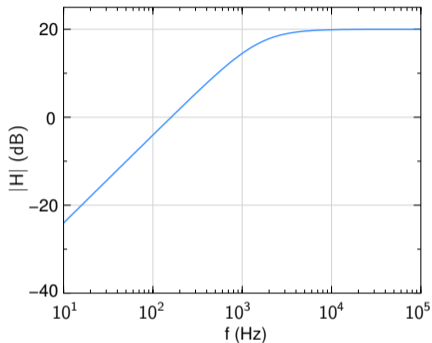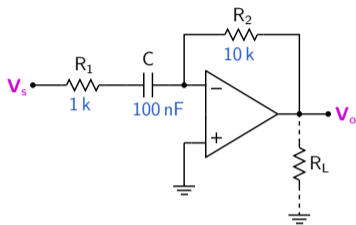This is a high-pass filter, with $\omega_0 = 1/R_1C$ (i.e., $f_0 = \omega_0/2\pi = 1.59\text{ kHz}$).




$$H(s) = -\frac{R_2}{R_1 + (1/sC)} = -\frac{sR_2C}{1 + sR_1C}.$$


This is a high-pass filter, with $\omega_0 = 1/R_1C$ (i.e., $f_0 = \omega_0/2\pi = 1.59$ kHz).

(SEQUEL file: ee101_op_filter_2.sqproj)

Op-amp filters: example

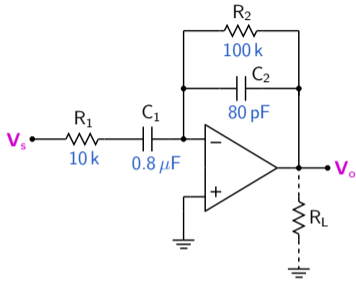


Op-amp filters: example

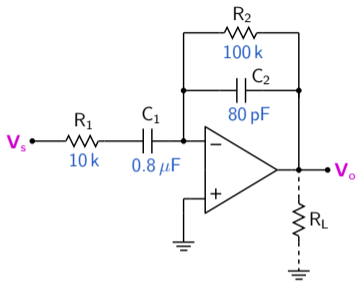

$$H(s) = -\frac{R_2 \parallel (1/sC_2)}{R_1 + (1/sC_1)} = -\frac{R_2}{R_1} \frac{sR_1 C_1}{(1 + sR_1 C_1)(1 + sR_2 C_2)}.$$

Op-amp filters: example


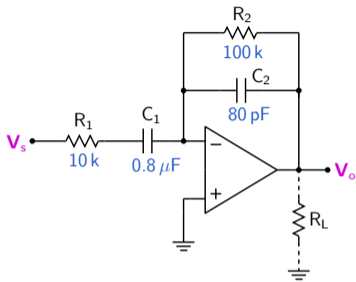


$$H(s) = -\frac{R_2 \parallel (1/sC_2)}{R_1 + (1/sC_1)} = -\frac{R_2}{R_1} \frac{sR_1 C_1}{(1 + sR_1 C_1)(1 + sR_2 C_2)}.$$

This is a band-pass filter, with $\omega_L = 1/R_1 C_1$ and $\omega_H = 1/R_2 C_2$.

$\rightarrow f_L = 20\text{ Hz}$, $f_H = 20\text{ kHz}$.

Op-amp filters: example

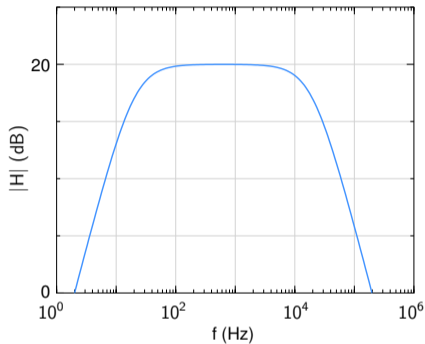
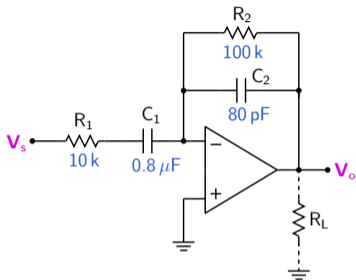


$$H(s) = -\frac{R_2 \parallel (1/sC_2)}{R_1 + (1/sC_1)} = -\frac{R_2}{R_1} \frac{sR_1 C_1}{(1 + sR_1 C_1)(1 + sR_2 C_2)}.$$

This is a band-pass filter, with $\omega_L = 1/R_1 C_1$ and $\omega_H = 1/R_2 C_2$.

$\rightarrow f_L = 20\text{ Hz}$, $f_H = 20\text{ kHz}$.

Op-amp filters: example

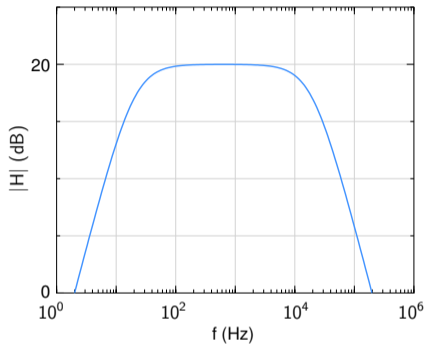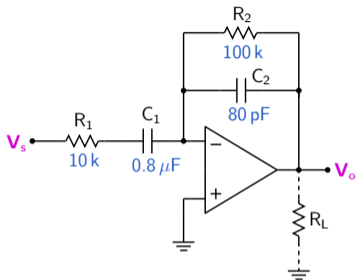



$$H(s) = -\frac{R_2 \parallel (1/sC_2)}{R_1 + (1/sC_1)} = -\frac{R_2}{R_1} \frac{sR_1 C_1}{(1 + sR_1 C_1)(1 + sR_2 C_2)}.$$

This is a band-pass filter, with $\omega_L = 1/R_1 C_1$ and $\omega_H = 1/R_2 C_2$.

$\rightarrow f_L = 20 \text{ Hz}$, $f_H = 20 \text{ kHz}$.



(SEQUEL file: ee101_op_filter_3.sqproj)

Graphic equalizer

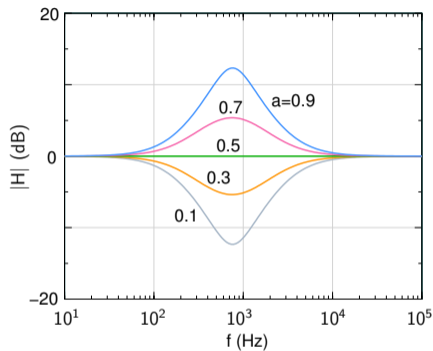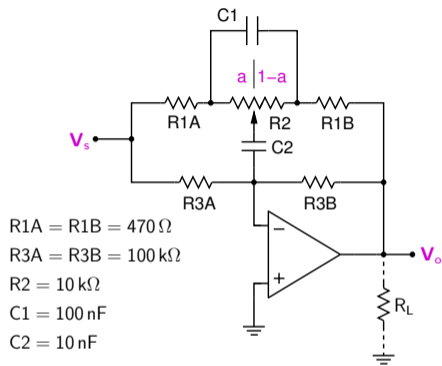



(Ref.: S. Franco, "Design with Op Amps and analog ICs")

Graphic equalizer

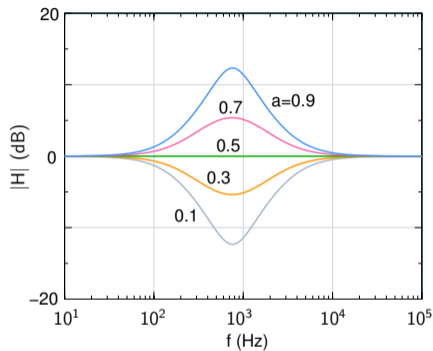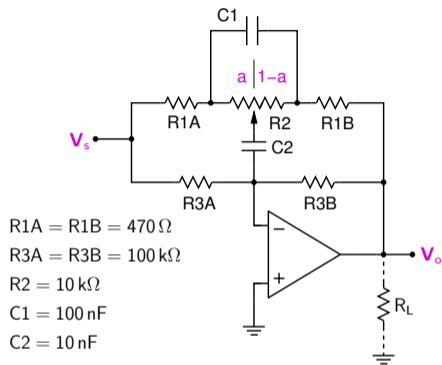

(Ref.: S. Franco, "Design with Op Amps and analog ICs")

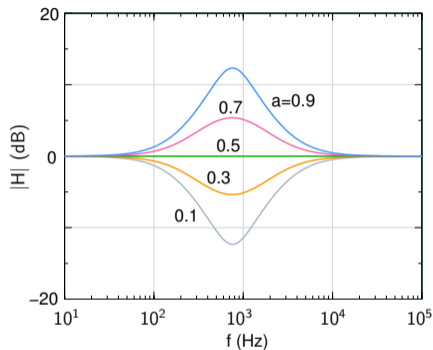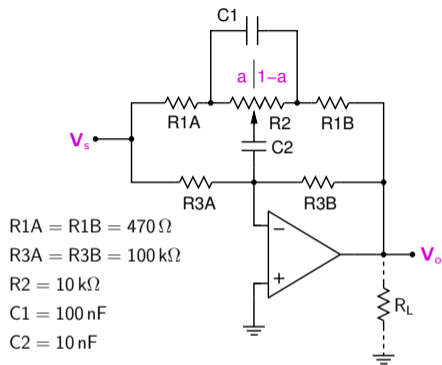- * Equalizers are implemented as arrays of narrow-band filters, each with an adjustable gain (attenuation) around a centre frequency.




(Ref.: S. Franco, "Design with Op Amps and analog ICs")

- * Equalizers are implemented as arrays of narrow-band filters, each with an adjustable gain (attenuation) around a centre frequency.
- * The circuit shown above represents one of the equalizer sections.
(SEQUEL file: ee101_op_filter_4.sqproj)



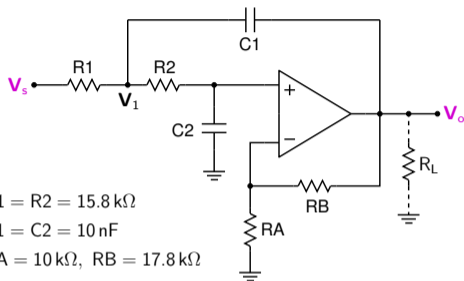Sallen-Key filter example (2nd order, low-pass)




$$R1 = R2 = 15.8 \text{ k}\Omega$$


$$C1 = C2 = 10 \text{ nF}$$

$$RA = 10 \text{ k}\Omega, RB = 17.8 \text{ k}\Omega$$

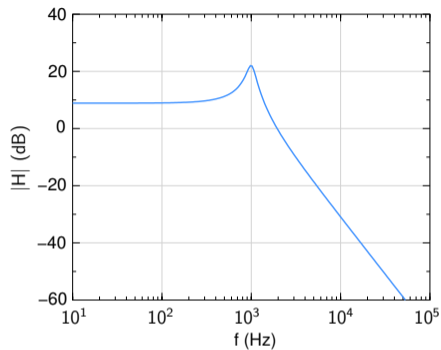(Ref.: S. Franco, "Design with Op Amps and analog ICs")



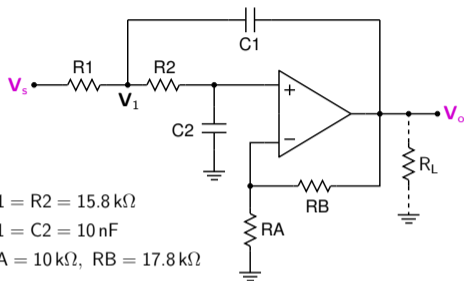Sallen-Key filter example (2nd order, low-pass)




$$R1 = R2 = 15.8 \text{ k}\Omega$$

$$C1 = C2 = 10 \text{ nF}$$


$$R_A = 10 \text{ k}\Omega, R_B = 17.8 \text{ k}\Omega$$

(Ref.: S. Franco, "Design with Op Amps and analog ICs")
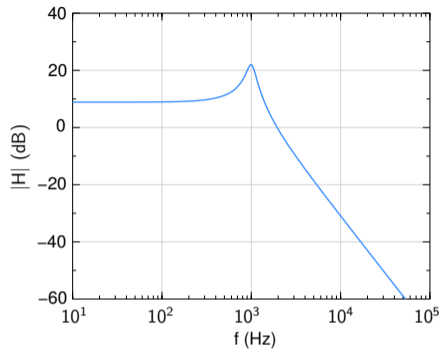
$$V_+ = V_- = V_o \frac{R_A}{R_A + R_B} \equiv V_o / K.$$



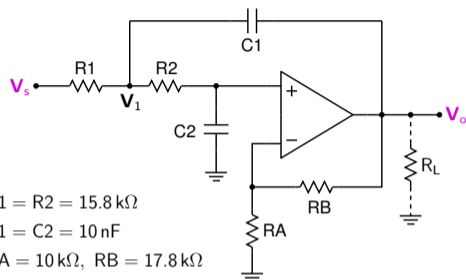Sallen-Key filter example (2nd order, low-pass)




$$R1 = R2 = 15.8 \text{ k}\Omega$$

$$C1 = C2 = 10 \text{ nF}$$

$$R_A = 10 \text{ k}\Omega, R_B = 17.8 \text{ k}\Omega$$

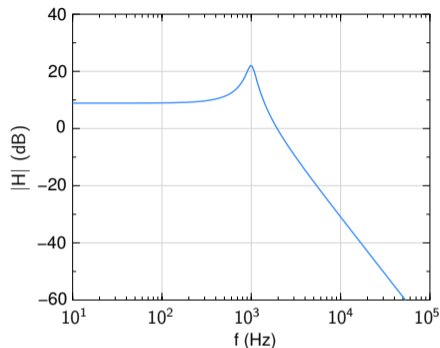
(Ref.: S. Franco, "Design with Op Amps and analog ICs")



$$\mathbf{V}_+ = \mathbf{V}_- = \mathbf{V}_o \frac{R_A}{R_A + R_B} \equiv \mathbf{V}_o / K.$$

$$\text{Also, } \mathbf{V}_+ = \frac{(1/sC_2)}{R_2 + (1/sC_2)} \mathbf{V}_1 = \frac{1}{1 + sR_2C_2} \mathbf{V}_1.$$

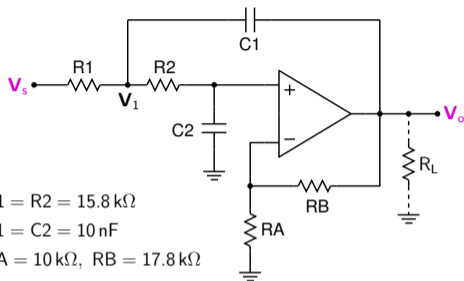Sallen-Key filter example (2nd order, low-pass)




$$R1 = R2 = 15.8 \text{ k}\Omega$$

$$C1 = C2 = 10 \text{ nF}$$

$$R_A = 10 \text{ k}\Omega, R_B = 17.8 \text{ k}\Omega$$

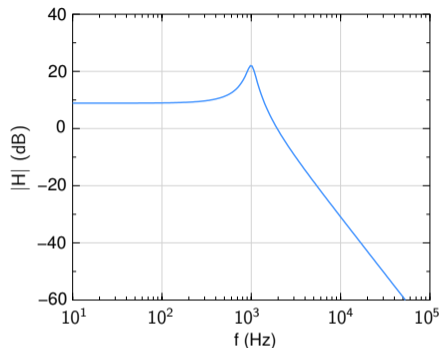(Ref.: S. Franco, "Design with Op Amps and analog ICs")




$$\mathbf{V}_+ = \mathbf{V}_- = \mathbf{V}_o \frac{R_A}{R_A + R_B} \equiv \mathbf{V}_o / K.$$

$$\text{Also, } \mathbf{V}_+ = \frac{(1/sC_2)}{R_2 + (1/sC_2)} \mathbf{V}_1 = \frac{1}{1 + sR_2C_2} \mathbf{V}_1.$$

$$\text{KCL at } \mathbf{V}_1 \rightarrow \frac{1}{R_1} (\mathbf{V}_s - \mathbf{V}_1) + sC_1 (\mathbf{V}_o - \mathbf{V}_1) + \frac{1}{R_2} (\mathbf{V}_+ - \mathbf{V}_1) = 0.$$

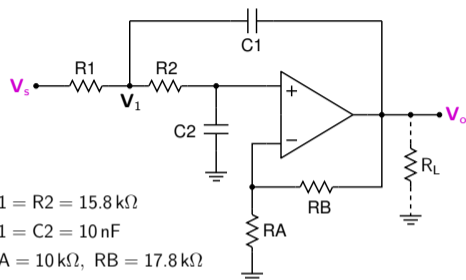Sallen-Key filter example (2nd order, low-pass)




$$R1 = R2 = 15.8 \text{ k}\Omega$$

$$C1 = C2 = 10 \text{ nF}$$

$$RA = 10 \text{ k}\Omega, RB = 17.8 \text{ k}\Omega$$

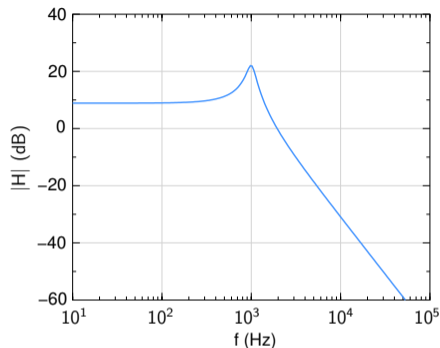(Ref.: S. Franco, "Design with Op Amps and analog ICs")



$$\mathbf{V}_+ = \mathbf{V}_- = \mathbf{V}_o \frac{R_A}{R_A + R_B} \equiv \mathbf{V}_o / K.$$



$$\text{Also, } \mathbf{V}_+ = \frac{(1/sC_2)}{R_2 + (1/sC_2)} \mathbf{V}_1 = \frac{1}{1 + sR_2C_2} \mathbf{V}_1.$$

$$\text{KCL at } \mathbf{V}_1 \rightarrow \frac{1}{R_1} (\mathbf{V}_s - \mathbf{V}_1) + sC_1 (\mathbf{V}_o - \mathbf{V}_1) + \frac{1}{R_2} (\mathbf{V}_+ - \mathbf{V}_1) = 0.$$

$$\text{Combining the above equations, } H(s) = \frac{K}{1 + s[(R_1 + R_2)C_2 + (1 - K)R_1C_1] + s^2R_1C_1R_2C_2}.$$

(SEQUEL file: ee101_op_filter_5.sqproj)

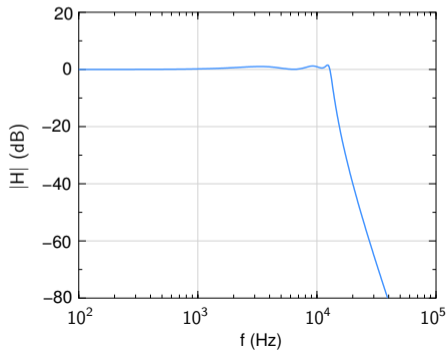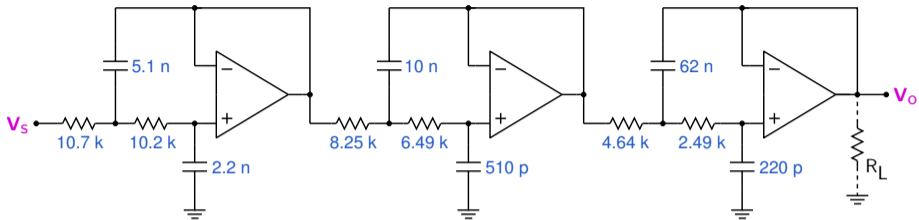
Sixth-order Chebyshev low-pass filter (cascade design)



(Ref.: S. Franco, "Design with Op Amps and analog ICs")


SEQUEL file: ee101_op_filter_6.sqproj

Third-order Chebyshev high-pass filter

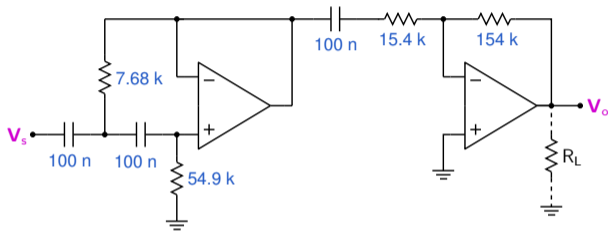


(Ref.: S. Franco, "Design with Op Amps and analog ICs")

SEQUEL file: ee101_op_filter_7.sqproj

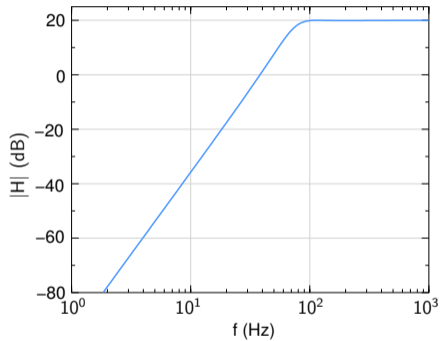


Band-pass filter example

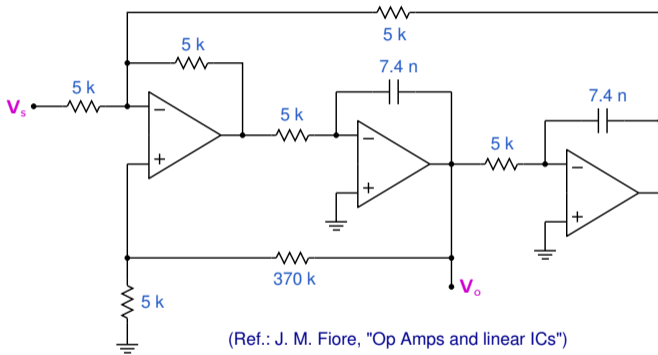


(Ref.: J. M. Fiore, "Op Amps and linear ICs")

SEQUEL file: ee101_op_filter_8.sqproj

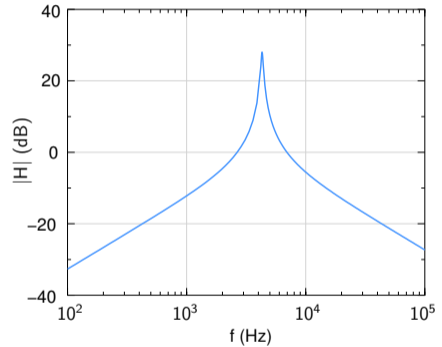

Notch filter example

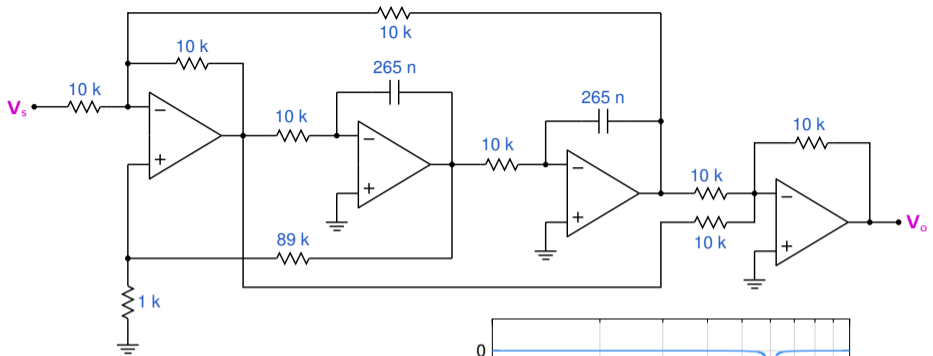

(Ref.: J. M. Fiore, "Op Amps and linear ICs")

SEQUEL file: ee101_op_filter_9.sqproj

