

## Op-Amp Circuits: Part 6

---




M. B. Patil


[mbpatil@ee.iitb.ac.in](mailto:mbpatil@ee.iitb.ac.in)

[www.ee.iitb.ac.in/~sequel](http://www.ee.iitb.ac.in/~sequel)

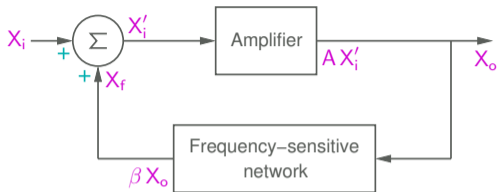Department of Electrical Engineering  
Indian Institute of Technology Bombay




Consider an amplifier with feedback.

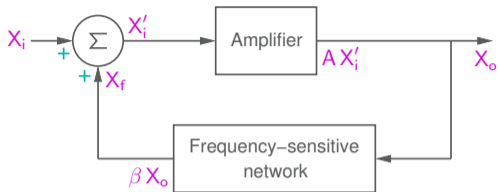

Consider an amplifier with feedback.

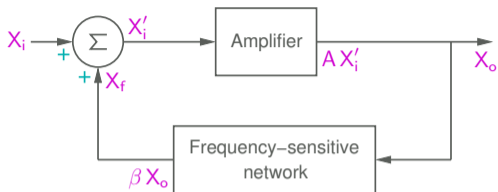
$$X_o = A X'_i = A (X_i + X_f) = A (X_i + \beta X_o) = A X_i + A \beta X_o$$



Consider an amplifier with feedback.

$$X_o = A X'_i = A (X_i + X_f) = A (X_i + \beta X_o) = A X_i + A \beta X_o$$
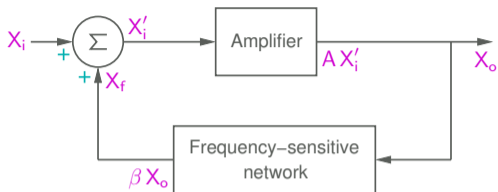
$$\rightarrow A_f \equiv \frac{X_o}{X_i} = \frac{A}{1 - A\beta}$$




Consider an amplifier with feedback.

$$X_o = A X'_i = A (X_i + X_f) = A (X_i + \beta X_o) = A X_i + A \beta X_o$$

$$\rightarrow A_f \equiv \frac{X_o}{X_i} = \frac{A}{1 - A\beta}$$

Since  $A$  and  $\beta$  will generally vary with  $\omega$ , we re-write  $A_f$  as
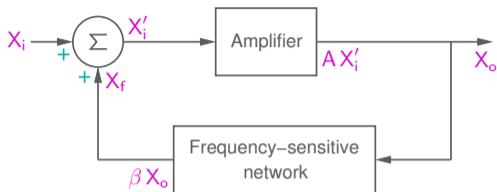
$$A_f(j\omega) = \frac{A(j\omega)}{1 - A(j\omega)\beta(j\omega)}$$



Consider an amplifier with feedback.


$$X_o = A X'_i = A (X_i + X_f) = A (X_i + \beta X_o) = A X_i + A \beta X_o$$

$$\rightarrow A_f \equiv \frac{X_o}{X_i} = \frac{A}{1 - A\beta}$$

Since  $A$  and  $\beta$  will generally vary with  $\omega$ , we re-write  $A_f$  as

$$A_f(j\omega) = \frac{A(j\omega)}{1 - A(j\omega)\beta(j\omega)}$$

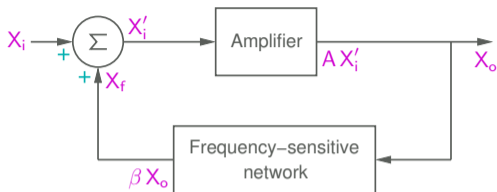As  $A(j\omega)\beta(j\omega) \rightarrow 1$ ,  $A_f(j\omega) \rightarrow \infty$ , and we get a finite  $X_o (= A_f X_i)$  even if  $X_i = 0$ .



Consider an amplifier with feedback.

$$X_o = A X'_i = A (X_i + X_f) = A (X_i + \beta X_o) = A X_i + A \beta X_o$$


$$\rightarrow A_f \equiv \frac{X_o}{X_i} = \frac{A}{1 - A\beta}$$

Since  $A$  and  $\beta$  will generally vary with  $\omega$ , we re-write  $A_f$  as


$$A_f(j\omega) = \frac{A(j\omega)}{1 - A(j\omega)\beta(j\omega)}$$

As  $A(j\omega)\beta(j\omega) \rightarrow 1$ ,  $A_f(j\omega) \rightarrow \infty$ , and we get a finite  $X_o (= A_f X_i)$  even if  $X_i = 0$ .

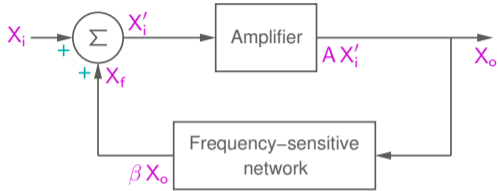
In other words, we can remove  $X_i$  and still get a non-zero  $X_o$ . This is the basic principle behind sinusoidal oscillators.






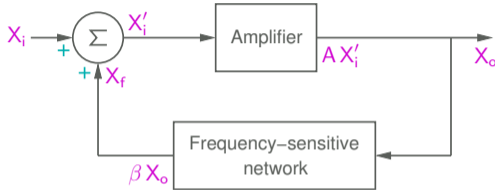

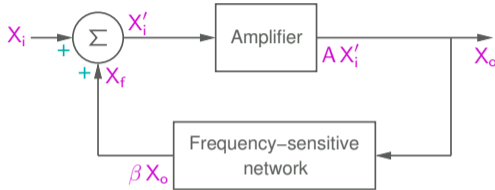- \* The condition,  $A(j\omega)\beta(j\omega) = 1$ , for a circuit to oscillate spontaneously (i.e., without any input), is known as the Barkhausen criterion.





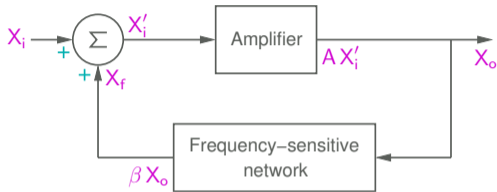
- \* The condition,  $A(j\omega)\beta(j\omega) = 1$ , for a circuit to oscillate spontaneously (i.e., without any input), is known as the Barkhausen criterion.
- \* For the circuit to oscillate at  $\omega = \omega_0$ , the  $\beta$  network is designed such that the Barkhausen criterion is satisfied only for  $\omega_0$ , i.e., all components except  $\omega_0$  get attenuated to zero.




- \* The condition,  $A(j\omega)\beta(j\omega) = 1$ , for a circuit to oscillate spontaneously (i.e., without any input), is known as the Barkhausen criterion.
- \* For the circuit to oscillate at  $\omega = \omega_0$ , the  $\beta$  network is designed such that the Barkhausen criterion is satisfied only for  $\omega_0$ , i.e., all components except  $\omega_0$  get attenuated to zero.
- \* The output  $X_o$  will therefore have a frequency  $\omega_0$  ( $\omega_0/2\pi$  in Hz), but what about the amplitude?

# Sinusoidal oscillators

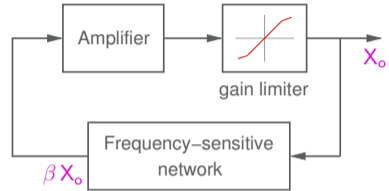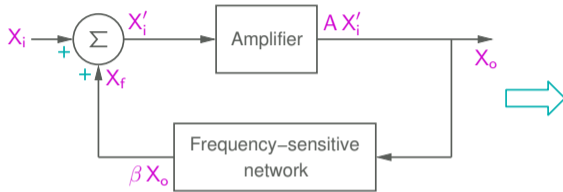


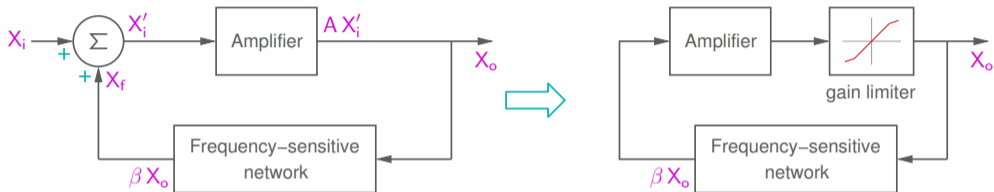

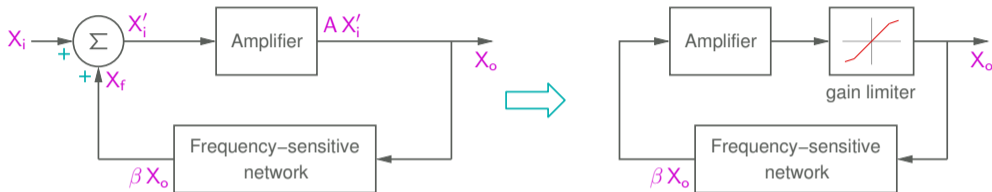\* A gain limiting mechanism is required to limit the amplitude of the oscillations.




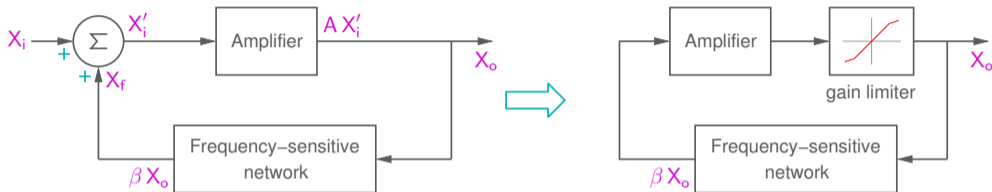- \* A gain limiting mechanism is required to limit the amplitude of the oscillations.
- \* Amplifier clipping can provide a gain limiter mechanism. For example, in an op-amp, the output voltage is limited to  $\pm V_{\text{sat}}$ , and this serves to limit the gain as the magnitude of the output voltage increases.



- \* A gain limiting mechanism is required to limit the amplitude of the oscillations.
- \* Amplifier clipping can provide a gain limiter mechanism. For example, in an op-amp, the output voltage is limited to  $\pm V_{\text{sat}}$ , and this serves to limit the gain as the magnitude of the output voltage increases.
- \* For a more controlled output with low distortion, diode-resistor networks are used for gain limiting.


## Gain limiting network: example

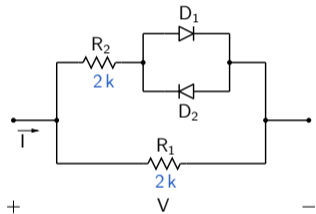



SEQUEL file: ee101\_diode\_circuit\_14.sqproj




# Gain limiting network: example

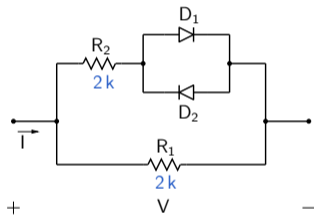

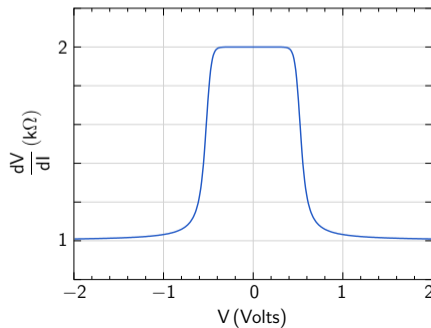
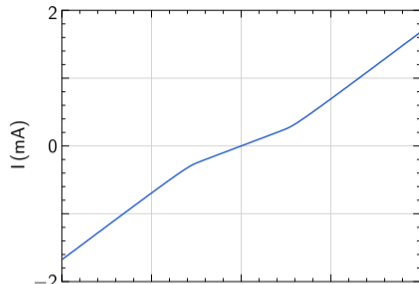
SEQUEL file: ee101\_diode\_circuit\_14.sqproj





## Gain limiting network: example

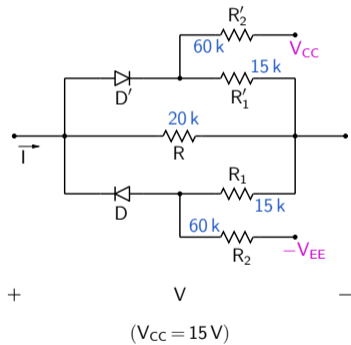


# Gain limiting network: example

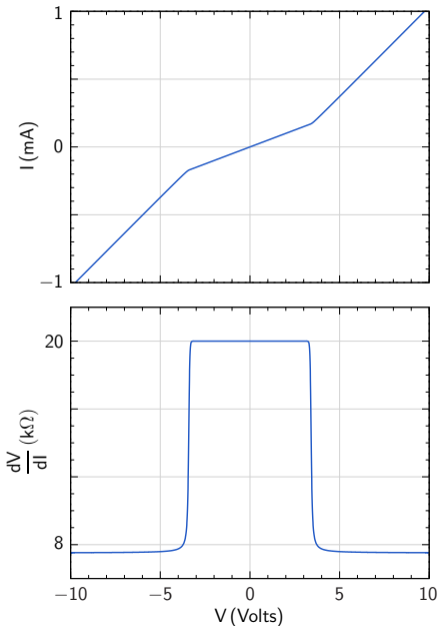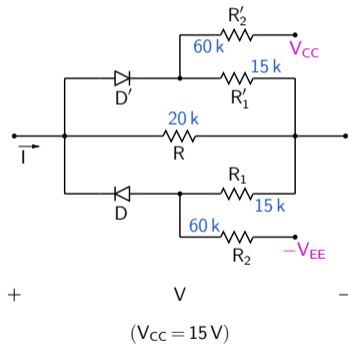

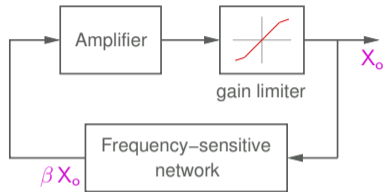


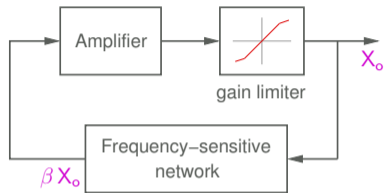

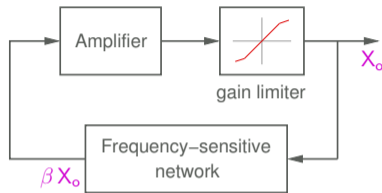- \* Up to about 100 kHz, an op-amp based amplifier and a  $\beta$  network of resistors and capacitors can be used.





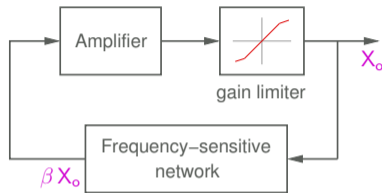- \* Up to about 100 kHz, an op-amp based amplifier and a  $\beta$  network of resistors and capacitors can be used.
- \* At higher frequencies, an op-amp based amplifier is not suitable because of frequency response and slew rate limitations of op-amps.





- \* Up to about 100 kHz, an op-amp based amplifier and a  $\beta$  network of resistors and capacitors can be used.
- \* At higher frequencies, an op-amp based amplifier is not suitable because of frequency response and slew rate limitations of op-amps.
- \* For high frequencies, transistor amplifiers are used, and  $LC$  tuned circuits or piezoelectric crystals are used in the  $\beta$  network.

# Wien bridge oscillator

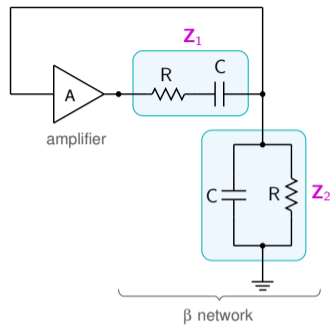
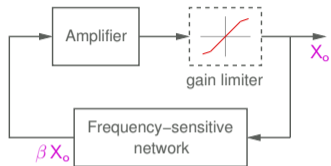




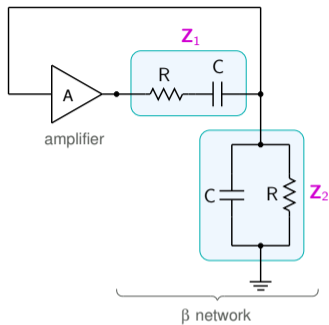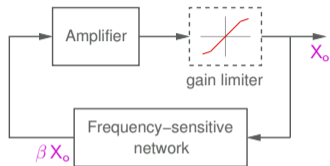

Assuming  $R_{in} \rightarrow \infty$  for the amplifier, we get
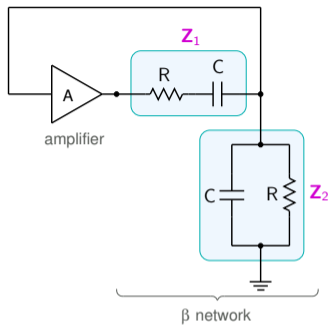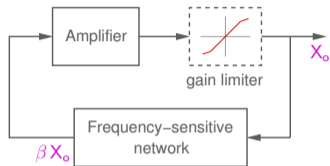
$$A(s)\beta(s) = A \frac{Z_2}{Z_1 + Z_2} = A \frac{R \parallel (1/sC)}{R + (1/sC) + R \parallel (1/sC)} = A \frac{sRC}{(sRC)^2 + 3sRC + 1}$$





Assuming  $R_{in} \rightarrow \infty$  for the amplifier, we get

$$A(s) \beta(s) = A \frac{Z_2}{Z_1 + Z_2} = A \frac{R \parallel (1/sC)}{R + (1/sC) + R \parallel (1/sC)} = A \frac{sRC}{(sRC)^2 + 3sRC + 1}.$$

For  $A\beta = 1$  (and with  $A$  equal to a real positive number),
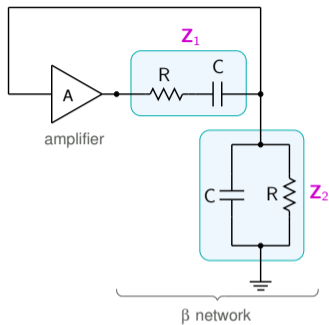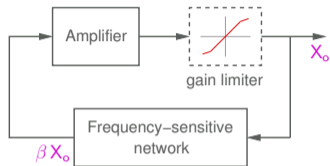
$$\frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1} \text{ must be real and equal to } 1/A.$$



Assuming  $R_{in} \rightarrow \infty$  for the amplifier, we get


$$A(s) \beta(s) = A \frac{Z_2}{Z_1 + Z_2} = A \frac{R \parallel (1/sC)}{R + (1/sC) + R \parallel (1/sC)} = A \frac{sRC}{(sRC)^2 + 3sRC + 1}$$

For  $A\beta = 1$  (and with  $A$  equal to a real positive number),


$$\frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1} \text{ must be real and equal to } 1/A.$$

$$\rightarrow \boxed{\omega = \frac{1}{RC}, A = 3}$$



# Wien bridge oscillator

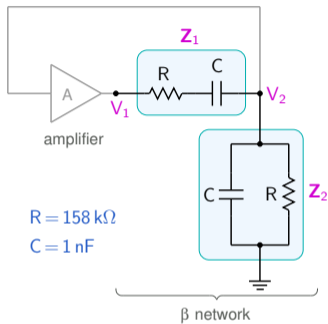
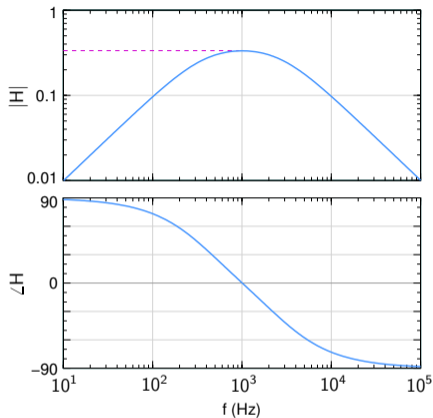
$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1}$$



# Wien bridge oscillator

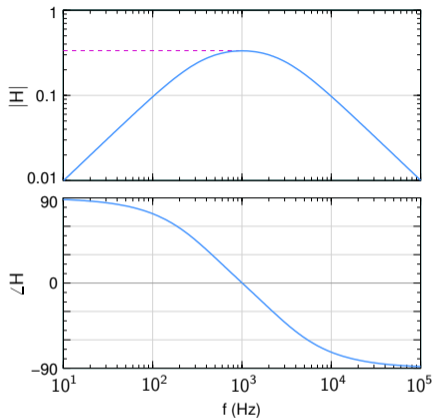
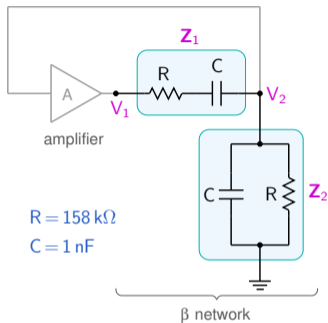


$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1}$$

Note that the condition  $\angle H = 0$  is satisfied only at one frequency,  $\omega_0 = 1/RC$ , i.e.,  $f_0 = 1 \text{ kHz}$ .

At this frequency,  $|H| = 0.33$ , i.e.,  $\beta(j\omega) = 1/3$ .

# Wien bridge oscillator

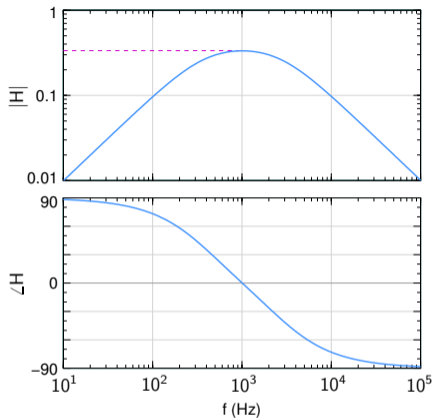
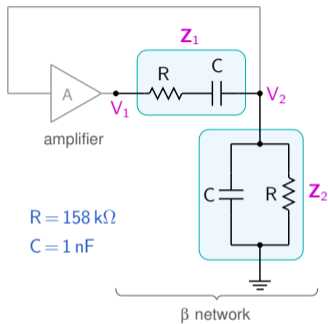


$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1}$$

Note that the condition  $\angle H = 0$  is satisfied only at one frequency,  $\omega_0 = 1/RC$ , i.e.,  $f_0 = 1 \text{ kHz}$ .

At this frequency,  $|H| = 0.33$ , i.e.,  $\beta(j\omega) = 1/3$ .

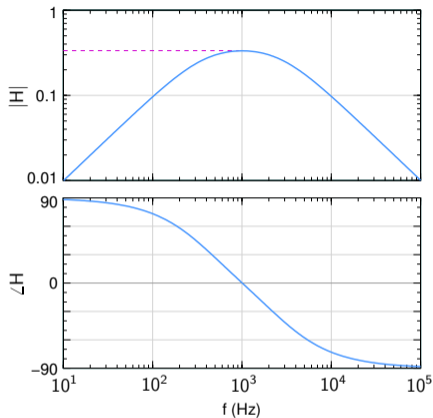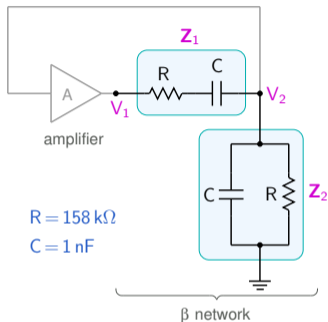For  $A\beta = 1 \rightarrow A = 3$ , as derived analytically.



$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{j\omega RC}{-\omega^2(RC)^2 + 3j\omega RC + 1}$$

Note that the condition  $\angle H = 0$  is satisfied only at one frequency,  $\omega_0 = 1/RC$ , i.e.,  $f_0 = 1 \text{ kHz}$ .


At this frequency,  $|H| = 0.33$ , i.e.,  $\beta(j\omega) = 1/3$ .

For  $A\beta = 1 \rightarrow A = 3$ , as derived analytically.


SEQUEL file: ee101\_osc\_1.sqproj

# Wien bridge oscillator


## Block diagram

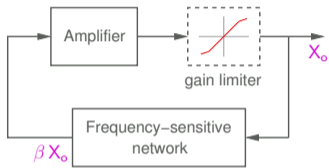

## Implementation

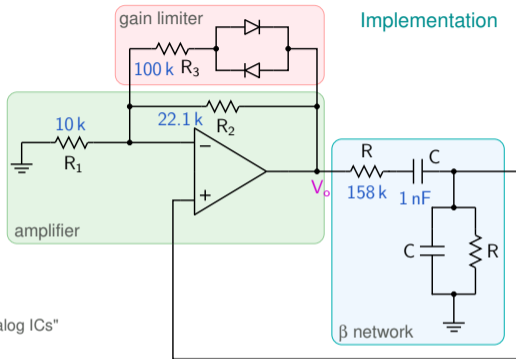

## Output voltage

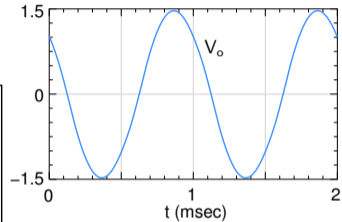


Ref.: S. Franco, "Design with Op Amps and analog ICs"

SEQUEL file: wien\_osc\_1.sqproj




# Wien bridge oscillator


## Block diagram

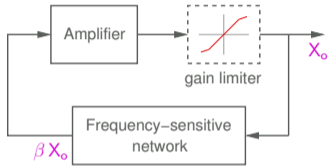

## Implementation

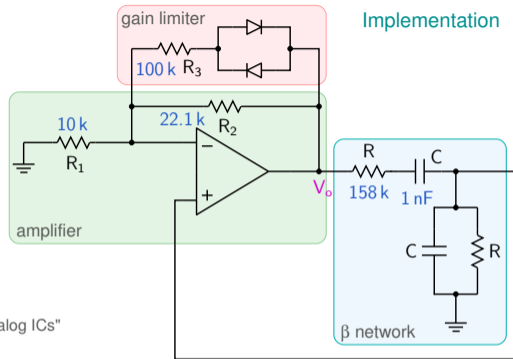

## Output voltage

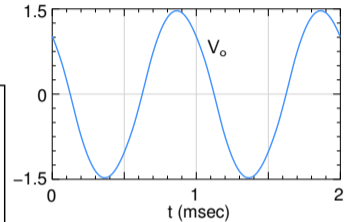


Ref.: S. Franco, "Design with Op Amps and analog ICs"

SEQUEL file: wien\_osc\_1.sqproj


$$* \omega_0 = \frac{1}{RC} = \frac{1}{(158\text{ k}) \times (1\text{ nF})} \rightarrow f_0 = 1\text{ kHz.}$$

# Wien bridge oscillator


## Block diagram

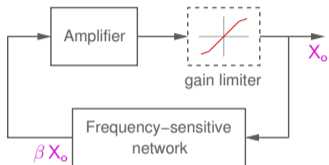

## Implementation

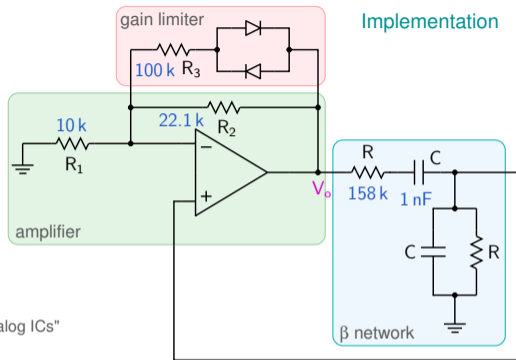

## Output voltage

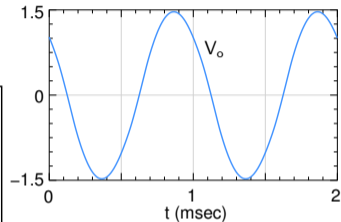

Ref.: S. Franco, "Design with Op Amps and analog ICs"


SEQUEL file: wien\_osc\_1.sqproj

$$* \omega_0 = \frac{1}{RC} = \frac{1}{(158 \text{ k}) \times (1 \text{ nF})} \rightarrow f_0 = 1 \text{ kHz.}$$


$$* \text{ Since the amplifier gain is required to be } A = 3, \text{ we must have } 1 + \frac{R_2}{R_1} = 3 \rightarrow R_2 = 2 R_1.$$

# Wien bridge oscillator


## Block diagram

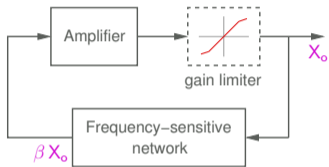

## Implementation

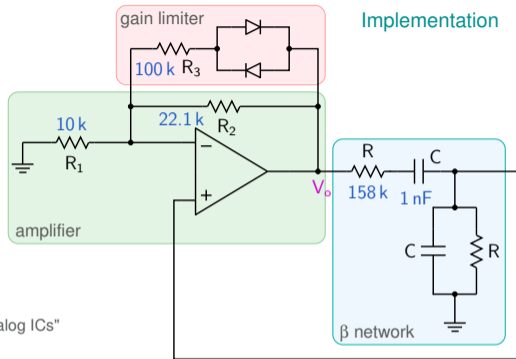

## Output voltage

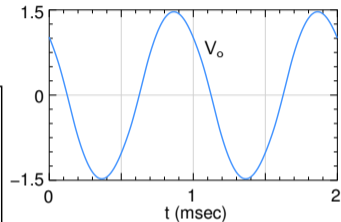

Ref.: S. Franco, "Design with Op Amps and analog ICs"

SEQUEL file: wien\_osc\_1.sqproj


$$* \omega_0 = \frac{1}{RC} = \frac{1}{(158 \text{ k}) \times (1 \text{ nF})} \rightarrow f_0 = 1 \text{ kHz.}$$

$$* \text{ Since the amplifier gain is required to be } A = 3, \text{ we must have } 1 + \frac{R_2}{R_1} = 3 \rightarrow R_2 = 2 R_1.$$


\* For gain limiting, diodes have been used. With one of the two diodes conducting,  $R_2 \rightarrow R_2 \parallel R_3$ , and the gain reduces.

# Wien bridge oscillator


## Block diagram

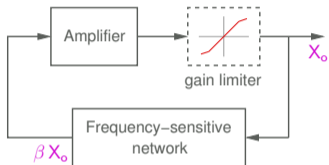

## Implementation

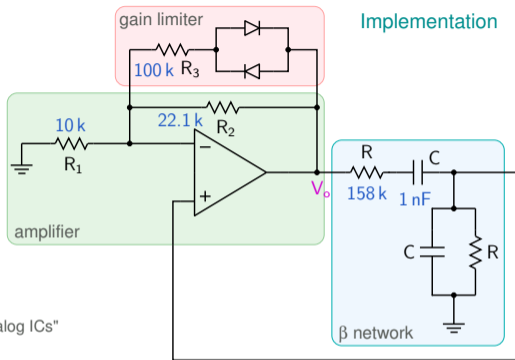

## Output voltage

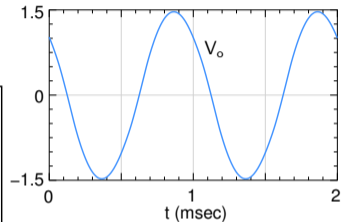

Ref.: S. Franco, "Design with Op Amps and analog ICs"


SEQUEL file: wien\_osc\_1.sqproj

$$* \omega_0 = \frac{1}{RC} = \frac{1}{(158\text{ k}) \times (1\text{ nF})} \rightarrow f_0 = 1\text{ kHz.}$$


$$* \text{ Since the amplifier gain is required to be } A = 3, \text{ we must have } 1 + \frac{R_2}{R_1} = 3 \rightarrow R_2 = 2R_1.$$

\* For gain limiting, diodes have been used. With one of the two diodes conducting,  $R_2 \rightarrow R_2 \parallel R_3$ , and the gain reduces.

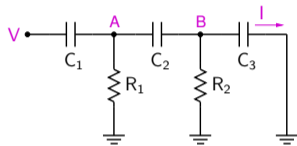\* Note that there was no need to consider loading of the  $\beta$  network by the amplifier because of the large input resistance of the op-amp. That is why  $\beta$  could be computed independently.




SEQUEL file: ee101\_osc\_4.sqproj

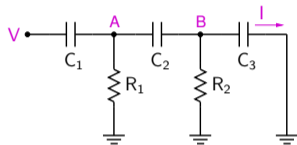

SEQUEL file: ee101\_osc\_4.sqproj

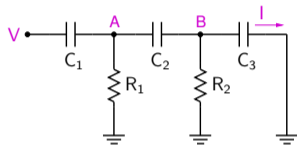Let  $R_1 = R_2 = R = 10\text{ k}$ ,  $G = 1/R$ , and  $C_1 = C_2 = C_3 = C = 16\text{ nF}$ .




SEQUEL file: ee101\_osc\_4.sqproj

Let  $R_1 = R_2 = R = 10 \text{ k}$ ,  $G = 1/R$ , and  $C_1 = C_2 = C_3 = C = 16 \text{ nF}$ .

Using nodal analysis,

$$sC(V_A - V) + GV_A + sC(V_A - V_B) = 0 \quad (1)$$
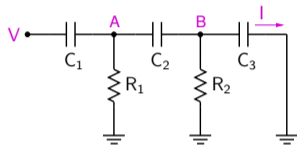
$$sC(V_B - V_A) + GV_B + sCV_B = 0 \quad (2)$$



SEQUEL file: ee101\_osc\_4.sqproj

Let  $R_1 = R_2 = R = 10 \text{ k}$ ,  $G = 1/R$ , and  $C_1 = C_2 = C_3 = C = 16 \text{ nF}$ .


Using nodal analysis,

$$sC(V_A - V) + GV_A + sC(V_A - V_B) = 0 \quad (1)$$


$$sC(V_B - V_A) + GV_B + sCV_B = 0 \quad (2)$$

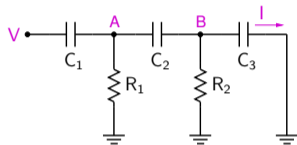Solving (1) and (2), we get  $I = \frac{1}{R} \frac{(sRC)^3}{3(sRC)^2 + 4sRC + 1} V$ .





SEQUEL file: ee101\_osc\_4.sqproj

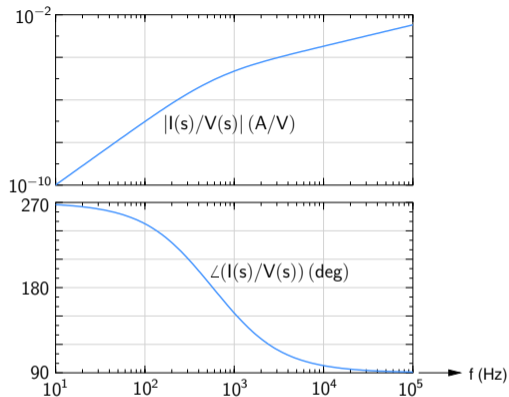


Let  $R_1 = R_2 = R = 10\text{ k}$ ,  $G = 1/R$ , and  $C_1 = C_2 = C_3 = C = 16\text{ nF}$ .

Using nodal analysis,


$$sC(V_A - V) + GV_A + sC(V_A - V_B) = 0 \quad (1)$$

$$sC(V_B - V_A) + GV_B + sCV_B = 0 \quad (2)$$

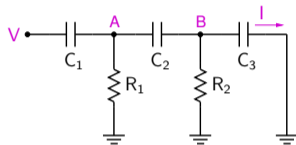Solving (1) and (2), we get  $I = \frac{1}{R} \frac{(sRC)^3}{3(sRC)^2 + 4sRC + 1} V$ .



SEQUEL file: ee101\_osc\_4.sqproj

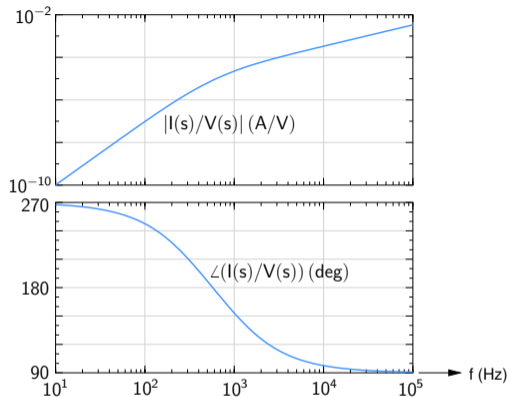

Let  $R_1 = R_2 = R = 10 \text{ k}$ ,  $G = 1/R$ , and  $C_1 = C_2 = C_3 = C = 16 \text{ nF}$ .


Using nodal analysis,

$$sC(V_A - V) + GV_A + sC(V_A - V_B) = 0 \quad (1)$$

$$sC(V_B - V_A) + GV_B + sCV_B = 0 \quad (2)$$

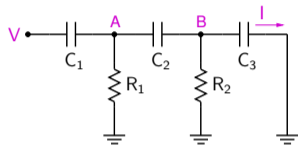Solving (1) and (2), we get  $I = \frac{1}{R} \frac{(sRC)^3}{3(sRC)^2 + 4sRC + 1} V$ .







SEQUEL file: ee101\_osc\_4.sqproj


( $R_1 = R_2 = R = 10\text{ k}$ , and  $C_1 = C_2 = C_3 = C = 16\text{ nF}$ .)
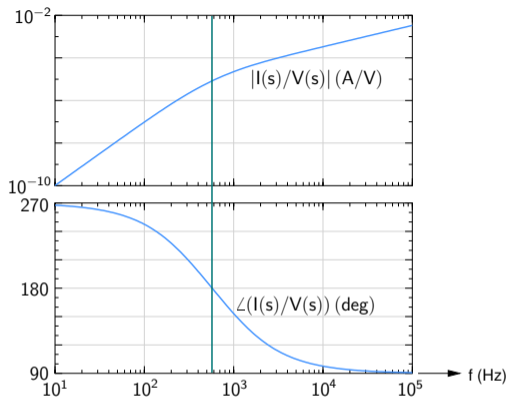
$$\beta(j\omega) = \frac{I(j\omega)}{V(j\omega)} = \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$



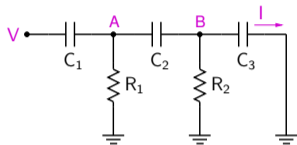

SEQUEL file: ee101\_osc\_4.sqproj

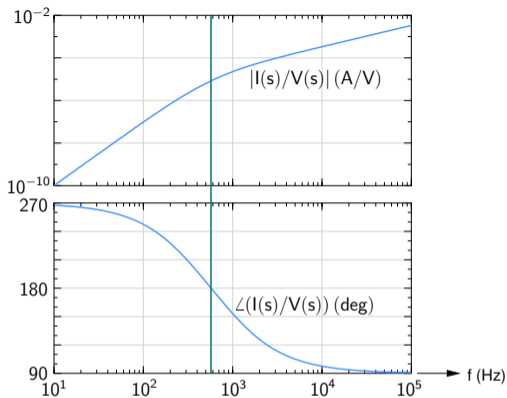


( $R_1 = R_2 = R = 10 \text{ k}$ , and  $C_1 = C_2 = C_3 = C = 16 \text{ nF}$ .)


$$\beta(j\omega) = \frac{I(j\omega)}{V(j\omega)} = \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$

For  $\beta(j\omega)$  to be a real number, the denominator must be purely imaginary.
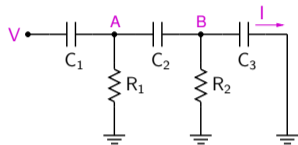
$$\rightarrow -3(\omega RC)^2 + 1 = 0, \text{ i.e., } 3(\omega RC)^2 = 1 \rightarrow \omega \equiv \omega_0 = \frac{1}{\sqrt{3}} \frac{1}{RC} \rightarrow f_0 = 574 \text{ Hz.}$$



SEQUEL file: ee101\_osc\_4.sqproj

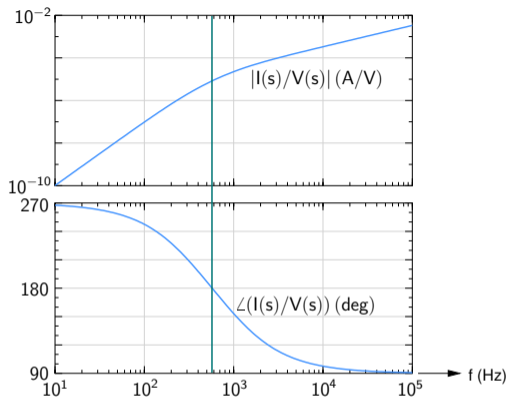


( $R_1 = R_2 = R = 10 \text{ k}$ , and  $C_1 = C_2 = C_3 = C = 16 \text{ nF}$ .)

$$\beta(j\omega) = \frac{I(j\omega)}{V(j\omega)} = \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$


For  $\beta(j\omega)$  to be a real number, the denominator must be purely imaginary.

$$\rightarrow -3(\omega RC)^2 + 1 = 0, \text{ i.e., } 3(\omega RC)^2 = 1 \rightarrow \omega \equiv \omega_0 = \frac{1}{\sqrt{3}} \frac{1}{RC} \rightarrow f_0 = 574 \text{ Hz.}$$
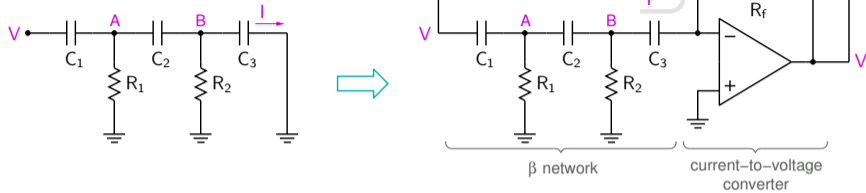
$$\text{Note that, at } \omega = \omega_0, \beta(j\omega_0) = \frac{1}{R} \frac{(j/\sqrt{3})^3}{4j/\sqrt{3}} = -\frac{1}{12R} = -8.33 \times 10^{-6}.$$




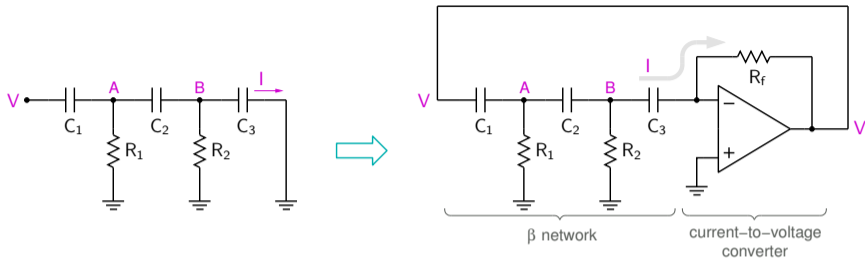Note that the functioning of the  $\beta$  network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the op-amp.



Note that the functioning of the  $\beta$  network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the op-amp.
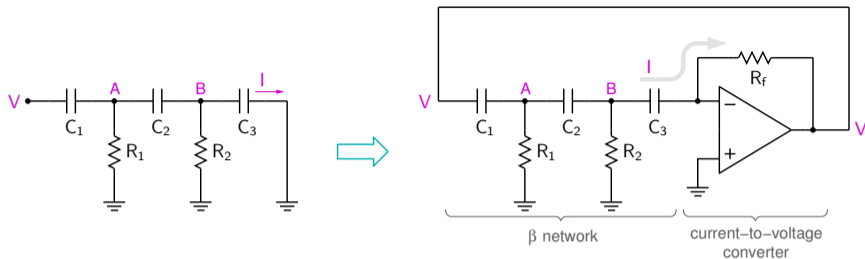
$$\text{The amplifier gain is } A(j\omega) \equiv \frac{V(j\omega)}{I(j\omega)} = \frac{0 - R_f I(j\omega)}{I(j\omega)} = -R_f.$$




Note that the functioning of the  $\beta$  network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the op-amp.

$$\text{The amplifier gain is } A(j\omega) \equiv \frac{V(j\omega)}{I(j\omega)} = \frac{0 - R_f I(j\omega)}{I(j\omega)} = -R_f.$$
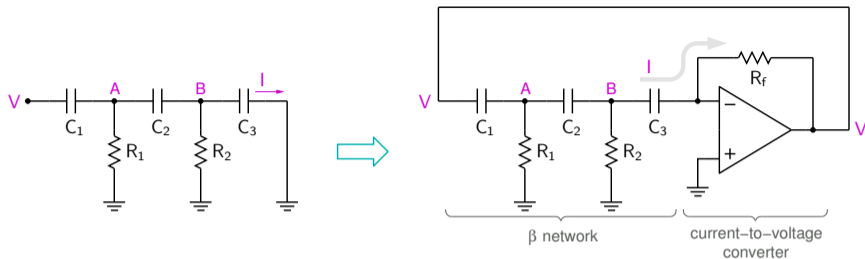
$$\rightarrow A(j\omega)\beta(j\omega) = -R_f \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}.$$






Note that the functioning of the  $\beta$  network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the op-amp.

$$\text{The amplifier gain is } A(j\omega) \equiv \frac{V(j\omega)}{I(j\omega)} = \frac{0 - R_f I(j\omega)}{I(j\omega)} = -R_f.$$

$$\rightarrow A(j\omega)\beta(j\omega) = -R_f \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}.$$
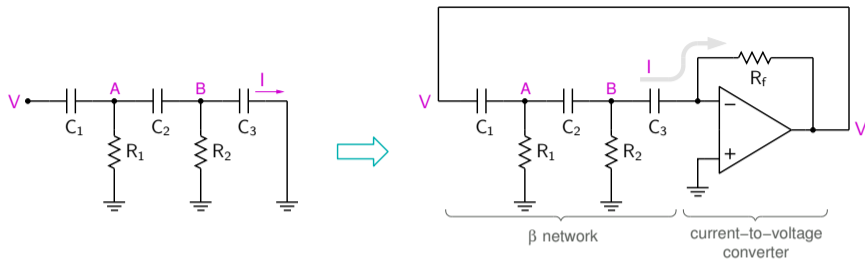
$$\text{As seen before, at } \rightarrow \omega = \omega_0 = \frac{1}{\sqrt{3}} \frac{1}{RC}, \text{ we have } \frac{I(j\omega)}{V(j\omega)} = -\frac{1}{12R}.$$




Note that the functioning of the  $\beta$  network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the op-amp.

$$\text{The amplifier gain is } A(j\omega) \equiv \frac{V(j\omega)}{I(j\omega)} = \frac{0 - R_f I(j\omega)}{I(j\omega)} = -R_f.$$

$$\rightarrow A(j\omega)\beta(j\omega) = -R_f \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}.$$

$$\text{As seen before, at } \omega = \omega_0 = \frac{1}{\sqrt{3}} \frac{1}{RC}, \text{ we have } \frac{I(j\omega)}{V(j\omega)} = -\frac{1}{12R}.$$
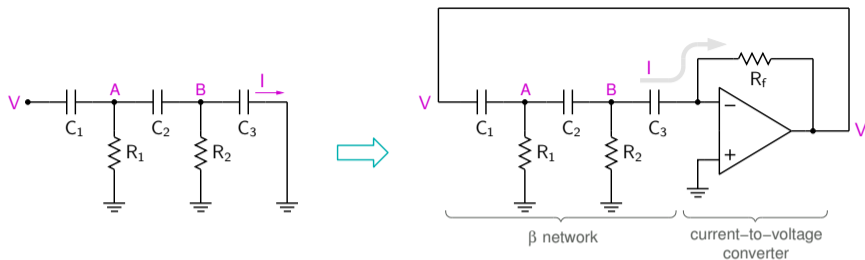
$$\text{For the circuit to oscillate, we need } A\beta = 1 \rightarrow -R_f \left( -\frac{1}{12R} \right) = 1, \text{ i.e., } \boxed{R_f = 12R}$$



Note that the functioning of the  $\beta$  network as a stand-alone circuit (left figure) and as a feedback block (right figure) is the same, thanks to the virtual ground provided by the op-amp.

$$\text{The amplifier gain is } A(j\omega) \equiv \frac{V(j\omega)}{I(j\omega)} = \frac{0 - R_f I(j\omega)}{I(j\omega)} = -R_f.$$


$$\rightarrow A(j\omega)\beta(j\omega) = -R_f \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}.$$

$$\text{As seen before, at } \omega = \omega_0 = \frac{1}{\sqrt{3}} \frac{1}{RC}, \text{ we have } \frac{I(j\omega)}{V(j\omega)} = -\frac{1}{12R}.$$


$$\text{For the circuit to oscillate, we need } A\beta = 1 \rightarrow -R_f \left( -\frac{1}{12R} \right) = 1, \text{ i.e., } \boxed{R_f = 12R}$$

In addition, we employ a gain limiter circuit to complete the oscillator design.


## Block diagram

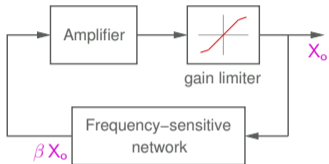

## Implementation

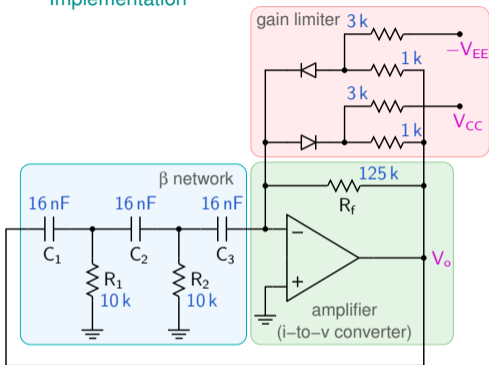

## Output voltage

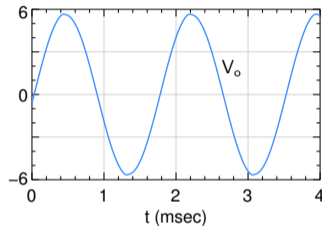


Ref.: Sedra and Smith, "Microelectronic circuits"


SEQUEL file: ee101\_osc\_3.sqproj

$$\omega_0 = \frac{1}{\sqrt{3}} \frac{1}{RC} \rightarrow f_0 = 574 \text{ Hz}, T = 1.74 \text{ ms}.$$

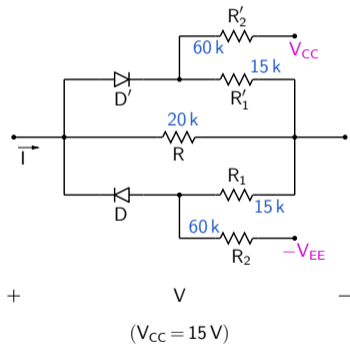
# Amplitude control using gain limiting network



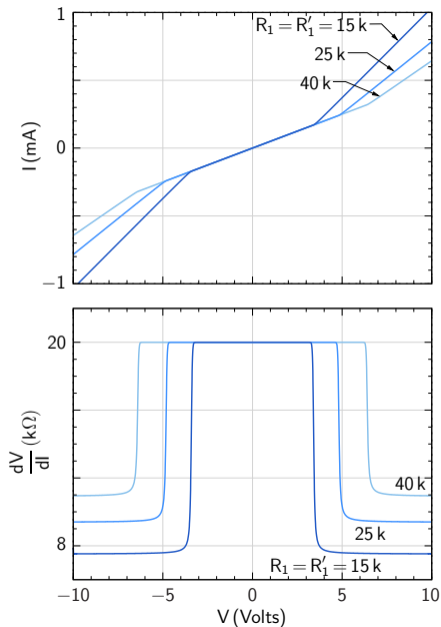
SEQUEL file: ee101\_diode\_circuit\_15.sqproj



## Inverting amplifier, revisited

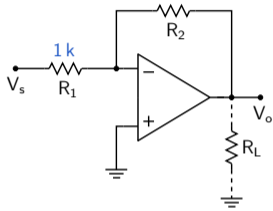


## Inverting amplifier, revisited

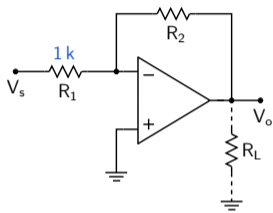

\* As seen earlier,  $A_V = -R_2/R_1 \rightarrow |A_V|$  should be independent of the signal frequency.


## Inverting amplifier, revisited

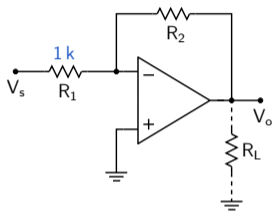


- \* As seen earlier,  $A_V = -R_2/R_1 \rightarrow |A_V|$  should be independent of the signal frequency.
- \* However, a measurement with a real op-amp will show that  $|A_V|$  starts reducing at higher frequencies.



## Inverting amplifier, revisited

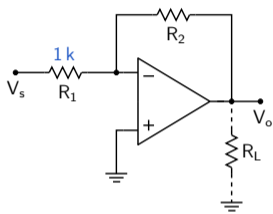


SEQUEL file: ee101\_inv\_amp\_3.sqproj

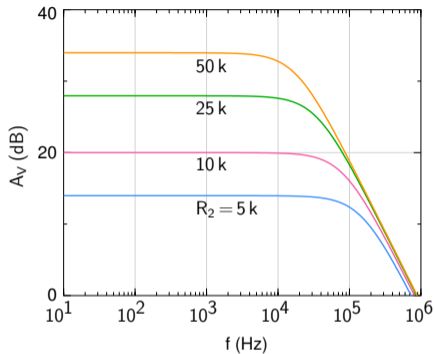


- \* As seen earlier,  $A_V = -R_2/R_1 \rightarrow |A_V|$  should be independent of the signal frequency.
- \* However, a measurement with a real op-amp will show that  $|A_V|$  starts reducing at higher frequencies.


## Inverting amplifier, revisited

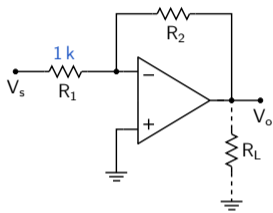


SEQUEL file: ee101\_inv\_amp\_3.sqproj

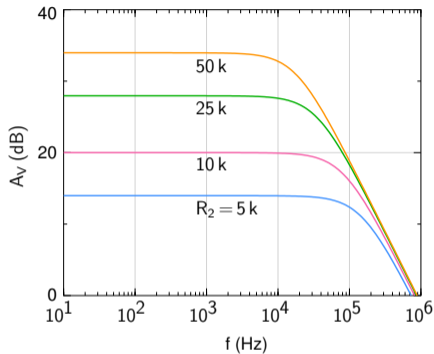

- \* As seen earlier,  $A_V = -R_2/R_1 \rightarrow |A_V|$  should be independent of the signal frequency.
- \* However, a measurement with a real op-amp will show that  $|A_V|$  starts reducing at higher frequencies.
- \* If  $|A_V|$  is increased, the gain “roll-off” starts at lower frequencies.


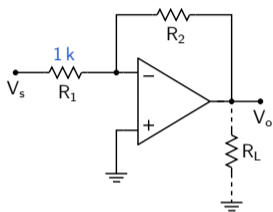


SEQUEL file: ee101\_inv\_amp\_3.sqproj

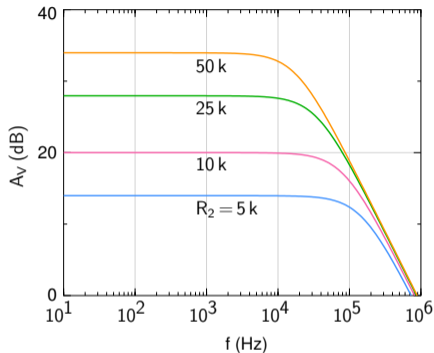



- \* As seen earlier,  $A_V = -R_2/R_1 \rightarrow |A_V|$  should be independent of the signal frequency.
- \* However, a measurement with a real op-amp will show that  $|A_V|$  starts reducing at higher frequencies.
- \* If  $|A_V|$  is increased, the gain “roll-off” starts at lower frequencies.
- \* This behaviour has to do with the frequency response of the op-amp which we have not considered so far.

## Frequency response of Op-Amp 741

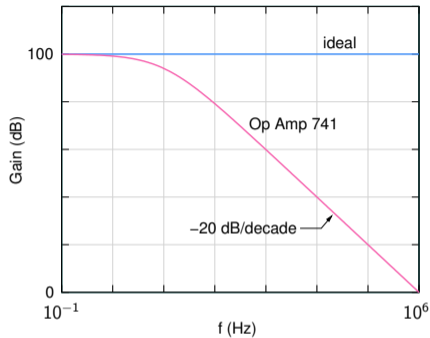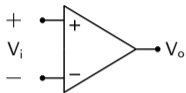



The gain of the 741 op-amp starts falling at rather low frequencies, with  $f_c \simeq 10$  Hz!

## Frequency response of Op-Amp 741

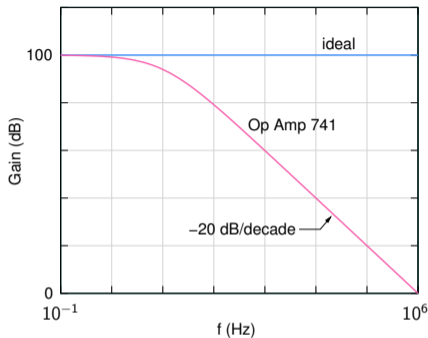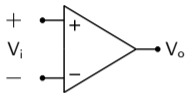

The gain of the 741 op-amp starts falling at rather low frequencies, with  $f_c \simeq 10$  Hz!

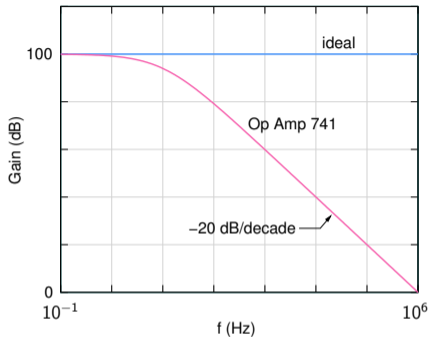
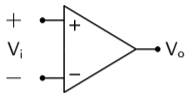
The 741 op-amp (and many others) are *designed* with this feature to ensure that, in typical amplifier applications, the overall circuit is stable (and not oscillatory).



The gain of the 741 op-amp starts falling at rather low frequencies, with  $f_c \simeq 10$  Hz!

The 741 op-amp (and many others) are *designed* with this feature to ensure that, in typical amplifier applications, the overall circuit is stable (and not oscillatory).

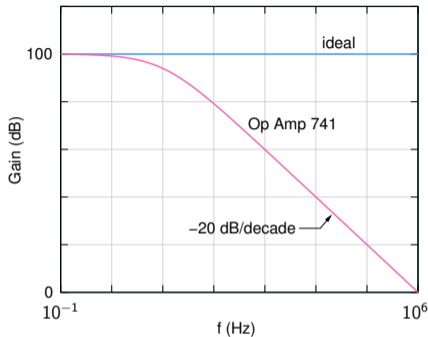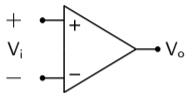In other words, the op-amp has been *internally compensated* for stability.



The gain of the 741 op-amp starts falling at rather low frequencies, with  $f_c \simeq 10$  Hz!

The 741 op-amp (and many others) are *designed* with this feature to ensure that, in typical amplifier applications, the overall circuit is stable (and not oscillatory).


In other words, the op-amp has been *internally compensated* for stability.

The gain of the 741 op-amp can be represented by,

$$A(s) = \frac{A_0}{1 + s/\omega_c},$$


with  $A_0 \approx 10^5$  (i.e., 100 dB),  $\omega_c \approx 2\pi \times 10$  rad/s.

# Frequency response of Op-Amp 741

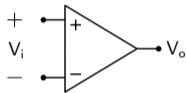


$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_c}, \quad \omega_c \approx 2\pi \times 10 \text{ rad/s.}$$
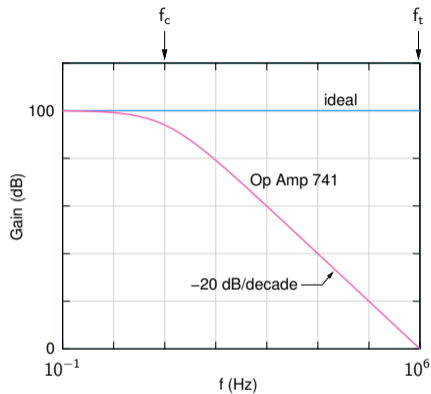
$$\text{For } \omega \gg \omega_c, \text{ we have } A(j\omega) \approx \frac{A_0}{j\omega/\omega_c}.$$






## Frequency response of Op-Amp 741


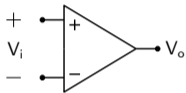


$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_c}, \quad \omega_c \approx 2\pi \times 10 \text{ rad/s.}$$

$$\text{For } \omega \gg \omega_c, \text{ we have } A(j\omega) \approx \frac{A_0}{j\omega/\omega_c}.$$

$|A(j\omega)|$  becomes 1 when  $A_0 = \omega/\omega_c$ , i.e.,  $\omega = A_0\omega_c$ .

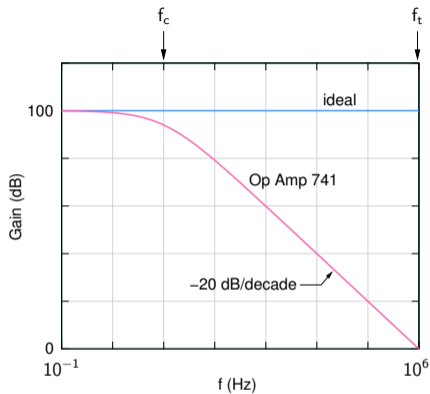

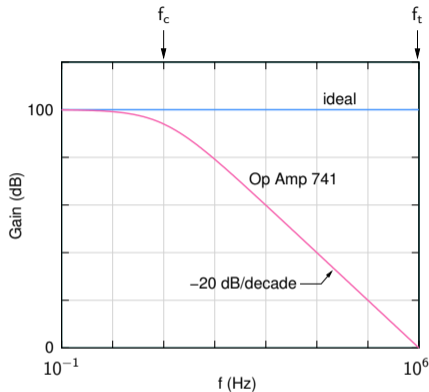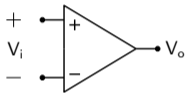



$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_c}, \quad \omega_c \approx 2\pi \times 10 \text{ rad/s.}$$

For  $\omega \gg \omega_c$ , we have  $A(j\omega) \approx \frac{A_0}{j\omega/\omega_c}$ .

$|A(j\omega)|$  becomes 1 when  $A_0 = \omega/\omega_c$ , i.e.,  $\omega = A_0\omega_c$ .

This frequency,  $\omega_t = A_0\omega_c$ , is called the unity-gain frequency.

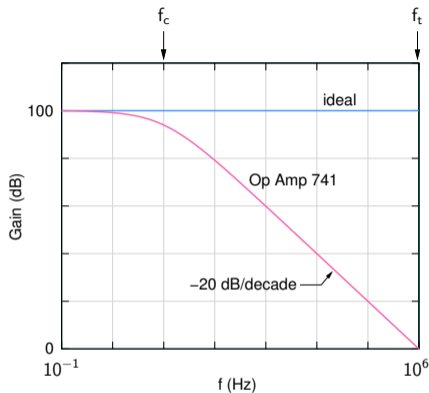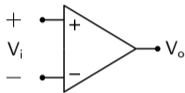For the 741 op-amp,  $f_t = A_0 f_c \approx 10^5 \times 10 = 10^6 \text{ Hz}$ .



$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_c}, \quad \omega_c \approx 2\pi \times 10 \text{ rad/s.}$$

For  $\omega \gg \omega_c$ , we have  $A(j\omega) \approx \frac{A_0}{j\omega/\omega_c}$ .


$|A(j\omega)|$  becomes 1 when  $A_0 = \omega/\omega_c$ , i.e.,  $\omega = A_0\omega_c$ .

This frequency,  $\omega_t = A_0\omega_c$ , is called the unity-gain frequency.


For the 741 op-amp,  $f_t = A_0 f_c \approx 10^5 \times 10 = 10^6 \text{ Hz}$ .

Let us see how the frequency response of the 741 op-amp affects the gain of an inverting amplifier.

# Inverting amplifier, revisited

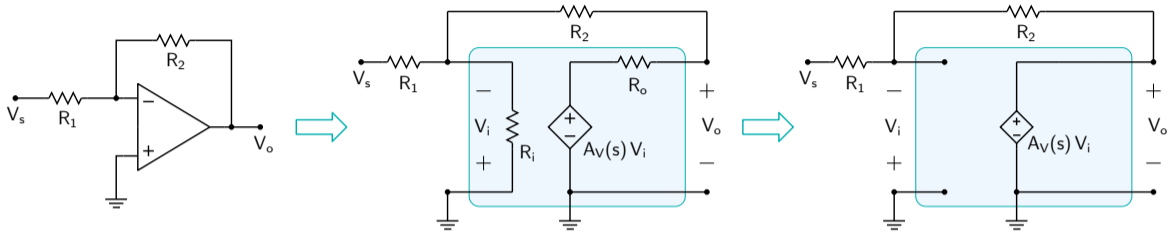


## Inverting amplifier, revisited

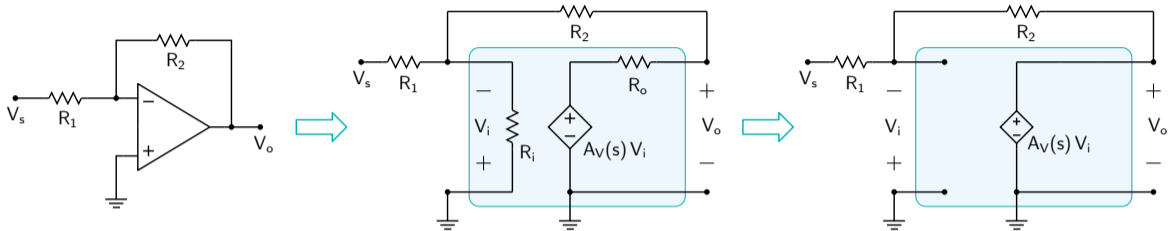

Assuming  $R_i$  to be large and  $R_o$  to be small, we get

$$-V_i(s) = V_s(s) \frac{R_2}{R_1 + R_2} + V_o(s) \frac{R_1}{R_1 + R_2}.$$

## Inverting amplifier, revisited

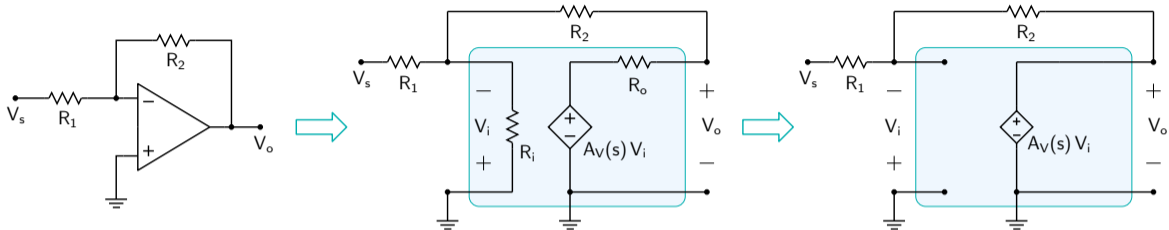


Assuming  $R_i$  to be large and  $R_o$  to be small, we get

$$-V_i(s) = V_s(s) \frac{R_2}{R_1 + R_2} + V_o(s) \frac{R_1}{R_1 + R_2}.$$

Using  $V_o(s) = A_V(s) V_i(s)$  and  $A_V(s) = \frac{A_0}{1 + s/\omega_c}$ , we get

$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{\left[1 + \left(\frac{R_1 + R_2}{R_1}\right) \frac{1}{A_0}\right] + \left(\frac{R_1 + R_2}{R_1 A_0}\right) \frac{s}{\omega_c}}$$

## Inverting amplifier, revisited

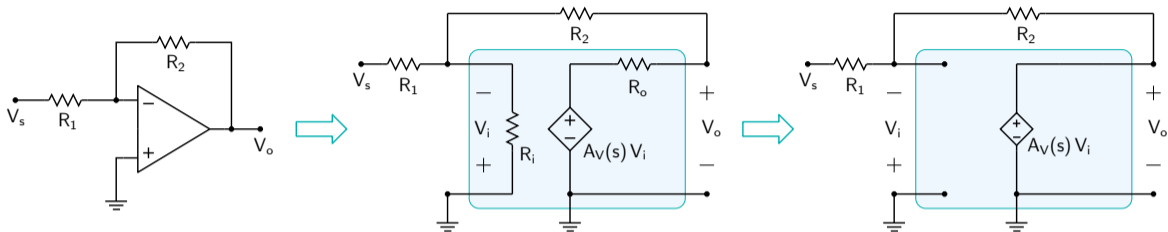


Assuming  $R_i$  to be large and  $R_o$  to be small, we get

$$-V_i(s) = V_s(s) \frac{R_2}{R_1 + R_2} + V_o(s) \frac{R_1}{R_1 + R_2}.$$

Using  $V_o(s) = A_V(s) V_i(s)$  and  $A_V(s) = \frac{A_0}{1 + s/\omega_c}$ , we get

$$\begin{aligned} \frac{V_o(s)}{V_s(s)} &= -\frac{R_2}{R_1} \frac{1}{\left[1 + \left(\frac{R_1 + R_2}{R_1}\right) \frac{1}{A_0}\right] + \left(\frac{R_1 + R_2}{R_1 A_0}\right) \frac{s}{\omega_c}} \\ &\approx -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c}, \quad \text{with } \omega'_c = \frac{\omega_c A_0}{1 + R_2/R_1} = \frac{\omega_t}{1 + R_2/R_1}. \end{aligned}$$


## Inverting amplifier, revisited

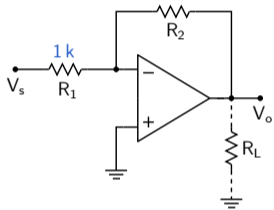

SEQUEL file: ee101\_inv\_amp\_3.sqproj




## Inverting amplifier, revisited

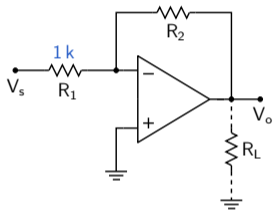

SEQUEL file: ee101\_inv\_amp\_3.sqproj

$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

## Inverting amplifier, revisited

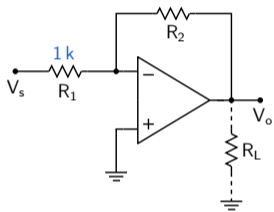


$R_2$	gain (dB)	$f_c'$ (kHz)
5 k	14	167

SEQUEL file: ee101\_inv\_amp\_3.sqproj


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

## Inverting amplifier, revisited

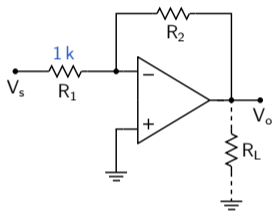


$R_2$	gain (dB)	$f_c'$ (kHz)
5 k	14	167

SEQUEL file: ee101\_inv\_amp\_3.sqproj

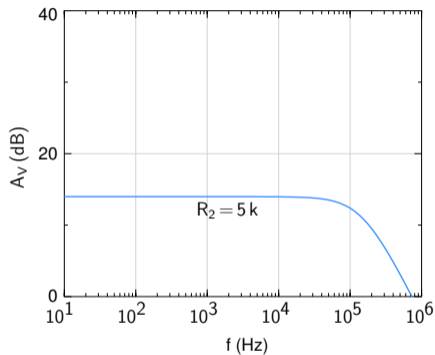


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega_c'} \quad \omega_c' = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

## Inverting amplifier, revisited

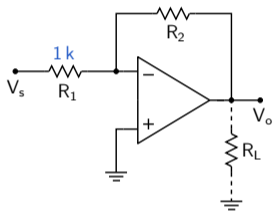


$R_2$	gain (dB)	$f_c'$ (kHz)
5 k	14	167
10 k	20	91

SEQUEL file: ee101\_inv\_amp\_3.sqproj

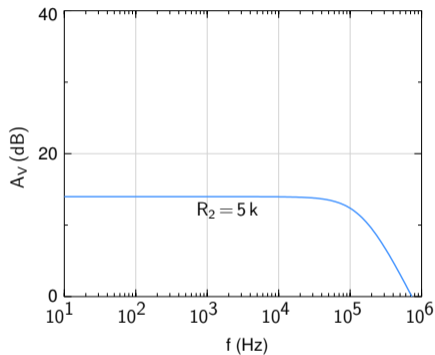


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega_c'} \quad \omega_c' = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

## Inverting amplifier, revisited

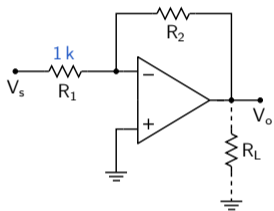


$R_2$	gain (dB)	$f'_c$ (kHz)
5 k	14	167
10 k	20	91

SEQUEL file: ee101\_inv\_amp\_3.sqproj

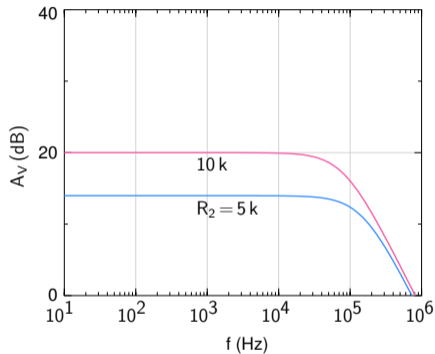


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

## Inverting amplifier, revisited

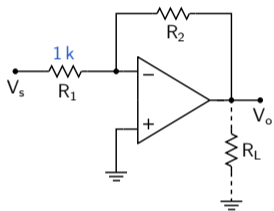


$R_2$	gain (dB)	$f'_c$ (kHz)
5 k	14	167
10 k	20	91
25 k	28	38

SEQUEL file: ee101\_inv\_amp\_3.sqproj

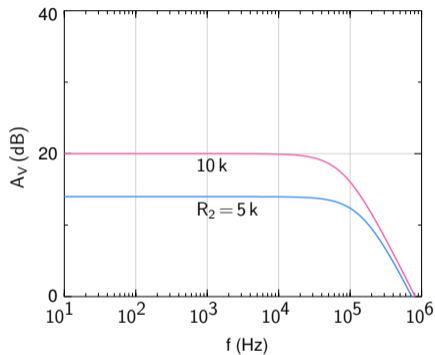


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

## Inverting amplifier, revisited

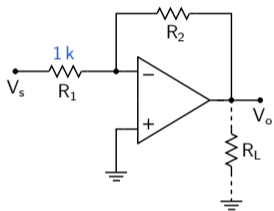


$R_2$	gain (dB)	$f'_c$ (kHz)
5 k	14	167
10 k	20	91
25 k	28	38

SEQUEL file: ee101\_inv\_amp\_3.sqproj

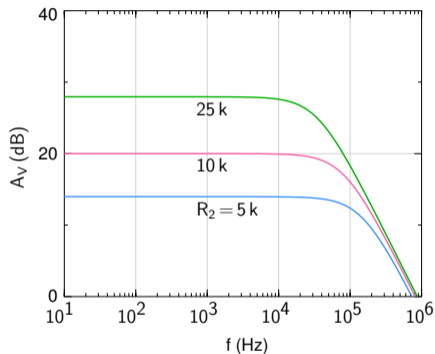


$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$

## Inverting amplifier, revisited

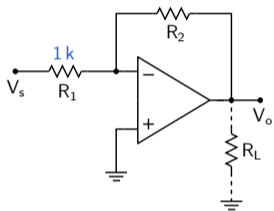

$R_2$	gain (dB)	$f'_c$ (kHz)
5 k	14	167
10 k	20	91
25 k	28	38
50 k	34	19.6


SEQUEL file: ee101\_inv\_amp\_3.sqproj

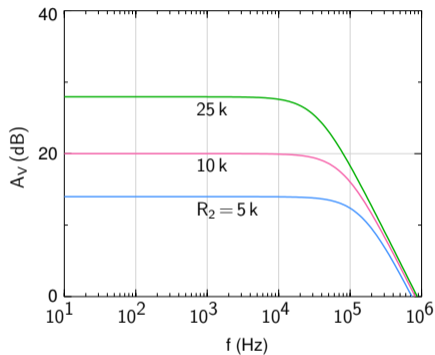

$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$




## Inverting amplifier, revisited

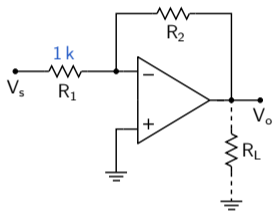

$R_2$	gain (dB)	$f_c'$ (kHz)
5 k	14	167
10 k	20	91
25 k	28	38
50 k	34	19.6

SEQUEL file: ee101\_inv\_amp\_3.sqproj

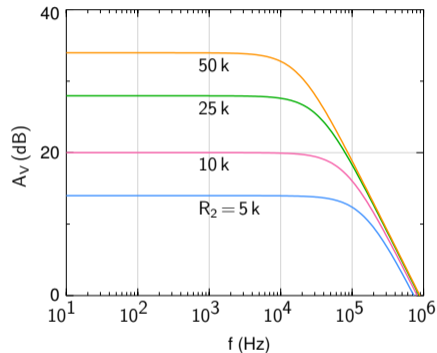

$$\frac{V_o(s)}{V_s(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s/\omega'_c} \quad \omega'_c = \frac{\omega_t}{1 + R_2/R_1}, \quad (f_t = 1 \text{ MHz}).$$