

RC and RL Circuits with Piecewise Constant Sources





M. B. Patil


mbpatil@ee.iitb.ac.in

www.ee.iitb.ac.in/~sequel

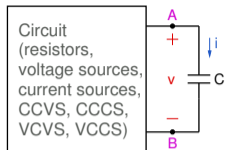
Department of Electrical Engineering
Indian Institute of Technology Bombay



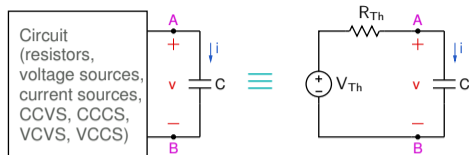

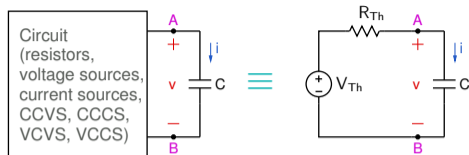


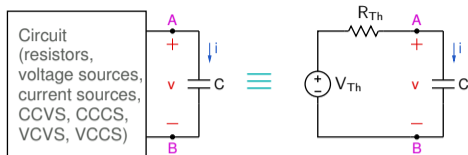* If all sources are DC (constant), $V_{Th} = \text{constant}$.



* If all sources are DC (constant), $V_{Th} = \text{constant}$.

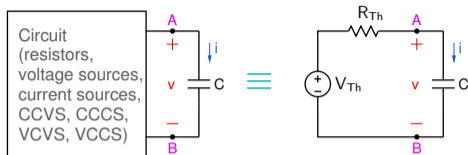* KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$.




* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$.

* Homogeneous solution:
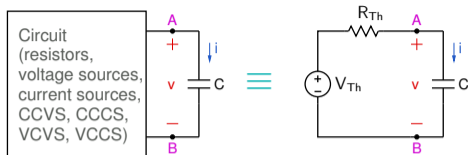
$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left(\frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$




* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$.

* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left(\frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$
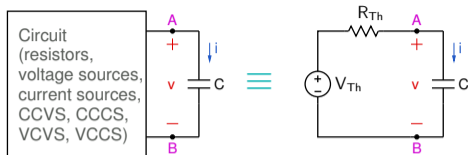
$$\rightarrow \frac{dv}{v} = -\frac{dt}{\tau} \rightarrow \log v = -\frac{t}{\tau} + K_0 \rightarrow v^{(h)} = \exp[(-t/\tau) + K_0] = K \exp(-t/\tau).$$



* If all sources are DC (constant), $V_{Th} = \text{constant}$.


* KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$.

* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left(\frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$

$$\rightarrow \frac{dv}{v} = -\frac{dt}{\tau} \rightarrow \log v = -\frac{t}{\tau} + K_0 \rightarrow v^{(h)} = \exp[(-t/\tau) + K_0] = K \exp(-t/\tau).$$

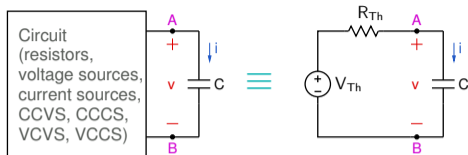* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $i = 0$, and we get $v^{(p)} = V_{Th}$ as a particular solution (which happens to be simply a constant).



* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$.


* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left(\frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$

$$\rightarrow \frac{dv}{v} = -\frac{dt}{\tau} \rightarrow \log v = -\frac{t}{\tau} + K_0 \rightarrow v^{(h)} = \exp[(-t/\tau) + K_0] = K \exp(-t/\tau).$$

* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $i = 0$, and we get $v^{(p)} = V_{Th}$ as a particular solution (which happens to be simply a constant).

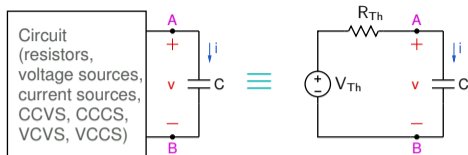* $v = v^{(h)} + v^{(p)} = K \exp(-t/\tau) + V_{Th}$.



* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$.

* Homogeneous solution:


$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left(\frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$

$$\rightarrow \frac{dv}{v} = -\frac{dt}{\tau} \rightarrow \log v = -\frac{t}{\tau} + K_0 \rightarrow v^{(h)} = \exp[(-t/\tau) + K_0] = K \exp(-t/\tau).$$

* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $i = 0$, and we get $v^{(p)} = V_{Th}$ as a particular solution (which happens to be simply a constant).


* $v = v^{(h)} + v^{(p)} = K \exp(-t/\tau) + V_{Th}$.

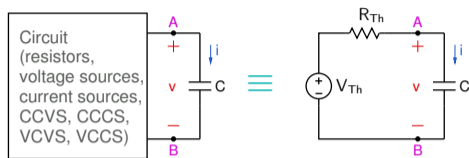* In general, $v(t) = A \exp(-t/\tau) + B$, where A and B can be obtained from known conditions on v .




- * If all sources are DC (constant), we have $v(t) = A \exp(-t/\tau) + B$, $\tau = R_{Th}C$.

RC circuits with DC sources (continued)

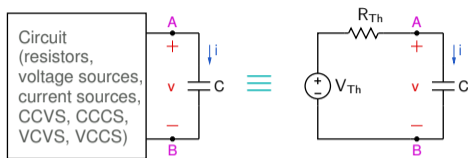


- * If all sources are DC (constant), we have $v(t) = A \exp(-t/\tau) + B$, $\tau = R_{Th}C$.
- * $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.

RC circuits with DC sources (continued)

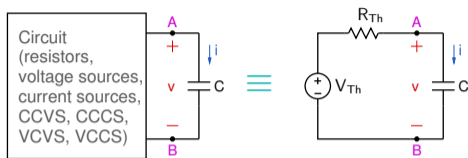

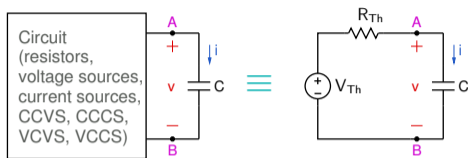- * If all sources are DC (constant), we have $v(t) = A \exp(-t/\tau) + B$, $\tau = R_{Th}C$.
- * $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.
- * As $t \rightarrow \infty$, $i \rightarrow 0$, i.e., the capacitor behaves like an open circuit since all derivatives vanish.



- * If all sources are DC (constant), we have $v(t) = A \exp(-t/\tau) + B$, $\tau = R_{Th}C$.
- * $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.
- * As $t \rightarrow \infty$, $i \rightarrow 0$, i.e., the capacitor behaves like an open circuit since all derivatives vanish.
- * Since the circuit in the black box is linear, *any* variable (current or voltage) in the circuit can be expressed as $x(t) = K_1 \exp(-t/\tau) + K_2$, where K_1 and K_2 can be obtained from suitable conditions on $x(t)$.

t/τ	$e^{-t/\tau}$	$1 - e^{-t/\tau}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	4.9787×10^{-2}	0.9502
4.0	1.8315×10^{-2}	0.9817
5.0	6.7379×10^{-3}	0.9933

t/τ	$e^{-t/\tau}$	$1 - e^{-t/\tau}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	4.9787×10^{-2}	0.9502
4.0	1.8315×10^{-2}	0.9817
5.0	6.7379×10^{-3}	0.9933

* For $t/\tau = 5$, $e^{-t/\tau} \simeq 0$, $1 - e^{-t/\tau} \simeq 1$.


t/τ	$e^{-t/\tau}$	$1 - e^{-t/\tau}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	4.9787×10^{-2}	0.9502
4.0	1.8315×10^{-2}	0.9817
5.0	6.7379×10^{-3}	0.9933

* For $t/\tau = 5$, $e^{-t/\tau} \simeq 0$, $1 - e^{-t/\tau} \simeq 1$.

* We can say that the transient lasts for about 5 time constants.

Plot of $f(t) = e^{-t/\tau}$

t/τ	$e^{-t/\tau}$	$1 - e^{-t/\tau}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	4.9787×10^{-2}	0.9502
4.0	1.8315×10^{-2}	0.9817
5.0	6.7379×10^{-3}	0.9933

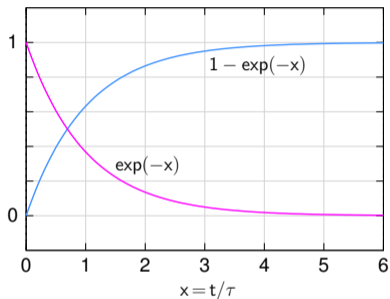

* For $t/\tau = 5$, $e^{-t/\tau} \simeq 0$, $1 - e^{-t/\tau} \simeq 1$.

* We can say that the transient lasts for about 5 time constants.

Plot of $f(t) = A e^{-t/\tau} + B$

Plot of $f(t) = A e^{-t/\tau} + B$

* At $t=0$, $f = A + B$.

Plot of $f(t) = A e^{-t/\tau} + B$

- * At $t=0$, $f = A + B$.
- * As $t \rightarrow \infty$, $f \rightarrow B$.

Plot of $f(t) = A e^{-t/\tau} + B$

- * At $t=0$, $f = A + B$.
- * As $t \rightarrow \infty$, $f \rightarrow B$.
- * The graph of $f(t)$ lies between $(A + B)$ and B .

Note: If $A > 0$, $A + B > B$. If $A < 0$, $A + B < B$.

Plot of $f(t) = A e^{-t/\tau} + B$

- * At $t=0$, $f = A + B$.
- * As $t \rightarrow \infty$, $f \rightarrow B$.
- * The graph of $f(t)$ lies between $(A + B)$ and B .

Note: If $A > 0$, $A + B > B$. If $A < 0$, $A + B < B$.

- * At $t=0$, $\frac{df}{dt} = A e^{-t/\tau} \left(-\frac{1}{\tau}\right) = -\frac{A}{\tau}$.

If $A > 0$, the derivative (slope) at $t=0$ is negative; else, it is positive.

Plot of $f(t) = A e^{-t/\tau} + B$

* At $t=0$, $f = A + B$.

* As $t \rightarrow \infty$, $f \rightarrow B$.

* The graph of $f(t)$ lies between $(A + B)$ and B .

Note: If $A > 0$, $A + B > B$. If $A < 0$, $A + B < B$.

* At $t=0$, $\frac{df}{dt} = A e^{-t/\tau} \left(-\frac{1}{\tau}\right) = -\frac{A}{\tau}$.

If $A > 0$, the derivative (slope) at $t=0$ is negative; else, it is positive.

* As $t \rightarrow \infty$, $\frac{df}{dt} \rightarrow 0$, i.e., f becomes constant (equal to B).

Plot of $f(t) = A e^{-t/\tau} + B$


- * At $t=0$, $f = A + B$.
- * As $t \rightarrow \infty$, $f \rightarrow B$.
- * The graph of $f(t)$ lies between $(A + B)$ and B .

Note: If $A > 0$, $A + B > B$. If $A < 0$, $A + B < B$.

- * At $t=0$, $\frac{df}{dt} = A e^{-t/\tau} \left(-\frac{1}{\tau}\right) = -\frac{A}{\tau}$.

If $A > 0$, the derivative (slope) at $t=0$ is negative; else, it is positive.

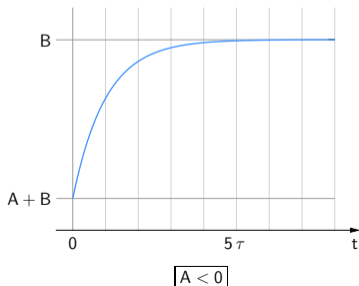- * As $t \rightarrow \infty$, $\frac{df}{dt} \rightarrow 0$, i.e., f becomes constant (equal to B).



Plot of $f(t) = A e^{-t/\tau} + B$


- * At $t=0$, $f = A + B$.
- * As $t \rightarrow \infty$, $f \rightarrow B$.
- * The graph of $f(t)$ lies between $(A + B)$ and B .

Note: If $A > 0$, $A + B > B$. If $A < 0$, $A + B < B$.


- * At $t=0$, $\frac{df}{dt} = A e^{-t/\tau} \left(-\frac{1}{\tau}\right) = -\frac{A}{\tau}$.

If $A > 0$, the derivative (slope) at $t=0$ is negative; else, it is positive.

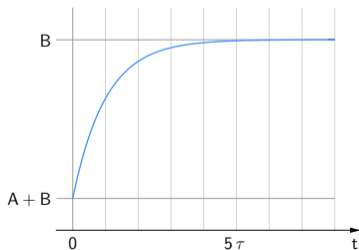
- * As $t \rightarrow \infty$, $\frac{df}{dt} \rightarrow 0$, i.e., f becomes constant (equal to B).





$A < 0$

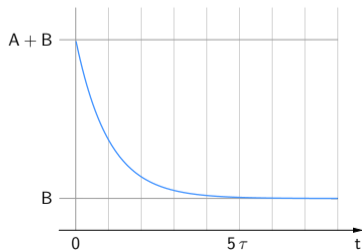


$A > 0$

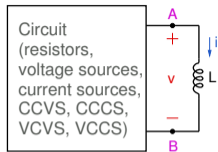

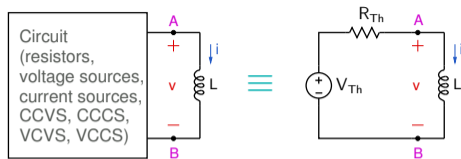

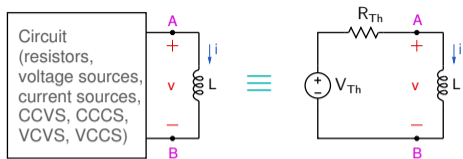


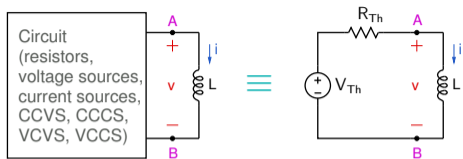* If all sources are DC (constant), $V_{Th} = \text{constant}$.



* If all sources are DC (constant), $V_{Th} = \text{constant}$.

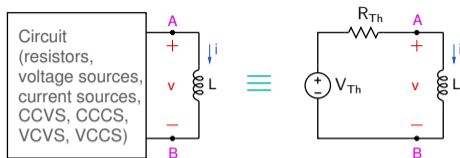* KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.




* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.

* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$
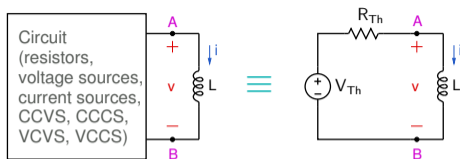
$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$



* If all sources are DC (constant), $V_{Th} = \text{constant}$.


* KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.

* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$

$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

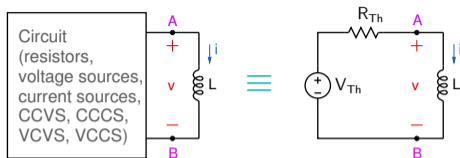* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $v = 0$, and we get $i^{(p)} = V_{Th}/R_{Th}$ as a particular solution (which happens to be simply a constant).



* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.


* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$

$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $v = 0$, and we get $i^{(p)} = V_{Th}/R_{Th}$ as a particular solution (which happens to be simply a constant).

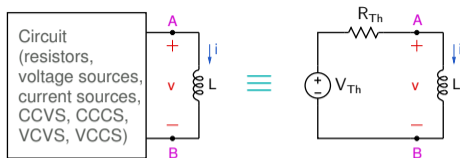* $i = i^{(h)} + i^{(p)} = K \exp(-t/\tau) + V_{Th}/R_{Th}$.



* If all sources are DC (constant), $V_{Th} = \text{constant}$.

* KVL: $V_{Th} = R_{Th} i + L \frac{di}{dt}$.

* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$


$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as $t \rightarrow \infty$, making $v = 0$, and we get $i^{(p)} = V_{Th}/R_{Th}$ as a particular solution (which happens to be simply a constant).


* $i = i^{(h)} + i^{(p)} = K \exp(-t/\tau) + V_{Th}/R_{Th}$.

* In general, $i(t) = A \exp(-t/\tau) + B$, where A and B can be obtained from known conditions on i .

RL circuits with DC sources (continued)

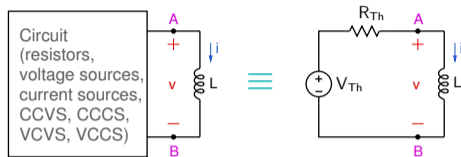

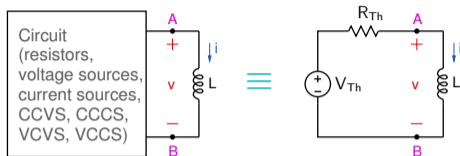
- * If all sources are DC (constant), we have $i(t) = A \exp(-t/\tau) + B$, $\tau = L/R_{Th}$.




- * If all sources are DC (constant), we have

$$i(t) = A \exp(-t/\tau) + B, \quad \tau = L/R_{Th}.$$

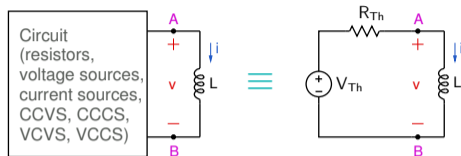- * $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau).$





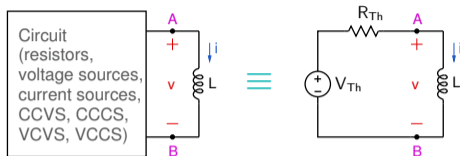- * If all sources are DC (constant), we have $i(t) = A \exp(-t/\tau) + B$, $\tau = L/R_{Th}$.
- * $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.
- * As $t \rightarrow \infty$, $v \rightarrow 0$, i.e., the inductor behaves like a short circuit since all derivatives vanish.




- * If all sources are DC (constant), we have $i(t) = A \exp(-t/\tau) + B$, $\tau = L/R_{Th}$.
- * $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$.
- * As $t \rightarrow \infty$, $v \rightarrow 0$, i.e., the inductor behaves like a short circuit since all derivatives vanish.
- * Since the circuit in the black box is linear, *any* variable (current or voltage) in the circuit can be expressed as $x(t) = K_1 \exp(-t/\tau) + K_2$, where K_1 and K_2 can be obtained from suitable conditions on $x(t)$.

RC circuits: Can V_C change “suddenly?”

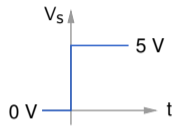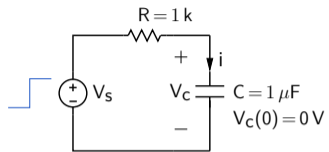


RC circuits: Can V_C change “suddenly?”

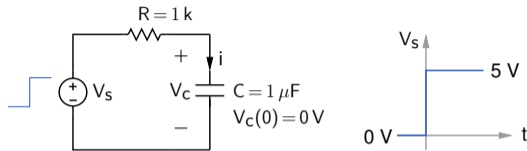


- * V_s changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?

RC circuits: Can V_C change “suddenly?”

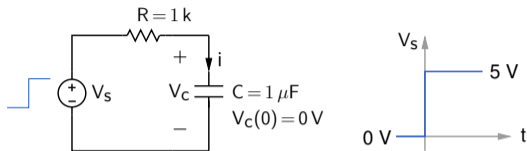


- * V_s changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\ \mu\text{s}$ at a constant rate of $1\text{ V}/1\ \mu\text{s} = 10^6\text{ V/s}$?

RC circuits: Can V_C change “suddenly?”

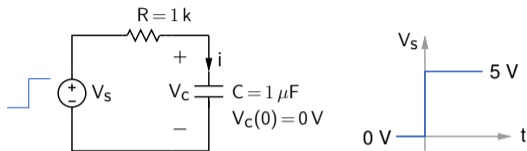


- * V_s changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\text{ }\mu\text{s}$ at a constant rate of $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$?
- * $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$.

RC circuits: Can V_C change “suddenly?”

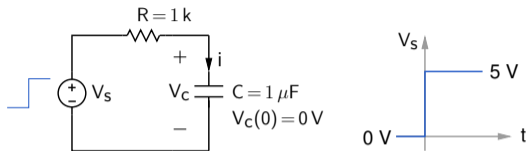


- * V_s changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\text{ }\mu\text{s}$ at a constant rate of $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$?
- * $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$.
- * With $i = 1\text{ A}$, the voltage drop across R would be 1000 V! Not allowed by KVL.

RC circuits: Can V_C change “suddenly?”

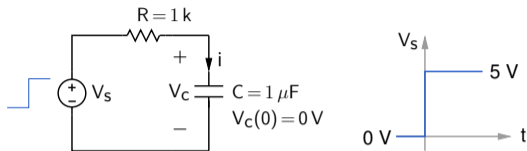


- * V_s changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\ \mu\text{s}$ at a constant rate of $1\text{ V}/1\ \mu\text{s} = 10^6\text{ V/s}$?
- * $i = C \frac{dV_C}{dt} = 1\ \mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$.
- * With $i = 1\text{ A}$, the voltage drop across R would be 1000 V ! Not allowed by KVL.
- * We conclude that $V_C(0^+) = V_C(0^-) \Rightarrow$ A capacitor does not allow abrupt changes in V_C if there is a finite resistance in the circuit.

RC circuits: Can V_C change “suddenly?”

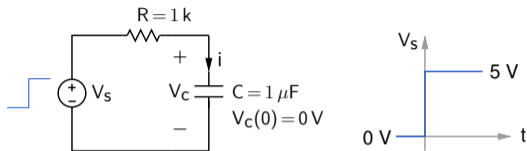


- * V_s changes from 0 V (at $t = 0^-$), to 5 V (at $t = 0^+$). As a result of this change, V_C will rise. How fast can V_C change?
- * For example, what would happen if V_C changes by 1 V in $1\ \mu\text{s}$ at a constant rate of $1\text{ V}/1\ \mu\text{s} = 10^6\text{ V/s}$?
- * $i = C \frac{dV_C}{dt} = 1\ \mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$.
- * With $i = 1\text{ A}$, the voltage drop across R would be 1000 V ! Not allowed by KVL.
- * We conclude that $V_C(0^+) = V_C(0^-) \Rightarrow$ A capacitor does not allow abrupt changes in V_C if there is a finite resistance in the circuit.
- * Similarly, an inductor does not allow abrupt changes in i_L .

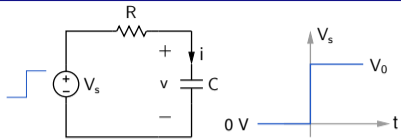RC circuits: charging and discharging transients




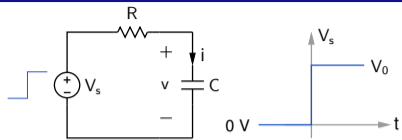RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

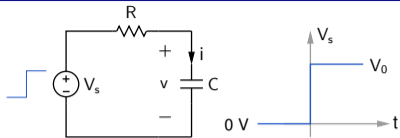RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$


$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$

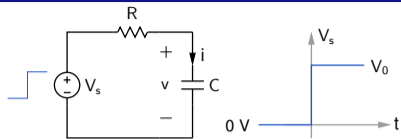RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

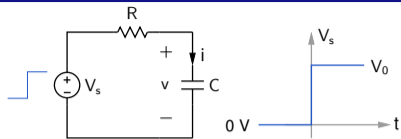RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$

Imposing (1) and (2) on Eq. (A), we get


$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

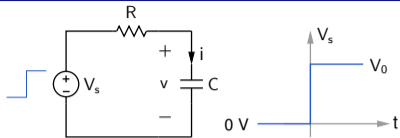RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) \quad v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$


$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

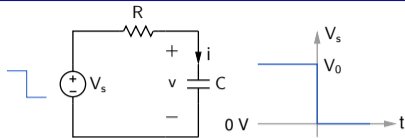

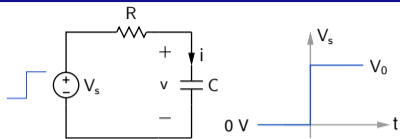RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) \quad v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$


$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

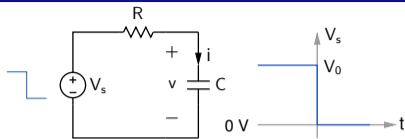

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

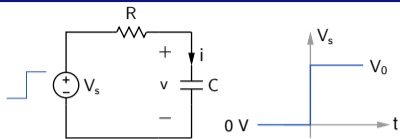RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

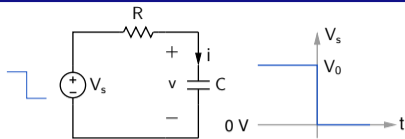

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) v(0^-) = V_S(0^-) = V_0$$


$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = 0 \text{ V}$$

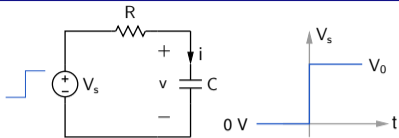RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) \quad v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

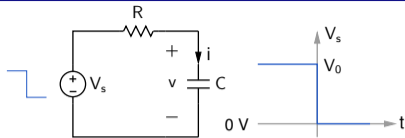

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) \quad v(0^-) = V_S(0^-) = V_0$$

$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = 0 \text{ V}$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: V_0 = A + B,$$

$$t \rightarrow \infty: 0 = B.$$

$$\text{i.e., } A = V_0, B = 0$$

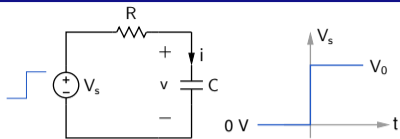RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) \quad v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

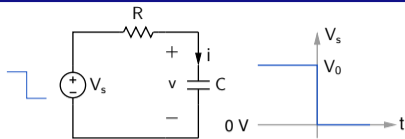

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on $v(t)$:

$$(1) \quad v(0^-) = V_S(0^-) = V_0$$

$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at 0^+ (and not at 0^-)

because Eq. (A) applies only for $t > 0$.

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = 0 \text{ V}$$

Imposing (1) and (2) on Eq. (A), we get


$$t = 0^+: V_0 = A + B,$$

$$t \rightarrow \infty: 0 = B.$$

$$\text{i.e., } A = V_0, B = 0$$


$$v(t) = V_0 \exp(-t/\tau)$$

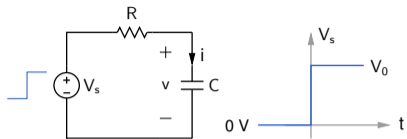RC circuits: charging and discharging transients




Compute $i(t)$, $t > 0$.

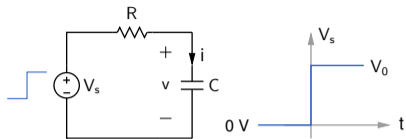RC circuits: charging and discharging transients



Compute $i(t)$, $t > 0$.
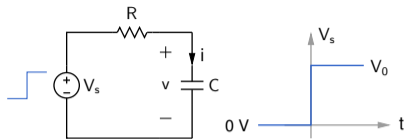
$$\begin{aligned} \text{(A) } i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain
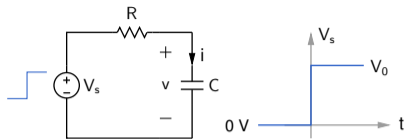
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$


$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain
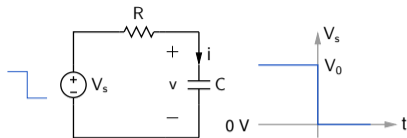
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute $i(t)$, $t > 0$.

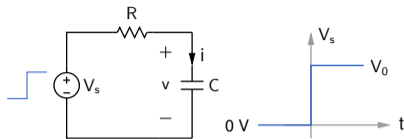

Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$


Using these conditions, we obtain
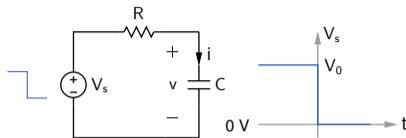
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute $i(t)$, $t > 0$.
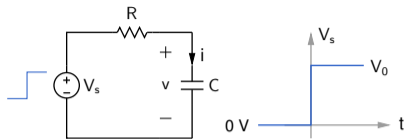
$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [\exp(-t/\tau)] \\ &= -\frac{CV_0}{\tau} \exp(-t/\tau) = -\frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain
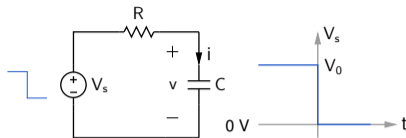
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute $i(t)$, $t > 0$.

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [\exp(-t/\tau)] \\ &= -\frac{CV_0}{\tau} \exp(-t/\tau) = -\frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$

(B) Let $i(t) = A' \exp(-t/\tau) + B'$, $t > 0$.


$$t = 0^+: v = V_0, V_s = 0 \Rightarrow i(0^+) = -V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain

$$A' = -\frac{V_0}{R}, B' = 0 \Rightarrow i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

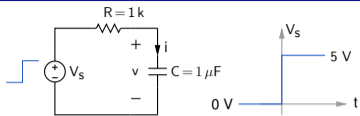
RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$


$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

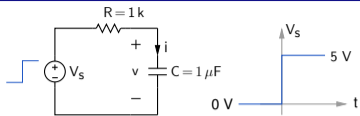RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$


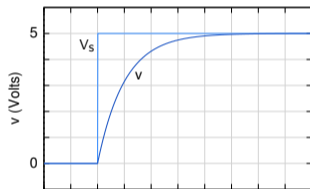


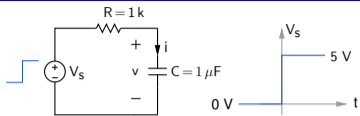RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$


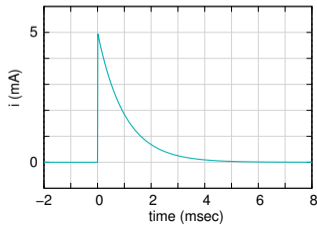
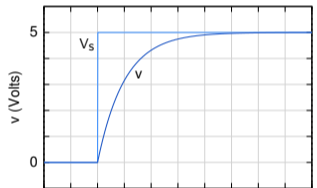


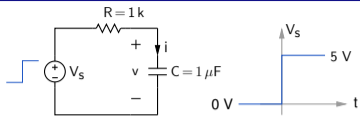RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$


$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

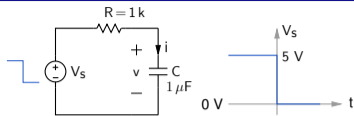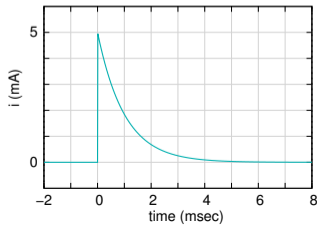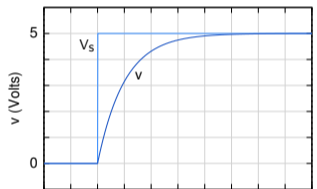

$$v(t) = V_0 \exp(-t/\tau)$$




$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

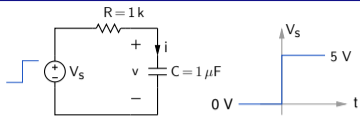RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

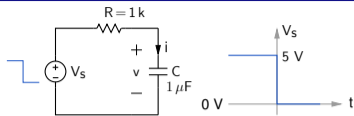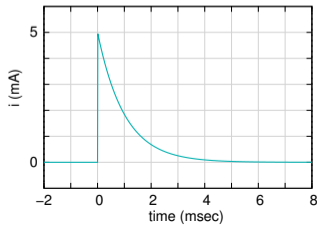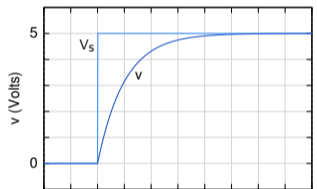


$$v(t) = V_0 \exp(-t/\tau)$$

$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$



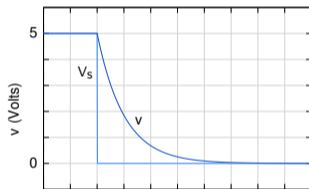


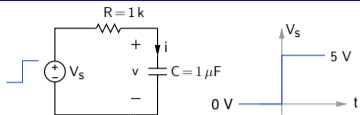RC circuits: charging and discharging transients





$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

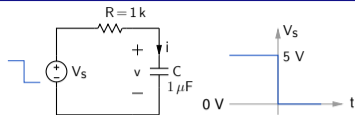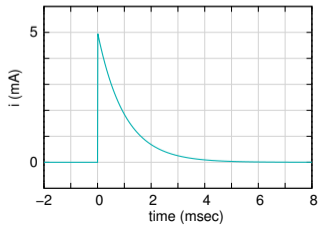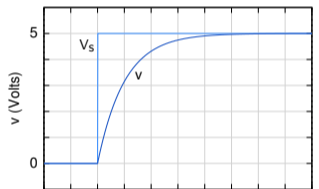


$$v(t) = V_0 \exp(-t/\tau)$$



$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

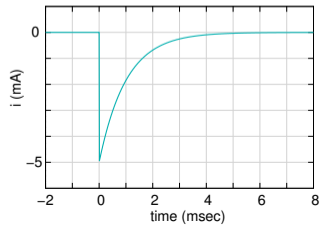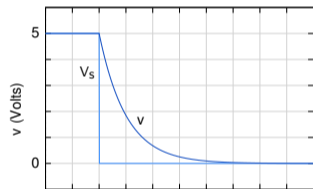

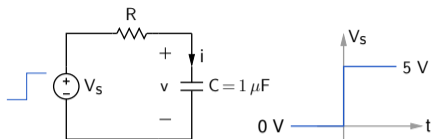
RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

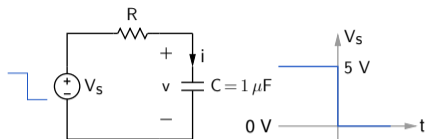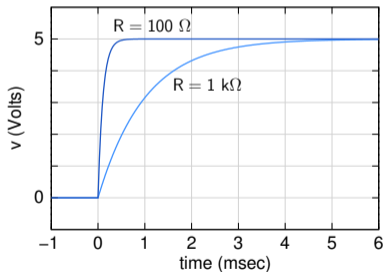


$$v(t) = V_0 \exp(-t/\tau)$$

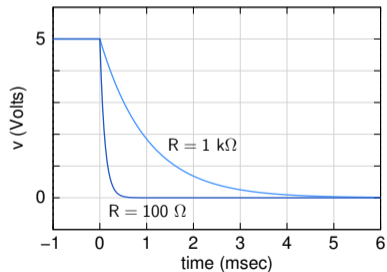

* Identify intervals in which the source voltages/currents are constant.

For example,

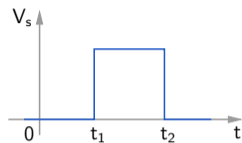


(1) $t < t_1$

(2) $t_1 < t < t_2$

(3) $t > t_2$

- * Identify intervals in which the source voltages/currents are constant.

For example,

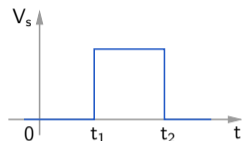

$$(1) t < t_1$$

$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

- * For *any* current or voltage $x(t)$, write general expressions such as,


$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- * Identify intervals in which the source voltages/currents are constant.

For example,

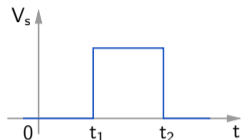

$$(1) t < t_1$$

$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

- * For any current or voltage $x(t)$, write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$


$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- * Work out suitable conditions on $x(t)$ at specific time points using

- * Identify intervals in which the source voltages/currents are constant.

For example,

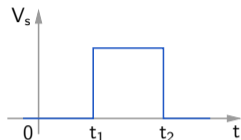

- (1) $t < t_1$
- (2) $t_1 < t < t_2$
- (3) $t > t_2$

- * For any current or voltage $x(t)$, write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$


- * Work out suitable conditions on $x(t)$ at specific time points using

- (a) If the source voltage/current has not changed for a "long" time (long compared to τ), all derivatives are zero.

$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$

- * Identify intervals in which the source voltages/currents are constant.

For example,

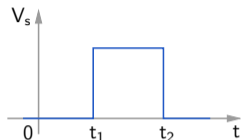

$$(1) t < t_1$$

$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

- * For any current or voltage $x(t)$, write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- * Work out suitable conditions on $x(t)$ at specific time points using

- If the source voltage/current has not changed for a “long” time (long compared to τ), all derivatives are zero.

$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$


- When a source voltage (or current) changes, say, at $t = t_0$,

$V_C(t)$ or $i_L(t)$ cannot change abruptly, i.e.,

$$V_C(t_0^+) = V_C(t_0^-), \text{ and } i_L(t_0^+) = i_L(t_0^-).$$

- * Identify intervals in which the source voltages/currents are constant.

For example,

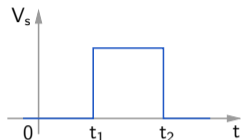

$$(1) t < t_1$$

$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

- * For any current or voltage $x(t)$, write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- * Work out suitable conditions on $x(t)$ at specific time points using

- If the source voltage/current has not changed for a “long” time (long compared to τ), all derivatives are zero.

$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$


- When a source voltage (or current) changes, say, at $t = t_0$,

$V_C(t)$ or $i_L(t)$ cannot change abruptly, i.e.,


$$V_C(t_0^+) = V_C(t_0^-), \text{ and } i_L(t_0^+) = i_L(t_0^-).$$

- * Compute A_1, B_1, \dots using the conditions on $x(t)$.

RL circuit: example

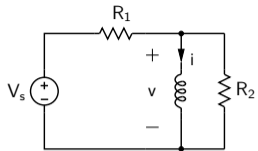

Find $i(t)$.

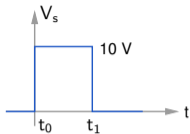

$$R_1 = 10 \Omega$$



$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

RL circuit: example

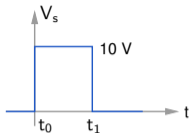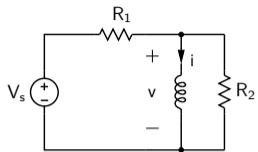

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find $i(t)$.



There are three intervals of constant V_s :

(1) $t < t_0$

(2) $t_0 < t < t_1$

(3) $t > t_1$

RL circuit: example

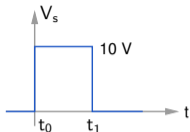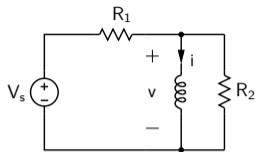

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find $i(t)$.


There are three intervals of constant V_s :

(1) $t < t_0$

(2) $t_0 < t < t_1$

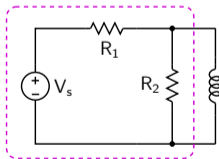(3) $t > t_1$



R_{Th} seen by L is the same in all intervals:



$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

RL circuit: example

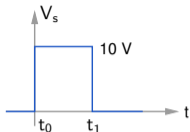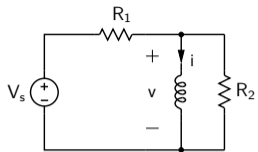

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find $i(t)$.


There are three intervals of constant V_s :

(1) $t < t_0$

(2) $t_0 < t < t_1$

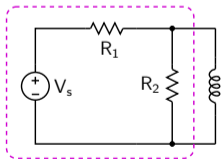(3) $t > t_1$

R_{Th} seen by L is the same in all intervals:





$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

At $t = t_0^-$, $v = 0 \text{ V}$, $V_s = 0 \text{ V}$.

$\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$.

RL circuit: example

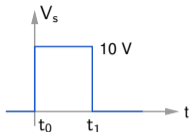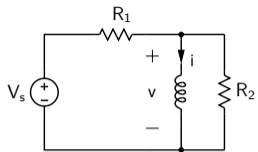

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find $i(t)$.


There are three intervals of constant V_s :

(1) $t < t_0$

(2) $t_0 < t < t_1$

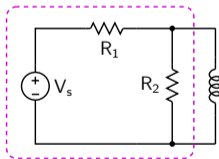(3) $t > t_1$

R_{Th} seen by L is the same in all intervals:




$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$



At $t = t_0^-$, $v = 0 \text{ V}$, $V_s = 0 \text{ V}$.
 $\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$.

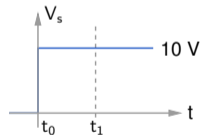If V_s did not change at $t = t_1$,
we would have



$v(\infty) = 0 \text{ V}$, $i(\infty) = 10 \text{ V}/10 \Omega = 1 \text{ A}$.

RL circuit: example

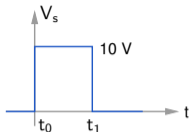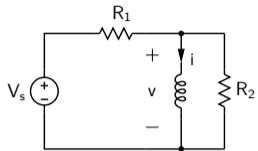

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find $i(t)$.


There are three intervals of constant V_s :

(1) $t < t_0$

(2) $t_0 < t < t_1$

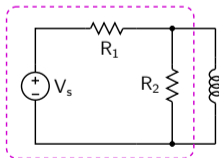(3) $t > t_1$

R_{Th} seen by L is the same in all intervals:




$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

At $t = t_0^-$, $v = 0 \text{ V}$, $V_s = 0 \text{ V}$.
 $\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$.


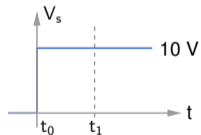
If V_s did not change at $t = t_1$,
we would have



$v(\infty) = 0 \text{ V}$, $i(\infty) = 10 \text{ V}/10 \Omega = 1 \text{ A}$.

Using $i(t_0^+)$ and $i(\infty)$, we can obtain
 $i(t)$, $t > 0$ (See next slide).

RL circuit: example

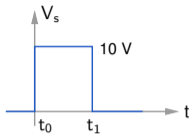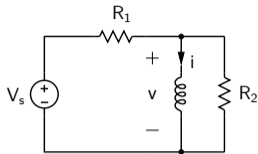


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$


$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$


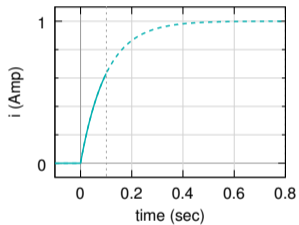


RL circuit: example

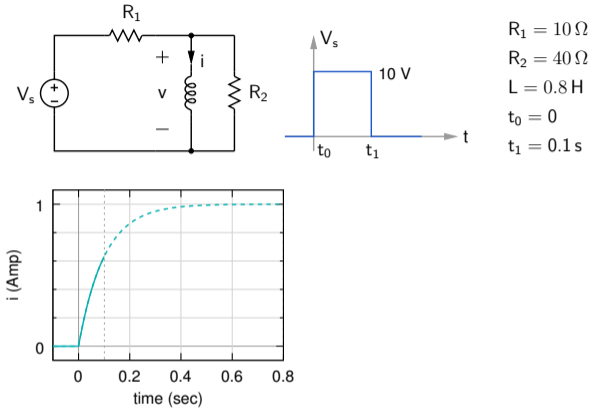

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

RL circuit: example

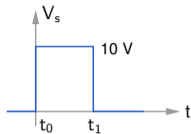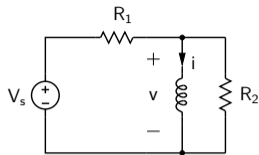


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$


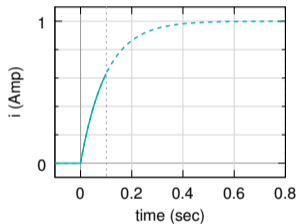


For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.

Consider $t > t_1$.

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

RL circuit: example

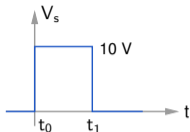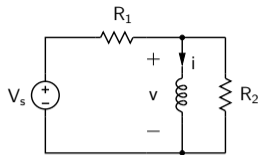


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

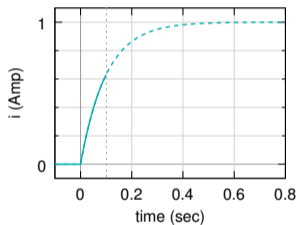

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.



For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.

Consider $t > t_1$.

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

RL circuit: example

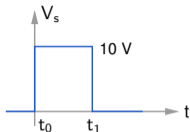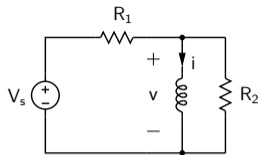


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

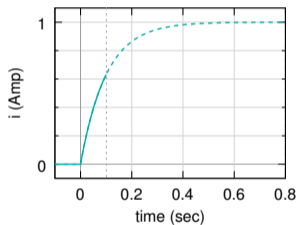

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.



Consider $t > t_1$.

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$

RL circuit: example

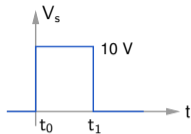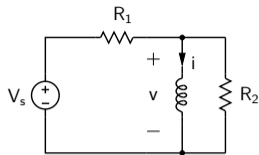


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

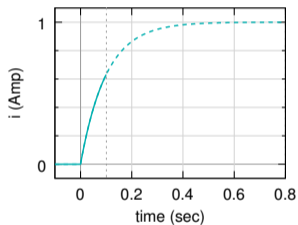

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.

Consider $t > t_1$.

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$



$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$

It is convenient to rewrite $i(t)$ as

$$i(t) = A' \exp[-(t - t_1)/\tau] + B.$$

RL circuit: example

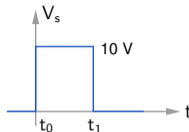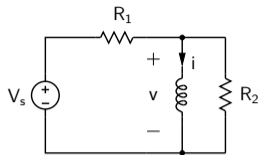


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

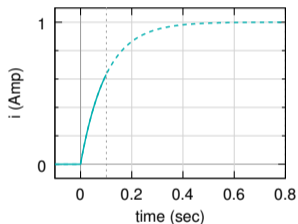

In reality, V_s changes at $t = t_1$,
and we need to work out the
solution for $t > t_1$ separately.

For $t_0 < t < t_1$, $i(t) = 1 - \exp(-t/\tau)$ Amp.

Consider $t > t_1$.

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$


It is convenient to rewrite $i(t)$ as

$$i(t) = A' \exp[-(t - t_1)/\tau] + B.$$

Using $i(t_1^+)$ and $i(\infty)$, we get

$$i(t) = 0.632 \exp[-(t - t_1)/\tau] \text{ A.}$$

RL circuit: example

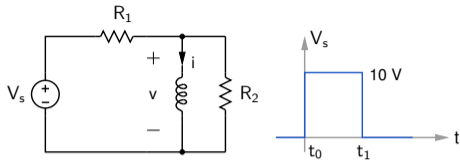

$$R_1 = 10 \Omega$$


$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$



$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$
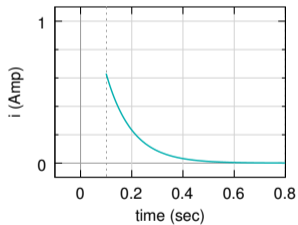
$$i(t) = 0.632 \exp[-(t - t_1)/\tau] \text{ A.}$$



RL circuit: example

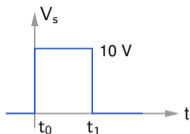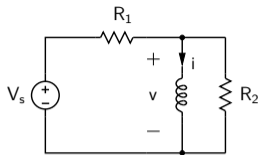

$$R_1 = 10 \Omega$$


$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$


$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$
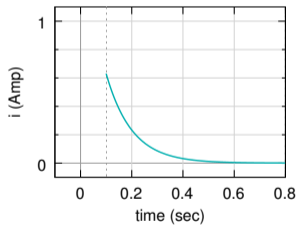
$$i(t) = 0.632 \exp[-(t - t_1)/\tau] \text{ A.}$$




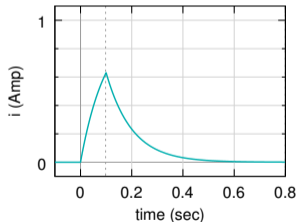Combining the solutions for $t_0 < t < t_1$ and $t > t_1$, we get




(SEQUEL file: ee101_rl1.sqproj)

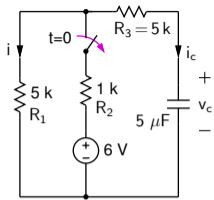
RC circuit: The switch has been closed for a long time and opens at $t = 0$.



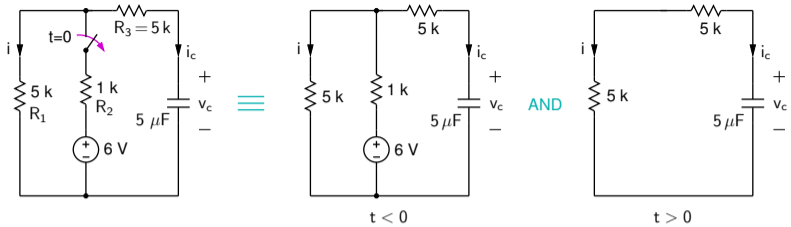RC circuit: The switch has been closed for a long time and opens at $t = 0$.




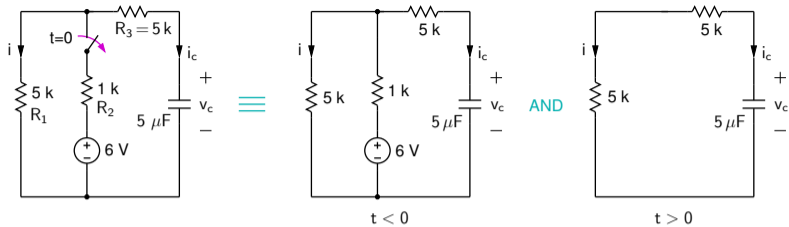RC circuit: The switch has been closed for a long time and opens at $t = 0$.



$t = 0^-$: capacitor is an open circuit $\Rightarrow i(0^-) = 6\text{ V} / (5\text{ k} + 1\text{ k}) = 1\text{ mA}$.

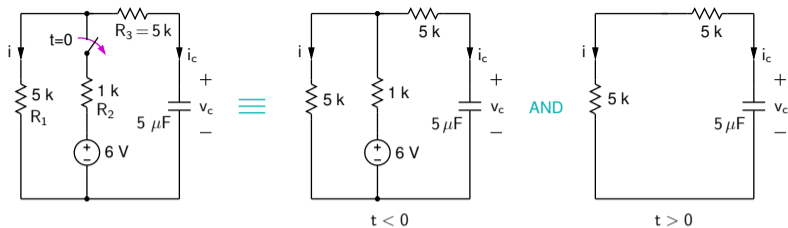
RC circuit: The switch has been closed for a long time and opens at $t = 0$.



$t = 0^-$: capacitor is an open circuit $\Rightarrow i(0^-) = 6\text{ V} / (5\text{ k} + 1\text{ k}) = 1\text{ mA}$.

$v_c(0^-) = i(0^-) R_1 = 5\text{ V} \Rightarrow v_c(0^+) = 5\text{ V}$

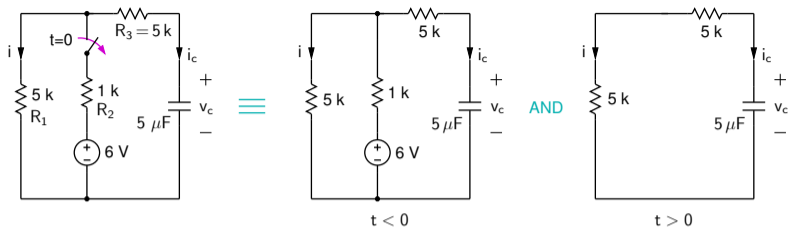RC circuit: The switch has been closed for a long time and opens at $t = 0$.




$t = 0^-$: capacitor is an open circuit $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$.

$v_c(0^-) = i(0^-) R_1 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$.

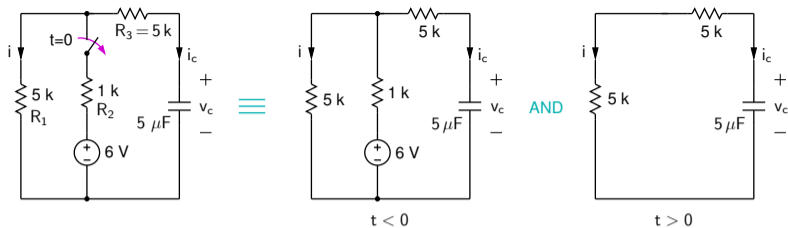RC circuit: The switch has been closed for a long time and opens at $t = 0$.




$t = 0^-$: capacitor is an open circuit $\Rightarrow i(0^-) = 6\ \text{V} / (5\ \text{k} + 1\ \text{k}) = 1\ \text{mA}$.

$v_c(0^-) = i(0^-) R_1 = 5\ \text{V} \Rightarrow v_c(0^+) = 5\ \text{V}$

$\Rightarrow i(0^+) = 5\ \text{V} / (5\ \text{k} + 5\ \text{k}) = 0.5\ \text{mA}$.

Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10\ \text{k} \times 5\ \mu\text{F} = 50\ \text{ms}$.

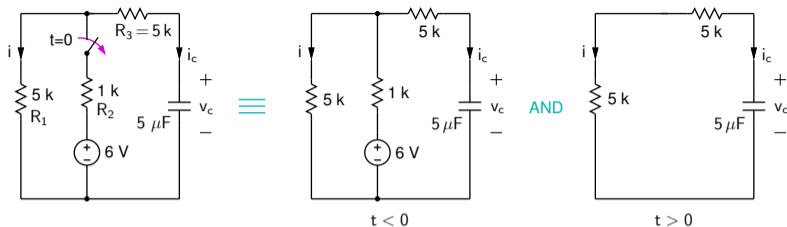RC circuit: The switch has been closed for a long time and opens at $t = 0$.



$t = 0^-$: capacitor is an open circuit $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$.

$v_c(0^-) = i(0^-) R_1 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$


$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$.

Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$.

Using $i(0^+)$ and $i(\infty) = 0 \text{ A}$, we get

$i(t) = 0.5 \exp(-t/\tau) \text{ mA}$.

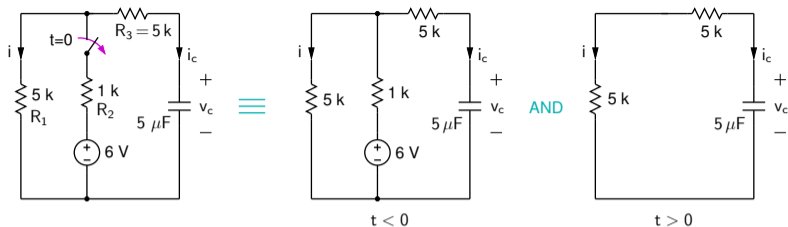RC circuit: The switch has been closed for a long time and opens at $t = 0$.



$t = 0^-$: capacitor is an open circuit $\Rightarrow i(0^-) = 6\text{ V}/(5\text{ k} + 1\text{ k}) = 1\text{ mA}$.


$v_c(0^-) = i(0^-) R_1 = 5\text{ V} \Rightarrow v_c(0^+) = 5\text{ V}$

$\Rightarrow i(0^+) = 5\text{ V}/(5\text{ k} + 5\text{ k}) = 0.5\text{ mA}$.


Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10\text{ k} \times 5\text{ }\mu\text{F} = 50\text{ ms}$.

Using $i(0^+)$ and $i(\infty) = 0\text{ A}$, we get

$i(t) = 0.5 \exp(-t/\tau)\text{ mA}$.

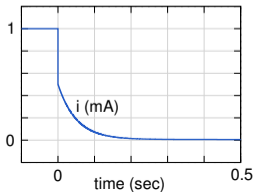

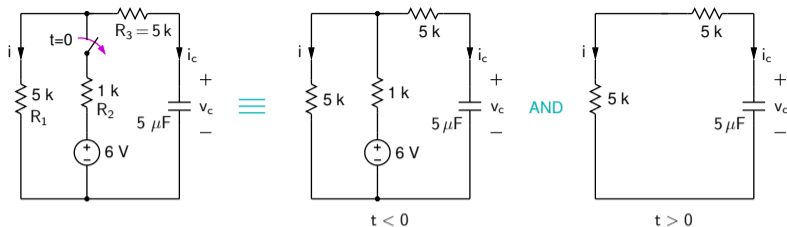RC circuit: The switch has been closed for a long time and opens at $t = 0$.



$t = 0^-$: capacitor is an open circuit $\Rightarrow i(0^-) = 6\ \text{V} / (5\ \text{k} + 1\ \text{k}) = 1\ \text{mA}$.


$v_c(0^-) = i(0^-) R_1 = 5\ \text{V} \Rightarrow v_c(0^+) = 5\ \text{V}$

$\Rightarrow i(0^+) = 5\ \text{V} / (5\ \text{k} + 5\ \text{k}) = 0.5\ \text{mA}$.


Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10\ \text{k} \times 5\ \mu\text{F} = 50\ \text{ms}$.

Using $i(0^+)$ and $i(\infty) = 0\ \text{A}$, we get

$i(t) = 0.5 \exp(-t/\tau)\ \text{mA}$.

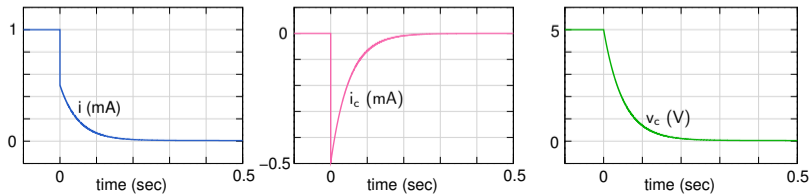

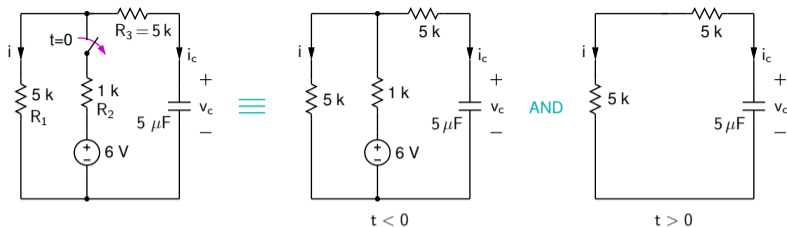RC circuit: The switch has been closed for a long time and opens at $t = 0$.



$t = 0^-$: capacitor is an open circuit $\Rightarrow i(0^-) = 6\ \text{V} / (5\ \text{k} + 1\ \text{k}) = 1\ \text{mA}$.

$v_c(0^-) = i(0^-) R_1 = 5\ \text{V} \Rightarrow v_c(0^+) = 5\ \text{V}$




$\Rightarrow i(0^+) = 5\ \text{V} / (5\ \text{k} + 5\ \text{k}) = 0.5\ \text{mA}$.

Let $i(t) = A \exp(-t/\tau) + B$ for $t > 0$, with $\tau = 10\ \text{k} \times 5\ \mu\text{F} = 50\ \text{ms}$.



Using $i(0^+)$ and $i(\infty) = 0\ \text{A}$, we get

$i(t) = 0.5 \exp(-t/\tau)\ \text{mA}$.


(SEQUEL file: ee101_rc2.sqproj)

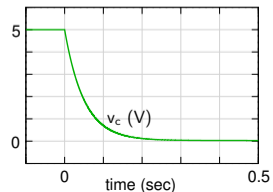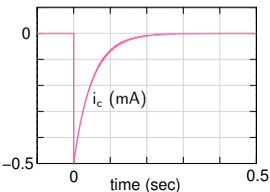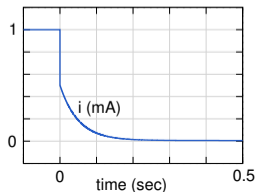



RC circuit: example

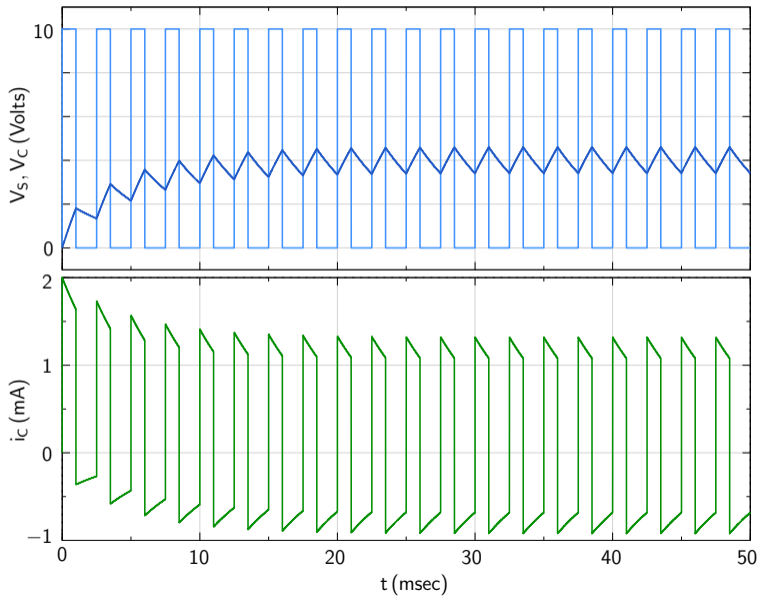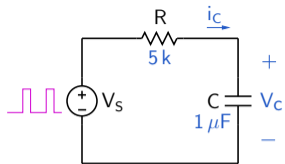




RC circuit: example

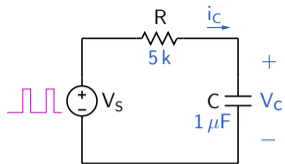


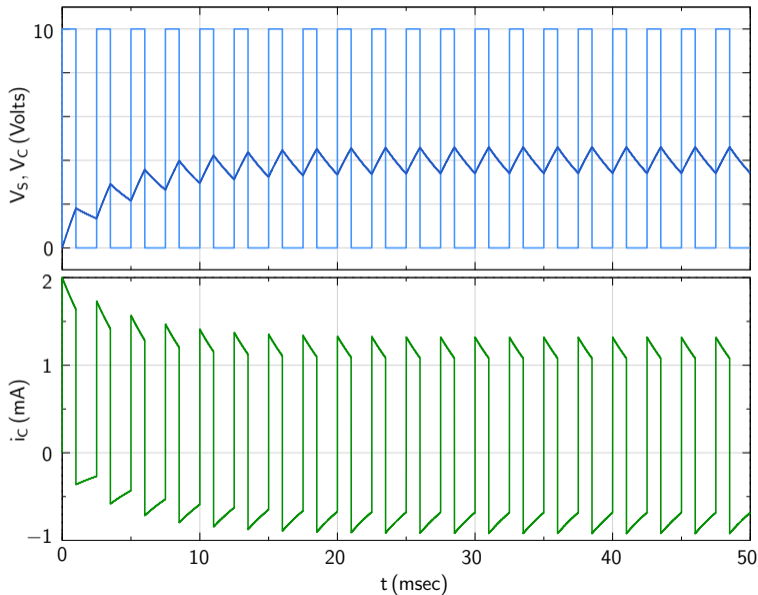
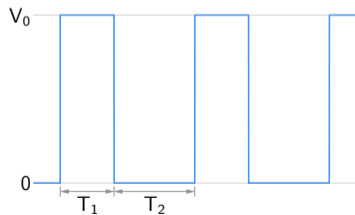
Find expressions for $V_C(t)$ and $i_C(t)$ in steady state (in terms of R , C , V_0 , T_1 , T_2).



RC circuit: example

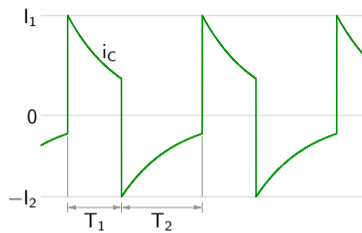
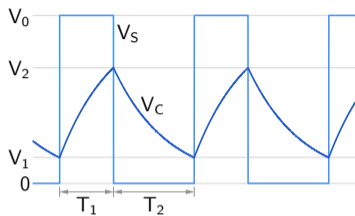
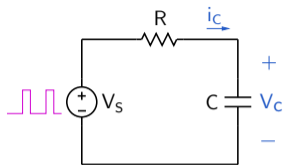


RC circuit: example

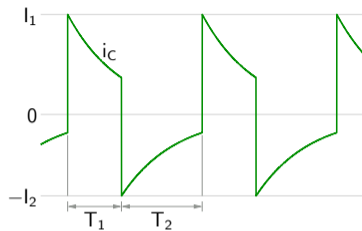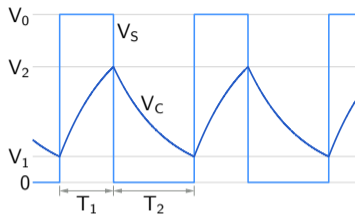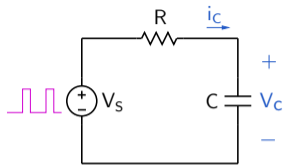

$0 < t < T_1$ Let $V_C^{(1)}(t) = A e^{-t/\tau} + B$




RC circuit: example

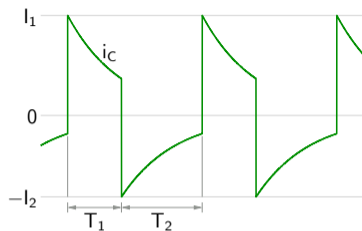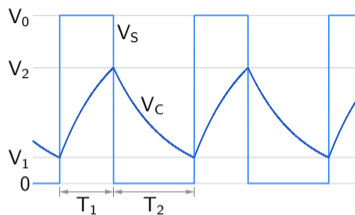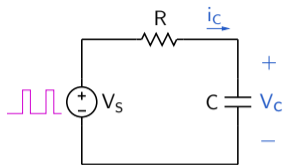

$0 < t < T_1$ Let $V_C^{(1)}(t) = A e^{-t/\tau} + B$

$V_C^{(1)}(0) = V_1, V_C^{(1)}(\infty) = V_0$

RC circuit: example

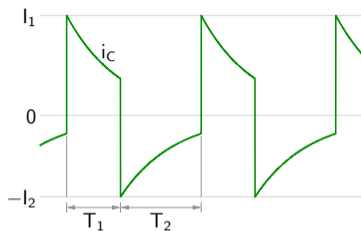
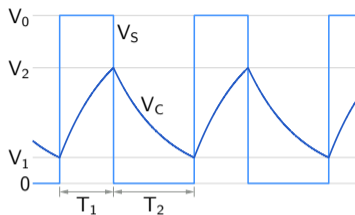
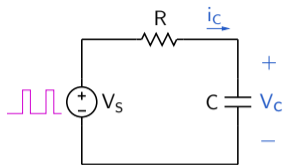


$0 < t < T_1$ Let $V_C^{(1)}(t) = A e^{-t/\tau} + B$

$V_C^{(1)}(0) = V_1, V_C^{(1)}(\infty) = V_0$

$\rightarrow B = V_0, A = V_1 - V_0.$

RC circuit: example

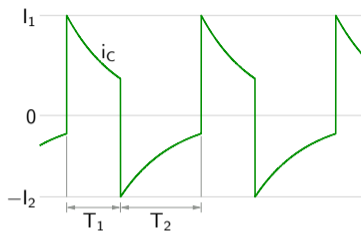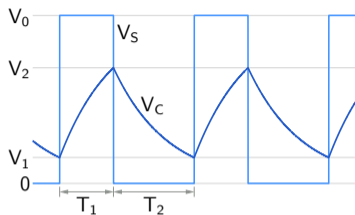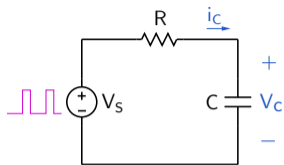




$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

RC circuit: example

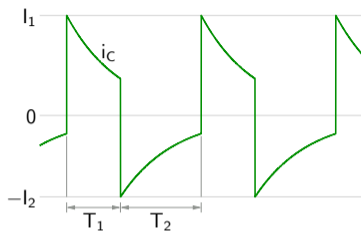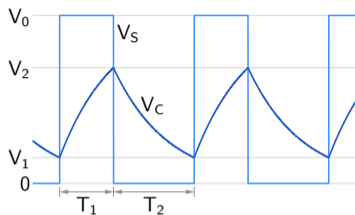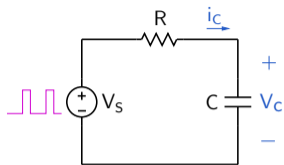

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$




$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

RC circuit: example

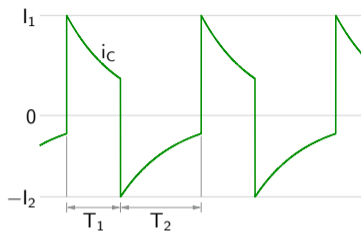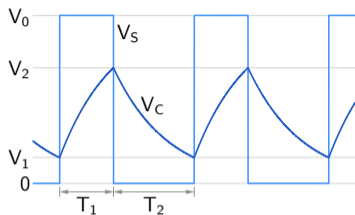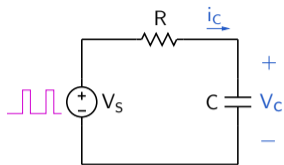

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$




$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

RC circuit: example

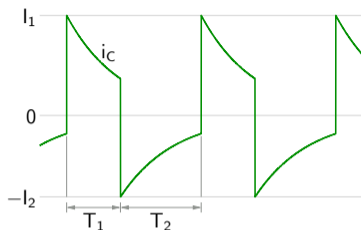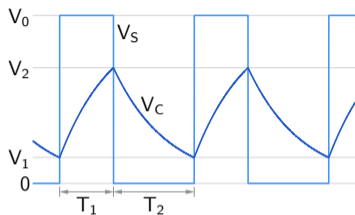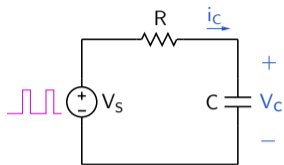

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$




$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

RC circuit: example

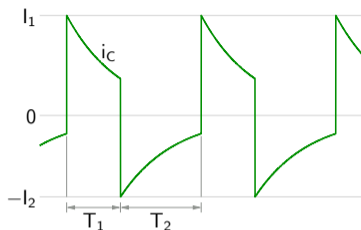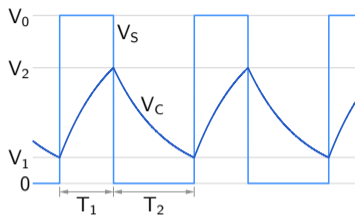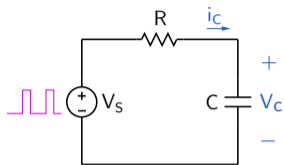

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$




$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

RC circuit: example

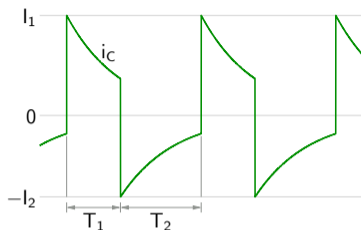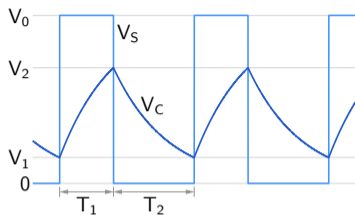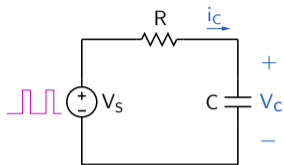

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$




$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

RC circuit: example

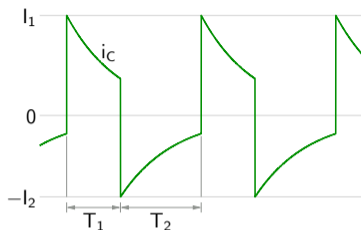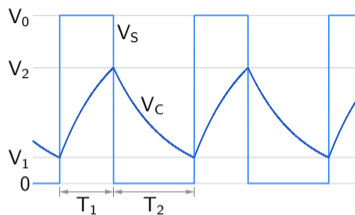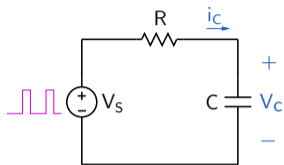

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$




$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

RC circuit: example

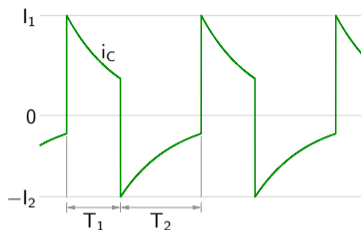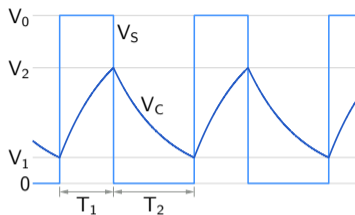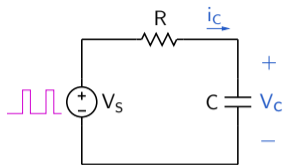

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$




Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

RC circuit: example

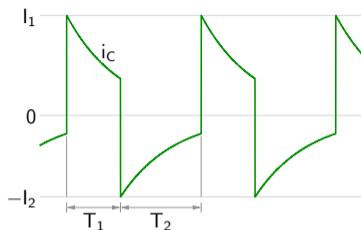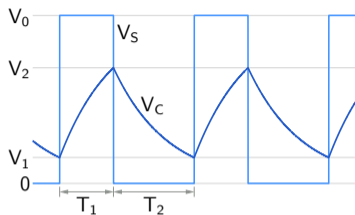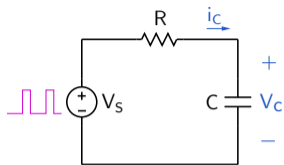

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:




$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

Rewrite with $a \equiv e^{-T_1/\tau}$, $b \equiv e^{-T_2/\tau}$.

RC circuit: example

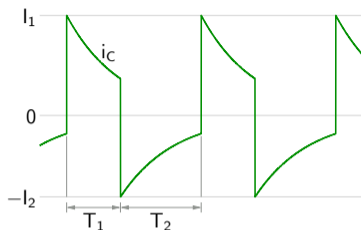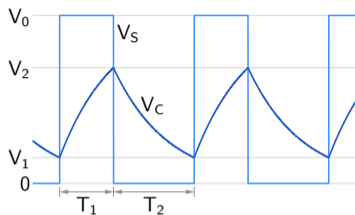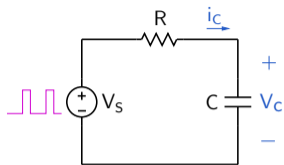

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$




$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

Rewrite with $a \equiv e^{-T_1/\tau}$, $b \equiv e^{-T_2/\tau}$.

$$V_2 = -(V_0 - V_1)a + V_0 \quad (5)$$

RC circuit: example

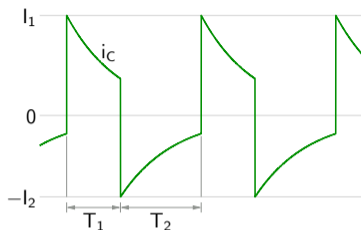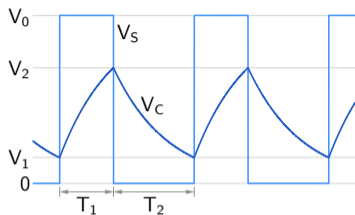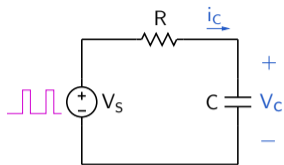

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$




$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

Rewrite with $a \equiv e^{-T_1/\tau}$, $b \equiv e^{-T_2/\tau}$.

$$V_2 = -(V_0 - V_1)a + V_0 \quad (5)$$

$$V_1 = b V_2 \quad (6)$$

RC circuit: example

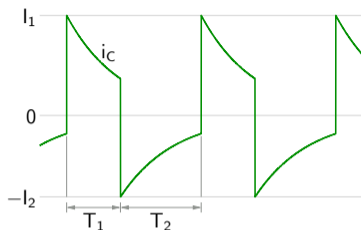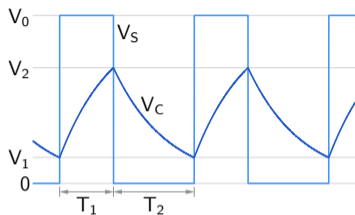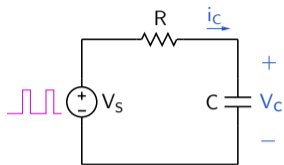

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

Rewrite with $a \equiv e^{-T_1/\tau}$, $b \equiv e^{-T_2/\tau}$.




$$V_2 = -(V_0 - V_1)a + V_0 \quad (5)$$

$$V_1 = b V_2 \quad (6)$$

Solve to get




$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}$$

RC circuit: example

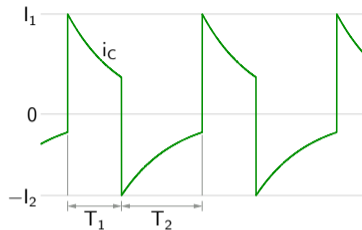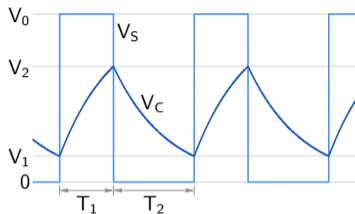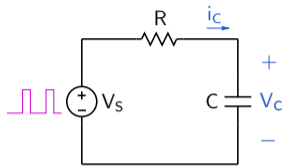

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$




RC circuit: example

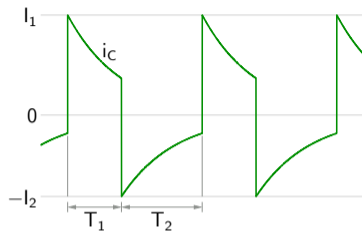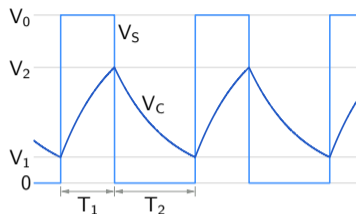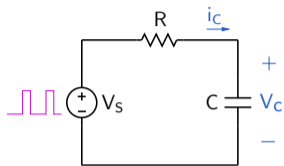

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

RC circuit: example

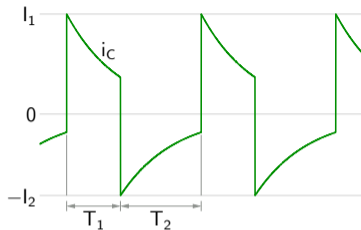
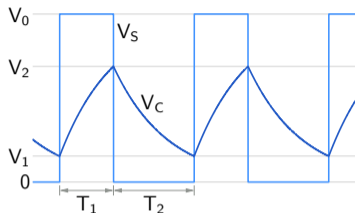
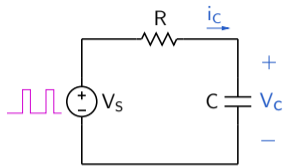


$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

Current calculation:

RC circuit: example

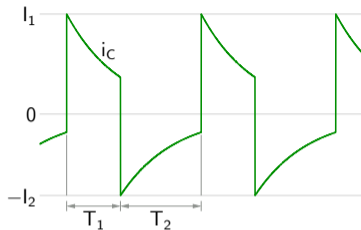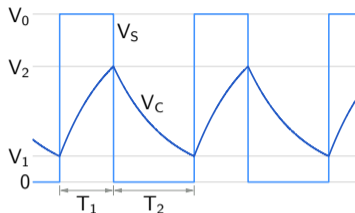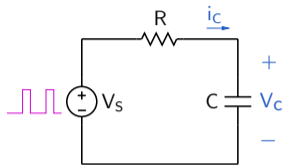

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$




$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

Current calculation:

Method 1:

$$i_c(t) = C \frac{dV_C}{dt} \quad (\text{home work})$$

RC circuit: example

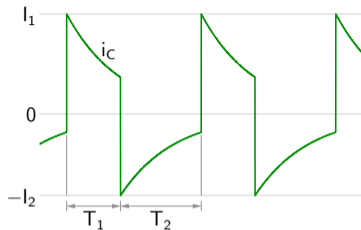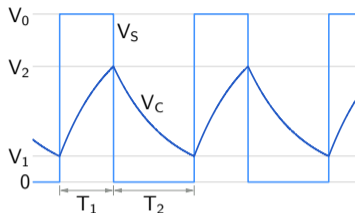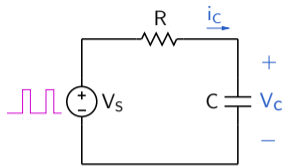

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

Current calculation:




Method 1:

$$i_c(t) = C \frac{dV_C}{dt} \text{ (home work)}$$

Method 2:

Start from scratch!

RC circuit: example

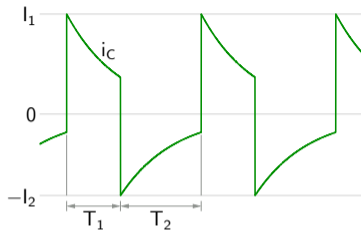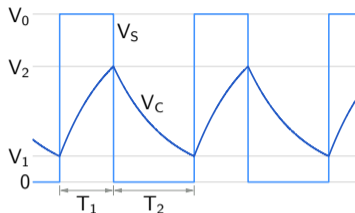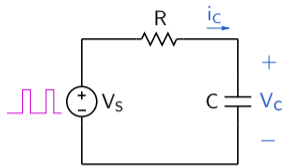

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

Current calculation:

Method 1:




$$i_c(t) = C \frac{dV_C}{dt} \text{ (home work)}$$

Method 2:




Start from scratch!



RC circuit: example

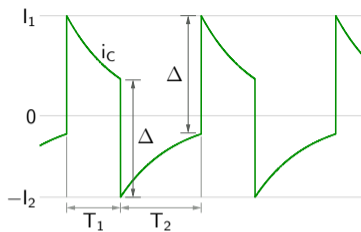
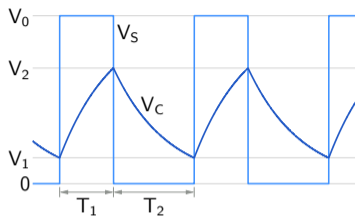
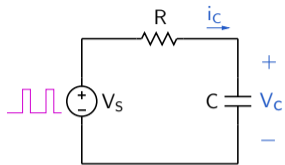


RC circuit: example

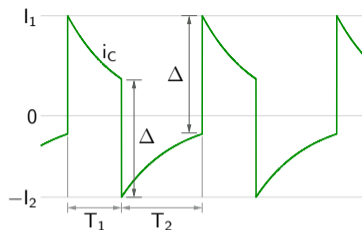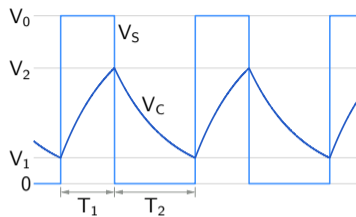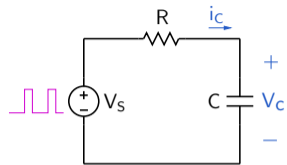

$0 < t < T_1$ Let $i_C^{(1)}(t) = Ae^{-t/\tau} + B$




RC circuit: example

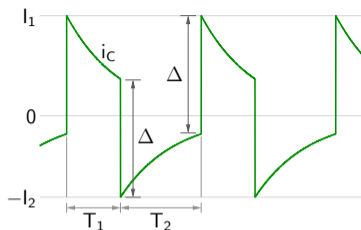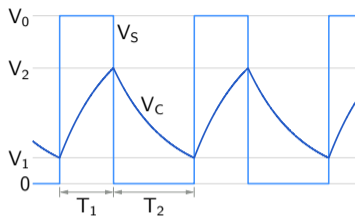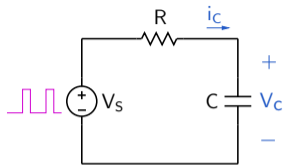

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = Ae^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

RC circuit: example

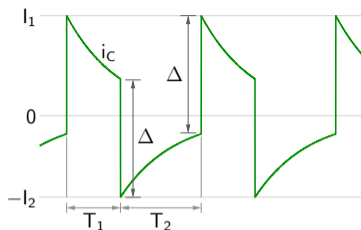
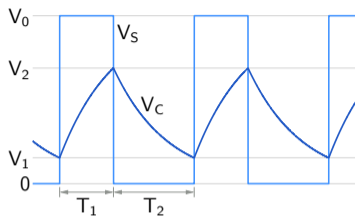
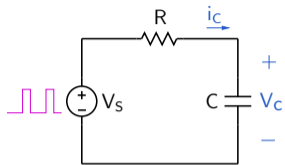


$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = Ae^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

RC circuit: example

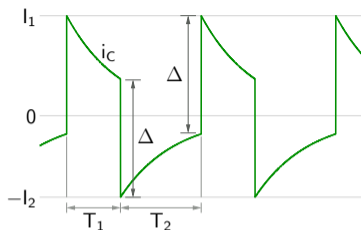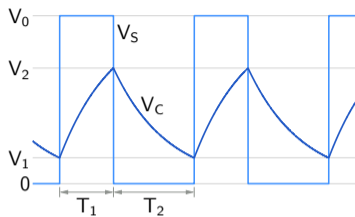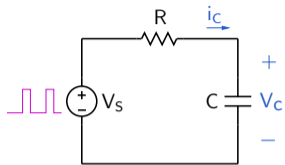




$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$

RC circuit: example

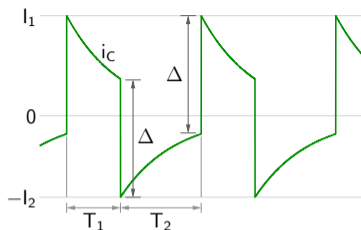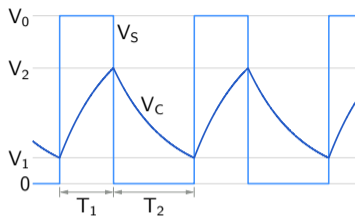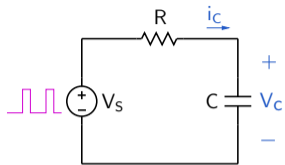

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$




$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

RC circuit: example

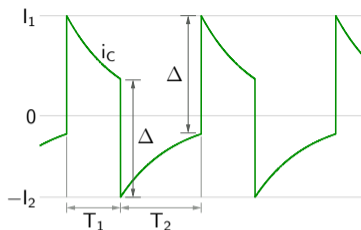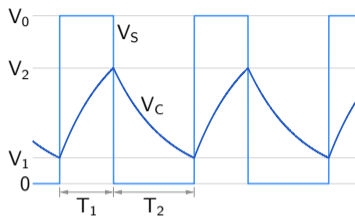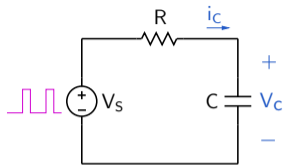

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = l_1, \quad i_C^{(1)}(\infty) = 0$$




$$\rightarrow B = 0, \quad A = l_1.$$

$$i_C^{(1)}(t) = l_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

RC circuit: example

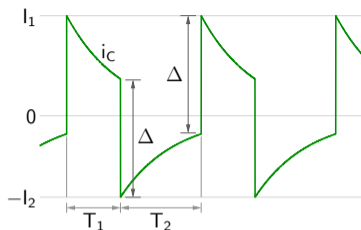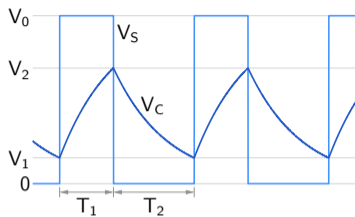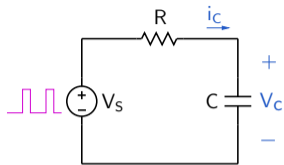

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = l_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = l_1.$$




$$i_C^{(1)}(t) = l_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

RC circuit: example

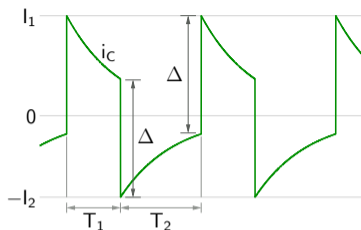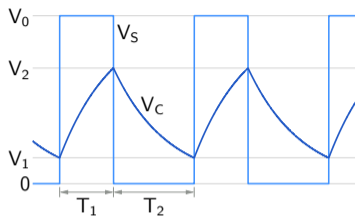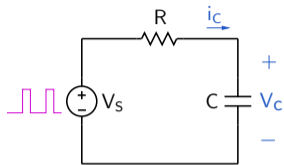

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = l_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = l_1.$$

$$i_C^{(1)}(t) = l_1 e^{-t/\tau} \quad (1)$$




$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

RC circuit: example

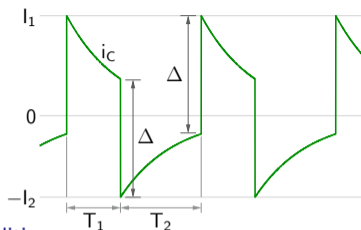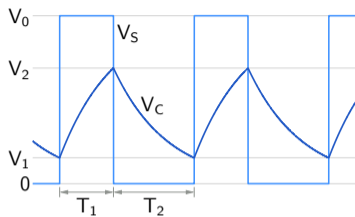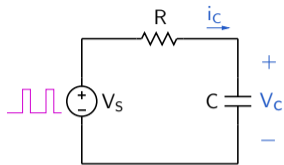

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = l_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = l_1.$$

$$i_C^{(1)}(t) = l_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$




$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

RC circuit: example

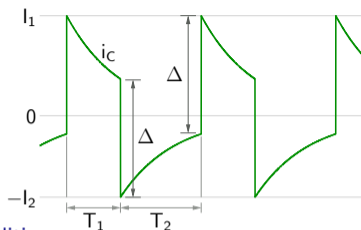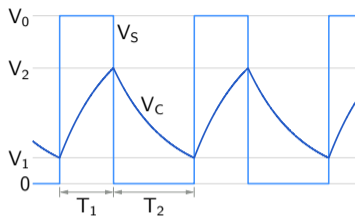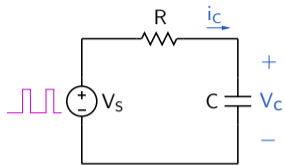

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -I_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -I_2 e^{T_1/\tau}.$$




$$i_C^{(2)}(t) = -I_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

RC circuit: example

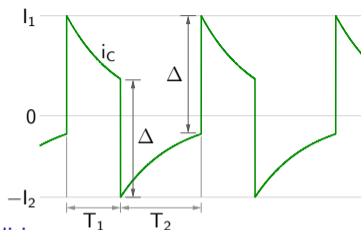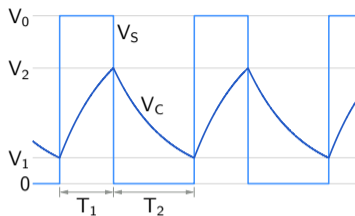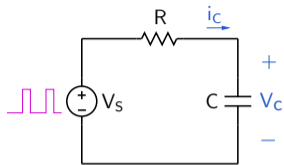

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = h_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = h_1.$$

$$i_C^{(1)}(t) = h_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$




Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

$$h_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

RC circuit: example

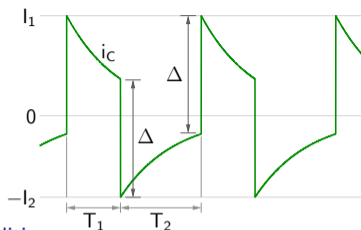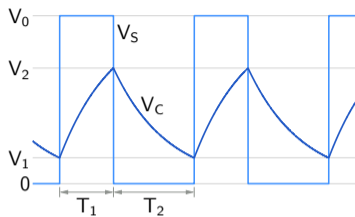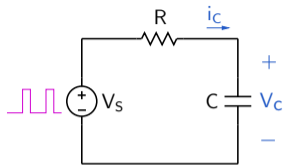

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = h_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = h_1.$$

$$i_C^{(1)}(t) = h_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:




$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

$$h_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

$$h_1 - (-l_2 e^{-(T_1+T_2-T_1)/\tau}) = \Delta \quad (4)$$

RC circuit: example

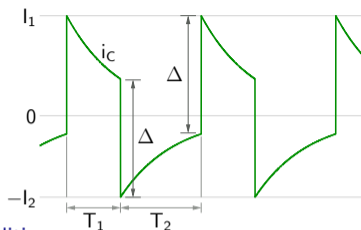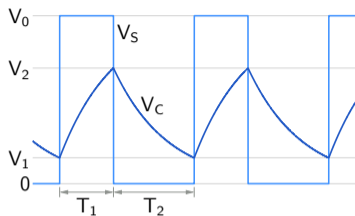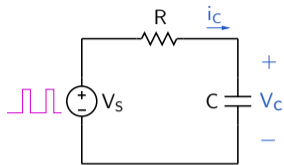

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = h_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = h_1.$$

$$i_C^{(1)}(t) = h_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$




$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

$$h_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

$$h_1 - (-l_2 e^{-(T_1+T_2-T_1)/\tau}) = \Delta \quad (4)$$

$$a h_1 + l_2 = \Delta \quad (5)$$

RC circuit: example

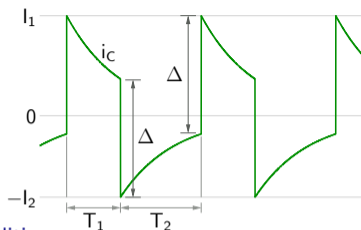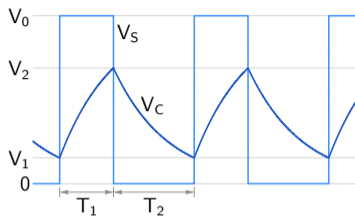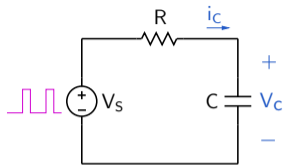

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = h_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = h_1.$$

$$i_C^{(1)}(t) = h_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$




$$h_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

$$h_1 - (-l_2 e^{-(T_1+T_2-T_1)/\tau}) = \Delta \quad (4)$$

$$a h_1 + l_2 = \Delta \quad (5)$$

$$h_1 + b l_2 = \Delta \quad (6)$$

RC circuit: example

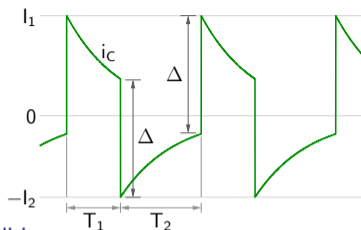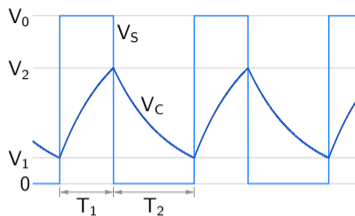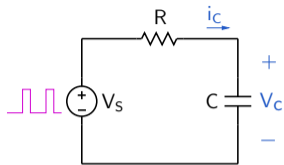

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = l_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = l_1.$$

$$i_C^{(1)}(t) = l_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

$$l_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

$$l_1 - (-l_2 e^{-(T_1+T_2-T_1)/\tau}) = \Delta \quad (4)$$

$$a l_1 + l_2 = \Delta \quad (5)$$


$$l_1 + b l_2 = \Delta \quad (6)$$

Solve to get




$$l_1 = \Delta \frac{1-b}{1-ab}, \quad l_2 = \Delta \frac{1-a}{1-ab}$$

$$(a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau})$$

RC circuit: example

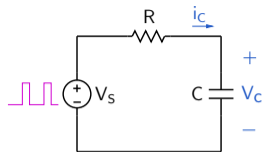


Charge conservation:

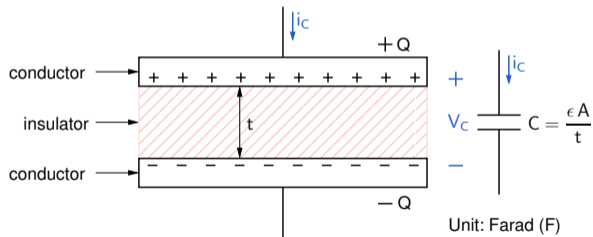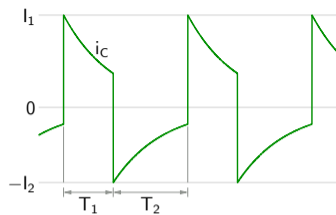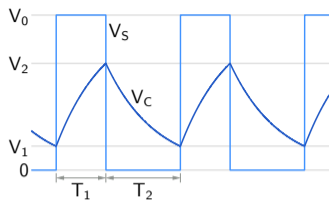




$$i_c = \frac{dQ}{dt} = C \frac{dV_c}{dt}$$

RC circuit: example

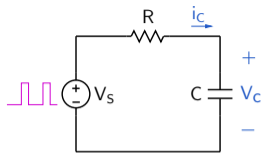




Charge conservation:

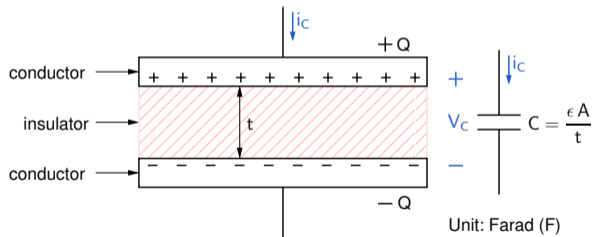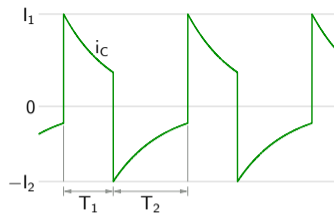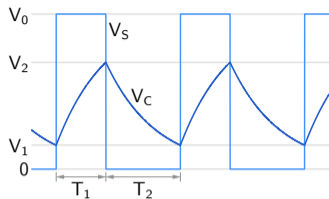Periodic steady state: All quantities are periodic, i.e.,
 $x(t_0 + T) = x(t_0)$



$$i_c = \frac{dQ}{dt} = C \frac{dV_c}{dt}$$


RC circuit: example

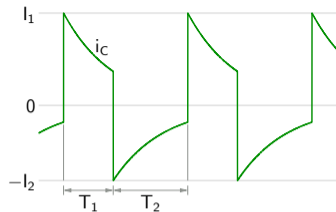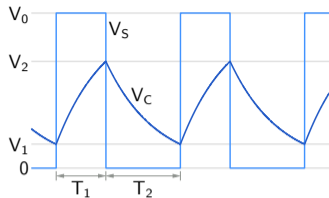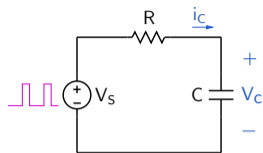

Charge conservation:




Periodic steady state: All quantities are periodic, i.e.,
 $x(t_0 + T) = x(t_0)$

Capacitor charge: $Q(t_0 + T) = Q(t_0)$

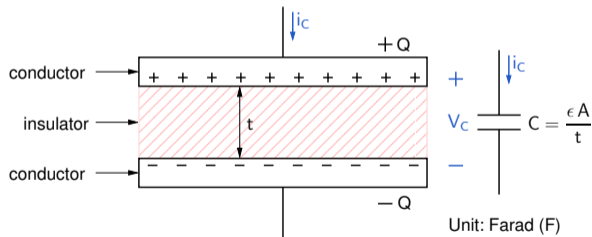

$$i_c = \frac{dQ}{dt} = C \frac{dV_c}{dt}$$

RC circuit: example

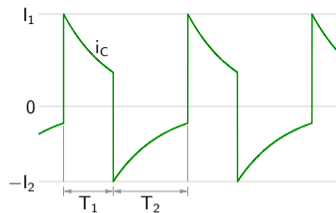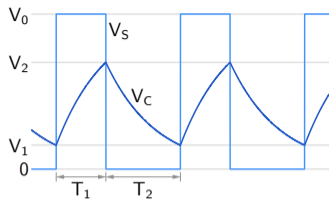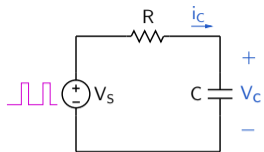


Charge conservation:

Periodic steady state: All quantities are periodic, i.e.,
 $x(t_0 + T) = x(t_0)$




Capacitor charge: $Q(t_0 + T) = Q(t_0)$
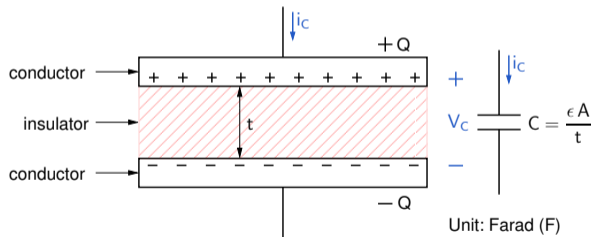
$$i_C = \frac{dQ}{dt} \rightarrow Q = \int i_C dt.$$



$$i_c = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

RC circuit: example

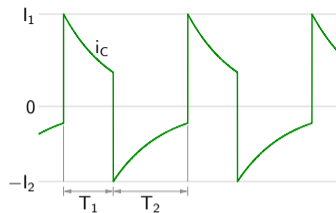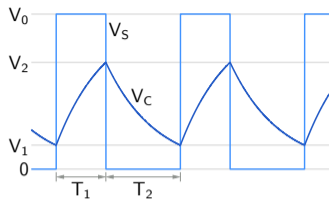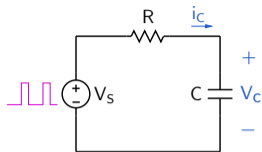

Charge conservation:


Periodic steady state: All quantities are periodic, i.e.,
 $x(t_0 + T) = x(t_0)$

Capacitor charge: $Q(t_0 + T) = Q(t_0)$

$$i_C = \frac{dQ}{dt} \rightarrow Q = \int i_C dt.$$




$$Q(t_0 + T) = Q(t_0) \rightarrow Q(t_0 + T) - Q(t_0) = 0$$
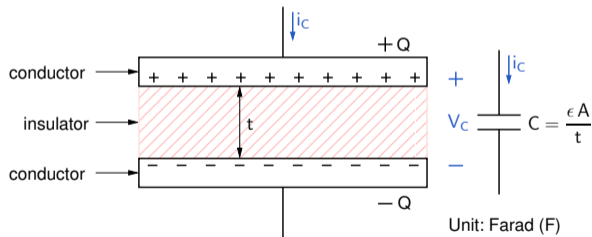
$$\rightarrow \int_{t_0}^{t_0+T} i_C dt = 0.$$



$$i_C = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

RC circuit: example

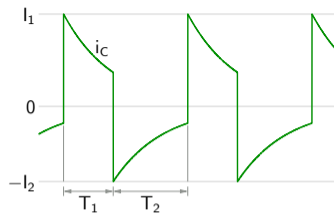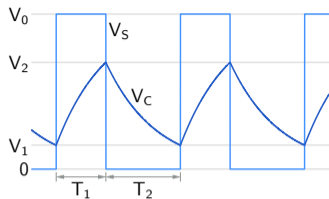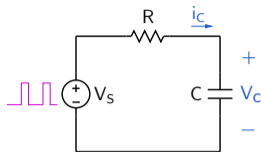

Charge conservation:

Periodic steady state: All quantities are periodic, i.e.,
 $x(t_0 + T) = x(t_0)$

Capacitor charge: $Q(t_0 + T) = Q(t_0)$


$$i_C = \frac{dQ}{dt} \rightarrow Q = \int i_C dt.$$

$$Q(t_0 + T) = Q(t_0) \rightarrow Q(t_0 + T) - Q(t_0) = 0$$

$$\rightarrow \int_{t_0}^{t_0+T} i_C dt = 0.$$

$$\int_0^T i_C dt = 0 \rightarrow \int_0^{T_1} i_C dt + \int_{T_1}^{T_1+T_2} i_C dt = 0$$
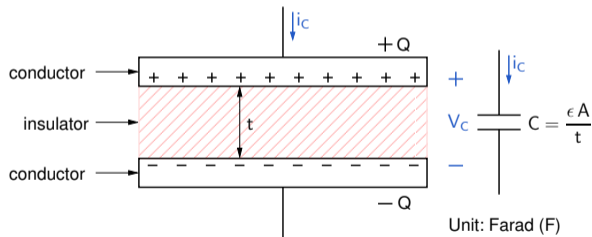
$$\rightarrow \int_{T_1}^{T_1+T_2} i_C dt = - \int_0^{T_1} i_C dt.$$







$$i_C = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

$T_1 = 1.5 \text{ msec}, T_2 = 1.5 \text{ msec}.$

$V_1 = 1.8 \text{ V}, V_2 = 8.2 \text{ V}.$

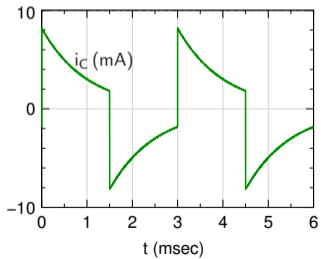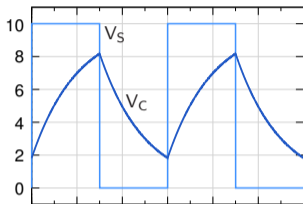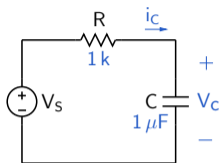$I_1 = 8.2 \text{ mA}, I_2 = 8.2 \text{ mA}.$





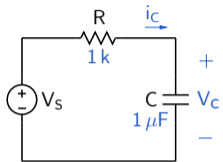

$$T_1 = 1.5 \text{ msec}, T_2 = 1.5 \text{ msec.}$$

$$V_1 = 1.8 \text{ V}, V_2 = 8.2 \text{ V.}$$

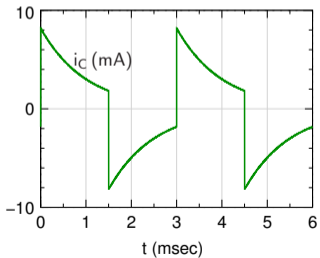
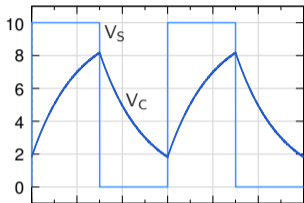
$$I_1 = 8.2 \text{ mA}, I_2 = 8.2 \text{ mA.}$$




$$T_1 = 1 \text{ msec}, T_2 = 2 \text{ msec.}$$

$$V_1 = 0.9 \text{ V}, V_2 = 6.7 \text{ V.}$$
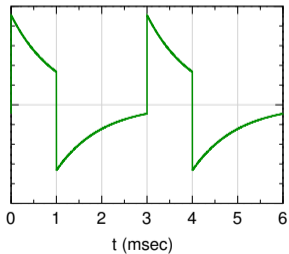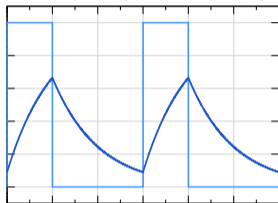
$$I_1 = 9.1 \text{ mA}, I_2 = 6.7 \text{ mA.}$$




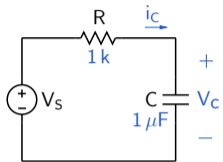

$$T_1 = 1.5 \text{ msec}, T_2 = 1.5 \text{ msec.}$$

$$V_1 = 1.8 \text{ V}, V_2 = 8.2 \text{ V.}$$

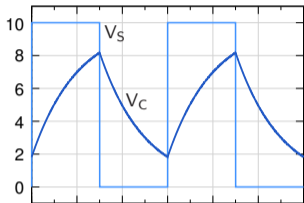
$$I_1 = 8.2 \text{ mA}, I_2 = 8.2 \text{ mA.}$$



$$T_1 = 1 \text{ msec}, T_2 = 2 \text{ msec.}$$

$$V_1 = 0.9 \text{ V}, V_2 = 6.7 \text{ V.}$$




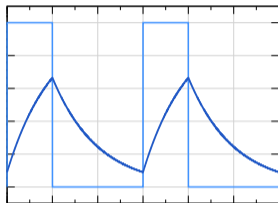
$$I_1 = 9.1 \text{ mA}, I_2 = 6.7 \text{ mA.}$$




$$T_1 = 2 \text{ msec}, T_2 = 1 \text{ msec.}$$



$$V_1 = 3.4 \text{ V}, V_2 = 9.1 \text{ V.}$$
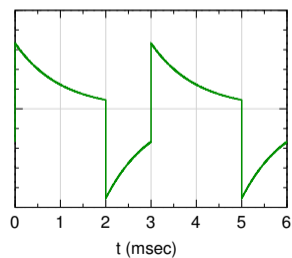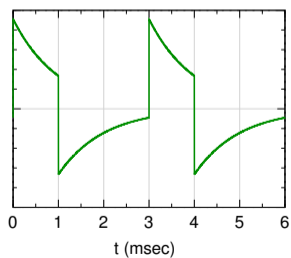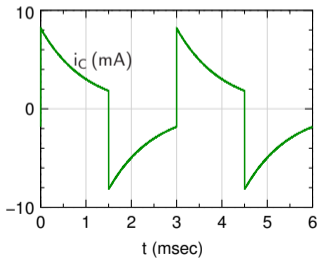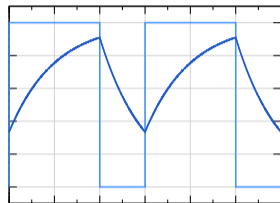
$$I_1 = 6.7 \text{ mA}, I_2 = 9.1 \text{ mA.}$$





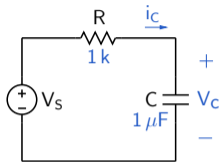

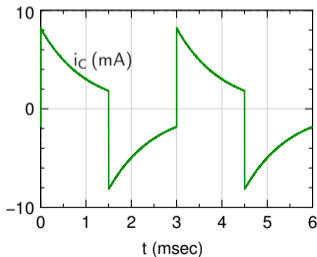
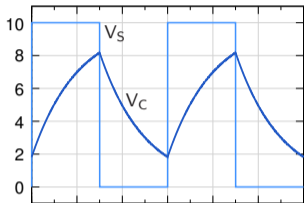
$T_1 = 1.5$ msec, $T_2 = 1.5$ msec.
 $V_1 = 1.8$ V, $V_2 = 8.2$ V.
 $I_1 = 8.2$ mA, $I_2 = 8.2$ mA.



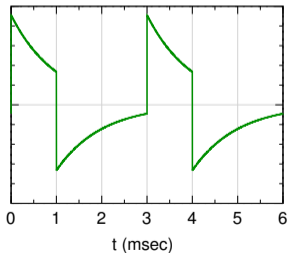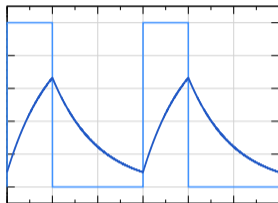$T_1 = 1$ msec, $T_2 = 2$ msec.
 $V_1 = 0.9$ V, $V_2 = 6.7$ V.
 $I_1 = 9.1$ mA, $I_2 = 6.7$ mA.



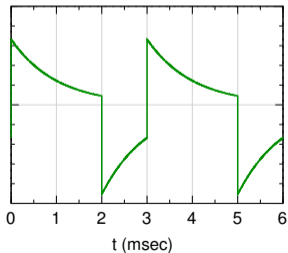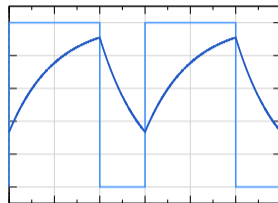$T_1 = 2$ msec, $T_2 = 1$ msec.
 $V_1 = 3.4$ V, $V_2 = 9.1$ V.
 $I_1 = 6.7$ mA, $I_2 = 9.1$ mA.



SEQUEL file: ee101_rc1b.sqproj

$T_1 = 1 \text{ msec}, T_2 = 2 \text{ msec}.$

$V_1 \approx 0 \text{ V}, V_2 = 10 \text{ V}.$

$I_1 = 100 \text{ mA}, I_2 = 100 \text{ mA}.$

