

# Network Theorems

---




M. B. Patil

[mbpatil@ee.iitb.ac.in](mailto:mbpatil@ee.iitb.ac.in)

[www.ee.iitb.ac.in/~sequel](http://www.ee.iitb.ac.in/~sequel)


Department of Electrical Engineering  
Indian Institute of Technology Bombay

## Thevenin's theorem

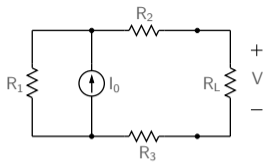

How is  $V$  related to the circuit parameters?


## Thevenin's theorem

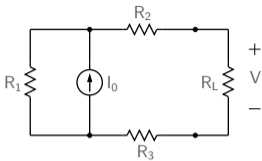

How is  $V$  related to the circuit parameters?

Assign node voltages with respect to a reference node.


## Thevenin's theorem

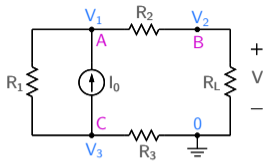

How is  $V$  related to the circuit parameters?

Assign node voltages with respect to a reference node.

## Thevenin's theorem

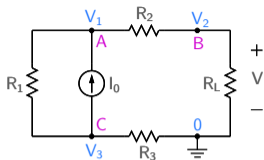


How is  $V$  related to the circuit parameters?

Assign node voltages with respect to a reference node.

Let  $G_1 \equiv 1/R_1$ , etc. Write KCL equation at each node, taking current leaving the node as positive.

## Thevenin's theorem

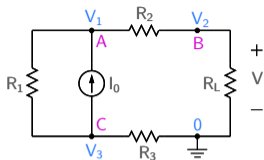

How is  $V$  related to the circuit parameters?


Assign node voltages with respect to a reference node.

Let  $G_1 \equiv 1/R_1$ , etc. Write KCL equation at each node, taking current leaving the node as positive.

$$\text{KCL at A : } G_1 (V_1 - V_3) + G_2 (V_1 - V_2) - I_0 = 0,$$

$$\text{KCL at B : } G_2 (V_2 - V_1) + G_L (V_2 - 0) = 0,$$
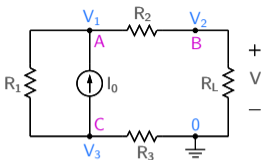
$$\text{KCL at C : } G_1 (V_3 - V_1) + G_3 V_3 + I_0 = 0.$$



How is  $V$  related to the circuit parameters?

Assign node voltages with respect to a reference node.

Let  $G_1 \equiv 1/R_1$ , etc. Write KCL equation at each node, taking current leaving the node as positive.


$$\begin{aligned} \text{KCL at A :} & \quad G_1 (V_1 - V_3) + G_2 (V_1 - V_2) - I_0 = 0, \\ \text{KCL at B :} & \quad G_2 (V_2 - V_1) + G_L (V_2 - 0) = 0, \\ \text{KCL at C :} & \quad G_1 (V_3 - V_1) + G_3 V_3 + I_0 = 0. \end{aligned}$$

Write in a matrix form:

$$\begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 \\ -G_2 & G_2 + G_L & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_0 \\ 0 \\ -I_0 \end{bmatrix},$$

i.e.,  $\mathbf{GV} = \mathbf{I}_s$ . We can solve this matrix equation to get  $V_2$ , i.e., the voltage across  $R_L$ .

## Thevenin's theorem

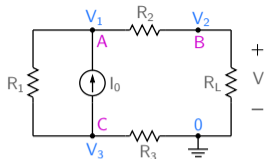


$V_2$  can be found using Cramer's rule:

$$V_2 = \frac{\det \begin{bmatrix} G_1 + G_2 & I_0 & -G_1 \\ -G_2 & 0 & 0 \\ -G_1 & -I_0 & G_1 + G_3 \end{bmatrix}}{\det(\mathbf{G})} \equiv \frac{\Delta_1}{\det(\mathbf{G})}$$




# Thevenin's theorem

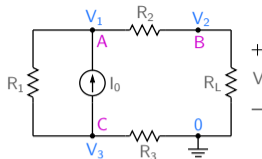


$V_2$  can be found using Cramer's rule: 
$$V_2 = \frac{\det \begin{bmatrix} G_1 + G_2 & I_0 & -G_1 \\ -G_2 & 0 & 0 \\ -G_1 & -I_0 & G_1 + G_3 \end{bmatrix}}{\det(\mathbf{G})} \equiv \frac{\Delta_1}{\det(\mathbf{G})}$$
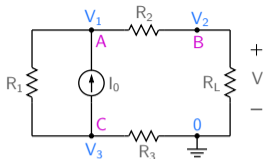
$$\det(\mathbf{G}) = \det \begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 \\ -G_2 & G_2 + G_L & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix}$$




$V_2$  can be found using Cramer's rule: 
$$V_2 = \frac{\det \begin{bmatrix} G_1 + G_2 & I_0 & -G_1 \\ -G_2 & 0 & 0 \\ -G_1 & -I_0 & G_1 + G_3 \end{bmatrix}}{\det(\mathbf{G})} \equiv \frac{\Delta_1}{\det(\mathbf{G})}$$
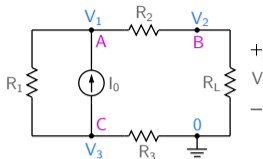
$$\begin{aligned} \det(\mathbf{G}) &= \det \begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 \\ -G_2 & G_2 + G_L & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} \\ &= \det \begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 \\ -G_2 & G_2 & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} + \det \begin{bmatrix} G_1 + G_2 & 0 & -G_1 \\ -G_2 & G_L & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} \end{aligned}$$



$V_2$  can be found using Cramer's rule: 
$$V_2 = \frac{\det \begin{bmatrix} G_1 + G_2 & I_0 & -G_1 \\ -G_2 & 0 & 0 \\ -G_1 & -I_0 & G_1 + G_3 \end{bmatrix}}{\det(\mathbf{G})} \equiv \frac{\Delta_1}{\det(\mathbf{G})}$$


$$\begin{aligned} \det(\mathbf{G}) &= \det \begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 \\ -G_2 & G_2 + G_L & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} \\ &= \det \begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 \\ -G_2 & G_2 & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} + \det \begin{bmatrix} G_1 + G_2 & 0 & -G_1 \\ -G_2 & G_L & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} \\ &= \Delta + G_L \Delta_2 \quad \text{where} \quad \Delta_2 = \det \begin{bmatrix} G_1 + G_2 & 0 & -G_1 \\ -G_2 & 1 & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix}. \end{aligned}$$

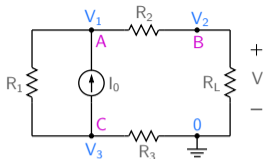


$V_2$  can be found using Cramer's rule: 
$$V_2 = \frac{\det \begin{bmatrix} G_1 + G_2 & I_0 & -G_1 \\ -G_2 & 0 & 0 \\ -G_1 & -I_0 & G_1 + G_3 \end{bmatrix}}{\det(\mathbf{G})} \equiv \frac{\Delta_1}{\det(\mathbf{G})}$$

$$\begin{aligned} \det(\mathbf{G}) &= \det \begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 \\ -G_2 & G_2 + G_L & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} \\ &= \det \begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 \\ -G_2 & G_2 & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} + \det \begin{bmatrix} G_1 + G_2 & 0 & -G_1 \\ -G_2 & G_L & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix} \\ &= \Delta + G_L \Delta_2 \quad \text{where} \quad \Delta_2 = \det \begin{bmatrix} G_1 + G_2 & 0 & -G_1 \\ -G_2 & 1 & 0 \\ -G_1 & 0 & G_1 + G_3 \end{bmatrix}. \end{aligned}$$

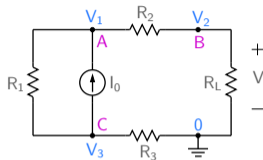i.e., 
$$V_2 = \frac{\Delta_1}{\det(\mathbf{G})} = \frac{\Delta_1}{\Delta + G_L \Delta_2} \quad (\text{Note: } \Delta, \Delta_1, \text{ and } \Delta_2 \text{ are independent of } G_L).$$



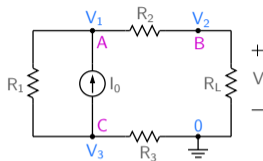
$$V_2 = \frac{\Delta_1}{\det(\mathbf{G})} = \frac{\Delta_1}{\Delta + G_L \Delta_2}.$$



$$V_2 = \frac{\Delta_1}{\det(\mathbf{G})} = \frac{\Delta_1}{\Delta + G_L \Delta_2}.$$

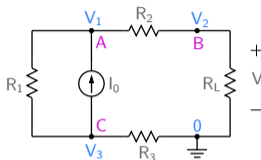
The "open-circuit" value of  $V_2$  is obtained by substituting  $R_L = \infty$ , i.e.,  $G_L = 0$ , leading to  $V_2^{\text{OC}} = \frac{\Delta_1}{\Delta}$ .



$$V_2 = \frac{\Delta_1}{\det(\mathbf{G})} = \frac{\Delta_1}{\Delta + G_L \Delta_2}.$$

The "open-circuit" value of  $V_2$  is obtained by substituting  $R_L = \infty$ , i.e.,  $G_L = 0$ , leading to  $V_2^{\text{OC}} = \frac{\Delta_1}{\Delta}$ .
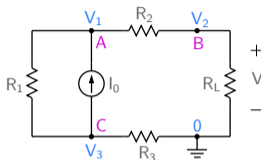
$$\text{We can now write } V_2 = \frac{\Delta_1/\Delta}{1 + G_L \Delta_2/\Delta} = \frac{V_2^{\text{OC}}}{1 + \frac{\Delta_2}{R_L \Delta}} = \frac{R_L}{R_L + \frac{\Delta_2}{\Delta}} V_2^{\text{OC}}.$$



$$V_2 = \frac{\Delta_1}{\det(\mathbf{G})} = \frac{\Delta_1}{\Delta + G_L \Delta_2}.$$


The "open-circuit" value of  $V_2$  is obtained by substituting  $R_L = \infty$ , i.e.,  $G_L = 0$ , leading to  $V_2^{\text{OC}} = \frac{\Delta_1}{\Delta}$ .

$$\text{We can now write } V_2 = \frac{\Delta_1/\Delta}{1 + G_L \Delta_2/\Delta} = \frac{V_2^{\text{OC}}}{1 + \frac{\Delta_2}{R_L \Delta}} = \frac{R_L}{R_L + \frac{\Delta_2}{\Delta}} V_2^{\text{OC}}.$$

Note that  $\Delta_2/\Delta$  has units of resistance. Define  $R_{\text{Th}} = \Delta_2/\Delta$  (Thevenin resistance). Then we have
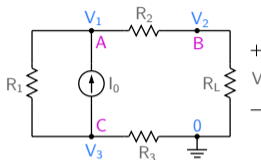
$$V_2 = \frac{R_L}{R_L + R_{\text{Th}}} V_2^{\text{OC}}.$$





$$V_2 = \frac{\Delta_1}{\det(\mathbf{G})} = \frac{\Delta_1}{\Delta + G_L \Delta_2}.$$

The "open-circuit" value of  $V_2$  is obtained by substituting  $R_L = \infty$ , i.e.,  $G_L = 0$ , leading to  $V_2^{\text{OC}} = \frac{\Delta_1}{\Delta}$ .

$$\text{We can now write } V_2 = \frac{\Delta_1/\Delta}{1 + G_L \Delta_2/\Delta} = \frac{V_2^{\text{OC}}}{1 + \frac{\Delta_2}{R_L \Delta}} = \frac{R_L}{R_L + \frac{\Delta_2}{\Delta}} V_2^{\text{OC}}.$$

Note that  $\Delta_2/\Delta$  has units of resistance. Define  $R_{\text{Th}} = \Delta_2/\Delta$  (Thevenin resistance). Then we have


$$V_2 = \frac{R_L}{R_L + R_{\text{Th}}} V_2^{\text{OC}}.$$


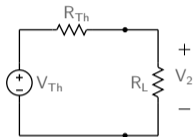
## Thevenin's theorem

$$V_2 = \frac{R_L}{R_L + R_{Th}} V_2^{OC}.$$


This is simply a voltage division formula, corresponding to the following “Thevenin equivalent circuit” (with  $V_{Th} = V_2^{OC}$ ).



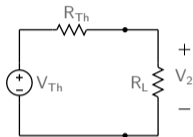
## Thevenin's theorem


$$V_2 = \frac{R_L}{R_L + R_{Th}} V_2^{OC}.$$

This is simply a voltage division formula, corresponding to the following “Thevenin equivalent circuit” (with  $V_{Th} = V_2^{OC}$ ).




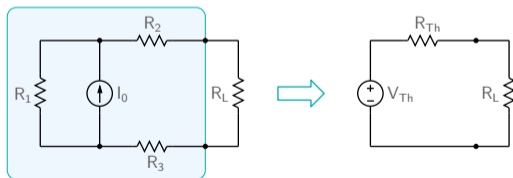This allows us to replace the original circuit with an equivalent, simpler circuit.




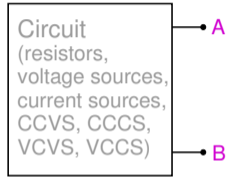

# Thevenin's theorem

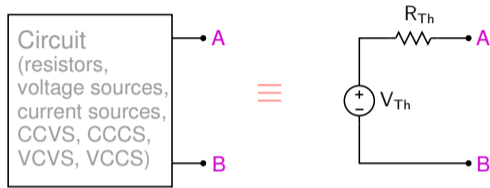


# Thevenin's theorem

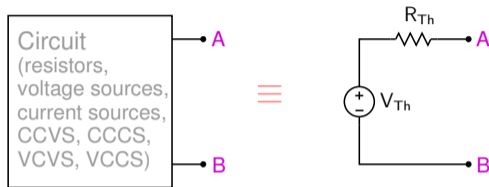

- \* Since the two circuits are equivalent, the open-circuit voltage must be the same in both cases. Let  $V_{oc}$  be the open-circuit voltage for the left circuit. For the Thevenin equivalent circuit, the open-circuit voltage is simply  $V_{Th}$  since there is no voltage drop across  $R_{Th}$  in this case.

$$\rightarrow V_{Th} = V_{oc}$$


# Thevenin's theorem

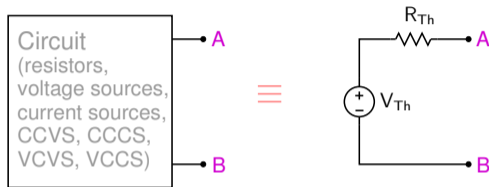

- \* Since the two circuits are equivalent, the open-circuit voltage must be the same in both cases. Let  $V_{oc}$  be the open-circuit voltage for the left circuit. For the Thevenin equivalent circuit, the open-circuit voltage is simply  $V_{Th}$  since there is no voltage drop across  $R_{Th}$  in this case.  
 $\rightarrow V_{Th} = V_{oc}$
- \*  $R_{Th}$  can be found by different methods.

# Thevenin's theorem: $R_{Th}$

Method 1:

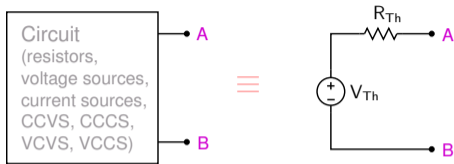


\* Deactivate all *independent* sources. This amounts to making  $V_{Th} = 0$  in the Thevenin equivalent circuit.



# Thevenin's theorem: $R_{Th}$


Method 1:

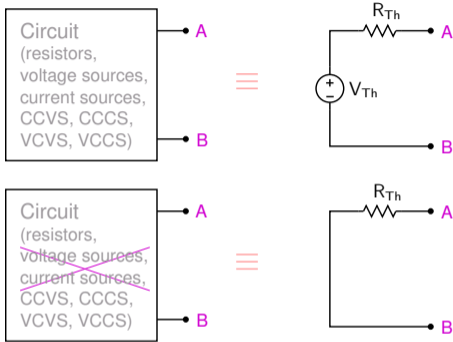

\* Deactivate all *independent* sources. This amounts to making  $V_{Th} = 0$  in the Thevenin equivalent circuit.

# Thevenin's theorem: $R_{Th}$


Method 1:

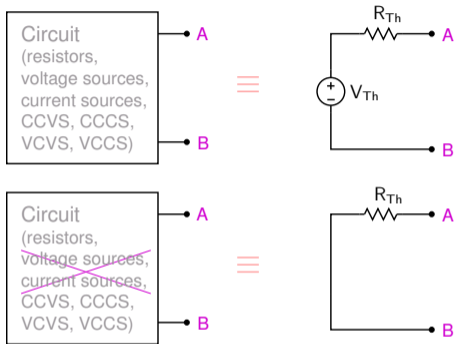

- \* Deactivate all *independent* sources. This amounts to making  $V_{Th} = 0$  in the Thevenin equivalent circuit.
- \* Often,  $R_{Th}$  can be found by inspection of the original circuit (with independent sources deactivated).

# Thevenin's theorem: $R_{Th}$


Method 1:

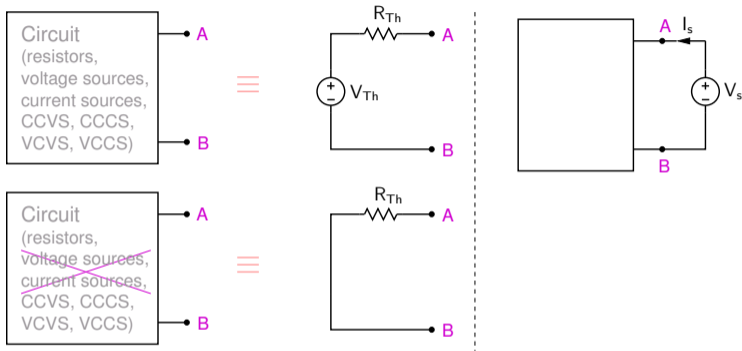

- \* Deactivate all *independent* sources. This amounts to making  $V_{Th} = 0$  in the Thevenin equivalent circuit.
- \* Often,  $R_{Th}$  can be found by inspection of the original circuit (with independent sources deactivated).
- \*  $R_{Th}$  can also be found by connecting a *test* source to the original circuit (with independent sources deactivated):  $R_{Th} = V_s / I_s$ .

# Thevenin's theorem: $R_{Th}$


Method 1:

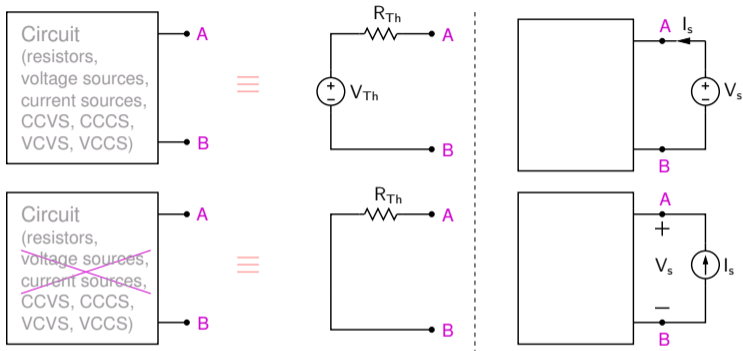

- \* Deactivate all *independent* sources. This amounts to making  $V_{Th} = 0$  in the Thevenin equivalent circuit.
- \* Often,  $R_{Th}$  can be found by inspection of the original circuit (with independent sources deactivated).
- \*  $R_{Th}$  can also be found by connecting a *test* source to the original circuit (with independent sources deactivated):  $R_{Th} = V_s / I_s$ .

# Thevenin's theorem: $R_{Th}$


Method 2:

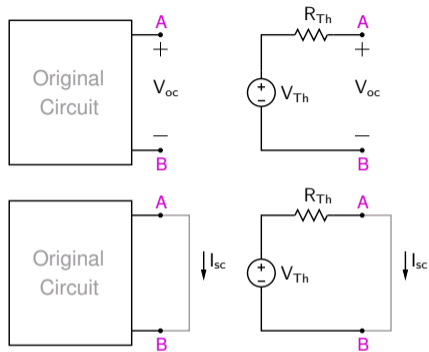

\* For the Thevenin equivalent circuit,  $V_{oc} = V_{Th}$ ,  $I_{sc} = \frac{V_{Th}}{R_{Th}} = \frac{V_{oc}}{R_{Th}} \rightarrow R_{Th} = \frac{V_{oc}}{I_{sc}}$ .

# Thevenin's theorem: $R_{Th}$

Method 2:

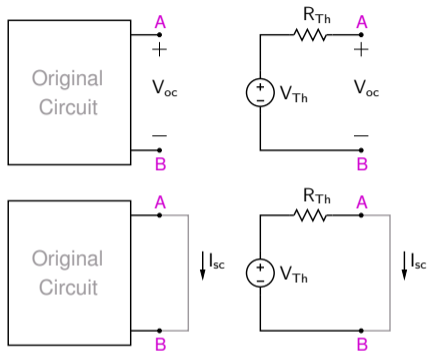


\* For the Thevenin equivalent circuit,  $V_{oc} = V_{Th}$ ,  $I_{sc} = \frac{V_{Th}}{R_{Th}} = \frac{V_{oc}}{R_{Th}} \rightarrow R_{Th} = \frac{V_{oc}}{I_{sc}}$ .

\* In the original circuit, find  $V_{oc}$  and  $I_{sc} \rightarrow R_{Th} = \frac{V_{oc}}{I_{sc}}$ .

# Thevenin's theorem: $R_{Th}$

Method 2:

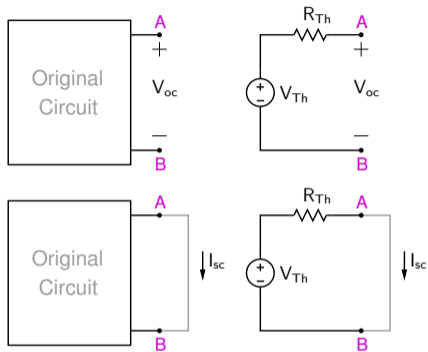


\* For the Thevenin equivalent circuit,  $V_{oc} = V_{Th}$ ,  $I_{sc} = \frac{V_{Th}}{R_{Th}} = \frac{V_{oc}}{R_{Th}} \rightarrow R_{Th} = \frac{V_{oc}}{I_{sc}}$ .

\* In the original circuit, find  $V_{oc}$  and  $I_{sc} \rightarrow R_{Th} = \frac{V_{oc}}{I_{sc}}$ .


\* Note: We do not deactivate any sources in this case.

## Thevenin's theorem: example


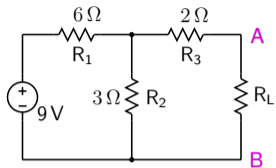






## Thevenin's theorem: example

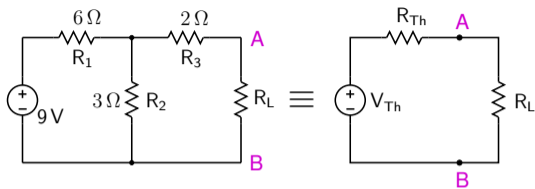

# Thevenin's theorem: example

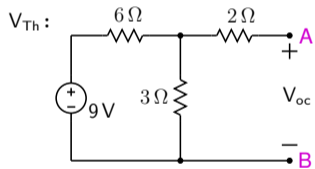
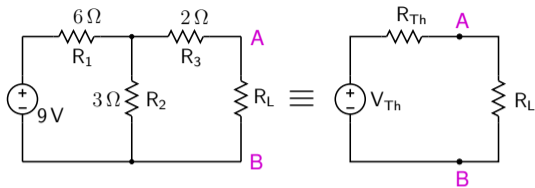


# Thevenin's theorem: example

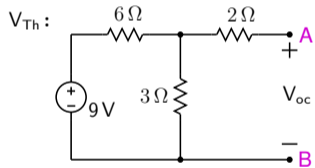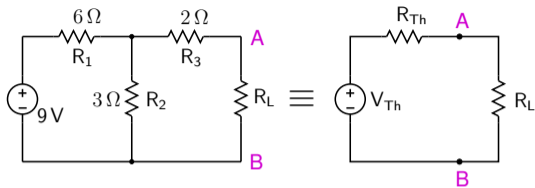


$$\begin{aligned}V_{oc} &= 9V \times \frac{3\Omega}{6\Omega + 3\Omega} \\ &= 9V \times \frac{1}{3} = 3V\end{aligned}$$



# Thevenin's theorem: example

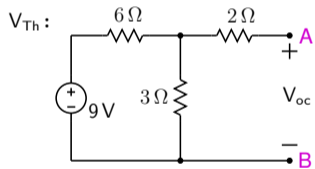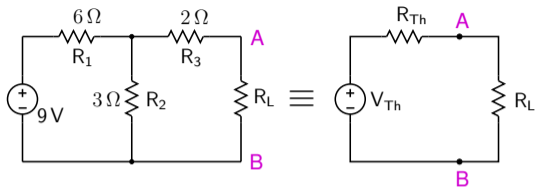

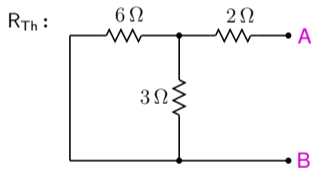
$$\begin{aligned}V_{oc} &= 9V \times \frac{3\Omega}{6\Omega + 3\Omega} \\ &= 9V \times \frac{1}{3} = 3V\end{aligned}$$



# Thevenin's theorem: example

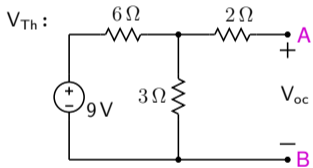
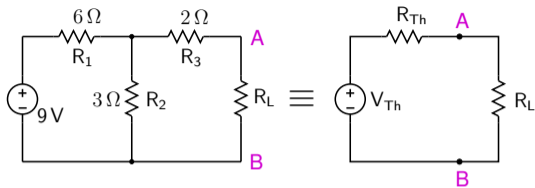

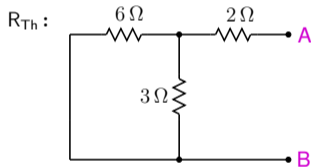
$$\begin{aligned}V_{oc} &= 9V \times \frac{3\Omega}{6\Omega + 3\Omega} \\ &= 9V \times \frac{1}{3} = 3V\end{aligned}$$




$$\begin{aligned}R_{Th} &= (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2 \\ &= 3 \times \left(\frac{1 \times 2}{1 + 2}\right) + 2 = 4\Omega\end{aligned}$$

# Thevenin's theorem: example

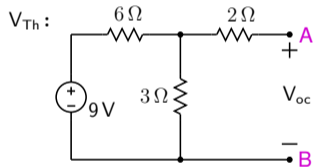
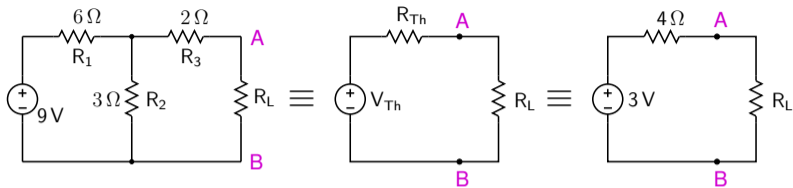

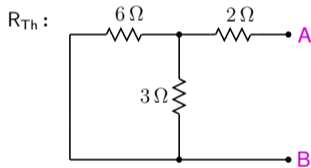
$$\begin{aligned}V_{oc} &= 9V \times \frac{3\Omega}{6\Omega + 3\Omega} \\ &= 9V \times \frac{1}{3} = 3V\end{aligned}$$




$$\begin{aligned}R_{Th} &= (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2 \\ &= 3 \times \left(\frac{1 \times 2}{1 + 2}\right) + 2 = 4\Omega\end{aligned}$$

# Thevenin's theorem: example

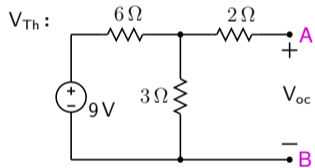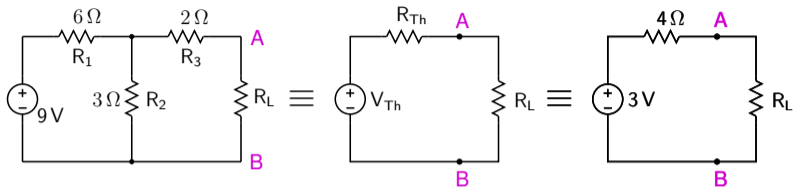

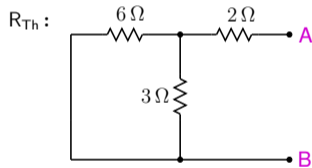
$$V_{oc} = 9V \times \frac{3\Omega}{6\Omega + 3\Omega}$$
$$= 9V \times \frac{1}{3} = 3V$$




$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$
$$= 3 \times \left( \frac{1 \times 2}{1 + 2} \right) + 2 = 4\Omega$$

## Thevenin's theorem: example

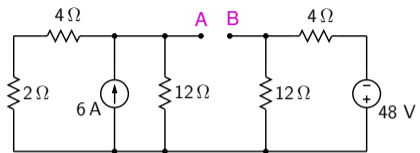





# Thevenin's theorem: example

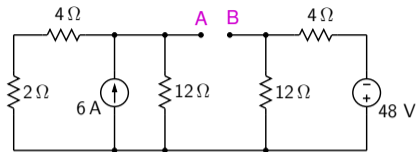



$R_{Th}$ :

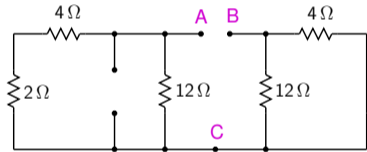


# Thevenin's theorem: example

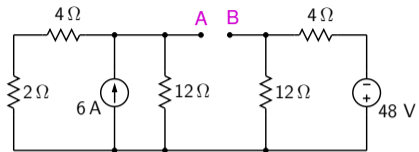



$R_{Th}$ :

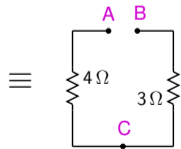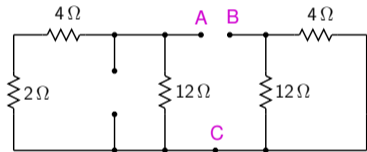



# Thevenin's theorem: example

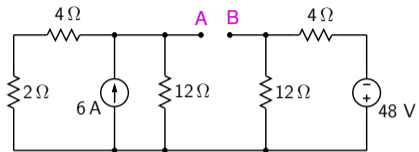



$R_{Th}$ :

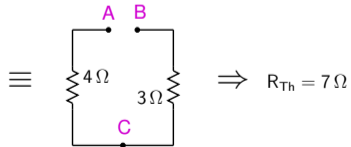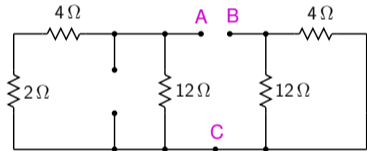


# Thevenin's theorem: example

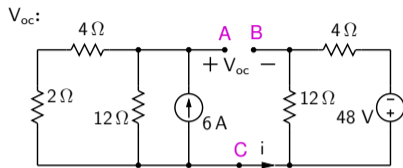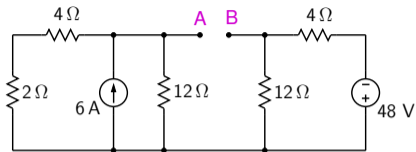




$R_{Th}$ :

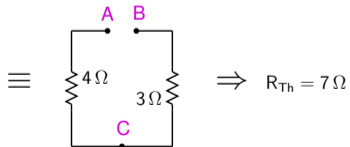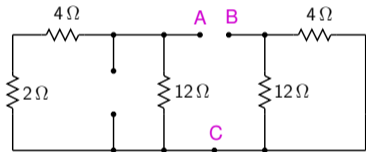

# Thevenin's theorem: example

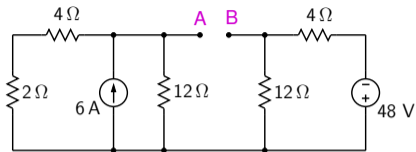


$R_{Th}$ :

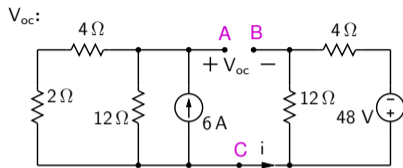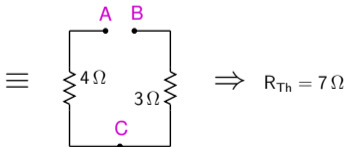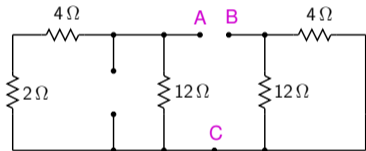




Note:  $i = 0$  (since there is no return path).

$$\begin{aligned}
 V_{AB} &= V_A - V_B \\
 &= (V_A - V_C) + (V_C - V_B) \\
 &= V_{AC} + V_{CB} \\
 &= 24\text{ V} + 36\text{ V} = 60\text{ V}
 \end{aligned}$$

# Thevenin's theorem: example

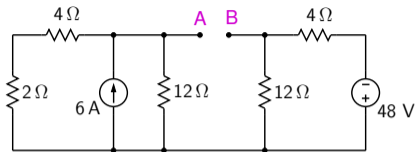

$R_{Th}$ :

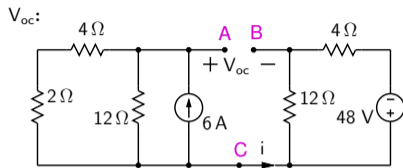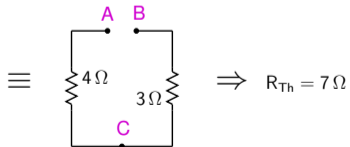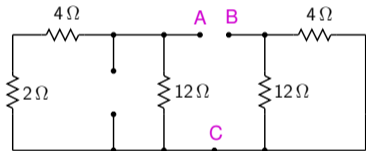


Note:  $i = 0$  (since there is no return path).

$$\begin{aligned}
 V_{AB} &= V_A - V_B \\
 &= (V_A - V_C) + (V_C - V_B) \\
 &= V_{AC} + V_{CB} \\
 &= 24\text{ V} + 36\text{ V} = 60\text{ V}
 \end{aligned}$$




$$V_{Th} = 60\text{ V}$$

$$R_{Th} = 7\ \Omega$$

# Thevenin's theorem: example

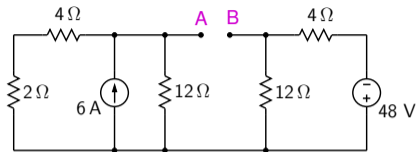


$R_{Th}$ :

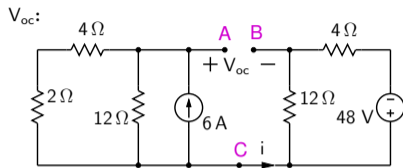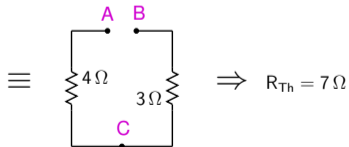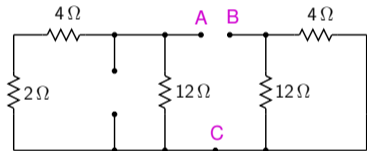



Note:  $i = 0$  (since there is no return path).

$$\begin{aligned} V_{AB} &= V_A - V_B \\ &= (V_A - V_C) + (V_C - V_B) \\ &= V_{AC} + V_{CB} \\ &= 24\text{ V} + 36\text{ V} = 60\text{ V} \end{aligned}$$
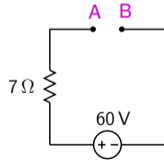
$$\begin{aligned} V_{Th} &= 60\text{ V} \\ R_{Th} &= 7\Omega \end{aligned}$$



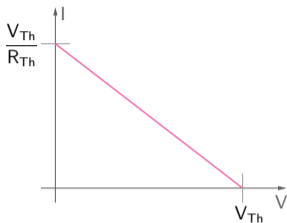
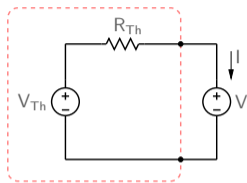
## Graphical method for finding $V_{Th}$ and $R_{Th}$



$$I = \frac{V_{Th} - V}{R_{Th}} \quad (\text{Note: negative slope for } I \text{ versus } V \text{ plot})$$



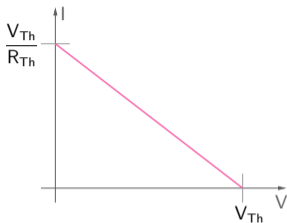
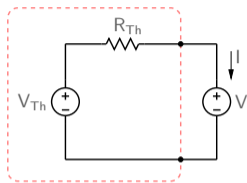
## Graphical method for finding $V_{Th}$ and $R_{Th}$



$$I = \frac{V_{Th} - V}{R_{Th}} \quad (\text{Note: negative slope for } I \text{ versus } V \text{ plot})$$

$$I = 0 \rightarrow V = V_{Th} \quad (\text{same as } V_{oc})$$
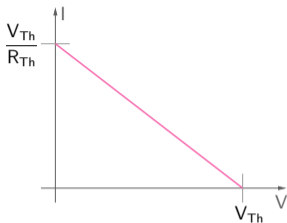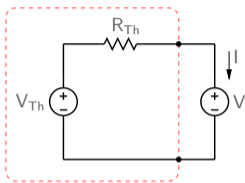
## Graphical method for finding $V_{Th}$ and $R_{Th}$





$$I = \frac{V_{Th} - V}{R_{Th}} \quad (\text{Note: negative slope for } I \text{ versus } V \text{ plot})$$

$$I = 0 \rightarrow V = V_{Th} \quad (\text{same as } V_{oc})$$

$$V = 0 \rightarrow I = \frac{V_{Th}}{R_{Th}} \quad (\text{same as } I_{sc})$$
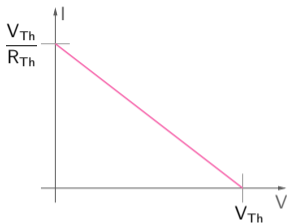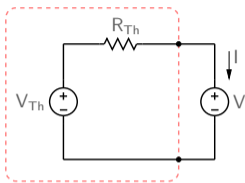
## Graphical method for finding $V_{Th}$ and $R_{Th}$





$$I = \frac{V_{Th} - V}{R_{Th}} \quad (\text{Note: negative slope for } I \text{ versus } V \text{ plot})$$

$$I = 0 \rightarrow V = V_{Th} \quad (\text{same as } V_{oc})$$

$$V = 0 \rightarrow I = \frac{V_{Th}}{R_{Th}} \quad (\text{same as } I_{sc})$$

i.e., a plot of  $I$  versus  $V$  can be used to find  $V_{Th}$  and  $R_{Th}$ .
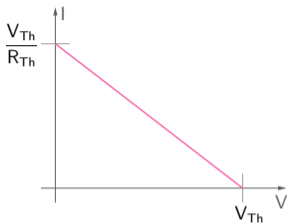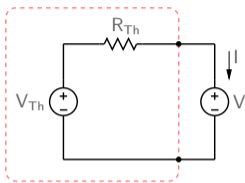
## Graphical method for finding $V_{Th}$ and $R_{Th}$



$$I = \frac{V_{Th} - V}{R_{Th}} \quad (\text{Note: negative slope for } I \text{ versus } V \text{ plot})$$

$$I = 0 \rightarrow V = V_{Th} \quad (\text{same as } V_{oc})$$


$$V = 0 \rightarrow I = \frac{V_{Th}}{R_{Th}} \quad (\text{same as } I_{sc})$$

i.e., a plot of  $I$  versus  $V$  can be used to find  $V_{Th}$  and  $R_{Th}$ .

(Instead of a voltage source, we could also connect a resistor load ( $R$ ), vary  $R$ , and then plot  $I$  versus  $V$ .)


# Graphical method for finding $V_{Th}$ and $R_{Th}$

SEQUEL file: ee101\_thevenin\_1.sqproj

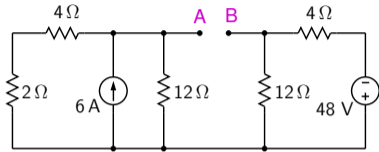


# Graphical method for finding $V_{Th}$ and $R_{Th}$

SEQUEL file: ee101\_thevenin\_1.sqproj

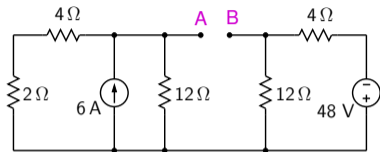

Connect a voltage source between A and B.

Plot  $i$  versus  $v$ .

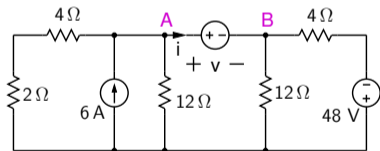


$V_{oc}$  = intercept on the  $v$ -axis.

$I_{sc}$  = intercept on the  $i$ -axis.


# Graphical method for finding $V_{Th}$ and $R_{Th}$

SEQUEL file: ee101\_thevenin\_1.sqproj

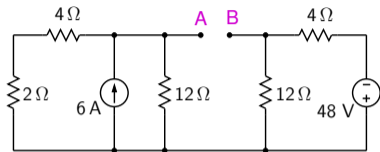


Connect a voltage source between A and B.

Plot  $i$  versus  $v$ .

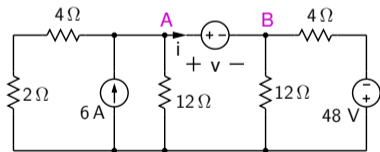


$V_{oc}$  = intercept on the  $v$ -axis.

$I_{sc}$  = intercept on the  $i$ -axis.

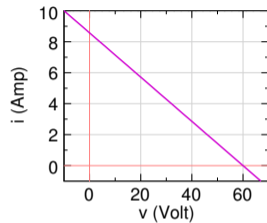


# Graphical method for finding $V_{Th}$ and $R_{Th}$

SEQUEL file: ee101\_thevenin\_1.sqproj

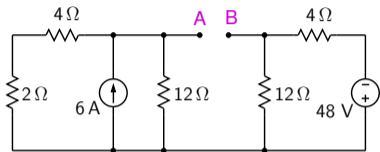


Connect a voltage source between A and B.

Plot  $i$  versus  $v$ .

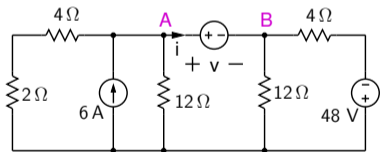

$V_{oc}$  = intercept on the  $v$ -axis.

$I_{sc}$  = intercept on the  $i$ -axis.

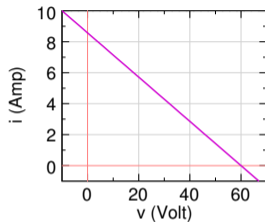


$$V_{oc} = 60\text{ V}, I_{sc} = 8.57\text{ A}$$

$$R_{Th} = V_{oc}/I_{sc} = 7\ \Omega$$




# Graphical method for finding $V_{Th}$ and $R_{Th}$

SEQUEL file: ee101\_thevenin\_1.sqproj

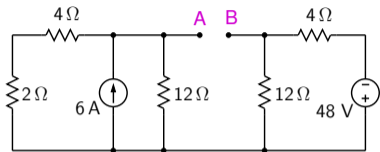


Connect a voltage source between A and B.

Plot  $i$  versus  $v$ .

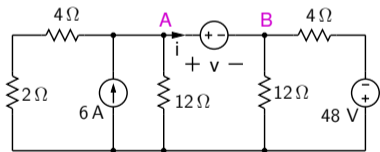


$V_{oc}$  = intercept on the  $v$ -axis.

$I_{sc}$  = intercept on the  $i$ -axis.

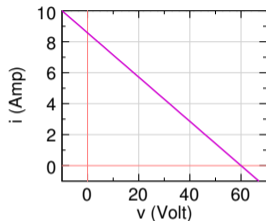


$$V_{oc} = 60 \text{ V}, I_{sc} = 8.57 \text{ A}$$


$$R_{Th} = V_{oc}/I_{sc} = 7 \Omega$$

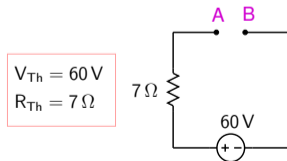


## Thevenin's theorem: example

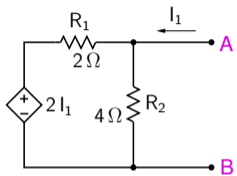


# Thevenin's theorem: example

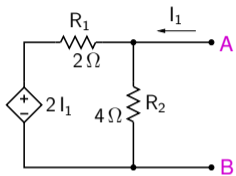



$$V_{Th} = V_{oc}$$

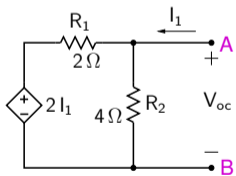

# Thevenin's theorem: example

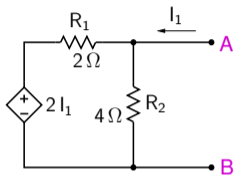


$$V_{Th} = V_{oc}$$

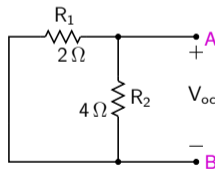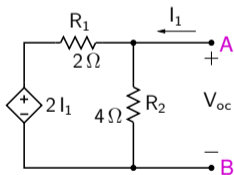


$$V_{Th} = 0$$

## Thevenin's theorem: example

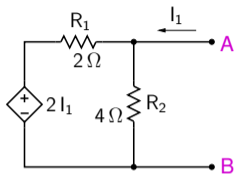


$R_{Th}$ : Deactivate independent sources, connect a test source.


## Thevenin's theorem: example

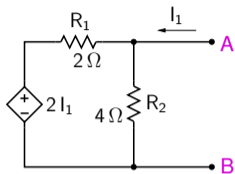

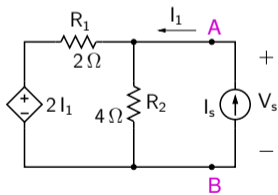
$R_{Th}$ : Deactivate independent sources, connect a test source.




## Thevenin's theorem: example

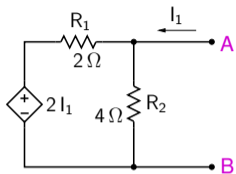

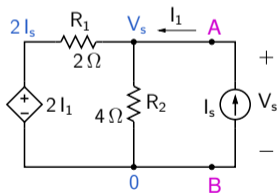
$R_{Th}$ : Deactivate independent sources, connect a test source.



# Thevenin's theorem: example

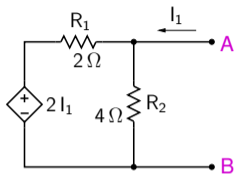

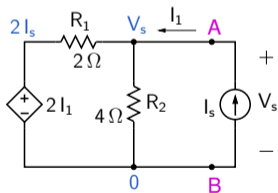$R_{Th}$ : Deactivate independent sources, connect a test source.




We need to compute  $R_{Th} = \frac{V_s}{I_s}$ .


$$\text{KCL: } -I_s + \frac{V_s}{R_2} + \frac{V_s - 2I_s}{R_1} = 0$$



## Thevenin's theorem: example

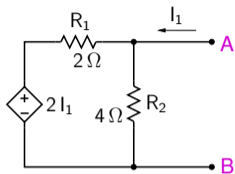

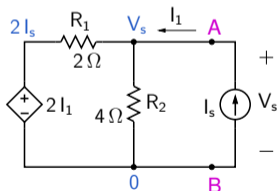$R_{Th}$ : Deactivate independent sources, connect a test source.




We need to compute  $R_{Th} = \frac{V_s}{I_s}$ .

$$\text{KCL: } -I_s + \frac{V_s}{R_2} + \frac{V_s - 2I_s}{R_1} = 0$$


$$\rightarrow V_s \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = I_s \left( 1 + \frac{2}{R_1} \right)$$

$$\rightarrow R_{Th} = \frac{V_s}{I_s} = \frac{8}{3} \Omega$$

# Thevenin's theorem: example

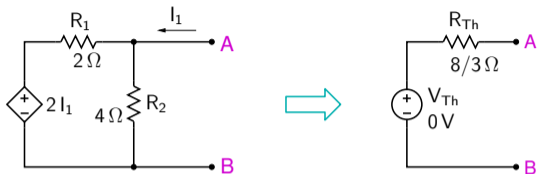

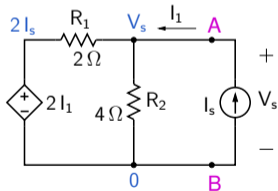$R_{Th}$ : Deactivate independent sources, connect a test source.




We need to compute  $R_{Th} = \frac{V_s}{I_s}$ .

$$\text{KCL: } -I_s + \frac{V_s}{R_2} + \frac{V_s - 2I_s}{R_1} = 0$$


$$\rightarrow V_s \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = I_s \left( 1 + \frac{2}{R_1} \right)$$

$$\rightarrow R_{Th} = \frac{V_s}{I_s} = \frac{8}{3} \Omega$$

# Thevenin's theorem: example

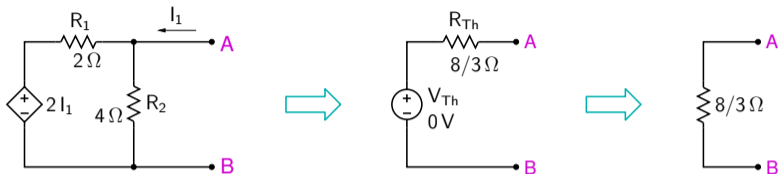

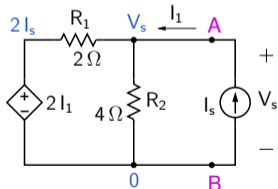$R_{Th}$ : Deactivate independent sources, connect a test source.




We need to compute  $R_{Th} = \frac{V_s}{I_s}$ .

$$\text{KCL: } -I_s + \frac{V_s}{R_2} + \frac{V_s - 2I_s}{R_1} = 0$$


$$\rightarrow V_s \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = I_s \left( 1 + \frac{2}{R_1} \right)$$

$$\rightarrow R_{Th} = \frac{V_s}{I_s} = \frac{8}{3} \Omega$$

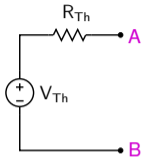
## Norton equivalent circuit (source transformation)


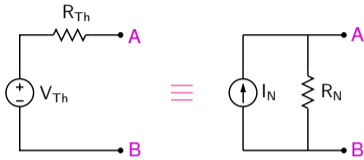
# Norton equivalent circuit (source transformation)



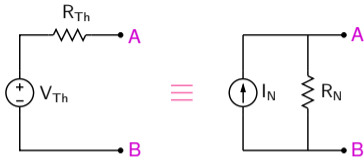
## Norton equivalent circuit (source transformation)



\* Consider the open circuit case.

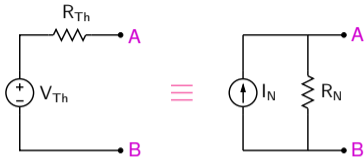
## Norton equivalent circuit (source transformation)



\* Consider the open circuit case.

Thevenin circuit:  $V_{AB} = V_{Th}$ .
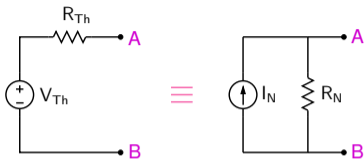
## Norton equivalent circuit (source transformation)




\* Consider the open circuit case.

Thevenin circuit:  $V_{AB} = V_{Th}$ .

Norton circuit:  $V_{AB} = I_N R_N$ .


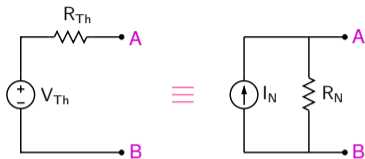
## Norton equivalent circuit (source transformation)




\* Consider the open circuit case.

Thevenin circuit:  $V_{AB} = V_{Th}$ .

Norton circuit:  $V_{AB} = I_N R_N$ .

$\Rightarrow V_{Th} = I_N R_N$ .
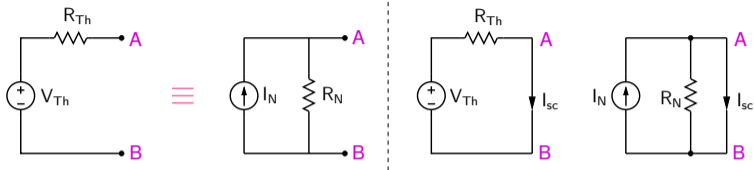
## Norton equivalent circuit (source transformation)



- \* Consider the open circuit case.


Thevenin circuit:  $V_{AB} = V_{Th}$ .

Norton circuit:  $V_{AB} = I_N R_N$ .

$$\Rightarrow V_{Th} = I_N R_N.$$

- \* Consider the short circuit case.
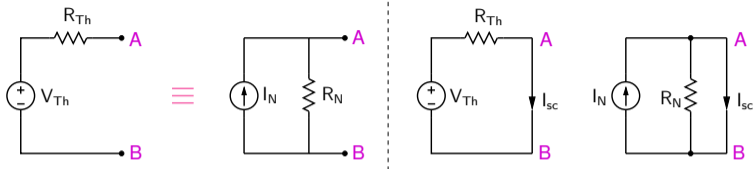
# Norton equivalent circuit (source transformation)



- \* Consider the open circuit case.

Thevenin circuit:  $V_{AB} = V_{Th}$ .


Norton circuit:  $V_{AB} = I_N R_N$ .

$$\Rightarrow V_{Th} = I_N R_N.$$

- \* Consider the short circuit case.

Thevenin circuit:  $I_{sc} = V_{Th}/R_{Th}$ .
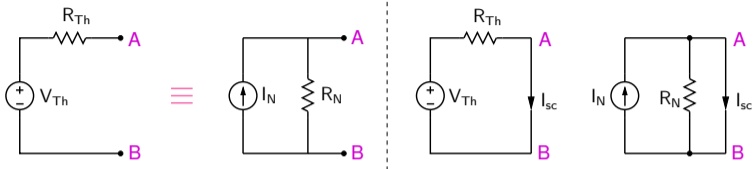
# Norton equivalent circuit (source transformation)



- \* Consider the open circuit case.

Thevenin circuit:  $V_{AB} = V_{Th}$ .

Norton circuit:  $V_{AB} = I_N R_N$ .


$$\Rightarrow V_{Th} = I_N R_N.$$

- \* Consider the short circuit case.

Thevenin circuit:  $I_{sc} = V_{Th}/R_{Th}$ .

Norton circuit:  $I_{sc} = I_N$ .
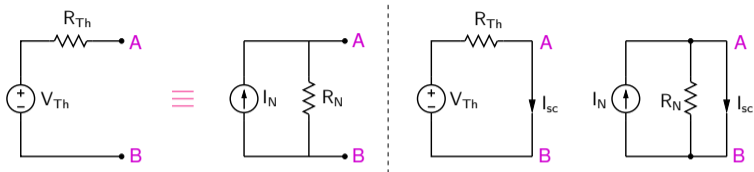
# Norton equivalent circuit (source transformation)



- \* Consider the open circuit case.

Thevenin circuit:  $V_{AB} = V_{Th}$ .

Norton circuit:  $V_{AB} = I_N R_N$ .

$$\Rightarrow V_{Th} = I_N R_N.$$


- \* Consider the short circuit case.

Thevenin circuit:  $I_{sc} = V_{Th}/R_{Th}$ .

Norton circuit:  $I_{sc} = I_N$ .

$$\Rightarrow V_{Th} = \frac{V_{Th}}{R_{Th}} R_N$$
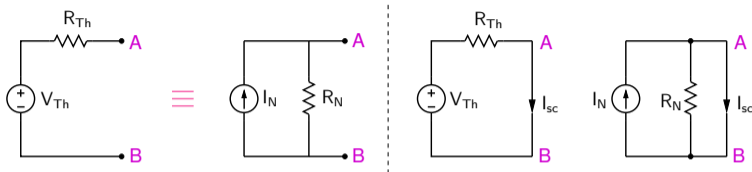
# Norton equivalent circuit (source transformation)



- \* Consider the open circuit case.

Thevenin circuit:  $V_{AB} = V_{Th}$ .

Norton circuit:  $V_{AB} = I_N R_N$ .

$$\Rightarrow V_{Th} = I_N R_N.$$


- \* Consider the short circuit case.

Thevenin circuit:  $I_{sc} = V_{Th}/R_{Th}$ .

Norton circuit:  $I_{sc} = I_N$ .

$$\Rightarrow V_{Th} = \frac{V_{Th}}{R_{Th}} R_N \rightarrow R_{Th} = R_N.$$
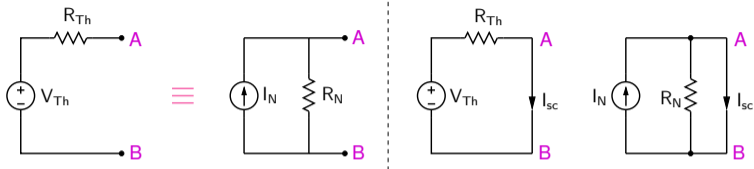
# Norton equivalent circuit (source transformation)



- \* Consider the open circuit case.

Thevenin circuit:  $V_{AB} = V_{Th}$ .

Norton circuit:  $V_{AB} = I_N R_N$ .

$$\Rightarrow V_{Th} = I_N R_N.$$

- \* Consider the short circuit case.


Thevenin circuit:  $I_{sc} = V_{Th}/R_{Th}$ .

Norton circuit:  $I_{sc} = I_N$ .

$$\Rightarrow V_{Th} = \frac{V_{Th}}{R_{Th}} R_N \rightarrow R_{Th} = R_N.$$

$$R_N = R_{Th}, I_N = \frac{V_{Th}}{R_{Th}}$$
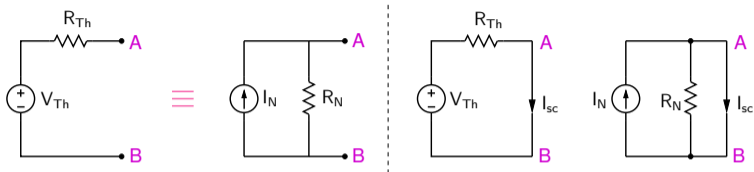
# Norton equivalent circuit (source transformation)



- \* Consider the open circuit case.

Thevenin circuit:  $V_{AB} = V_{Th}$ .

Norton circuit:  $V_{AB} = I_N R_N$ .

$$\Rightarrow V_{Th} = I_N R_N.$$

- \* Consider the short circuit case.

Thevenin circuit:  $I_{sc} = V_{Th}/R_{Th}$ .

Norton circuit:  $I_{sc} = I_N$ .


$$\Rightarrow V_{Th} = \frac{V_{Th}}{R_{Th}} R_N \rightarrow R_{Th} = R_N.$$

$$R_N = R_{Th}, I_N = \frac{V_{Th}}{R_{Th}}$$



$$R_{Th} = R_N, V_{Th} = I_N R_N$$






## Source transformation: example

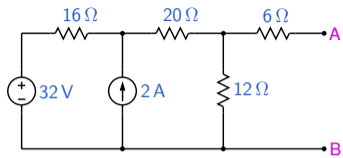





## Source transformation: example

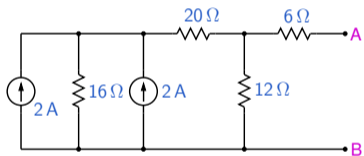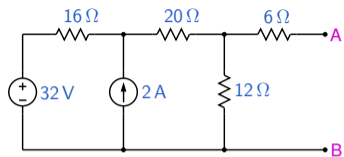






## Source transformation: example

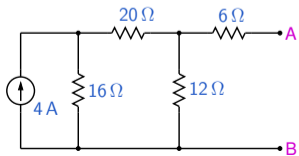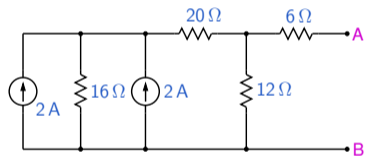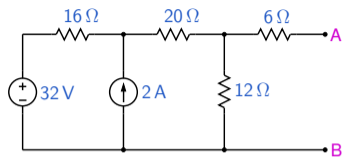


## Source transformation: example

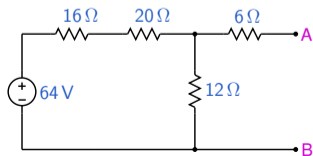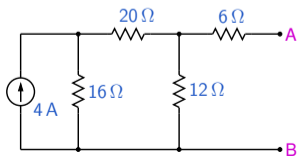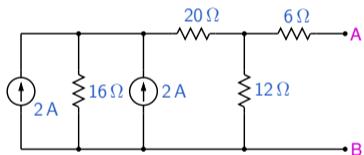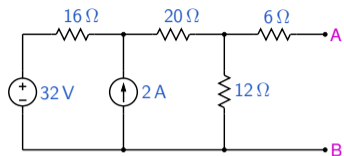


# Source transformation: example

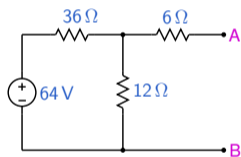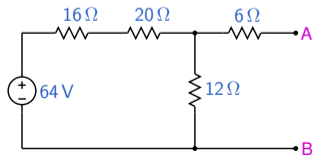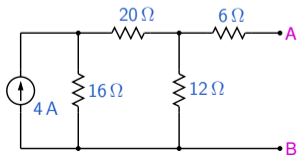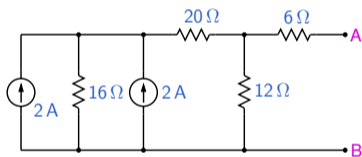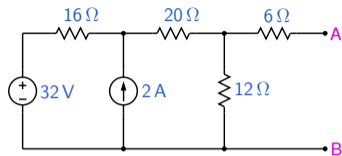


# Source transformation: example

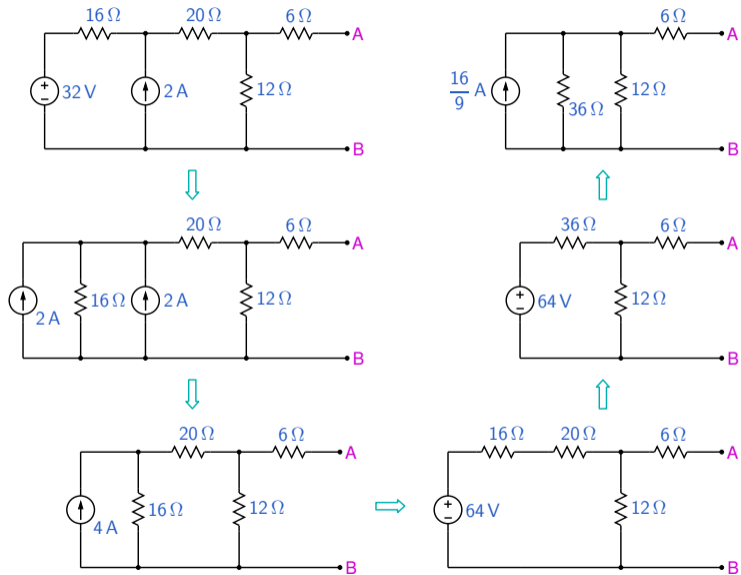

# Source transformation: example

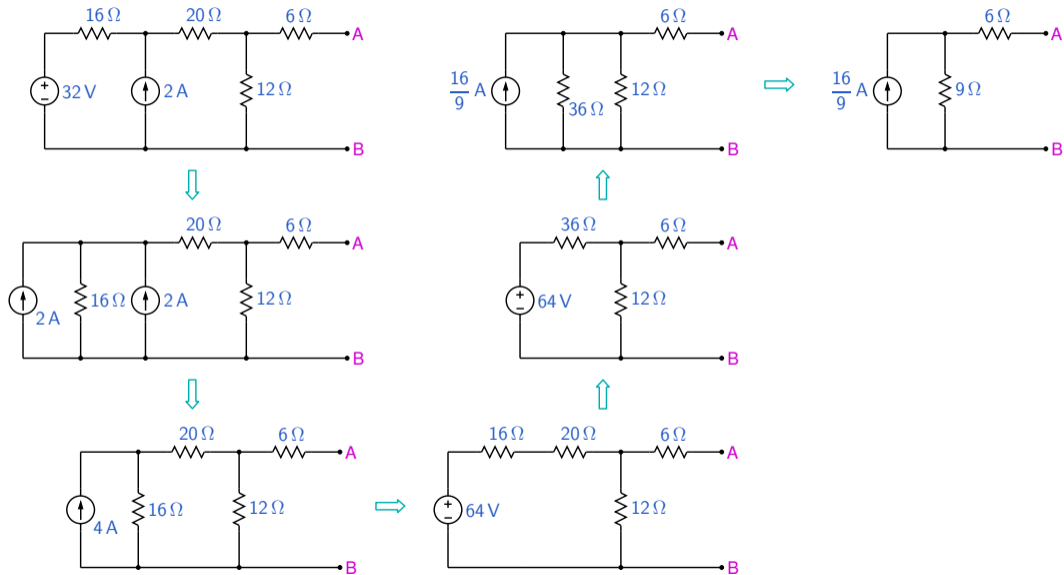


# Source transformation: example

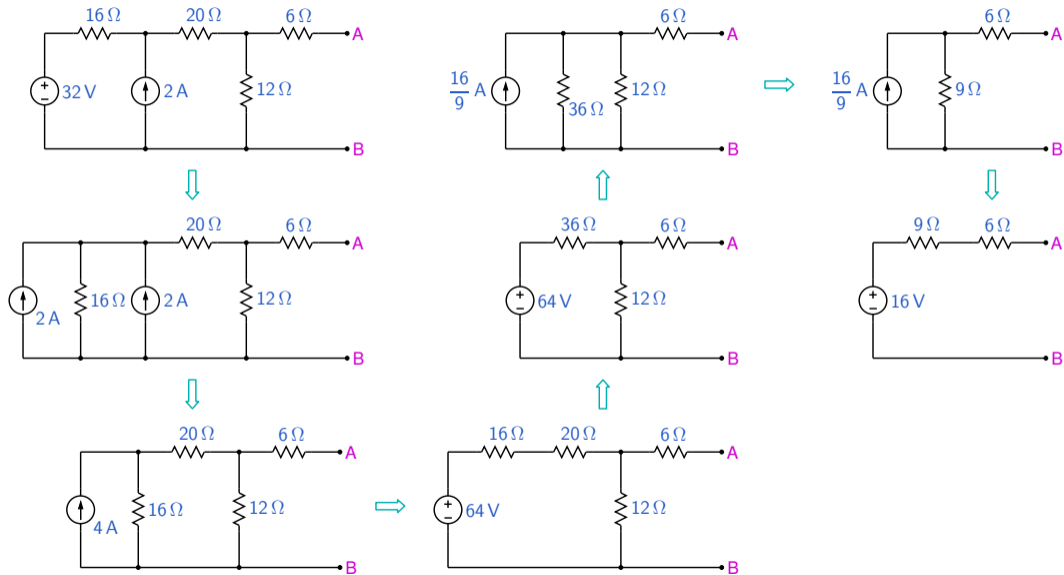





# Source transformation: example

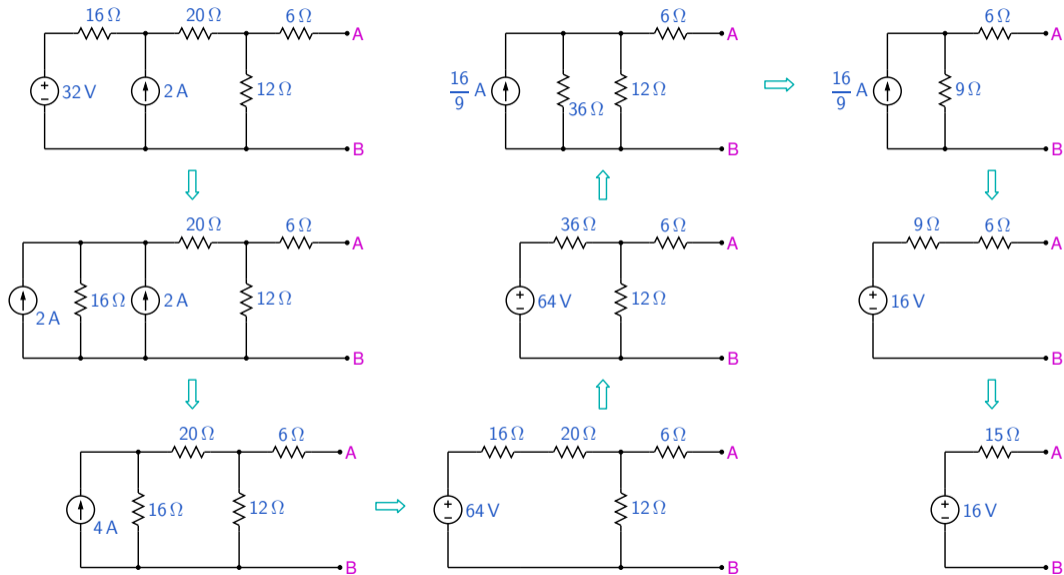

# Maximum power transfer

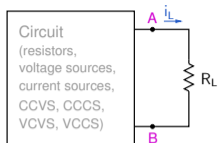


## Maximum power transfer

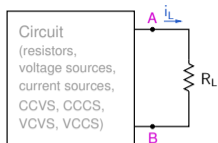


\* Power "transferred" to load is,  $P_L = i_L^2 R_L$ .

## Maximum power transfer

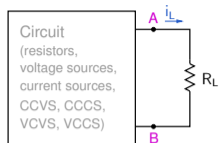



- \* Power "transferred" to load is,  $P_L = i_L^2 R_L$ .
- \* For a given black box, what is the value of  $R_L$  for which  $P_L$  is maximum?

## Maximum power transfer

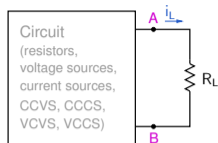



- \* Power "transferred" to load is,  $P_L = i_L^2 R_L$ .
- \* For a given black box, what is the value of  $R_L$  for which  $P_L$  is maximum?
- \* Replace the black box with its Thevenin equivalent.

# Maximum power transfer

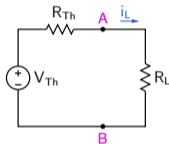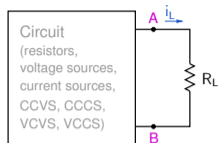


- \* Power "transferred" to load is,  $P_L = i_L^2 R_L$ .
- \* For a given black box, what is the value of  $R_L$  for which  $P_L$  is maximum?
- \* Replace the black box with its Thevenin equivalent.

# Maximum power transfer

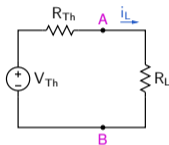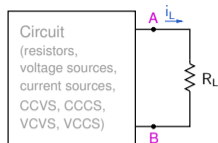

- \* Power "transferred" to load is,  $P_L = i_L^2 R_L$ .
- \* For a given black box, what is the value of  $R_L$  for which  $P_L$  is maximum?
- \* Replace the black box with its Thevenin equivalent.
- \*  $i_L = \frac{V_{Th}}{R_{Th} + R_L}$ ,  $P_L = V_{Th}^2 \times \frac{R_L}{(R_{Th} + R_L)^2}$ .

## Maximum power transfer

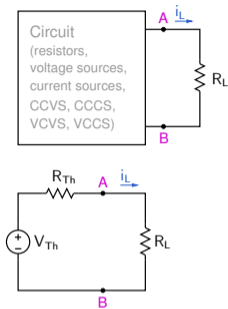

- \* Power “transferred” to load is,  $P_L = i_L^2 R_L$ .
- \* For a given black box, what is the value of  $R_L$  for which  $P_L$  is maximum?
- \* Replace the black box with its Thevenin equivalent.

$$* i_L = \frac{V_{Th}}{R_{Th} + R_L}, P_L = V_{Th}^2 \times \frac{R_L}{(R_{Th} + R_L)^2}.$$




- \* For  $\frac{dP_L}{dR_L} = 0$ , we need

$$\frac{(R_{Th} + R_L)^2 - R_L \times 2(R_{Th} + R_L)}{(R_{Th} + R_L)^4} = 0,$$

$$\text{i.e., } R_{Th} + R_L = 2R_L \Rightarrow R_L = R_{Th}.$$



# Maximum power transfer

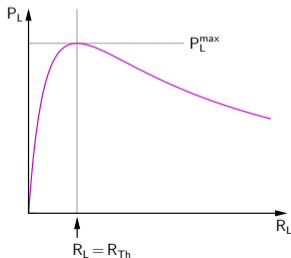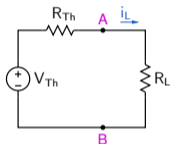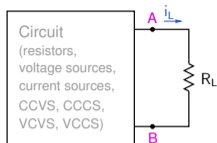

- \* Power "transferred" to load is,  $P_L = i_L^2 R_L$ .
- \* For a given black box, what is the value of  $R_L$  for which  $P_L$  is maximum?
- \* Replace the black box with its Thevenin equivalent.


$$* i_L = \frac{V_{Th}}{R_{Th} + R_L}, P_L = V_{Th}^2 \times \frac{R_L}{(R_{Th} + R_L)^2}.$$

- \* For  $\frac{dP_L}{dR_L} = 0$ , we need



$$\frac{(R_{Th} + R_L)^2 - R_L \times 2(R_{Th} + R_L)}{(R_{Th} + R_L)^4} = 0,$$

$$\text{i.e., } R_{Th} + R_L = 2R_L \Rightarrow R_L = R_{Th}.$$


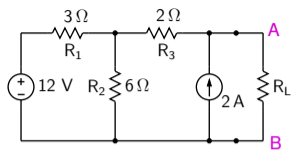
Find  $R_L$  for which  $P_L$  is maximum.



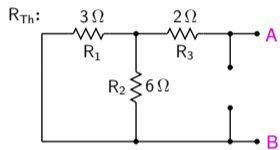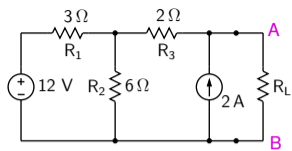Find  $R_L$  for which  $P_L$  is maximum.



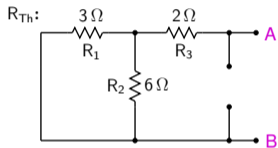
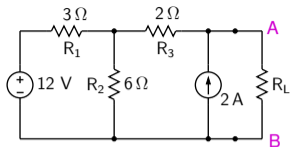
Find  $R_L$  for which  $P_L$  is maximum.



$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$


$$= 3 \times \left( \frac{1 \times 2}{1 + 2} \right) + 2 = 4\ \Omega$$

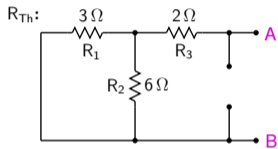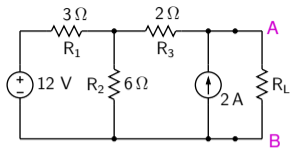Find  $R_L$  for which  $P_L$  is maximum.





$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$
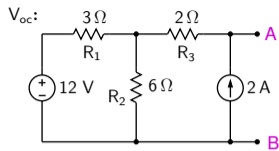
$$= 3 \times \left( \frac{1 \times 2}{1 + 2} \right) + 2 = 4 \Omega$$




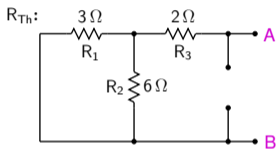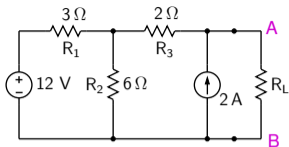Find  $R_L$  for which  $P_L$  is maximum.





$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$


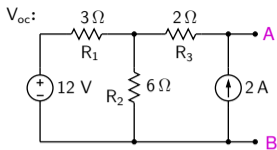
$$= 3 \times \left( \frac{1 \times 2}{1 + 2} \right) + 2 = 4 \Omega$$



Use superposition to find  $V_{oc}$ :

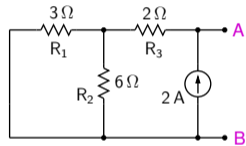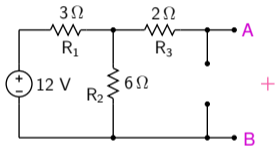


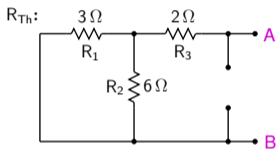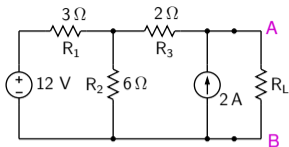Find  $R_L$  for which  $P_L$  is maximum.





$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$


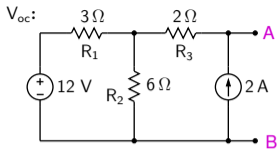
$$= 3 \times \left( \frac{1 \times 2}{1 + 2} \right) + 2 = 4 \Omega$$



Use superposition to find  $V_{oc}$ :

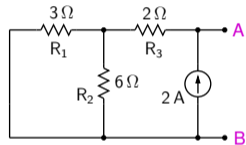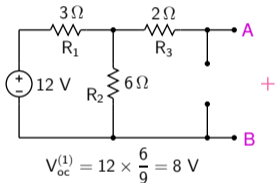


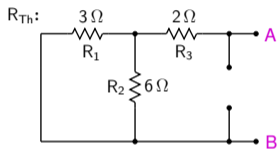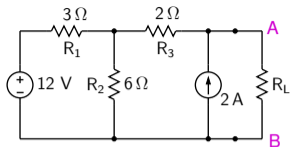Find  $R_L$  for which  $P_L$  is maximum.





$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$
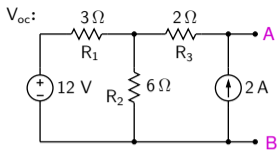
$$= 3 \times \left( \frac{1 \times 2}{1 + 2} \right) + 2 = 4 \Omega$$





Use superposition to find  $V_{oc}$ :

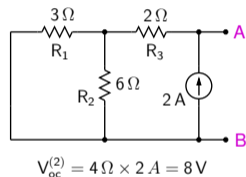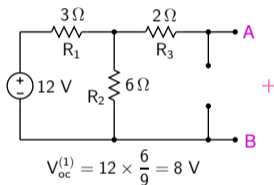




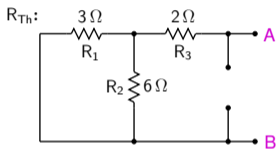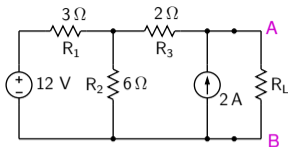Find  $R_L$  for which  $P_L$  is maximum.




$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$

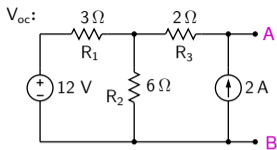
$$= 3 \times \left( \frac{1 \times 2}{1 + 2} \right) + 2 = 4 \Omega$$



Use superposition to find  $V_{oc}$ :

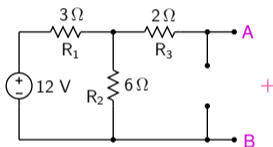


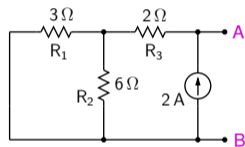
$$V_{oc}^{(1)} = 12 \times \frac{6}{9} = 8 \text{ V}$$



$$V_{oc}^{(2)} = 4 \Omega \times 2 \text{ A} = 8 \text{ V}$$



$$V_{oc} = V_{oc}^{(1)} + V_{oc}^{(2)} = 8 + 8 = 16 \text{ V}$$

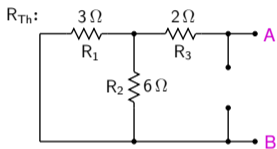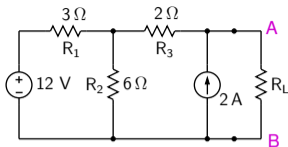Find  $R_L$  for which  $P_L$  is maximum.




$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$

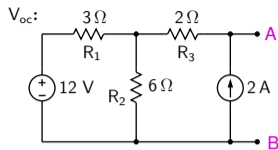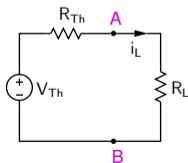
$$= 3 \times \left( \frac{1 \times 2}{1 + 2} \right) + 2 = 4 \Omega$$



Use superposition to find  $V_{oc}$ :

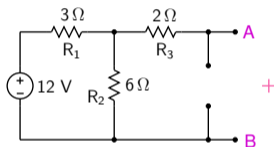
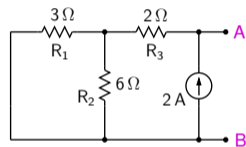
$$V_{oc}^{(1)} = 12 \times \frac{6}{9} = 8 \text{ V}$$



$$V_{oc}^{(2)} = 4 \Omega \times 2 \text{ A} = 8 \text{ V}$$

$$V_{oc} = V_{oc}^{(1)} + V_{oc}^{(2)} = 8 + 8 = 16 \text{ V}$$




$P_L$  is maximum when  $R_L = R_{Th} = 4 \Omega$

$$\Rightarrow i_L = V_{Th} / (2R_{Th}) = 2 \text{ A}$$


$$P_L^{\max} = 2^2 \times 4 = 16 \text{ W.}$$

# Maximum power transfer: simulation results

SEQUEL file: ee101\_maxpwr\_1.sqproj

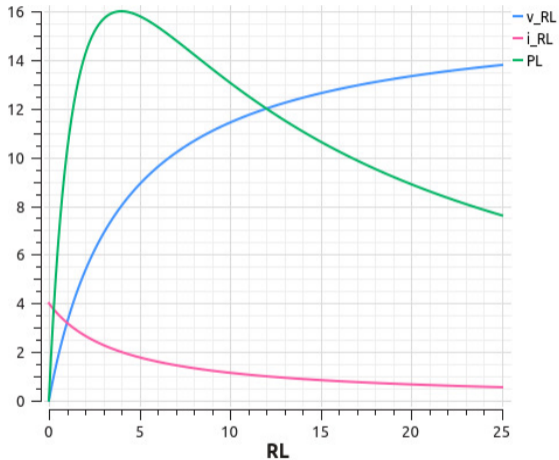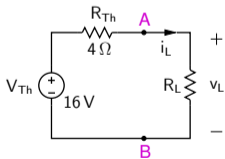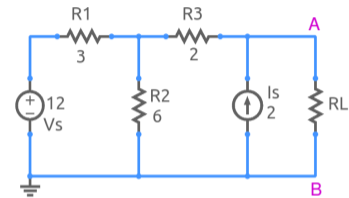

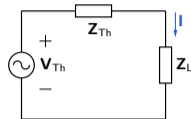
## Maximum power transfer (sinusoidal steady state)


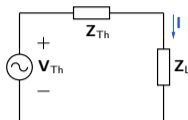
## Maximum power transfer (sinusoidal steady state)

Let  $\mathbf{Z}_L = R_L + jX_L$ ,  $\mathbf{Z}_{Th} = R_{Th} + jX_{Th}$ , and  $\mathbf{I} = I_m \angle \phi$ .




## Maximum power transfer (sinusoidal steady state)

Let  $\mathbf{Z}_L = R_L + jX_L$ ,  $\mathbf{Z}_{Th} = R_{Th} + jX_{Th}$ , and  $\mathbf{I} = I_m \angle \phi$ .

The power absorbed by  $\mathbf{Z}_L$  is,

$$\begin{aligned} P &= \frac{1}{2} I_m^2 R_L \\ &= \frac{1}{2} \left| \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + \mathbf{Z}_L} \right|^2 R_L \\ &= \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} R_L. \end{aligned}$$

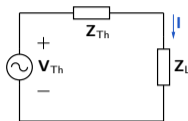


## Maximum power transfer (sinusoidal steady state)

Let  $\mathbf{Z}_L = R_L + jX_L$ ,  $\mathbf{Z}_{Th} = R_{Th} + jX_{Th}$ , and  $\mathbf{I} = I_m \angle \phi$ .

The power absorbed by  $\mathbf{Z}_L$  is,

$$\begin{aligned} P &= \frac{1}{2} I_m^2 R_L \\ &= \frac{1}{2} \left| \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + \mathbf{Z}_L} \right|^2 R_L \\ &= \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} R_L. \end{aligned}$$

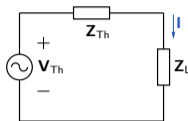For  $P$  to be maximum,  $(X_{Th} + X_L)$  must be zero.  $\Rightarrow X_L = -X_{Th}$ .



## Maximum power transfer (sinusoidal steady state)

Let  $\mathbf{Z}_L = R_L + jX_L$ ,  $\mathbf{Z}_{Th} = R_{Th} + jX_{Th}$ , and  $\mathbf{I} = I_m \angle \phi$ .

The power absorbed by  $\mathbf{Z}_L$  is,


$$\begin{aligned} P &= \frac{1}{2} I_m^2 R_L \\ &= \frac{1}{2} \left| \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + \mathbf{Z}_L} \right|^2 R_L \\ &= \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} R_L. \end{aligned}$$

For  $P$  to be maximum,  $(X_{Th} + X_L)$  must be zero.  $\Rightarrow X_L = -X_{Th}$ .

With  $X_L = -X_{Th}$ , we have,

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2}{(R_{Th} + R_L)^2} R_L,$$

which is maximum for  $R_L = R_{Th}$ .

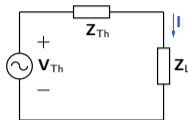



## Maximum power transfer (sinusoidal steady state)

Let  $\mathbf{Z}_L = R_L + jX_L$ ,  $\mathbf{Z}_{Th} = R_{Th} + jX_{Th}$ , and  $\mathbf{I} = I_m \angle \phi$ .

The power absorbed by  $\mathbf{Z}_L$  is,

$$\begin{aligned} P &= \frac{1}{2} I_m^2 R_L \\ &= \frac{1}{2} \left| \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + \mathbf{Z}_L} \right|^2 R_L \\ &= \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} R_L. \end{aligned}$$

For  $P$  to be maximum,  $(X_{Th} + X_L)$  must be zero.  $\Rightarrow X_L = -X_{Th}$ .


With  $X_L = -X_{Th}$ , we have,

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2}{(R_{Th} + R_L)^2} R_L,$$


which is maximum for  $R_L = R_{Th}$ .

Therefore, for maximum power transfer to the load  $\mathbf{Z}_L$ , we need,


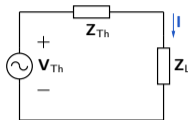
$$R_L = R_{Th}, X_L = -X_{Th}, \text{ i.e., } \boxed{\mathbf{Z}_L = \mathbf{Z}_{Th}^*}$$





# Impedance matching

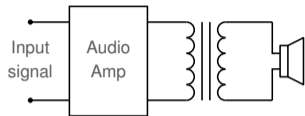



# Impedance matching

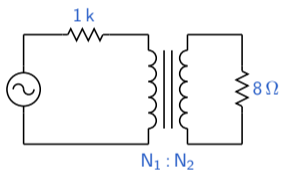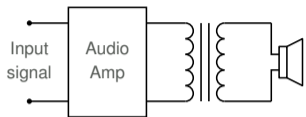



# Impedance matching

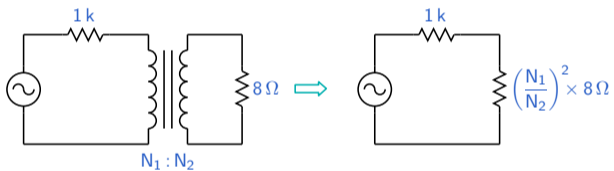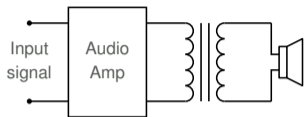

# Impedance matching

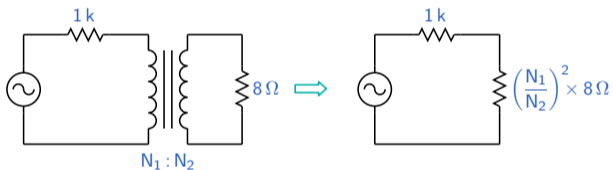
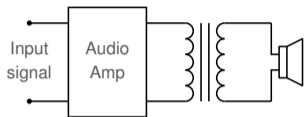


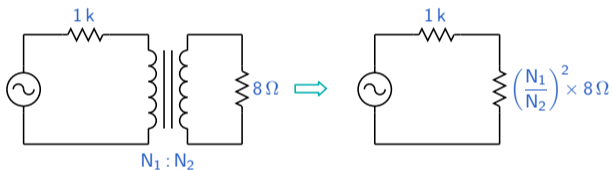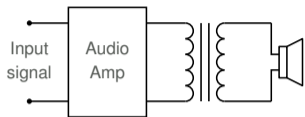Calculate the turns ratio to provide maximum power transfer of the audio signal.





Calculate the turns ratio to provide maximum power transfer of the audio signal.

$$Z_L = Z_{Th}^*$$

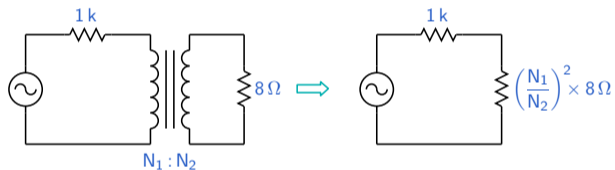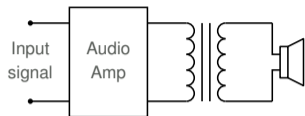

Calculate the turns ratio to provide maximum power transfer of the audio signal.
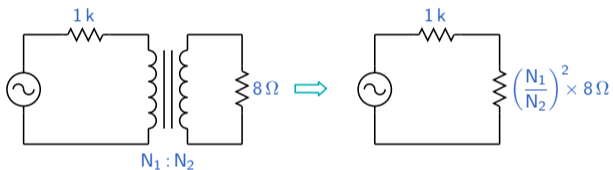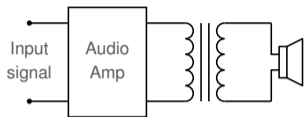
$$Z_L = Z_{Th}^* \rightarrow \left(\frac{N_1}{N_2}\right)^2 \times 8 \Omega = 1 \text{ k}\Omega$$



Calculate the turns ratio to provide maximum power transfer of the audio signal.

$$Z_L = Z_{Th}^* \rightarrow \left(\frac{N_1}{N_2}\right)^2 \times 8\Omega = 1\text{ k}\Omega \rightarrow \frac{N_1}{N_2} = \sqrt{\frac{1000}{8}} = 11.2$$