

## Op Amp Circuits

### Schmitt Trigger, Monostable, and Astable Circuits

#### Positive and negative feedback

The inverting amplifier circuit is shown in Fig. 1 (a). Let us show qualitatively that the

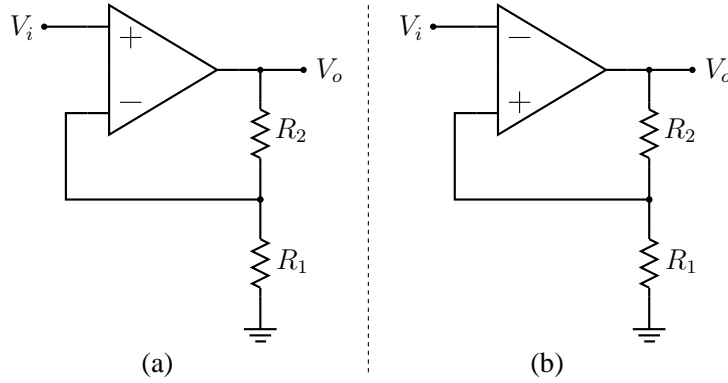


Figure 1: (a) Inverting amplifier, (b) Schmitt trigger.

feedback in this circuit is *negative*. Consider an increase in the output voltage  $V_o$ . This causes an increase in  $V_- = \frac{R_1}{R_1 + R_2} V_o$ . Since the op amp output is  $V_o = A_V (V_s - V_-)$ , an increase in  $V_-$  causes  $V_o$  to decrease. We see that there is a balancing process here: an increase in  $V_o$  has resulted in a decrease in  $V_o$ . The circuit is therefore stable, with the op amp operating in the linear region<sup>1</sup>.

Consider now the circuit in Fig. 1 (b), which is identical to the inverting amplifier except that the inverting and non-inverting inputs of the op amp have been interchanged. Imagine once again  $V_o$  to have increased. Consequently,  $V_+ = \frac{R_1}{R_1 + R_2} V_o$  also increases, and  $V_o = A_V (V_+ - V_s)$  increases further. The feedback process is now *positive*, making the circuit unstable. In practice, the op amp output cannot increase or decrease indefinitely and saturates at  $+V_{\text{sat}}$  or  $-V_{\text{sat}}$ .

Is such an unstable circuit of any use at all? It surely is, as we will see in this experiment.

#### $V_o$ versus $V_i$ relationship

When  $V_s$  is sufficiently large, the output voltage  $V_o$  of the circuit of Fig. 1 (b) (known as the ‘‘Schmitt trigger’’) is  $-V_{\text{sat}}$  as shown in Fig. 2. The voltage at the non-inverting input terminal of the op amp  $V_+$  (with respect to ground) is then  $V_+ \equiv V_{TL} = -V_{\text{sat}} \frac{R_1}{R_1 + R_2}$ . As  $V_i$  is reduced and becomes smaller than  $V_{TL}$ , the op amp output changes from  $-V_{\text{sat}}$  to  $+V_{\text{sat}}$  (since  $V_- < V_+$ ), as shown in Fig. 2. Now,  $V_+$  is equal to  $V_+ \equiv V_{TH} = +V_{\text{sat}} \frac{R_1}{R_1 + R_2}$ . If  $V_i$  is reduced further, this state of affairs continues to hold. If  $V_i$  is increased, the output flips when  $V_i$  crosses  $V_{TH}$ .

<sup>1</sup>We will assume that the input voltage or the gain  $R_2/R_1$  is small enough so that the op amp does not enter saturation.

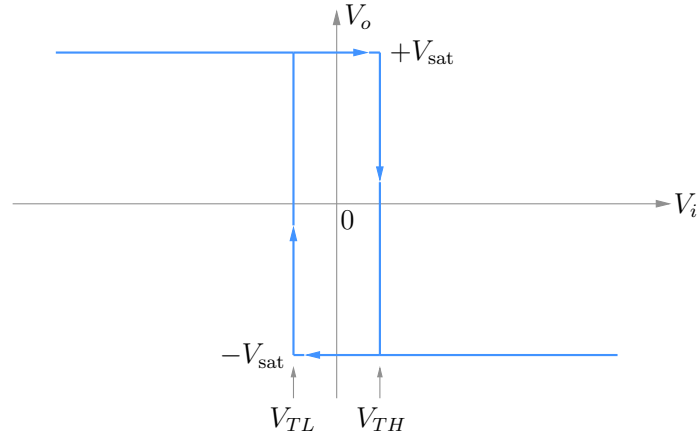


Figure 2:  $V_o$  versus  $V_i$  relationship for the Schmitt trigger of Fig. 1 (b).

We can see that the Schmitt trigger is a comparator with hysteresis (or “memory”). Since the input threshold voltage ( $V_{TH}$  or  $V_{TL}$ ), at which the output flips, depends on the “state” of the circuit.

Note that the high and low threshold voltages,  $V_{TH}$  and  $V_{TL}$ , respectively, are symmetric about 0 V for the Schmitt trigger circuit of Fig. 1 (b), i.e.,  $V_{TH} = -V_{TL}$ . By connecting a DC voltage source  $V_a$ , we can make them asymmetric (see Fig. 3), as shown below.

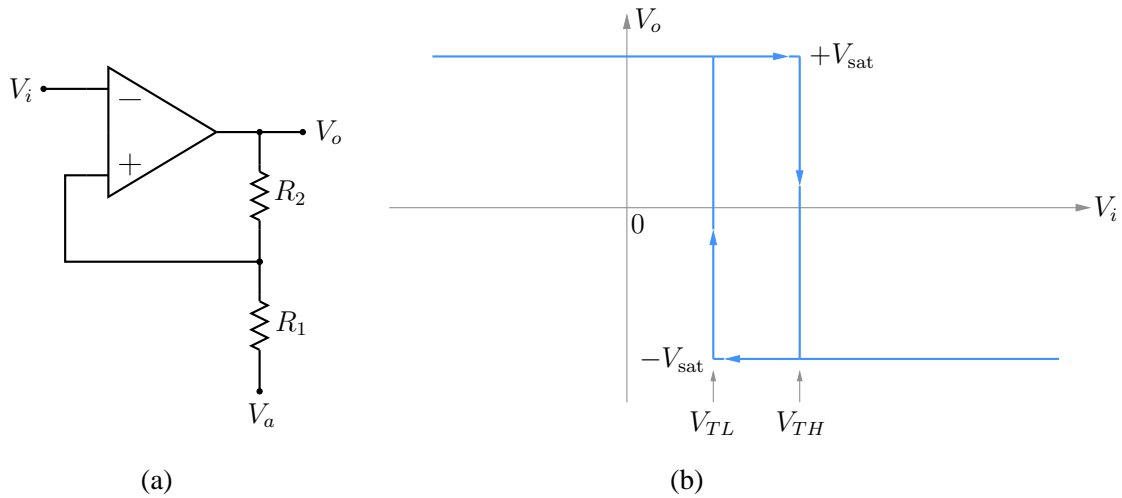


Figure 3: (a) Schmitt trigger circuit with asymmetric threshold voltages, (b)  $V_o$  versus  $V_i$  relationship. Note that  $\frac{V_{TH} + V_{TL}}{2} = V_a \frac{R_2}{R_1 + R_2}$ .

When  $V_o$  is  $+V_{sat}$ , we have

$$V_+ = +V_{sat} \frac{R_1}{R_1 + R_2} + V_a \frac{R_2}{R_1 + R_2} \quad (1)$$

since the current entering the non-inverting input of the op amp can be neglected. Similarly,

when  $V_o$  is  $-V_{\text{sat}}$ , we have

$$V_+ = -V_{\text{sat}} \frac{R_1}{R_1 + R_2} + V_a \frac{R_2}{R_1 + R_2}. \quad (2)$$

As an example, let  $V_{\text{sat}} = 12 \text{ V}$ ,  $V_a = 2 \text{ V}$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 9 \text{ k}\Omega$ , then the threshold voltages can be calculated using Eqs. 1 and 2 as  $V_{TH} = 3 \text{ V}$  and  $V_{TL} = 0.4 \text{ V}$ .

The output voltage of the Schmitt trigger can be limited by using a Zener pair as shown in Fig. 4. Let the breakdown voltage of the Zener diode be  $V_Z = 4.3 \text{ V}$  and the turn-on voltage be  $V_{\text{on}} = 0.7 \text{ V}$ . Consider the op amp output  $V_{o1}$  to be  $+V_{\text{sat}}$ , say,  $+12 \text{ V}$ . Because of the diode pair,

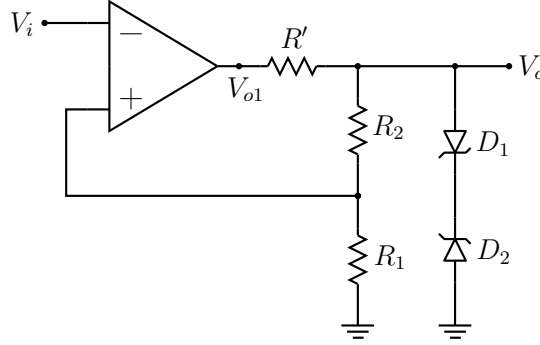


Figure 4: Schmitt trigger circuit with  $V_o$  limited to  $\pm(V_Z + V_{\text{on}})$ .

the output voltage  $V_o$  gets limited to  $V_{\text{on}} + V_Z = 5 \text{ V}$ , with  $D_1$  in forward conduction, and  $D_2$  in reverse breakdown. Note that the difference between  $V_{o1}$  and  $V_o$  appears across the resistor  $R'$  which must be chosen to limit the op amp output current to a reasonable value (a few mAs). Connecting the diode pair directly to the op amp output would lead to unhealthy events.

In a similar manner, when  $V_{o1}$  is  $-V_{\text{sat}}$  ( $-12 \text{ V}$ ), the output voltage  $V_o$  gets limited to  $-(V_{\text{on}} + V_Z) = -5 \text{ V}$ , with  $D_2$  in forward conduction, and  $D_1$  in reverse breakdown.

### Astable multivibrator

The astable multivibrator (see Fig. 5 (a)) is an oscillator which produces a square wave output voltage. Its frequency can be controlled by changing the  $R$  and  $C$  values. To understand the operation of this circuit, let us assume that  $V_C = 0 \text{ V}$  and  $V_o = V_m$  at  $t = 0$  (i.e., we are at  $(0, V_m)$  in the  $V_C$ - $V_o$  plane of Fig. 5 (c)). Since the op amp input resistance is very large, we have a simple situation of a capacitor charging to  $+V_m$  with a time constant  $\tau = RC$ , i.e.,  $V_C(t) = V_m (1 - e^{-t/RC})$ , as shown in Fig. 6 (a). However, when  $V_C$  crosses  $V_{TH}$  (see Fig. 5 (c)),  $V_o$  changes to  $-V_m$ , and now the capacitor starts discharging toward  $-V_m$  (again, with the same time constant  $\tau = RC$ ). When  $V_C$  crosses  $V_{TL}$ , the output flips to  $+V_m$ , and this process continues, resulting in a square wave output.

To calculate the frequency of oscillation, let  $V_C(0) = V_{TL}$ , as shown in Fig. 6 (b). The capacitor voltage in the interval  $0 < t < t_1$  is given by

$$V_C(t) = A e^{-t/\tau} + B, \quad (3)$$

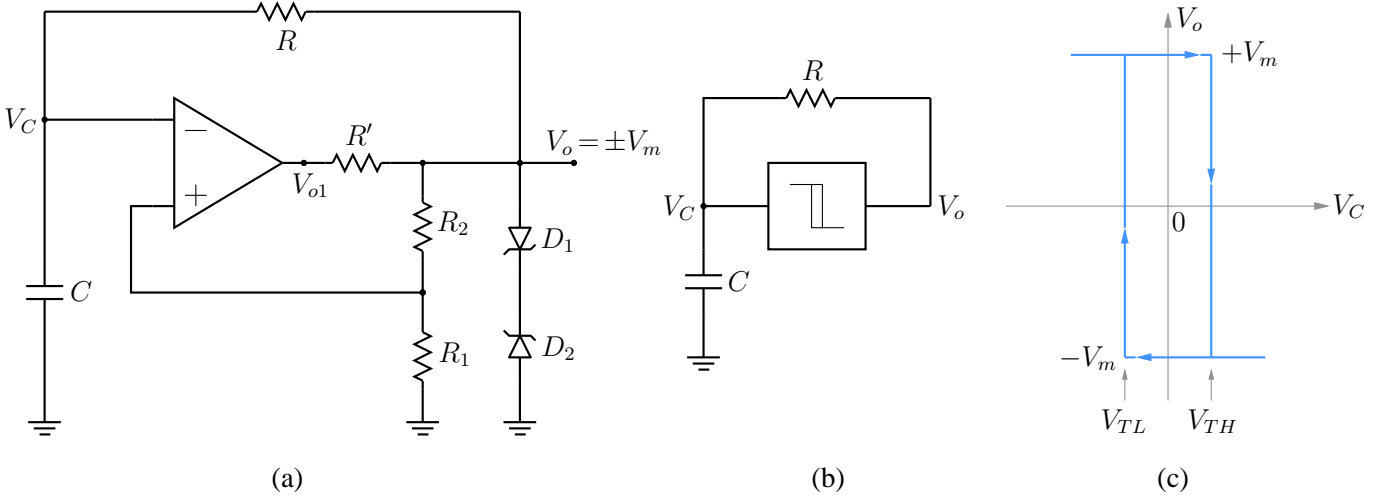


Figure 5: (a) Astable multivibrator circuit, (b) simplified diagram, (c)  $V_o$  versus  $V_C$  relationship.

where  $A + B = V_{TL}$  (since  $V_C(0) = V_{TL}$ ), and  $B = V_m$  (since the capacitor is charging toward  $V_m$ ), giving

$$V_C(t) = (V_{TL} - V_m) e^{-t/\tau} + V_m \quad \text{for } 0 < t < t_1. \quad (4)$$

At  $t = t_1$ , we have  $V_C = V_{TH}$ , i.e.,

$$V_{TH} = (V_{TL} - V_m) e^{-t_1/\tau} + V_m \rightarrow t_1 = \tau \log \left( \frac{V_m - V_{TL}}{V_m - V_{TH}} \right). \quad (5)$$

In the interval  $t_1 < t < T$ , the capacitor discharges toward  $-V_m$ , and we can write

$$V_C(t) = A' e^{-(t-t_1)/\tau} + B', \quad (6)$$

where  $A' + B' = V_C(t_1) = V_{TH}$ , and  $B' = V_C(\infty) = -V_m$ . We now get

$$V_C(t) = (V_{TH} + V_m) e^{-(t-t_1)/\tau} - V_m \quad \text{for } t_1 < t < T. \quad (7)$$

Since  $V_C(T) = V_{TL}$ , we can find  $(T - t_1)$  as

$$V_{TL} = (V_{TH} + V_m) e^{-(T-t_1)/\tau} - V_m \rightarrow (T - t_1) = \tau \log \left( \frac{V_m + V_{TH}}{V_m + V_{TL}} \right). \quad (8)$$

If  $V_{TH} = -V_{TL} \equiv V_T$ , the intervals  $t_1$  and  $(T - t_1)$  are equal, and we get

$$t_1 = T - t_1 \equiv \frac{T}{2} = \tau \log \left( \frac{V_m + V_T}{V_m - V_T} \right), \quad (9)$$

and the period of oscillation is

$$T = 2\tau \log \left( \frac{V_m + V_T}{V_m - V_T} \right). \quad (10)$$

Those who prefer dimensionless elegance can write  $T$  as

$$T = 2\tau \log \left( \frac{1 + \beta}{1 - \beta} \right), \quad \text{with } \beta = \frac{V_T}{V_m}. \quad (11)$$

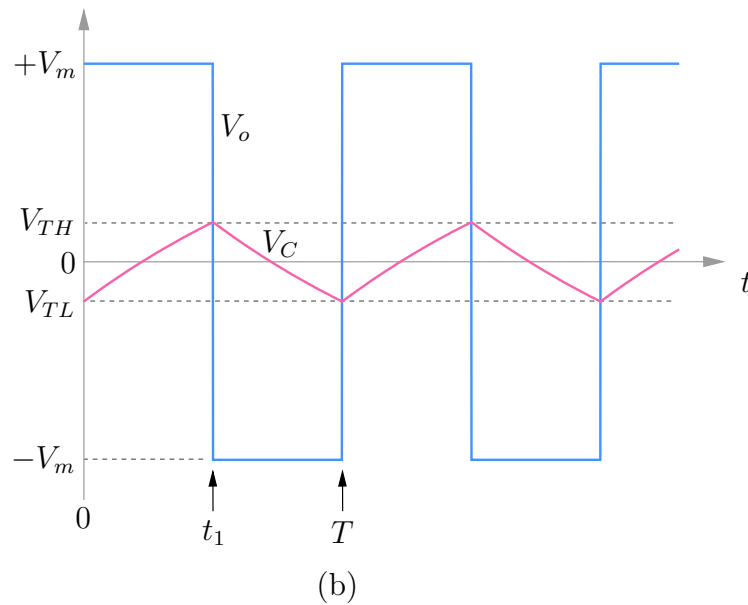
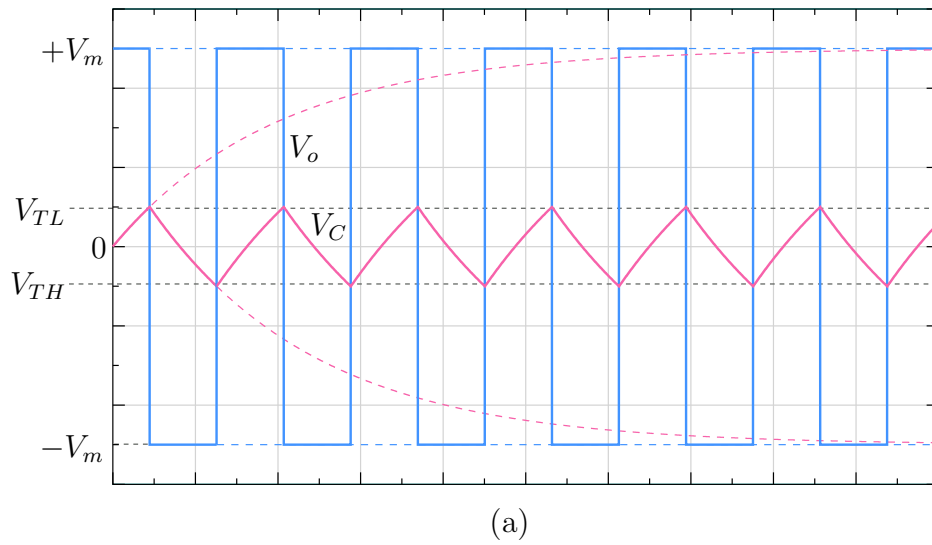


Figure 6: Waveforms for the astable multivibrator: (a) waveforms starting from  $V_C(0) = 0\text{ V}$ , (b) waveforms in the steady state.

### Monostable multivibrator

A monostable multivibrator has a “stable” state (say,  $V_o = 0\text{ V}$ ) and a “transient” state (say,  $V_o = V_{\text{high}}$ ). Consider the circuit to be in the stable state (see Fig. 7) in the beginning. When a certain “event” occurs, it enters the transient state, remains in that state for a time interval  $T$ , and then returns to its stable state.

Fig. 8 (a) shows an implementation of the monostable multivibrator circuit using the Schmitt trigger of Fig. 4. Assume that the circuit is in the stable state in the beginning, viz., the push button is in the released state, the capacitor has charged to  $+V' - (-V') = 2V'$ , the input voltage  $V_-$  for the Schmitt trigger (with respect to ground) is  $V_o = -V_m$  (with  $V_m = V_Z + V_{\text{on}}$ ),

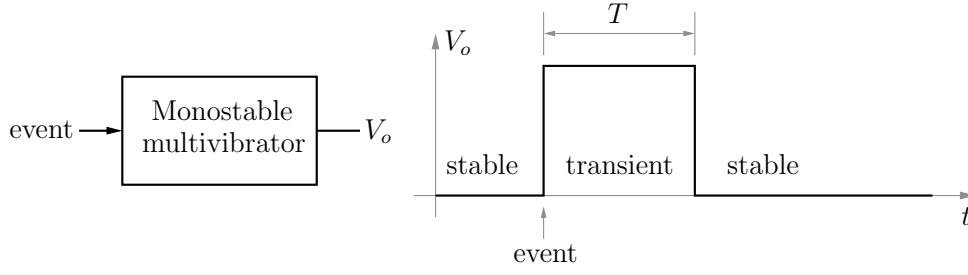


Figure 7: Operation of a monoastable multivibrator.

and  $V_+ = -V_m \frac{R_1}{R_1 + R_2}$  (see Figs. 8(c) and 8(d)). At  $t = t_1$ , the push button is closed and released<sup>2</sup>. Closing the button discharges the capacitor,  $V_C$  becomes 0V,  $V_-$  changes to  $-V'$ , and the output  $V_o$  to  $+V_m$ . When the push button is released, the capacitor starts charging. Since the input current of the op amp is negligibly small, the charging process can be described by

$$V_-(t) = A e^{-(t-t_1)/\tau} + B, \quad \text{for } t > t_1, \quad (12)$$

where  $\tau = RC$ . Using  $V_-(t_1) = -V'$  and  $V(\infty) = +V'$ , we get  $A = -2V'$ ,  $B = V'$ , i.e.,

$$V_-(t) = V' (1 - 2e^{-(t-t_1)/\tau}). \quad (13)$$

When  $V_-$  crosses  $V_{TH}$ , the output changes to  $+V_m$  (at  $t = t_1 + T$  in Fig. 8(c)). The capacitor continues to charge, and in about five time constants, we have once again the original stable state that we started with at  $t = 0$ .

To calculate  $T$ , we simply substitute  $V_-(t_1 + T) = V_{TH}$  in Eq. 13 and obtain

$$V_{TH} = V' (1 - 2e^{-T/\tau}) \quad \rightarrow \quad T = RC \times \log \left( \frac{2V'}{V' - V_{TH}} \right). \quad (14)$$

---

<sup>2</sup>We will assume that the time taken for pushing and releasing the button is much smaller than the time constant  $RC$ .

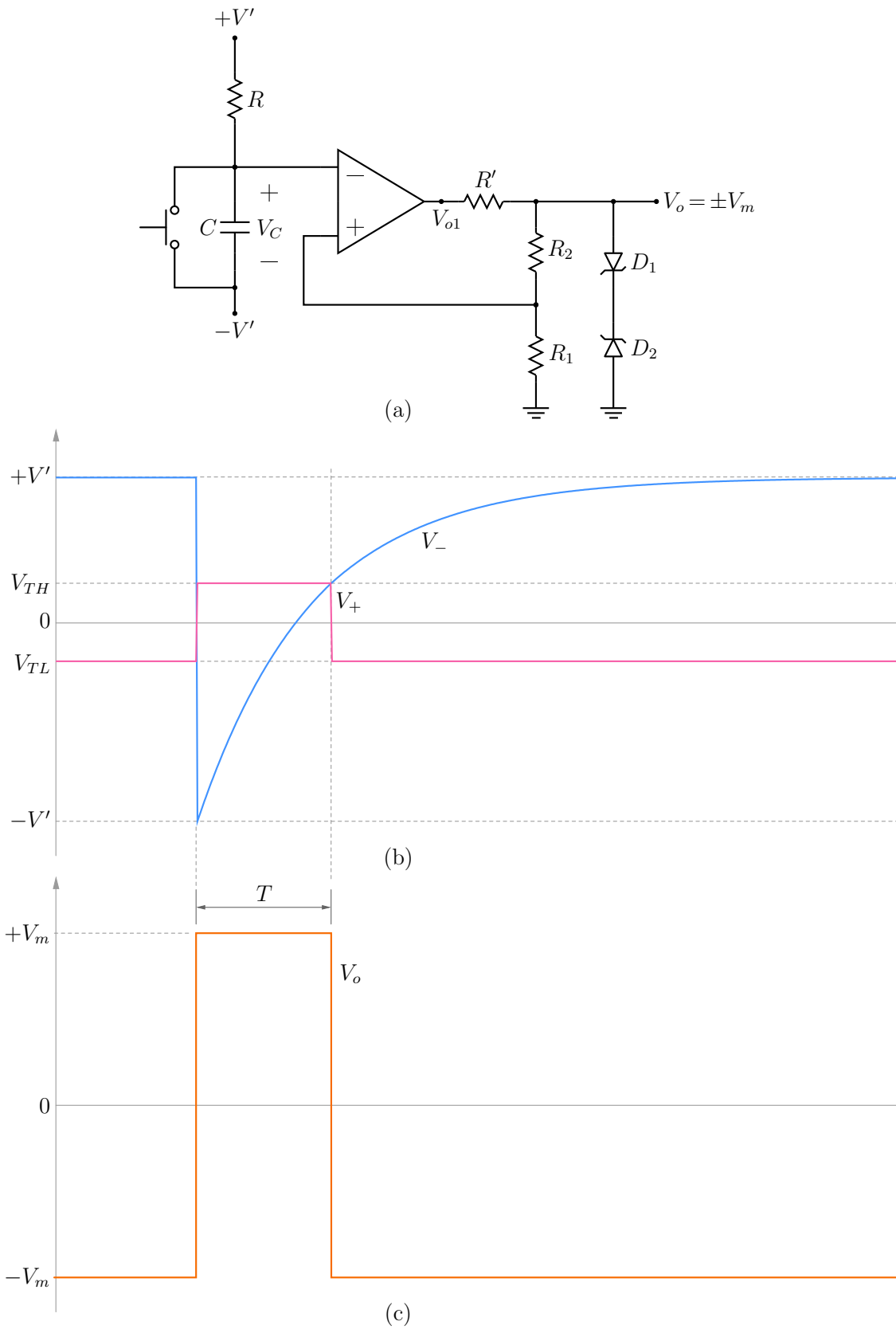


Figure 8: (a) Monoastable multivibrator circuit using a Schmitt trigger, (b)  $V_+$  and  $V_-$  waveforms, (c)  $V_o$  waveform.