

# bass\_equalizer.sqproj

## Description

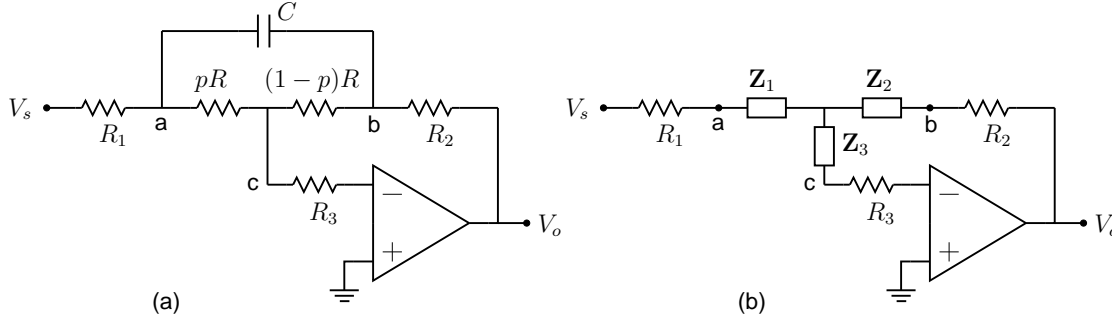


Figure 1: (a) Circuit schematic for bass equalizer, (b) simplified circuit.

The bass equalizer shown in Fig. 1 (a) can be simplified using  $\Delta \rightarrow Y$  transformation (see Fig. 1 (b)). The gain is then obtained as (show this),

$$\frac{V_o(s)}{V_i(s)} = -\frac{R_2 + Z_2}{R_1 + Z_1} \quad (1)$$

$$= -\frac{R_2}{R_1} \left\{ \frac{\left[ 1 + (1-p)\frac{R}{R_2} \right] + sRC}{\left[ 1 + p\frac{R}{R_1} \right] + sRC} \right\}. \quad (2)$$

The above transfer function has one zero and one pole. By changing the value of  $p$  (which is  $< 1$ ) with a pot, we can obtain  $|z| > |p|$  or  $|z| < |p|$ . This circuit is used to boost or cut low frequencies in an audio amplifier.

## Exercise Set

1. Derive the transfer function given in the above equation.
2. Simulate the circuit with  $R_1 = R_2 = R_3 = 11 \text{ k}$ ,  $R = 100 \text{ k}$ , and  $C = 22 \text{ nF}$ , for various values of  $p$  (between 0 and 1). Plot  $\log |V_o|$  versus  $\log f$  for the different  $p$  values on the same plot so that the effect of changing  $p$  can be clearly observed.
3. What is  $|H(j\omega)|$  for  $\omega \rightarrow 0$  for (a)  $p \approx 0$ , (b)  $p \approx 1$ ? Verify your answers with simulation results.

## References:

1. J. M. Fiore, *Op amps and linear integrated circuits*, Delmar, 2001.