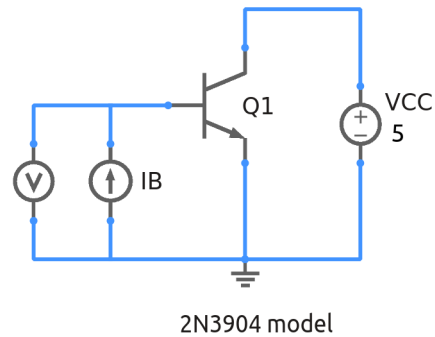


bjt_beta_ic.sqproj



In a BJT, the current gain β varies as a function of the bias collector current I_C although we often ignore this dependence in circuit analysis. The purpose of this example is to illustrate this relationship.

Exercise Set

1. Run the simulation. Plot I_C and I_B (both on log scale) versus V_{BE} . The difference between the two curves (at a given V_{BE}) gives $\log \beta$.
2. Plot the output variable `ic_by_ib` (which is equal to β versus I_C (both on log scale). What is the approximate value of β for this transistor for I_C in the range 10 mA to 100 mA?

References

1. B.G. Streetman and S.K. Banerjee, *Solid State Electronic Devices*, Pearson Education, 2006.
2. N. Dasgupta and A. Dasgupta, *Semiconductor Devices Modelling and Technology*, Prentice-Hall of India, 2004.