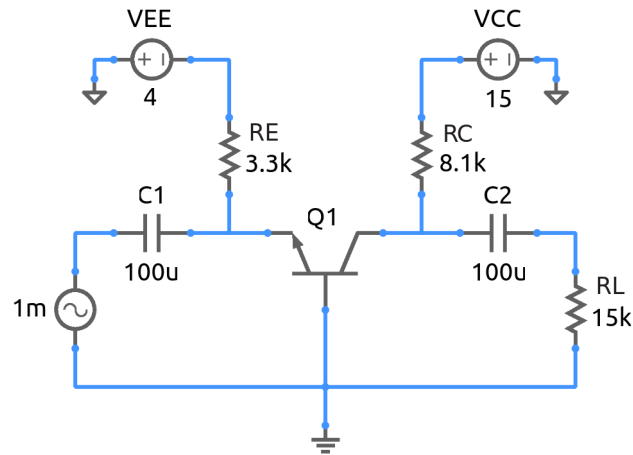


## bjt\_cb\_amp.sqproj



Shown in the figure is a common-base amplifier. We are interested in computing the mid-band gain of the amplifier. Assume that the BJT is working in the active mode.

### Exercise Set

1. What is the emitter bias voltage  $V_E$ ?
2. Using the above value of  $V_E$ , calculate the DC current through  $R_E$ . This current is the same as  $I_E$  since the coupling capacitor  $C_1$  blocks DC current.
3. Assuming  $\beta$  to be large,  $I_C \approx I_E$ . Using the bias currents obtained, find  $V_{CB}$  and  $V_{CE}$ , and make sure that the BJT is indeed operating in the active region.
4. Calculate the small-signal parameters  $r_\pi$ ,  $g_m$ ,  $r_e$ .
5. Draw the small-signal equivalent circuit of the amplifier using the  $T$  model for the BJT, and estimate the gain  $v_o/v_s$ .
6. Run the simulation, and compare your estimated gain with simulation results (of the first solve block). Note that the frequency has been specified to be in the mid-band region. This will become clear after you plot the frequency response of the amplifier.
7. What is the input resistance of this amplifier (as seen from  $v_s$ )? Is it desirable?

8. Using simulation results, plot the gain magnitude versus frequency (log-log plot). See how the frequency response changes if  $C_1$  or  $C_2$  is changed.

## References

1. J. Millman and A. Grabel, *Microelectronics*, McGraw-Hill, 1988.
2. A. S. Sedra, K. C. Smith, and A. .N. Chandorkar, *Microelectronic Circuits*, Oxford University Press, 2004.