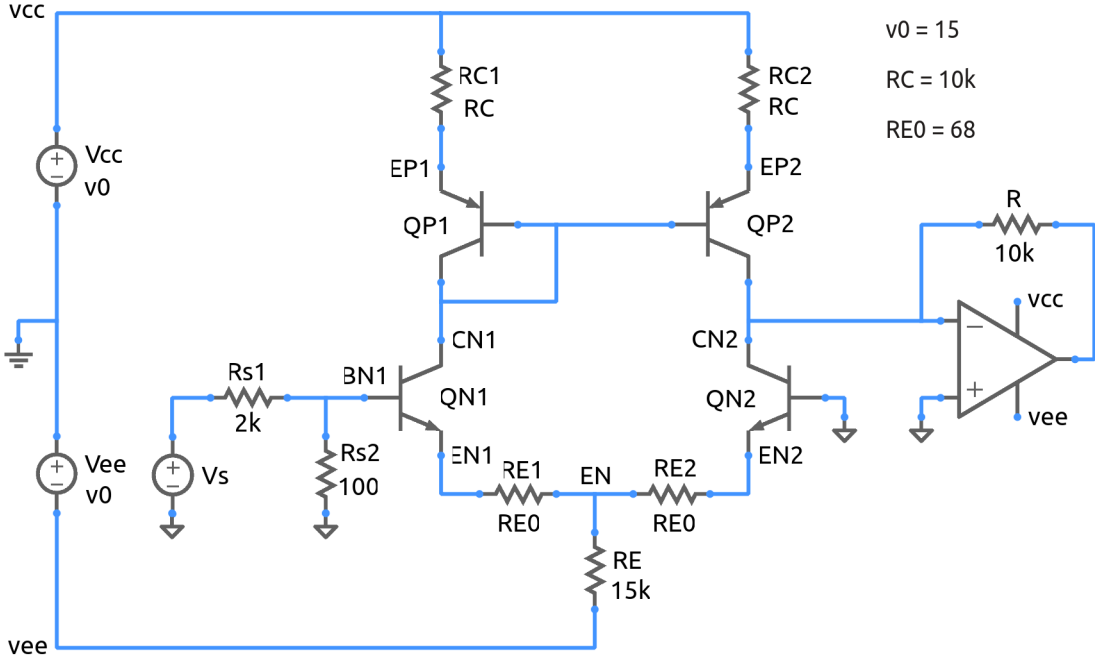


bjt\_tri\_to\_sin.sqproj



(S. Franco, Design with Op Amps and Analog ICs)

Figure 1: BJT circuit to convert triangular wave to sine wave.

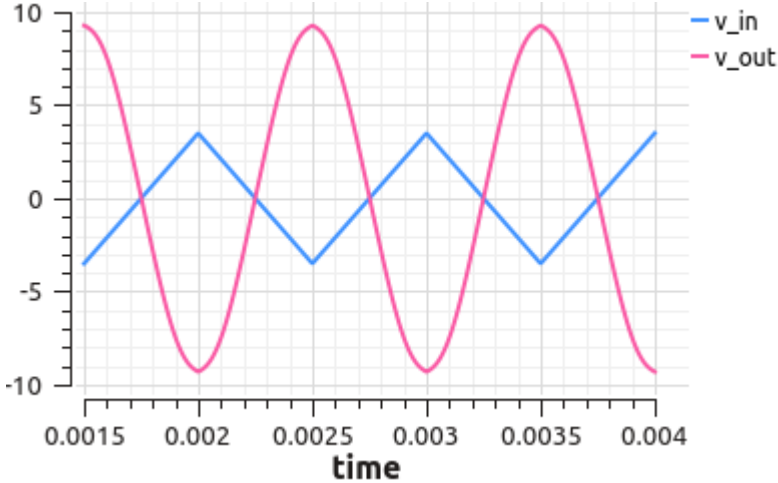


Figure 2:  $V_i$  and  $V_o$  versus time for the circuit of Fig. 1.

Shown in Fig. 1 is a wave shaper circuit which converts a triangular wave to a sine wave. In this circuit, the nonlinear nature of a BJT  $I_C-V_{BE}$  curve is used. If the input voltage is small

in magnitude, the circuit works as an amplifier. If the input is large, the output tends to saturate gradually, and this feature helps in converting a triangular wave to a sine wave. Note that the BJT part of the circuit is a voltage-to-current (transconductance) amplifier, the output of the amplifier being the current entering the Op Amp circuit at node  $CN2$ . One of the input voltages  $V_{in}^2$  (the base of  $Q_{N2}$ ) of the transconductance amplifier is held constant at 0 V. When the other input  $V_{in}^1$  (i.e., the base of  $Q_{N1}$ ) is also 0 V,  $Q_{N1}$  and  $Q_{N2}$  carry the same current (say,  $I_0$ ). The current through  $Q_{P1}$  is also  $I_0$  since it is in series with  $Q_{N1}$ . Because of the mirror action of the  $Q_{P1}$ - $Q_{P2}$  pair, the current through  $Q_{P2}$  is  $I_0$  as well. No current flows through the Op Amp circuit, and the output voltage is 0 V.

Consider now the case that  $V_{in}^1 = v_1$ , where  $v_1$  is a positive voltage. The current through  $Q_{N1}$  (and therefore the current through  $Q_{P1}$ ) increases to  $I_0 + i_1$ , and that through  $Q_{N2}$  decreases to  $I_0 - i_1$ . Because of the mirror action of the  $Q_{P1}$ - $Q_{P2}$  pair, the current through  $Q_{P2}$  also increases to  $I_0 + i_1$ . Applying KCL at node  $CN2$ , we find that the current going into the Op Amp circuit is  $(I_0 + i_1) - (I_0 - i_1) = 2i_1$ , producing an output voltage  $V_{out} = -2i_1R$ . The key feature of this circuit is that  $i_1$  is a nonlinear function of  $v_1$ , and that makes it possible to “distort” a triangular input voltage to a sinusoidal output voltage.

## Exercise Set

1. Simulate the circuit. Plot  $V_{in}$  and  $V_{out}$  versus time, and verify that the circuit functions as a triangular-to-sine converter.
2. Plot the Fourier spectrum of  $V_{in}$  and  $V_{out}$  (using the second solve block).
3. Reduce the input voltage by a factor of 10 (or equivalently, reduce  $R_{S2}$  by a factor of 10), and simulate the circuit. Plot  $V_{in}$  and  $V_{out}$  versus time. Note that the circuit is now working as an amplifier.
4. Plot the currents  $I_{Q_{N1}}$  and  $I_{RC1}$  (together) versus time. Repeat for  $I_{Q_{N2}}$  and  $I_{RC2}$ . Explain your observations.
5. Plot  $V_{out}$  versus  $V_{in}$ , and observe the nonlinear nature of the transfer curve.
6. How will you change the output voltage magnitude without changing the spectrum?

## References

1. S. Franco, *Design with Operation Amplifiers and Analog Integrated Circuits*, McGraw-Hill, 1998.