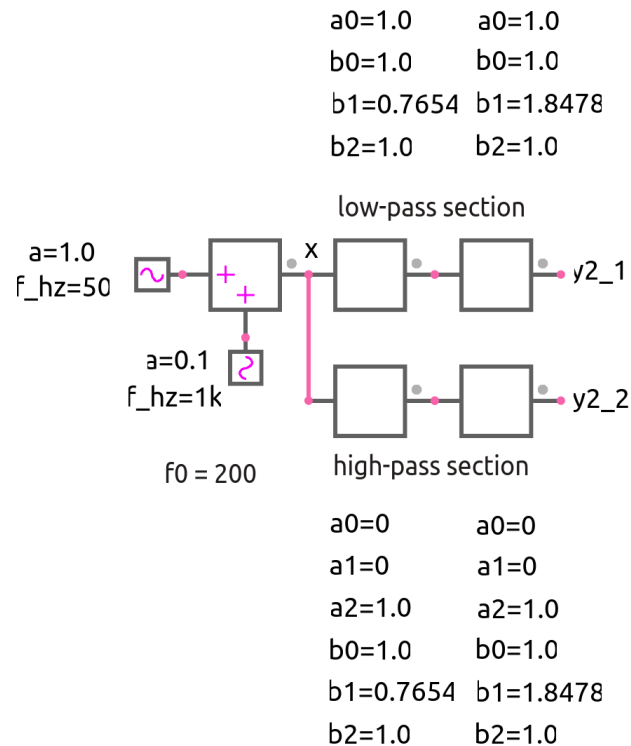


butterworth_4_trns.sqproj



Shown in the figure are 4th-order low-pass and 4th-order high-pass Butterworth filters. Note that the high-pass transfer function is obtained from the low-pass function by substituting $s \leftarrow 1/s$. The filter functions have been implemented with normalised coefficients. The actual coefficients are computed internally using the parameter f_0 of the filter elements. In this exercise, we want to understand the operation of the filters in the time domain.

(The frequency-domain behaviour of the filters is described in `butterworth_4_ac.sqproj`.)

Exercise Set

1. Run the simulation. Plot the input to the filters (x), and the outputs of the low-pass and high-pass sections (y_{2_1} and y_{2_2} , respectively) versus time. Verify the low-pass and high-pass functionality.
2. Interchange the amplitudes of x_1 and x_2 , and repeat (1).

References

1. A. S. Sedra, K. C. Smith, and A. N. Chandorkar, *Microelectronic Circuits: Theory and Applications*, Fifth edition, Oxford University Press, 2009.
2. S. Franco, *Design with Operation Amplifiers and Analog Integrated Circuits*, McGraw-Hill, 1998.