

## decade\_sync\_counter.sqproj

 


Figure 1: Circuit schematic for synchronous decade counter.

In a synchronous counter, all flip-flops receive the same clock signal. Design of a synchronous counter is based on the following state transition tables:

| $J$ | $K$ | $Q_{n+1}$        |
|-----|-----|------------------|
| 0   | 0   | $Q_n$            |
| 0   | 1   | 0                |
| 1   | 0   | 1                |
| 1   | 1   | $\overline{Q_n}$ |

Table A

| $Q_n$ | $Q_{n+1}$ | $J$ | $K$ |
|-------|-----------|-----|-----|
| 0     | 0         | 0   | X   |
| 0     | 1         | 1   | X   |
| 1     | 0         | X   | 1   |
| 1     | 1         | X   | 0   |

Table B

From the required sequence of counter states, logical functions for  $J$  and  $K$  of each flip-flop are constructed and then minimized using the Karnaugh map technique. Finally, the design is implemented with gates. Fig. 1 shows the design obtained for a decade counter with the sequence 0000, 0001,  $\dots$ , 1001, and then 0000 again.

### Exercise Set

1. Design the decade counter using the procedure above, and verify that the connections given in Fig. 1 are appropriate.
2. Starting with the initial state 0000, work out the counter sequence using Table A above, and verify (on paper) that it will count as desired. Verify with simulation.

3. Design a synchronous counter with the sequence given below.

| $Q_3$ | $Q_2$ | $Q_1$ | $Q_0$ |
|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     |
| 0     | 0     | 0     | 1     |
| 0     | 0     | 1     | 0     |
| 0     | 1     | 0     | 0     |
| 1     | 0     | 0     | 0     |
| 1     | 1     | 0     | 0     |
| 1     | 1     | 1     | 0     |
| 1     | 1     | 1     | 1     |
| 0     | 0     | 0     | 0     |

4. Simulate the counter designed in (a), and verify its operation.