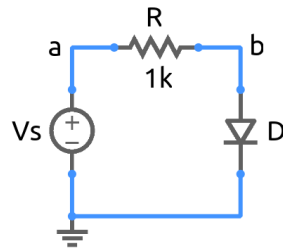


diode_iv.sqproj



The SPICE diode model is based on the Shockley diode equation [1]. The purpose of this exercise is to see how the I - V curve of a diode depends on the parameter I_s (saturation current) and the device temperature. To obtain the diode I - V curve, the input voltage in the circuit shown in the figure is varied, and the diode current is then plotted against the diode voltage.

Exercise Set

- Simulate the circuit and plot the I_D - V_D curve.
- Change I_s by a factor of 2, 5, 10, and see its effect on the I - V curve. Explain your observations.
- Simulate the circuit at $T = 300\text{ K}$, 320 K , 350 K . How does the I - V curve change? Explain the results on the basis of the Shockley equation.

References

- P. Antognetti and G. Massabrio, *Semiconductor device modeling with SPICE*, McGraw-Hill: New York, 1988.
- B.G. Streetman and S.K. Banerjee, *Solid State Electronic Devices*, Pearson Education, 2006.
- N. Dasgupta and A. Dasgupta, *Semiconductor Devices Modelling and Technology*, Prentice-Hall of India, 2004.