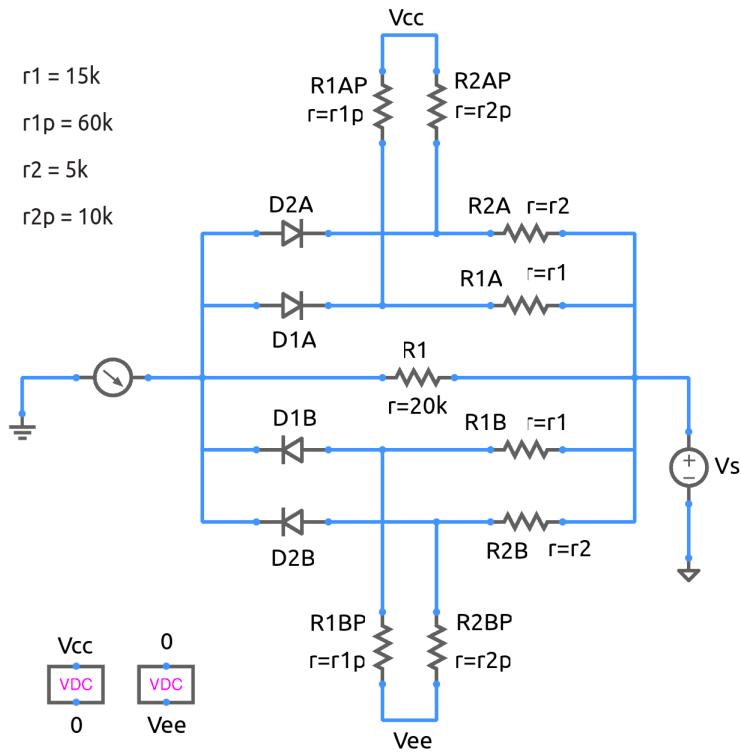


ee101_diode_circuit_10.sqproj



The diode/resistor network shown in the figure can be used (along with an Op Amp) to convert a triangular input voltage into a (nearly) sinusoidal output voltage. The purpose of this exercise is to understand the functioning of the diode/resistor network. The complete circuit, which includes an Op Amp, will be included in another simulation example (`ee101_wave_shaper.sqproj`).

Consider the applied voltage (from source V_s) to be positive. When the voltage is sufficiently small, none of the diodes conduct, and the current I is simply V_s/R_1 (where I is the current measured by the ammeter).

As the source voltage increases, the voltage across diode D1B increases, and at some point, it turns on. As that happens, the slope of the $I-V_s$ relation changes. As the source voltage increases further, diode D2B also turns on, changing the slope once again.

Similar changes happen when a negative V_s is applied.

Exercise Set

1. Calculate the input voltage values at which diodes D1B and D2B are expected to turn on. Verify your values by running the simulation and plotting I_{D1B} , I_{D2B} versus V_s .

2. Keeping only the diode(s) which are conducting, calculate the slope of the I - V_s relation in each region. Check against simulation results.
3. If we replace the DC voltage source V_s with a triangular input voltage, the current measured by the ammeter would be approximately sinusoidal. How would you convert this current into a voltage?