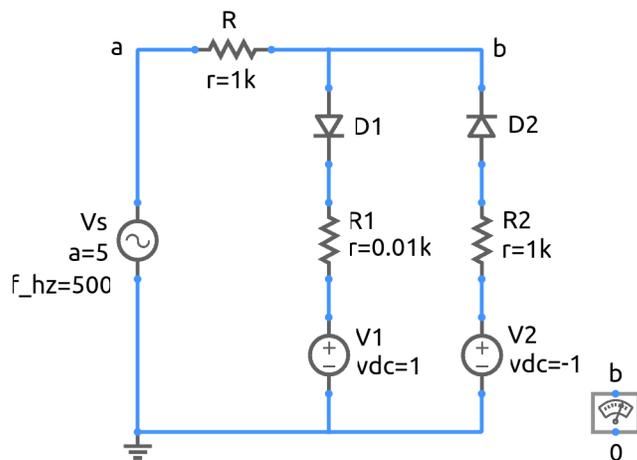


# ee101\_diode\_clipper\_3.sqproj



Assume the turn-on voltage of the diodes to be  $0.7\text{ V}$ .

## Exercise Set

1. Plot  $V_o$  versus  $V_i$ .
2. Plot the diode currents versus  $V_i$ .
3. Plot the voltage across each diode versus  $V_i$ .
4. Compare your results with simulation.