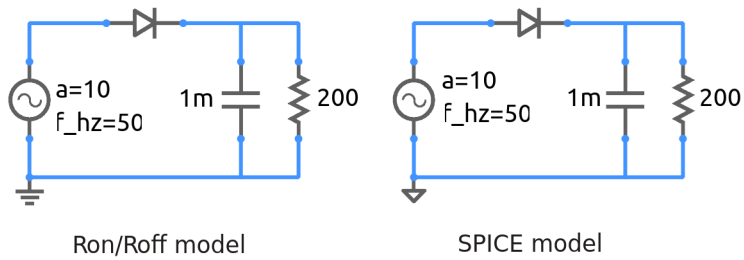


## ee101\_half\_rectifier.sqproj



The purpose of this simulation exercise is to understand the operation of a half-wave rectifier and also to compare the simulation results obtained for two diode models (see figure):

(a) simple  $R_{on}/R_{off}$  model with a given  $V_{on}$  and (b) a more accurate model (used in SPICE) which incorporates the Shockley diode equation.

### Exercise Set

1. For the given circuit parameter values, calculate the ripple voltage  $V_R$ .
2. Estimate the peak diode current.
3. Compare your values with simulation results obtained with the two diode models.
4. Comment on the validity of the simple diode model.