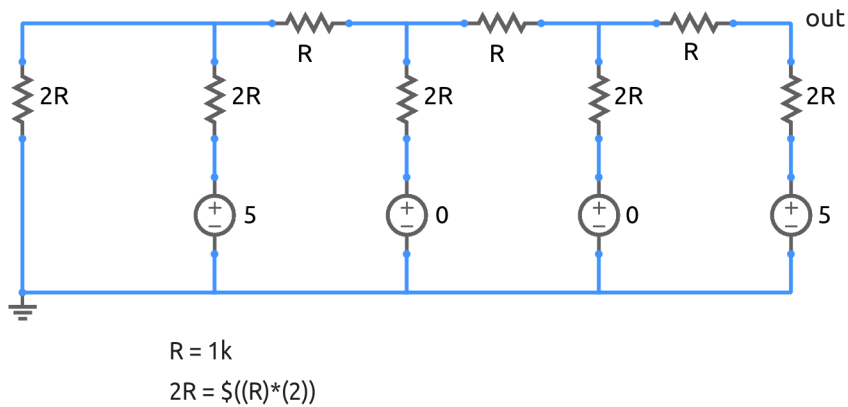


ee101_network_3.sqproj



The circuit shown in the figure is the well-known “ R - $2R$ ladder” used in some of the digital-to-analog converters (DACs). Each source voltage is either 5 V or 0 V.

Exercise Set

1. Find an expression for the output voltage in terms of the four source voltages (call them V_{S0} , V_{S1} , V_{S2} , V_{S3} from left to right) using superposition. (Hint: Thevenin’s theorem is convenient in this exercise.)
2. Verify your results with simulation for a few specific cases such as that shown in the figure.