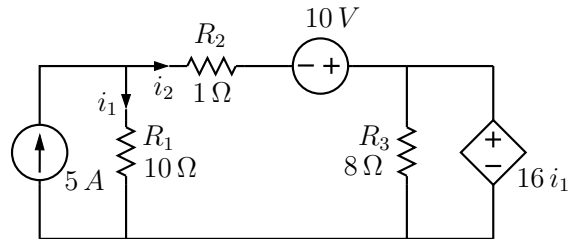


# ee101\_network\_9.sqproj

## Description



In the circuit shown in the figure,

1. Find the currents  $i_1$  and  $i_2$  using mesh analysis. The three meshes,  $I_S$ - $R_1$ ,  $R_1$ - $R_2$ - $V_S$ - $R_3$ ,  $R_3$ - $ccvs1$ , are convenient (with the current in the first mesh already known). Verify your answers with simulation.
2. Find the currents  $i_1$  and  $i_2$  by superposition. Verify your individual responses (i.e., with one source active and the other deactivated) with simulation results. Note that the dependent source should *not* be deactivated in using superposition.