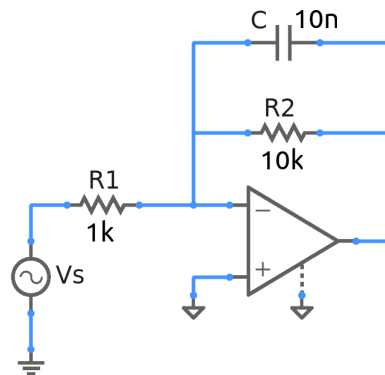


## ee101\_op\_filter\_1.sqproj



### Exercise Set

For the low-pass active filter is shown in the figure,

1. Find the transfer function.
2. From the transfer function, find the low-frequency gain and the cut-off frequency  $f_0$ .
3. Find the low-frequency gain directly using the fact that  $Z_C \rightarrow \infty$  as  $f \rightarrow 0$ .
4. What will happen to the magnitude frequency response of the filter if  $R_2$  is changed to  $20\text{ k}\Omega$ ?
5. What will happen to the magnitude frequency response of the filter if  $C$  is changed to  $100\text{ nF}$ ?
6. Check your answers against simulation.