

Figure 1: (a) Block diagram of a sinusoidal oscillator, (b) A specific example of the  $\beta$  network.

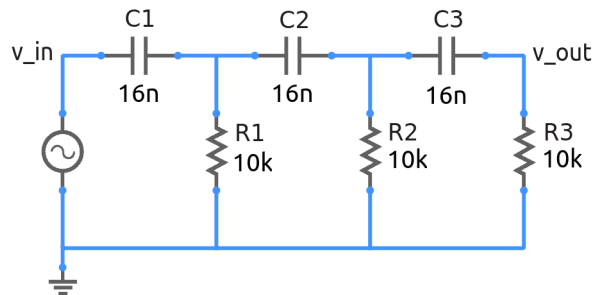


Figure 2: Circuit diagram of  $\beta$  network with component values.

Fig. 1 shows the block diagram of a sinusoidal oscillator based on positive feedback. It consists of an amplifier with gain  $A$  and a feedback network which is characterised by  $\beta = v_{out}/v_{in}$  (see Fig. 2). The condition for oscillation is given by the Barkhausen criterion, viz.,

$$A(j\omega) \beta(j\omega) = 1. \tag{1}$$

(See ee101/ee101\_osc\_2a.sqproj for an oscillator circuit using the above  $\beta$  network.)

### Exercise Set

1. Apply the Barkhausen criterion and find the condition for oscillation, i.e., the frequency of oscillation and the condition to be satisfied by  $A$  for oscillations to occur (assuming  $A$  to be real).

2. Simulate the circuit and plot the magnitude and phase of  $\beta$  as a function of frequency.  
From the plots, find the numerical value of  $A$  that is required for the circuit to oscillate.
3. Compare the values you obtained in (1) with the simulation results.

## References

1. S. Franco, *Design with Operation Amplifiers and Analog Integrated Circuits*, McGraw-Hill, 1998.
2. J. Millman and A. Grabel, *Microelectronics*, McGraw-Hill, 1988.