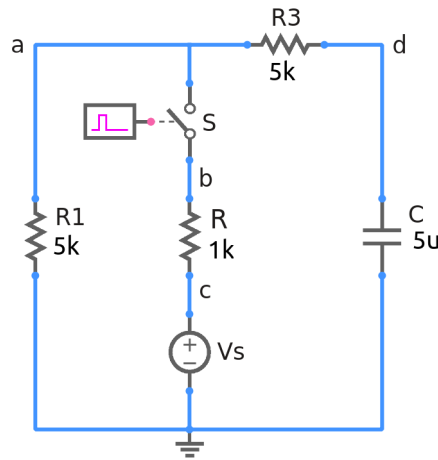


ee101_rc2.sqproj



In the RC circuit shown in the figure, the switch has been closed for a long time and is opened at $t = 0$.

Exercise Set

1. Find the initial value (at $t = 0^-$) of the capacitor voltage (V_d in the figure).
2. What is the time constant of the circuit for $t > 0$? Obtain expressions for the capacitor voltage and current for $t > 0$ sec. Use the condition that $V_C(0^+) = V_C(0^-)$.
3. Obtain the current through R_1 in two ways: (a) Use $V_C(t)$ obtained in (2). (b) Start with the general form $i_{R_1}(t) = A \exp(-t/\tau) + B$, find A and B using conditions on i_{R_1} at $t = 0^+$ and $t \rightarrow \infty$.
4. Plot $V_C(t)$ and $i_{R_1}(t)$ for $-0.1 \text{ sec} < t < 0.5 \text{ sec}$.
5. Compare your plots with simulation results.