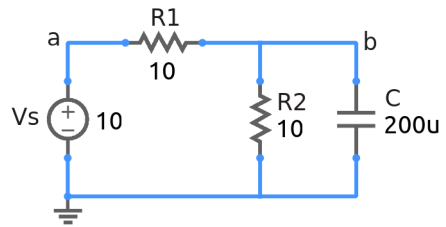


## ee101\_rc3.sqproj



In the  $RC$  circuit shown in the figure, the initial capacitor voltage (at  $t = 0$ ) is 0 V.

### Exercise Set

1. What is the time constant of the circuit?
2. Obtain expressions for the capacitor voltage and current for  $t > 0$  sec.
3. Obtain the current through  $R_2$  in two ways: (a) Use  $V_C(t)$  obtained in (2). (b) Start with the general form  $i_{R_1}(t) = A \exp(-t/\tau) + B$ , find  $A$  and  $B$  using conditions on  $i_{R_2}$  at  $t = 0^+$  and  $t \rightarrow \infty$ .
4. Plot  $V_C(t)$ ,  $i_{V_s}$ ,  $i_C$ , and  $i_{R_2}(t)$  for  $t > 0$  sec.
5. Compare your plots with simulation results.