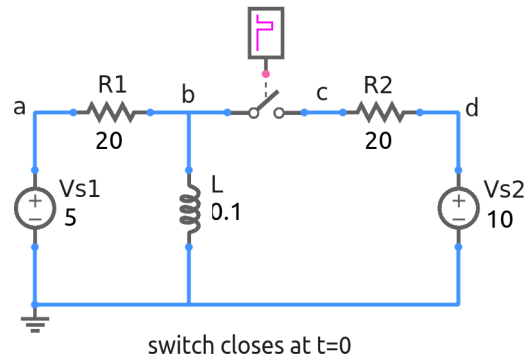


ee101\_r12.sqproj



In the  $RL$  circuit shown in the figure, the switch has been open for a long time and is closed at  $t=0$ .

### Exercise Set

1. Find the circuit time constant for  $t > 0$ .
2. What is the initial current through the inductor  $i_L(0^-)$ ?
3. What is the final current through the inductor  $i_L(\infty)$ ?
4. Obtain an expression for  $i_L(t)$  for  $t > 0$ .
5. Obtain an expression for  $i_{R2}(t)$  for  $t > 0$ .
6. Sketch  $i_L(t)$  and  $i_{R2}(t)$  for  $-20 \text{ ms} < t < 80 \text{ ms}$ .
7. Verify your answers with simulation.