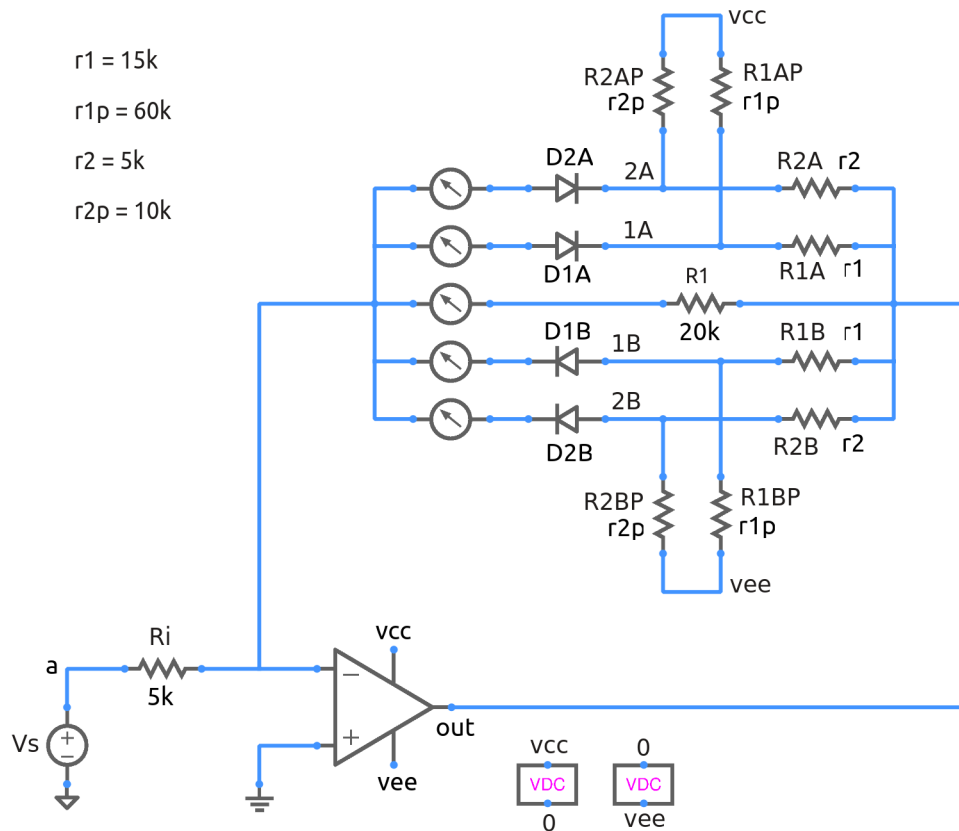


# ee101\_wave\_shaper.sqproj



Shown in the figure is a triangle-to-sine converter circuit. It is essentially an inverting amplifier circuit with the feedback resistor replaced by the diode network. The  $I$ - $V$  relationship of the diode network has been designed such that, for a triangular input voltage (going from  $-5\text{ V}$  to  $5\text{ V}$ ), the output voltage is nearly sinusoidal.

The inverting terminal of the Op Amp is at virtual ground; therefore, the voltage across the diode network is equal to  $V_{\text{out}}$ . If we know how the input current  $i_{\text{in}}$  (the current through  $R_i$ ) varies with  $V_{\text{out}}$ , we can obtain a relationship between  $V_i$  and  $V_{\text{out}}$  using  $i_{\text{in}} = V_i/R_i$ .

To understand the circuit operation, simulate the circuit and plot  $i_{\text{in}}$  versus  $V_{\text{out}}$  along with the individual diode branch currents (measured by the ammeters connected in series with the diodes). Observe how the total current is affected as each diode turns on.

(See ee101\_diode\_circuit\_10.sqproj for the behaviour of the diode network.)

## Exercise Set

1. Consider  $V_{\text{out}} > 0 \text{ V}$ . As  $V_{\text{out}}$  increases, the diode  $D1B$  turns on at some point. Assuming  $V_{\text{on}}$  to be  $0.7 \text{ V}$  for the diodes, calculate the value of  $V_{\text{out}}$  at which  $D1B$  just turns on. Check against the simulation plot mentioned above.
2. As  $V_{\text{out}}$  increases further, the diode  $D2B$  also turns on at some point. Calculate the value of  $V_{\text{out}}$  at which  $D2B$  just turns on. Check against the simulation plot mentioned above.  
  
Similarly, calculate the values of  $V_{\text{out}}$  at which diodes  $D1A$  and  $D2A$  just turn on.
3. Simulate the circuit and plot  $V_i$  and  $V_{\text{out}}$  versus time. Note that the output voltage is approximately sinusoidal.
4. Plot the Fourier spectrum for  $V_i$  and  $V_{\text{out}}$  (individually) and observe that  $V_{\text{out}}$  has a lower harmonic distortion.

## References

1. J. M. Fiore, *Op Amps and Linear Integrated Circuits*, Delmar, 2001.