

miller_1.sqproj

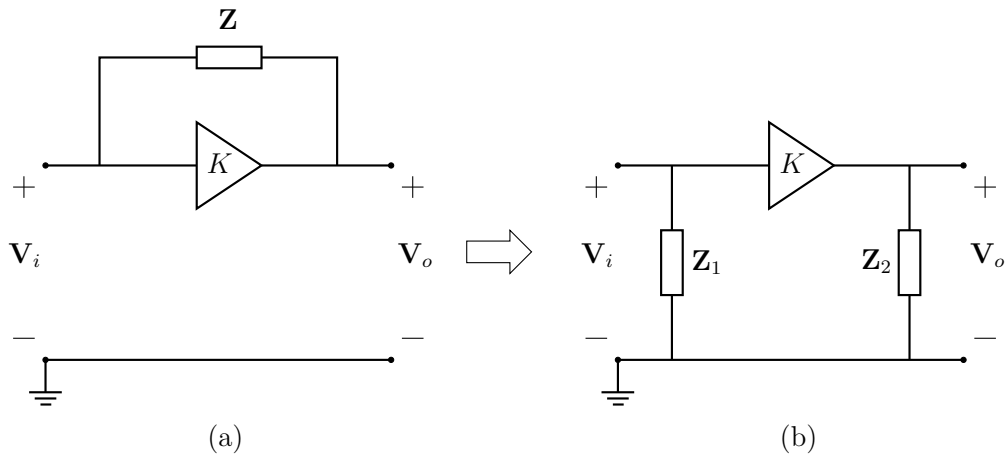


Figure 1: (a) Original circuit, (b) Equivalent circuit after application of Miller's theorem.

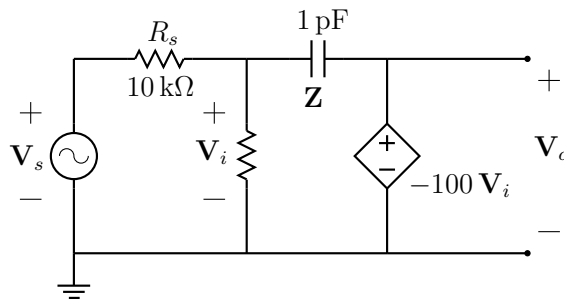


Figure 2: Example for application of Miller's theorem.

Miller's theorem can be used to simplify the small-signal equivalent circuit of an amplifier when an impedance appears between the input and output nodes. Fig. 1 (a) shows an amplifier with gain K , and an impedance Z connected between the input and output nodes. Using Miller's theorem, Z can be replaced with Z_1 and Z_2 as shown in Fig. 1 (b), where

$$\mathbf{Z}_1 = \frac{\mathbf{Z}}{1 - K}, \quad \mathbf{Z}_2 = \frac{\mathbf{Z}}{1 - (1/K)}. \quad (1)$$

In this exercise, we want to analyse the circuit shown in Fig. 2 using Miller's theorem. We will treat R_i to be infinite for simplicity.

Exercise Set

1. Find $\mathbf{Z}_1(s)$ and $\mathbf{Z}_2(s)$ for the circuit shown in Fig. 2.

2. Replace \mathbf{Z} with \mathbf{Z}_1 and \mathbf{Z}_2 , and obtain the transfer function $H(s) = V_o(s)/V_s(s)$.
3. Plot $H(j\omega)$ versus frequency (Bode plot).
4. Verify your results with simulation.

References

1. A. S. Sedra, K. C. Smith, and A. N. Chandorkar, *Microelectronic Circuits: Theory and Applications*, Fifth edition, Oxford University Press, 2009.