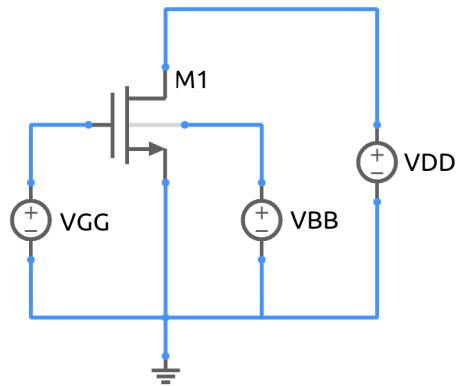


mos\_iv\_1.sqproj



Shown in the figure is a simulation set-up for plotting the  $I$ - $V$  curves of an  $n$ -channel MOS transistor. The source terminal is treated as the reference. For convenience, three solve blocks have been set up which can be used as follows.

1. Solve block 1 can be used to plot  $I_D$ - $V_D$  characteristics of the transistor for different values of  $V_G$ , with  $V_B$  held constant at  $V_B = 0$  V.
2. Solve block 2 can be used to plot  $I_D$ - $V_G$  characteristics of the transistor for different values of  $V_B$ , with  $V_D$  held constant at  $V_D = 0.1$  V.
3. Solve block 3 can be used to plot  $I_D$ - $V_G$  characteristics of the transistor for different values of  $V_B$ , with  $V_D$  held constant at  $V_D = 5$  V.

### Exercise Set

1. Run the simulation. Plot the  $I$ - $V$  characteristics mentioned in the above list.
2. What would be the effect changing the following parameters on the  $I$ - $V$  characteristics?  
(a)  $W$ , (b)  $L$ , (c) threshold voltage, (d) mobility.

Run the simulation by systematically changing (one at a time) the above parameters, and compare the  $I$ - $V$  curves with the original curves.

## References

1. B.G. Streetman and S.K. Banerjee, *Solid State Electronic Devices*, Pearson Education, 2006.
2. N. Dasgupta and A. Dasgupta, *Semiconductor Devices Modelling and Technology*, Prentice-Hall of India, 2004.