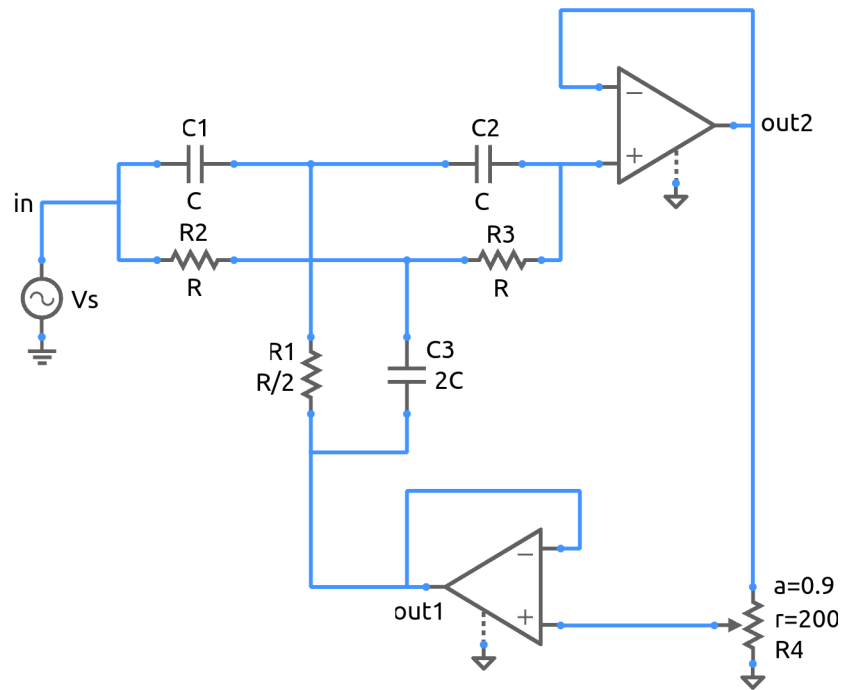


## notch\_filter.sqproj



A “Twin T” notch filter is shown in the figure. The transfer function (with output taken at the node **out2**) is given by

$$H(s) = \frac{V_o(s)}{V_s(s)} = \frac{s^2 + \omega_0^2}{s^2 + (4\omega_0 a)s + \omega_0^2}, \quad (1)$$

where  $\omega_0 = 1/RC$ , and  $a$  denotes the pot resistance fraction. Since the numerator becomes zero at  $\omega = \omega_0$ , we get a “notch” in the filter transfer function at  $\omega_0$ . Note that, for  $\omega \gg \omega_0$  and  $\omega \ll \omega_0$ ,  $|H(s)|$  approaches 1. By changing the pot fraction  $a$ , the quality factor of the filter can be changed.

### Exercise Set

1. Run the simulation. Plot  $V_{\text{out2}}$  versus frequency (log-log plot), and verify the notch filter functionality.
2. If  $R$  is doubled, how would the filter response change? Verify with simulation.
3. Repeat for different values of  $a$  (the pot setting) and observe the effect on the filter response.

## References

1. [http://www.radio-electronics.com/info/circuits/opamp\\_notch\\_filter/opamp\\_notch\\_filter.php](http://www.radio-electronics.com/info/circuits/opamp_notch_filter/opamp_notch_filter.php)