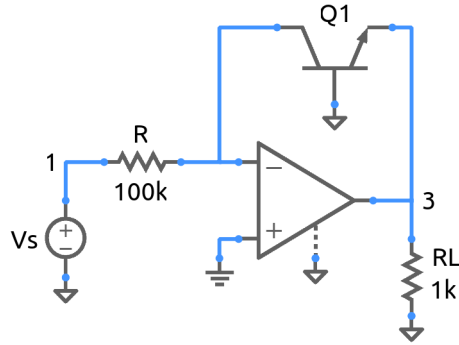


## opamp\_log.sqproj



In a BJT operating in the active mode, the collector current  $I_C$  is an exponential function of the base-emitter voltage  $V_{BE}$ , given by

$$I_C \approx I_{CS} \exp\left(\frac{V_{BE}}{\eta V_T}\right), \quad (1)$$

where  $V_T = k_B T / q$  is the thermal voltage. In the circuit shown in the figure, assuming the Op Amp to be operating in the linear region, the collector of the BJT is at virtual ground, and the BJT operates in the active mode as long as the current through the resistor  $R$  is positive (going from left to right). For this condition, we can write

$$I_C = \frac{V_s}{R} = I_{CS} \exp\left(\frac{V_{BE}}{\eta V_T}\right) = I_{CS} \exp\left(\frac{-V_o}{\eta V_T}\right). \quad (2)$$

The above equation can be rewritten as

$$V_o = -\eta V_T \log\left(\frac{V_s}{R I_{CS}}\right). \quad (3)$$

### Exercise Set

1. Run the simulation. Plot  $V_o$  (linear scale) versus  $V_s$  (log scale). Comment on the plot. Estimate the value of  $I_{CS}$ .
2. How will the plot change if  $R$  is changed from 100 k $\Omega$  to 10 k $\Omega$ ? Verify with simulation.

### References

1. J. Millman and A. Grabel, *Microelectronics*, McGraw-Hill, 1988.